

Electronic Systems

Active Filters

Lecture 8


Dr. Roaa Mubarak

The Active Filters Contents:

1. Introduction to Filters.
2. Low Pass Filter.
3. High Pass Filter.
4. Band Pass Filter.
5. Butterworth Filter.
6. Chebyshev Filter.
7. Bessel Filter.
8. KHN Biquad Filter.
9. State Variable Filters.
- 10. Multiple Feedback Filters.**

Multiple Feedback single op-amp Filter


Multiple Feedback BPF

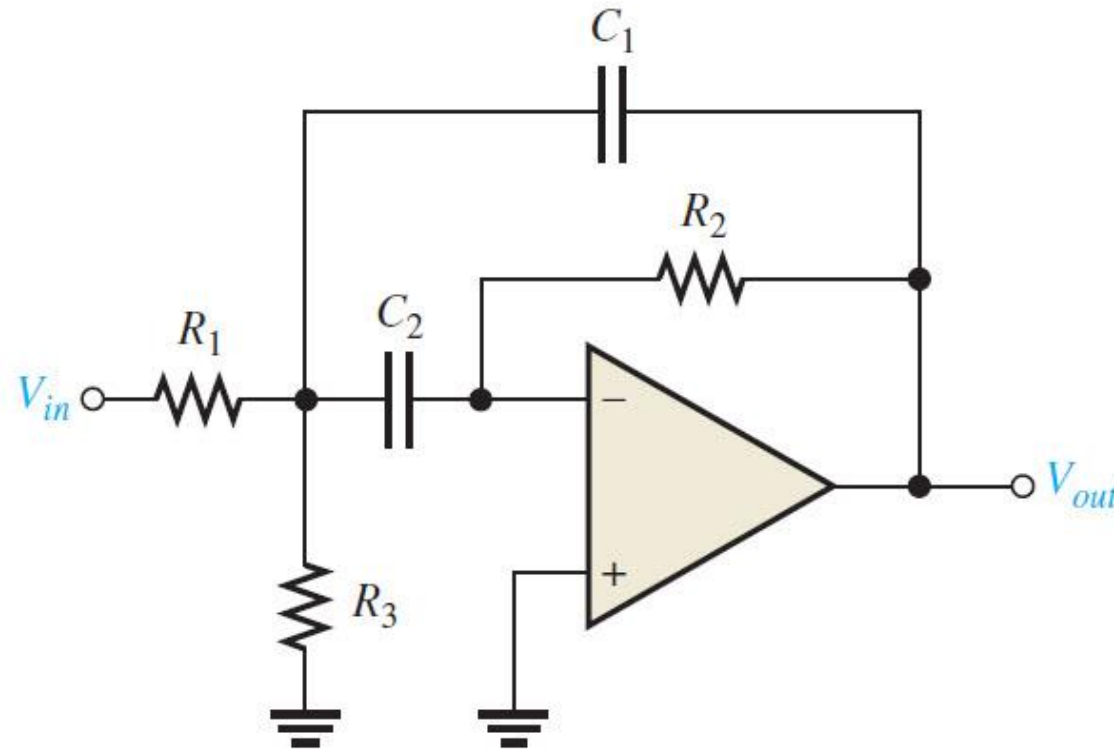

- The multiple feedback band-pass filter circuit has two feedback, the path from output via R_2 back to input and the path from output via C_1 back to the input. That is why it is referred as multiple-feedback. The circuit has both low pass filter and high pass filter. The capacitor C_1 and resistor R_1 forms the LPF while the capacitor C_2 and R_2 forms the HPF.


Multiple Feedback BPF

- LPF: R_1 , C_1
- HPF: C_2 , R_2

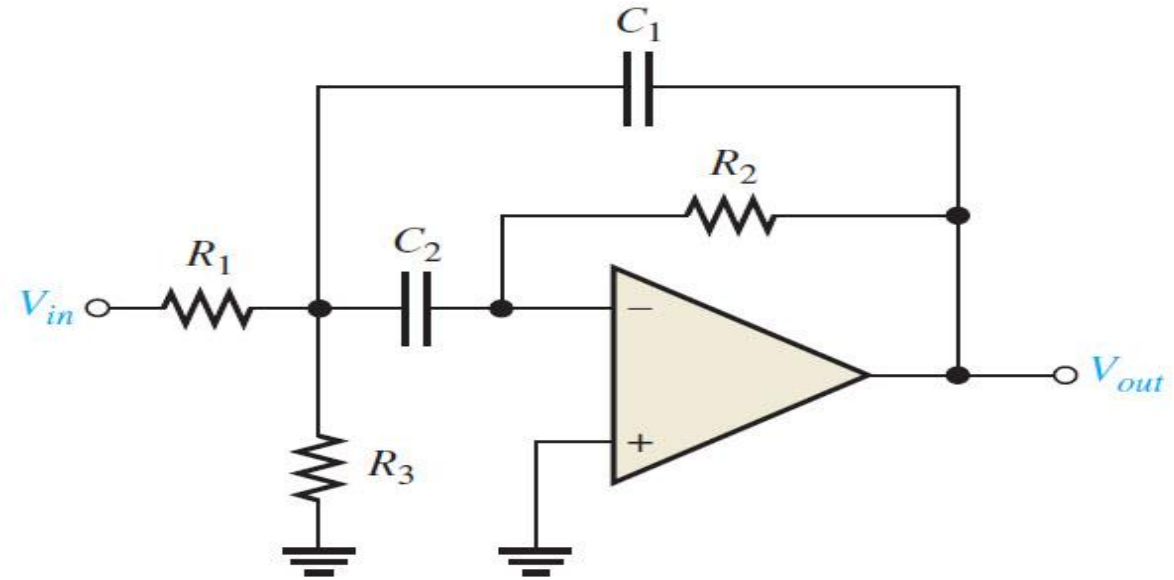

- The 2 feedback paths moving through the resistance R_2 and capacitor C_1 .
- The elements Resistance R_1 and C_1 offer the low pass response and resistance R_2 and capacitor C_2 offer the high pass response.
- The extreme gain value is A_0 , which exists at the center frequency. Q values of lesser than the ten generally exist in this category of the filter.
- The relation for the mid-frequency is created as regarding the resistance R_1 and R_3 indicates in parallel combination are shown from the capacitor C_1 .

Multiple Feedback BPF

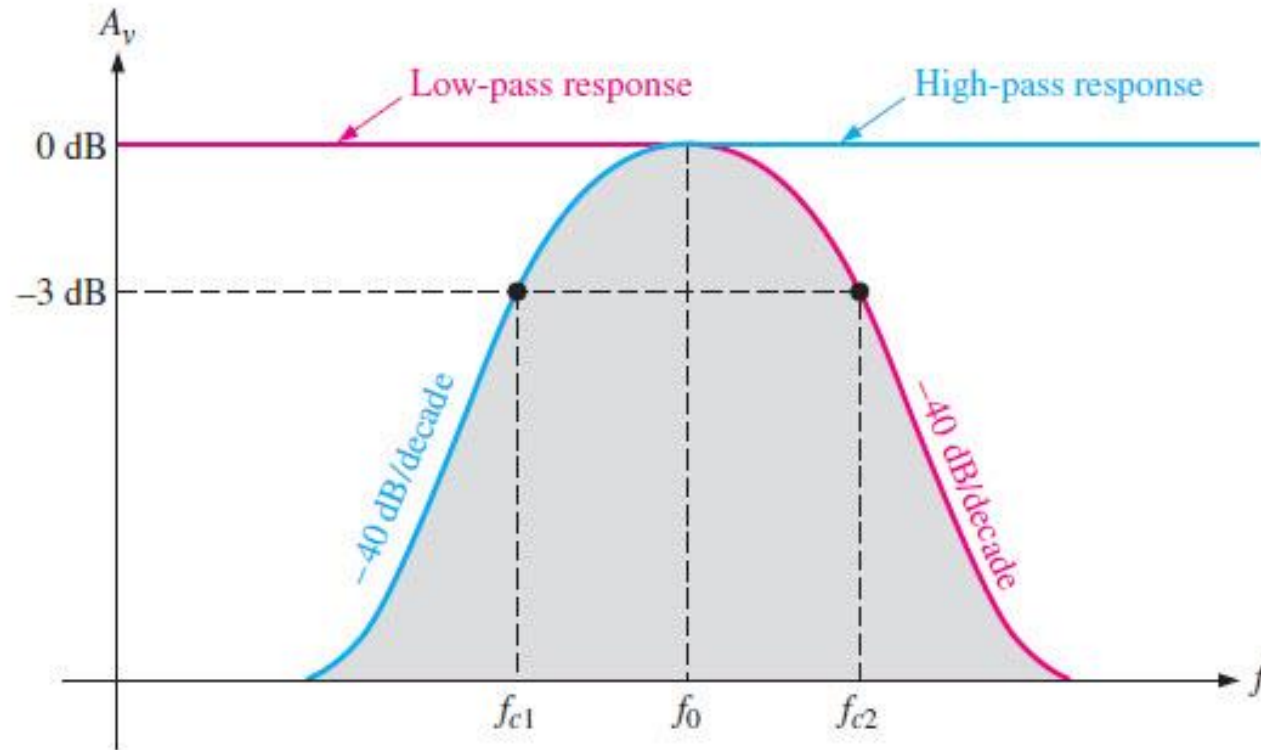


- The center frequency f_0 of the band-pass filter can be expressed as,

$$f_c = \frac{1}{2\pi\sqrt{(R_1||R_3)R_2C_1C_2}}$$

Multiple Feedback BPF

- if $C_1 = C_2 = C$
- $$F_c = \frac{1}{2\pi\sqrt{(R_1 \parallel R_3)R_2}C^2} = \frac{1}{2\pi C\sqrt{(R_1 \parallel R_3)R_2}}$$
$$= \frac{1}{2\pi C\sqrt{\frac{(R_1 R_3)R_2}{(R_1 + R_3)}}}$$
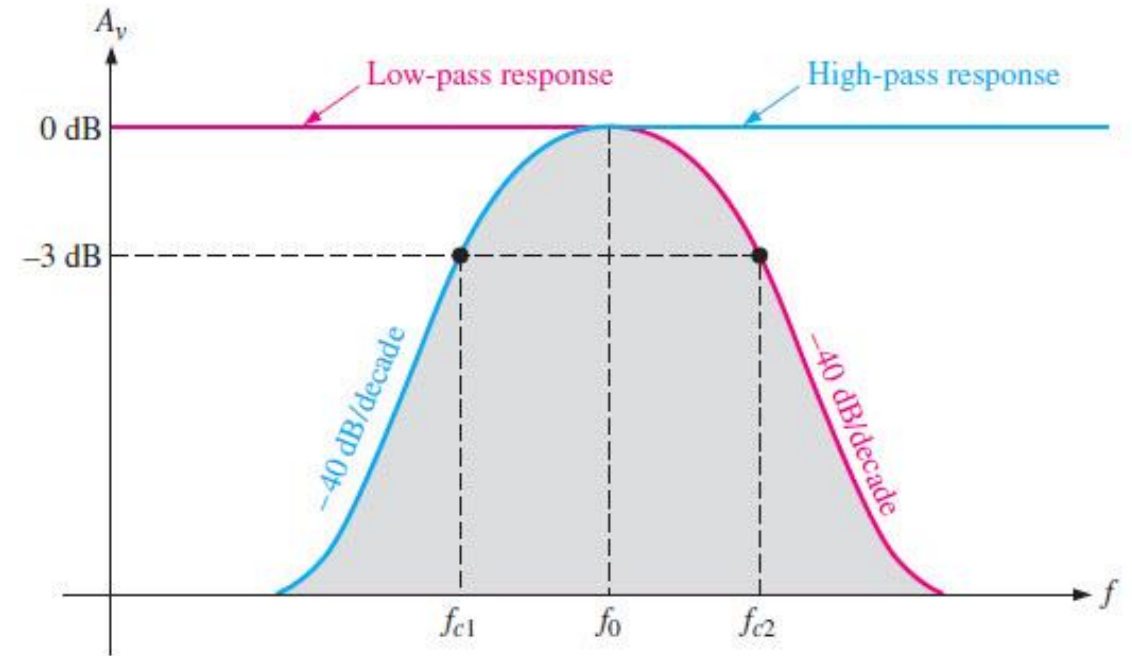
$$f_c = \frac{1}{2\pi C} \sqrt{\frac{R_1 + R_3}{R_1 R_2 R_3}}$$



Multiple Feedback BPF

- The **Quality factor** or **Q-factor** is,

$$Q = \frac{f_0}{BW}$$

$$Q = \frac{f_0}{f_{c2} - f_{c1}}$$

- Without derivation, the value of the three **resistors R1,R2 and R3** are as follows,

$$R_1 = \frac{Q}{2\pi f_0 C A_0}$$

$$R_2 = \frac{Q}{\pi f_0 C}$$

$$R_3 = \frac{Q}{2\pi f_0 C (2Q^2 - A_0)}$$

Multiple Feedback BPF

- For the creation of the gain values, we solve Q in the expression or resistance R1 and R2.

$$Q = 2\pi f_0 A_0 C R_1$$

$$Q = \pi f_0 C R_2$$

so

$$2\pi f_0 A_0 C R_1 = \pi f_0 C R_2$$

$$2A_0 R_1 = R_2$$

$$A_0 = R_2 / 2R_1$$

$$A_0 = \frac{R_2}{2R_1}$$

Multiple Feedback BPF

Proof: $f_c = \frac{1}{2\pi\sqrt{(R_1 || R_3)R_2C_1C_2}}$

$$* I_3 = \frac{V_X - 0}{1/sC_2} = \frac{0 - V_o}{R_2}$$

$$sC_2 V_X = -\frac{V_o}{R_2}$$


$$V_X = -\frac{V_o}{sC_2 R_2}$$

* Node (V_X)

$$I_1 = I_2 + I_3 + I_4$$

$$\frac{V_{in} - V_X}{R_1} = \frac{V_X}{R_3} + \frac{V_X - 0}{1/sC_2} + \frac{V_X - V_o}{1/sC_1}$$
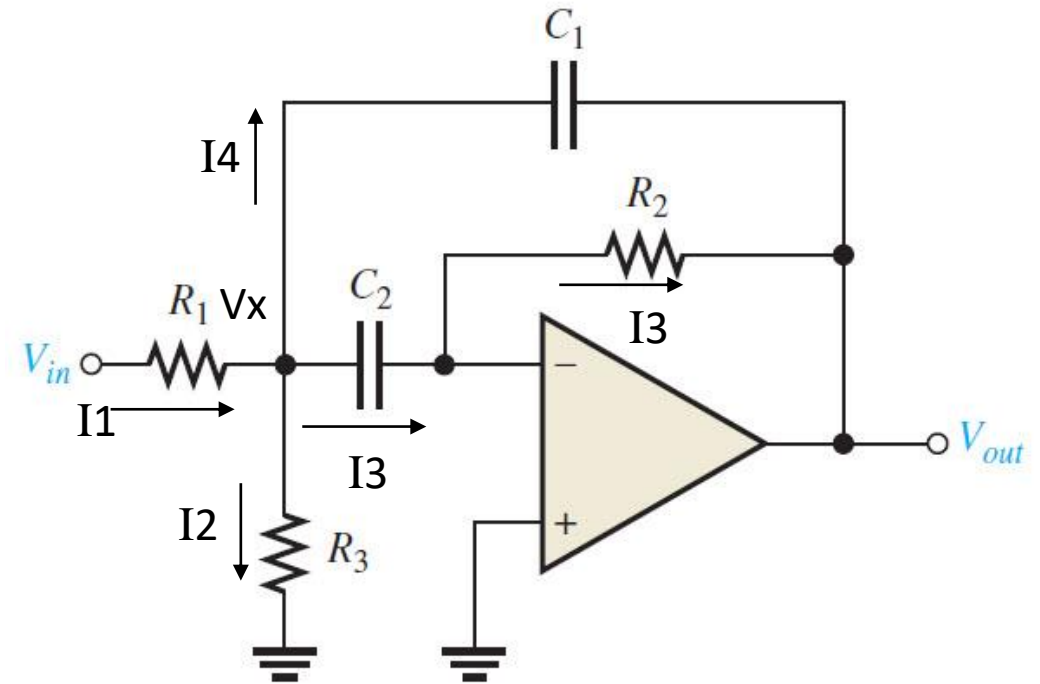
$$\frac{V_{in}}{R_1} - \frac{V_X}{R_1} = \frac{V_X}{R_3} + sC_2 V_X + sC_1 V_X - sC_1 V_o$$



Multiple Feedback BPF

$$\frac{V_{in}}{R_1} = V_x \left[\frac{1}{R_1} + \frac{1}{R_3} + sC_2 + sC_1 \right] - sC_1 V_o$$

$$V_{in} = (V_x) \left[\left(1 + \frac{R_1}{R_3}\right) + sC_2 R_1 + sC_1 R_1 \right] - sC_1 R_1 V_o$$


$$= \frac{-V_o}{sC_2 R_2} \left[\left(1 + \frac{R_1}{R_3}\right) + sC_2 R_1 + sC_1 R_1 \right] - sC_1 R_1 V_o$$

$$- V_o \left[\frac{\left(1 + \frac{R_1}{R_3}\right) + (C_1 R_1 + C_2 R_1) s}{sC_2 R_2} + sC_1 R_1 \right]$$

$$= -V_o \left[\frac{\left(1 + \frac{R_1}{R_3}\right) + (C_1 R_1 + C_2 R_1) s + s^2 C_1 C_2 R_1 R_2}{sC_2 R_2} \right]$$

$$A_v = H(s) = \frac{V_o}{V_{in}} = \frac{-sC_2 R_2}{s^2 C_1 C_2 R_1 R_2 + (C_1 R_1 + C_2 R_1) s + \left(\frac{R_1 + R_3}{R_3}\right)}$$
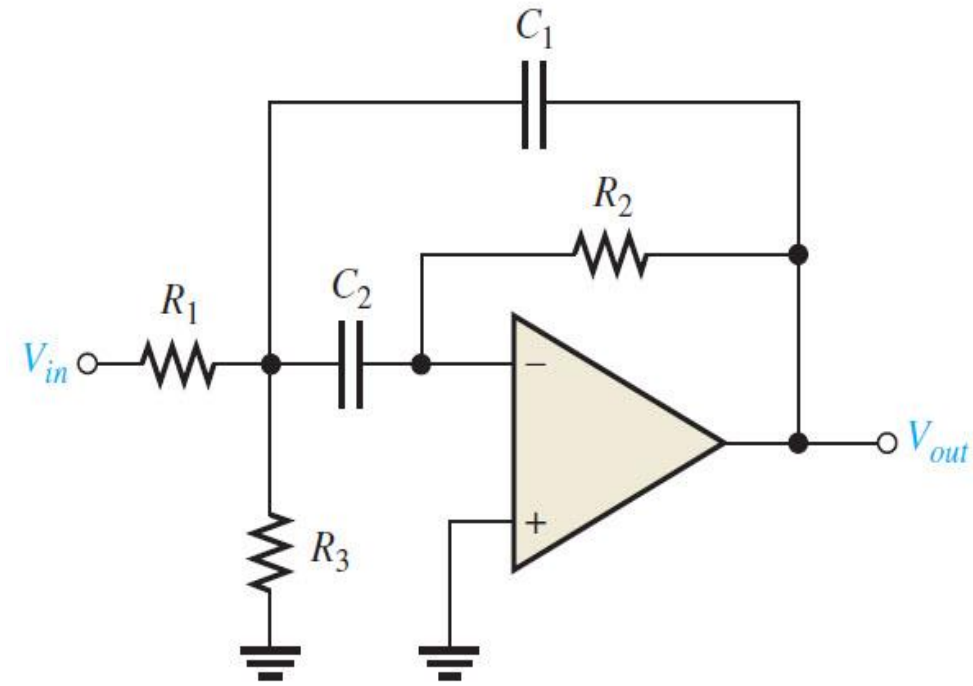
$$A_v = \frac{-sC_2 R_2}{\frac{R_1 + R_3}{R_3} \left[s^2 \frac{R_3}{R_1 + R_3} \cdot C_1 C_2 R_1 R_2 + \frac{C_1 R_1 + C_2 R_1}{R_1 + R_3} \cdot R_3 s + 1 \right]}$$



Multiple Feedback BPF

$$A_v = \frac{-sC_2 \frac{R_2 R_3}{R_1 + R_3}}{s^2 (R_1 \parallel R_3) C_1 C_2 R_2 + \frac{R_1 C_1 + R_1 C_2}{R_1 + R_3} R_3 s + 1}$$

$$A_v = \frac{-a_1 s}{\left(\frac{s}{\omega_o}\right)^2 + 2K\left(\frac{s}{\omega_o}\right) + 1}$$

$$\frac{1}{\omega_o^2} = (R_1 \parallel R_3) C_1 C_2 R_2$$

$$\omega_o = \frac{1}{\sqrt{(R_1 \parallel R_3) R_2 C_1 C_2}}$$

$$\therefore f_o = \frac{1}{2\pi \sqrt{(R_1 \parallel R_3) R_2 C_1 C_2}}$$

Multiple Feedback BPF

Example 1:

Design a multiple-feedback band pass active filter using parameters value as following. For design simplification, assume equal value capacitors are $0.01\mu\text{F}$. Illustrate the circuit designed and label all the circuit components.

$$F_o = 25 \text{ KHZ}, BW = 500, A_o = 3.98$$

Multiple Feedback BPF

Solution

i) Find Q value,

$$C_1 = C_2 = C = 0.01\mu F$$


$$Q = \frac{f_o}{BW} = \frac{25k}{500} = 50$$

ii) Find R_1 , R_2 and R_3

$$R_1 = \frac{Q}{2\pi f_o C A_o} = 8k\Omega$$

$$R_2 = \frac{Q}{\pi f_o C} = 63.66k\Omega$$
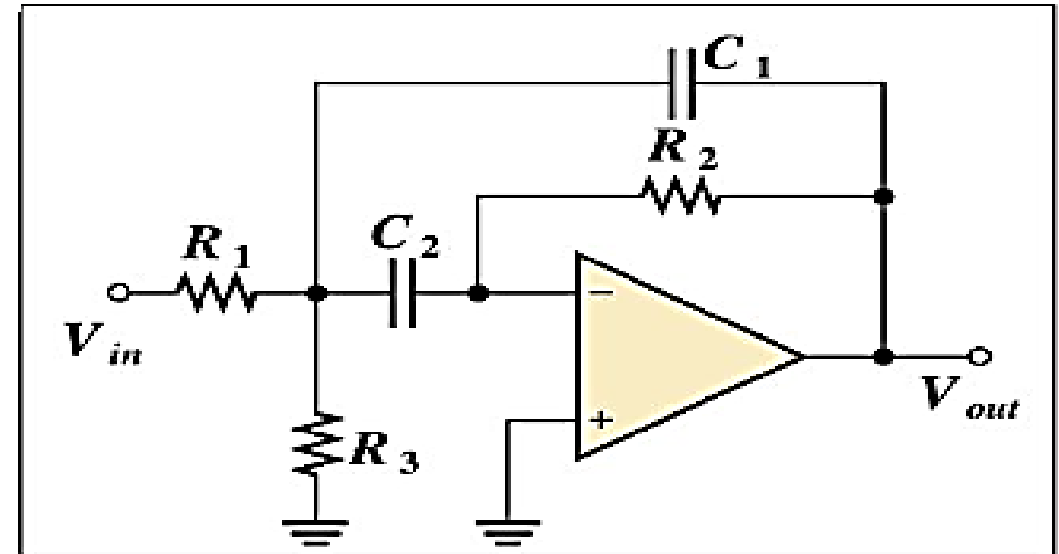
$$R_3 = \frac{Q}{2\pi f_o C (2Q^2 - A_o)} = 6.37\Omega$$



Thus,

i) $R_1 = 8k\Omega$

iv) $C_1 = 0.01\mu F$

ii) $R_2 = 63.66k\Omega$

v) $C_2 = 0.01\mu F$

iii) $R_3 = 6.37\Omega$

Multiple Feedback BPF

Example 2:

- Prove $F_o = \frac{1}{2\pi\sqrt{(R_1 R_3) R_2 C_1 C_2}}$


- Calculate:

- ☐ Center Frequency gain (A_o)

- ☐ Quality Factor (Q)

- ☐ Band-width (B.W)

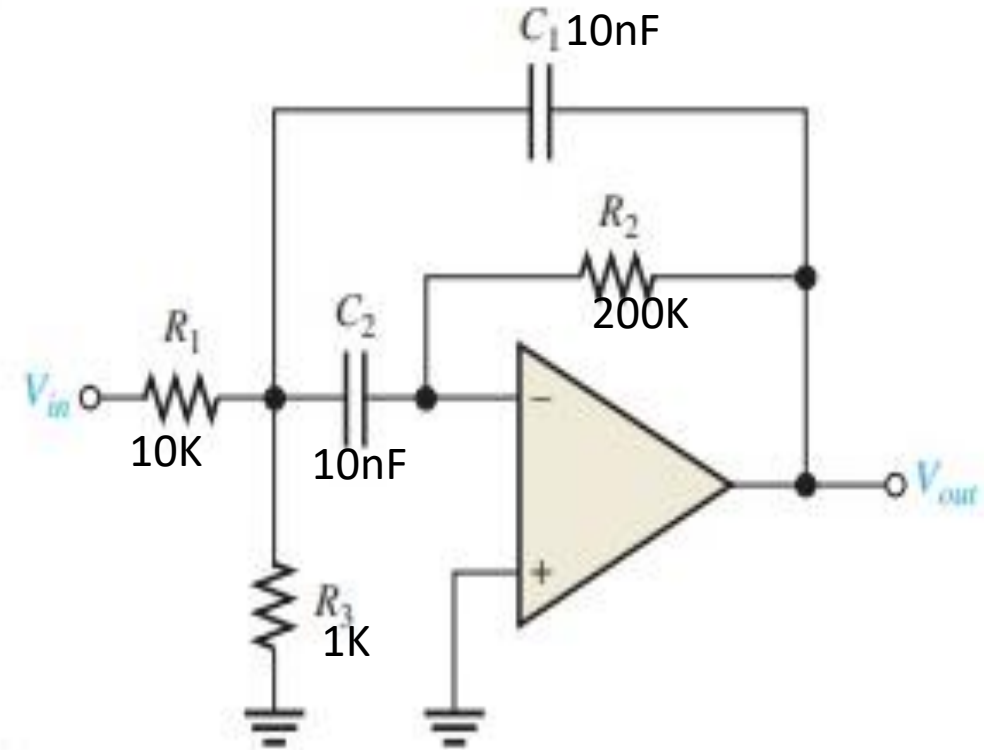- ☐ Lower and higher cut-off Frequencies (F_1 'F_L' & F_2 'F_H'))



Solution

① Prove ✓

$$② * A_0 = \frac{R_2}{2R_1} = \frac{200}{2 \times 10}$$

$$A_0 = 10$$

$$f_0 = \frac{1}{2\pi C \sqrt{(R_1 R_3) R_2}}$$

$$f_0 = \frac{1}{2\pi (10 \times 10^{-9}) \sqrt{\left(\frac{10}{11} \times 10^3\right) (200 \times 10^3)}}$$

$$f_0 = 1180.3 \text{ Hz}$$

$$* Q = \pi f_0 R_2 C = \pi (1180.3) (200 \times 10^3) (10 \times 10^{-9})$$

$$Q = 7.42$$

$$* B.W = \frac{f_0}{Q} = \frac{1180.3 \text{ Hz}}{7.42}$$

$$B.W = 159.1 \text{ Hz}$$


$$* f_1 = f_L = f_0 - \frac{B.W}{2} \approx 1260 \text{ Hz}$$

$$* f_2 = f_H = f_0 + \frac{B.W}{2} \approx 1419 \text{ Hz}$$

Multiple Feedback BSF

$$f_o = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

- LPF: R_1 , C_1
- HPF: C_2 , R_2

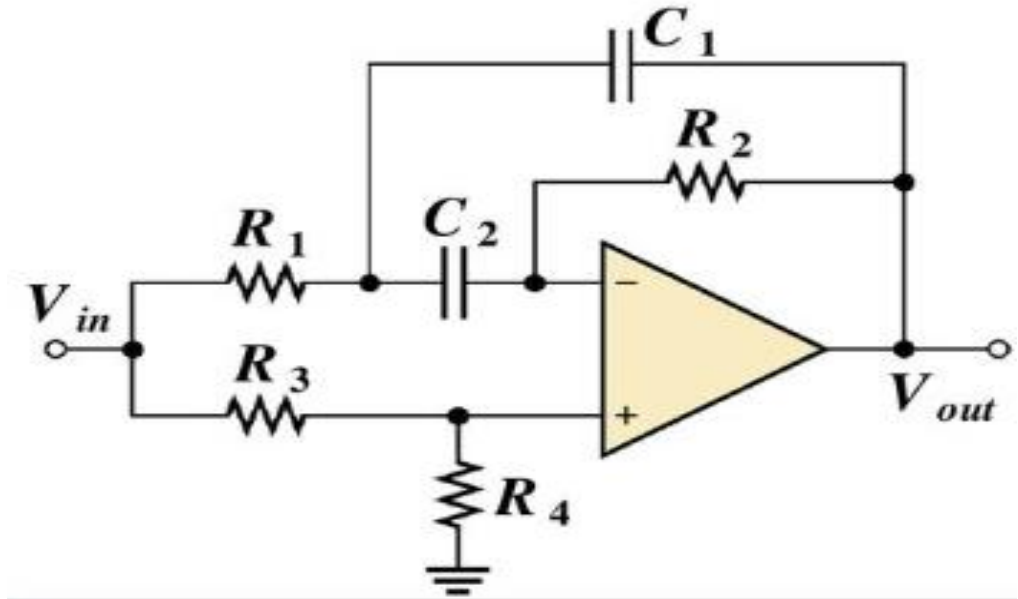

- ☐ The configuration is **similar** to the band-pass version BUT **R_3** has been **moved** and **R_4** has been **added**.
- ☐ The BSF is opposite of BPF in that it blocks a specific band of frequencies

$$\frac{\omega_o}{Q} = \frac{R_1 C_1 + R_1 C_2}{R_1 R_2 C_1 C_2}$$

$$Q = \frac{\sqrt{\frac{R_2}{R_1}}}{\sqrt{\frac{C_2}{C_1}} + \sqrt{\frac{C_1}{C_2}}}$$

Multiple Feedback BSF

$$\times V_1 = I_2 \cdot R_4 = \frac{V_{in}}{R_3 + R_4} R_4$$

$$V_1 = \frac{R_4}{R_3 + R_4} \cdot V_{in} = k V_{in} \quad [1]$$

$$\times I_3 = \frac{V_2 - V_1}{1/sC_2} = \frac{V_1 - V_o}{R_2}$$

$$sC_2 V_2 - sC_2 V_1 = \frac{V_1 - V_o}{R_2} \times R_2$$


$$sC_2 R_2 V_2 - sC_2 R_2 V_1 = V_1 - V_o$$

$$V_o = [1 + sC_2 R_2] V_1 - sC_2 R_2 V_2$$

$$V_o = [1 + sC_2 R_2] k V_{in} - sC_2 R_2 V_2$$

$$sC_2 R_2 V_2 = [1 + sC_2 R_2] k V_{in} - V_o$$
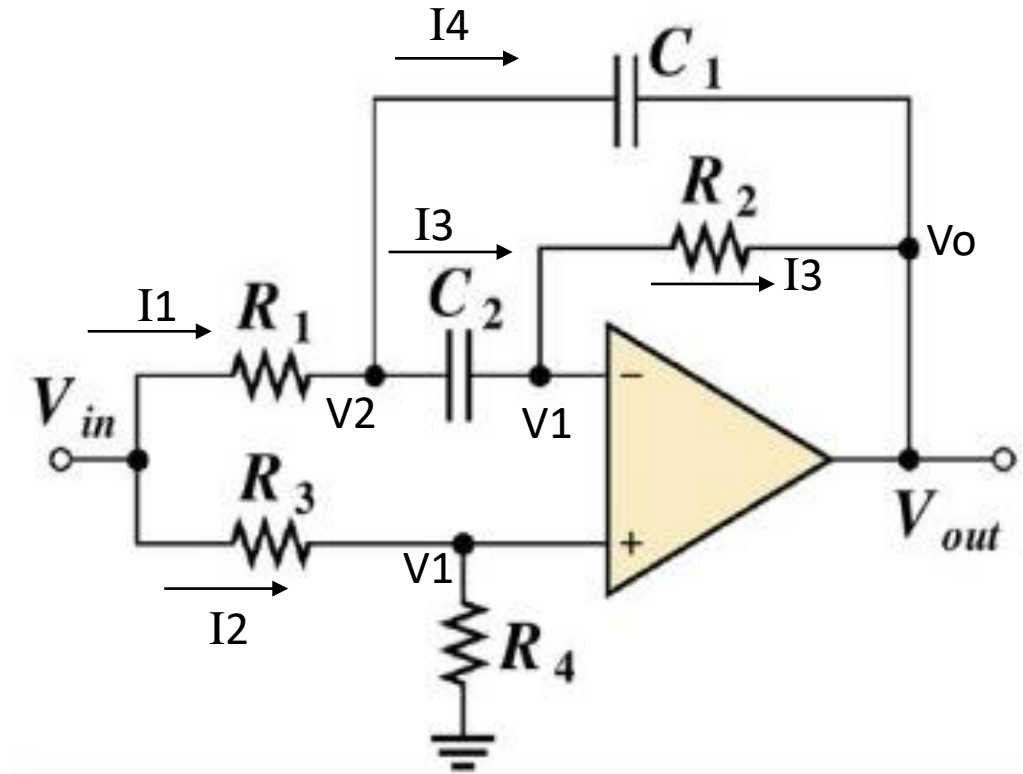
$$\therefore V_2 = \frac{k[1 + sC_2 R_2]}{sC_2 R_2} V_{in} - \frac{1}{sC_2 R_2} V_o \quad [2]$$



Multiple Feedback BSF

$$I_1 = I_3 + I_4$$

$$\frac{V_{in} - V_2}{R_1} = \frac{V_2 - V_1}{1/sC_2} + \frac{V_2 - V_o}{1/sC_1}$$

$$\frac{V_{in} - V_2}{R_1} = sC_2 V_2 - sC_2 V_1 + sC_1 V_2 - sC_1 V_o$$


$$V_{in} - V_2 = sC_2 R_1 V_2 - sC_2 R_1 V_1 + sC_1 R_1 V_2 - sC_1 R_1 V_o$$

$$V_{in} = [1 + sC_2 R_1 + sC_1 R_1] V_2 - sC_2 R_1 V_1 - sC_1 R_1 V_o$$

$$V_{in} = [1 + sC_1 R_1 + sC_2 R_1] \left\{ \frac{k(1 + sC_2 R_2)}{sC_2 R_2} V_{in} - \frac{1}{sC_2 R_2} V_o \right\} - sC_2 R_1 V_1 - sC_1 R_1 V_o$$

$$V_{in} = \frac{(1 + sC_1 R_1 + sC_2 R_1)(1 + sC_2 R_2)}{sC_2 R_2} V_{in} k - \frac{1 + sC_1 R_1 + sC_2 R_1}{sC_2 R_2} V_o - sC_2 R_1 V_1 - sC_1 R_1 V_o$$
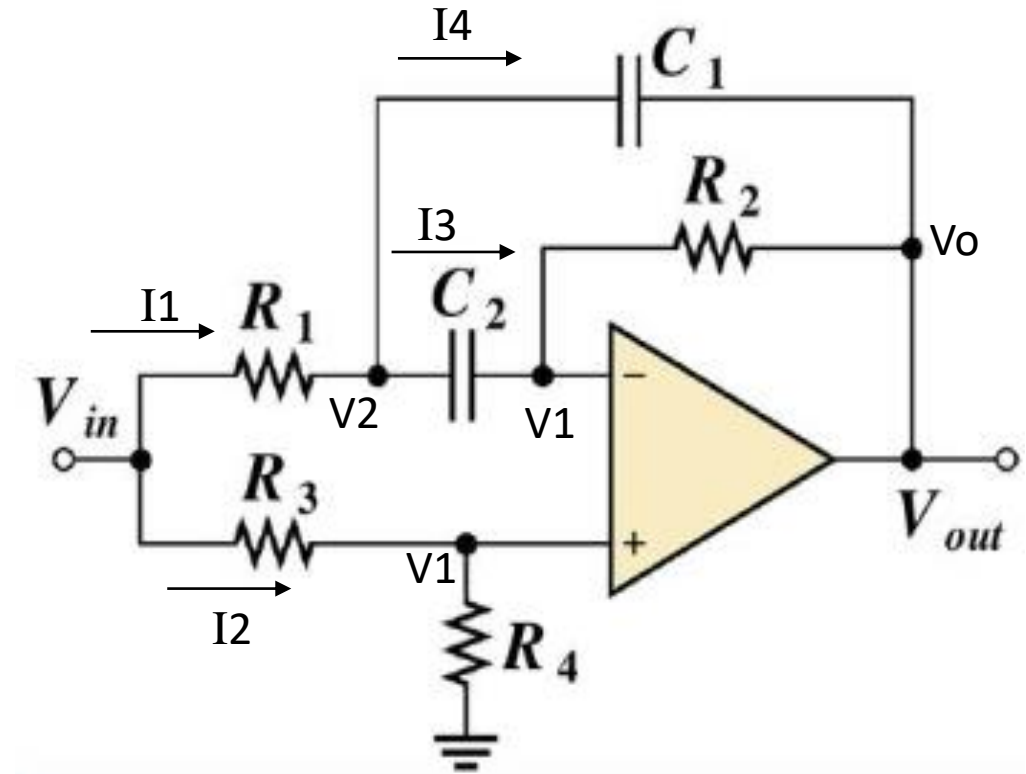
$$sC_2 R_2 V_{in} = (1 + sC_1 R_1 + sC_2 R_1)(1 + sC_2 R_2) k V_{in} - (1 + sC_1 R_1 + sC_2 R_1) V_o - s^2 C_1 C_2 R_1 R_2 k V_{in} - s^2 C_1 C_2 R_1 R_2 V_o$$



Multiple Feedback BSF

$$V_o \{ 1 + s C_1 R_1 + s C_2 R_1 + s^2 R_1 R_2 C_1 C_2 \}$$

$$= \{ K(1 + s C_1 R_1 + s C_2 R_1)(1 + s C_2 R_1) - s C_2 R_2 - s^2 C_2^2 R_1 R_2 K \} V_{in}$$


$$\therefore \frac{V_o}{V_{in}} = \frac{K(1 + s C_1 R_1 + s C_2 R_1)(1 + s C_2 R_1) - s C_2 R_2 - s^2 C_2^2 R_1 R_2 K}{s^2 R_1 R_2 C_1 C_2 + (R_1 C_1 + R_1 C_2) s + 1}$$

$$\frac{V_o}{V_{in}} = \frac{K(1 + s C_1 R_1 + s C_2 R_1)(1 + s C_2 R_1) - s C_2 R_2 - s^2 C_2^2 R_1 R_2 K}{R_1 R_2 C_1 C_2 \left[s^2 + \left(\frac{R_1 C_1 + R_1 C_2}{R_1 R_2 C_1 C_2} \right) s + \frac{1}{R_1 R_2 C_1 C_2} \right]}$$

$$\frac{V_o}{V_{in}} = \frac{K f(s)}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

$$\therefore \omega_0^2 = \frac{1}{R_1 R_2 C_1 C_2} \rightarrow \omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$
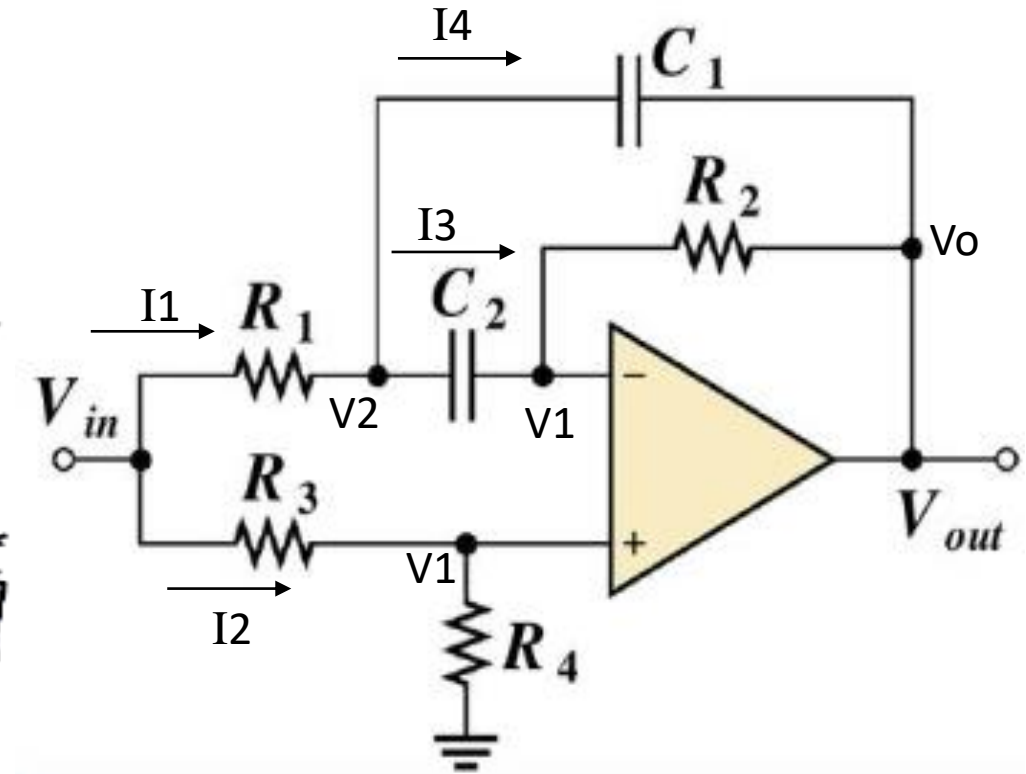
$$\therefore f_0 = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$



Multiple Feedback BSF

$$f_o = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

$$\frac{\omega_o}{Q} = \frac{R_1 C_1 + R_1 C_2}{R_1 R_2 C_1 C_2}$$

$$Q = \frac{\sqrt{\frac{R_2}{R_1}}}{\sqrt{\frac{C_2}{C_1}} + \sqrt{\frac{C_1}{C_2}}}$$

$$BW = \frac{f_o}{Q}$$

$$f_l = f_o - \frac{BW}{2}$$

$$f_h = f_o + \frac{BW}{2}$$