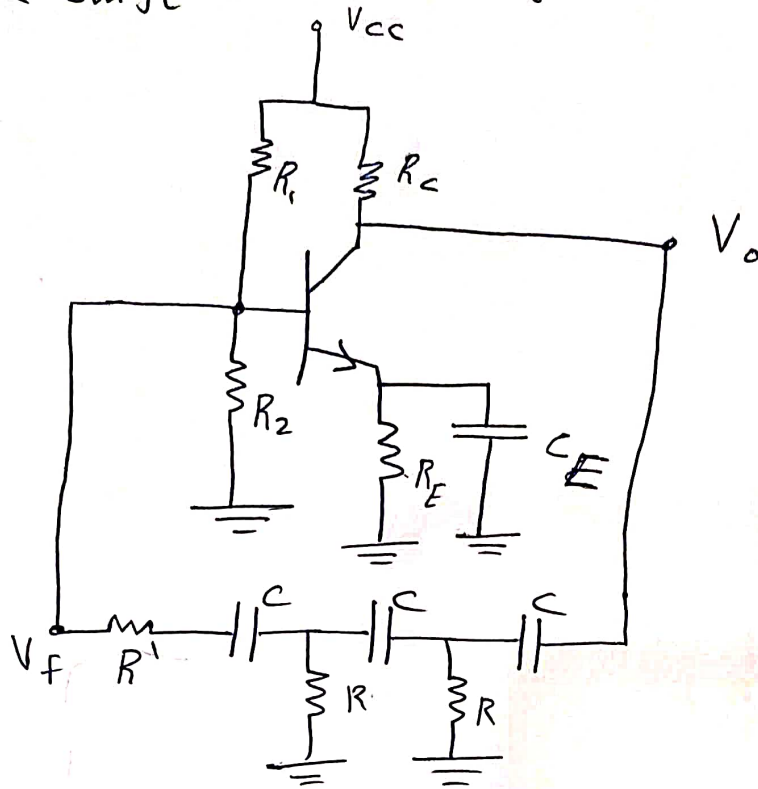


BJT phase shift oscillator :




$$R' + (R_{\pi} \parallel R_1 \parallel R_2)$$

should be equal to R

* Breaking the f/b loop & taking I_b as i/p & having I_3 as o/p current \Rightarrow

* using mesh analysis:

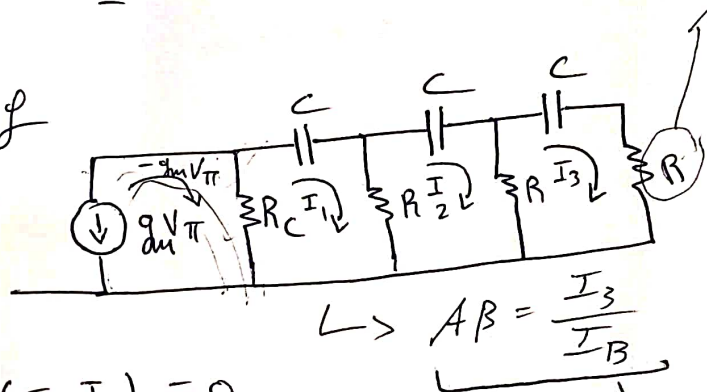

$$A\beta = \frac{I_3}{I_1}$$

①

we will depend on current gain here (more simple in this case)

②

③

$$\Rightarrow R_c (I_1 + g_m V_{\pi}) + \frac{I_1}{sC} + R(I_1 - I_2) = 0$$

$$\Rightarrow I_1 [R_c + R + \frac{1}{sC}] + I_2 [-R] = -g_m V_{\pi} R_c$$

$$\Rightarrow (I_2 - I_1)R + \frac{I_2}{sC} + R(I_2 - I_3) = 0$$

$$\Rightarrow I_1 [-R] + I_2 [2R + \frac{1}{sC}] + I_3 [-R] = 0$$

$$\Rightarrow R[I_3 - I_2] + \frac{I_3}{sC} + I_3 R = 0$$

$$\Rightarrow I_2 [-R] + I_3 [2R + \frac{1}{sC}] = 0$$

$$\Rightarrow \Delta = \begin{vmatrix} R_c + R + \frac{1}{sC} & -R & 0 \\ -R & 2R + \frac{1}{sC} & -R \\ 0 & -R & 2R + \frac{1}{sC} \end{vmatrix} = (R_c + R + \frac{1}{sC}) \left[(2R + \frac{1}{sC})^2 - R^2 \right] + R [-R (2R + \frac{1}{sC})]$$

$$\Rightarrow \Delta = R_c \left(3R^2 + \frac{4R}{sC} + (\frac{1}{sC})^2 \right) + R \left(3R^2 + \frac{4R}{sC} + (\frac{1}{sC})^2 \right) + \frac{1}{sC^2} \left[3R^2 + \frac{4R}{sC} + (\frac{1}{sC})^2 \right] - R^2 (2R + \frac{1}{sC})$$

$$\Delta = R_c \left(3R^2 + \frac{4R}{sC} + (\frac{1}{sC})^2 \right) + R^3 \frac{6R^2}{sC} + \frac{5R}{(sC)^2} + \frac{1}{(sC)^3}$$

$$\Rightarrow \Delta = R_c \left[3R^2 + \frac{4R}{j\omega C} + \left(-\frac{1}{\omega^2 C^2} \right) \right] + R^3 + \frac{6R^2}{j\omega C} - \frac{5R}{\omega^2 C^2} - \frac{1}{j\omega^3 C^3}$$

$$\Rightarrow \Delta = \left(3R^2 R_c - \frac{R_c}{\omega^2 C^2} + R^3 - \frac{5R}{\omega^2 C^2} \right) + j \left(-\frac{4RR_c}{\omega C} - \frac{6R^2}{\omega C} + \frac{1}{\omega^3 C^3} \right)$$

$$\Rightarrow \Delta_3 = \begin{vmatrix} R_c + R + \frac{1}{sC} & -R & \textcircled{+} \\ -R & 2R + \frac{1}{sC} & \textcircled{-} \\ 0 & -R & \textcircled{+} \end{vmatrix}$$

$$= -g_m V_{\pi} R_c [R^2] = -g_m V_{\pi} R_c R^2$$

$$\Rightarrow A\beta = \frac{I_3}{I_b}$$

$$\Rightarrow A\beta = 1$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{-g_m V_{\pi} R_c R^2}{\left(3R^2 R_c - \frac{R_c}{\omega^2 C^2} + R^3 - \frac{5R}{\omega^2 C^2} \right) + j \left(-\frac{4RR_c}{\omega C} - \frac{6R^2}{\omega C} + \frac{1}{\omega^3 C^3} \right)}$$

$$\Rightarrow I_b = \frac{V_{\pi}}{r_{\pi}}$$

$$\Rightarrow A\beta = \frac{I_3}{I_b} = \frac{\overbrace{-g_m V_{\pi}}^{\beta} R_c R^2}{\left(3R^2 R_c - \frac{R_c}{\omega^2 C^2} + R^3 - \frac{5R}{\omega^2 C^2} \right) + j \left(-\frac{4RR_c}{\omega C} - \frac{6R^2}{\omega C} + \frac{1}{\omega^3 C^3} \right)}$$

$$\Rightarrow -\frac{4RR_c}{\omega C} - \frac{6R^2}{\omega C} + \frac{1}{\omega^3 C^3} = 0$$

$$\Rightarrow -\omega^2 C^2 [4RR_c + 6R^2] + 1 = 0$$

$$\Rightarrow \omega_0^2 C^2 = \frac{1}{4RR_c + 6R^2} \Rightarrow \omega_0 = \frac{1}{RC \sqrt{6 + 4\frac{R_c}{R}}}$$

$$\Rightarrow A\beta = 1$$

at ω_0 :

$$\Rightarrow \frac{-\beta R_c R^2}{3\beta^2 R_c - \frac{R_c}{\omega_0^2 C^2} + R^3 - \frac{5R}{\omega_0^2 C^2}} = 1$$

$$\Rightarrow \frac{-\beta}{3 - \frac{1}{\omega_0^2 C^2 R^2} + \frac{R}{R_c} - \frac{5R}{\omega_0^2 R^2 C^2 R_c}} = 1$$

$$\Rightarrow \beta = -3 + \frac{1}{\omega_0^2 R^2 C^2} - \frac{R}{R_c} + \frac{5R}{\omega_0^2 R^2 C^2 R_c}$$

$$\omega_0 = [RC\sqrt{6+4R_c/R}]^{-1}$$

$$\Rightarrow \beta = -3 + \frac{\cancel{R^2 C^2} (6+4\frac{R_c}{R})}{\cancel{R^2 C^2}} - \frac{R}{R_c} + \frac{5R(\cancel{R^2 C^2})(6+4\frac{R_c}{R})}{\cancel{R^2 C^2} R_c}$$

$$= -3 + 6 + 4\frac{R_c}{R} - \frac{R}{R_c} + \frac{5R(6+4R_c/R)}{R_c}$$

$$= 3 + 4\frac{R_c}{R} - \frac{R}{R_c} + \frac{30R}{R_c} + 20$$

$$\boxed{\beta = 23 + 4\frac{R_c}{R} + \frac{29R}{R_c}}$$

\hookrightarrow min value for β