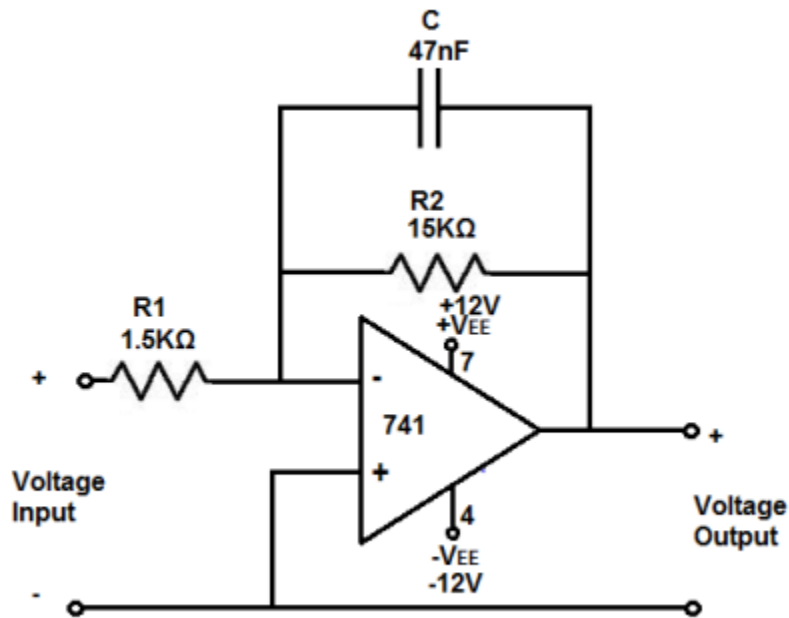


## Active op amp LPF and HPF

### 1. Active Inverting Op Amp Low Pass Filter Circuit



### Procedure:

Construct the circuit shown, then Fill the following table with  $V_{in} = 20 \text{ mV}_{P-P}$   
Calculate the output voltage ( $V_0$ ) and gain ( $A_0$ ) with frequency starting from 10 Hz  
till 1 M Hz.

[illegible]

Frequency (KH z)	1	2	5	10	20	50	80	100	200	500
$V_{in}$ (mV)	20 mV <sub>pp</sub>									
$V_{out}$ (mV)										
Gain= $A_v$										

Frequency (MH z)	1	1.5	2	2.5	3	3.5	4	4.5	5	10
$V_{in}$ (mV)	20 mV <sub>pp</sub>									
$V_{out}$ (mV)										
Gain= $A_v$										


Plot a graph showing the relation between the gain ( $A_v$ ) and frequency (Hz).

From graph determine:

Maximum gain  $A_o$  = .....

Lower Cut-off frequency  $f_L$  = .....
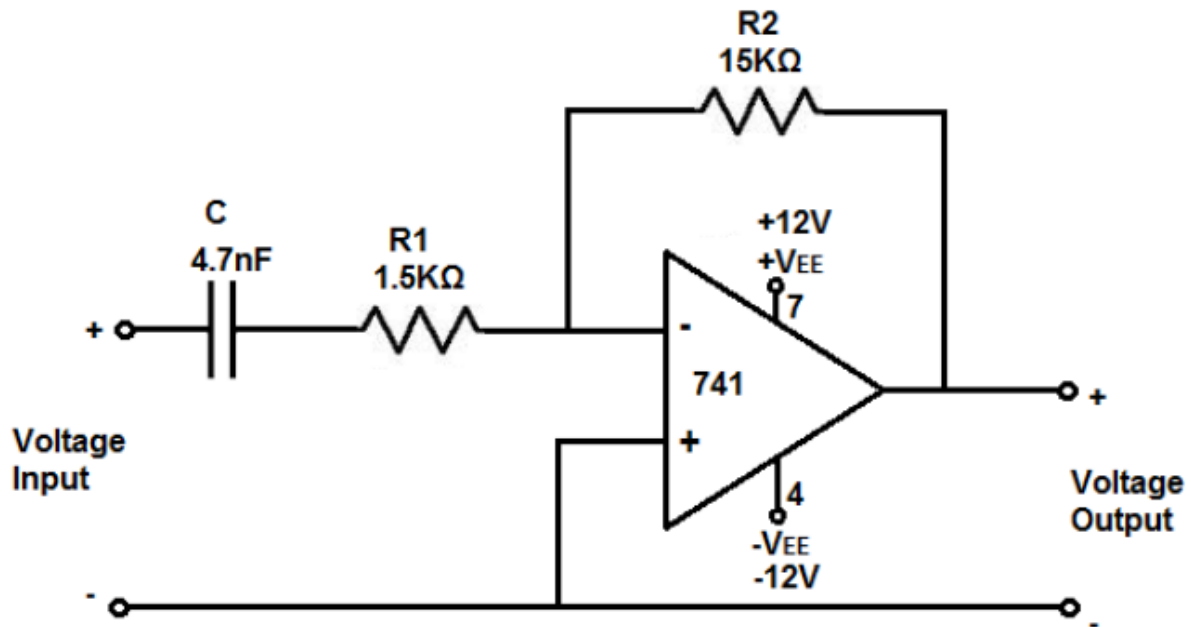
## 2. Active Inverting Op Amp High Pass Filter Circuit



Construct the circuit shown, then Fill the following table with  $V_{in} = 20 \text{ mV}_{P-P}$   
Calculate the output voltage ( $V_0$ ) and gain ( $A_0$ ) with frequency starting from 10 Hz  
till 1 M Hz.

[illegible][illegible]

Frequency (MH z)	1	1.5	2	2.5	3	3.5	4	4.5	5	10
$V_{in}$ (mV)	20 mV <sub>pp</sub>									
$V_{out}$ (mV)										
Gain= $A_v$										

Plot a graph showing the relation between the gain ( $A_v$ ) and frequency (Hz).

From graph determine:

Maximum gain  $A_o = \dots\dots\dots$

Lower Cut-off frequency  $f_H = \dots\dots\dots$