



Electronics and Communications Department

Analog Electronics

Lab 4 Notes

Direct Coupling

Name	عبدالرحمن علي موسى
Section	4
Date	2/5/2023

- **Part I**


❖ **The figure of the circuit below shows that.**

○ **At $V_{B1} = 1.5V$**

$$V_{RC1} = 12.8V \quad , \quad V_{RC2} = 3.42V$$

$$V_{RE1} = 0.85V \quad , \quad V_{RE2} = 1.56V$$
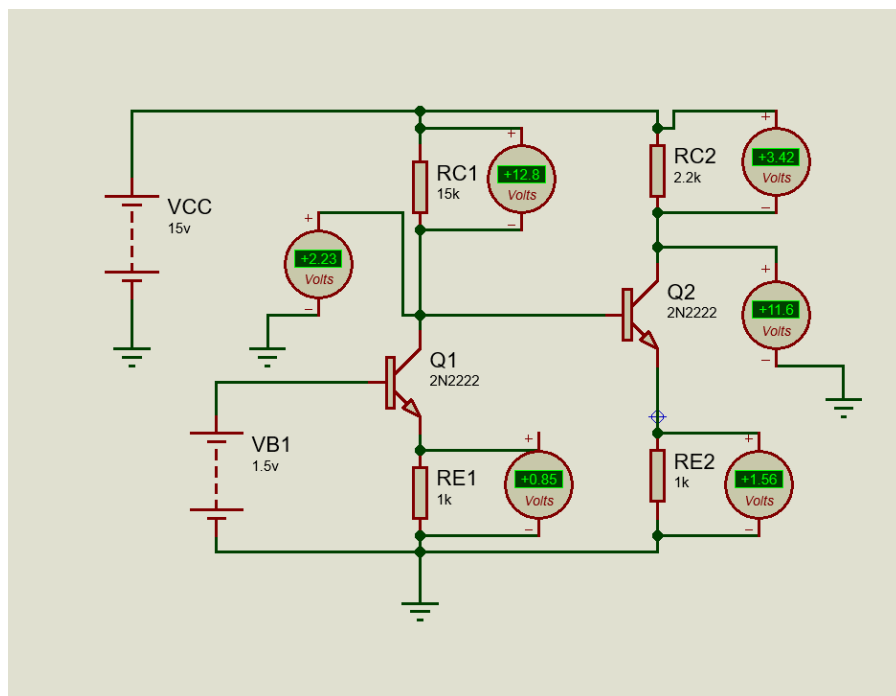
$$V_{C1} = 2.23V \quad , \quad V_{C2} = 11.6V$$




➤ Calculate the overall voltage gain, $A_v = \frac{\Delta V_{C2}}{\Delta V_{B1}}$

○ At $V_{B1} = 1.4V \longrightarrow V_{C2} = 8.7V$

○ At $V_{B1} = 1.6V \longrightarrow V_{C2} = 14.1V$

$$\therefore A_v = \frac{14.1 - 8.7}{1.6 - 1.4} = 27 \text{ V/V}$$

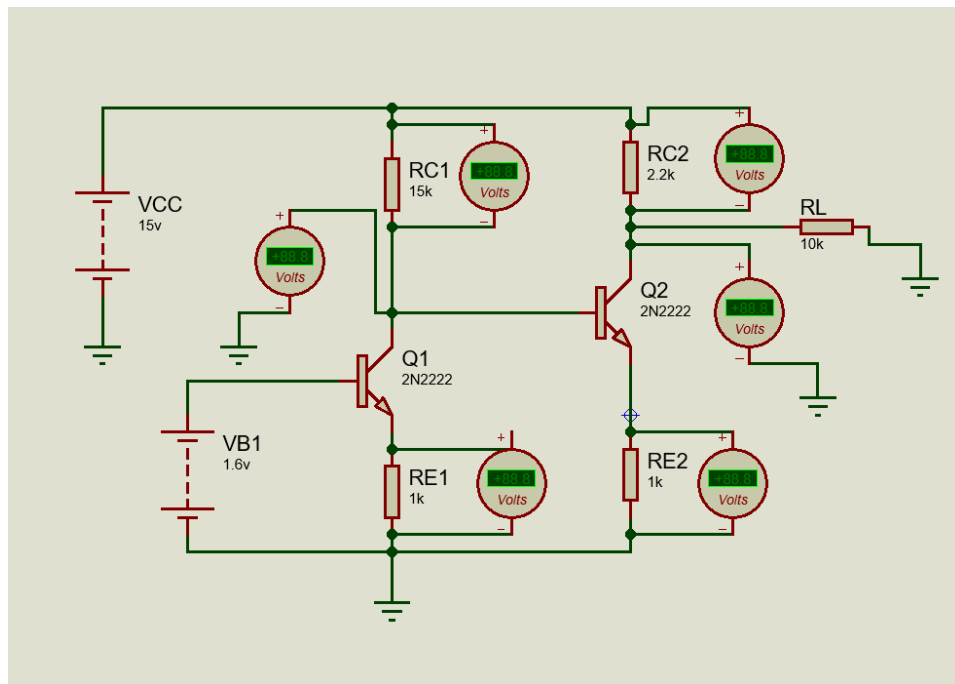❖ The figure below shows the circuit after connecting 10KΩ load.



➤ Calculate the overall voltage gain, $G_v = \frac{\Delta V_{C2}}{\Delta V_{B1}}$


○ At $V_{B1} = 1.4V \longrightarrow V_{C2} = 7.14V$

○ At $V_{B1} = 1.6V \longrightarrow V_{C2} = 11.5V$

$$\therefore G_v = \frac{11.5 - 7.14}{1.6 - 1.4} = 21.8 \text{ V/V}$$

- part II

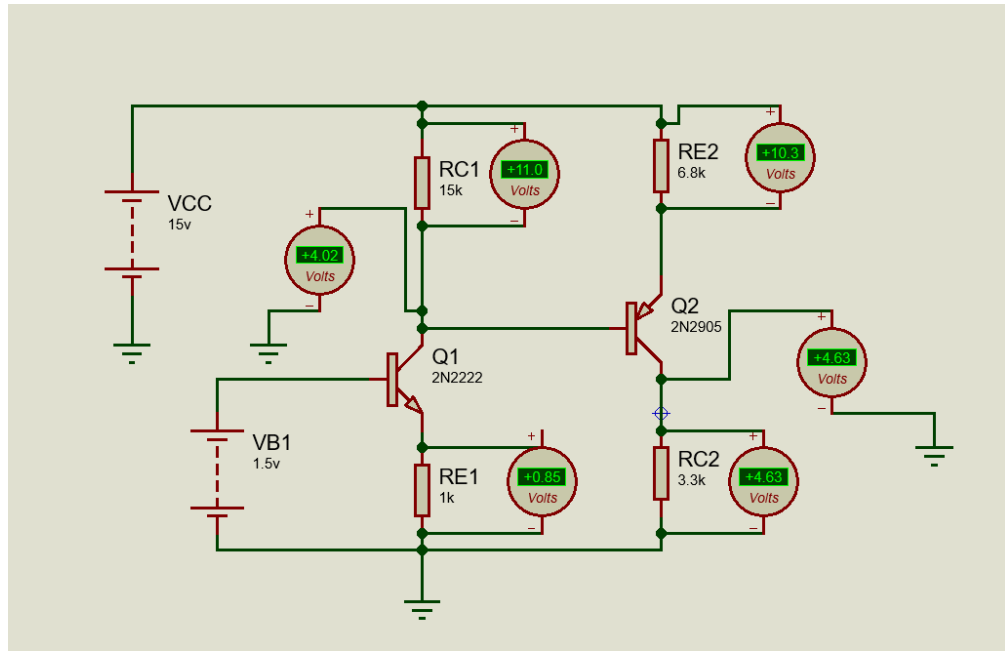- ❖ The figure below shows the circuit after changing the NPN transistor (Q₂) to PNP transistor and the DC voltages at each node.



- Calculate the overall voltage gain, $A_v = \frac{\Delta V_{C2}}{\Delta V_{B1}}$

- At $V_{B1} = 1.4V \longrightarrow V_{C2} = 4.79V$

- At $V_{B1} = 1.6V \longrightarrow V_{C2} = 4.45V$

$$\therefore A_v = \frac{4.45 - 4.49}{1.6 - 1.4} = -0.2 \text{ V/V}$$