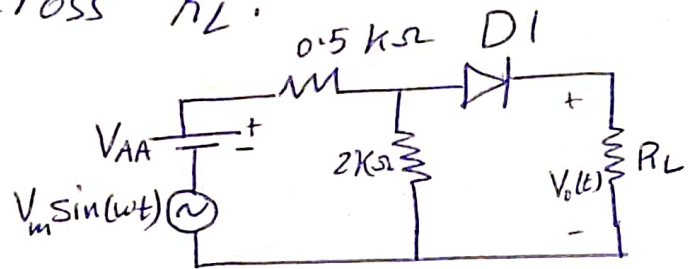


Sheet #3

1. For the ct. shown $V_{AA} = 8V$, $V_m = 0.5V$ & $R_L = 1K\Omega$.
 In the Large signal model of the diode $V_f = 0.7V$,
 $R_f = 20\Omega$ & $\eta = 2$, Determine:
 a) The alternating component of voltage across R_L
 b) The Total voltage across R_L .

Sol:



* DC analysis using Large signal Model:

→ Assuming D1 is ON.

Loop 1:

$$\Rightarrow 8 = 0.5 I_1 + 2(I_1 - I_2) \quad V_{AA} = 8V$$

Loop 2:

$$\Rightarrow 0 = 2(I_2 - I_1) + 0.7 + (0.02 + 1)I_2$$

$$\Rightarrow 0 = 3.02 I_2 - 2 I_1 + 0.7$$

$$\Rightarrow I_1 = \frac{1}{2} (3.02 I_2 + 0.7) \dots (1)$$

sub. by (1) in (2):

$$\Rightarrow 8 = \left[\frac{1}{2} (3.02 I_2 + 0.7) (2.5) - 2 I_2 \right]$$

$$\Rightarrow I_2 = 4.014 \text{ mA} \quad (\text{In the same direction of diode})$$

$$= I_{D1}$$

→ Assumption is true (D1 ON)


$$\Rightarrow V_o = I_2 R_L = 4.014 \text{ Volt}$$

* AC Analysis using small signal Model:

$$\therefore r_d = \frac{\eta V_T}{I_D}$$

(small signal resistance of the diode)

$$= \frac{(2)(0.025)}{(4.014)} = 0.0129 \text{ K}\Omega \approx 13 \Omega$$

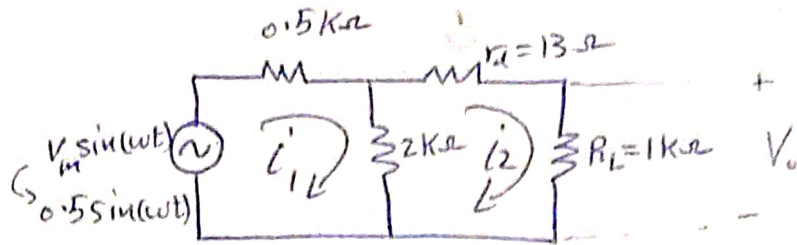

Loop 1 :

$$\Rightarrow 0.5 \sin(\omega t) = i_1(0.5) + 2(i_1 - i_2)$$

$$\Rightarrow 0.5 \sin(\omega t) = 2.5 i_1 - 2 i_2 \quad \dots (3)$$

Loop 2 :

$$\Rightarrow 0 = i_2(0.013) + i_2(1) + 2(i_2 - i_1)$$

$$\Rightarrow 0 = 3.013 i_2 - 2 i_1$$

$$\Rightarrow i_1 = \frac{3.013 i_2}{2} \quad \dots (4)$$

- sub by (4) in (3) :

$$\Rightarrow 0.5 \sin(\omega t) = 2.5 \left(\frac{3.013}{2} \right) i_2 - 2 i_2$$



$$\Rightarrow i_2 = 0.283 \sin(\omega t) \text{ mA}$$

a) $\Rightarrow V_o(t) = i_2 R_L = 0.283 \sin(\omega t) \text{ mA}$

b) $\Rightarrow V_{o \text{ Total}}(t) = V_o + V_o(t) = 4.014 + 0.283 \sin(\omega t) \text{ Volt}$

2) * Assuming ideal diodes.

- The sine wave fluctuates from $-6V$ to $+6V$.

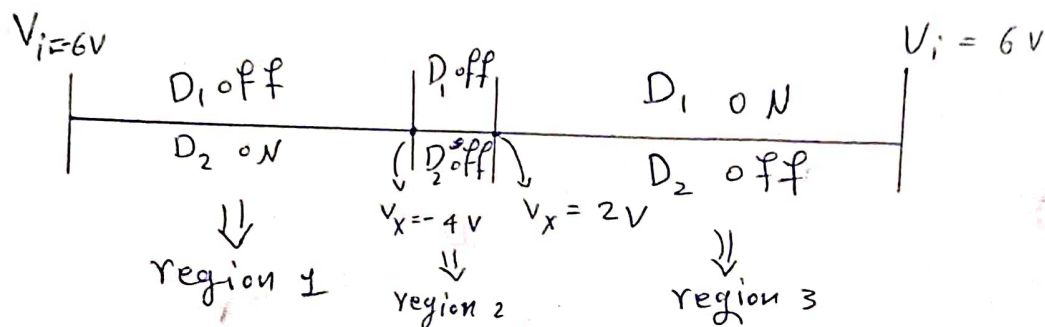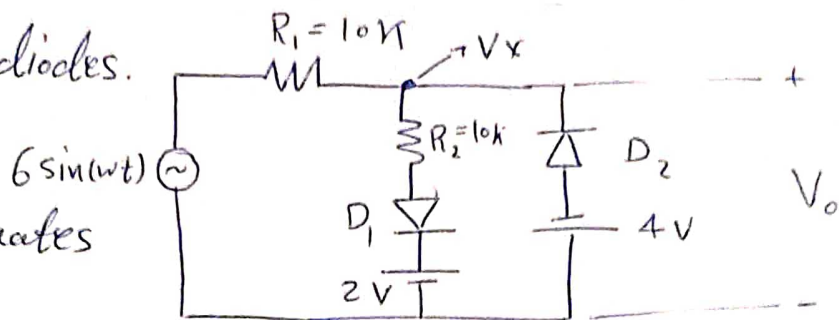


* Region 1 : (D_1 off, D_2 on)

$$-6 \leq V_i \leq -4$$

$$V_x = -4V$$


$$\Rightarrow V_o = V_x = -4V$$

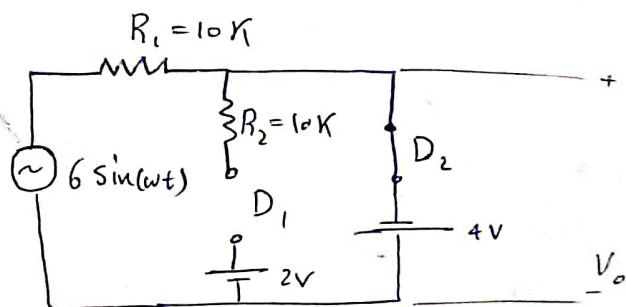

* Region 2 : (D_1 off, D_2 off)

$$-4 \leq V_i \leq 2$$


$$\Rightarrow -4 \leq V_x \leq 2$$

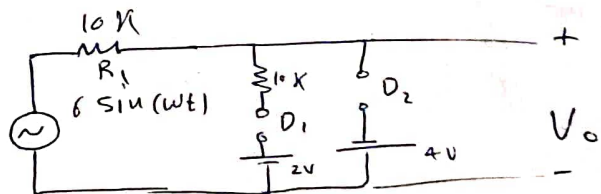

$$\Rightarrow V_o = V_i = V_x \quad (\because \text{no current is flowing through } R_1)$$

* Region 3 : (D_1 on , D_2 off)

$$2 \leq V_i \leq 6$$

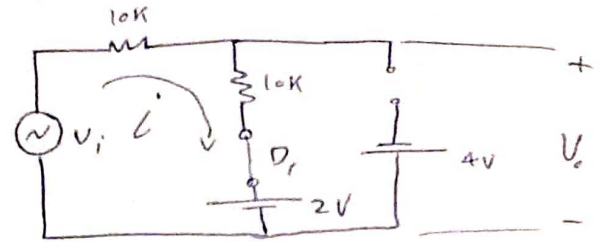

$$\Rightarrow V_o = V_X$$

$$\Rightarrow V_o = 10i + 2$$

$$\Rightarrow V_o = 16 \left(\frac{V_i - 2}{20} \right) + 2$$


$$\Rightarrow V_o = \frac{1}{2} V_i - 1 + 2$$

$$V_o = \frac{1}{2} V_i + 1$$

$$(V_i = 6 \sin(\omega t))$$



$$\Rightarrow V_o = 3 \sin(\omega t) + 1$$
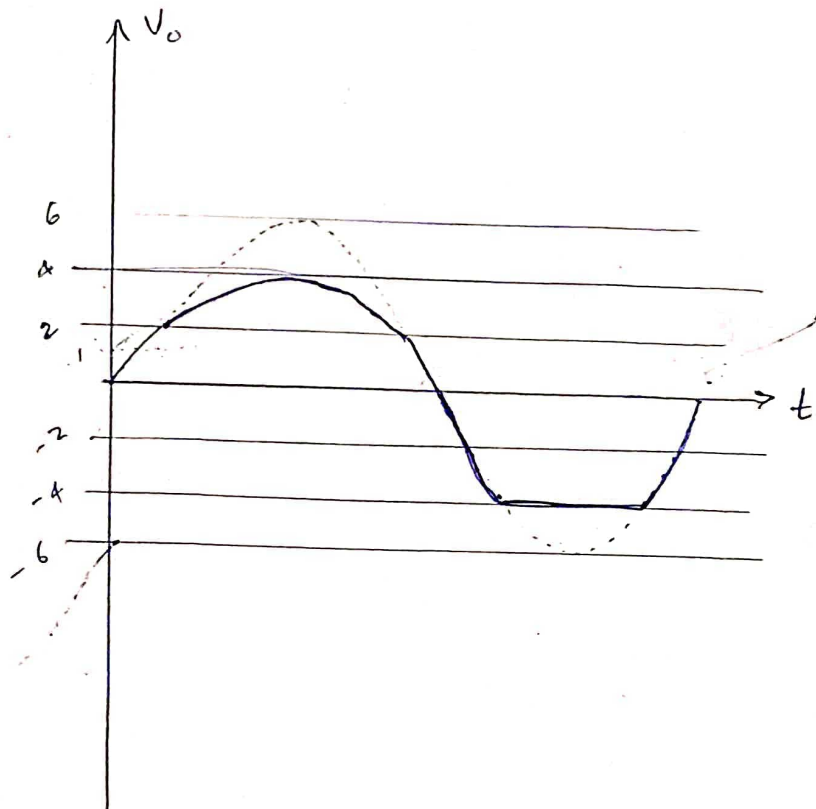
$$\Rightarrow V_o = \begin{cases} -4 & , -6 \leq V_i \leq -4 \\ 6 \sin(\omega t) & , -4 \leq V_i \leq 2V \\ 1 + 3 \sin(\omega t) & , 2 \leq V_i \leq 6V \end{cases}$$



3) a) $V_f = 0.6V$, $R_f = 0$

$V_{in} = 20 \sin(\omega t)$

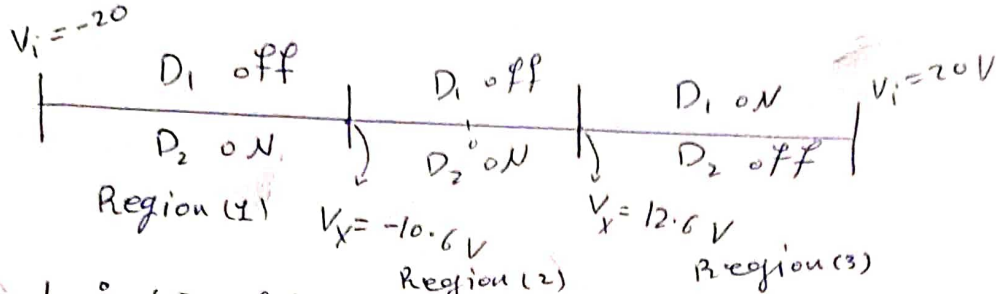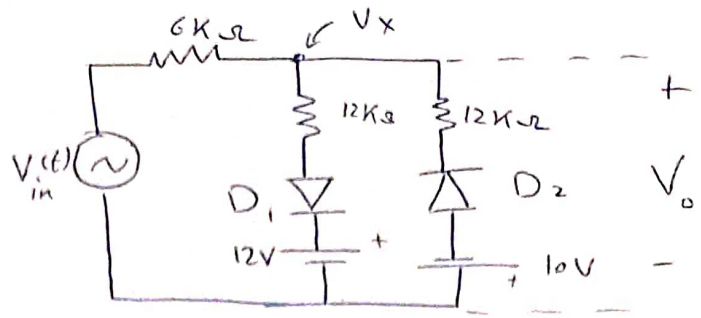

* Region 1 : (D_1 off, D_2 on)

$-20V \leq V_i \leq -10.6V$

$V_x = V_o$

$\Rightarrow V_o = 12i - 10.6$

$i = \frac{V_{in} - [-10.6]}{18}$

$\Rightarrow V_o = 12 \left(\frac{V_{in} + 10.6}{18} \right) - 10.6$

$\Rightarrow V_o = \frac{2}{3} V_{in} - 3.5333$

\Rightarrow at $V_x = -10.6V \Rightarrow V_{in} = -10.6V$

at $V_{in} = -20 \Rightarrow V_x = -16.87V$

$\Rightarrow -20 \leq V_o \leq -16.87$


* Region 2 : (D_1 off, D_2 off)

$-10.6 \leq V_i \leq 12.6$

$-10.6 \leq V_x \leq 12.6$

$\Rightarrow V_o = V_x = V_i$

(no current through 6K resistor)

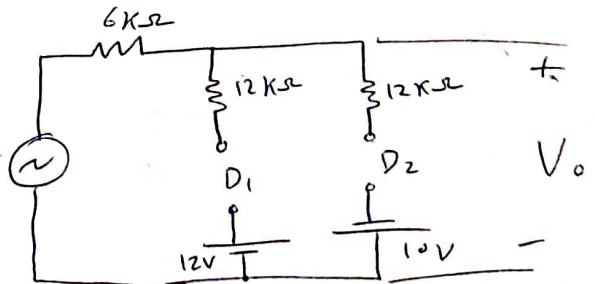



* Region 3 : (D_1 on, D_2 off)

$$12.6V \leq V_{in} \leq 20V$$


$$\Rightarrow V_o = V_x \Rightarrow V_o = 12i + 12.6$$

$$\Rightarrow V_o = 18 \left(\frac{V_{in} - 12.6}{18} \right) + 12.6$$

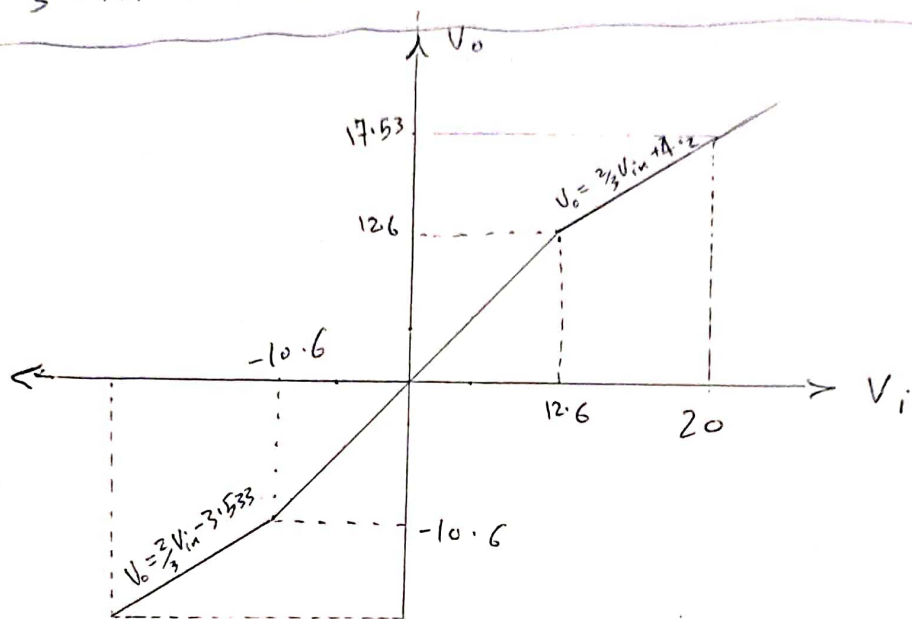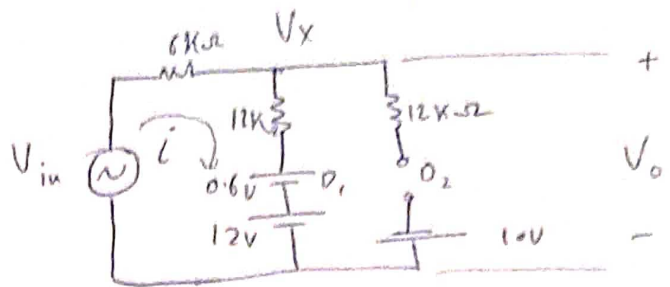
$$\Rightarrow V_o = \frac{2}{3} V_{in} + 4.2$$




b)

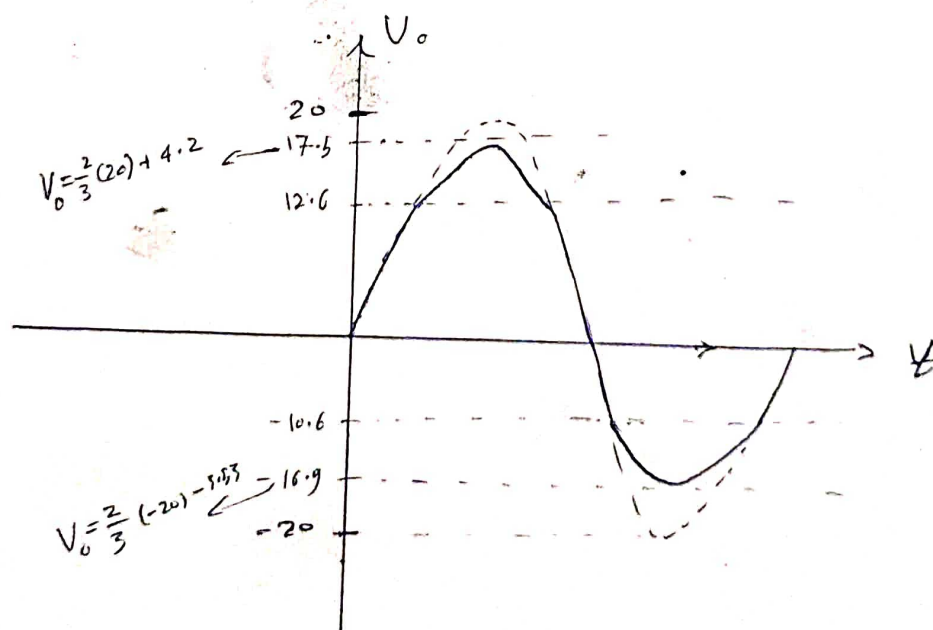

4)

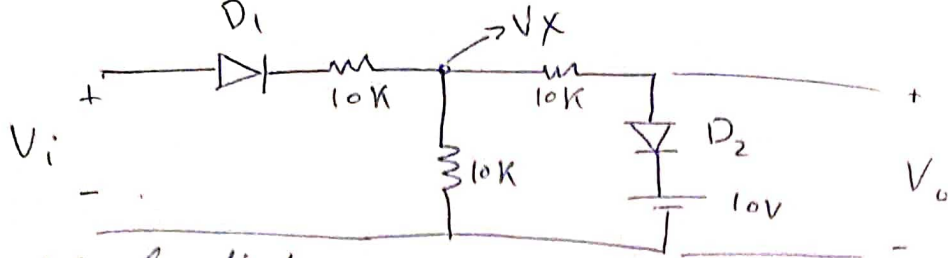


* Assuming ideal diode:

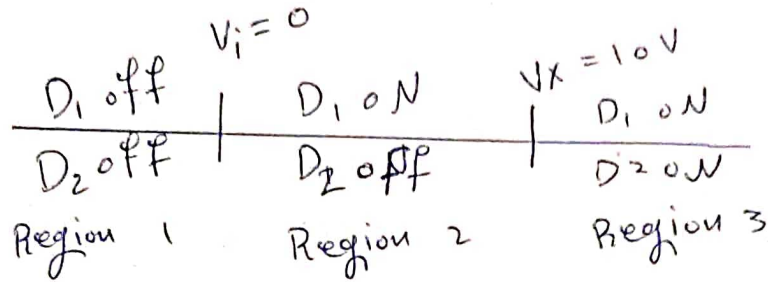

* Region 1 (D_1 off & D_2 off):

$$V_i \leq 0$$
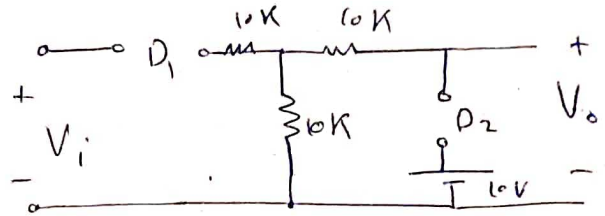
$$\Rightarrow V_o = V_X = 0 \quad (i=0)$$




* Region 2 (D_1 on, D_2 off):

$$0 \leq V_i, \quad 0 \leq V_X \leq 10$$

$$\Rightarrow V_o = V_X$$

$$\Rightarrow V_o = i(10) = \frac{V_i}{20}(10)$$

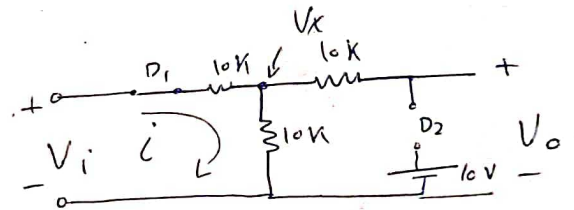
$$\Rightarrow \boxed{V_o = \frac{1}{2} V_i} \quad 0 \leq V_i \leq 20$$




* Region 3 (D_1 on, D_2 on):

$$20 \leq V_i, \quad 10 \leq V_X$$

$$\Rightarrow \boxed{V_o = 10V}$$


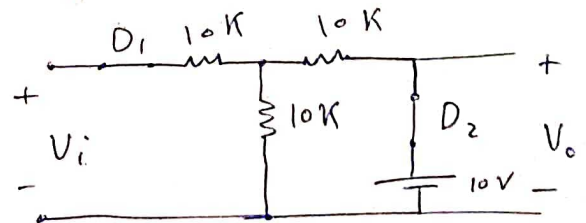


* Transfer characteristic:

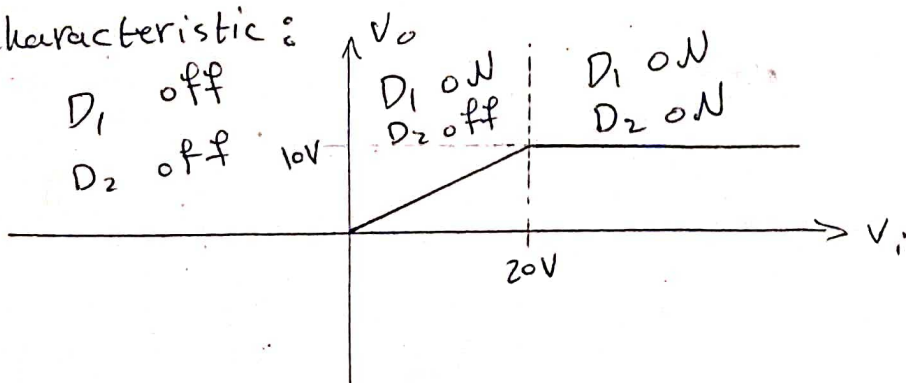

5)

Assuming ideal diodes.

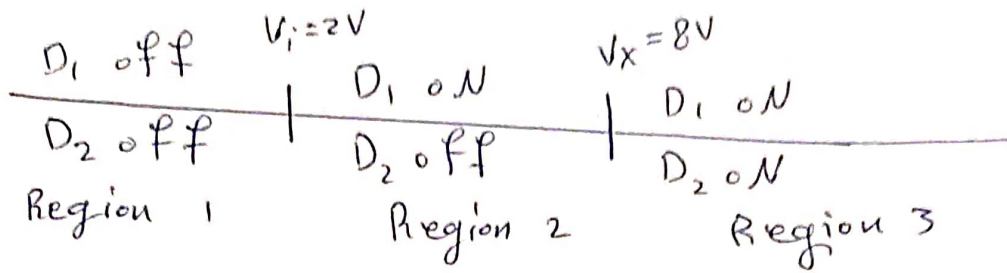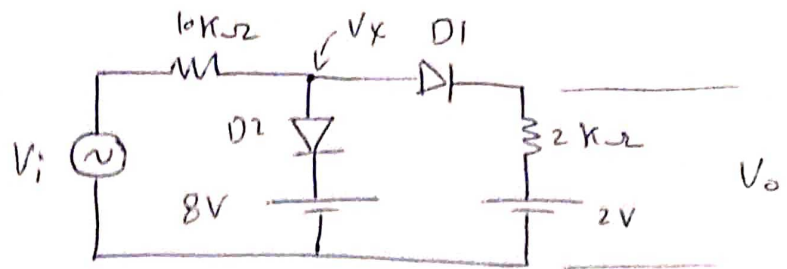


* Region 1 (D_1 off, D_2 off) :

$$V_i \leq 2V$$

$$V_x = V_i$$

$$V_x \leq 2$$

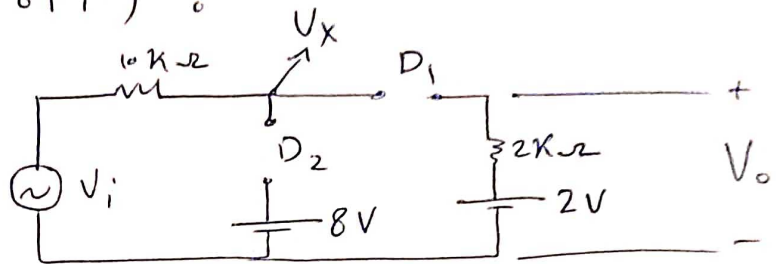

$$\Rightarrow V_o = 2V \quad (i=0)$$

* Region 2 (D_1 on, D_2 off) :

$$2 < V_i, \quad 2 < V_x \leq 8$$

$$\Rightarrow V_o = V_x$$


$$\Rightarrow V_o = 2i + 2$$

$$\Rightarrow V_o = 2 \left(\frac{V_i - 2}{12} \right) + 2$$

$$\Rightarrow V_o = \frac{V_i}{6} + 1.667$$

$$\text{at } V_x = 8 = V_o \Rightarrow V_i = 38V$$


$$\Rightarrow 2 < V_i < 38$$

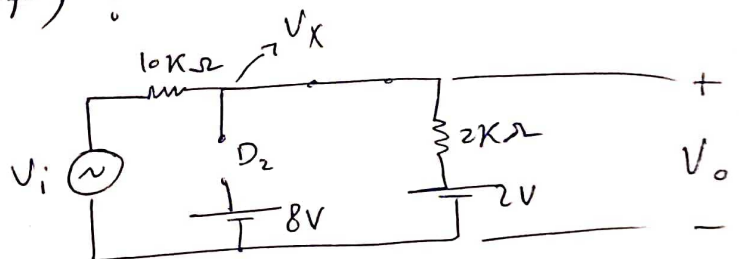

* Region 3 (D_1 on, D_2 on)

$$38 \leq V_i, \quad 8 < V_x$$


$$\Rightarrow V_o = V_x = 8V$$

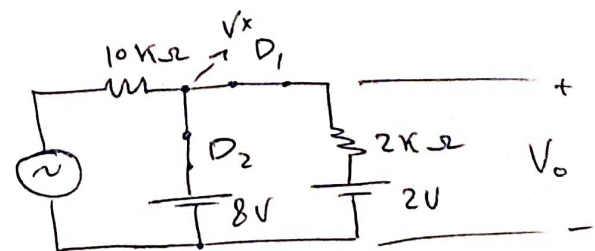

$$\Rightarrow V_o = \begin{cases} 2 & , V_i \leq 2 \\ \frac{1}{8} V_i + 1.667 & , 2 < V_i \leq 38 \\ 8 & , 38 < V_i \end{cases}$$

6)

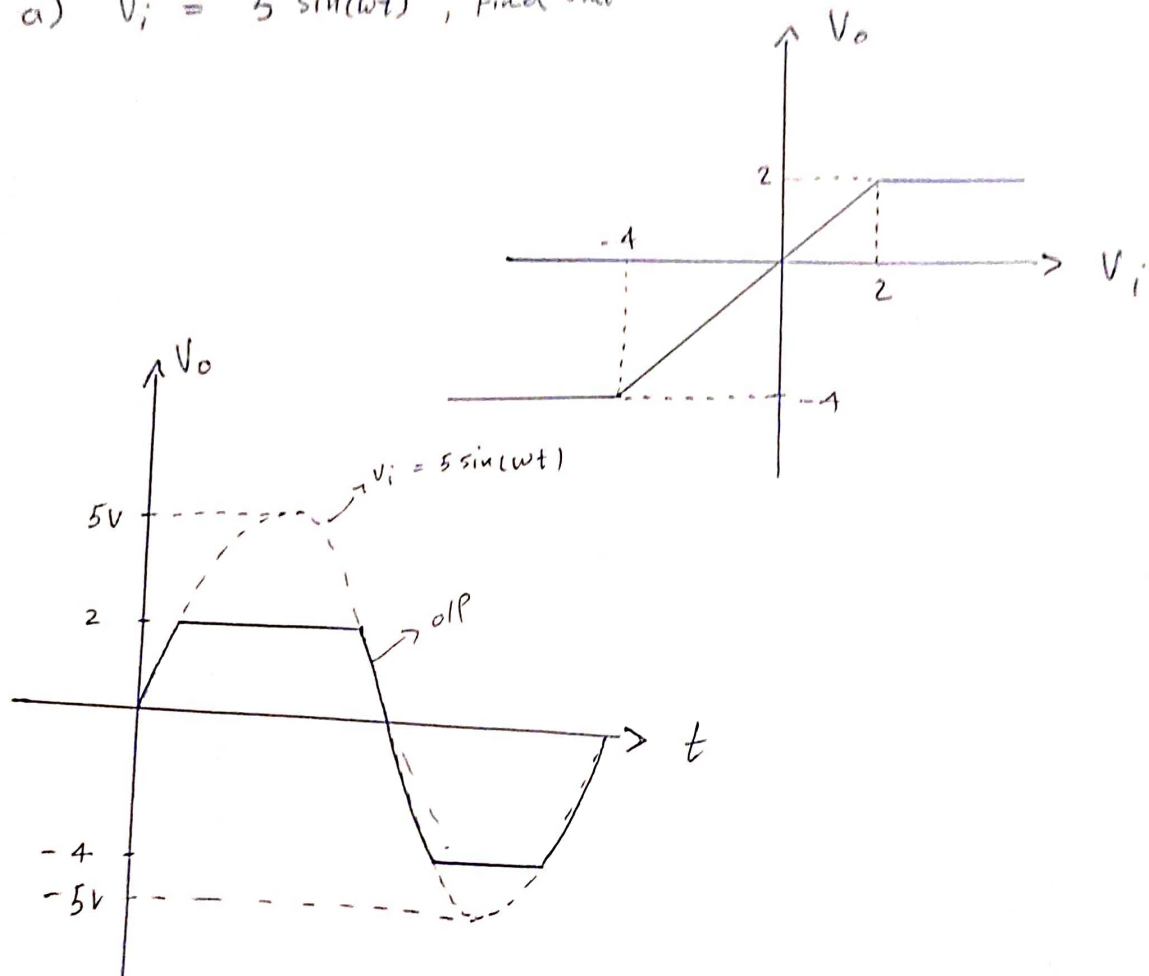a) $V_i = 5 \sin(\omega t)$, Find V_{out}



b)

