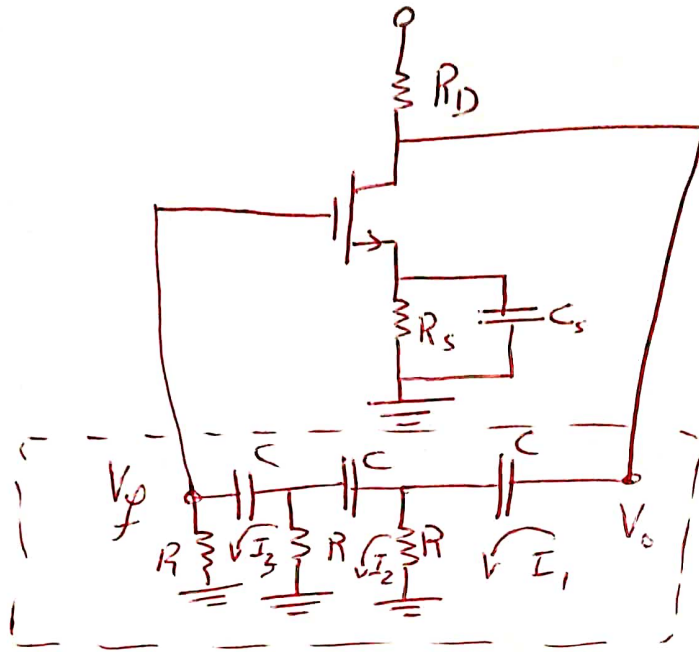


FET - phase shift oscillator



$$\Rightarrow V_o = I_1 \left(R + \frac{1}{sC} \right) + I_2 R$$

$$0 = I_2 \left(2R + \frac{1}{sC} \right) - I_1 R - I_3 R$$

$$0 = I_3 \left(2R + \frac{1}{sC} \right) - I_2 R$$

$$\Rightarrow V_g = I_3 R$$

$$\Rightarrow \Delta = \begin{vmatrix} R + \frac{1}{sC} & -R & 0 \\ -R & 2R + \frac{1}{sC} & -R \\ 0 & -R & 2R + \frac{1}{sC} \end{vmatrix} = \left(R + \frac{1}{sC} \right) \left[\left(2R + \frac{1}{sC} \right)^2 - R^2 \right] + R(-R) \left(2R + \frac{1}{sC} \right)$$

$$= \left(R + \frac{1}{sC} \right) \left[4R^2 + \frac{4R}{sC} + \frac{1}{s^2 C^2} - R^2 \right] - R \left(2R + \frac{1}{sC} \right)$$

$$= \frac{4R^3}{sC} + \frac{4R^2}{sC} + \frac{R}{s^2 C^2} - R^3 + \frac{4R^2}{sC} + \frac{4R}{s^2 C^2} + \frac{1}{s^3 C^3}$$

$$- \frac{R^2}{sC} - 2R^3 - \frac{R^2}{sC}$$

$$= R^3 + \frac{6R^2}{sC} + \frac{5R}{s^2 C^2} + \frac{1}{s^3 C^3}$$

$$\Rightarrow \Delta_3 = \begin{vmatrix} R + \frac{1}{sC} & -R & V_o \\ -R & 2R + \frac{1}{sC} & 0 \\ 0 & -R & 0 \end{vmatrix}$$

$$= V_o R^2$$

$$\Rightarrow I_3 = \frac{\Delta_3}{\Delta} = \frac{V_o R^2}{R^3 + \frac{6R^2}{sC} + \frac{5R}{s^2 C^2} + \frac{1}{s^3 C^3}}$$

$$\Rightarrow V_f = I_3 R = \frac{V_o R^2}{R^3 + \frac{6R^2}{sC} + \frac{5R}{s^2 C^2} + \frac{1}{s^3 C^3}}$$

$$\Rightarrow V_f = \frac{V_o R^3}{\left(R^3 - \frac{5R}{\omega^2 C^2}\right) + j\left(-\frac{6R^2}{\omega C} + \frac{1}{\omega^3 C^3}\right)}$$

at $\omega = \omega_o$

$$\frac{6R^2}{\omega_o R} = \frac{1}{\omega_o^3 C^3}$$

$$\Rightarrow \omega_o^2 = \frac{1}{6R^2 C^2}$$

$$\omega_o = \frac{1}{\sqrt{6} RC}$$


$$f_o = \frac{1}{2\pi\sqrt{6} RC}$$

* gain condition: at $\omega = \omega_o$

$$\Rightarrow \frac{V_f}{V_o} = \frac{R^3}{R^3 - \frac{5R(6R^2)}{C^2}} = \frac{R^3}{R^3 - 30R^3} = -\frac{1}{29}$$

$$\Rightarrow |A_v| \geq 29$$
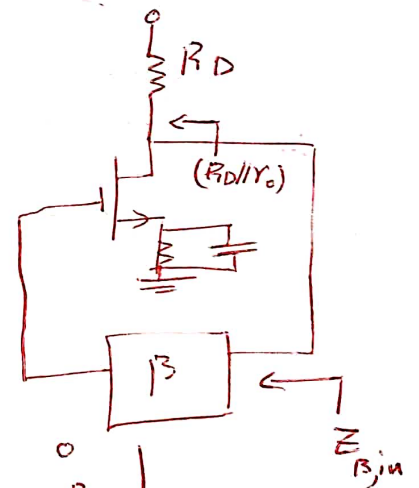
$$A_v = -g_m R_{out} \text{ , } R_{out} = Z_{B,in} \parallel (R_D \parallel r_o)$$



$$Z_{B,in} = \frac{V_o}{I_1} = \frac{V_o \Delta}{\Delta_1} \quad , \quad \Delta_1 = \begin{vmatrix} V_o & -R & 0 \\ 0 & 2R + \frac{1}{sC} & -R \\ 0 & -R & 2R + \frac{1}{sC} \end{vmatrix}$$

sub. by Δ & Δ_1

$$= V_o \left(\frac{1}{s^2 C^2} + \frac{4R}{sC} + 3R^2 \right)$$

$$\Rightarrow Z_{B,in} = R \frac{(s^3 R^3 C^3 + 6s^2 R^2 C^2 + 5sRC + 1)}{3s^3 R^3 C^3 + 4s^2 R^2 C^2 + sRC}$$

$$= R \frac{(1 - 6\omega^2 R^2 C^2) + j\omega RC(5 - \omega^2 R^2 C^2)}{-4\omega^2 R^2 C^2 + j\omega RC(1 - 3\omega^2 R^2 C^2)}$$

$$\Rightarrow A_v = -g_m (Z_{in} \parallel R_D \parallel r_o)$$

at $\omega = \omega_0$

$$\begin{aligned} \Rightarrow Z &= R \frac{(1 - \frac{6R^2C^2}{6R^2C^2}) + j \frac{-RC}{\sqrt{6}RC} (5 - \frac{R^2C^2}{6R^2C^2})}{-4(\frac{1}{6R^2C^2})R^2C^2 + j \frac{RC}{\sqrt{6}RC} (1 - 3\frac{R^2C^2}{6R^2C^2})} \\ &= R \frac{j \frac{5 - \frac{1}{6}}{\sqrt{6}}}{-\frac{4}{6} + j \frac{1}{\sqrt{6}} (1 - \frac{1}{2})} \\ &= R \frac{j \frac{29}{6\sqrt{6}}}{-\frac{4}{6} + j \frac{1}{\sqrt{6}} (\frac{1}{2})} = R \frac{j 29}{-4\sqrt{6} + j 3} \Omega \\ &= (2.82 \angle -72.4^\circ) R \Omega \end{aligned}$$

* To avoid load the o/p of the Amplifier:


$$\begin{aligned} 2.82R &\gg (R_D \parallel r_o) \\ \Rightarrow A_v &\approx -g_m (R_D \parallel r_o) > 29 \end{aligned}$$

Note: if the effect of loading is taken into consideration \Rightarrow we can get to result similar to that of phase-shift BJT (By the same analysis)

* By analogy:

$$\frac{V_{gs}}{g_m V_{gs}} = \frac{I_b R_o}{h_{fe} I_b} \quad \begin{array}{|c|c|} \hline \text{BJT} & \text{MOS} \\ \hline \frac{I_b R_o}{V_{be}} & \frac{I_b R_o}{V_{gs}} \\ \hline \end{array}$$

\hookrightarrow o/p current

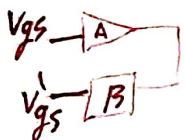

$$\therefore \frac{V_{gs}}{V_{gs}} = \frac{I_b}{I_b} = 1$$

$$\begin{aligned} \Rightarrow g_m \frac{1}{h_{fe}} &\Rightarrow \frac{R}{h_{fe}} \Rightarrow g_m R \Rightarrow h_{fe} \\ \text{in BJT: } h_{fe} &> 23 + 4\left(\frac{R_o}{R}\right) + 29\frac{R}{R_o} \\ \text{in MOS: } g_m R &> 23 + 4\frac{R_o}{R} + 29\frac{R}{R_o} \end{aligned}$$