

# **Electronic Circuits Analysis III**


**Lecture (2)**

**Oscillators**

**Wein-Bridge oscillator**


**Fall 2020**

# Wien-Bridge Oscillator

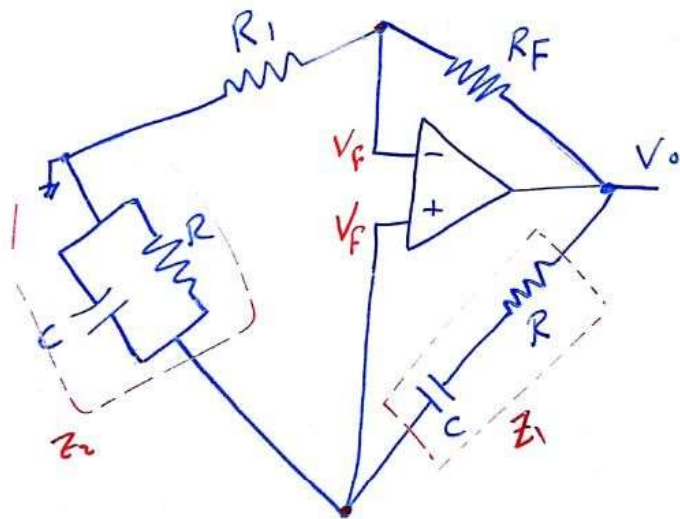


Balanced - Bridge
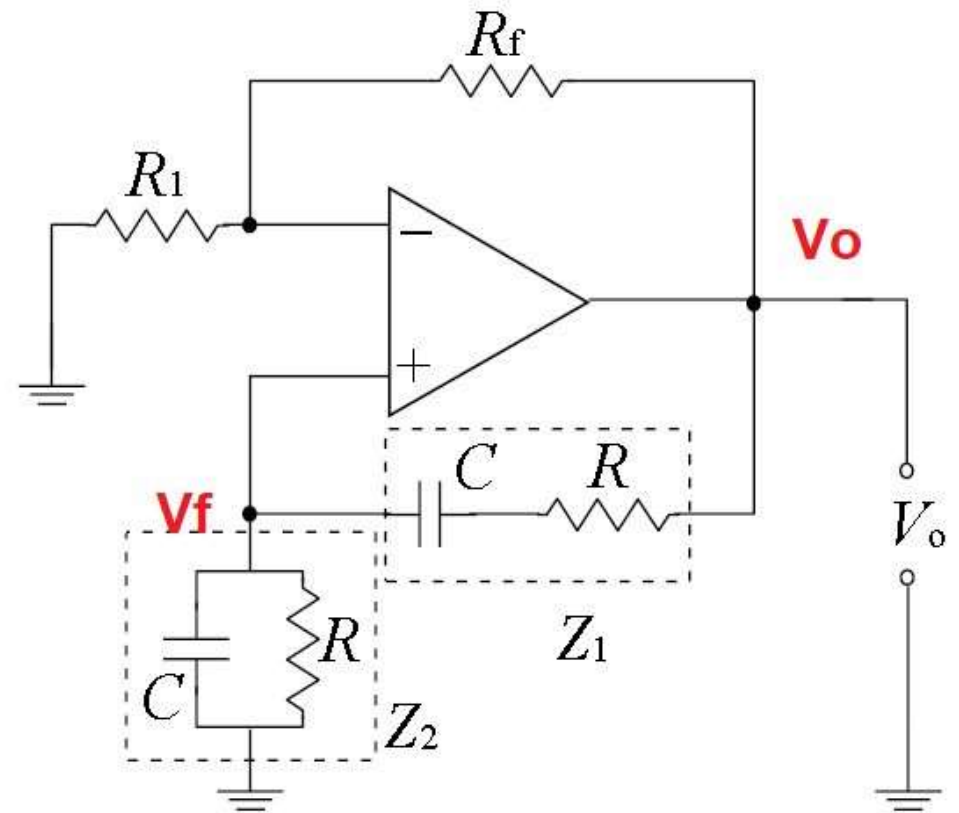
$$\therefore \frac{R_F}{R_1} = \frac{Z_1}{Z_2}$$



Wien Bridge Oscillator

Proof:

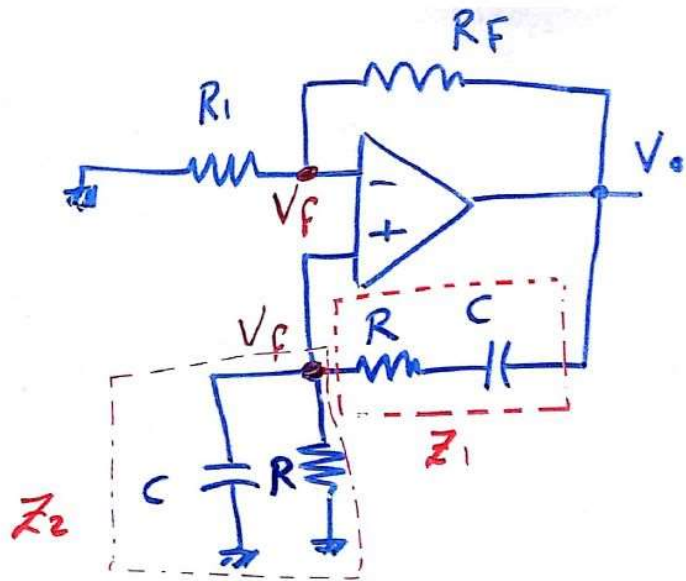


$$A = \frac{V_o}{V_F}, \quad \beta = \frac{V_F}{V_o}$$

$$* V_o = \left(1 + \frac{R_F}{R_1}\right) V_F$$

$$\therefore \boxed{A = \frac{V_o}{V_F} = 1 + \frac{R_F}{R_1}}$$

B\_circuit

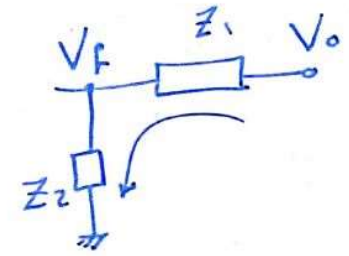

$$* V_F = \frac{V_o}{Z_1 + Z_2} \cdot Z_2$$

$$\therefore \beta = \frac{V_F}{V_o} = \frac{Z_2}{Z_1 + Z_2}$$

For oscillation

$$A = \frac{1}{\beta} = \frac{Z_1 + Z_2}{Z_2} = 1 + \frac{Z_1}{Z_2}$$

$$1 + \frac{R_F}{R_1} = 1 + \frac{Z_1}{Z_2}$$

$$\frac{R_F}{R_1} = \frac{Z_1}{Z_2}$$

$$* Z_1 = R + \frac{1}{j\omega C} = R - jX_C$$

$$Z_1 = R + \frac{1}{sC} = \frac{sCR + 1}{sC}$$

$$* Z_2 = \frac{R \cdot \frac{1}{sC}}{R + \frac{1}{sC}} = \frac{R}{sCR + 1}$$



$$\frac{R_F}{R_1} = \frac{SCR+1}{sC} \times \frac{(SCR+1)}{R}$$

$$\frac{R_F}{R_1} = \frac{(SCR+1)^2}{SCR}$$

$$\frac{R_F}{R_1} = \frac{s^2 C^2 R^2 + 2SCR + 1}{SCR}$$

$$\frac{R_F}{R_1} = SCR + 2 + \frac{1}{SCR}$$

$$s = j\omega$$

$$\frac{R_F}{R_1} = j\omega RC + 2 + \frac{1}{j\omega RC}$$

$$\frac{R_F}{R_1} = 2 + j\left[\omega RC - \frac{1}{\omega RC}\right]$$

$$\text{Im} = 0$$

$$\omega RC = \frac{1}{\omega RC}$$

$$\omega^2 = \frac{1}{R^2 C^2}$$

$$\omega = \frac{1}{RC} = 2\pi f_0$$


$$\therefore \left\{ f_0 = \frac{1}{2\pi RC} \right\} \text{ oscillation Frequency}$$

Oscillation Condition

$$\left\{ \frac{R_F}{R_1} = 2 \right\}$$



## Feedback Factor ( $\beta$ )

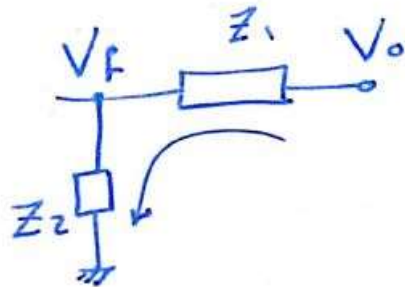

$$* V_f = \frac{V_o}{Z_1 + Z_2} \cdot Z_2$$

$$\therefore \beta = \frac{V_f}{V_o} = \frac{Z_2}{Z_1 + Z_2}$$

$$* Z_2 = \frac{R \cdot \frac{1}{sC}}{R + \frac{1}{sC}} = \frac{R}{sCR + 1}$$

$$* Z_1 = R + \frac{1}{sC} = \frac{sCR + 1}{sC}$$

$$\beta = \frac{\frac{R}{sCR + 1}}{\frac{sCR + 1}{sC} + \frac{R}{sCR + 1}}$$

$$\beta = \frac{R}{\frac{(sCR + 1)^2}{sC} + R}$$

$$\beta = \frac{sCR}{(sCR + 1)^2 + sCR}$$

$$\beta = \frac{sCR}{s^2 C^2 R^2 + 2sCR + 1 + sCR}$$

$$\beta = \frac{sCR}{s^2 C^2 R^2 + 3sCR + 1}$$

put  $s = j\omega$



$$\beta = \frac{j\omega RC}{(j\omega)^2 C^2 R^2 + 3j\omega RC + 1}$$

$$\beta = \frac{j\omega RC}{-\omega^2 C^2 R^2 + 1 + j3\omega RC}$$

$$\beta = \frac{j\omega RC}{[1 - \omega^2 C^2 R^2] + j3\omega RC}$$

But  $A = 1 + \frac{R_F}{R_1}$  Real,  
 $A\beta = 1 \therefore \beta$  must be Real

$\beta \rightarrow$  Real

$$1 - \omega^2 C^2 R^2 = 0$$

$$\omega^2 R^2 C^2 = 1 \quad \therefore \omega = \frac{1}{RC}$$

$$\beta = \frac{j\omega RC}{j3\omega RC} \rightarrow \boxed{\beta = \frac{1}{3}} \therefore \frac{1}{\beta} = 3 = 1 + \frac{R_F}{R_1} \rightarrow \boxed{\frac{R_F}{R_1} = 2}$$

$$\text{Im} = 0$$

$$\omega RC = \frac{1}{\omega RC}$$

$$\omega^2 = \frac{1}{R^2 C^2}$$

$$\omega = \frac{1}{RC} = 2\pi f_0$$

$$\therefore \boxed{f_0 = \frac{1}{2\pi RC}} \text{ Oscillation Frequency}$$

Oscillation Condition

$$\boxed{\frac{R_F}{R_1} = 2}$$

# Wien Bridge Oscillator


$$\beta = \frac{RX_C}{3RX_C + j(R^2 - X_C^2)}$$

$$\angle A = 0$$

$$\angle \beta = 0$$

Imaginary part of (B) = 0

$$\beta = \frac{1}{3}$$

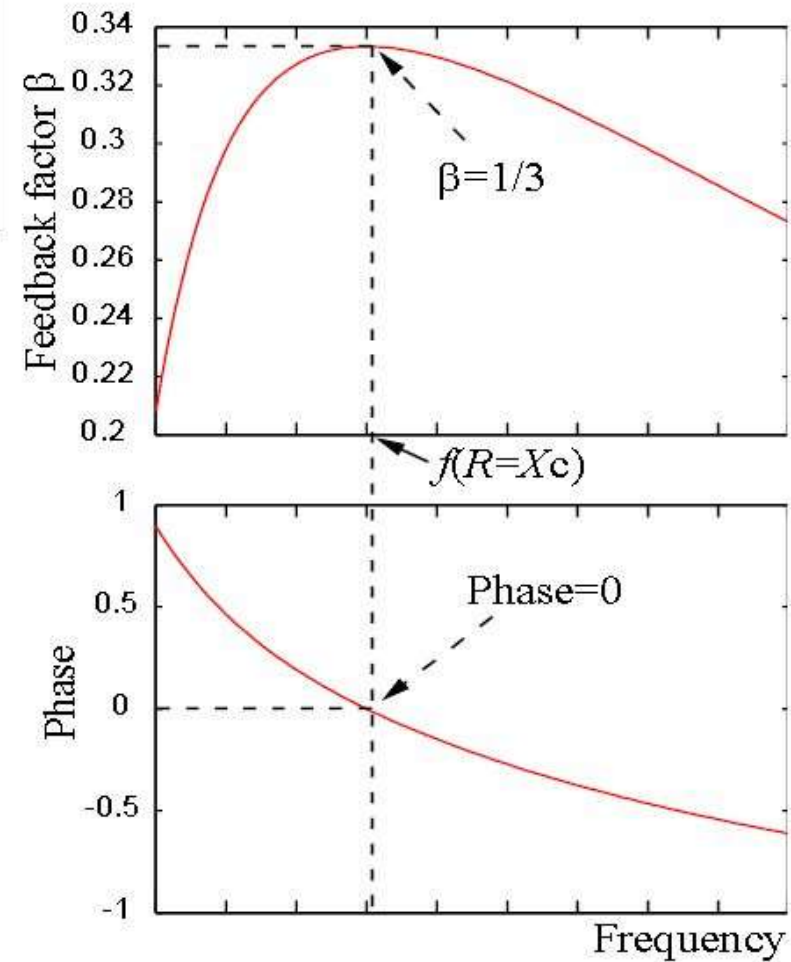

# Wien Bridge Oscillator

$$\beta = \frac{1}{3}$$

Due to *Barkhausen Criterion*,


Loop gain  $A_v\beta = 1$

where

$A_v$  : Gain of the amplifier

$$A_v\beta = 1 \Rightarrow A_v = 3 = 1 + \frac{R_f}{R_1}$$


Therefore,  $\frac{R_f}{R_1} = 2$

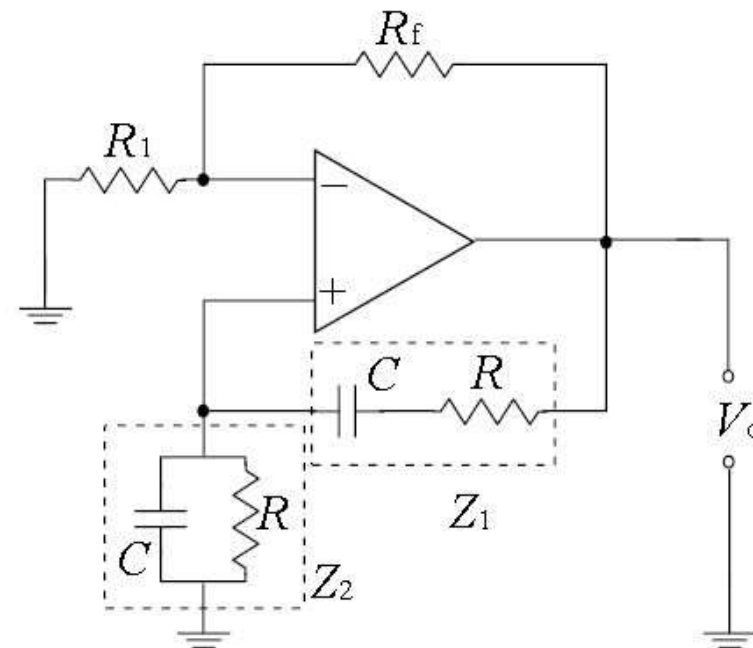

Wien Bridge Oscillator



# Wien Bridge Oscillator

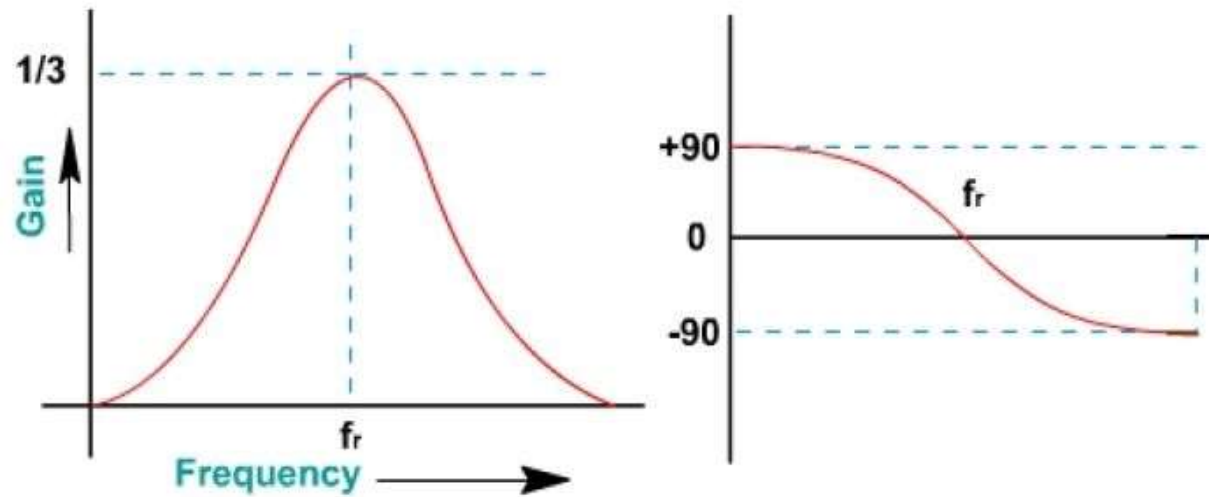

$$\beta = \frac{1}{3}$$

$$\omega = 1 / \sqrt{R_1 R_2 C_1 C_2}$$

$$\omega = 1 / RC$$

$$f_r = \frac{1}{2\pi RC}$$

## Example

Design a wein-Bridge oscillator of frequency 10 KHz.

Sol.

$$f_o = \frac{1}{2\pi RC} = 10 \times 10^3$$

Let  $C = 0.01 \text{ MF}$

$$10^4 = \frac{1}{2\pi R (0.01 \times 10^6)}$$


$$R = 1592 \Omega = 1.592 \text{ k}\Omega$$

$$* \frac{R_F}{R_1} = 2 \rightarrow \text{let } \begin{cases} R_1 = 10 \text{ k}\Omega \\ R_F = 20 \text{ k}\Omega \end{cases}$$


	RC Phase Shift Oscillator	Wien Bridge Oscillator
1.	It is a phase shift oscillator used for low frequency range.	It is also a phase shift oscillator used for low frequency range.
2.	The <b>feedback</b> network is RC network with three RC sections.	The <b>feedback</b> network is lead-lag network which is called Wien bridge circuit.
3.	The <b>feedback</b> network introduces $180^\circ$ phase shift.	The <b>feedback</b> network does not introduce any phase shift.
4.	Amplifier circuit introduces $180^\circ$ phase shift.	Amplifier circuit does not introduce any phase shift.
5.	The frequency of oscillations is, $f = \frac{1}{2\pi RC\sqrt{6}}$	The frequency of oscillations is, $f = \frac{1}{2\pi RC}$
6.	The amplifier gain condition is, $ A  \geq 29$	The amplifier gain condition is, $ A  \geq 3$
7.	The frequency variation is difficult.	Mounting the two capacitors on common shaft and varying their values, frequency can be varied.



# Transistor Phase-Shift Oscillator

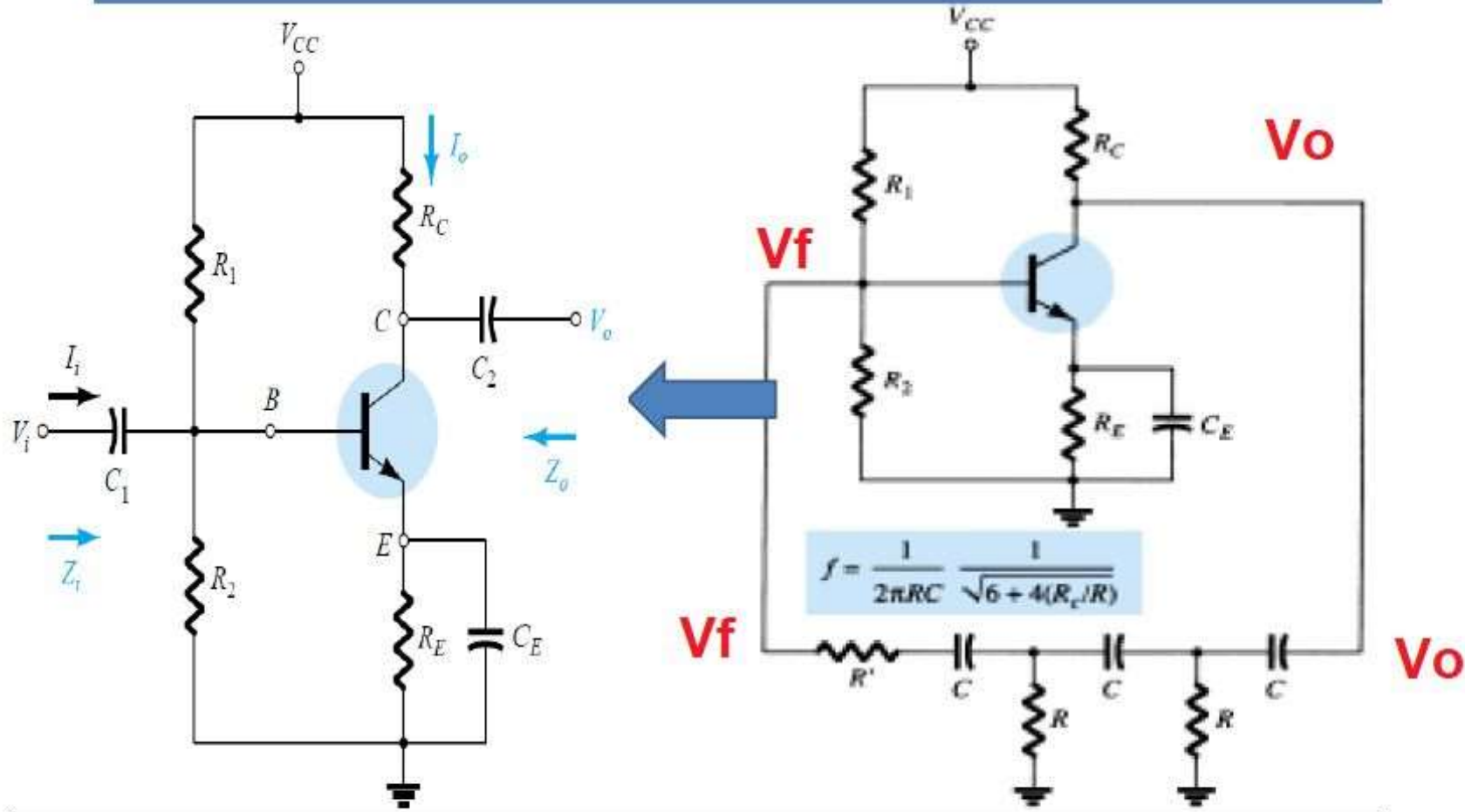

# FET Phase-Shift Oscillator

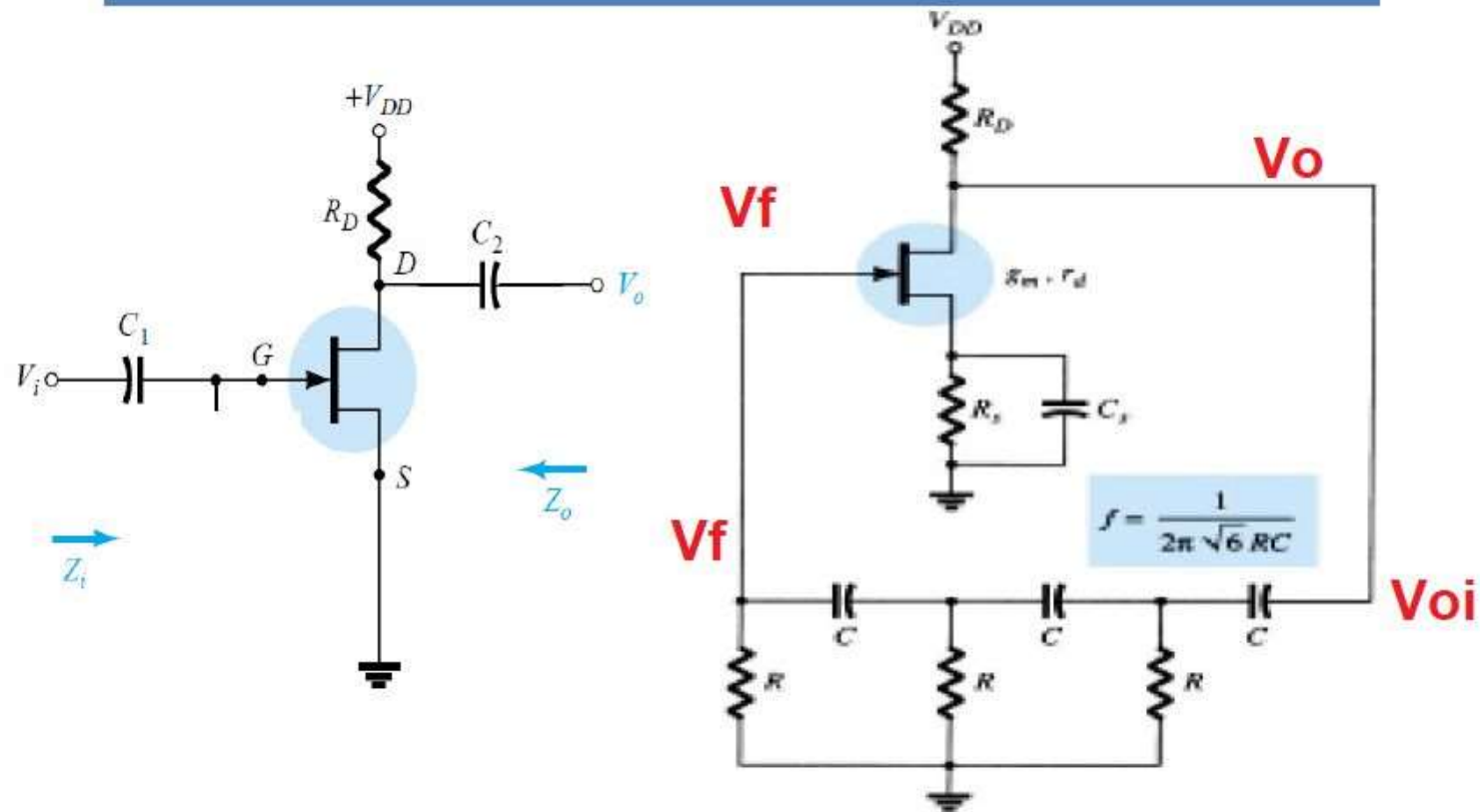




## Example

Analyze the oscillator circuit shown in Figure.

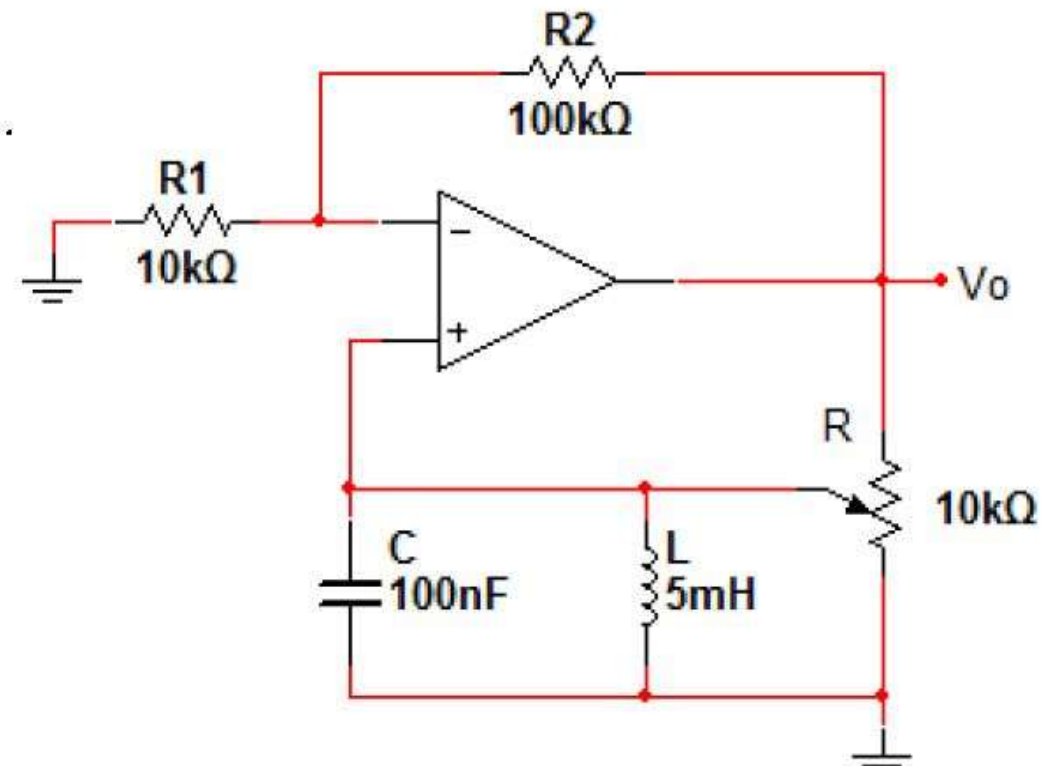1. Derive an expression for the oscillation frequency ( $f_o$ ).
2. Calculate the minimum value of  $R$  for oscillation.
3. Calculate the frequency of oscillation.



# Solution

1. Derive an expression for the oscillation frequency ( $f_o$ ).

\* open-loop gain

$$A = 1 + \frac{R_2}{R_1} = \frac{V_o}{V_f}$$

\*  $\beta = \frac{V_f}{V_o} = \frac{Z}{R+Z}$

oscillation condition

$$A = \frac{1}{\beta} = \frac{R+Z}{Z}$$

$$\downarrow$$




$$1 + \frac{R_2}{R_1} = \frac{R}{Z} + 1$$

$$\therefore \boxed{\frac{R}{Z} = \frac{R_2}{R_1}} \quad [I]$$

\*  $\frac{1}{Z} = \frac{1}{10-R} + sC + \frac{1}{sL}$

At oscillation frequency,  $s = j\omega_o$
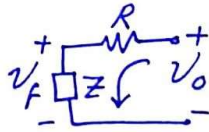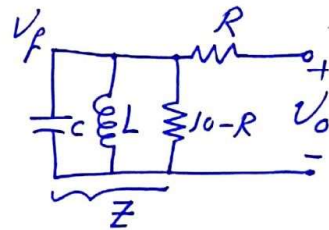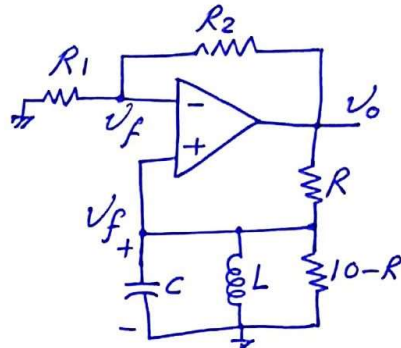
$$\therefore \frac{1}{Z} = \frac{1}{10-R} + j\omega_o C + \frac{1}{j\omega_o L}$$



$$\therefore \frac{1}{Z} = \frac{1}{10-R} + j\omega_o C - j\frac{1}{\omega_o L}$$

$$\boxed{\frac{1}{Z} = \frac{1}{10-R} + j(\omega_o C - \frac{1}{\omega_o L})}$$

sub. in to [I]

$$\therefore R \left[ \frac{1}{10-R} + j(\omega_o C - \frac{1}{\omega_o L}) \right] = \frac{R_2}{R_1}$$

$$\frac{R}{10-R} + j(\omega_o C - \frac{1}{\omega_o L}) = \frac{R_2}{R_1} + j0$$

$$\therefore \omega_o C - \frac{1}{\omega_o L} = 0$$

$$\therefore \omega_o^2 = \frac{1}{L \cdot C} \rightarrow \omega_o = \frac{1}{\sqrt{L \cdot C}} = 2\pi f_o$$

$$\therefore \boxed{f_o = \frac{1}{2\pi \sqrt{L \cdot C}}} \quad \text{oscillation Frequency}$$

Condition  $\boxed{\frac{R}{10-R} = \frac{R_2}{R_1}}$

2. Calculate the minimum value of R for oscillation.

$$\frac{R}{10-R} = \frac{R_2}{R_1} = \frac{100}{10} = 10$$

$$\therefore 10(10-R) = R$$

$$100 - 10R = R$$

$$100 = 11R$$

$$R = \frac{100}{11} = 9.091 \text{ k}\Omega \quad \# \Rightarrow \text{min. value of } R \text{ to sustain oscillation.}$$

3. Calculate the frequency of oscillation.


$$f_o = \frac{1}{2\pi\sqrt{L.C}} = \frac{1}{2\pi\sqrt{(5 \times 10^{-3})(100 \times 10^{-9})}}$$

$$\{f_o = 7.11763 \text{ kHz}\} \quad \#$$

# Example

Analyze the Wien-bridge oscillator with amplitude limiter shown in Figure

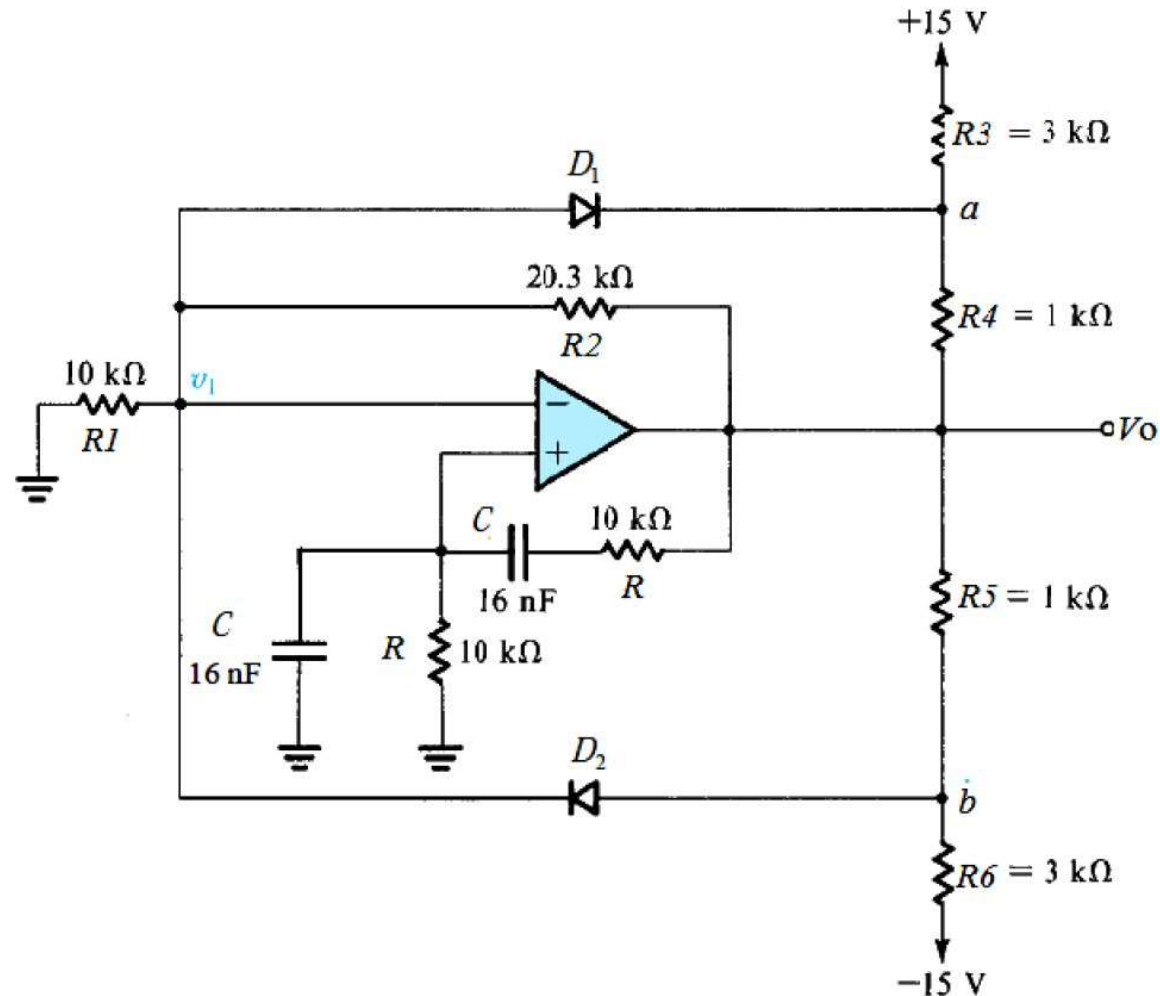1. Derive an expression for the oscillation frequency ( $f_o$ ).
2. Calculate the frequency of oscillation.
3. Calculate the peak-to-peak output voltage ( $V_{o-pp}$ )




$$* A = \frac{V_o}{V_f} = 1 + \frac{R_2}{R_1}$$

$$* \beta = \frac{V_f}{V_o} = \frac{Z_2}{Z_1 + Z_2}$$

$$* \frac{1}{\beta} = \frac{Z_1 + Z_2}{Z_2} = 1 + \frac{Z_1}{Z_2}$$

$$A \cdot \beta = 1 \Rightarrow A = \frac{1}{\beta}$$
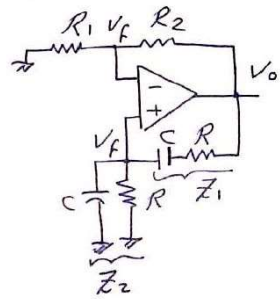
$$1 + \frac{R_2}{R_1} = 1 + \frac{Z_1}{Z_2}$$



$$\frac{R_2}{R_1} = \frac{Z_1}{Z_2}$$

$$* Z_1 = R + \frac{1}{sC} = \frac{sCR + 1}{sC}$$

$$* Z_2 = \frac{R \cdot \frac{1}{sC}}{R + \frac{1}{sC}} = \frac{R}{sCR + 1}$$

$$\therefore \frac{R_2}{R_1} = \frac{sCR + 1}{sC} \cdot \frac{sCR + 1}{R}$$

$$\frac{R_2}{R_1} = \frac{s^2 C^2 R^2 + 2sCR + 1}{sCR}$$

$$\frac{R_2}{R_1} = sCR + 2 + \frac{1}{sCR} \quad \text{put } s = j\omega$$

$$\frac{R_2}{R_1} = j\omega_0 RC + 2 + \frac{1}{j\omega_0 RC}$$

$$\frac{R_2}{R_1} = j\omega_0 RC + 2 - j \frac{1}{\omega_0 RC}$$

$$\frac{R_2}{R_1} = 2 + j[\omega_0 RC - \frac{1}{\omega_0 RC}]$$

$$\therefore \boxed{\frac{R_2}{R_1} = 2} \text{ oscillation condition.}$$

$$\therefore \omega_0 RC = \frac{1}{\omega_0 RC}$$

$$\omega_0^2 = \frac{1}{(RC)^2}$$

$$\omega_0 = \frac{1}{RC}$$

$$2\pi f_0 = \frac{1}{RC}$$

$$\therefore \boxed{f_0 = \frac{1}{2\pi RC}} \text{ \# oscillation frequency}$$



2. Calculate the frequency of oscillation.

$$f_o = \frac{1}{2\pi(10^4)(16 \times 10^{-9})}$$

$$f_o = 994.72 \text{ Hz}$$

3. Calculate the peak-to-peak output voltage ( $V_{opp}$ )

\* As  $V_o$  goes positive

$$V_x = \frac{V_o}{R_1 + R_2} \cdot R_2 = \frac{V_o}{10 + 20.3} \cdot 10 = 0.33 V_o$$

$$V_x = 0.33 V_o \quad (1) \quad (0.5)$$

$$* V_b = \frac{-V_{cc} \cdot R_5}{R_5 + R_6} + \frac{V_o \cdot R_6}{R_5 + R_6}$$

$$V_b = \frac{-15 \times 1}{1 + 3} + \frac{V_o \times 3}{1 + 3}$$

$$V_b = -3.75 + 0.75 V_o \quad (2) \quad (0.5)$$

For  $D_2$  to be ON  $V_b - V_x = 0.7 \text{ V}$

$$(-3.75 + 0.75 V_o) - (0.33 V_o) = 0.7$$

$$0.42 V_o = 4.45$$

$$V_o \cong 10.6 \text{ V} \quad (\text{+ve peak}) \quad \text{10.6V}$$

\* As  $V_o$  goes negative

$$V_a = \frac{V_{cc} R_4}{R_3 + R_4} + \frac{V_o R_3}{R_3 + R_4}$$

$$V_a = \frac{15 \times 1}{4} + \frac{3 V_o}{4}$$

$$V_a = 3.75 + 0.75 V_o \quad (3)$$

For  $D_1$  to be ON  $V_x - V_a = 0.7$

$$0.33 V_o - (3.75 + 0.75 V_o) = 0.7$$

$$V_o = -10.6 \text{ V} \quad (\text{-ve peak}) \quad -10.6 \text{ V}$$

∴ The peak-to-peak output voltage is

$$V_{opp} = 10.6 - (-10.6)$$

$$V_{opp} = 21.2 \text{ V} \quad \#$$