

Electronic Devices

Lecture 8 P-N Junction

Dr. Roaa Mubarak



Diode Applications

- Rectifying
- **Clipping**
- Clamping


Clipping

- It used in wave shaping, limit or “clip” signal portions.
- Eliminate signal portions that are above or below a specified level.
- **Application:**

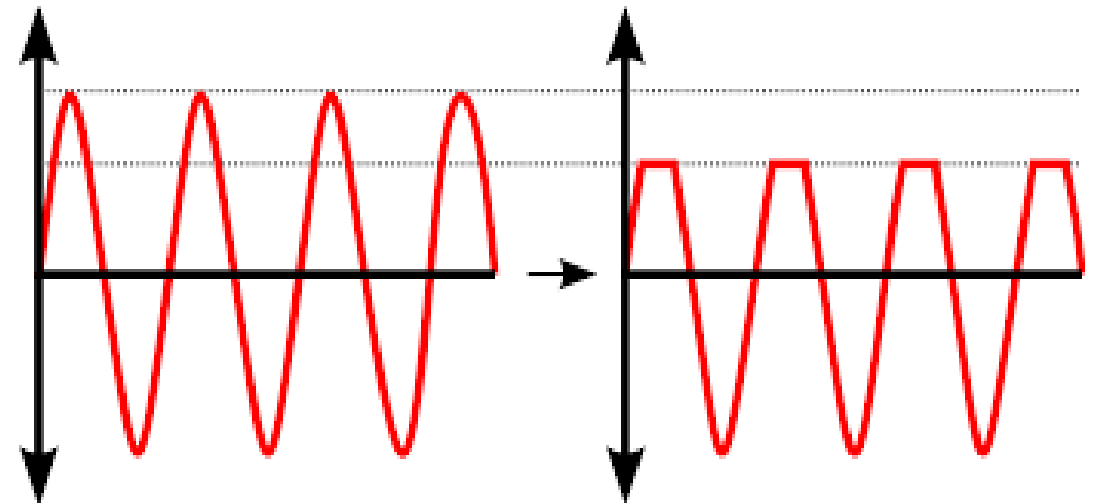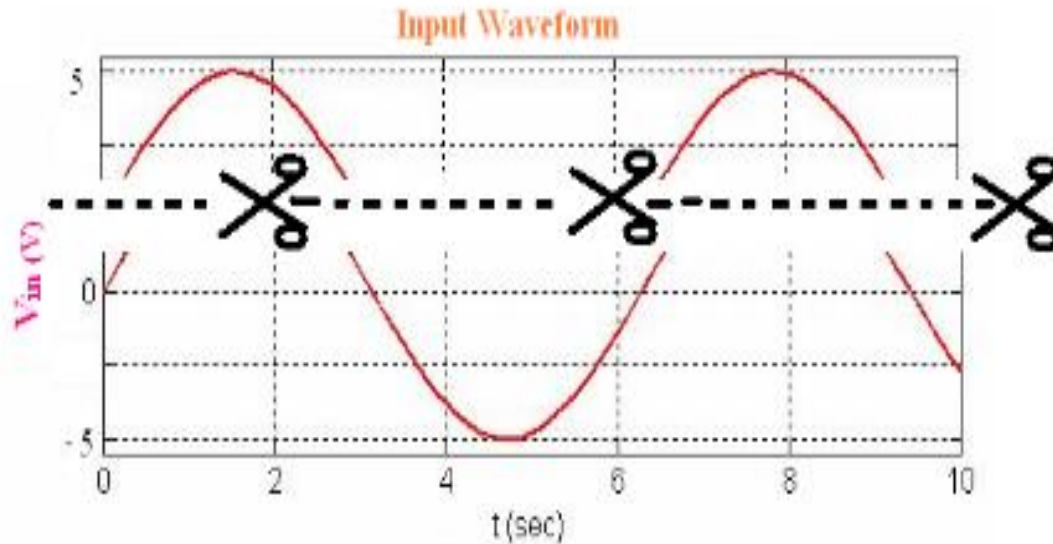
Limit input voltage to an electronic circuit to prevent component damage.




Clipping

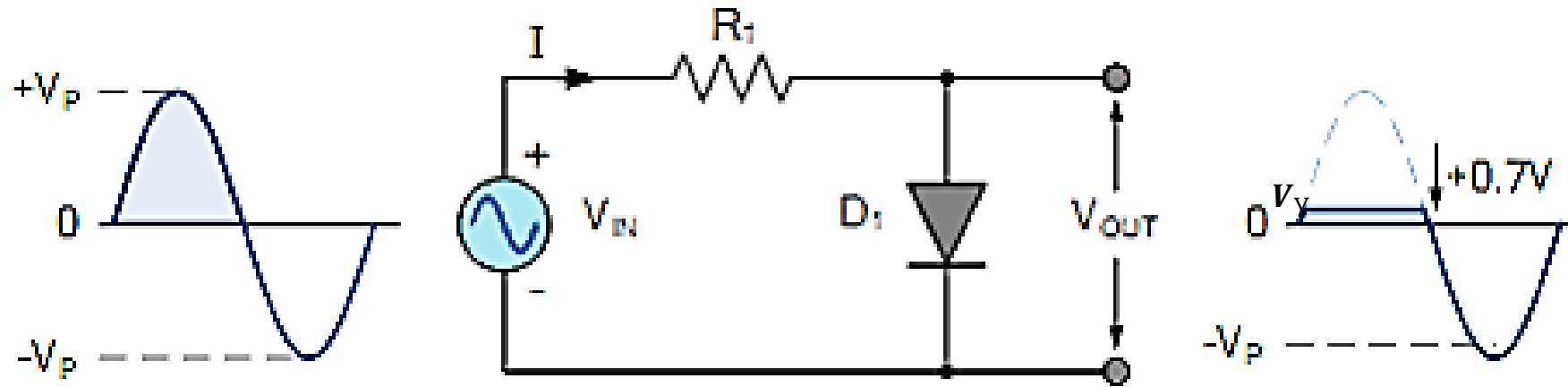

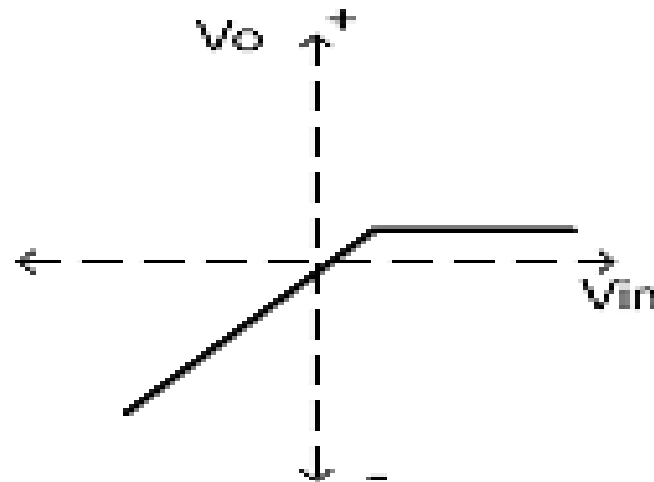- $V_s > V_Y \rightarrow D \text{ is ON} \rightarrow V_o = V_Y$
- $V_s < V_Y \rightarrow D \text{ is OFF} \rightarrow V_o = V_s$




Transfer characteristics

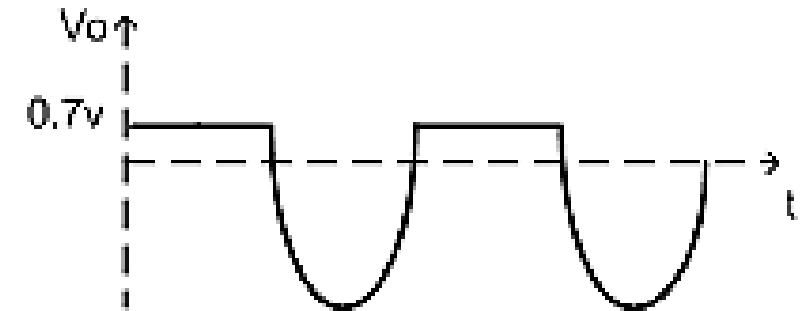


Output Waveform


Clipping

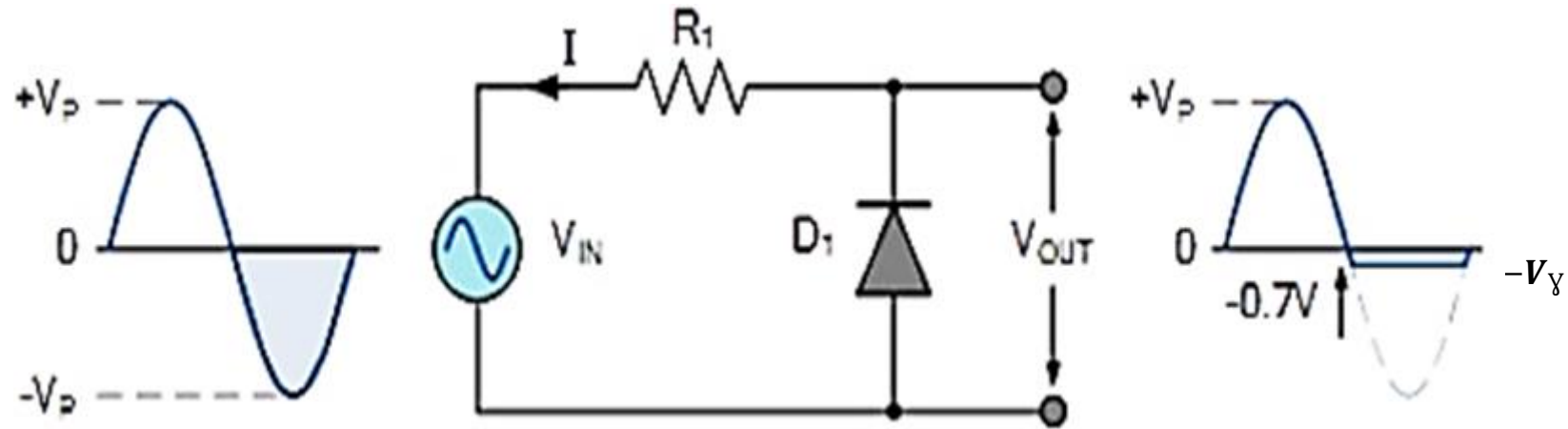

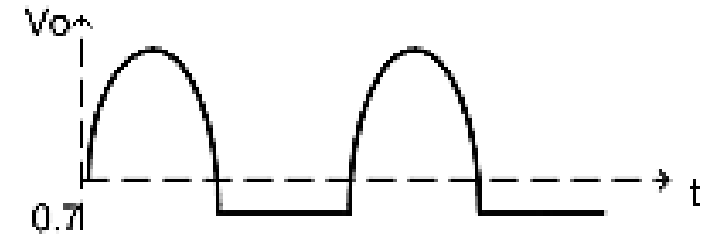- $V_s > -V_Y \rightarrow D \text{ is FF} \rightarrow V_o = V_s$
- $V_s < -V_Y \rightarrow D \text{ is ON} \rightarrow V_o = -V_Y$





Output Waveform

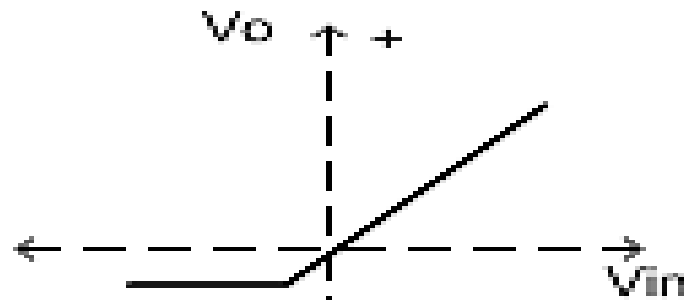


Transfer characteristics

Clipping

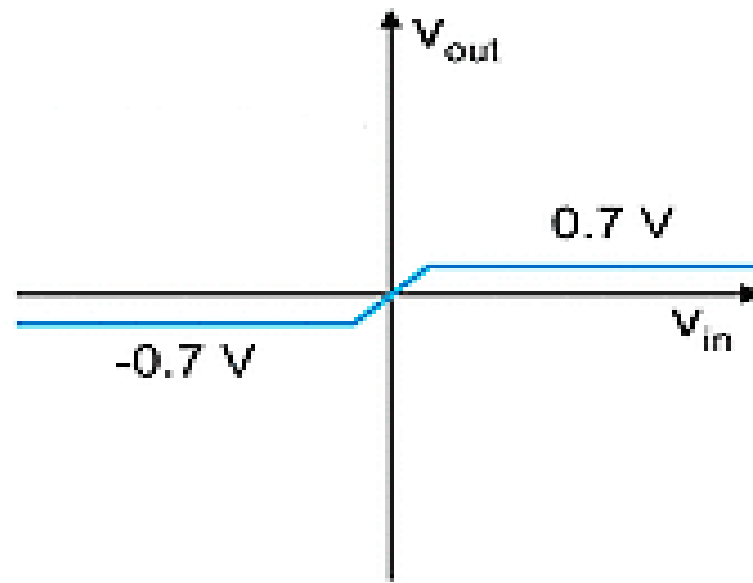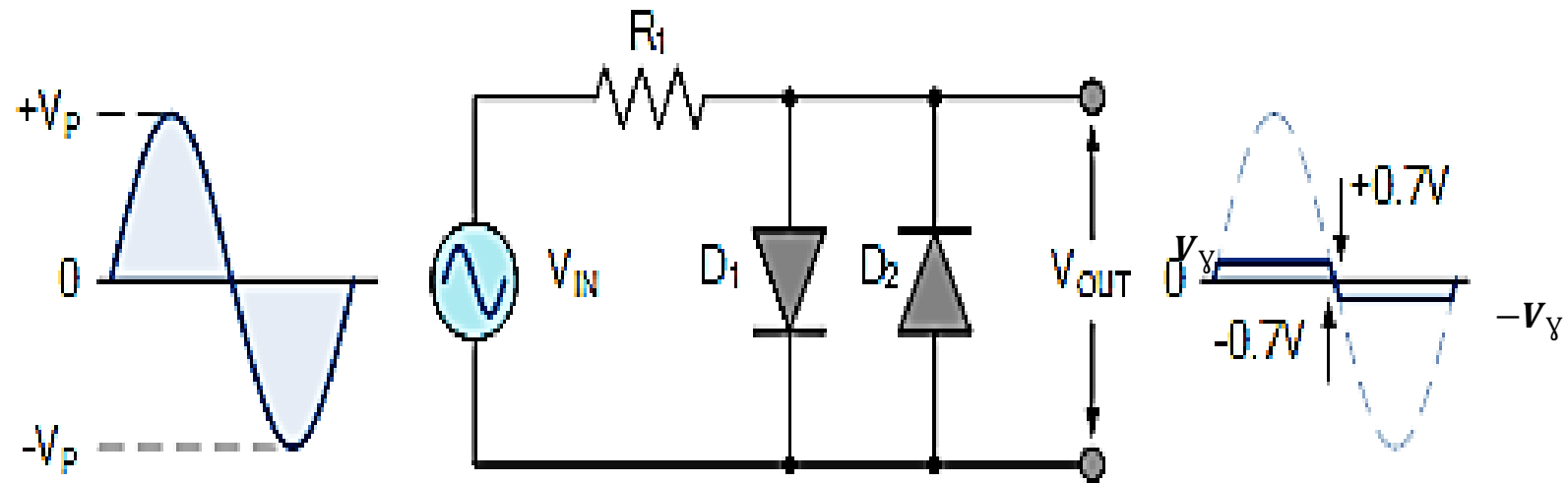


Transfer characteristics

Clipping

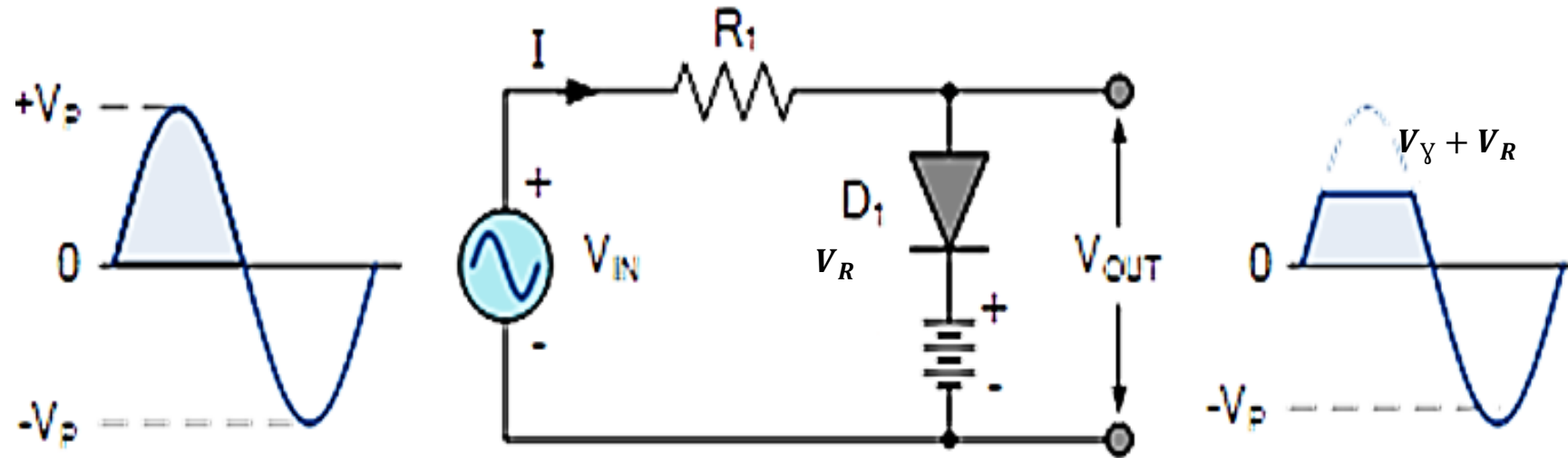



- $V_S > V_Y + V_R \rightarrow D \text{ ON} \rightarrow V_O = V_Y + V_R$
- $V_S < V_Y + V_R \rightarrow D \text{ OFF} \rightarrow V_O = V_S$

Clipping

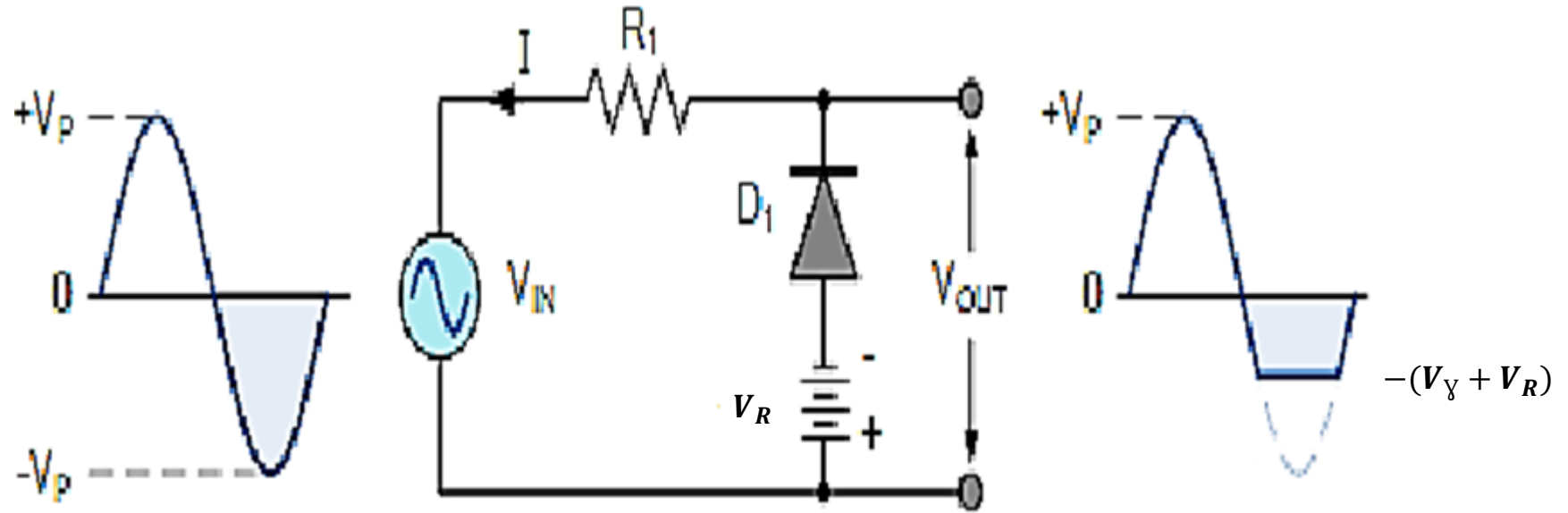


- $V_S < -(V_Y + V_R) \rightarrow D \text{ ON} \rightarrow V_O = -(V_Y + V_R)$
- $V_S > -(V_Y + V_R) \rightarrow D \text{ OFF} \rightarrow V_O = V_S$

Clipping

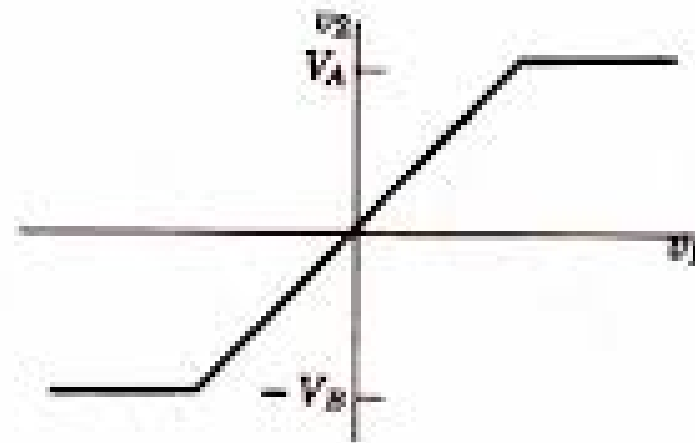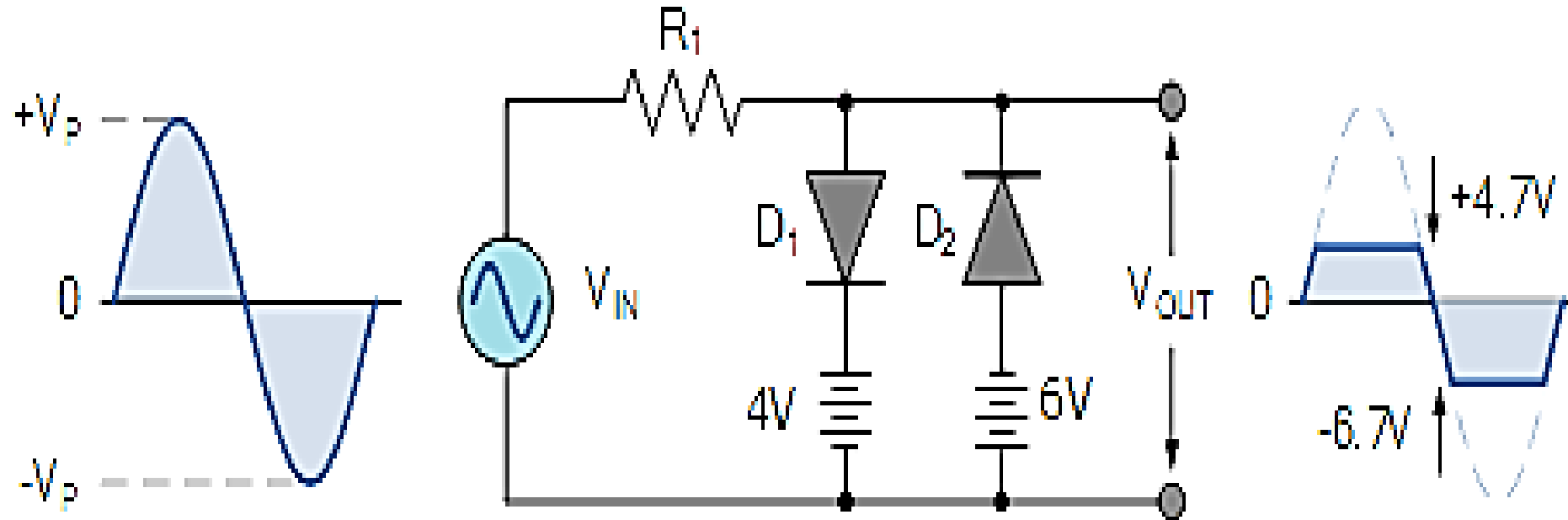


Transfer characteristics


Clipping

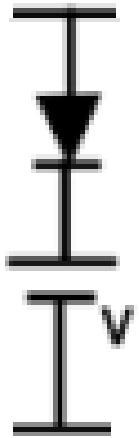


$$V_Y + V$$

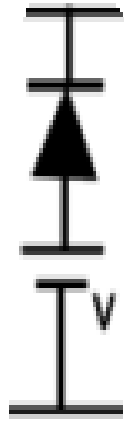

$$-V_Y + V$$



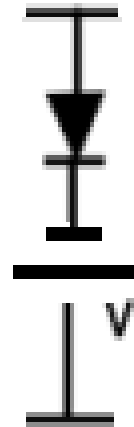


$$V_Y - V$$

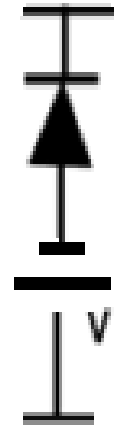

$$-V_Y - V$$

Clipping

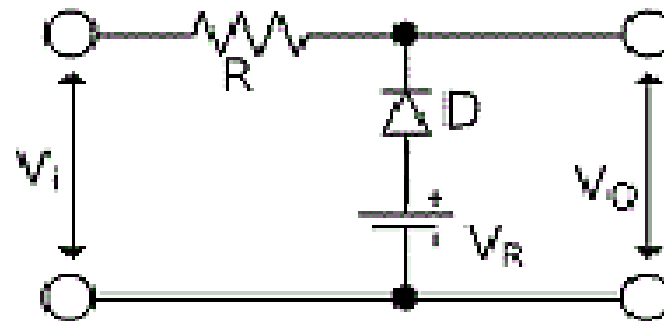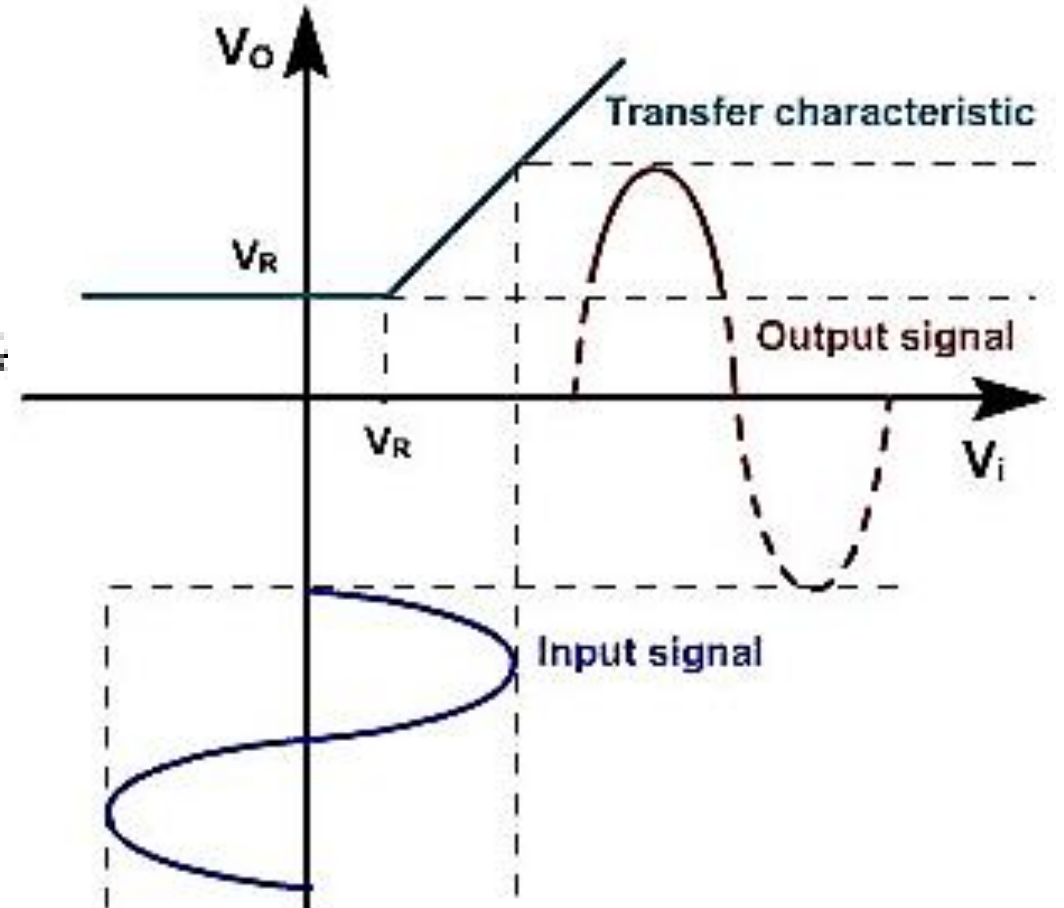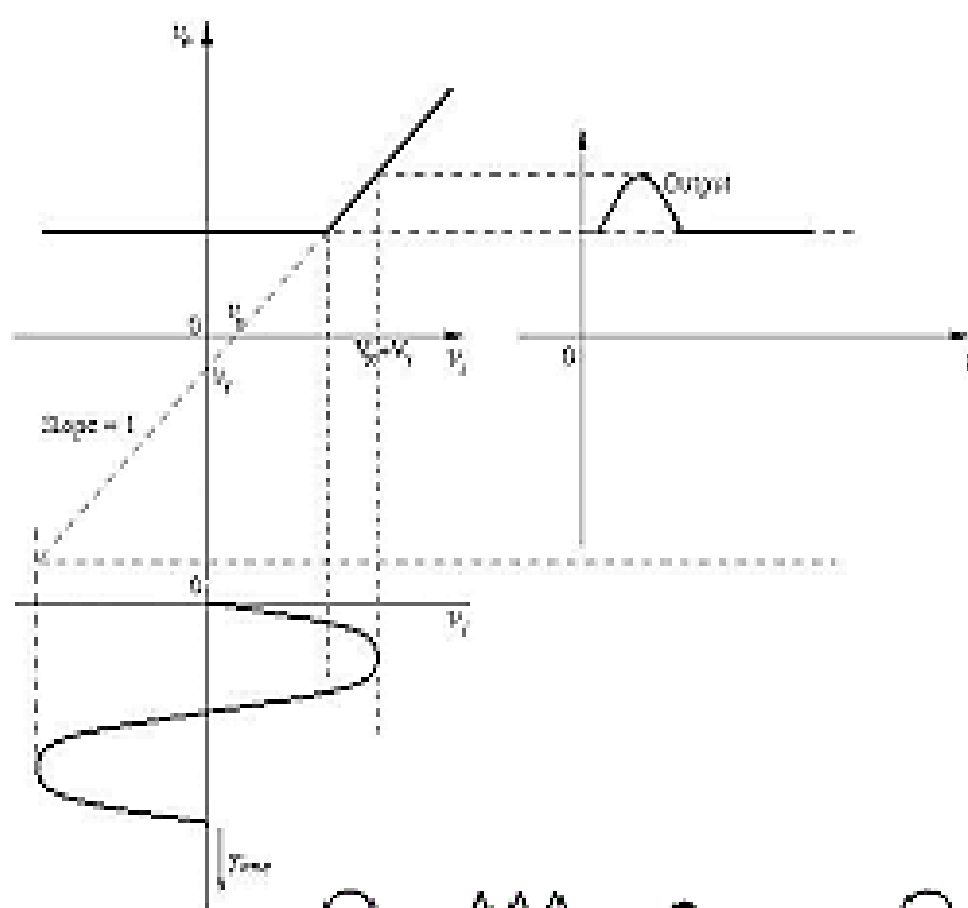

Diode Applications


- Rectifying
- Clipping
- **Clamping**

Clamping


- Shift the entire signal voltage by a DC voltage level.

- **Application:**

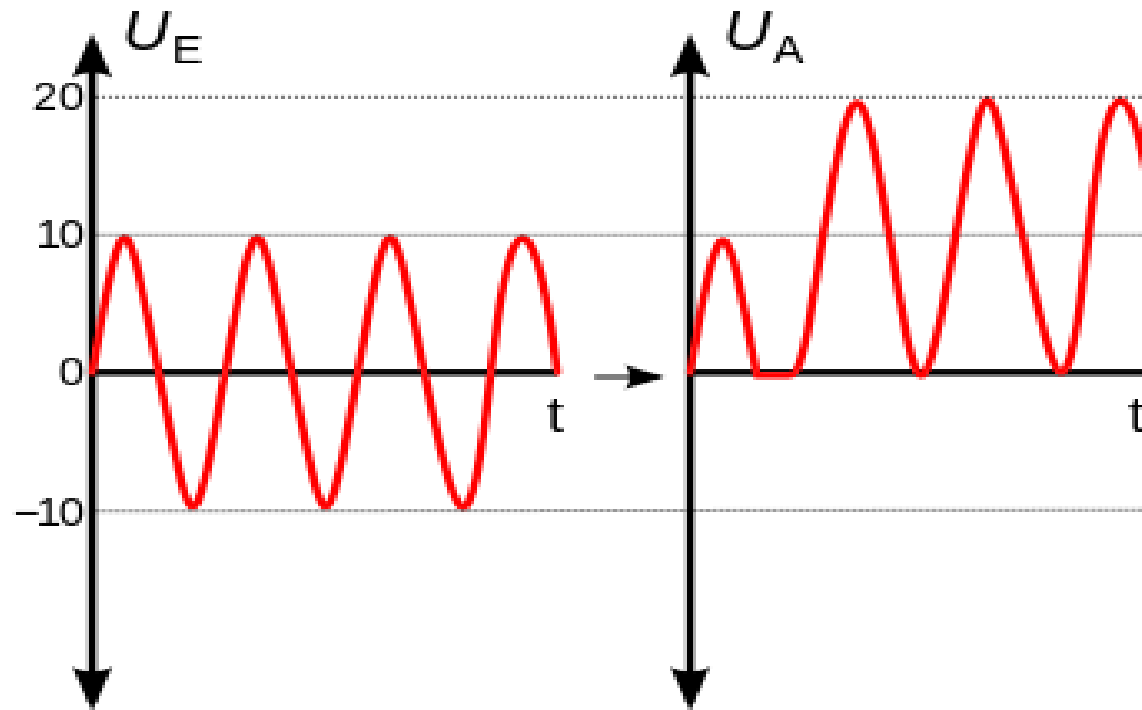Restoring lost DC level in signal from transmission (e.g. Television signal)




Clamping

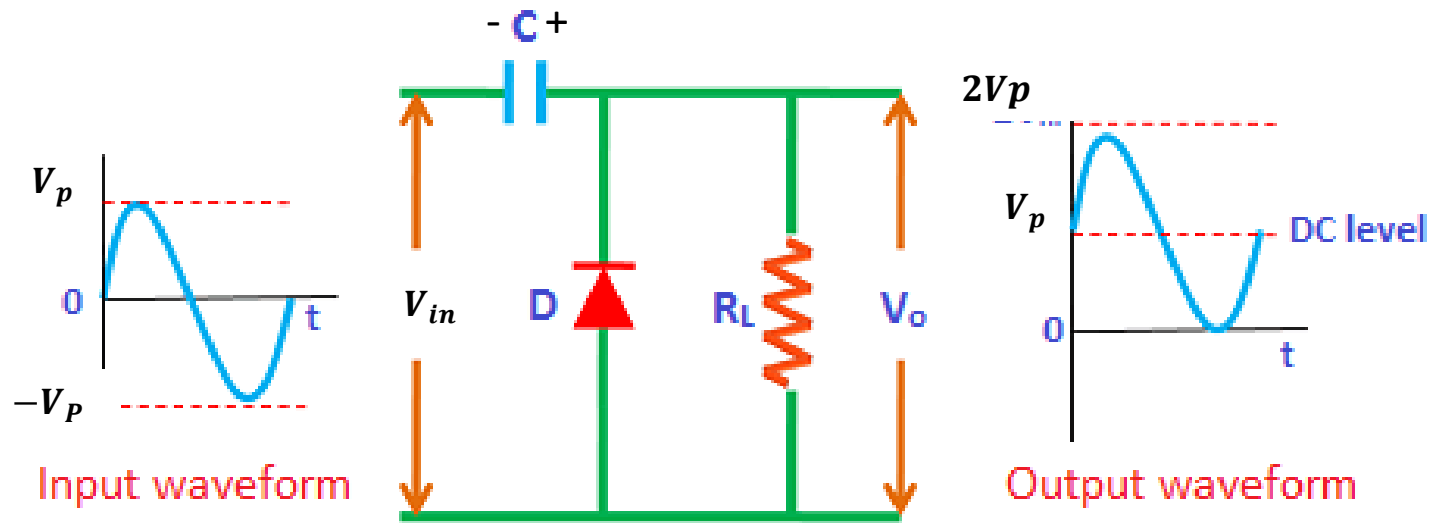


(Negative half cycle) D ON “ short circuit” $\rightarrow V_c = V_p$

(positive half cycle) D OFF “ open circuit” $\rightarrow V_o = V_{in} + V_c$

$$V_o = V_{in} + V_p$$

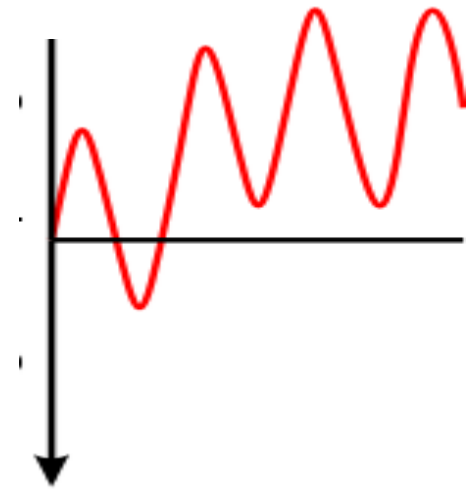


Clamping

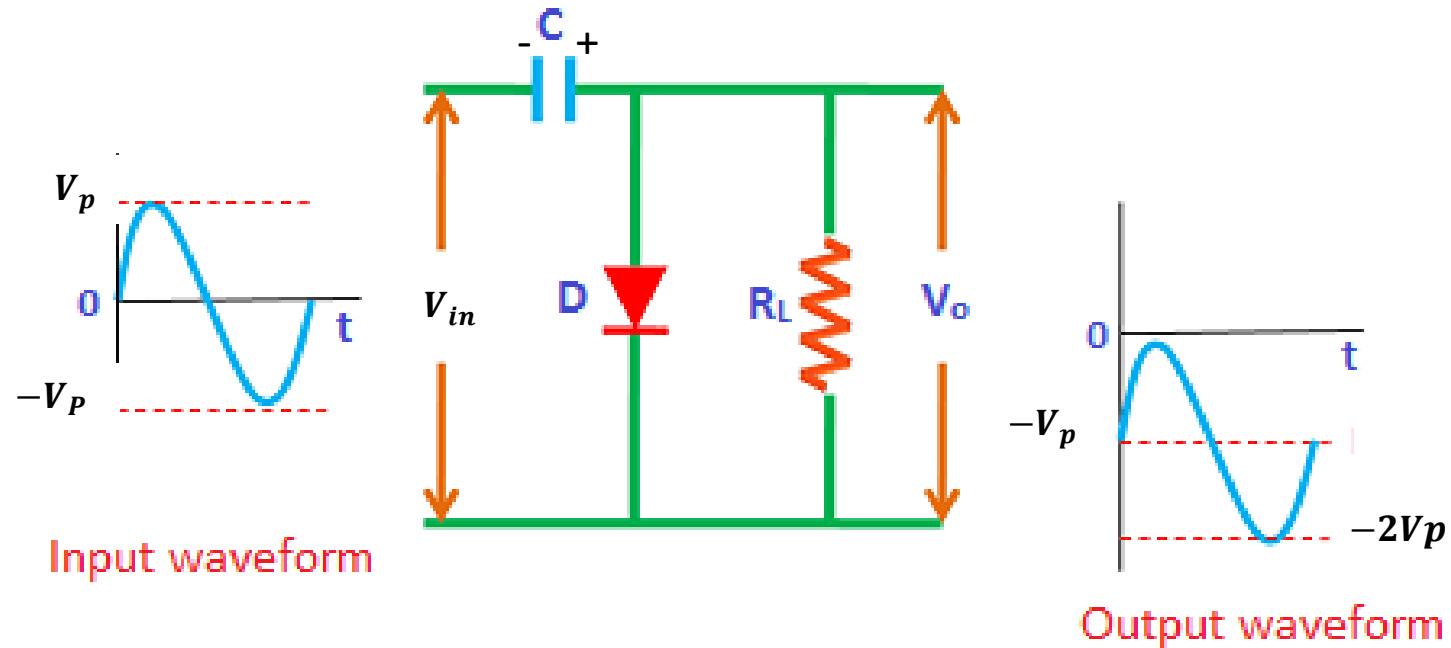

(Positive half cycle) D ON “short circuit” $\rightarrow V_c = -V_p$

(Negative half cycle) D OFF “open circuit” $\rightarrow V_o = V_{in} + V_c \rightarrow V_o = V_{in} - V_p$

Clamping

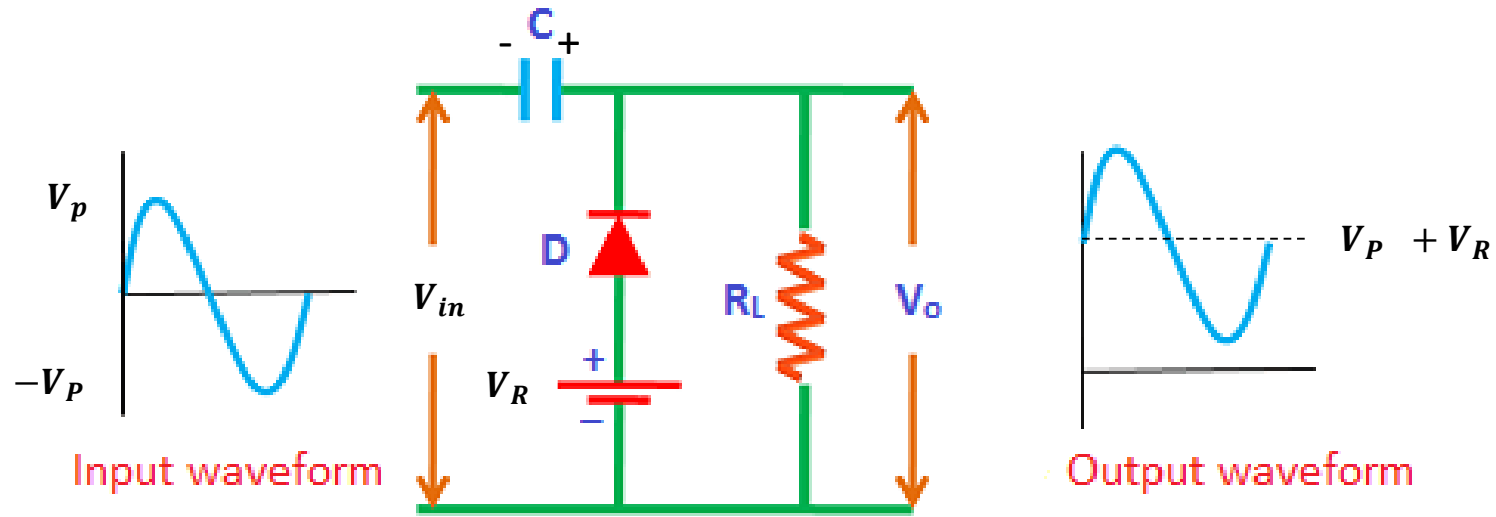


$$V_c = V_p + V_R$$

$$V_o = V_{in} + V_c$$

$$V_o = V_{in} + V_p + V_R$$

Clamping

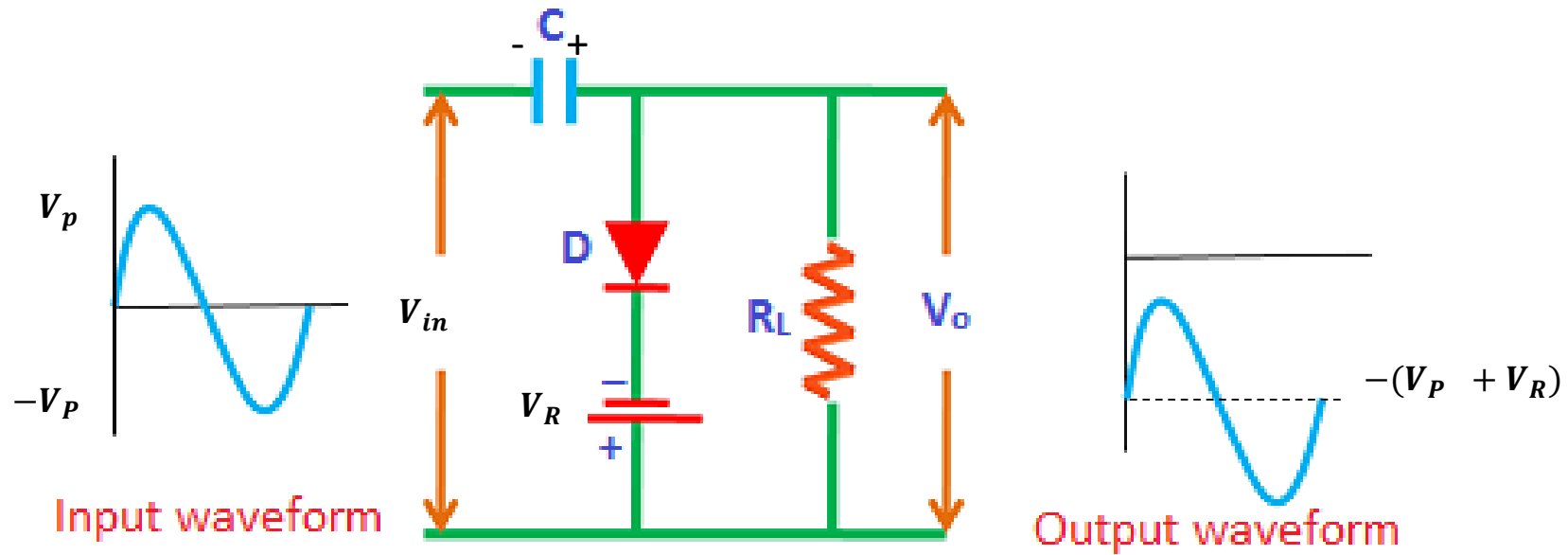


$$V_c = -(V_p + V_R)$$

$$V_o = V_{in} + V_c$$



$$V_o = V_{in} - (V_p + V_R)$$

Clamping

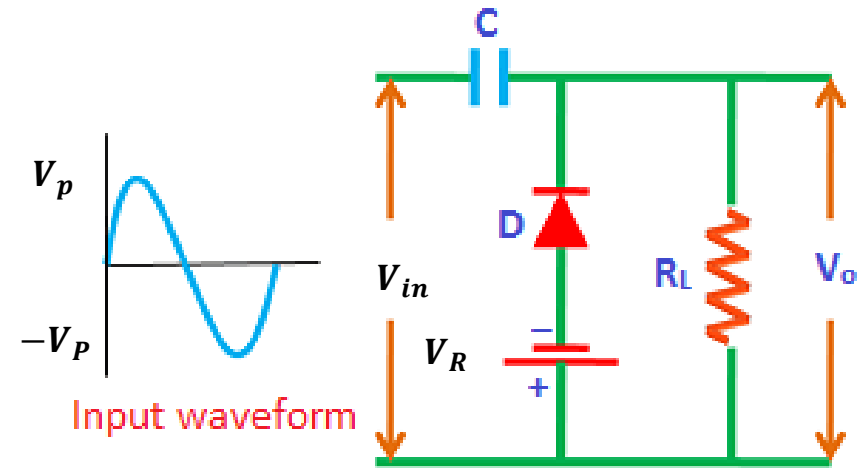

$$V_c = V_p - V_R$$

$$V_o = V_{in} + (V_p - V_R)$$

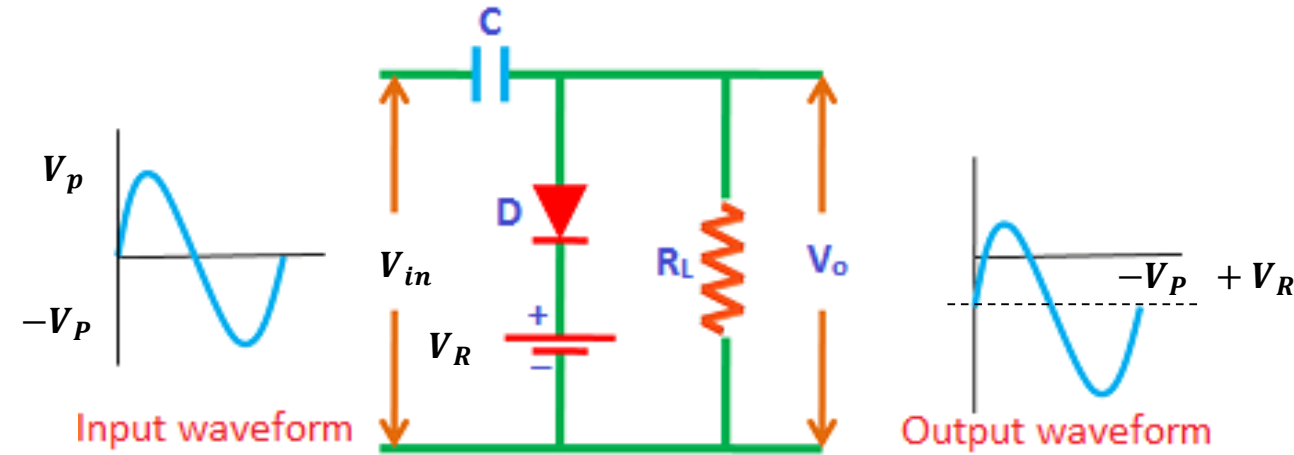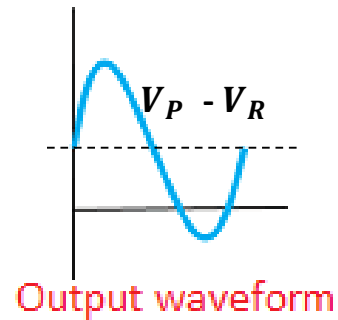

$$V_c = -V_p + V_R$$

$$V_o = V_{in} + (-V_p + V_R)$$