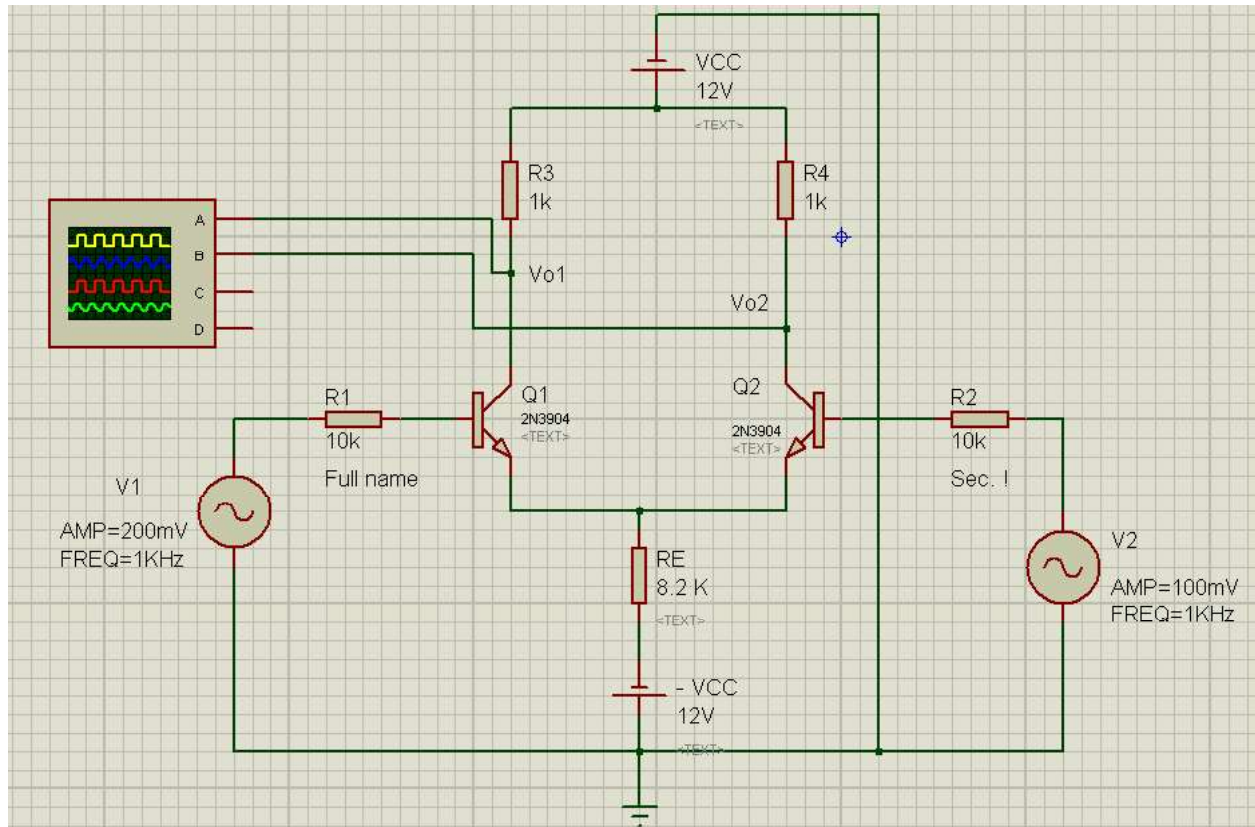


## Exp. 2 (Analog) – Differential Amplifier



### Steps:

- 1- Implement the circuit as the figure.
- 2- Add your full name to R1 text, and Sec. to R2 text (without delete the description), and change the style to COMPONENT ID.
- 3- Get  $I_{C1}$ ,  $I_{E1}$ ,  $I_{B1}$  with Ammeter. Then calculate  $\beta$ ,  $r_e$ ,  $g_m$  and fill Table 1.
- 4- Fix V1 at 200mV and fill Table 2 ( Vo1 and Vo2 ) at the three modes of the Differential Amplifier:
  - a- Double input mode by putting V2 at 100mV (lick the figure).
  - b- Single input mode by deleting V2 source and connect R2 to the ground.
  - c- Common input mode by connecting R2 to V1 (the same source for 2 input).

- 5- Right click oscilloscope figure and chose Digital oscilloscope. Put all oscilloscope's channels Off except Ch. B to calculate Vo2. Then change Ch. A to be AC and calculate Vo1 (Important order).
- 6- Take 3 screen for the Oscilloscope results at the three modes. Then print them in 1 page, and don't present results without your name (it's really dangerous).
- 7- Calculate  $Av_{dm}$ ,  $Av_{cm}$ , and  $CMRR$  and compare it with simulation results.

DC Analysis	$I_{C1}$	$I_{E1}$	$I_{B1}$	$\beta$	$r_e = \frac{V_T}{I_E}$	$g_m = \frac{I_C}{V_T}$
Simulation						
Measurements						

Table 1

V1	V2	Vo1	Vo2	$Av = \frac{Vo1}{V1-V2}$
200mV	100mV			$Av_{dm} = \dots\dots\dots$
200mV	0			$Av_{dm} = \dots\dots\dots$
The same source (200mV)				$Av_{cm} = \dots\dots\dots$

Table 2

$$r_{\pi} = \frac{V_T}{I_B} = \dots\dots\dots, \quad r_{ie} = \frac{R_B + r_{\pi}}{1 + \beta} + r_e = \dots\dots\dots$$

$$Av_{dm} = \frac{-R_c}{r_{ie}} = \dots\dots\dots, \quad Av_{cm} = \frac{-R_c}{2R_E} = \dots\dots\dots$$

$$CMRR = \frac{Av_{dm}}{Av_{cm}} = \dots\dots\dots, \dots\dots\dots$$