
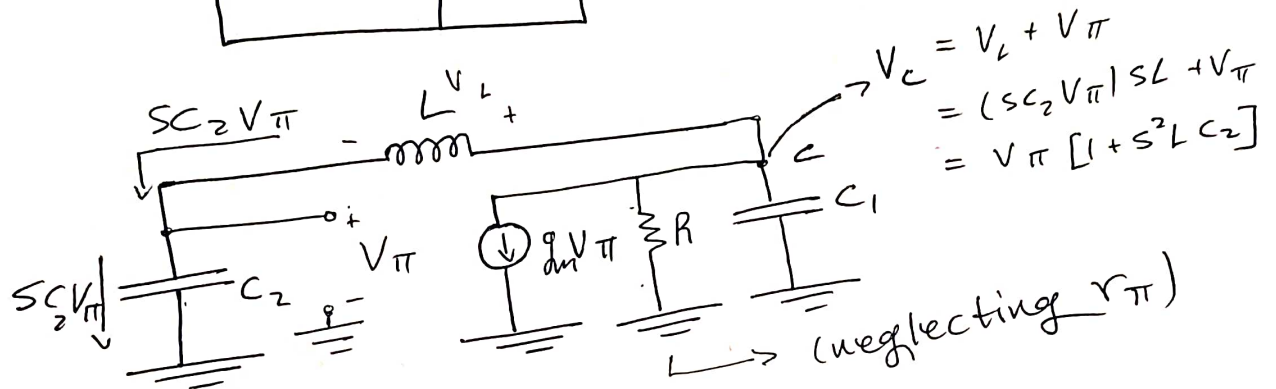


LC oscillators:

9

1- Colpitts oscillator :

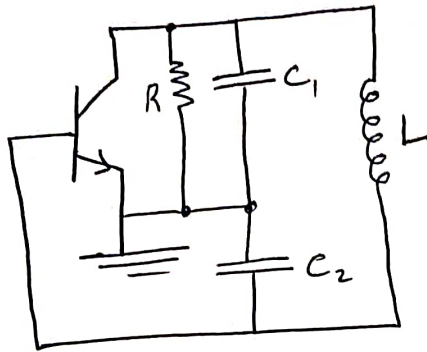

* KCL at node C :

$$g_m V_{\pi} + \frac{V_c}{R} + \frac{V_c}{\left(\frac{1}{sC_1}\right)} + sC_2 V_{\pi} = 0$$

$$\Rightarrow g_m V_{\pi} + \frac{V_{\pi}}{R} (1 + s^2 LC_2) \left(\frac{1}{R} + sC_1\right) + sC_2 V_{\pi} = 0$$

$$\Rightarrow g_m + sC_2 + \frac{1}{R} + sC_1 + s^2 \frac{LC_2}{R} + s^3 LC_1 C_2 = 0$$


($s = j\omega$) :

$$\Rightarrow \left(g_m + \frac{1}{R} - \frac{\omega^2 LC_2}{R}\right) + j \left[\omega C_2 + \omega C_1 - \omega^3 LC_1 C_2\right] = 0$$

$$\begin{aligned} \hookrightarrow g_m + \frac{1}{R} &= \frac{\omega^2 LC_2}{R} \\ \Rightarrow g_m R + 1 &= \left(\frac{C_1 + C_2}{LC_1 C_2}\right) (LC_2) \\ \Rightarrow g_m R &= \frac{C_1 + C_2}{C_1} - 1 = \frac{C_2}{C_1} \Rightarrow \boxed{g_m R = \frac{C_2}{C_1}} \rightarrow \text{oscillation condition} \end{aligned}$$

$$\begin{aligned} \hookrightarrow \omega(C_1 + C_2) &= \omega^3 LC_1 C_2 \\ \Rightarrow \omega_o^2 &= \frac{C_1 + C_2}{LC_1 C_2} \\ \Rightarrow \omega_o &= \sqrt{\frac{C_1 + C_2}{LC_1 C_2}} \rightarrow \text{frequency of oscillation} \end{aligned}$$

2- Hartley oscillator :

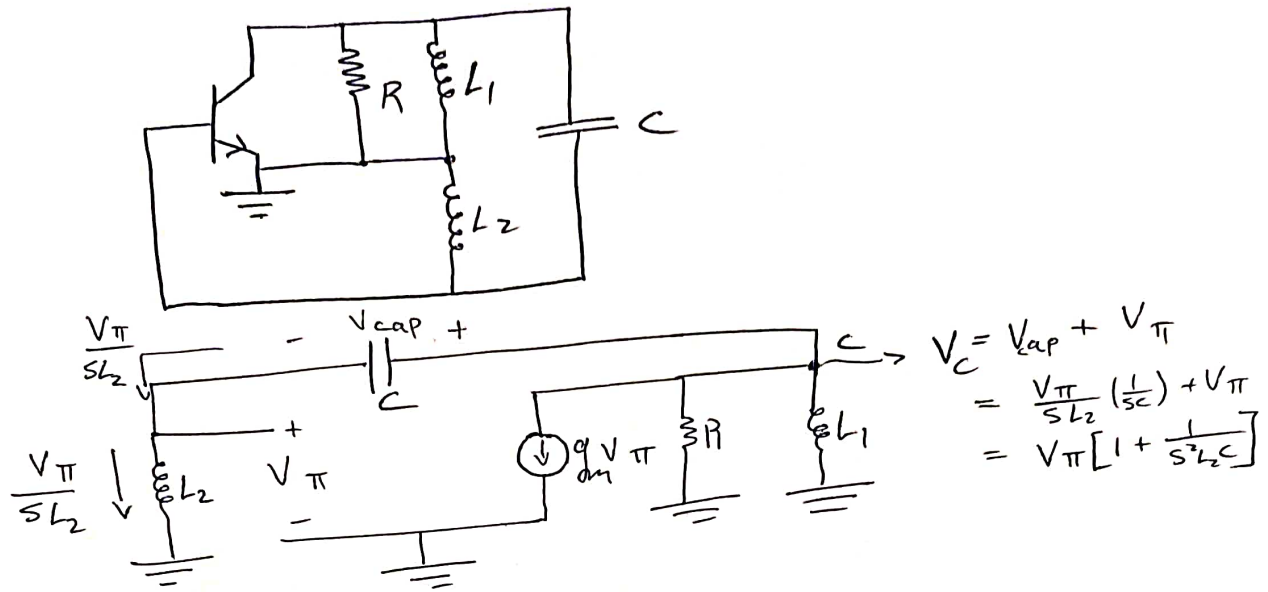

* KCL at node C :

$$\Rightarrow g_m V_\pi + V_\pi \left[1 + \frac{1}{s^2 L_2 C} \right] \left[\frac{1}{R} + \frac{1}{sL_1} \right] + \frac{V_\pi}{sL_2} = 0$$

$$\Rightarrow g_m + \frac{1}{R} + \frac{1}{sL_1} + \frac{1}{s^2 RL_2 C} + \frac{1}{sL_1 L_2 C} + \frac{1}{sL_2} = 0$$

$$\Rightarrow (s = j\omega) :$$

$$\Rightarrow \left[g_m + \frac{1}{R} - \frac{1}{\omega^2 RL_2 C} \right] + j \left[-\frac{1}{\omega L_1} - \frac{1}{\omega L_2} + \frac{1}{\omega^3 L_1 L_2 C} \right] = 0$$

$$\Rightarrow g_m + \frac{1}{R} = \frac{1}{\omega_o^2 RL_2 C}$$

$$\Rightarrow \frac{1}{\omega_o L_1} + \frac{1}{\omega_o L_2} = \frac{1}{\omega_o^3 L_1 L_2 C}$$

$$\Rightarrow \omega_o^2 \left[\frac{1}{L_1} + \frac{1}{L_2} \right] = \frac{1}{L_1 L_2 C}$$

$$\Rightarrow \omega_o^2 [L_2 + L_1] = \frac{1}{C}$$


$$\Rightarrow \omega_o = \sqrt{\frac{1}{C(L_1 + L_2)}}$$

$$\Rightarrow g_m R + 1 = \frac{C(L_1 + L_2)}{L_2 C}$$

$$\Rightarrow g_m R = \frac{L_1 + L_2 - L_2}{L_2}$$

$$\Rightarrow \boxed{g_m R = \frac{L_1}{L_2}}$$

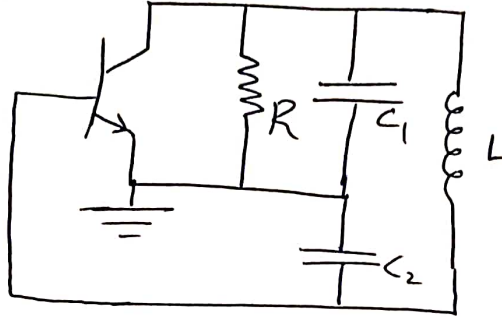Ex: using a BJT biased at $I_C = 1\text{mA}$, design 3
 a Colpitts oscillator to operate at $\omega_0 = 10^6 \text{ rad/s}$
 use $C_1 = 0.01 \mu\text{F}$, $R = 2 \text{ k}\Omega$.



Sol :

$$\therefore g_m = \frac{I_C}{V_T} = \frac{1\text{mA}}{0.025} = 40 \text{ mS}$$

$$\Rightarrow \omega_0 = \sqrt{\frac{C_1 + C_2}{LC_1C_2}}$$

$$\Rightarrow L = \frac{C_1 + C_2}{\omega_0^2 C_1 C_2}$$


$$\Rightarrow g_m R = \frac{C_2}{C_1}$$

$$\Rightarrow C_2 = (40 \times 10^{-3}) (2 \times 10^3) (0.01 \times 10^{-6}) = 0.4 \mu\text{F}$$

$$\Rightarrow L = \frac{(0.01 + 0.4) \times 10^{-6}}{(10^6)^2 (0.01 \times 10^{-6}) (0.4 \times 10^{-6})} =$$


Q₁: For each of the given colpitts oscillator circuits. derive an equation governing the circuit operation, find the frequency of oscillation & the gain condition that ensures that oscillation will start. 4

a)

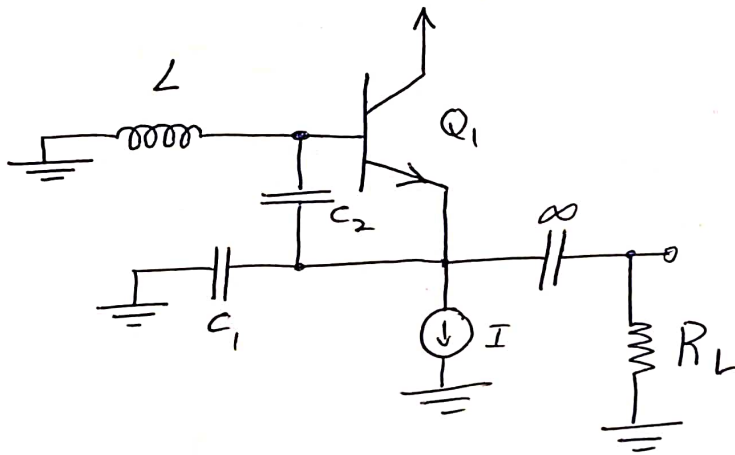

Sol:

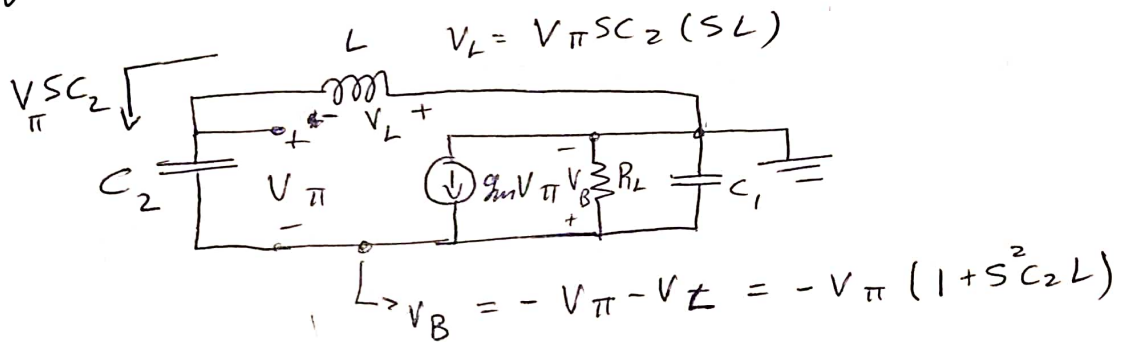- small signal model: (assuming large r_{π})



- KCL at node B:

$$V_{\pi} SC_2 + g_m V_{\pi} + \frac{(-V_B)}{R} + \frac{(-V_B)}{(\frac{1}{SC_1})} = 0$$

$$\Rightarrow V_{\pi} SC_2 + g_m V_{\pi} + V_{\pi} (1 + S^2 C_2 L) \left(\frac{1}{R} + SC_1 \right) = 0$$

$$\Rightarrow SC_2 + g_m + \frac{1}{R} + SC_1 + \frac{S^2 C_2 L}{R} + S^3 C_1 C_2 L = 0$$



$$\Rightarrow \left(g_m + \frac{1}{R} - \frac{\omega^2 C_2 L}{R} \right) + j \left[\omega (C_1 + C_2) - \omega^3 C_1 C_2 L \right] = 0$$

$$\Rightarrow g_m + \frac{1}{R} - \frac{\omega^2 C_2 L}{R} = 0 \quad \Rightarrow \omega_0 = \sqrt{\frac{C_1 + C_2}{LC_1 C_2}}$$

$$\Rightarrow g_m R = \frac{C_2}{C_1}$$

b)

[5]

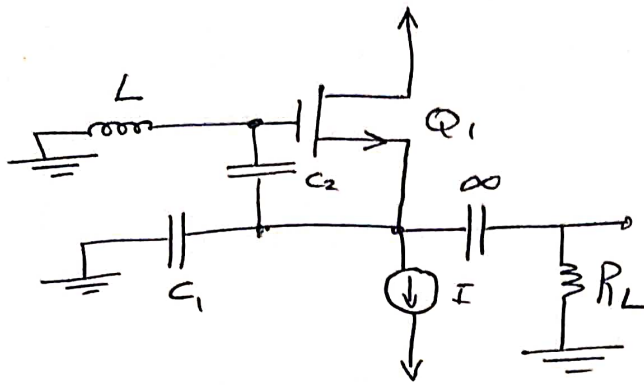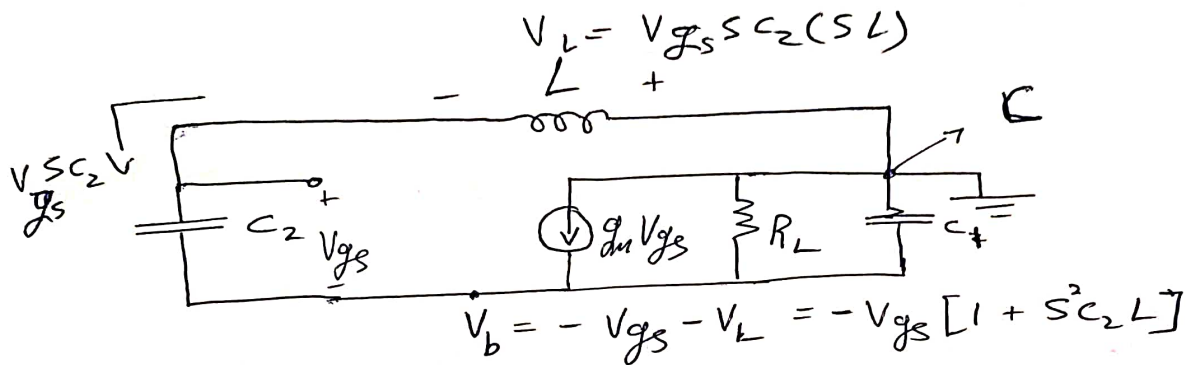SoP:

- KCL at node C :

$$\Rightarrow V_{gs} s C_2 + g_m V_{gs} + \left[\frac{0 - V_b}{R_L} \right] + \left[\frac{0 - V_b}{\frac{1}{s C_1}} \right] = 0$$

$$\Rightarrow \cancel{V_{gs}} s C_2 + g_m \cancel{V_{gs}} + \cancel{V_{gs}} [1 + s^2 C_2 L] \left[\frac{1}{R_L} + s C_1 \right] = 0$$

$$\Rightarrow s C_2 + g_m + \frac{1}{R_L} + s C_1 + \frac{s^2 C_2 L}{R_L} + s^3 C_1 C_2 L = 0$$

 $s = j\omega$:

$$\Rightarrow \left[g_m + \frac{1}{R_L} - \frac{\omega^2 C_2 L}{R_L} \right] + j \left[\omega C_1 + C_2 - \omega^3 C_1 C_2 L \right] = 0$$

$$\hookrightarrow \boxed{g_m R_L = \frac{C_2}{C_1}}$$


$$\hookrightarrow \cancel{\omega_0} (C_1 + C_2) - \cancel{\omega_0}^3 C_1 C_2 L = 0$$

$$\Rightarrow \boxed{\omega_0 = \sqrt{\frac{C_1 + C_2}{L C_1 C_2}}}$$

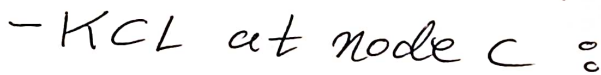9)



[assuming $r_{\pi} \gg$ negligible in parallel connection)]




$$\Rightarrow g_m + \frac{1}{R_L} + \frac{s^2 L C_1}{R_L} + s C_2 + s C_1 + s^3 L C_1 C_2 = 0$$

$$\Rightarrow \underbrace{g_m + \frac{1}{R_L} - \frac{\omega^2 L C_1}{R_L}}_{=0} + j \underbrace{\left[\omega (C_1 + C_2) - \omega^3 L C_1 C_2 \right]}_{=0} = 0$$

$$\Rightarrow Z_{R_L} = \frac{C_2}{C_1}$$

$$\text{sub. } \omega_0 = \sqrt{\frac{C_1 + C_2}{LC_1 C_2}}$$


d)

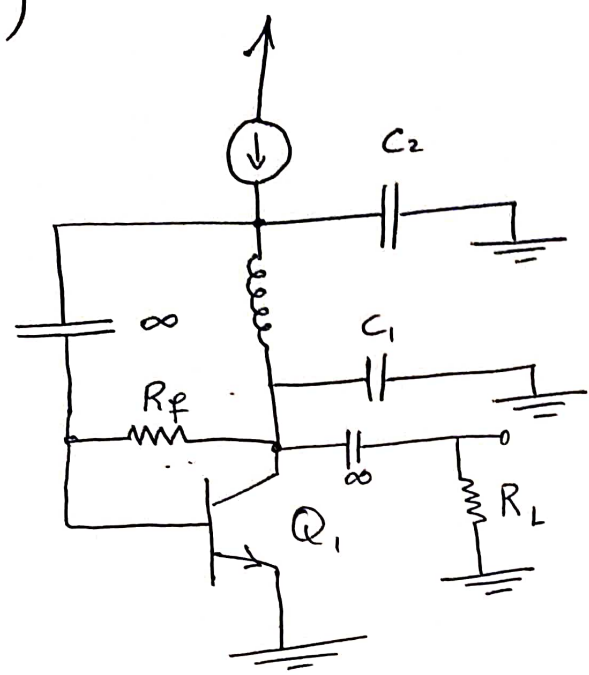

(Assume $R_f \gg \omega_0 L$)

Sol:

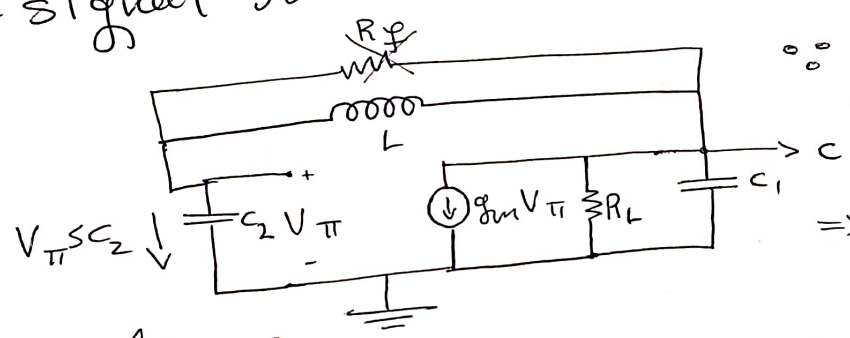- small-signal Model : (assuming $r_{\pi} \gg$)



$\because R_f \gg \omega_0 L$
 $\Rightarrow (R_f // \omega_0 L) \approx \omega_0 L$
 $\Rightarrow V_c = V_{\pi} + V_{\pi} s C_2 (s L)$

- KCL at node c :

$$\Rightarrow g_m V_{\pi} + V_{\pi} [1 + s^2 C_2 L] \left[\frac{1}{R_L} + s C_1 \right] + V_{\pi} s C_2 = 0$$

at $s = j\omega$

$$\Rightarrow g_m + \frac{1}{R_L} + s C_1 + \frac{s^2 C_2 L}{R_L} + s^3 C_1 C_2 L + s C_2 = 0$$


$$\Rightarrow g_m + \frac{1}{R_L} - \frac{\omega^2 C_2 L}{R_L} + j \left[\omega (C_1 + C_2) - \omega^3 C_1 C_2 L \right] = 0$$

$\Rightarrow \boxed{g_m R_L = \frac{C_2}{C_1}}$

$L \gg \omega_0^2 (C_1 + C_2) - \omega_0^3 C_1 C_2 L = 0$
 $\Rightarrow \boxed{\omega_0 = \sqrt{\frac{C_1 + C_2}{L C_1 C_2}}}$

Q2 consider the oscillator ct. & assume that $\beta = \infty$ for simplicity.


8

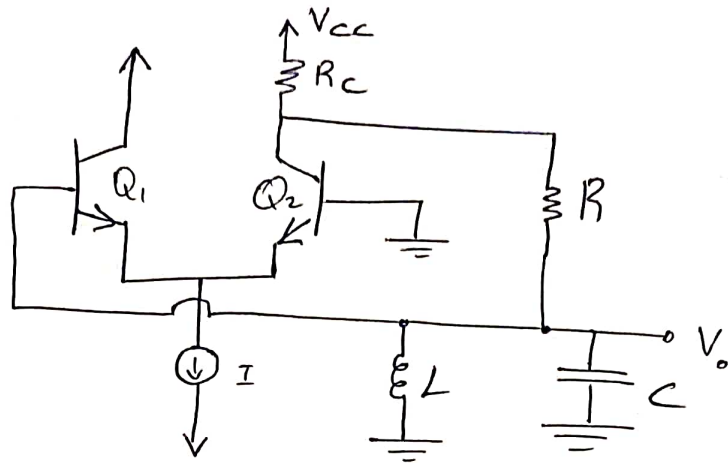

a) Find the frequency of oscillation & min. value of R_C (in terms of bias current I) for oscillation to start.

sof

* Feedback network:

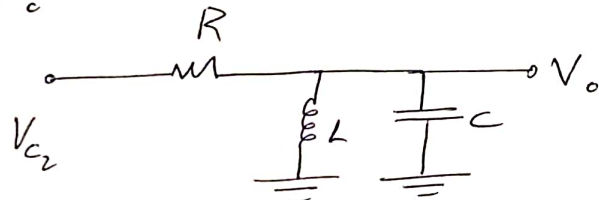

$$\Rightarrow V_0 = V_{c2} \frac{(sL \parallel \frac{1}{sC})}{R + (sL \parallel \frac{1}{sC})}$$

$$\Rightarrow B = \frac{V_0}{V_{c2}} = \frac{\frac{sL(\frac{1}{sC})}{sL + \frac{1}{sC}}}{R + \frac{sL(\frac{1}{sC})}{sL + \frac{1}{sC}}} = \frac{L/C}{R(sL + \frac{1}{sC}) + \frac{L}{C}}$$

imaginary $\rightarrow 0$


$$\omega_0 L - \frac{1}{\omega_0 C} = 0$$

$$\boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$$

* Gain (open-loop):

$$\Rightarrow A = \frac{V_{c2}}{V_{in}}$$
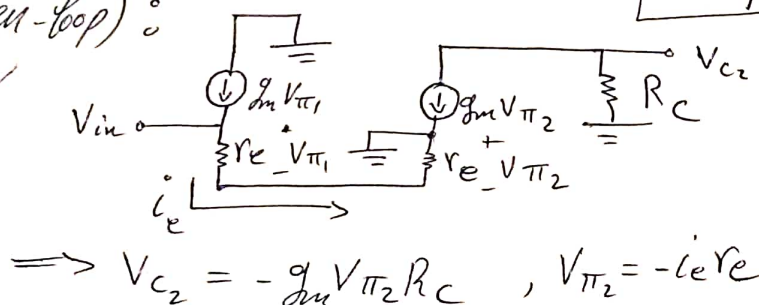
$$\Rightarrow i_e = \frac{V_{in}}{2r_e}$$



$$\Rightarrow V_{c2} = -g_m V_{\pi 2} R_C, \quad V_{\pi 2} = -i_e r_e$$

$$\therefore i_e = \frac{v_{in}}{2r_e}$$

$$\Rightarrow V_{c_2} = g_m R_c \cancel{r_e} \left(\frac{v_{in}}{\cancel{2r_e}} \right)$$

$$\Rightarrow A = \frac{V_{c_2}}{v_{in}} = \frac{g_m R_c}{2}$$

$$\Rightarrow |AB| = 1 \quad (\text{Magnitude condition})$$

at $\omega = \omega_0$

$$\Rightarrow \beta = \frac{(\frac{1}{2})}{(\frac{1}{2})} = 1$$

$$\Rightarrow \frac{g_m R_c}{2} = 1, \quad \therefore g_m = \frac{I_c}{V_T}, \quad I_c = \frac{I}{2}$$

$$= \frac{I}{2V_T}$$

$$\Rightarrow \frac{I R_c}{4 V_T} \geq 1$$

$$\Rightarrow R_c \geq \frac{4 V_T}{I}, \quad V_T = 0.025$$

$$\Rightarrow \boxed{R_c \geq \frac{0.1}{I}}$$

b) If $R_c = (\frac{4}{I}) \text{ k}\Omega$, prove that oscillations will start. if oscillations grow to pt. that V_0 is large enough. to turn BJTs on & off, show that the voltage at the collector of Q_2 will be a square wave of 1 V peak to peak.

solⁿ

$$\text{at } R_c = \frac{1}{I} \Rightarrow A = \frac{I R_c}{4(0.025)} = \frac{(1)(\frac{1}{I})}{0.1} = \underline{\underline{10}}$$

$$\Rightarrow AB = 10 \text{ at } \omega_0 \Rightarrow AB \gg 1$$

\Rightarrow oscillation will start

for large V_o :

$$\begin{aligned} \text{at } V_o \uparrow &\Rightarrow Q_1 \text{ has } I_{C1} = I, \text{ \& } I_{C2} = 0 \\ &\Rightarrow Q_2 \rightarrow \text{cutt-off} \\ &\Rightarrow V_{C2} = V_{CC} \end{aligned}$$

$$\text{at } V_o \downarrow \Rightarrow Q_1 \text{ has } I_{C1} = 0 \Rightarrow I_{C2} = I$$

$$\Rightarrow Q_2 \rightarrow \text{Max current}$$

$$\Rightarrow V_{C2} = V_{CC} - I R_C$$

$$= V_{CC} - 1 \quad (\because R_C = \frac{1}{I})$$

$$\Rightarrow V_{PP} = V_{CC} - (V_{CC} - 1) = 1 V_{PP}$$
