

Electronic Systems

Active Filters

Lecture 2

Dr. Roaa Mubarak

1. Inverting Amplifier (Finite-Gain): Closed Loop

Where

A_m = The closed loop maximum gain

A_o = The Open Loop maximum gain

W_c = The Closed Loop Band Width

W_b = The Open Loop Band Width

$$A_m = -\frac{R_2}{R_1} \quad \text{and} \quad W_c = \frac{A_o W_b}{\left(1 + \frac{R_2}{R_1}\right)}$$

Closed Loop Gain-Band width product:

$$\text{GBP(Closed-Loop)} = A_m W_c = \left(\frac{R_2}{R_1}\right) \left(\frac{A_o W_b}{\left(1 + \frac{R_2}{R_1}\right)}\right) = A_o W_b = \text{GBP(Open-Loop)}$$

$$\text{Since } \frac{R_2}{R_1} \gg 1$$

2. Non-Inverting Amplifier (Finite-Gain): Closed Loop

Where

A_m = The closed loop maximum gain

A_o = The Open Loop maximum gain

W_c = The Closed Loop Band Width

W_b = The Open Loop Band Width

$$A_m = 1 + \frac{R_2}{R_1} \quad \text{and} \quad W_c = \frac{A_o W_b}{\left(1 + \frac{R_2}{R_1}\right)}$$

Closed Loop Gain-Band width product:

$$\text{GBP(Closed-Loop)} = A_m W_c = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{A_o W_b}{\left(1 + \frac{R_2}{R_1}\right)} \right) = A_o W_b = \text{GBP(Open-Loop)}$$

Example 1

Analyze the circuit shown in Figure :


- (1) Derive an expression for the closed loop gain ($H(s) = V_o/V_{in}$) in terms of the finite open loop gain (A).
- (2) If the open loop gain is given by:

$$A(S) = \frac{A_o}{1 + \frac{S}{\omega_b}}$$

Where: $A_o = 10^4$, and $\omega_b = 10$ rad/sec.

Derive $H(s)$ and sketch the closed loop frequency response.

- (3) Calculate the Gain-Band-width product (GBP) for open and closed loop cases..

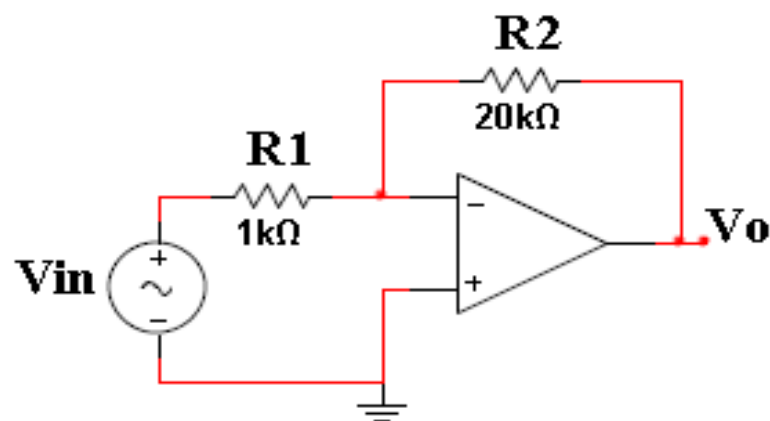


Example 1

$$* V_o = A(V_2 - V_1), V_2 = 0$$

$$\therefore V_o = -A V_1$$
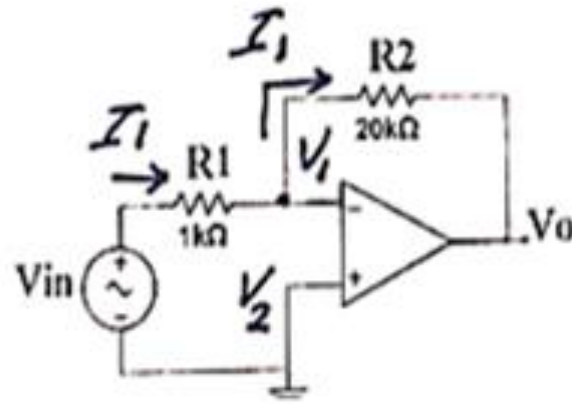
$$\therefore \boxed{V_1 = -\frac{V_o}{A}} \quad [1]$$



$$* I_1 = \frac{V_{in} - V_1}{R_1} = \frac{V_1 - V_o}{R_2}$$

$$\therefore \frac{V_{in}}{R_1} - \frac{V_1}{R_1} = \frac{V_1}{R_2} - \frac{V_o}{R_2} \quad \times R_2$$

$$\frac{R_2}{R_1} V_{in} - \frac{R_2}{R_1} V_1 = V_1 - V_o$$

$$\frac{R_2}{R_1} V_{in} = \left[1 + \frac{R_2}{R_1}\right] V_1 - V_o \quad \text{Sub. From [1]}$$

$$\therefore \frac{R_2}{R_1} V_{in} = \left[1 + \frac{R_2}{R_1}\right] \frac{-V_o}{A} - V_o$$

$$\frac{R_2}{R_1} V_{in} = \left\{ \left[1 + \frac{R_2}{R_1}\right] \frac{1}{A} + 1 \right\} (-V_o)$$

$$\therefore H(s) = \frac{V_o}{V_{in}} = \frac{-\left(\frac{R_2}{R_1}\right)}{1 + \left(\frac{1 + \frac{R_2}{R_1}}{A}\right)}$$

$$\therefore H(s) = \frac{V_o}{V_{in}} = \frac{-\left(\frac{R_2}{R_1}\right)}{1 + \left(\frac{1 + \frac{R_2}{R_1}}{A}\right)}$$

$$H(s) = \frac{-(R_2/R_1)}{1 + \frac{1 + (R_2/R_1)}{A(s)}}$$

Example 1

ii- Derive $H(s)$ and sketch the closed loop frequency response.

$$H(s) = \frac{-(R_2/R_1)}{1 + \frac{1 + R_2/R_1}{\left(\frac{A_o}{1 + \frac{s}{\omega_b}}\right)}} = \frac{-(R_2/R_1)}{1 + \frac{1 + R_2/R_1}{A_o} + \frac{(1 + R_2/R_1)s}{A_o \omega_b}}$$


$$H(s) \cong \frac{-(R_2/R_1)}{1 + \frac{s}{\left(\frac{A_o \omega_b}{1 + \frac{R_2}{R_1}}\right)}} = \frac{-A_m}{1 + \frac{s}{\omega_c}}$$

$$\boxed{A_m = \frac{R_2}{R_1} = 20}$$

$$\omega_c = \frac{A_o \omega_b}{1 + \frac{R_2}{R_1}}$$

$$\boxed{\omega_c = 4761.9 \text{ rad/sec}}$$

$$H(s) \cong \frac{-20}{1 + \frac{s}{4762}}$$

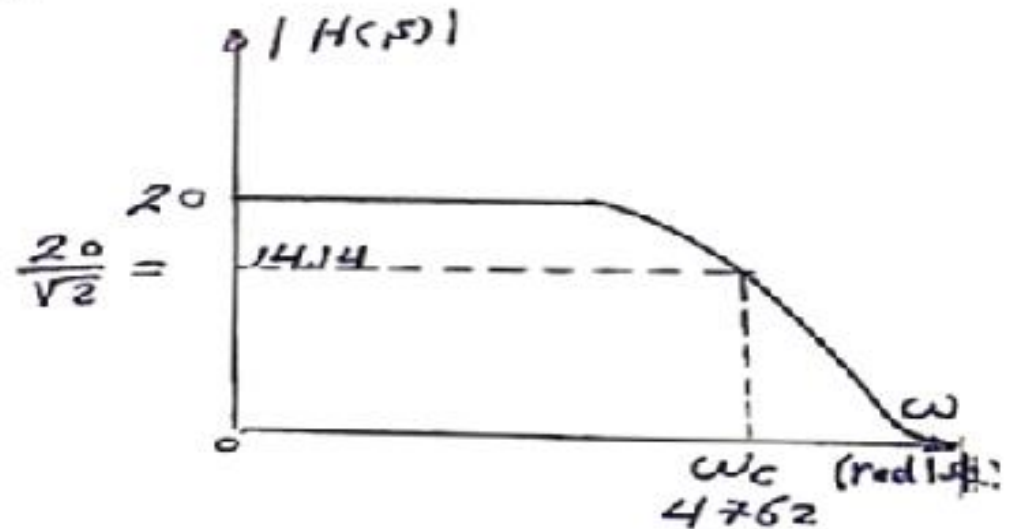

Example 1

iii- Calculate the Gain-Band-width product (GBP) for open and closed loop cases.

- $\text{GBP(Open-Loop)} = A_o \omega_b = 10^5 \text{ rad/sec} = 100000 \text{ rad/Sec}$
- $\text{GBP(Closed-Loop)} = A_m \omega_c = 20 \times 4762 = 95240 \text{ rad/Sec}$

Example 2

(a) Derive an expression for the closed loop gain ($H(s) = V_o/V_{in}$) in terms of the finite open loop gain (A).


(b) If the open loop gain is given by:

$$A(s) = \frac{A_o}{1 + \frac{s}{\omega_b}}$$

Where: $A_o = 10^5$, and $\omega_b = 10$ rad/sec.

Derive $H(s)$ and sketch the closed loop frequency response.

(c) Calculate the Gain-Band-width product(GBP).

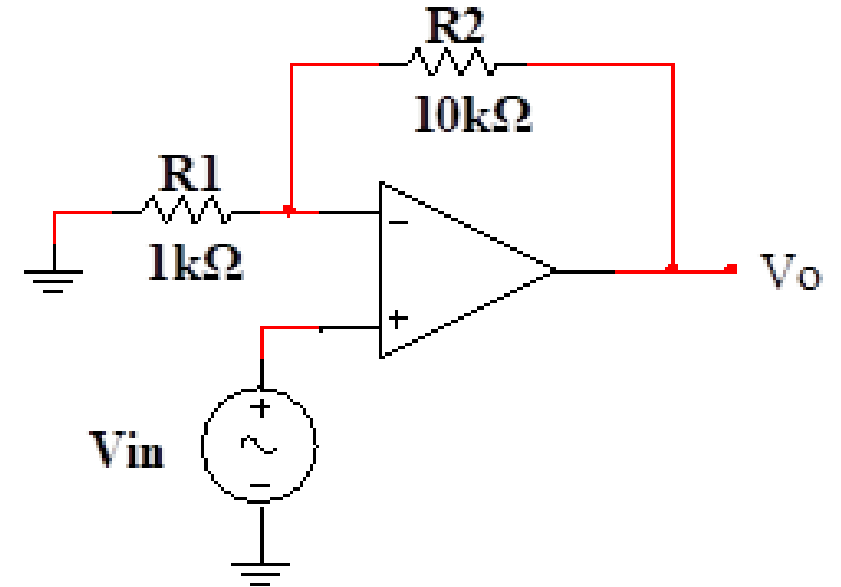

Example 2

(a) Derive an expression for the closed loop gain ($H(s) = V_o/V_{in}$) in terms of the finite open loop gain (A).

$$* V_o = (V_2 - V_1) \cdot A$$

$$V_o = \left[V_{in} - \frac{V_o \cdot R_1}{R_1 + R_2} \right] A$$


$$V_o = A V_{in} - \frac{A R_1}{R_1 + R_2} V_o$$

$$V_o \left[1 + \frac{A}{1 + \frac{R_2}{R_1}} \right] = A \cdot V_{in}$$

$$\therefore H(s) = \frac{V_o}{V_{in}} = \frac{A}{1 + \frac{A}{1 + \frac{R_2}{R_1}}} \times \frac{(1 + \frac{R_2}{R_1})}{A}$$

$$H(s) = \frac{(1 + \frac{R_2}{R_1})}{1 + \frac{(1 + \frac{R_2}{R_1})}{A}} = \frac{K}{1 + \frac{K}{A}}$$

where: $K = 1 + \frac{R_2}{R_1}$

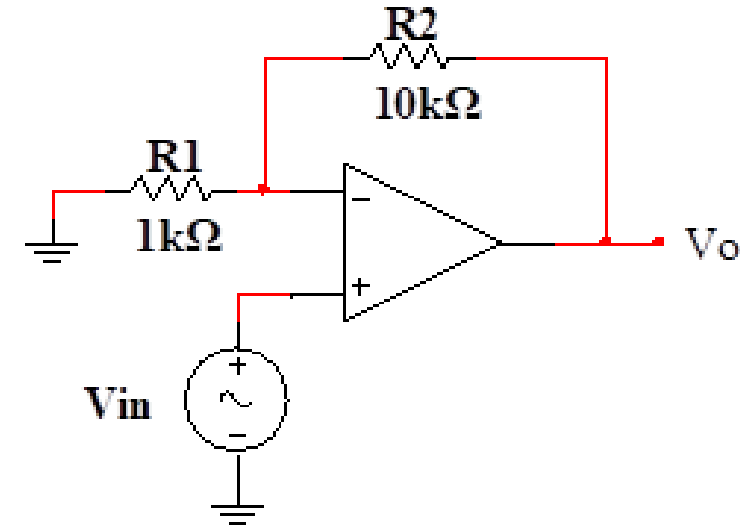

Example 2

Derive $H(s)$ and sketch the closed loop frequency response.

$$H(s) = \frac{K}{1 + \frac{K}{A_0} \left(1 + \frac{s}{\omega_b}\right)} = \frac{K}{1 + \frac{K}{A_0} + \frac{Ks}{A_0 \omega_b}}$$


$$H(s) = \frac{K}{1 + \frac{s}{\left(\frac{A_0 \omega_b}{K}\right)}} = \frac{K}{1 + \frac{s}{\omega_c}}$$

* New d.c gain $= K = 1 + \frac{R_2}{R_1} = 11$

* New cut-off Frequency

$$\omega_c = \frac{A_0 \omega_b}{K} = 90.91 \times 10^3 \text{ rad/sec.}$$

$$K = 1 + \frac{R_2}{R_1}$$
$$\frac{K}{\sqrt{2}}$$

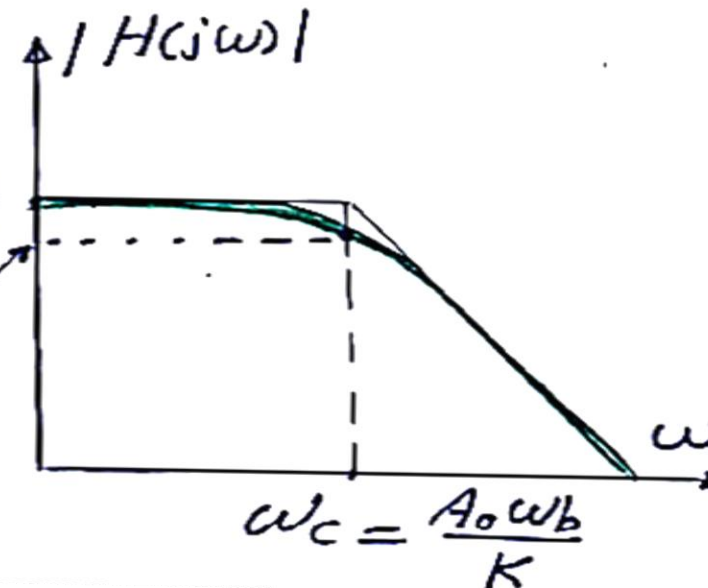

Example 2

(c) Calculate the Gain-Band-width product(GBP).


- $\text{GBP}(\text{Open-Loop}) = A_o \omega_b = 10^6 \text{ rad/sec}$
- $\text{GBP}(\text{Closed-Loop}) = K \omega_c = K \frac{A_o \omega_b}{K} = A_o \omega_b = 10^6 \text{ rad/Sec}$
- $\text{GBP} = \text{Constant}$

Types of Filters

Types of Filters

- The four primary types of filters include:
 1. The Low-pass filter.
 2. The High-pass filter.
 3. The Band-pass filter.
 4. The Notch filter (band-reject or band-stop filter).
- The terms "low" and "high" do not refer to any absolute values of frequency, but rather they are relative values with respect to the cutoff frequency.




Impact of High Order Filters

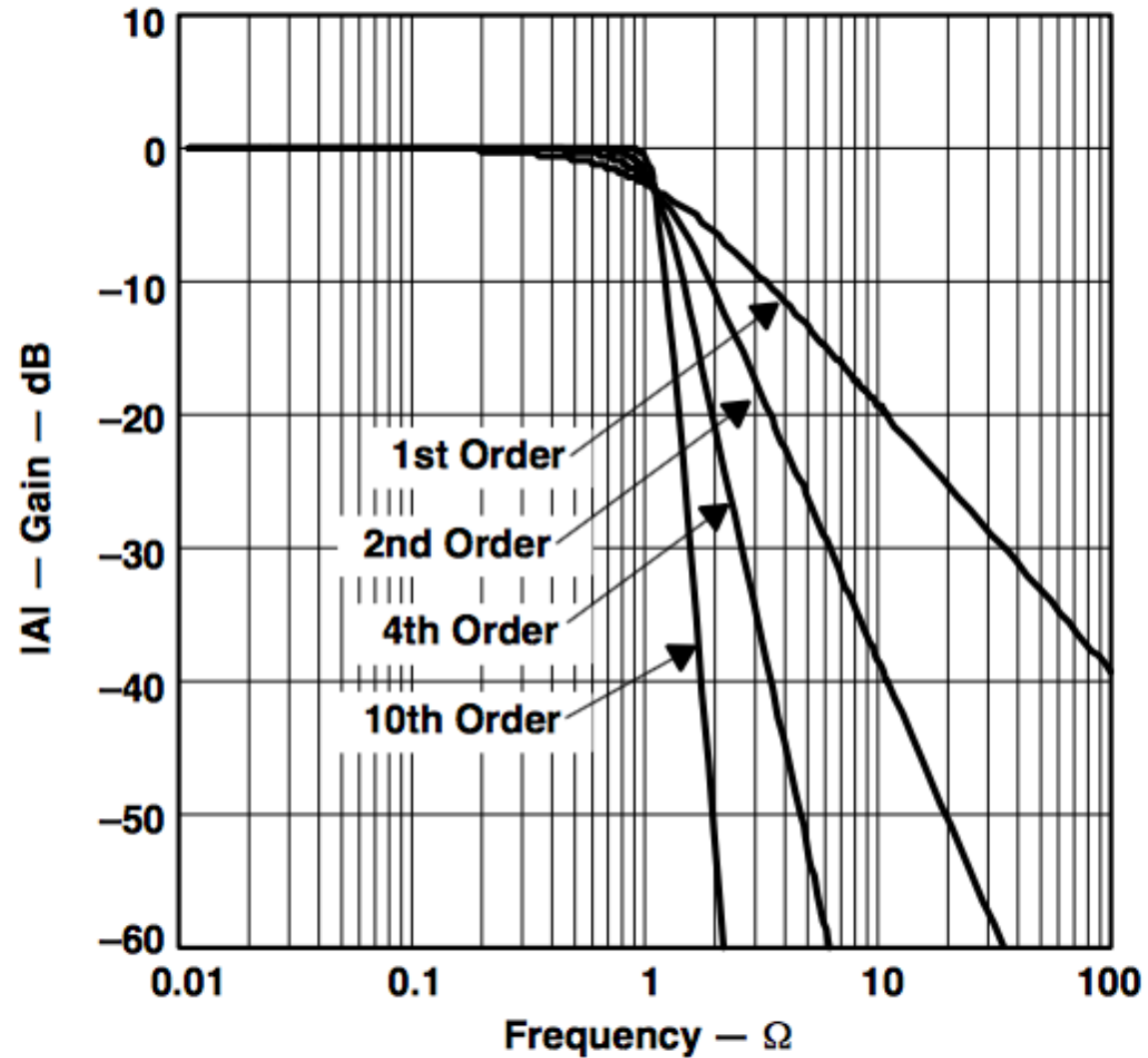

First Order Filters: Low pass filter (LPF)


$$A(S) = \frac{A_m}{1 + \frac{S}{W_c}}$$

$A_m \rightarrow$ is the maximum gain (DC Gain),
 $W_c \rightarrow$ is the Cut-Off Frequency rad/Sec
 $W_c = 2\pi f_c$
 $f_c \rightarrow$ is the Cut-Off Frequency Hz

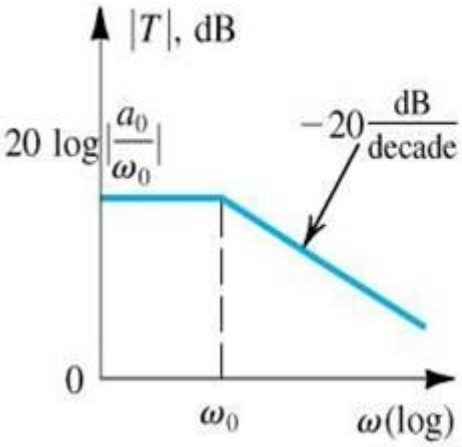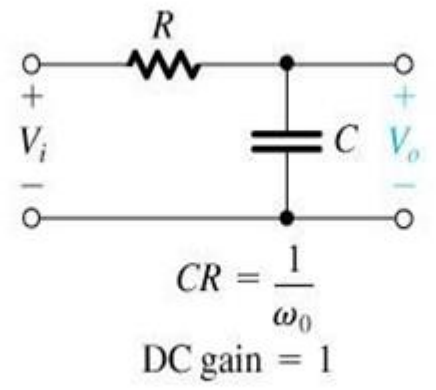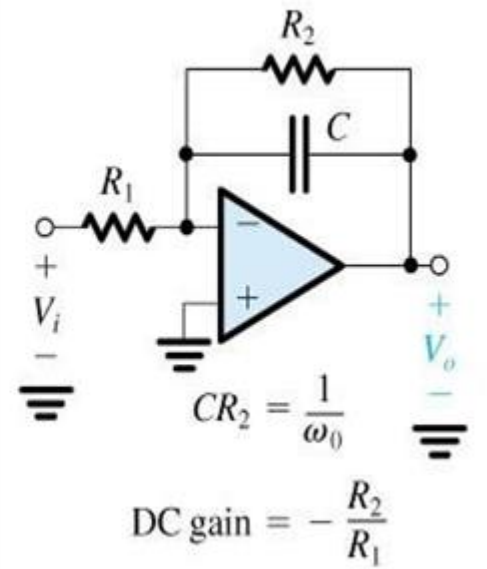Bode Plot for $ T $	Passive Realization	Op Amp-RC Realization
 <p> $20 \log \left \frac{a_0}{\omega_0} \right$ $-20 \frac{\text{dB}}{\text{decade}}$ ω_0 $\omega(\log)$ </p>	 <p> $CR = \frac{1}{\omega_0}$ DC gain = 1 </p>	 <p> $CR_2 = \frac{1}{\omega_0}$ DC gain = $-\frac{R_2}{R_1}$ </p>

$$\begin{aligned}
 A(s) &= -\frac{R_2 \parallel \frac{1}{sC}}{R_1} = -\frac{1}{R_1} \times \frac{R_2 \times \frac{1}{sC}}{R_2 + \frac{1}{sC}} \\
 &= -\frac{R_2}{R_1} \times \frac{1}{1 + sCR_2}
 \end{aligned}$$

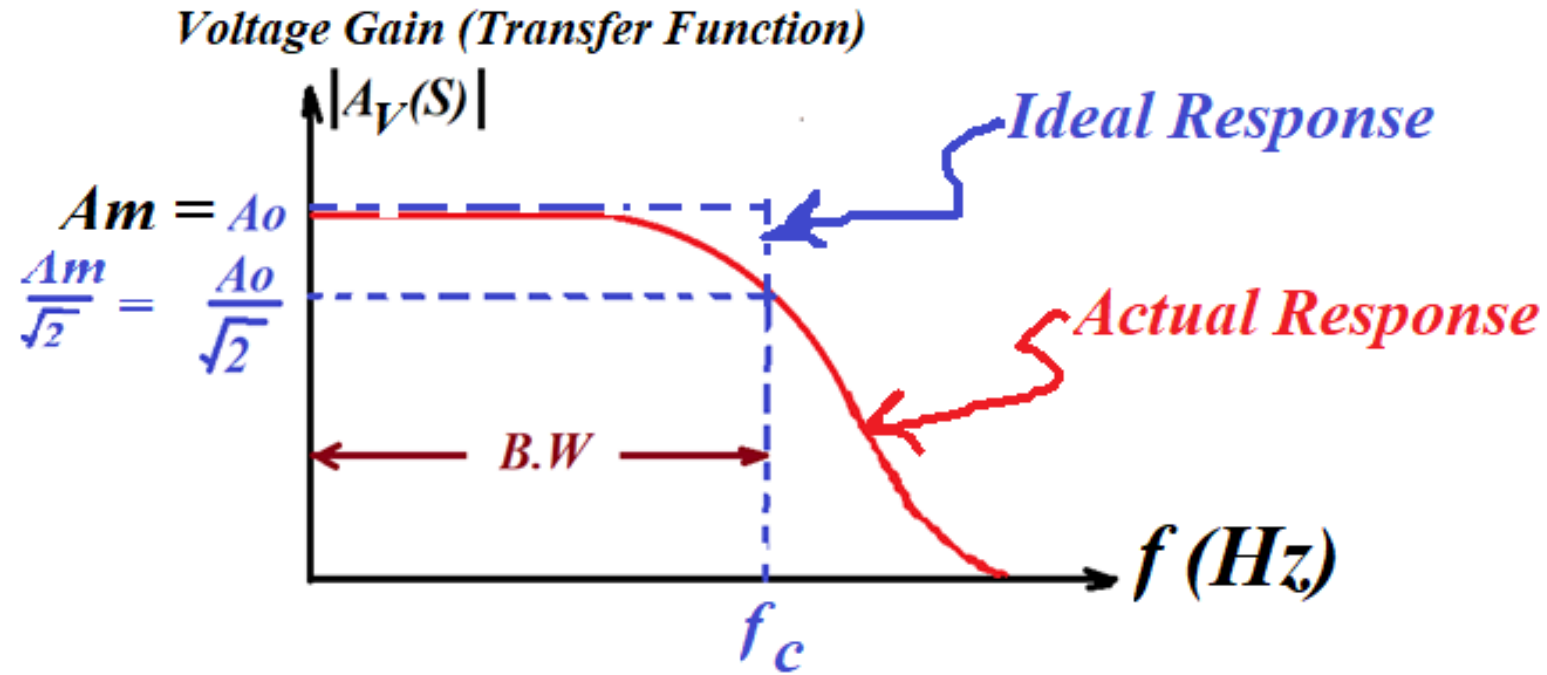First Order Filters: Low pass filter (LPF)




f_c = The Cut-Off Frequency

A_m = The Maximum (DC) Gain

First Order Filters: Low pass filter (LPF)

Example 1

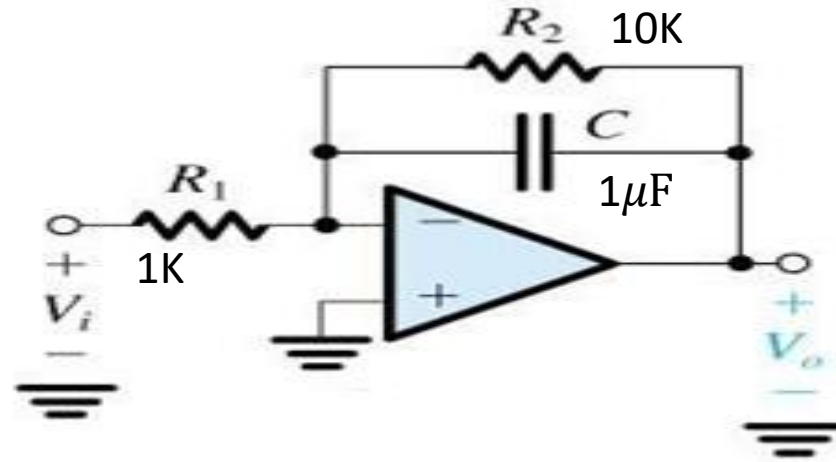

For the circuit shown, Assuming ideal Op-Amp :

- 1) Derive the transfer function $H(S)$ (V_o/V_{in}).*
- 2) Calculate the DC gain (A_m) and the Cut-off Frequency (f_c).*
- 3) Calculate the unity gain frequency (f_T)*

1-Circuit Transfer Function A_v or $H(s)$

$$A_v = \frac{V_o}{V_{in}} = - \frac{Z_2}{Z_1}$$

$$\ast Z_2 = \frac{R_2 \frac{1}{sC}}{R_2 + \frac{1}{sC}} = \frac{R_2}{sCR_2 + 1}$$

$$\ast Z_1 = R_1$$

$$\therefore A_v = - \frac{(R_2/R_1)}{1 + sR_2C}$$

$$A_v = - \frac{(\frac{R_2}{R_1})}{1 + \frac{s}{(\frac{1}{R_2C})}} = - \frac{A_m}{1 + \frac{s}{\omega_c}}$$

$$= - \frac{10}{1 + \frac{s}{100}}$$


2- Calculate the DC gain and the cutoff frequency

$$A_m = \frac{R_2}{R_1} = 10$$

Cut-off frequency

$$\omega_c = \frac{1}{R_2C} = 100 \text{ rad/sec.}$$
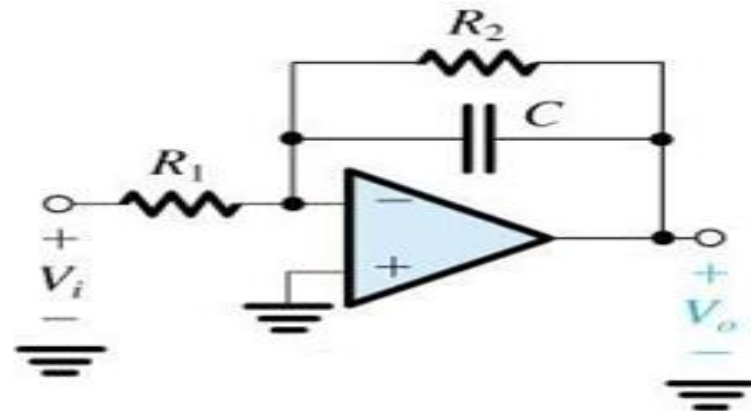
$$f_c = \frac{\omega_c}{2\pi} = \frac{100}{2\pi} = 15.92 \text{ Hz}$$



3- Calculate the unity gain frequency F_T

$$A_v = \frac{A_{m1}}{1 + \frac{s}{\omega_c}}$$


$$A_v(j\omega) = \frac{A_{m1}}{1 + j \frac{\omega}{\omega_c}}$$

$$|A_v| = \frac{A_{m1}}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

$$|A_v| = \frac{A_{m1}}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

$$|A_v| = \frac{10}{\sqrt{1 + \left(\frac{f}{15.92}\right)^2}} = 1$$


$$f_T \approx 158.4 \text{ Hz}$$

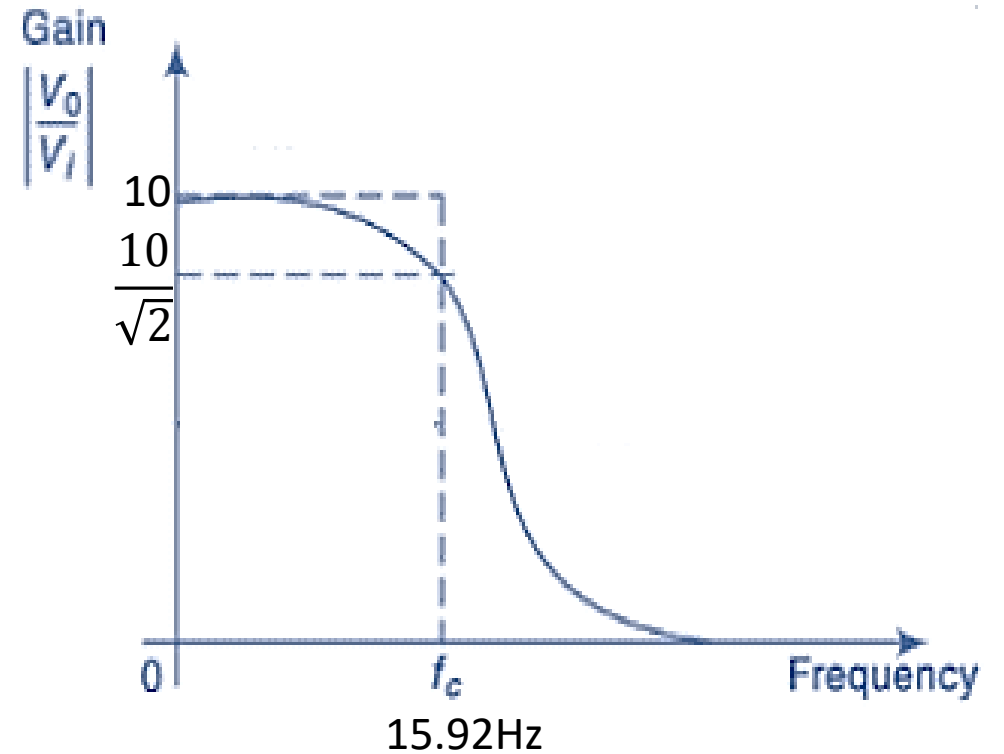

First Order Filters: High pass filter (HPF)


$$A(S) = \frac{A_m}{1 + \frac{W_c}{S}}$$

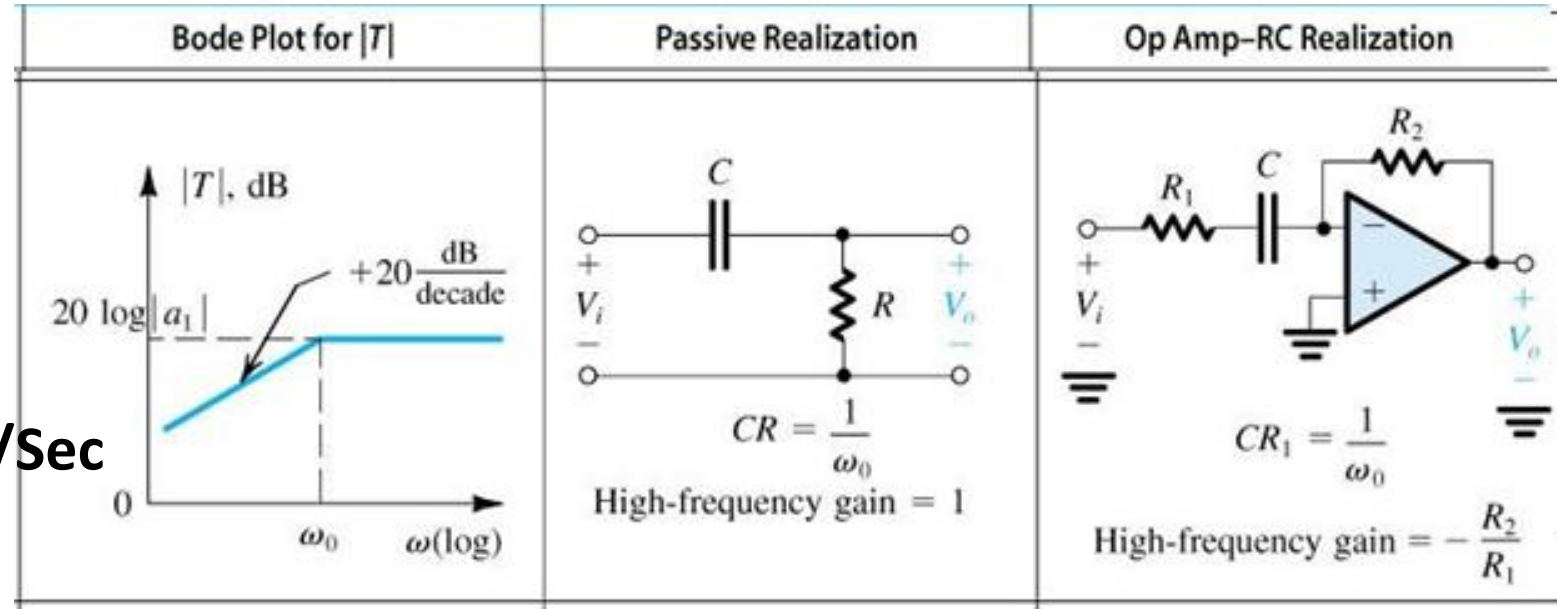$A_m \rightarrow$ is the maximum gain
 (High Frequency Gain),
 $W_c \rightarrow$ is the Cut-Off Frequency rad/Sec
 $W_c = 2\pi f_c$
 $f_c \rightarrow$ is the Cut-Off Frequency Hz



$$A(s) = -\frac{R_2}{R_1 + \frac{1}{sC}} = -\frac{R_2}{R_1} \times \frac{1}{1 + \frac{1}{sCR_1}}$$

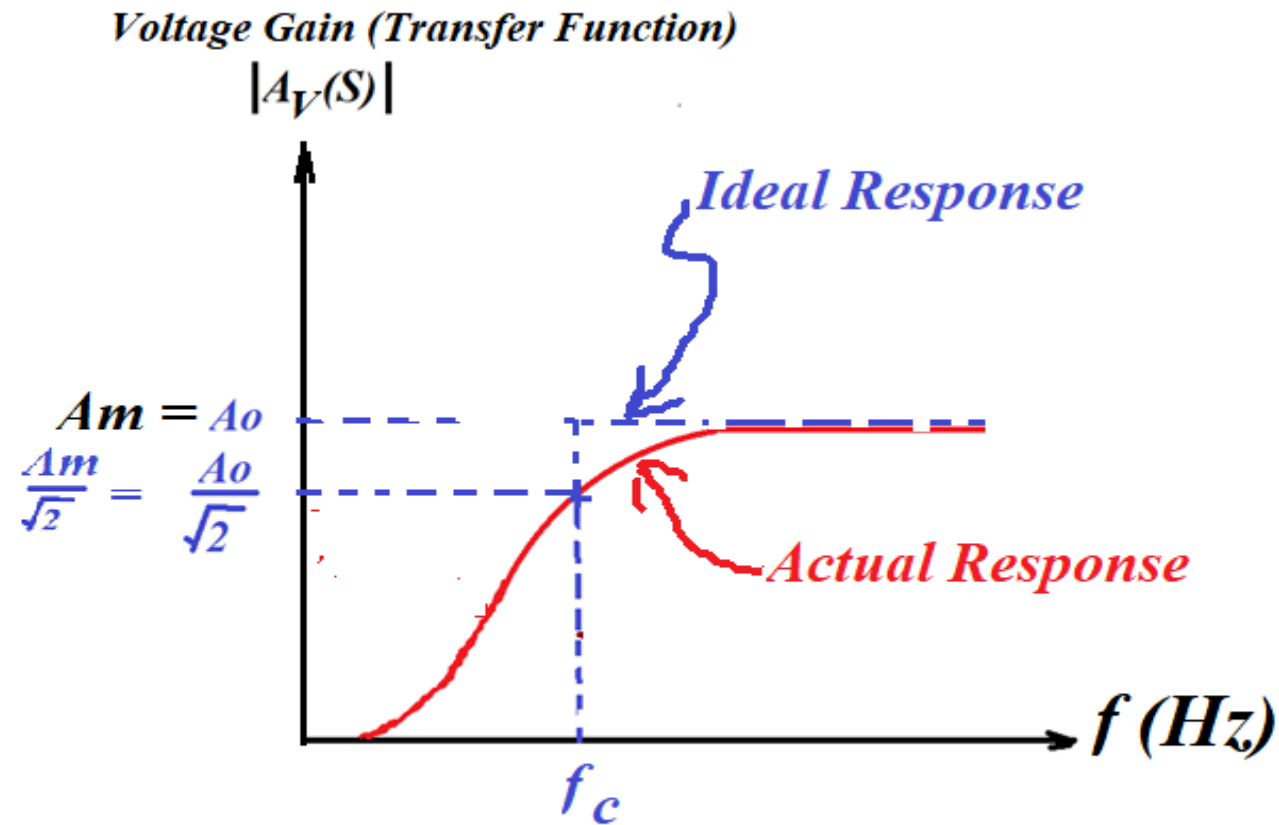First Order Filters: High pass filter (HPF)




f_c = The Cut-Off Frequency

A_m = The Maximum (High-frequency) Gain

First Order Filters: High pass filter (HPF)

Example 2

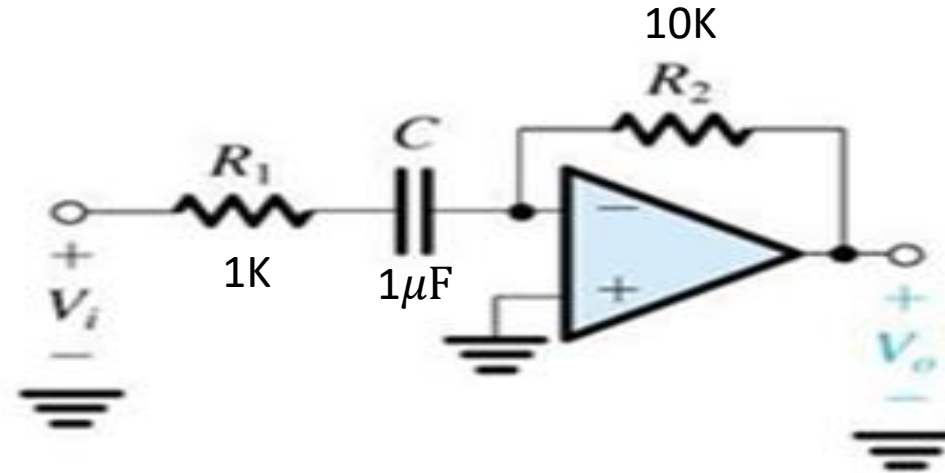

For the circuit shown, Assuming ideal Op-Amp :

- 1) Derive the transfer function $H(S)$ (V_o/V_i).*
- 2) Calculate the DC gain (A_m) and the Cut-off Frequency (f_c).*
- 3) Calculate the unity gain frequency (f_T)*

1-Circuit Transfer Function A_v or $H(s)$

Sol.

① Inverting Amp D: F: 1r

$$A_v = \frac{V_o}{V_{in}} = - \frac{Z_2}{Z_1}$$

$$* Z_2 = R_2$$

$$* Z_1 = R_1 + \frac{1}{sC}$$

$$A_v = \frac{V_o}{V_{in}} = - \frac{R_2}{R_1 + \frac{1}{sC}}$$

$$A_v = - \frac{(R_2/R_1)}{1 + \frac{1}{sCR_1}} = - \frac{(R_2/R_1)}{1 + \frac{(1/R_1C)}{s}}$$

First Order Filters: High pass filter (HPF)

$$A_v = - \frac{(R_1 | R_2)}{1 + \frac{1/R_2}{s}}$$

$$A_v = \frac{A_m}{1 + \frac{\omega_c}{s}}$$

$$A_v = - \frac{10}{1 + \frac{1000}{s}}$$

⑥ Max. gain

$$A_m = \frac{R_2}{R_1} = 10$$

$$\omega_c = \frac{1}{R_1 C} = 1000 \text{ rad/sec}$$

$$f_c = \frac{\omega_c}{2\pi} = \frac{1000}{2\pi} = 159.2 \text{ Hz}$$

$$\textcircled{c} A_v = - \frac{10}{1 + \frac{1000}{s}}$$


$$A_v = \frac{-10}{1 + \frac{1000}{j\omega}}$$

$$A_v = - \frac{10}{1 - j \frac{1000}{\omega}}$$

$$|A_v| = \frac{10}{\sqrt{1 + \left(\frac{\omega_c}{\omega}\right)^2}} = \frac{10}{\sqrt{1 + \left(\frac{f_c}{f}\right)^2}}$$

$$|A_v| = \frac{10}{\sqrt{1 + \left(\frac{159.2}{f}\right)^2}} = 1$$

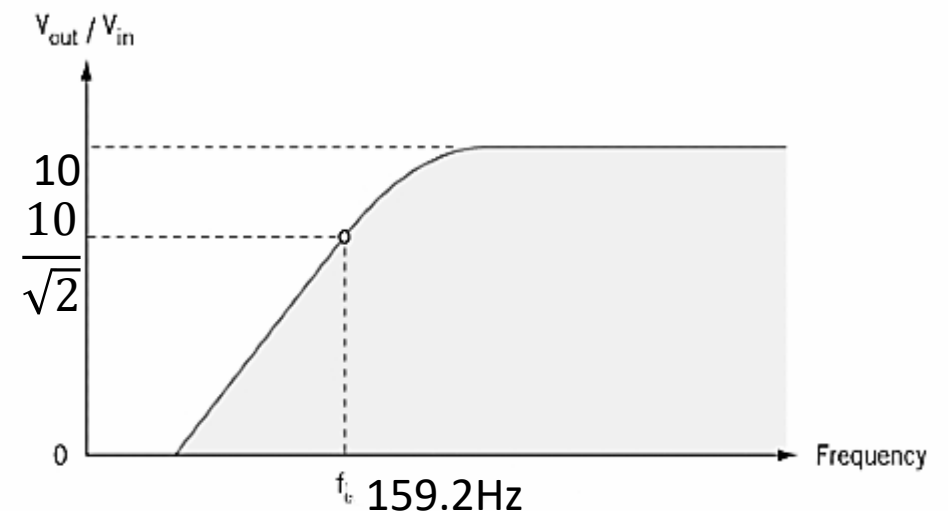solving $\left\{ f_T \approx 16 \text{ Hz} \right\}$



First Order Filters: Band pass filter (BPF)

$$Z_1 = R_1 + \frac{1}{j\omega C_1}$$

$$Z_2 = R_2 || \frac{1}{j\omega C_2}$$



$$Z_2 = \frac{R_2 \frac{1}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}}$$

$$H(j\omega) = -\frac{Z_2}{Z_1}$$

$$= -\frac{\frac{R_2}{j\omega C_2}}{(R_2 + \frac{1}{j\omega C_2})(R_1 + \frac{1}{j\omega C_1})}$$

$$= -\frac{\frac{R_2}{j\omega C_2}}{(\frac{R_2 j\omega C_2 + 1}{j\omega C_2})(\frac{R_1 j\omega C_1 + 1}{j\omega C_1})}$$
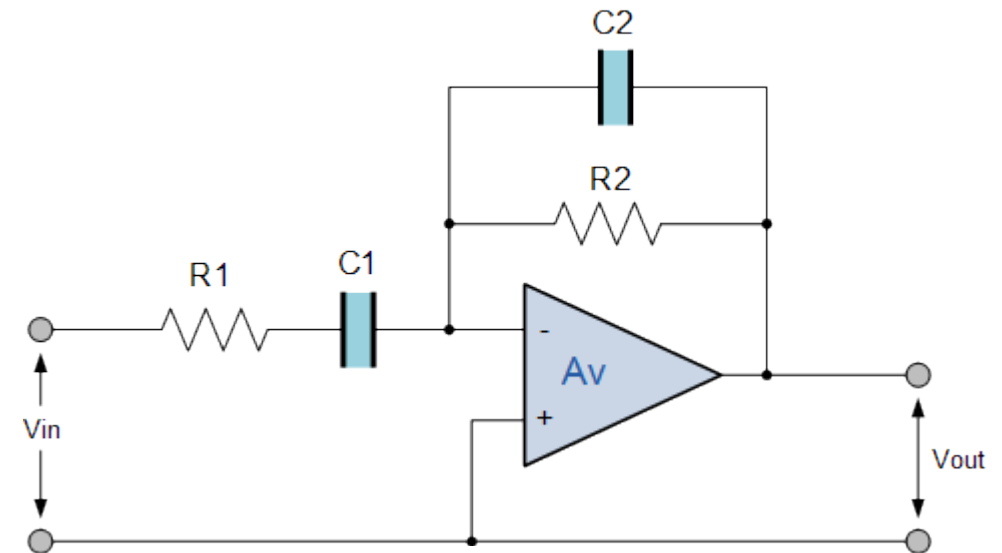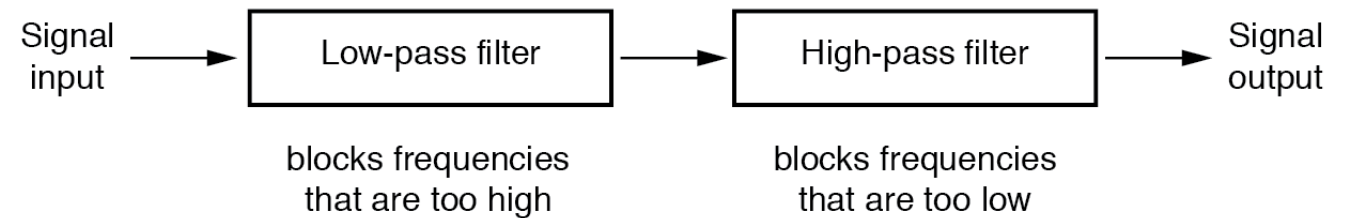
$$= -\frac{jR_2\omega C_1}{(1 + j\omega C_2 R_2)(1 + j\omega C_1 R_1)}$$




$$\text{Voltage Gain} = -\frac{R_2}{R_1}$$

$$f_{c_1} = \frac{1}{2\pi R_1 C_1}, \quad f_{c_2} = \frac{1}{2\pi R_2 C_2}$$

First Order Filters: Band pass filter (BPF)

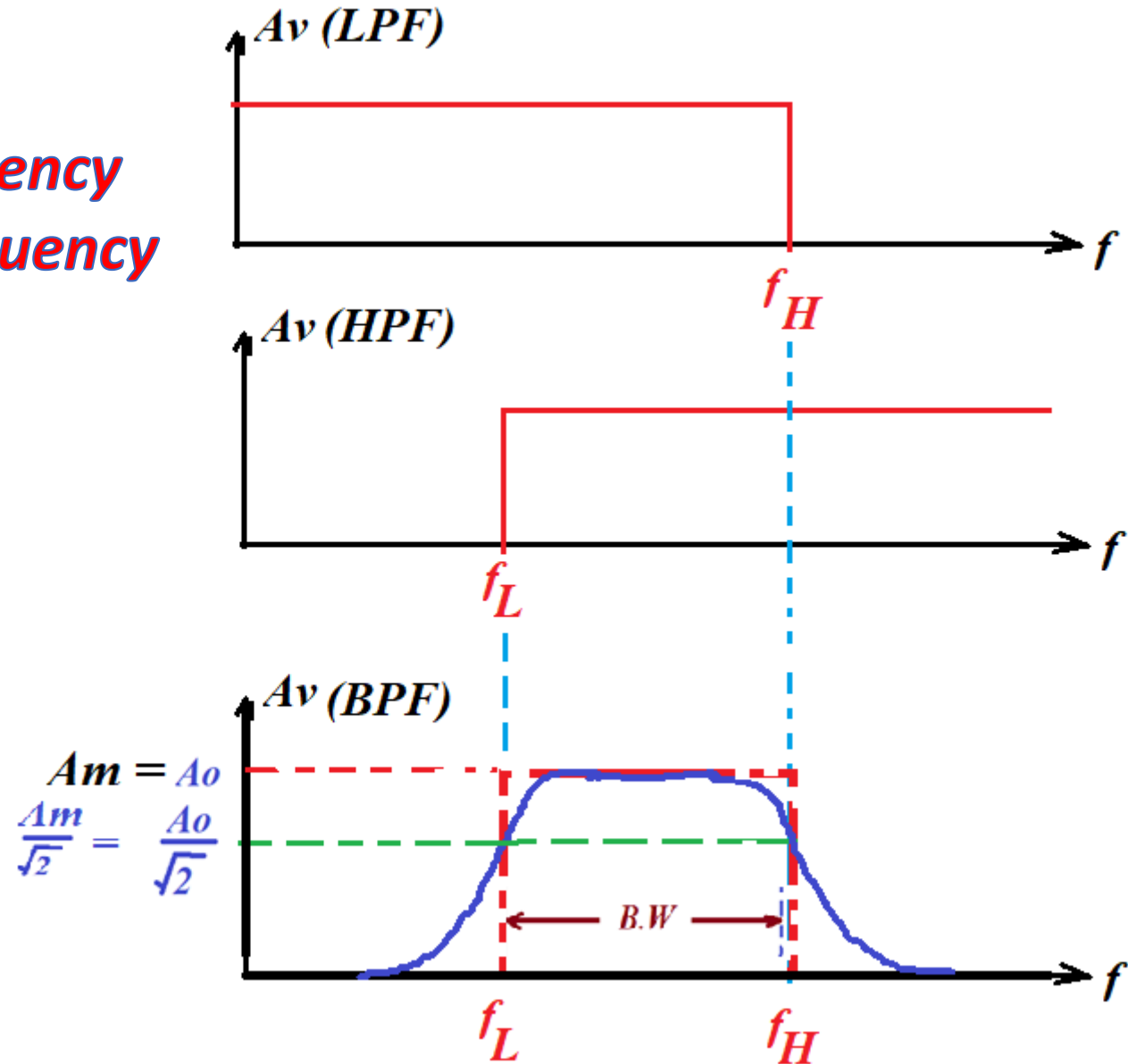- f_L is the lower Cut-off Frequency
- f_H is the Higher Cut-off Frequency
- $B.W$ is the Band-Width
- $B.W = f_H - f_L$




Tuned Filter (Narrow B.W Band pass filter)

The Center Frequency (Tuned Freq.)

$$f_o = \sqrt{f_L \cdot f_H}$$

*The Quality Factor
(How Sharp is the response)*

$$Q = \frac{f_o}{B.W}$$


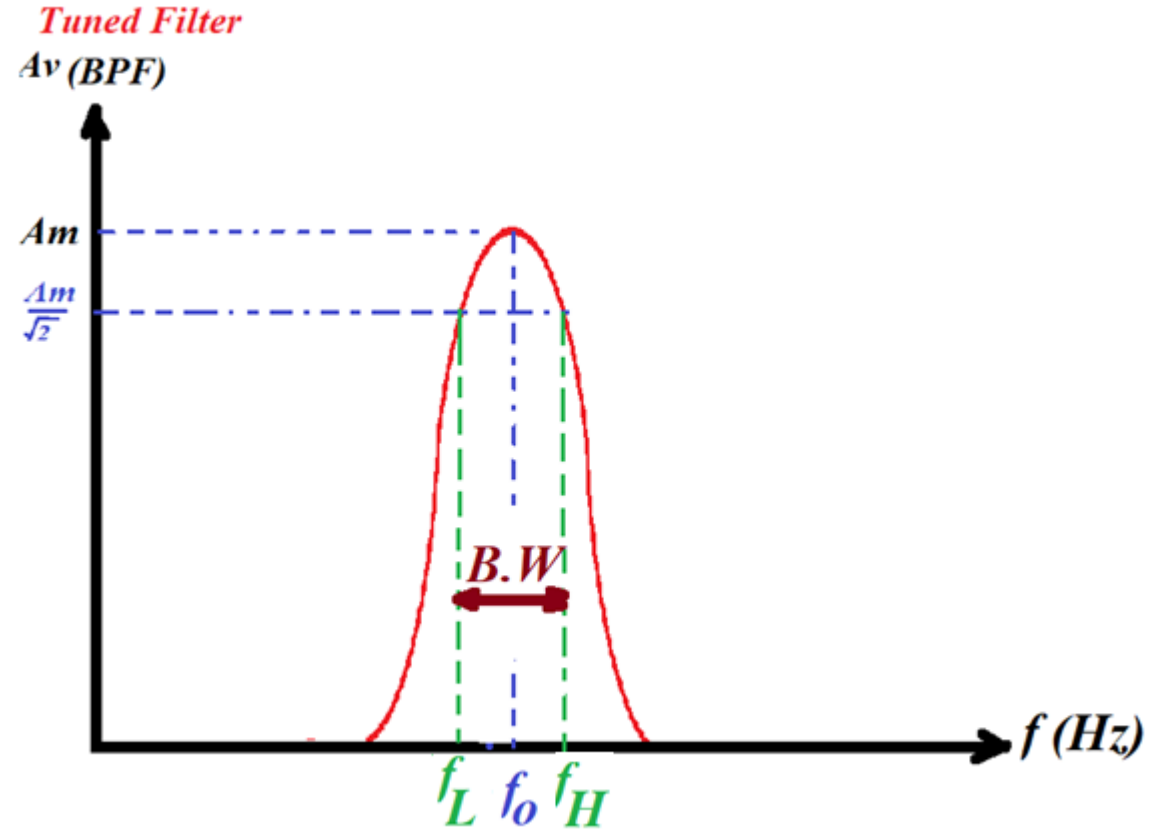


f_o is the Center Frequency


f_L is the Lower Cut-Off frequency

f_H is the Higher Cut-Off frequency

Band Stop filter (BSF)

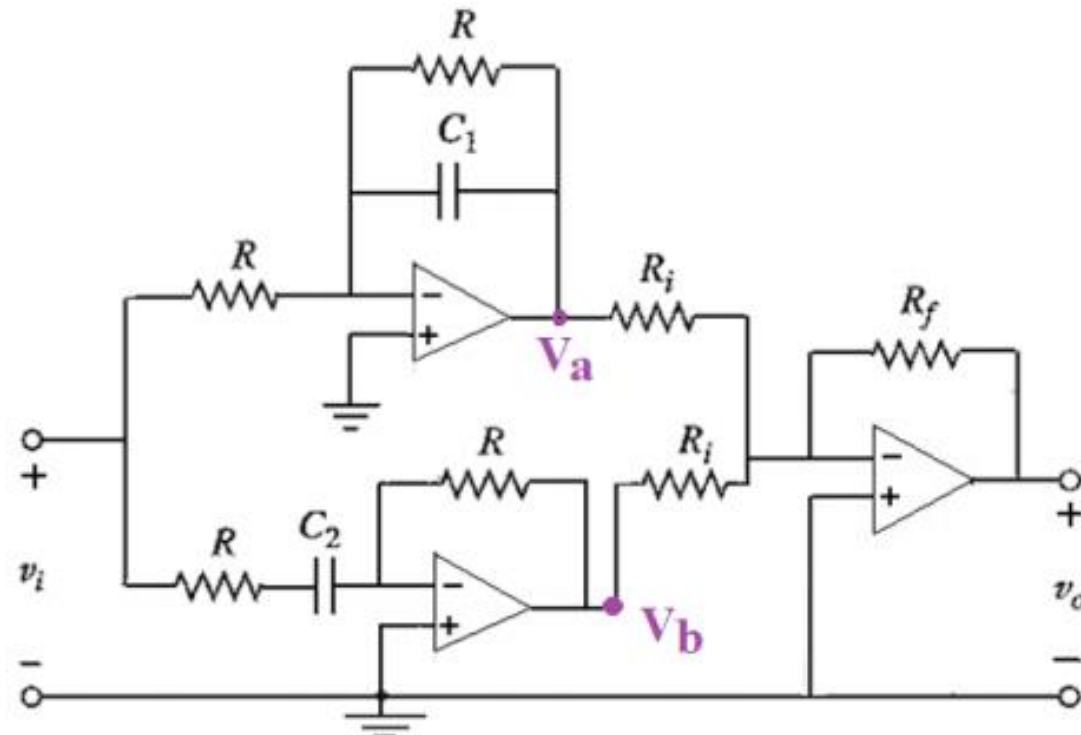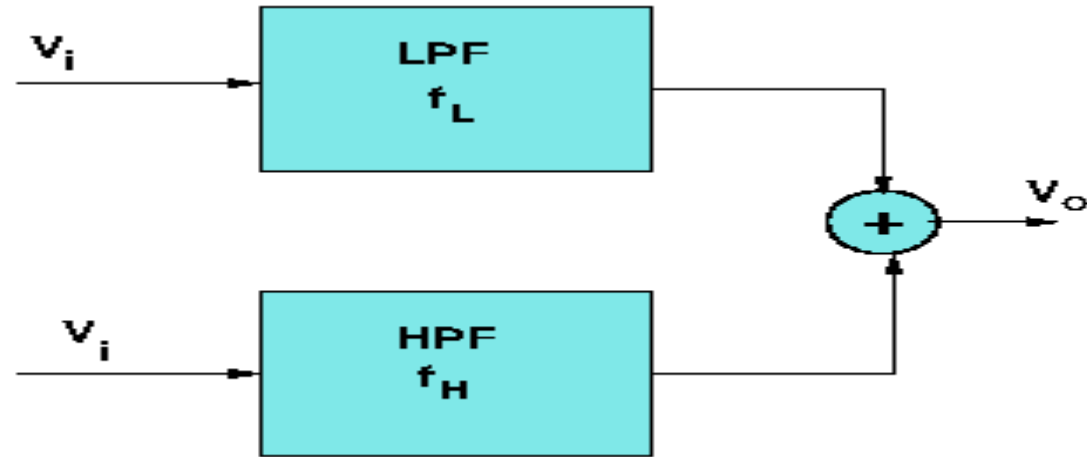


Band Stop filter (BSF)

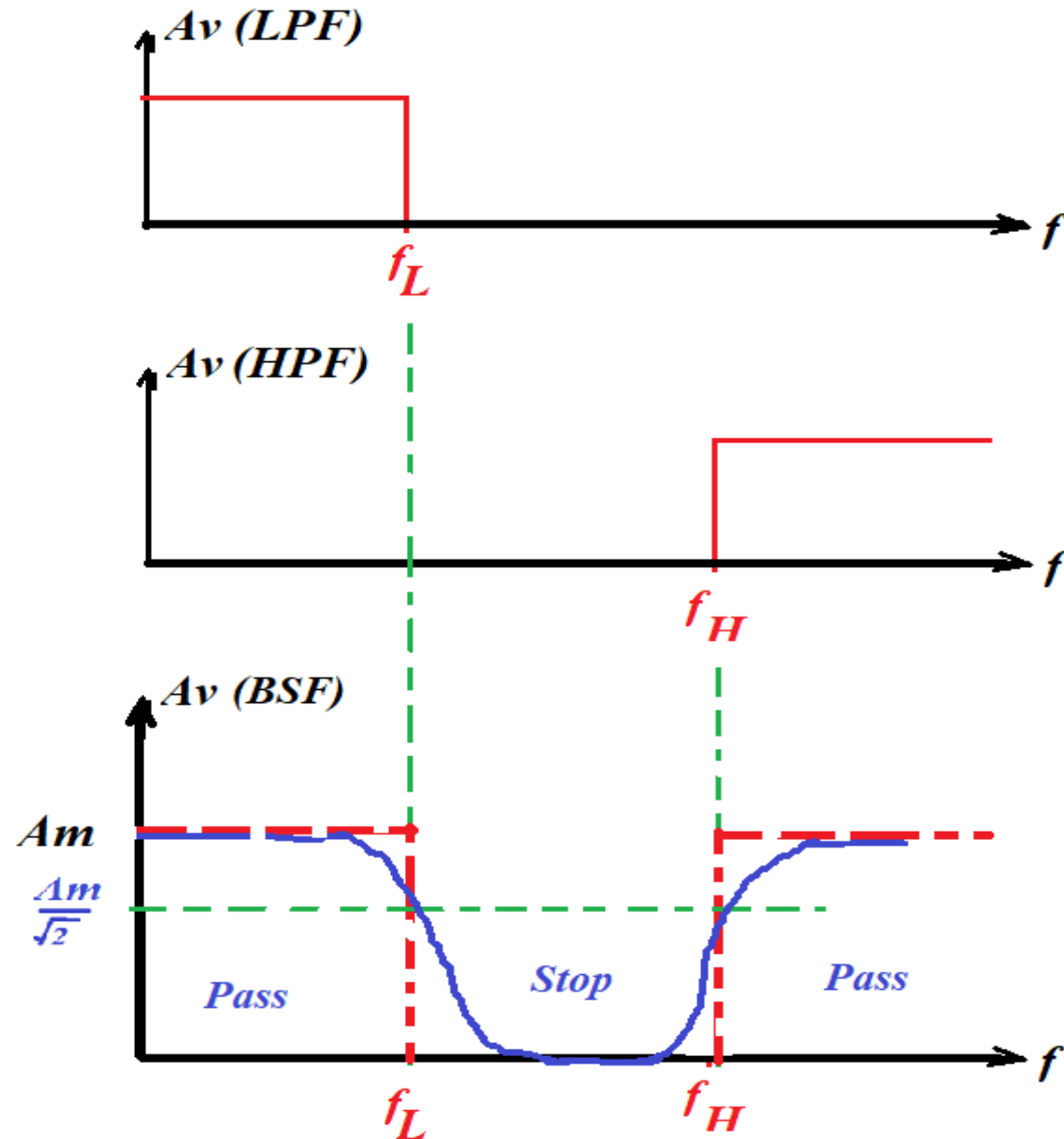

Example 3

Analyze the circuit shown in Figure :


- (a) Derive an expression for the circuit transfer function $H(s)$.
- (b) Calculate the lower and upper cut-off frequencies (f_L and f_H).
- (c) Sketch the frequency response

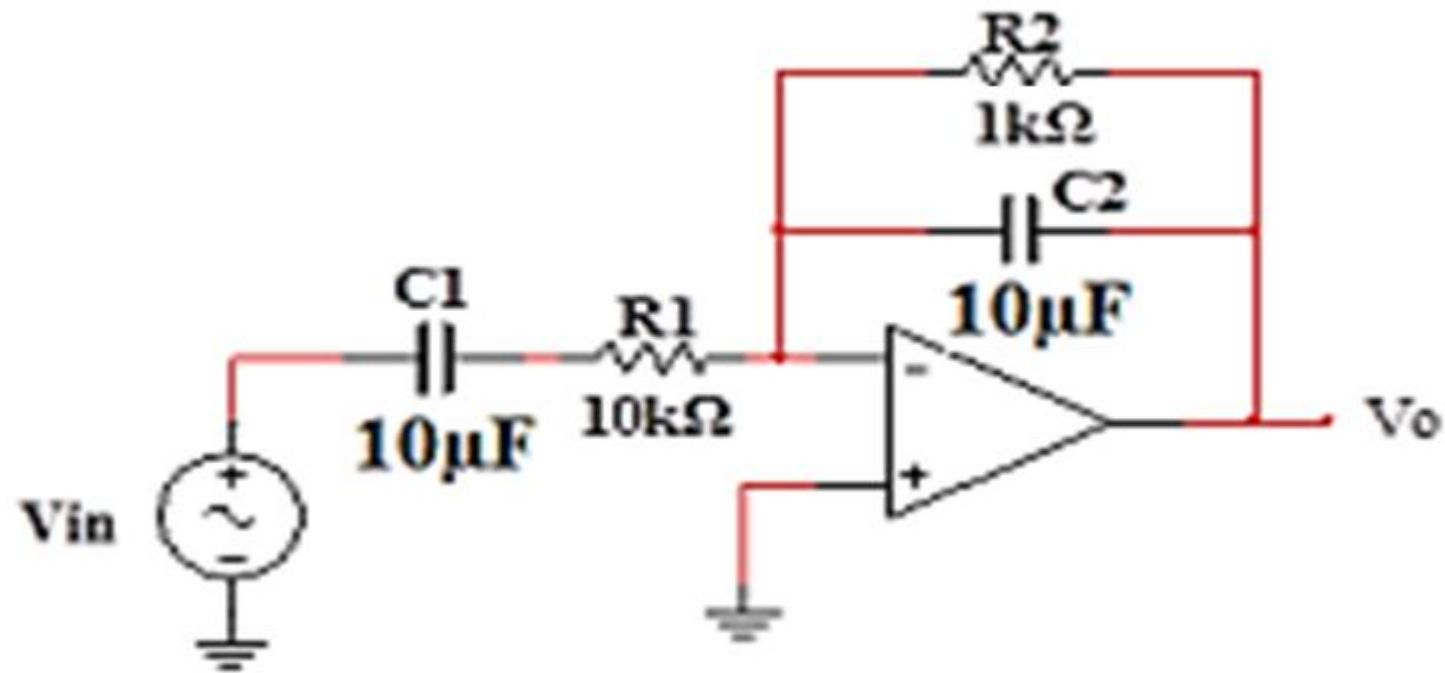

Example 3

1-Circuit Transfer Function A_v or $H(s)$

$$H(s) = - \frac{Z_2}{Z_1}$$
$$\times Z_2 = \frac{R_2 \cdot \frac{1}{sC_2}}{R_2 + \frac{1}{sC_2}} = \frac{R_2}{sC_2R_2 + 1}$$
$$\times Z_1 = R_1 + \frac{1}{sC_1}$$
$$\therefore H(s) = - \frac{R_2}{(sC_2R_2 + 1)} \frac{1}{R_1 + \frac{1}{sC_1}}$$
$$H(s) = - \frac{(R_2/R_1)}{[sC_2R_2 + 1][1 + \frac{1}{sC_1R_1}]}$$

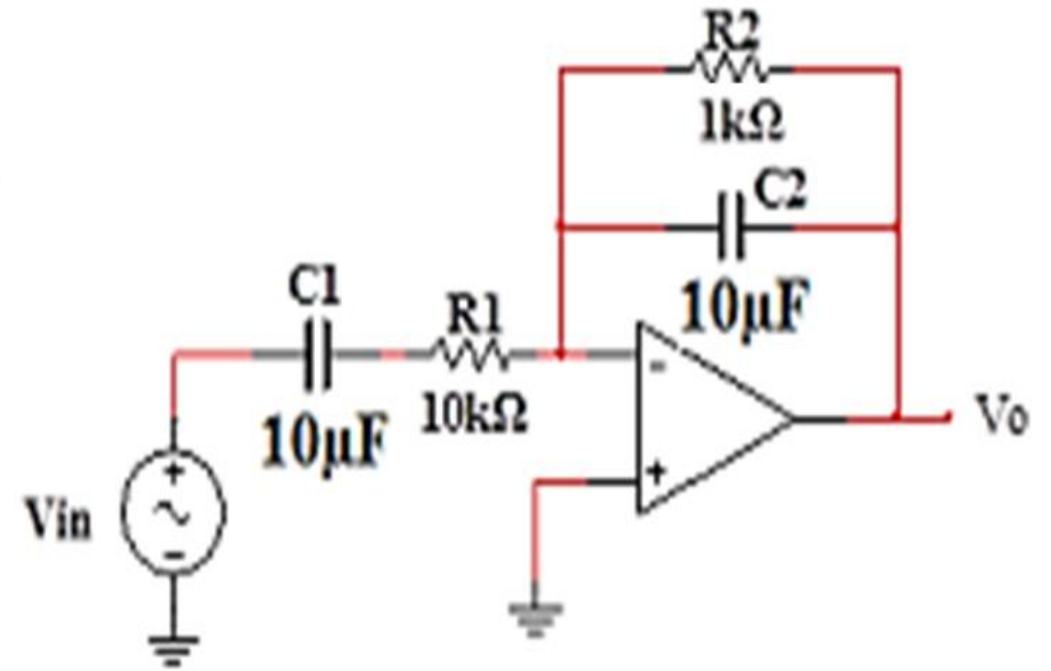

Example 3

$$H(s) = - \frac{(R_2/R_1)}{[s(R_2C_2 + 1)] [1 + \frac{1}{sC_1R_1}]}$$

$$H(s) = - \frac{(R_2/R_1)}{[1 + \frac{s}{1/R_2C_2}] [1 + \frac{1/R_1C_1}{s}]}$$

$$H(s) = - \frac{(R_2/R_1)}{[1 + \frac{s}{\omega_2}] [1 + \frac{\omega_1}{s}]} = - \frac{10}{\underbrace{[1 + \frac{s}{100}]}_{\text{LPF}} \underbrace{[1 + \frac{10}{s}]}_{\text{HPF}}}$$

$$H(s) = \frac{-10}{[1 + \frac{s}{100}] [1 + \frac{10}{s}]}$$

$$\omega_2 = 100 \text{ rad/sec}$$

$$\omega_1 = 10 \text{ rad/sec.}$$

Example 3

2- Calculate the lower and upper cutoff frequencies

$$\ast \omega_L = 10 \text{ rad/sec.} = 2\pi f_L$$


$$\therefore f_L = \frac{10}{2\pi}$$

$$f_L = 1.592 \text{ Hz}$$

$$\ast \omega_H = 100 \text{ rad/sec} = 2\pi f_H$$

$$\therefore f_H = \frac{100}{2\pi}$$

$$f_H = 15.92 \text{ Hz}$$

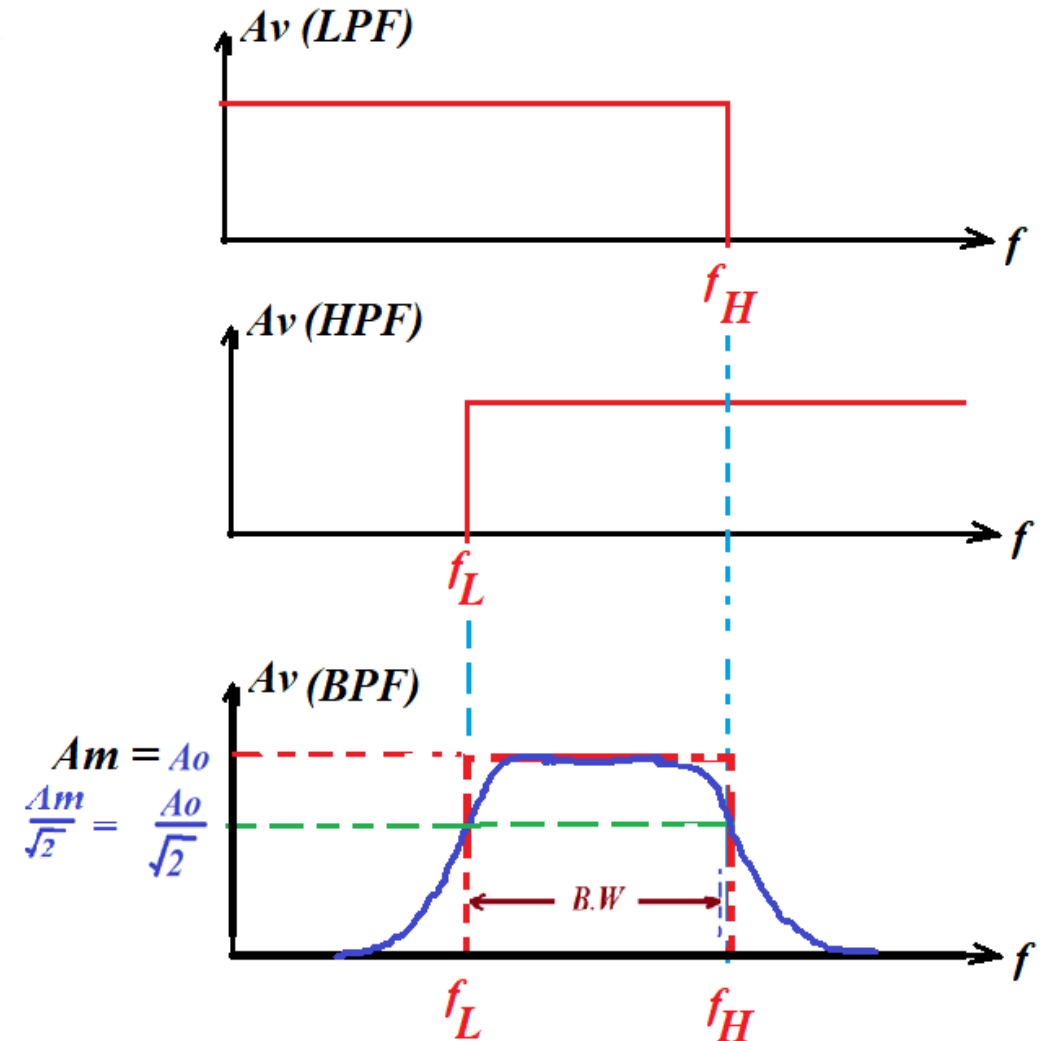

Example 3

3- Sketch the frequency response

