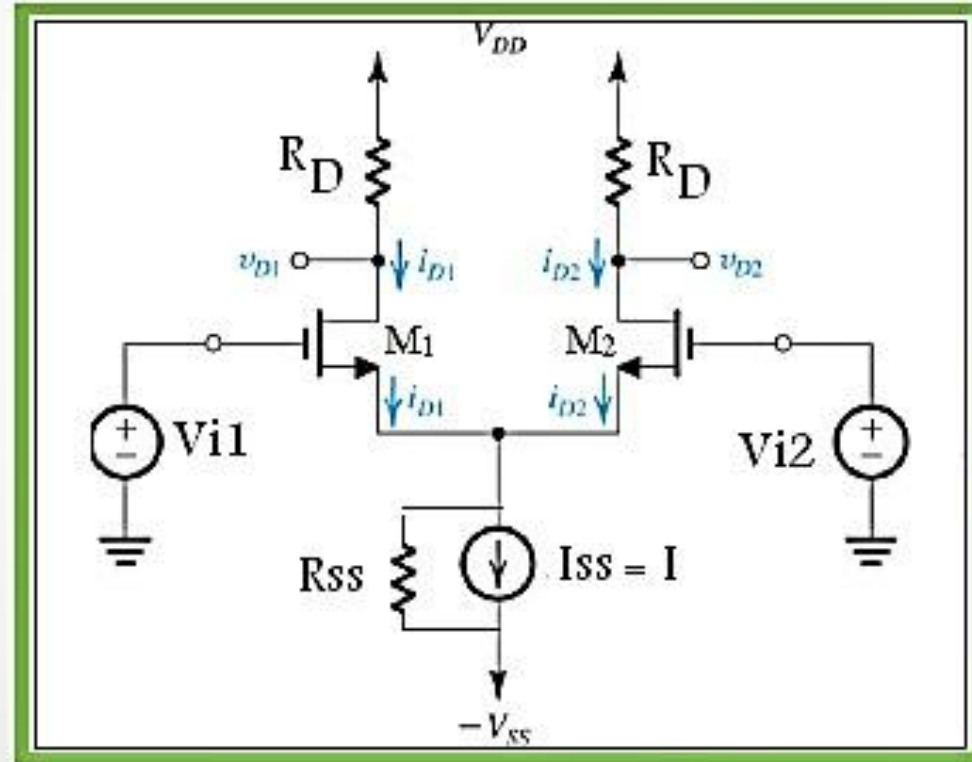


MOS Differential Amplifier/Pair

- Source Coupled Circuit:
 - Two matched MOS-FET (**Same K and V_T**)
 - Their Sources are connected together
 - The input signals are connected to the M's Gates
 - A Constant DC biasing Current ' I ' is used to set the DC operating point.



$$i_{D1} + i_{D2} = I$$


Source Coupled Circuit Large Signal Analysis (Saturation Mode)

- If Gate 1 and 2 are connected together (Common mode signal), then the two drain currents will be equal

$$v_{GS1} = v_{GS2} = v_{CM}$$

$$i_{D1} = i_{D2} = \frac{I}{2}$$
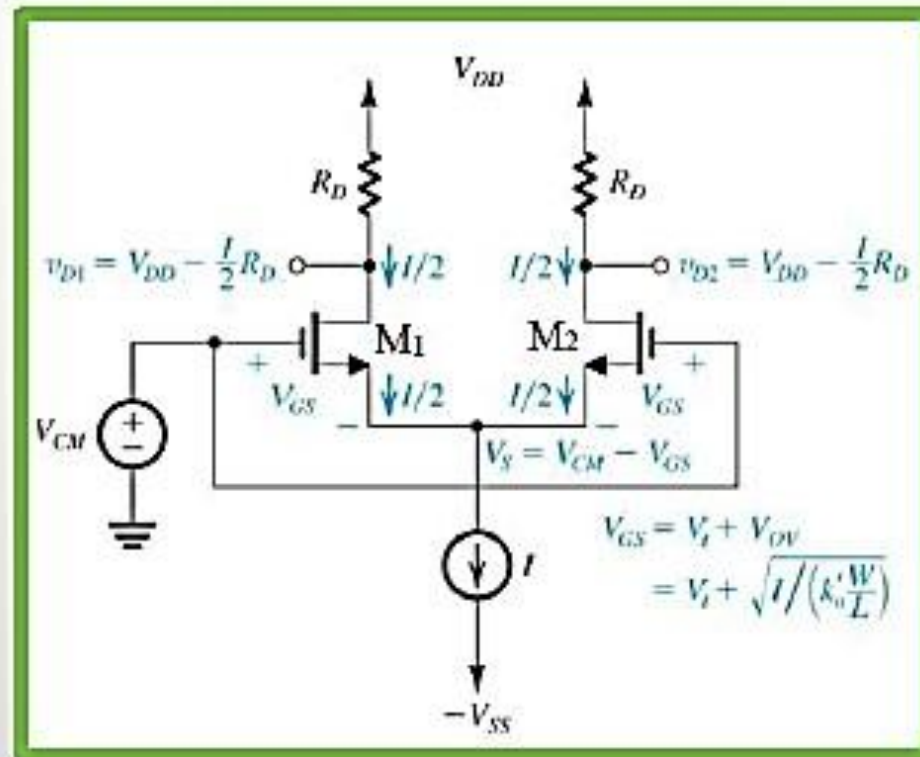
$$v_{D1} = v_{D2} = V_{DD} - \frac{I}{2} R_D$$




Differential Amplifier Large Signal Analysis (Cont.):

- Changing the value of the common mode signal will not change the transistors currents

$$v_{GS1} = v_{GS2} = v_{CM}$$
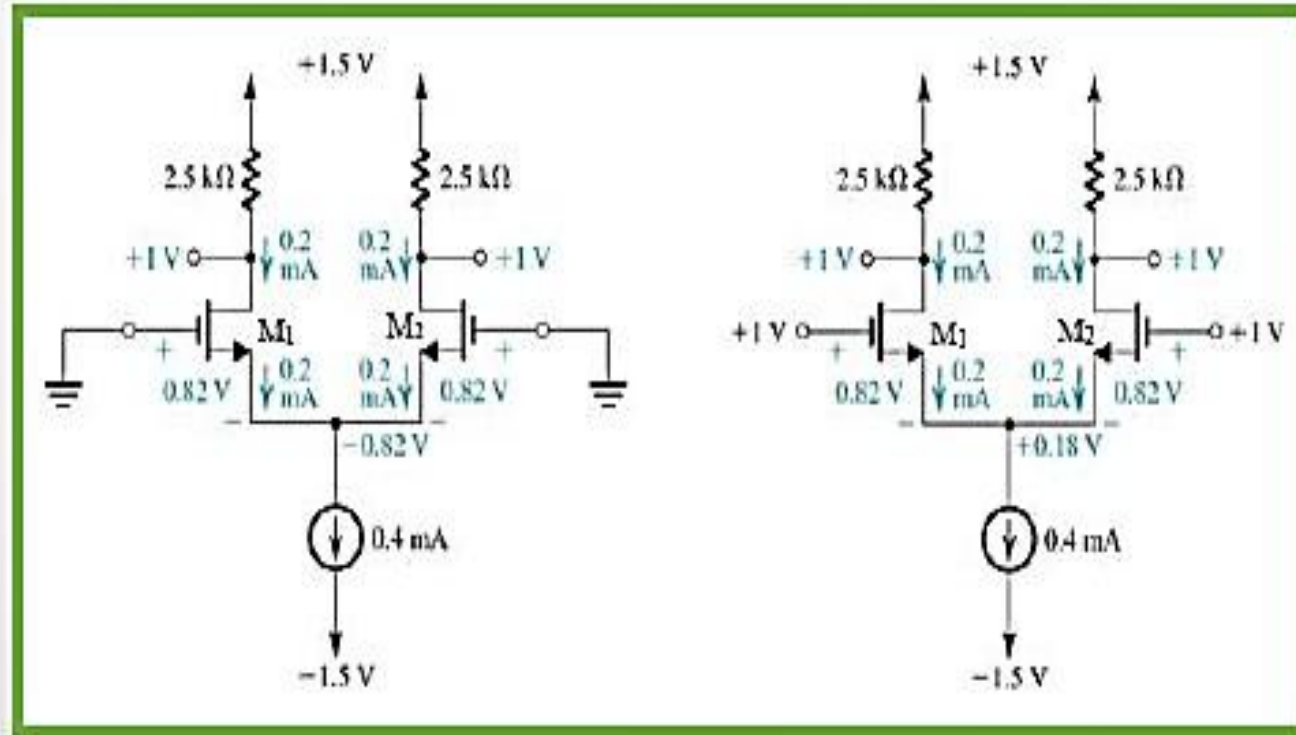
$$v_{D1} = v_{D2} = V_{DD} - \frac{I}{2} R_D$$



The DA rejects the common mode Signal

MOS Differential Amplifier/Pair

- Source Coupled Circuit Large Signal Analysis:
 - If Gate 1 and 2 are not connected together (**Differential signal**), then the two drain currents **won't be equal**

$$v_{GS1} - v_{GS2} = v_{ID}$$


$$i_{D1} \neq i_{D2}$$

If $v_{ID} \gg 0$ such that M1 is Linear and M2 is Off

$$i_{D1} = I \text{ \& } i_{D2} = 0$$

If $v_{ID} \ll 0$ such that M1 is OFF and M2 is Linear

$$i_{D1} = 0 \text{ \& } i_{D2} = I$$

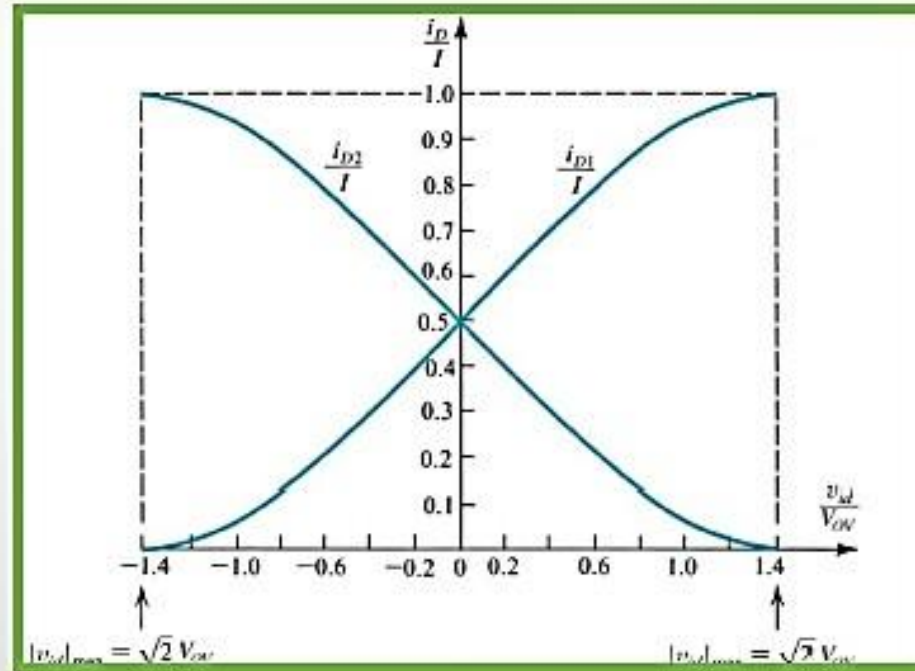

The DA responds to any change in the Differential mode Signal

MOS Differential Amplifier/Pair

□ Source Coupled Circuit Large Signal Analysis:

□ M1 and M2 are Saturated and matched

$$i_{D1} = \frac{K}{2} (v_{GS1} - V_t)^2$$

$$i_{D2} = \frac{K}{2} (v_{GS2} - V_t)^2$$


$$i_{D1} + i_{D2} = I$$

$$\sqrt{i_{D1}} = \sqrt{\frac{K}{2}} (v_{GS1} - V_t)$$

$$\sqrt{i_{D2}} = \sqrt{\frac{K}{2}} (v_{GS2} - V_t)$$

$$\sqrt{i_{D1}} - \sqrt{i_{D2}} = \sqrt{\frac{K}{2}} v_{ID}$$


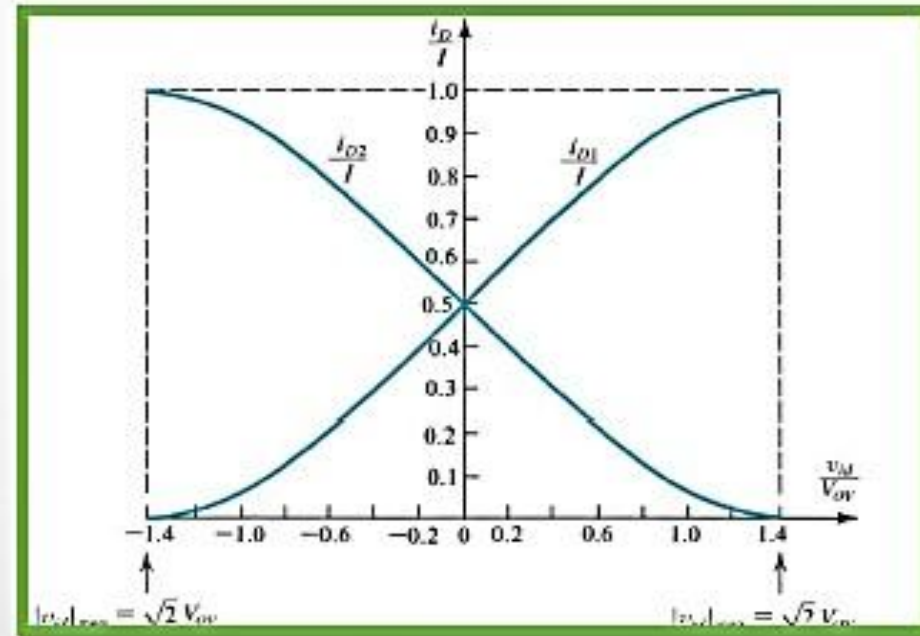
$$2\sqrt{i_{D1}i_{D2}} = I - \frac{K}{2} v_{ID}^2$$



$$i_{D1} = \frac{I}{2} + \sqrt{KI} \left(\frac{v_{ID}}{2} \right) \sqrt{1 - \frac{\left(\frac{v_{ID}}{2} \right)^2}{I/K}}$$

$$i_{D2} = \frac{I}{2} - \sqrt{KI} \left(\frac{v_{ID}}{2} \right) \sqrt{1 - \frac{\left(\frac{v_{ID}}{2} \right)^2}{I/K}}$$

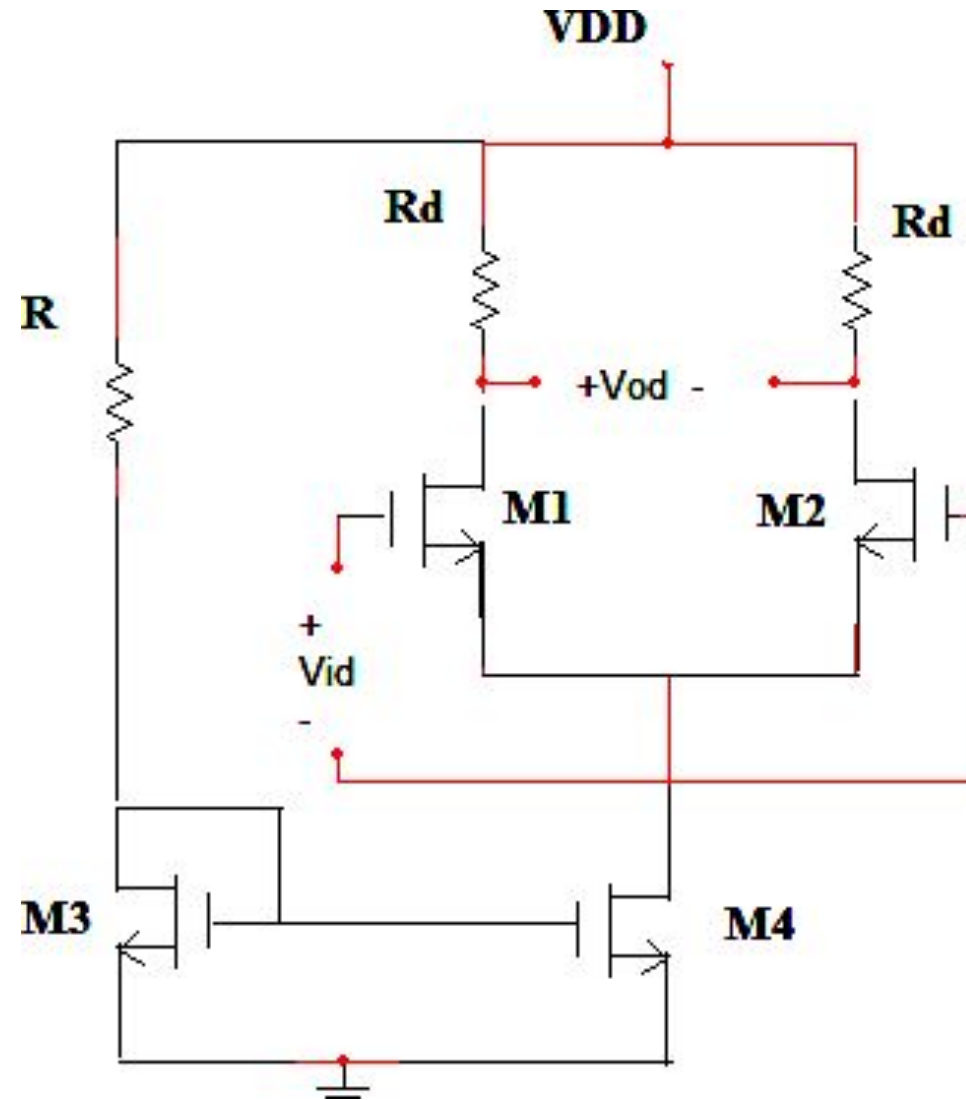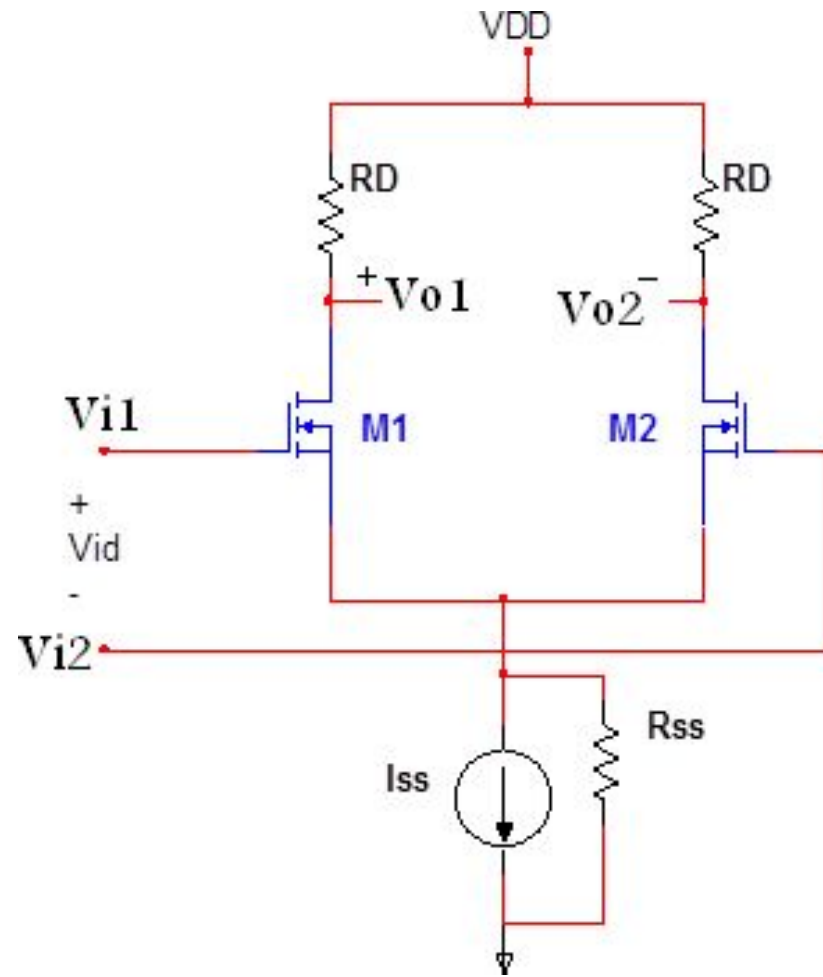
Summary of MOSFET Differential Amplifier Analysis



Example(1)


Analyze the MOS-differential amplifier circuit shown in Figure if M1 and M2 are matched with $K = 2\text{mA/V}^2$, $V_T = 1\text{V}$ and r_{ds} is neglected. M3 and M4 are matched with $K = 1\text{mA/V}^2$, $V_T = 1\text{V}$ and $r_{ds} = 100\text{K}\Omega$. Calculate:

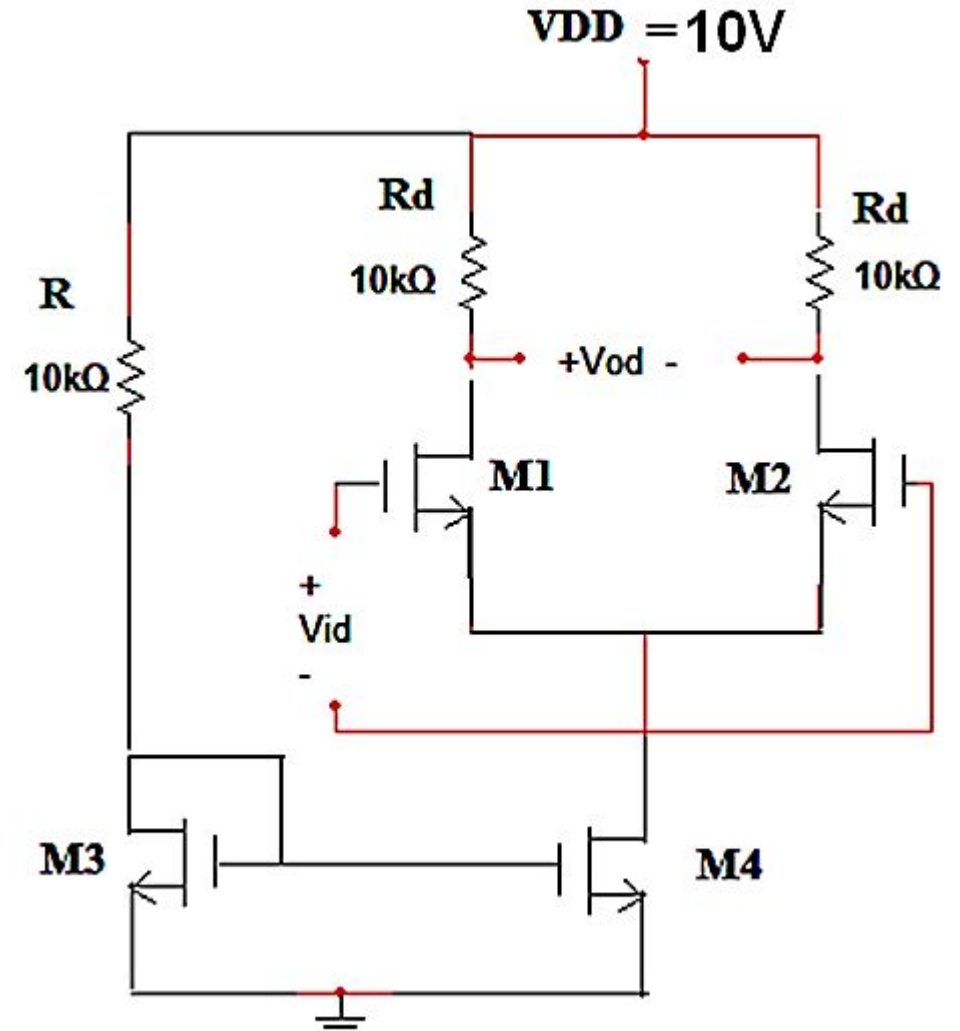- (a) ALL DC Drain currents.
- (b) The differential mode gain (A_{dm})
- (c) The common mode gain (A_c).
- (d) The CMRR in dB.



Solution:

(a) DC Analysis

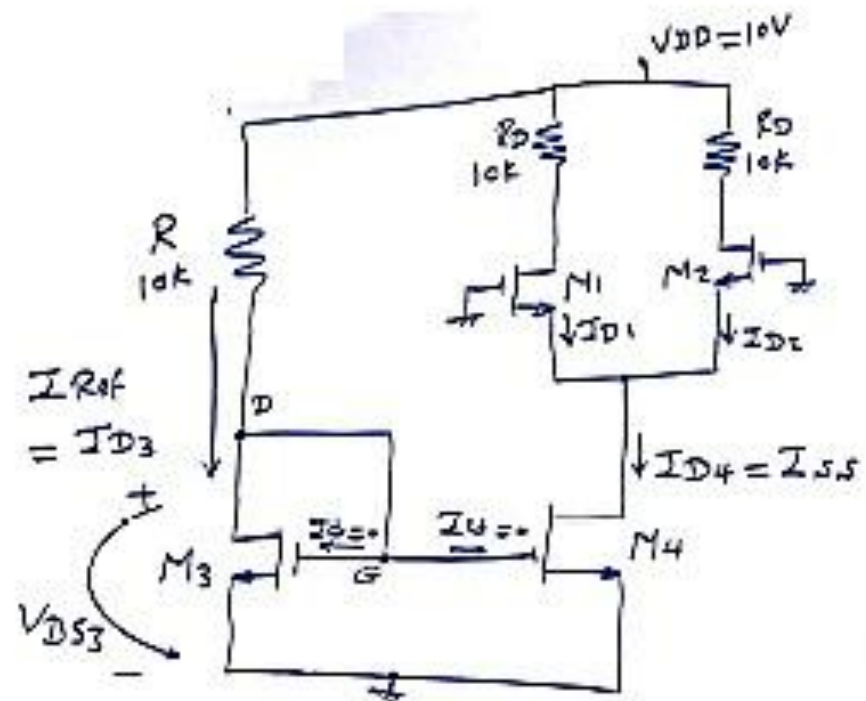

Condition for saturation

$$V_{DS} > V_{GS} - V_T$$
$$\left| \begin{array}{l} V_{GS} = V_G - V_S \\ V_{DS} = V_D - V_S \end{array} \right.$$

For M3

$$V_{GS3} = V_{DS3}$$

\therefore M3 is saturation

$$\text{K.V.L } 10 = 10 I_{D3} + V_{DS3}$$

$$10 = 10 I_{D3} + V_{GS3}$$

$$I_{D3} = \frac{10 - V_{GS3}}{10}$$

$$I_{D3} = 1 - 0.1 V_{GS3} \quad (1)$$

We have $I_{D3} = \frac{K}{2} (V_{GS3} - V_T)^2$

$$1 - 0.1 V_{GS3} = \frac{1}{2} (V_{GS3} - 1)^2$$

$$2 - 0.2 V_{GS3} = V_{GS3}^2 - 2 V_{GS3} + 1$$

$$V_{GS3}^2 - 1.8V_{GS3} - 1 = 0$$

solving

$$V_{GS3} = \begin{cases} 2.2454V \text{ ok } > V_T \\ -0.443V \text{ Rejected } < V_T \end{cases}$$

$$V_{GS3} = 2.2454V$$

Sub. into ①

$$I_{D3} = 0.7755 \text{ mA}$$

$$\therefore V_{GS4} = V_{GS3}$$

$$\therefore I_{D4} = I_{D3}$$

$$\therefore I_{D4} = I_{SS} = 0.7755 \text{ mA}$$

$$\therefore V_{GS1} = V_{GS2}$$

$$\therefore I_{D1} = I_{D2} = \frac{I_{SS}}{2}$$

$$I_{D1} = I_{D2} = 0.3877 \text{ mA}$$

$$* g_m = \sqrt{2K I_D}$$

$$g_{m1} = g_{m2} = g_m = \sqrt{2 \times 2 \times 0.3877}$$

$$g_m = 1.2454 \text{ mS} = 1.2454 \text{ mA/V}$$

$$* r_{ds1} = r_{ds2} = \frac{V_{A1}}{I_{D1}} = \frac{\infty}{I_{D1}} = \infty$$

$$* R_{SS} = r_{ds4} = \frac{V_{A4}}{I_{D4}} = \frac{100V}{0.7755 \text{ mA}} = 128.95 \text{ k}\Omega$$

(b) AC Analysis


$$V_{i1} = V_{ic} + \frac{V_{id}}{2}$$

$$V_{i2} = V_{ic} - \frac{V_{id}}{2}$$

② Differential Mode Gain (AdM)

$$V_{i1} = \frac{V_{id}}{2}, V_{i2} = -\frac{V_{id}}{2} \therefore V_{S=0}$$

Using half-circuit

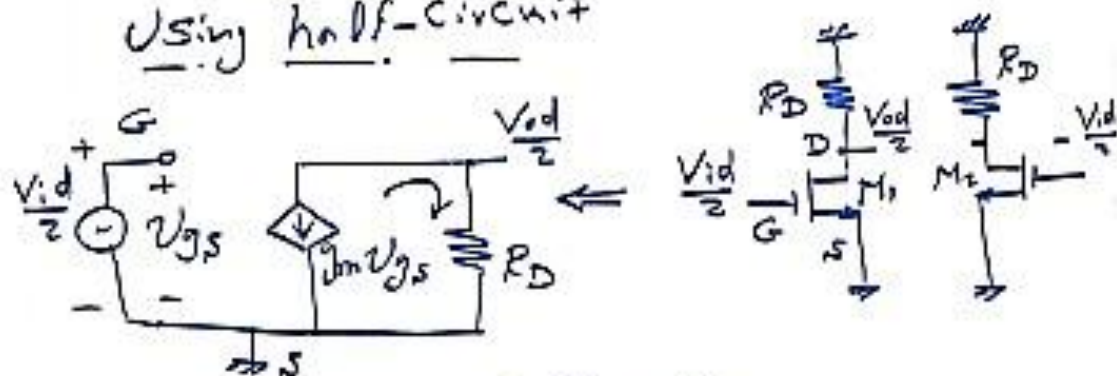

$$A_{dM} = \frac{V_{od/2}}{V_{id/2}} = \frac{-g_m V_{gs} \cdot R_D}{V_{gs}}$$

Gain of
Signal



$$\therefore A_{dM} = -g_m R_D = -1.2454 \times 10 = -12.454$$

③ Common Mode Gain (AcM)

$$V_{i1} = V_{ic}, V_{i2} = V_{ic}$$

$$V_S \neq 0$$

Using half-circuit concept

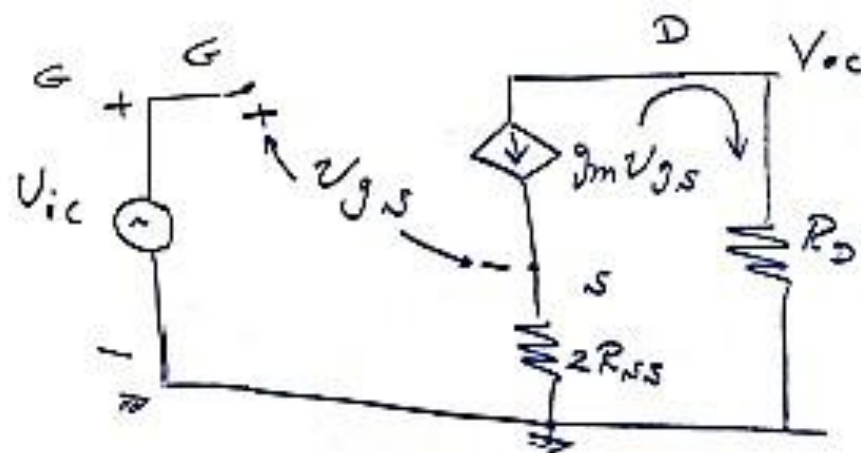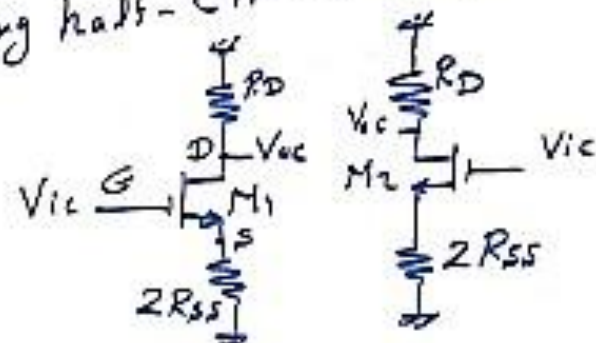

$$A_{CM} = \frac{V_{oc}}{V_{ic}}$$

$$A_{CM} = \frac{-g_m V_{gs} R_D}{V_{gs} + g_m V_{gs} 2R_{SS}}$$

$$A_{CM} = \frac{-g_m R_D V_{gs}}{[1 + 2g_m R_{SS}] V_{gs}}$$

$$A_{CM} = \frac{-g_m R_D}{1 + 2g_m R_{SS}}$$

$$A_{CM} = \frac{-1.2454 \times 10}{1 + 2 \times 1.2454 \times 120.95}$$

$$A_{CM} = -0.0386544$$

Gain of Noise

4 Common Mode Rejection Ratio

$$CMRR = \left| \frac{A_{DM}}{A_{CM}} \right|$$

$$CMRR = \frac{12.454}{0.0386544}$$

$$CMRR = 322.2$$

$$CMRR(dB) = 20 \log 322.2$$

$$CMRR(dB) = 50.2 \text{ dB}$$

Example(2)


Repeat the last example if $V_{A1} = V_{A2} = 100V$ (rds of M1 and M2 are not neglected)

.Solution:(1) DC Drain currents will not changed

$$* r_{ds1} = r_{ds2} = \frac{V_{A1}}{I_{D1}} = \frac{100V}{0.3877} = 257.93K$$

$$r_{ds1} = r_{ds2} = r_{ds} = 257.93k\Omega$$

② Differential Mode gain

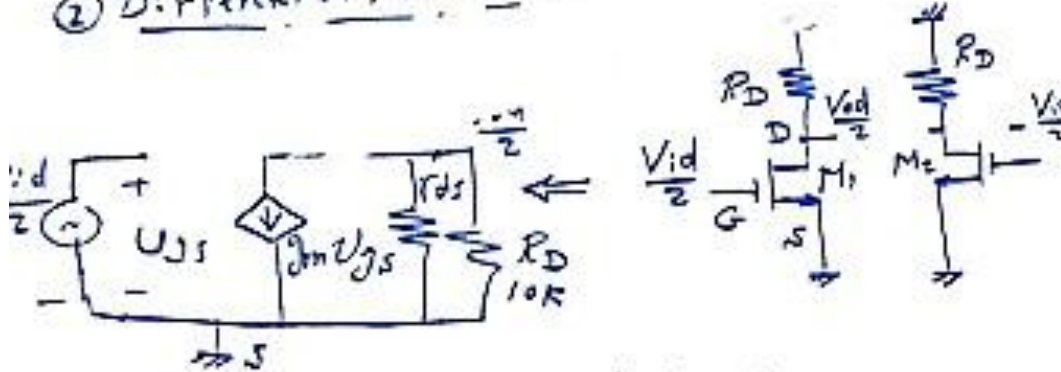

$$A_{dM} = \frac{V_{od12}}{V_{id12}} = \frac{-g_m V_{gs} (r_{ds} \parallel R_D)}{V_{gs}}$$

Gain of Signal



$$\therefore A_{dM} = -9.03 \times 1.2454 = -11.989 \approx -12$$

3] Common Mode gain (ACM)


$U_{in} = U_{ic}$, $U_{iz} = U_{ic}$

$V_S \neq 0$

Using half-circuit concept

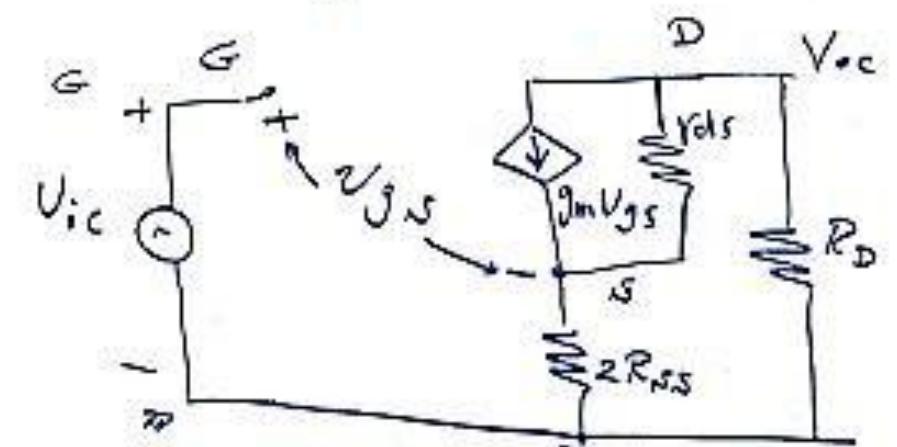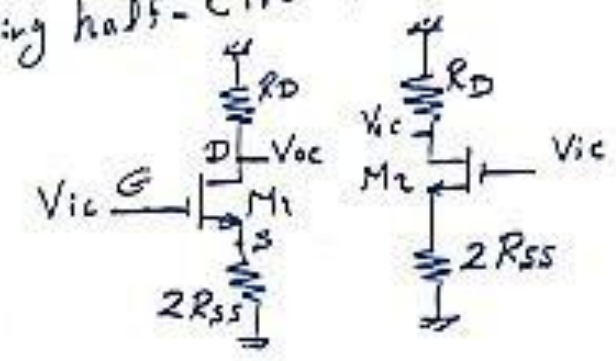

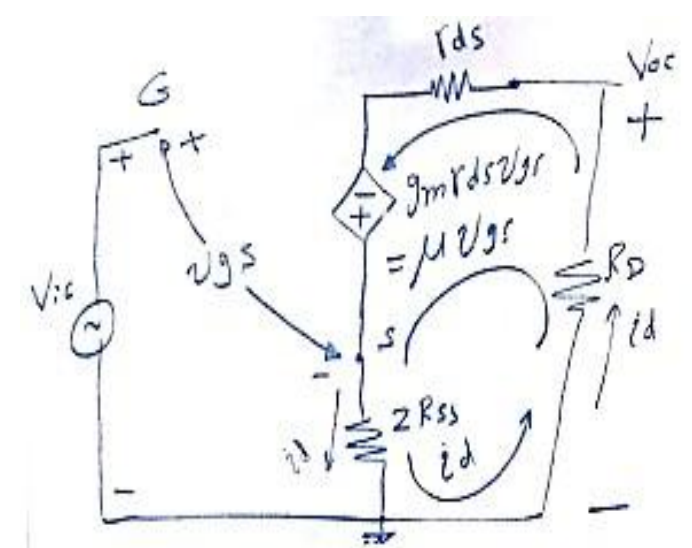Amplification factor $\mu = g_m r_{ds} = 321.23$



$$i_d = \frac{\mu V_{gs}}{r_{ds} + R_D + 2R_{SS}} \quad (1)$$

$$V_{oc} = -i_d R_D$$

$$V_{oc} = \frac{-\mu R_D V_{gs}}{r_{ds} + R_D + 2R_{SS}} \quad (2)$$

$$V_{ic} = V_{gs} + i_d 2R_{SS}$$

$$= V_{gs} + \frac{2\mu R_{SS} V_{gs}}{r_{ds} + R_D + 2R_{SS}}$$

$$V_{ic} = \left[1 + \frac{2\mu R_{SS}}{r_{ds} + R_D + 2R_{SS}} \right] V_{gs} \quad (3)$$

$$V_{ic} = \frac{r_{ds} + R_D + 2R_{SS} + 2\mu R_{SS}}{r_{ds} + R_D + 2R_{SS}} V_{gs} \quad (4)$$

$$(2) \div (4) \quad ACM = \frac{V_{oc}}{V_{ic}} = \frac{-\mu R_D}{r_{ds} + R_D + (1+\mu)2R_{SS}}$$

$$ACM = -0.03744$$

$$(4) \quad CMRR = \frac{12}{0.03744} = 320.5$$


$$CMRR(dB) = 20 \log 320.5 = 50.1 \text{ dB}$$

Example(3)

Analyze the MOS-differential amplifier circuit shown in Figure if M1 and M2 are matched with $g_m = 2\text{mA/V}$ and r_{ds} is neglected.

Calculate:

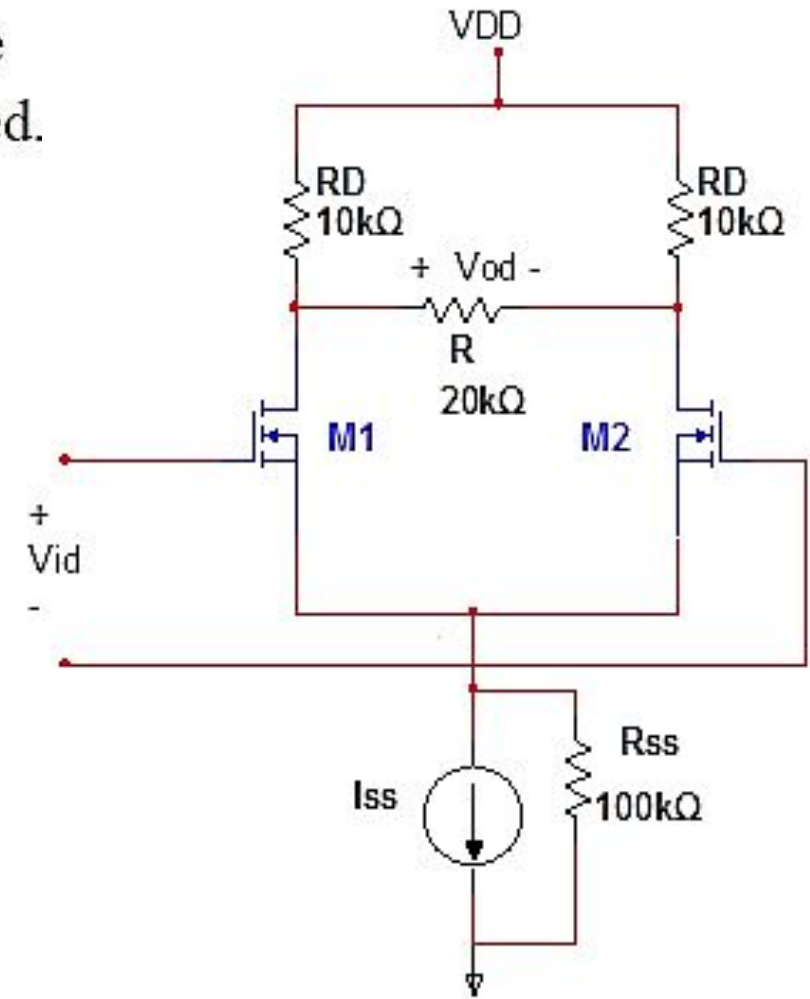
- (a) The differential mode gain (A_{dm}).
- (b) The common mode gain (A_{cm}).
- (c) The CMRR in dB.



Solution:

(a) The differential mode gain (A_{dm}).

Using the half-circuit concept

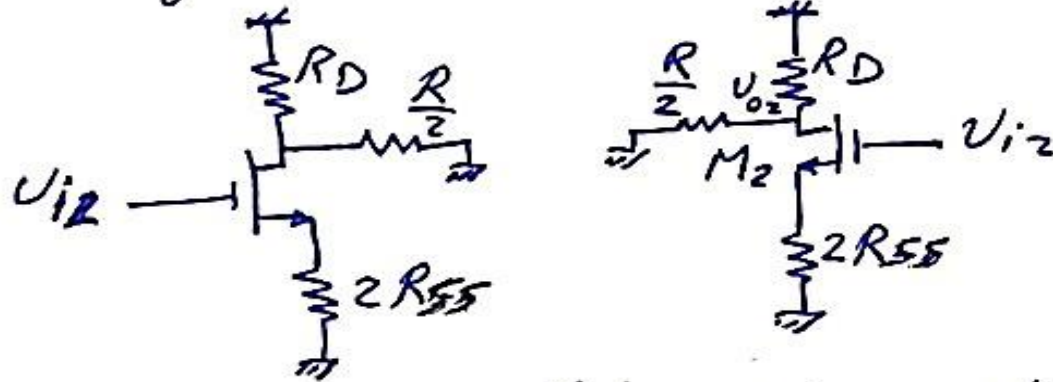


$$v_{i1} = v_{ic} + \frac{v_{id}}{2}, \quad v_{i2} = v_{ic} - \frac{v_{id}}{2}$$

* Differential Mode $v_{i1} = \frac{v_{id}}{2}, \quad v_{i2} = -\frac{v_{id}}{2} \therefore v_{is} = 0$

$$A_{dm} = \frac{v_{od}}{v_{id}} = \frac{v_{od}/2}{v_{id}/2}$$
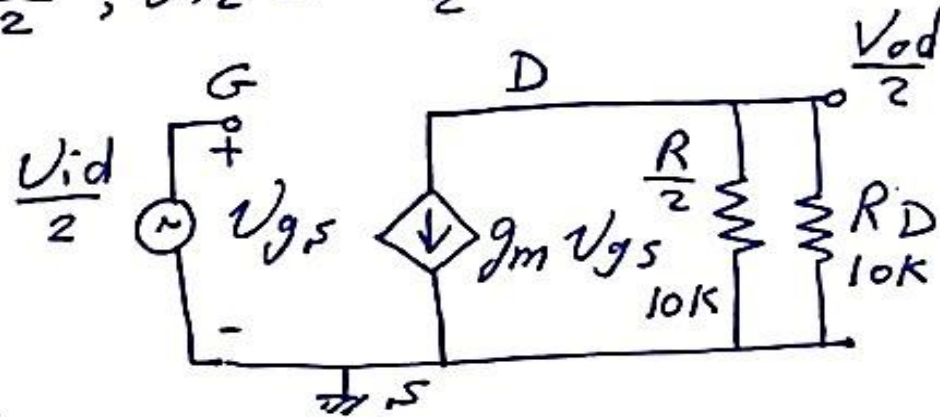
$$A_{dm} = \frac{-g_m v_{gs} (\frac{R}{2} \parallel R_D)}{v_{gs}}$$



$$\boxed{A_{dm} = -g_m (\frac{R}{2} \parallel R_D)} \quad \# \quad A_{dm} = -2 [10 \parallel 10] = -10$$

(b) The common mode gain (A_{cm}).

$$V_{i1} = V_{i2}, V_{i2} = V_{i1}$$

$$\therefore V_i \neq 0$$

$$* V_{i1} = V_{gs} + g_m V_{gs} (2R_{SS})$$

$$\boxed{V_{i1} = [1 + 2g_m R_{SS}] V_{gs}} \quad (1)$$


$$* \boxed{V_{oc} = -g_m V_{gs} \left(\frac{R}{2} \parallel R_D \right)} \quad (2)$$

$$(2) \div (1) \rightarrow \therefore A_{cm} = \frac{V_{oc}}{V_{i1}}$$

$$\boxed{A_{cm} = \frac{-g_m \left(\frac{R}{2} \parallel R_D \right)}{[1 + 2g_m R_{SS}]} \neq}$$

$$A_{cm} = \frac{-2 [10 \parallel 10]}{1 + 2 \times 2 \times 100} = \frac{-10}{1 + 400}$$

$$\boxed{A_{cm} \approx -0.02494} \neq$$

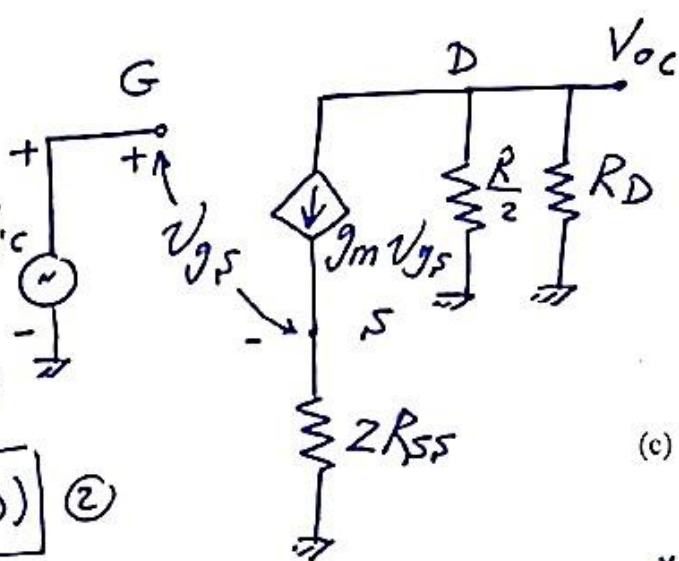

(c) The CMRR in dB.

$$* CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = \frac{10}{0.02494} \approx 401$$

$$* CMRR(dB) = 20 \log \left| \frac{A_{dm}}{A_{cm}} \right| = 20 \log 401$$

$$\boxed{CMRR(dB) = 52.063 \text{ dB}} \neq$$