
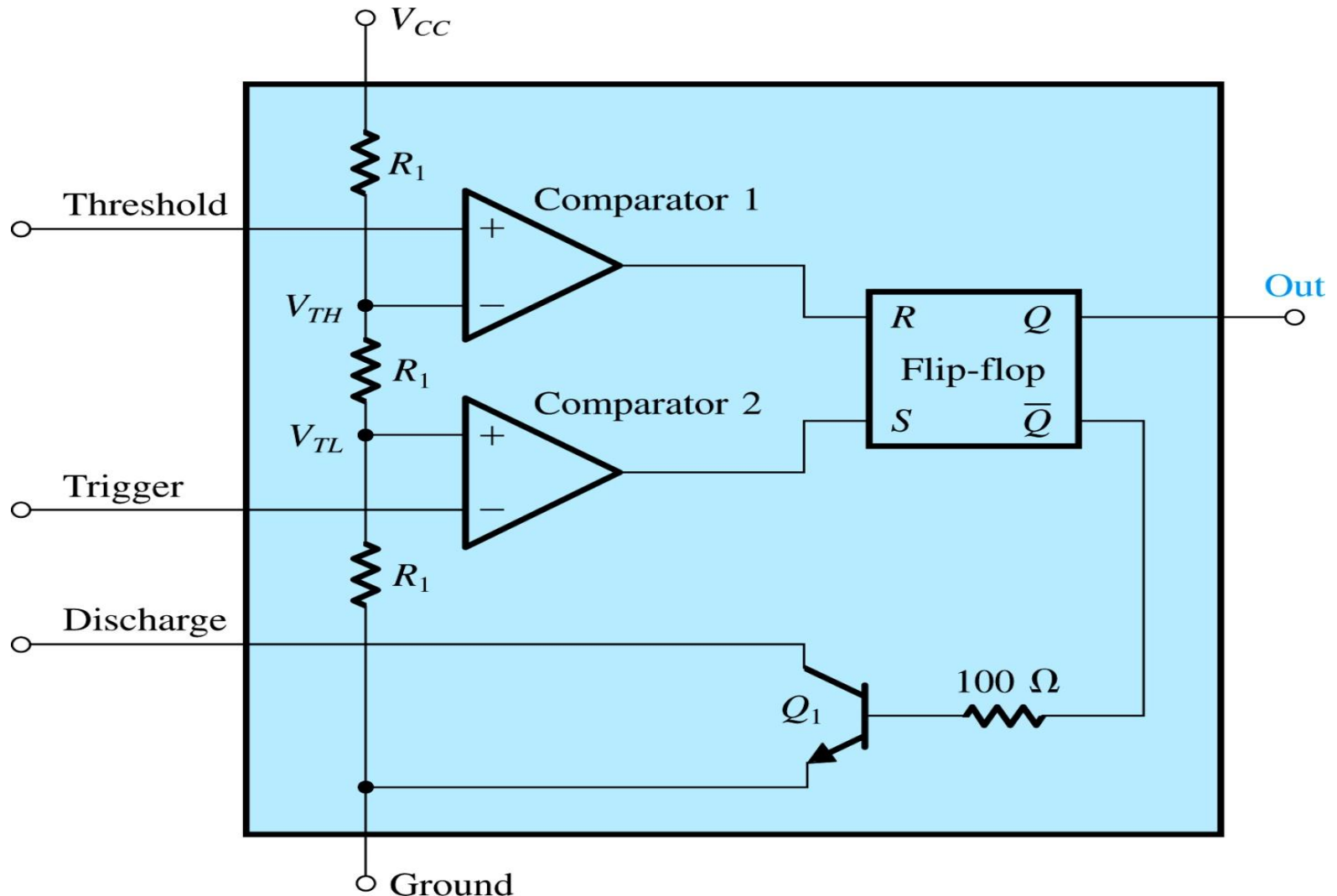


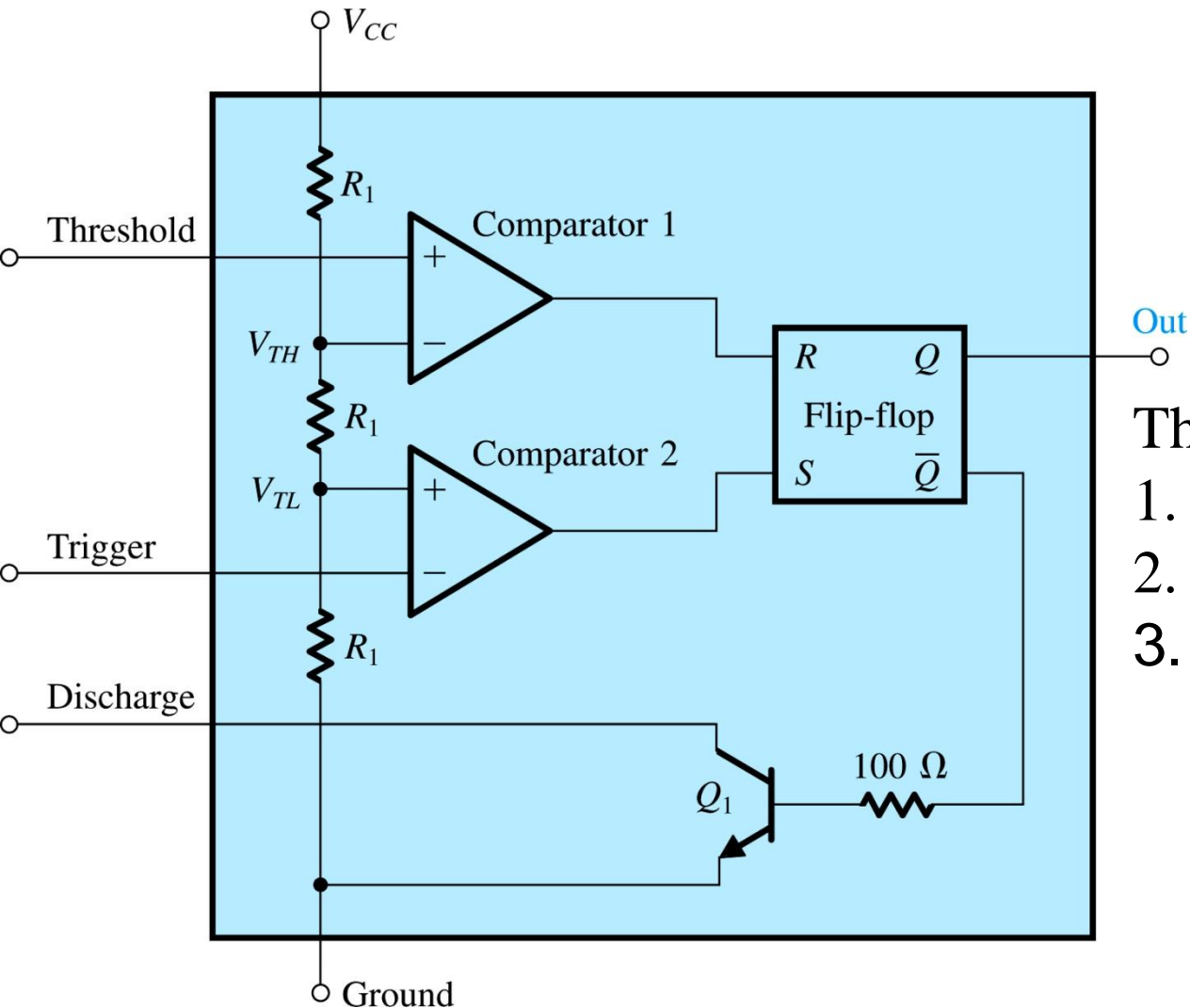Block Diagram Representation of 555 Timer Circuit




Block Diagram Representation of 555 Timer Circuit



The circuit consists of

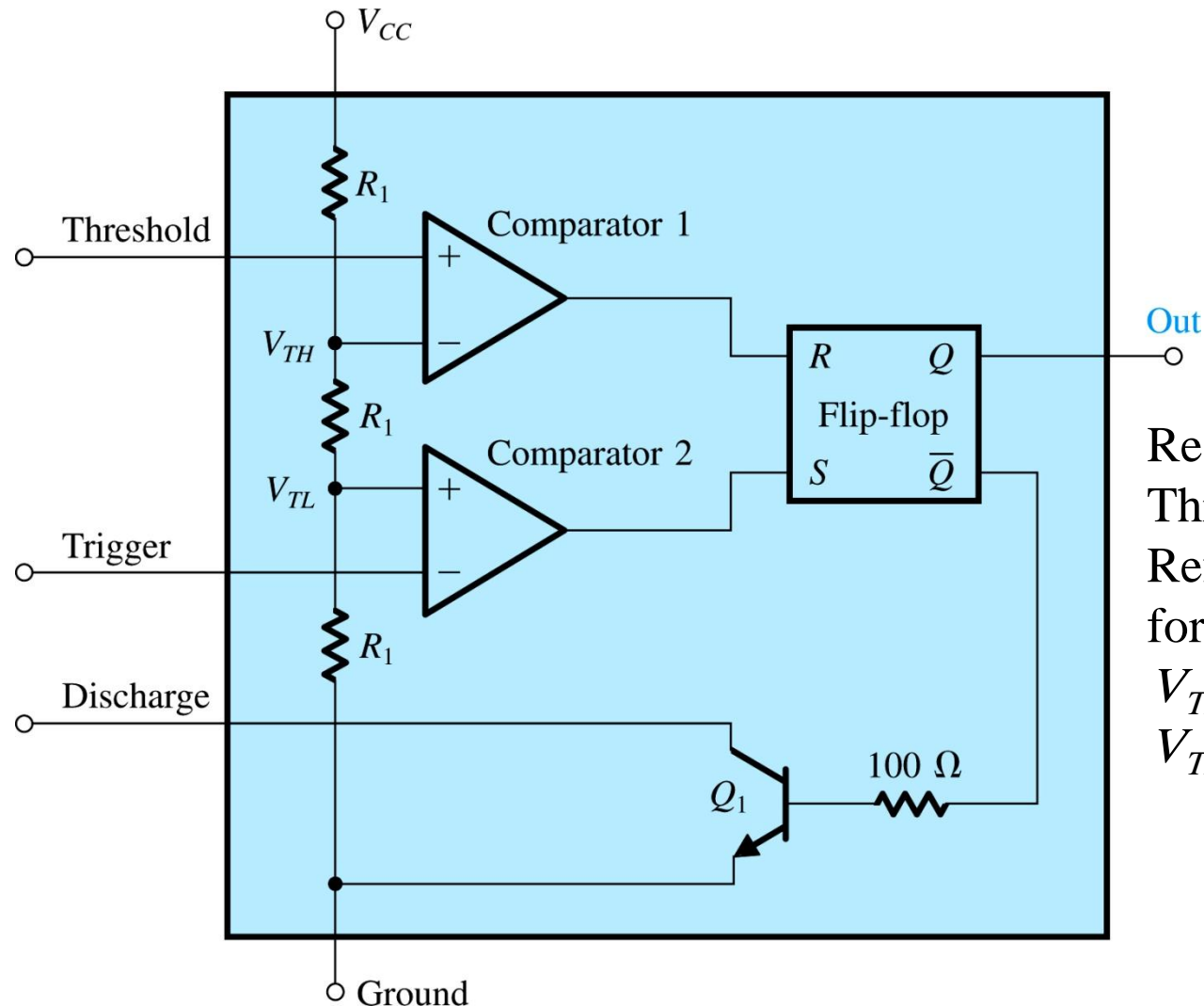
1. Two comparators,
2. SR flip-flop,
3. Transistor Q_1 (switch)

Block Diagram Representation of 555 Timer Circuit




Resistive Voltage Divider,
Three equal-valued resistors
Reference (threshold) voltages
for the two comparators.
 $V_{TH} = 2/3 V_{CC}$ for comparator 1
 $V_{TL} = 1/3 V_{CC}$ for comparator 2

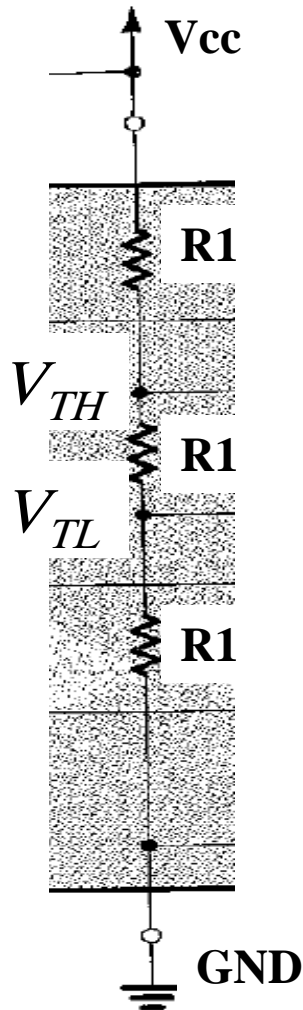Block Diagram Representation of 555 Timer Circuit




- $V_{TH} = 2/3 V_{CC}$ for comparator 1
- $V_{TL} = 1/3 V_{CC}$ for comparator 2

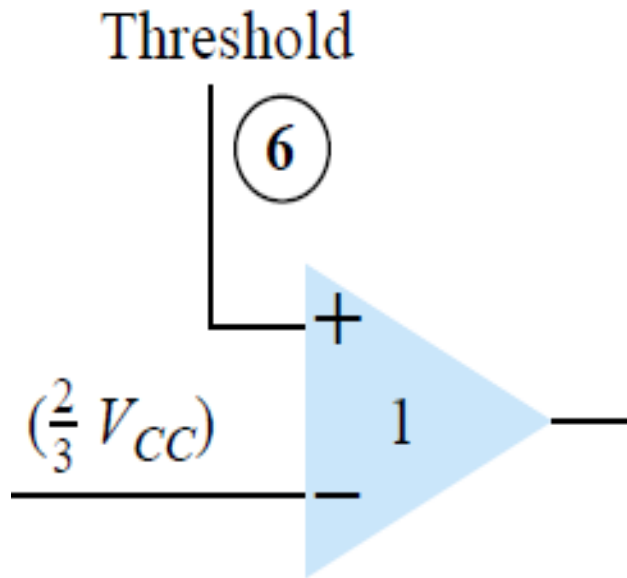Block Diagram Representation of 555 Timer Circuit




- For Comparator 1
- $V_{TH} = \frac{2}{3} V_{CC}$
- *IF $V_6 > V_{TH}$, $V_O = 1$, High*
- *IF $V_6 < V_{TH}$, $V_O = 0$, Low*

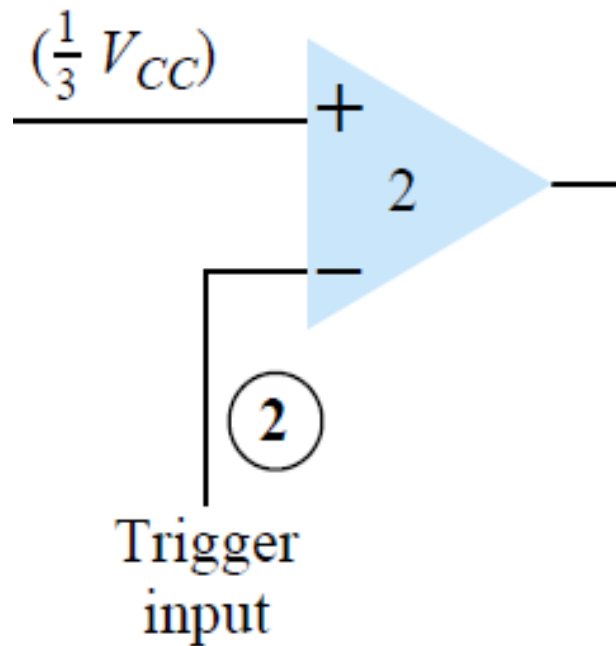Block Diagram Representation of 555 Timer Circuit



- For Comparator 2
- $V_{TL} = 1/3 V_{CC}$
- IF $V_2 > V_{TL}$, $V_O = 0$, Low
- IF $V_2 < V_{TL}$, $V_O = 1$, High

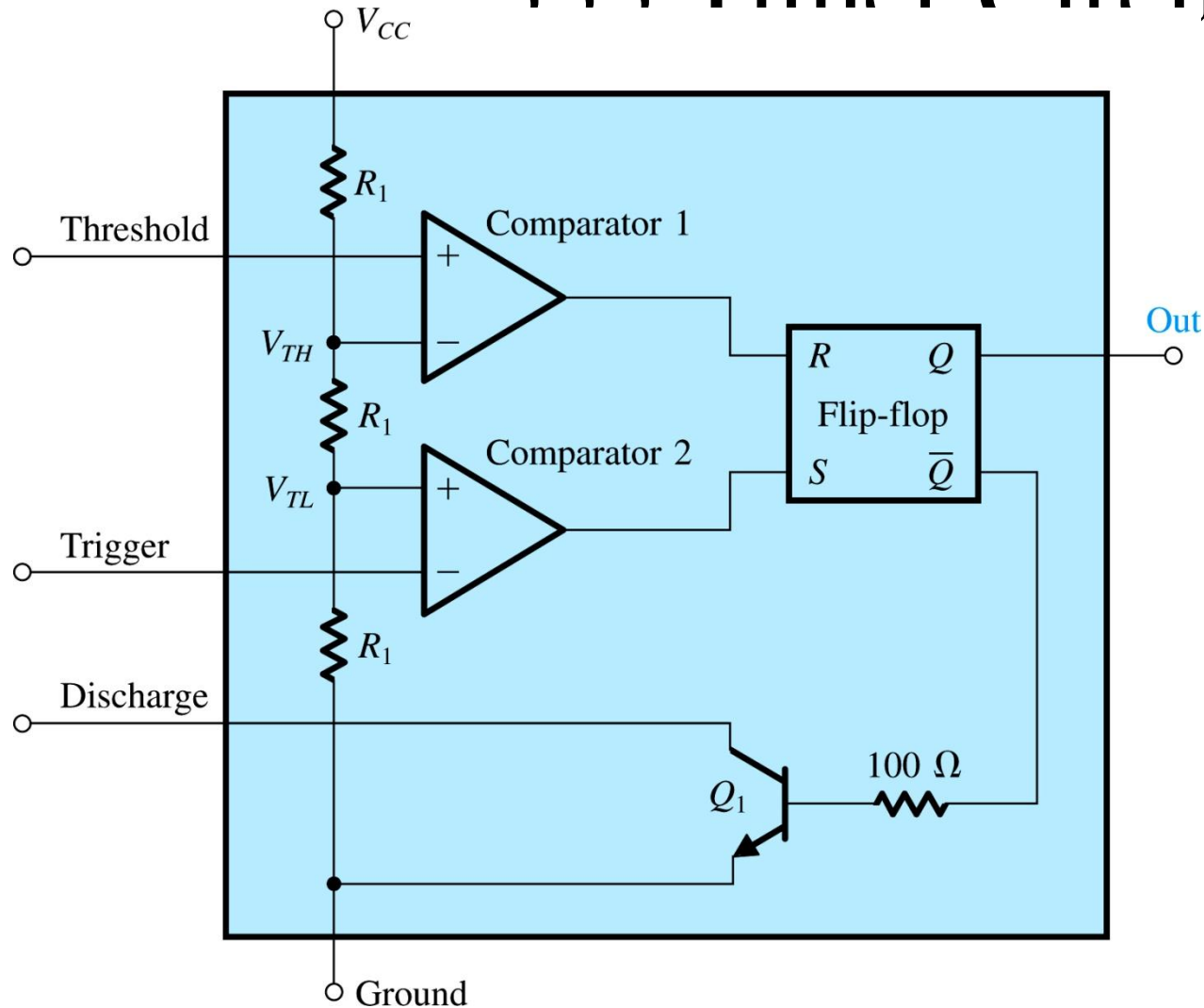
Block Diagram Representation of 555 Timer Circuit



Truth Table for SR Flip Flop

S	R	Q^+
0	0	Q
0	1	0
1	0	1
1	1	X

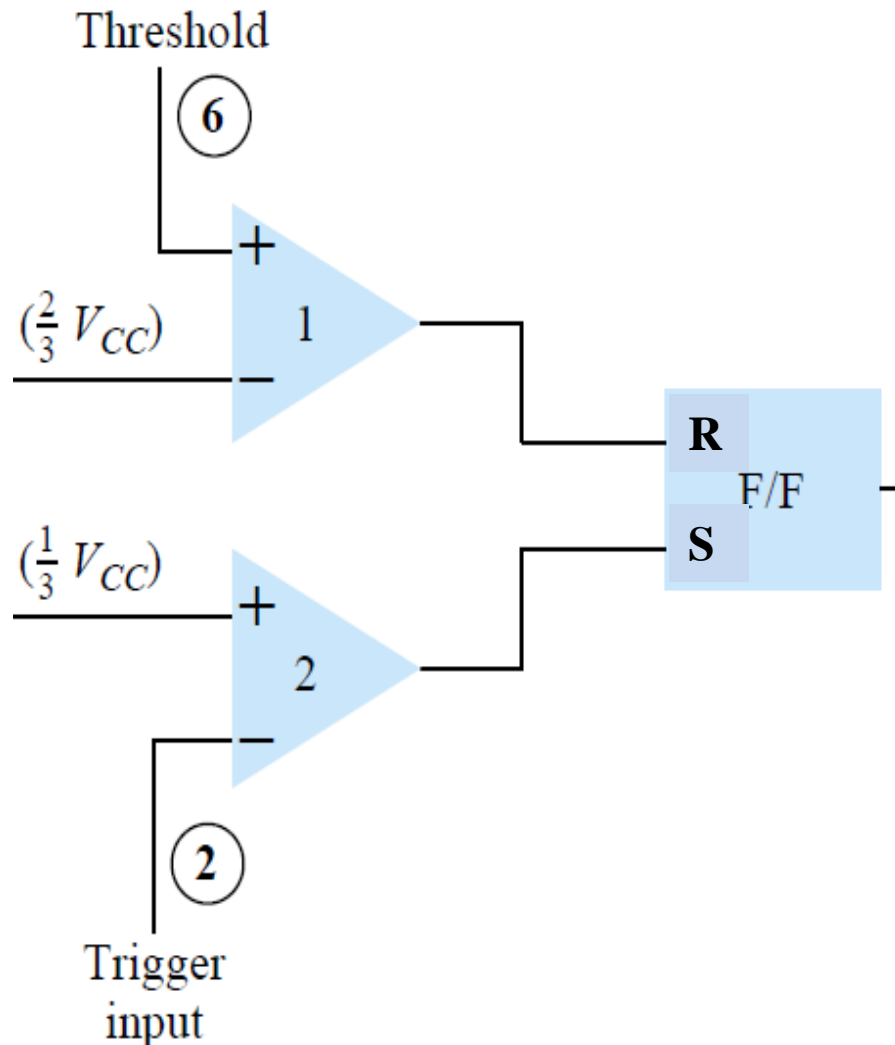Block Diagram Representation of 555 Timer Circuit



For Comparator 1

- $V_{TH} = \frac{2}{3} V_{CC}$
- *IF $V_6 > V_{TH}$, $V_O = 1$, High*
- *IF $V_6 < V_{TH}$, $V_O = 0$, Low*


For Comparator 2

- $V_{TL} = \frac{1}{3} V_{CC}$
- *IF $V_2 > V_{TL}$, $V_O = 0$, Low*
- *IF $V_2 < V_{TL}$, $V_O = 1$, High*

For RS Latch

- *$Q = 0$, $Q^- = 1$*
- *$Q = 1$, $Q^- = 0$*

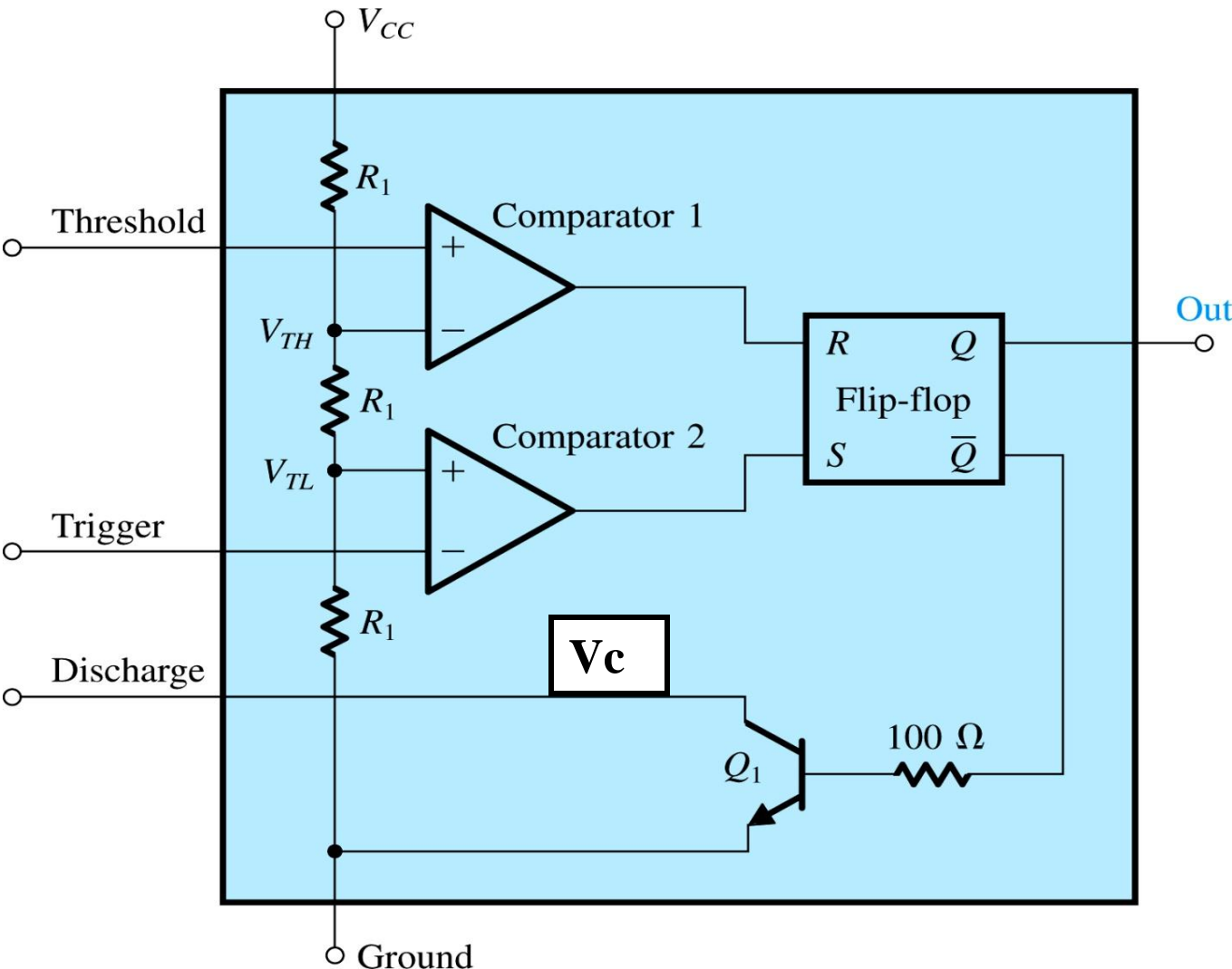
Block Diagram Representation of 555 Timer Circuit




For RS Latch

- $Q = 0, \bar{Q} = 1$
- $V_o = 0$
- Q1 is ON
- $V_c = V_{sat} = 0.2$
- $Q = 1, \bar{Q} = 0$
- $V_o = 1$
- Q1 is OFF
- $V_c = V_{off} = V_{cc}$

Monostable Multivibrator (555 IC)

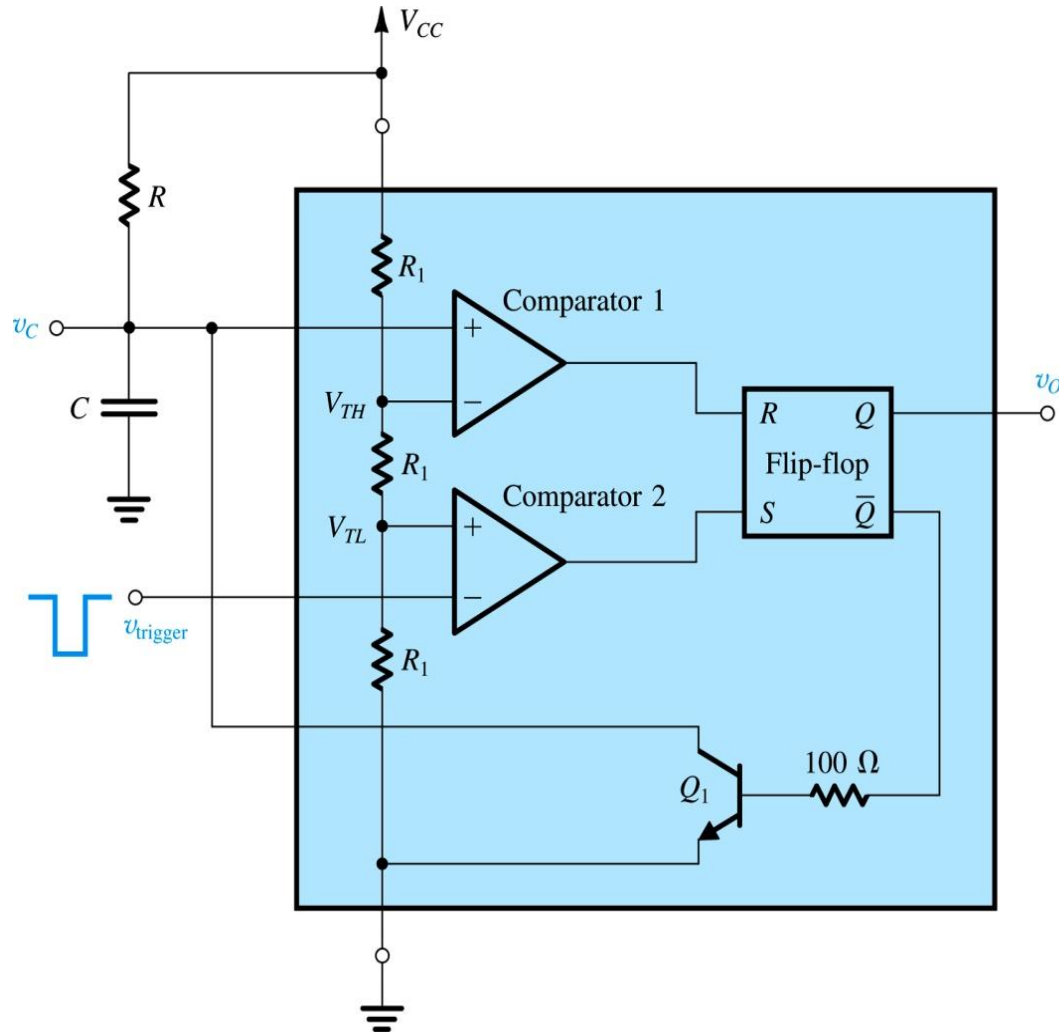

(a)

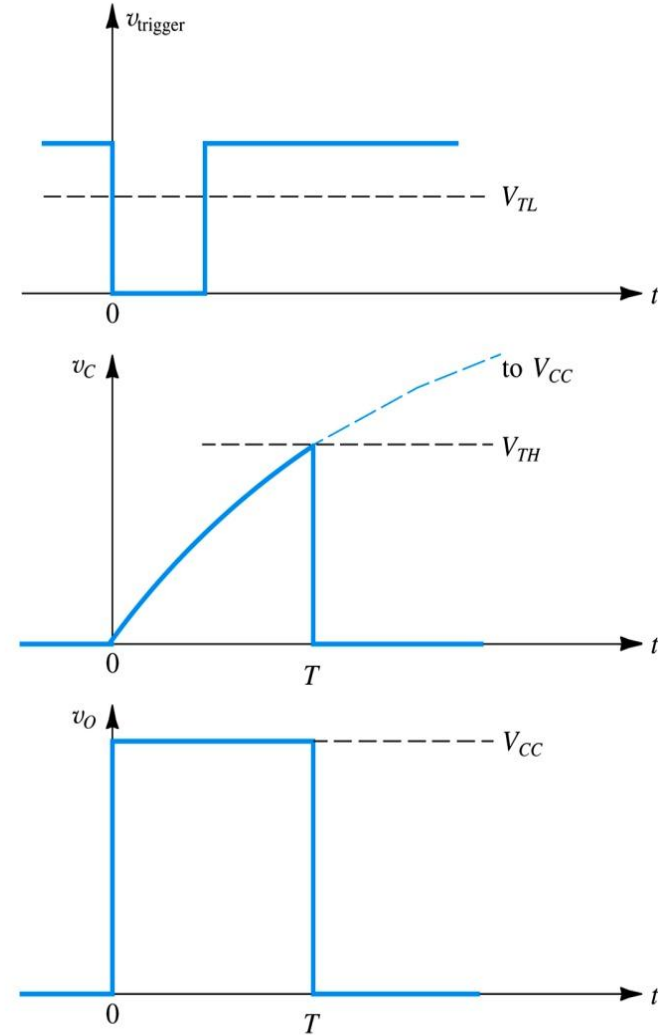


(b)

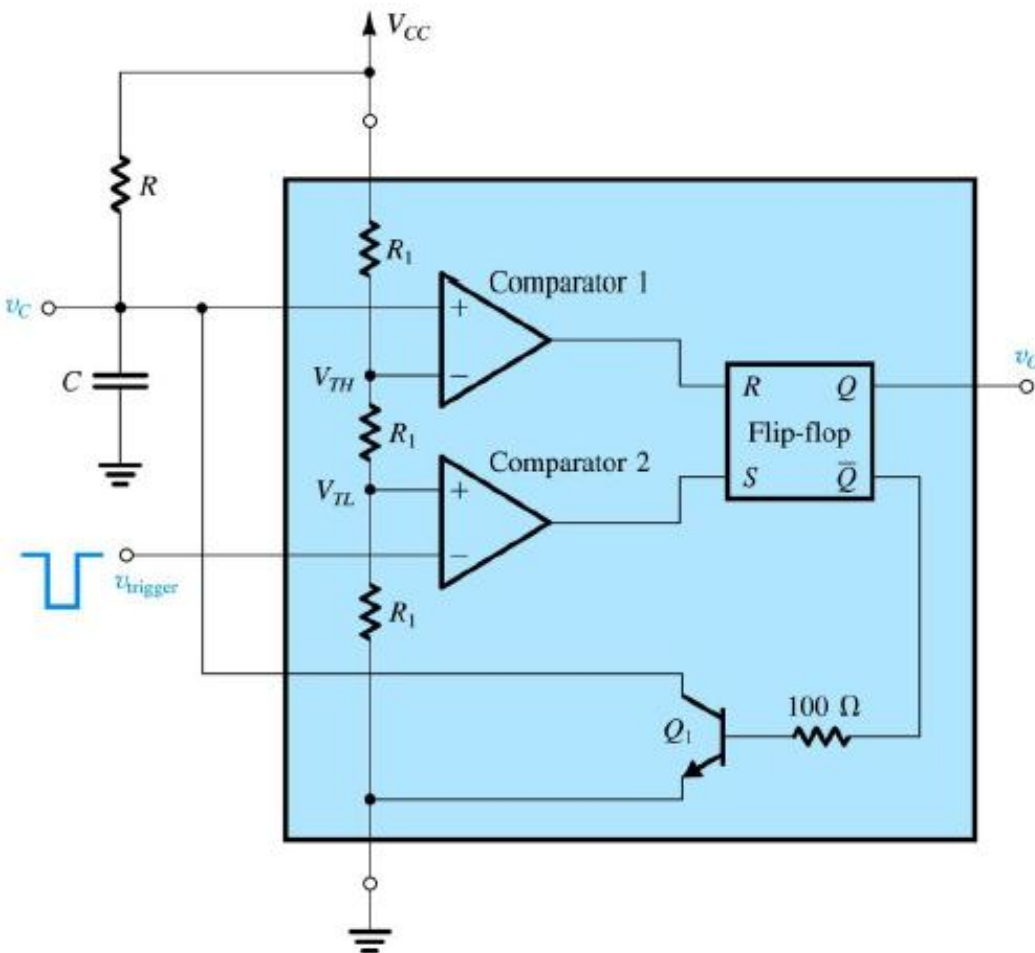- (a) The 555 timer connected to implement a monostable multivibrator.
(b) Waveforms of the circuit in.

Monostable Multivibrator (555 IC)

In the stable state , $V_{trigger} = 1$, high



SR flip-flop is in the **Reset State**,

$Q = 0$, output will be low

$\bar{Q} = 1$, output will be high

Turning ON transistor Q_1

Q_1 is saturated

V_C will be close to 0 V,

Comparator 1 output will be low

$V_{trigger} = 1$, high (greater than V_{TL})

Comparator 2 output will be low


SR flip-flop is in the reset state,

$Q = 0$, low

$V_o = 0\text{ V}$, low

Monostable Multivibrator (555 IC)

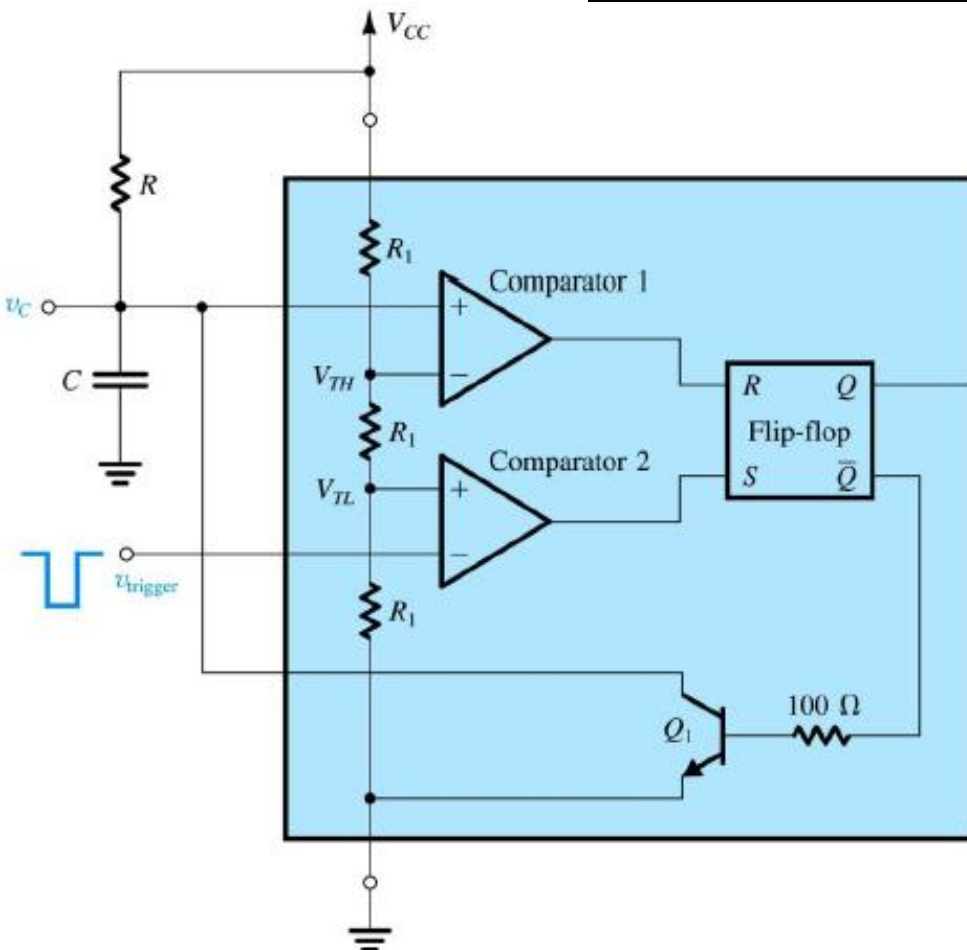
Triggering monostable multivibrator, a negative input pulse is applied on $V_{trigger}$



$V_{trigger} = 0$, low (lower than V_{TL})
Comparator 2 output will be high
SR flip-flop is in the **Set State**,
 $Q = 1$, output will be high
 $\bar{Q} = 0$, output will be low
Turning OFF transistor Q_1
Capacitor C now begins to charge up through resistor R , and its voltage V_C rises exponentially toward V_{CC} .
Monostable multivibrator is now in its **Quasi-Stable state**.

Monostable Multivibrator (555 IC)

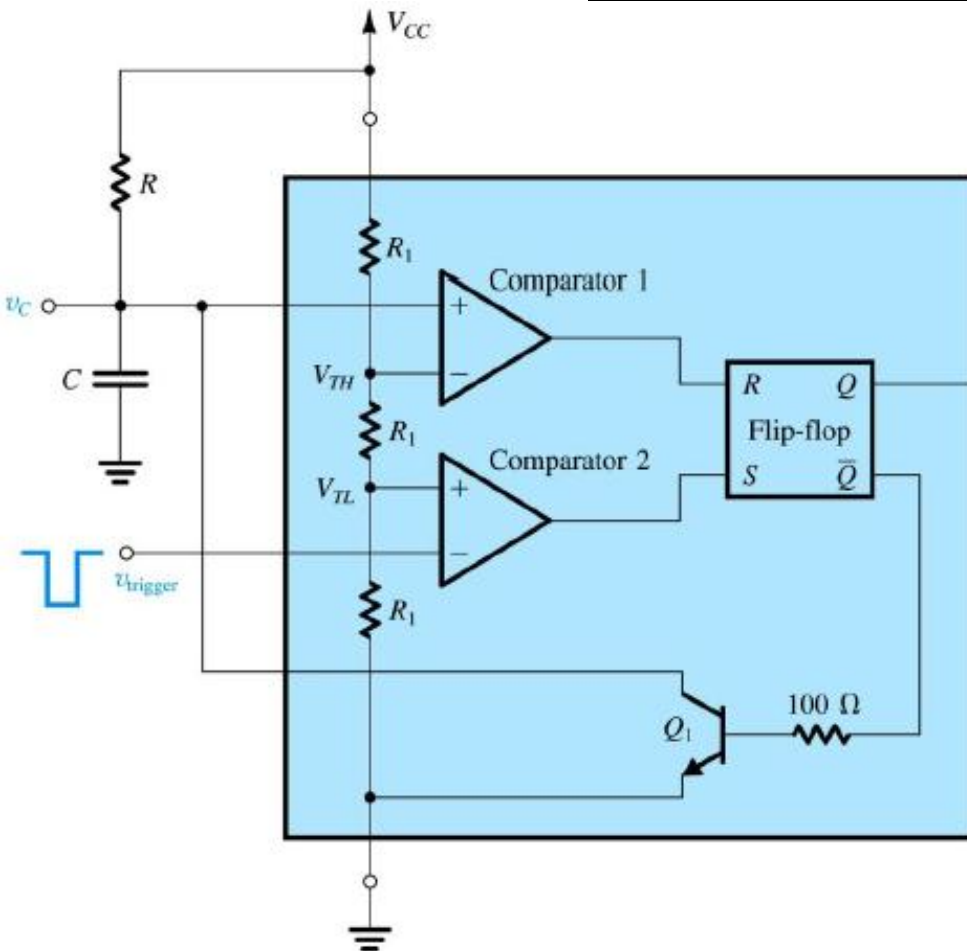Triggering monostable multivibrator, a negative input pulse is applied on $V_{trigger}$



Charging V_C until reaches, begins to exceed, V_{TH} ,

Comparator 1 output will be high
SR flip-flop is in the **Ret State**,

$Q = 0$, LOW

$Q^- = 1$, High

Transistor Q_1 on ($V_{sat} = 0.2V$)

Transistor Q_1 rapidly discharges capacitor C , causing V_C to go to $0V$.


When the flip-flop is reset

Q output goes low,

$V_O = 0V$.

Monostable Multivibrator (555 IC)

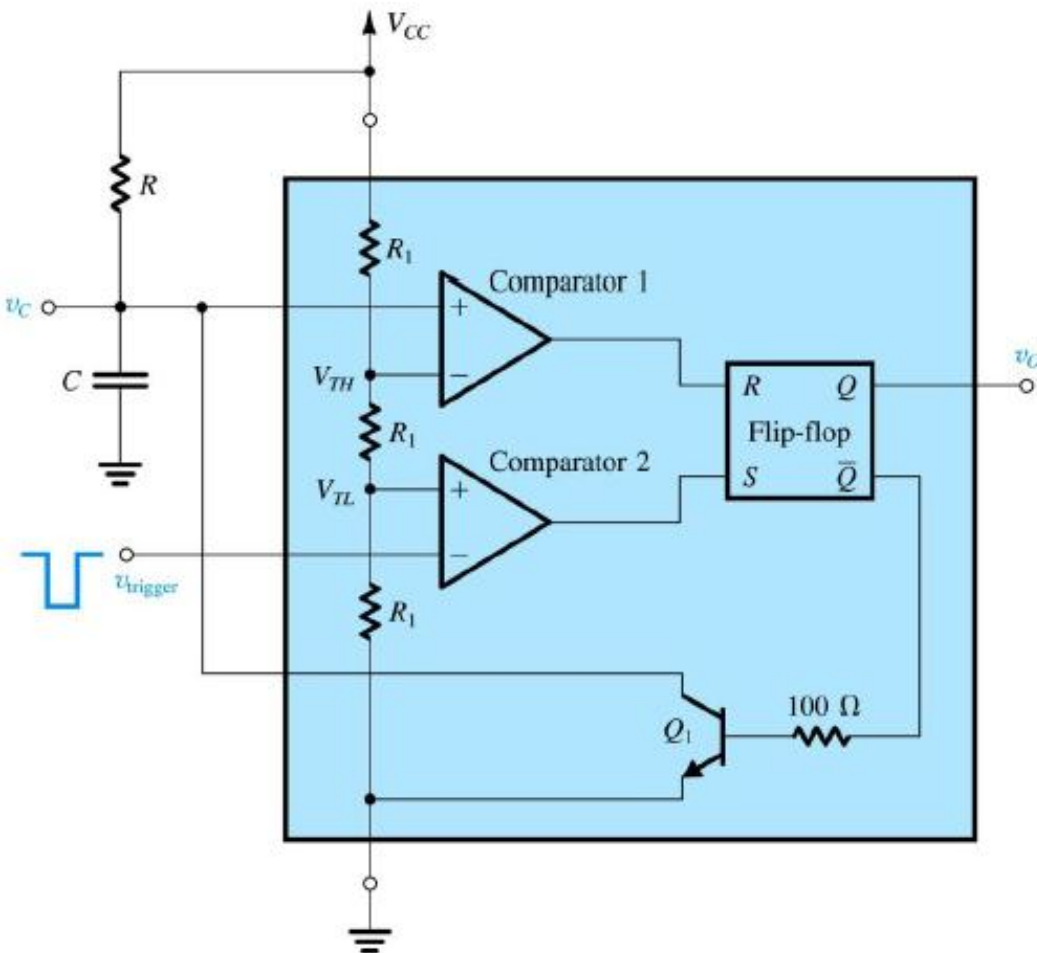
Triggering monostable multivibrator, a negative input pulse is applied on $V_{trigger}$




When the flip-flop is **Reset** its Q output goes low, V_O goes back to 0 V.

The monostable multivibrator is now back in its stable state. It is ready to receive a new triggering pulse.

Monostable Multivibrator (555 IC)

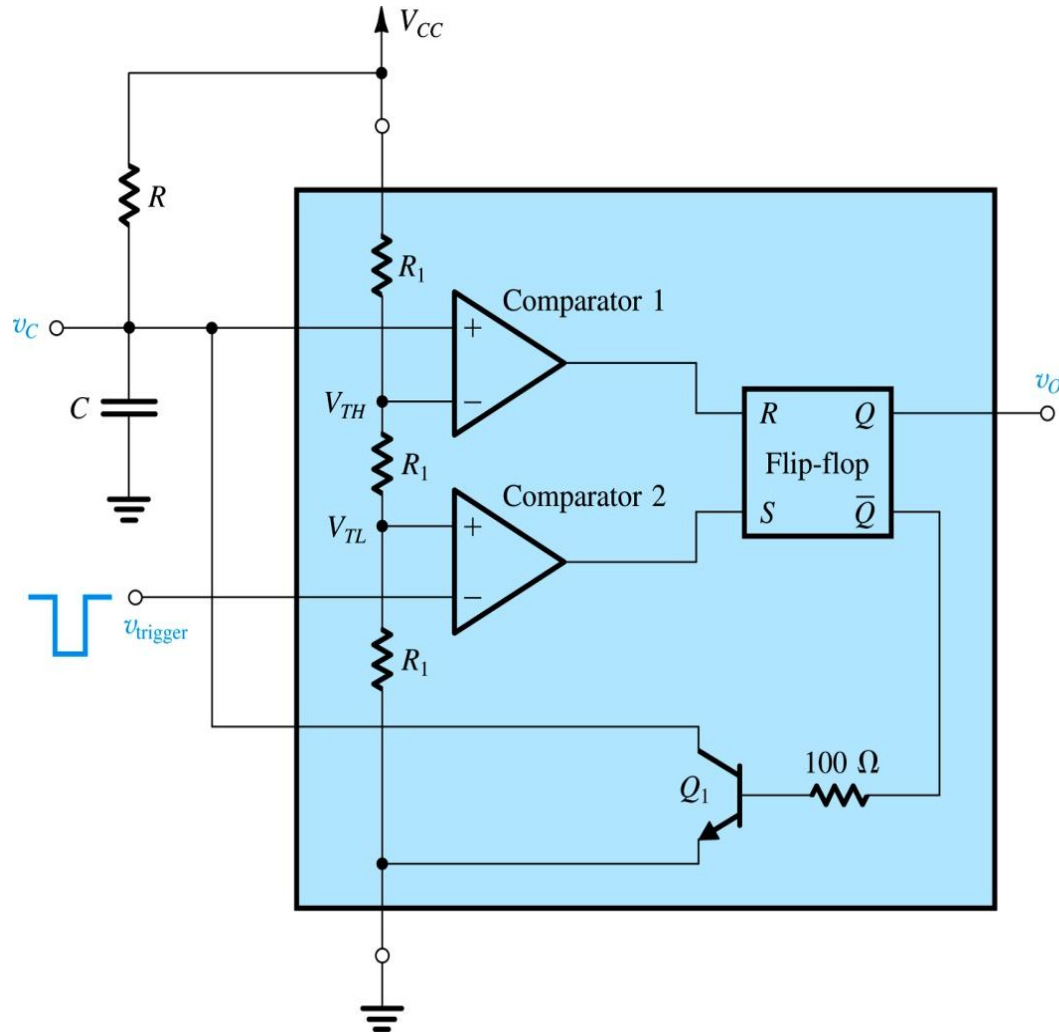

(a)

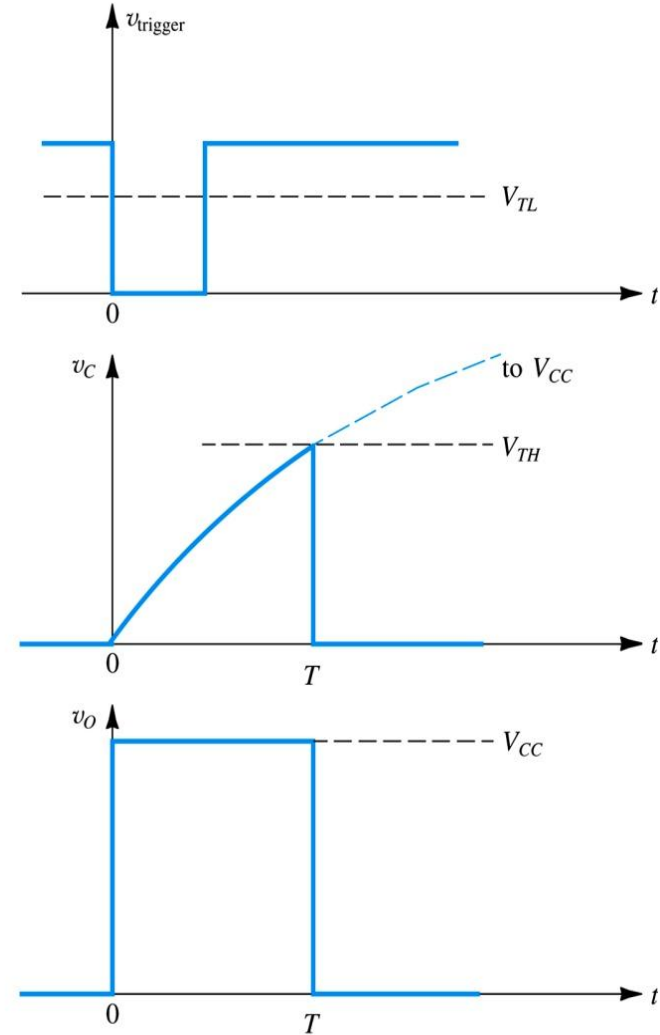

(b)

- (a) The 555 timer connected to implement a monostable multivibrator.
(b) Waveforms of the circuit in.

Monostable Multivibrator (555 IC)

The exponential waveform of V_c can be expressed as

$$V_C = V_{final} - (V_{final} - V_{initial})e^{-t/\tau}$$

$$V_C = V_{CC} - (V_{CC} - 0)e^{-t/\tau}$$


$$V_C = V_{CC}(1 - e^{-t/\tau})$$

where $\tau = RC$


$$V_C = V_{TH} = \frac{2}{3}V_{CC} \quad \text{at} \quad t = T$$

$$\frac{2}{3}V_{CC} = V_{CC}(1 - e^{-T/\tau})$$

$$T = RC \ln 3 \cong 1.1RC$$

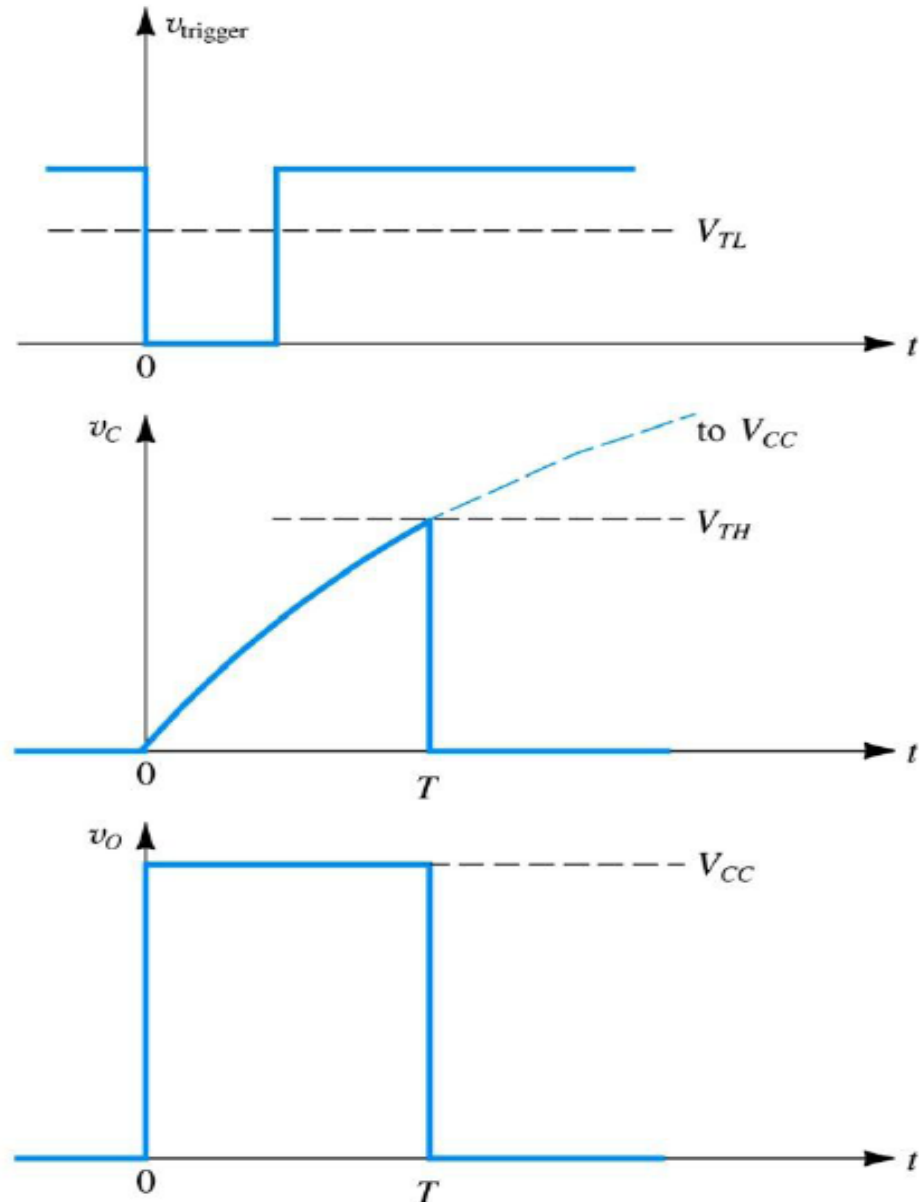


Monostable Multivibrator (555 IC)

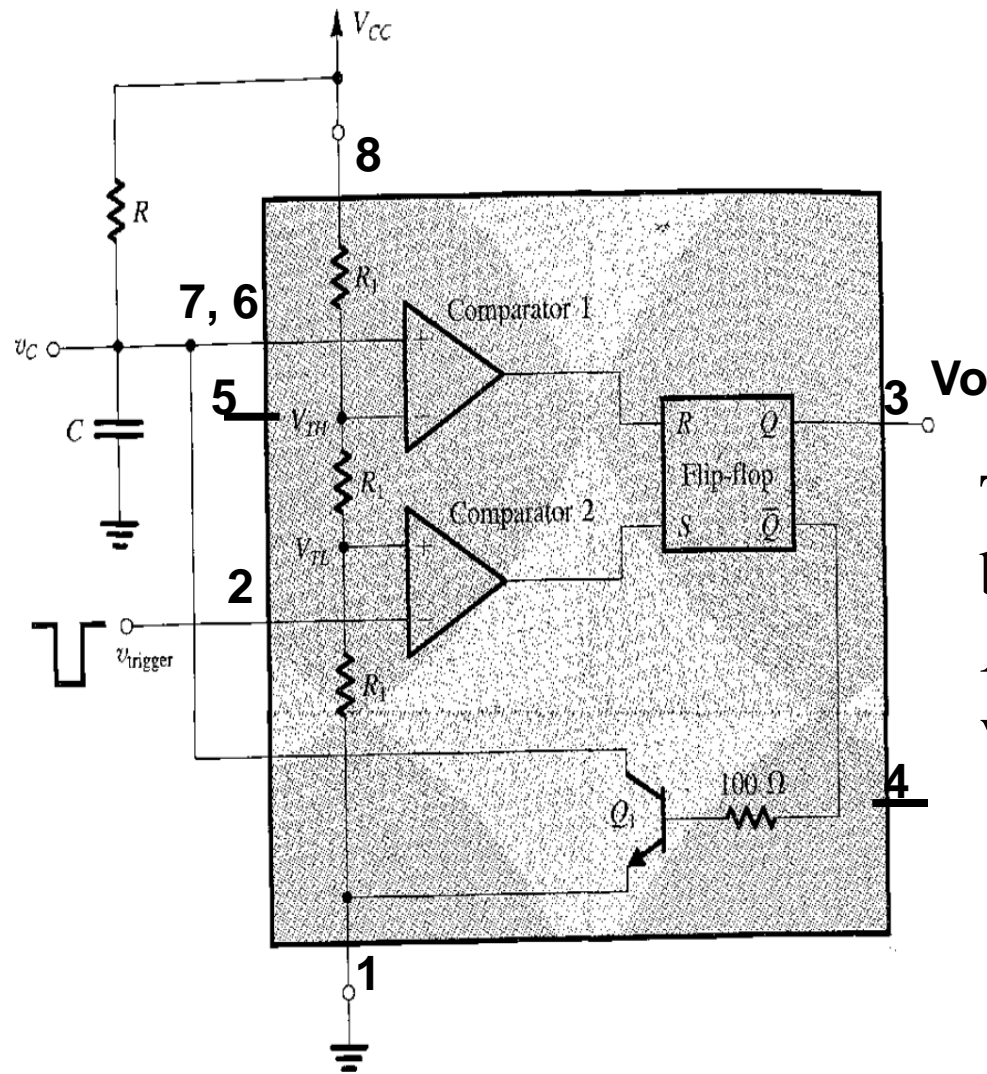

$$T = RC \ln 3 \cong 1.1RC$$

Thus the pulse width is determined by the external components C and R , which can be selected to have values as precise as desired.

Monostable Multivibrator (555 IC)

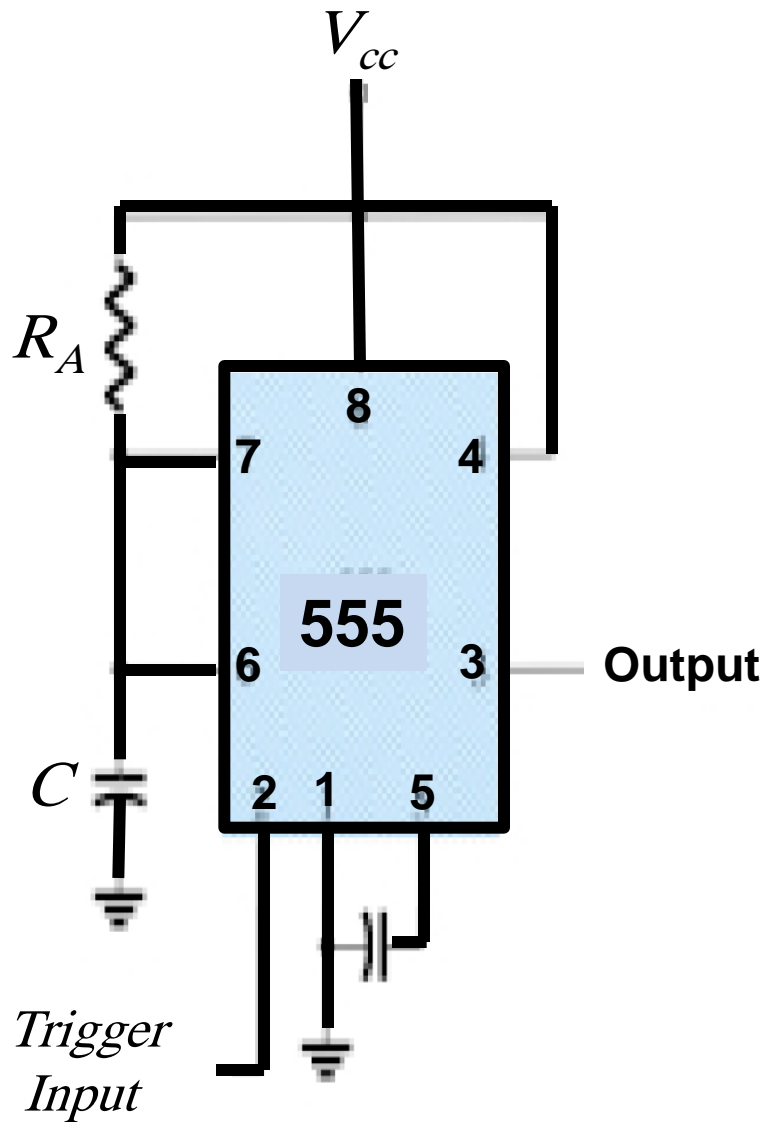


*High
Trigger*




*Input Triggering
-ve edge*

Output

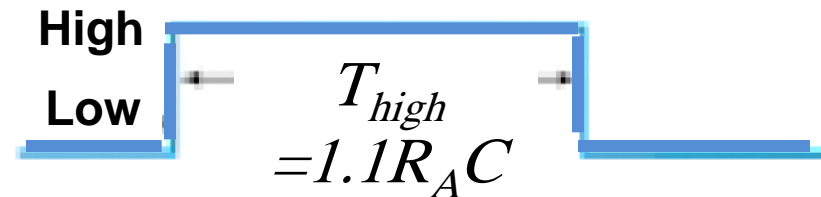


Monostable Multivibrator (555 IC)

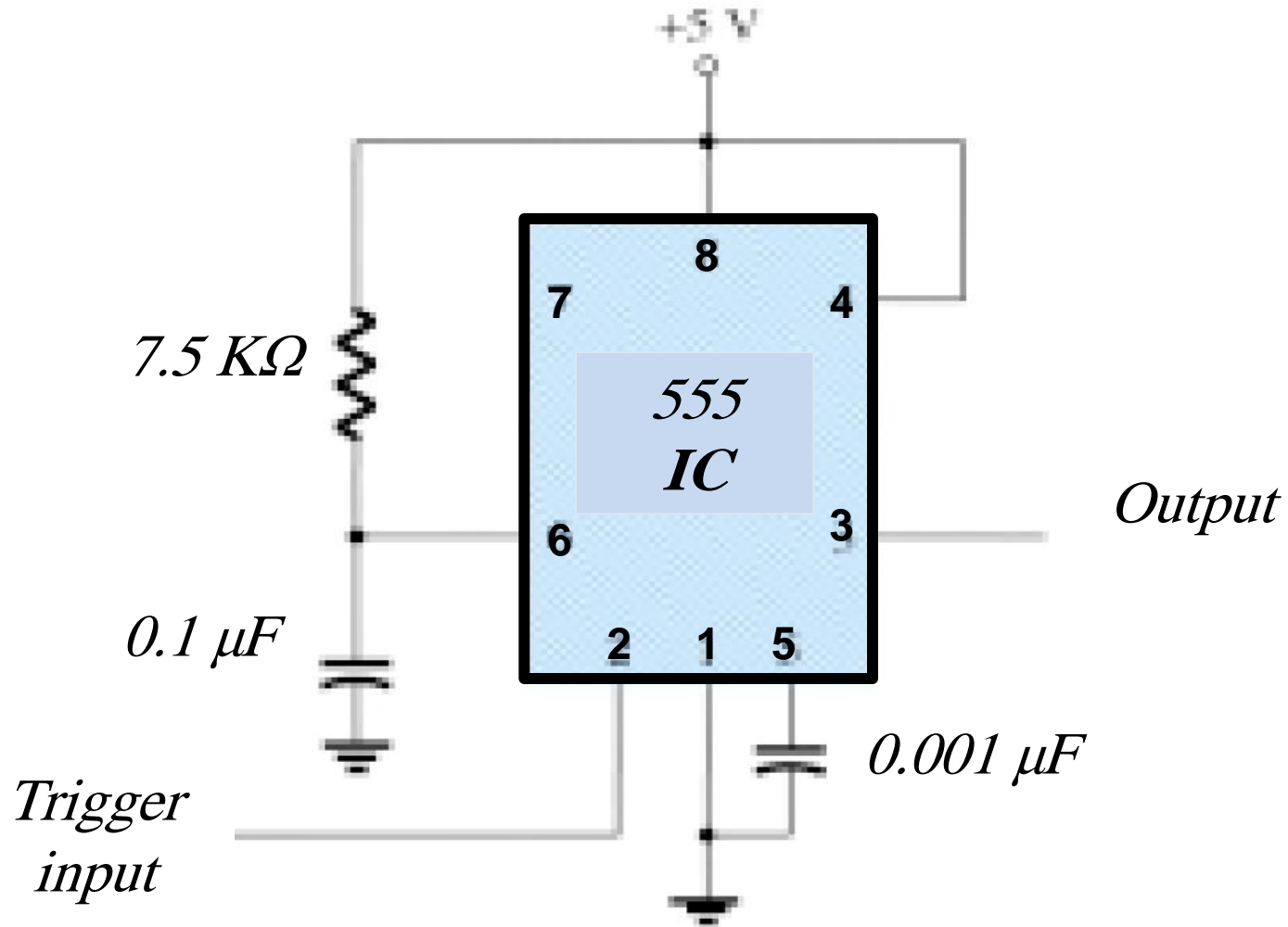


$$T_{\text{high}} = 1.1R_A C = 1.1(7.5 \times 10^3)(0.1 \times 10^{-6}) = \mathbf{0.825 \text{ ms}}$$

Astable Multivibrator (555 IC)

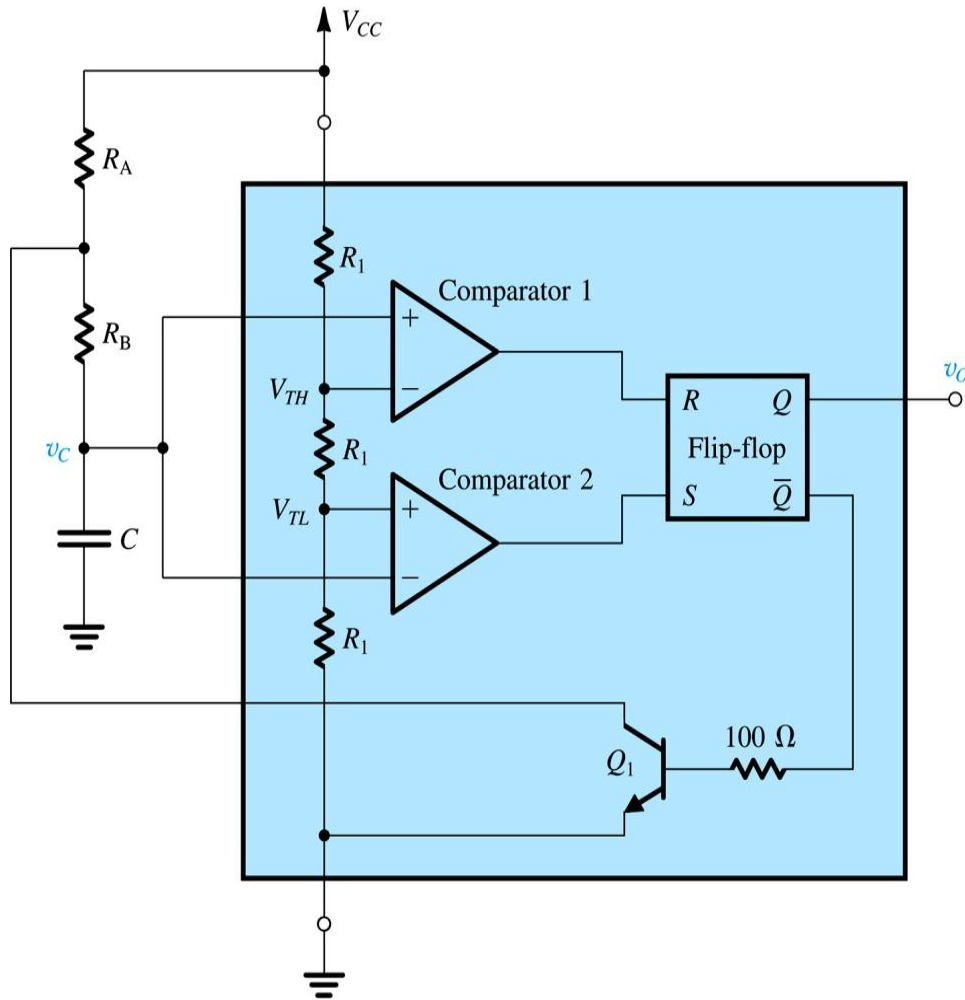

(a)

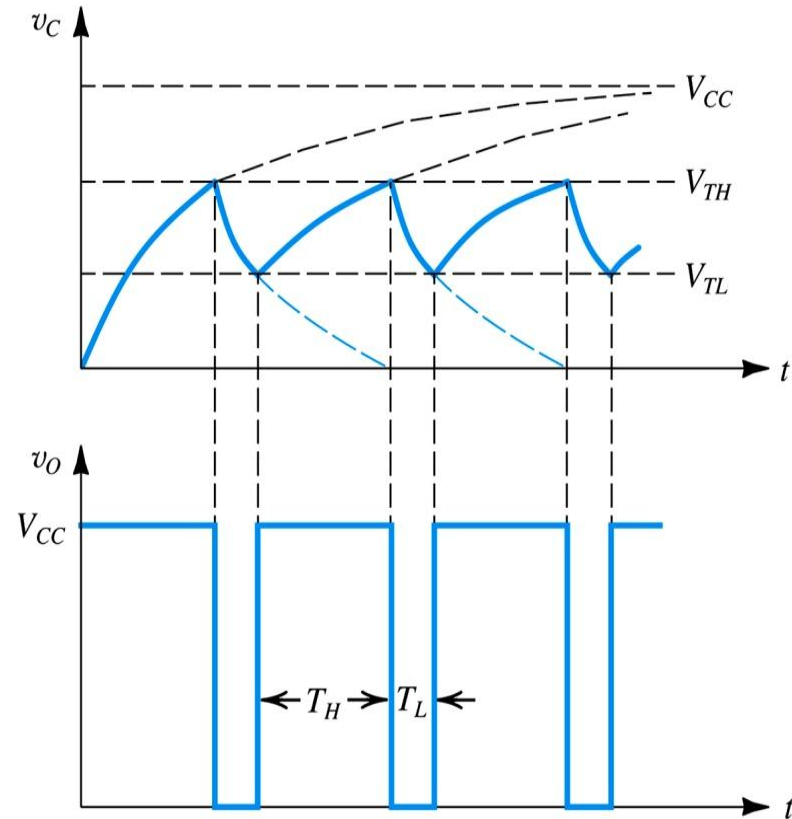

(b)

- (a) 555 timer connected to implement an astable multivibrator.
(b) Waveforms of the circuit in.

Astable Multivibrator (555 IC)

The expression of T_H
 C charges from V_{TL} to V_{CC}

$$V_C = V_{final} - (V_{final} - V_{initial})e^{-t/\tau}$$


$$V_C = V_{CC} - (V_{CC} - V_{TL})e^{-t/\tau}$$

$$V_C = V_{CC} - (V_{CC} - \frac{1}{3}V_{CC})e^{-t/\tau}$$

where $\tau = (R_A + R_B)C$

$$V_C = V_{TH} = \frac{2}{3}V_{CC} \quad \text{at} \quad t = T_H$$

$$T_H = 0.69(R_A + R_B)C$$

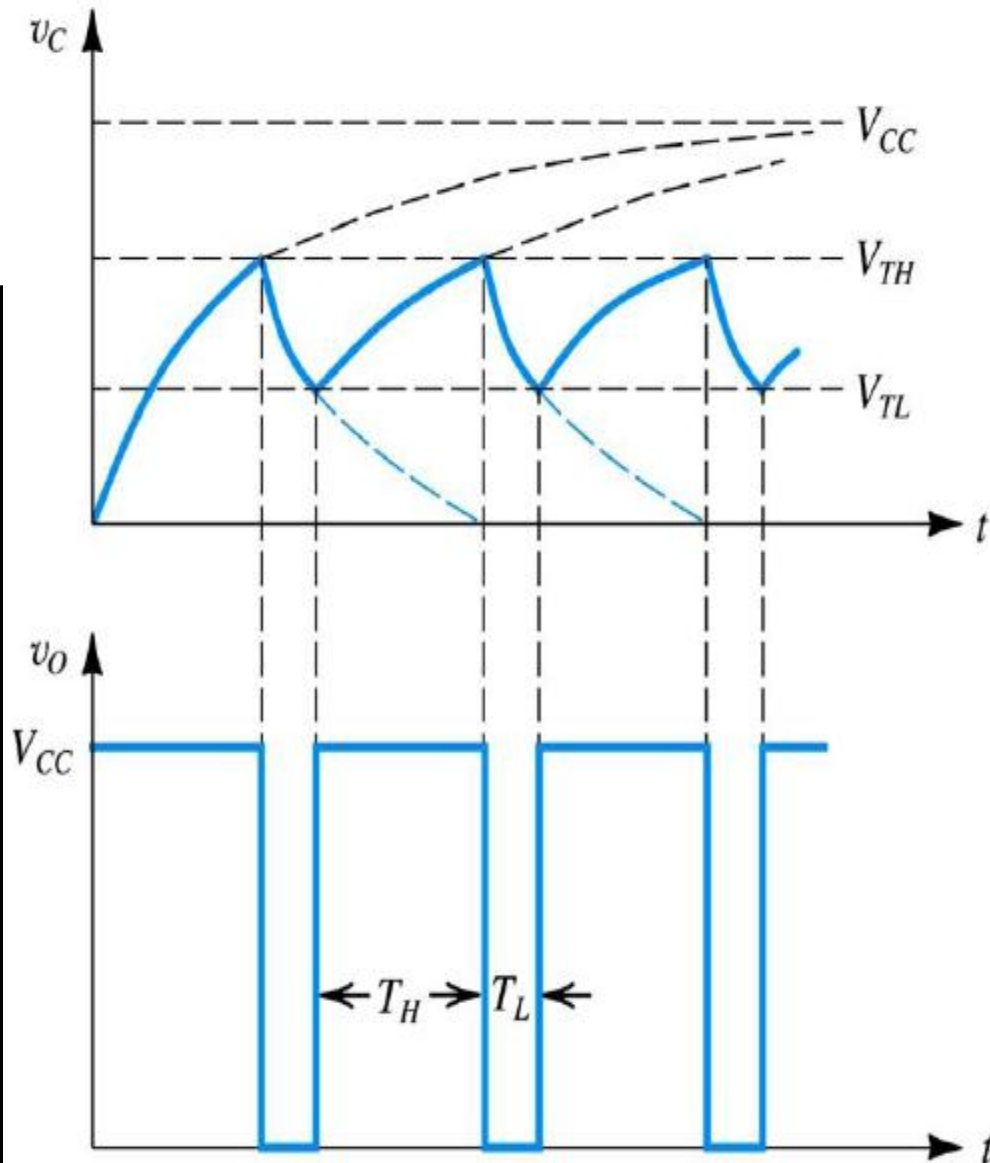

Astable Multivibrator (555 IC)

The expression of T_L
 C discharges from V_{TH} to 0

$$V_C = V_{final} - (V_{final} - V_{initial})e^{-t/\tau}$$


$$V_C = 0 - (0 - V_{TH})e^{-t/\tau}$$

$$V_C = 0 - (0 - \frac{2}{3}V_{CC})e^{-t/\tau}$$

where $\tau = R_B C$

$$V_C = V_{TL} = \frac{1}{3}V_{CC} \quad \text{at} \quad t = T_L$$

$$T_L = 0.69R_B C$$

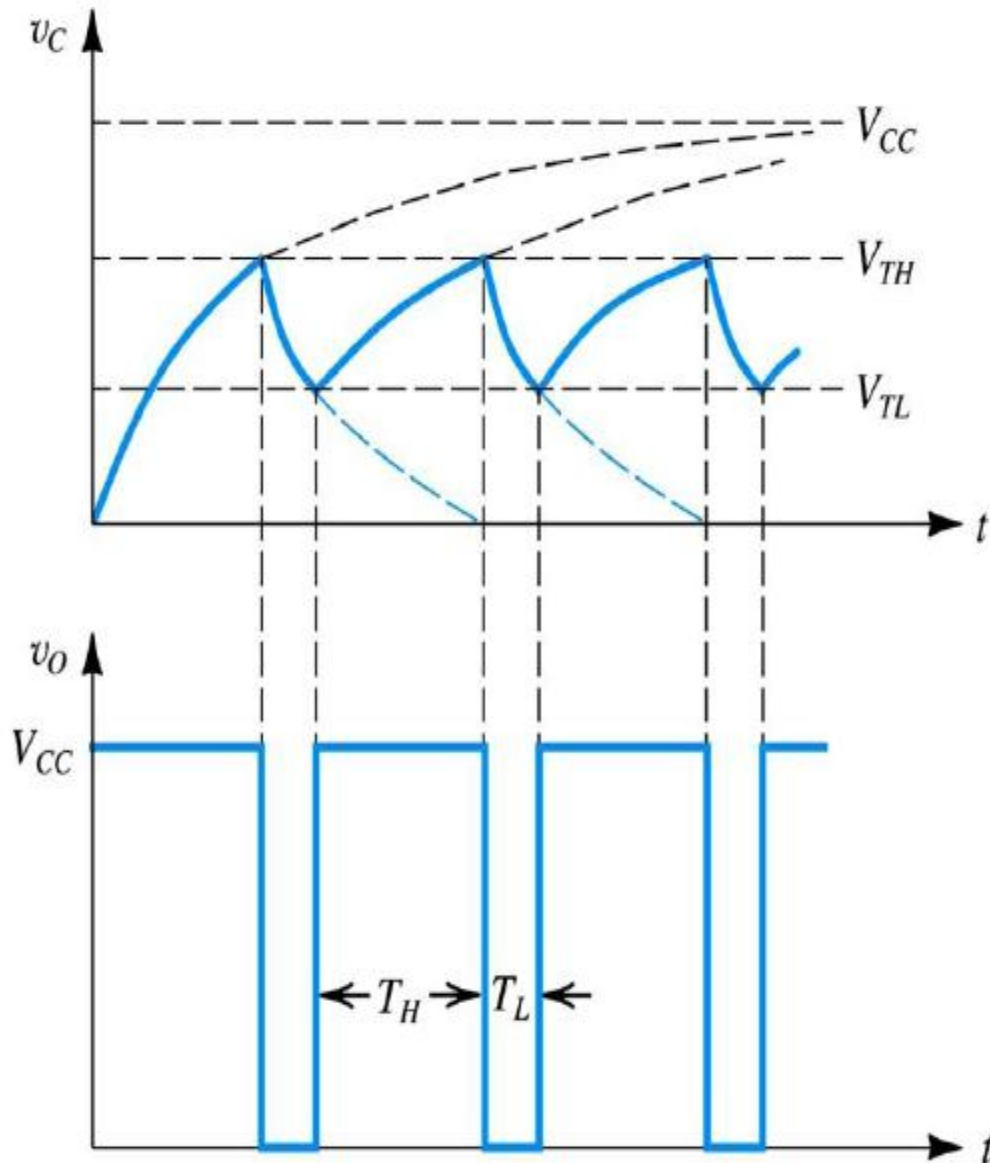

Astable Multivibrator (555 IC)

$$f = \frac{1}{T} = \frac{1}{T_H + T_L}$$

$$f = \frac{1}{0.69(R_A + 2R_B)C}$$

$$\text{Duty cycle} = \frac{T_H}{T_H + T_L}$$

$$\text{Duty cycle} = \frac{R_A + R_B}{R_A + 2R_B}$$

