

JFET :

→ ohmic Region : $V_p \leq V_{GS} \leq 0$, $V_{DS} \leq V_{GS} - V_p$ (N-channel)

$$I_D = I_{DSS} \left(2 \left(1 - \frac{V_{GS}}{V_p} \right) \left(\frac{V_{DS}}{-V_p} \right) - \left(\frac{V_{DS}}{V_p} \right)^2 \right)$$

→ Saturation Region : $V_p \leq V_{GS} \leq 0$, $V_{DS} \geq V_{GS} - V_p$ (N-channel)

$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_p} \right]^2$$

→ Breakdown :


$$V_{DS} \gg V_p$$

→ cut-off : $V_{GS} < V_p$ (N-channel)

* For p-channel reverse all polarities of the above conditions.

Part 2
Sheet 5
(JFET)

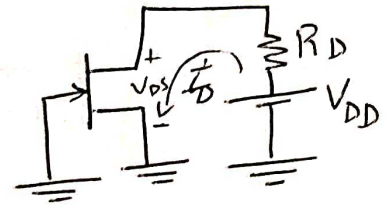1. $V_{GS(off)} = -4V$, $I_{DSS} = 12 \text{ mA}$
Find min. V_{DD} to put the device
in constant-current region.



Sol:
 $\Rightarrow V_{GS} = 0$

In constant-current (saturation) Region: $V_{DS} \geq V_P$ (at $V_{GS}=0$)

$$\Rightarrow \text{for min } V_{DD} \Rightarrow V_{DS} = V_P = -V_{GS(off)} = 4 \text{ V}$$

$$\Rightarrow V_{DD} = V_{DS} + (560 \Omega) I_D$$

$$\Rightarrow I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$
$$= I_{DSS} = 12 \text{ mA}$$

$$\Rightarrow V_{DD} = (4) + 0.56 (12) = 10.72 \text{ V}$$


2. A JFET has values of $V_{GS(off)} = -8V$ & $I_{DSS} = 16mA$.
Find the values of V_{GS} , I_D & V_{DS} for the ct.

Sol:
 $\Rightarrow V_{GS(off)} = -8V, I_{DSS} = 16mA$

$\because I_G = 0 \Rightarrow V_{GS} = -5V$

$$\begin{aligned} \Rightarrow I_D &= I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right)^2 \\ &= 16 \left(1 - \frac{(-5)}{(-8)}\right)^2 \\ &= 2.25 \text{ mA} \end{aligned}$$
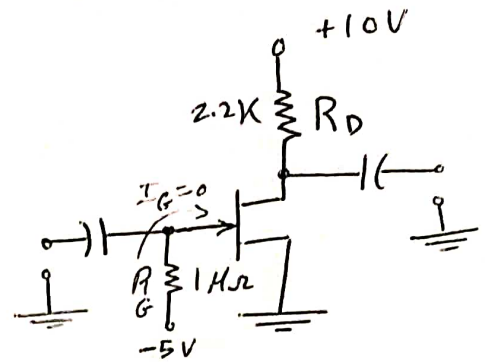
$$\begin{aligned} \Rightarrow V_{DS} &= 10 - I_D R_D \\ &= 10 - (2.25)(2.2) = 5.05 \text{ V} \end{aligned}$$




3. Find V_{DS} & V_{GS} in the ct. shown given $I_D = 5mA$.

Sol:
 \Rightarrow Applying KVL at o/p loop:
 $\Rightarrow 15 = I_D (R_D + R_S) + V_{DS}$
 $\Rightarrow V_{DS} = 15 - 5(1 + 0.47)$
 $= 7.65 \text{ V}$

$\because V_G = 0 \quad (I_D = 0)$
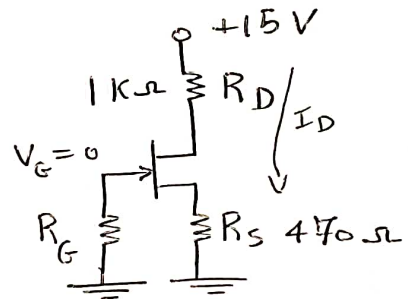
$$\Rightarrow V_{GS} = 0 - I_D R_S = -5(0.47) = -2.35 \text{ V}$$



4. In a self-bias n-channel JFET, The operating point is $I_D = 1.5 \text{ mA}$ & $V_{DS} = 10 \text{ V}$.


$$I_{DSS} = 5 \text{ mA} \text{ \& } V_{GS(off)} = -2 \text{ V}$$

Find R_S & R_D given $V_{DD} = 20 \text{ V}$.

Sol:

$$I_D = 1.5 \text{ mA} \text{ \& } V_{DS} = 10 \text{ V}$$
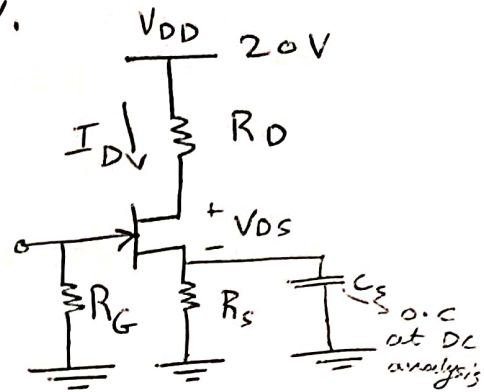
$$I_{DSS} = 5 \text{ mA} \text{ \& } V_{GS(off)} = -2 \text{ V}$$



$$\because I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right)^2$$

$$\Rightarrow V_{GS} = V_{GS(off)} \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right)$$

$$\Rightarrow V_{GS} = (-2) \left(1 - \sqrt{\frac{1.5}{5}}\right) = -0.9045 \text{ V}$$

$$\because I_G = 0 \Rightarrow V_{GS} = 0 - I_D R_S$$

$$\Rightarrow R_S = -\frac{V_{GS}}{I_D} = \frac{0.9045}{1.5 \text{ mA}} = 0.6 \text{ K}\Omega$$

* Applying KVL at o/p Loop:

$$\Rightarrow 20 = I_D (R_D + R_S) + V_{DS}$$

$$\Rightarrow 20 = 1.5 (R_D + R_S) + 10$$

$$\Rightarrow R_D + R_S = \frac{20}{3}, \quad \boxed{R_S = 0.6 \text{ K}}$$


$$\Rightarrow \boxed{R_D = 6.066 \text{ K}\Omega}$$

5. Determine I_D & V_{GS} for the JFET with voltage divider bias in ct. given that $V_D = 7V$.

Sol :

$\because V_D = 7V$ (Drain voltage)
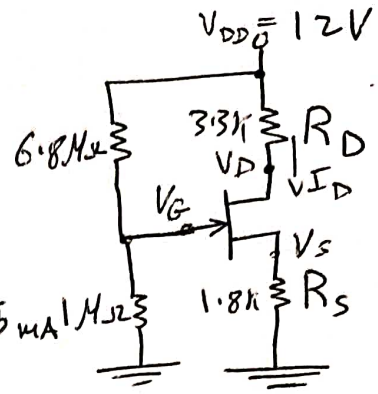
$$\Rightarrow I_D = \frac{V_{DD} - V_D}{R_D} = \frac{12 - 7}{3.3} = 1.515 \text{ mA}$$



$$\Rightarrow V_G = (12) \left(\frac{1}{1 + 6.8} \right) = 1.538 \text{ V}$$


$$\Rightarrow V_{GS} = V_G - I_D R_S = 1.538 - (1.515)(1.8) \\ \Rightarrow V_{GS} = -1.189 \text{ V}$$

6. The JFET Amp. has $g_m = 1 \text{ mA/V}$. If the source Resistance as compared to R_G , find the voltage gain of the Amp.


Sol:

$$g_m = 1 \text{ mA/V}$$

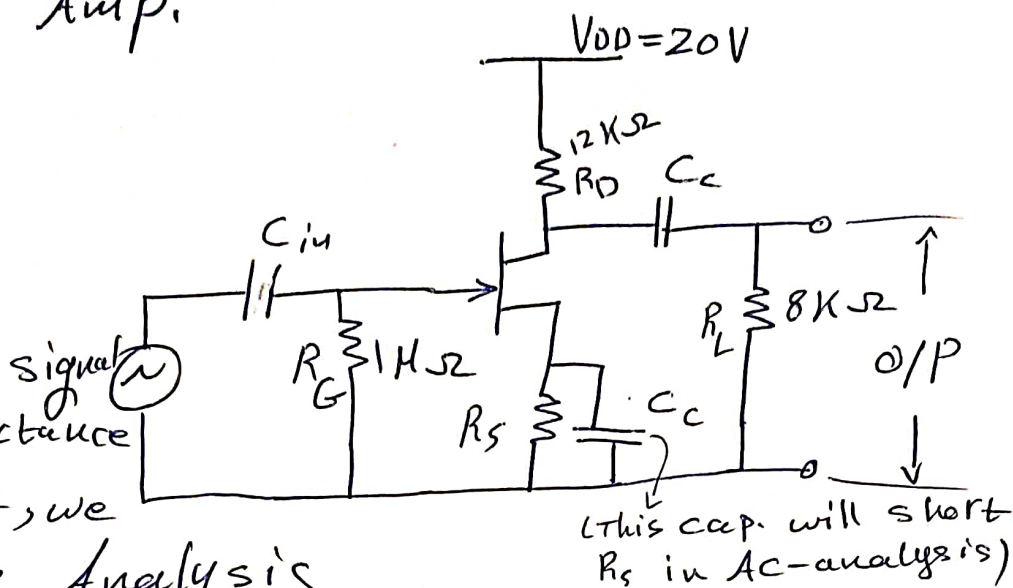so, the transconductance is already given, we don't need DC Analysis



AC (small-signal) Analysis :

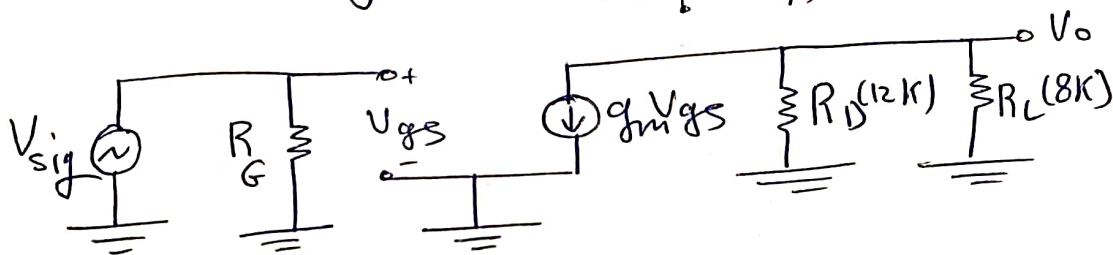

$$\Rightarrow A_v = \frac{V_o}{V_{sig}}$$

$$\because V_o = -g_m V_{gs} (R_D \parallel R_L)$$

$$\because V_{gs} = V_{sig}$$

$$\Rightarrow V_o = -g_m V_{sig} (R_D \parallel R_L)$$


$$\Rightarrow \frac{V_o}{V_{sig}} = A_v = -g_m (R_D \parallel R_L) = -(10^{-3}) \left[\frac{12 \times 10^3 \times 8 \times 10^3}{(12 + 8) \times 10^3} \right] = -4.8$$

6. The JFET Amp. has $g_m = 1 \text{ mA/V}$. If the source Resistance as compared to R_G , find the voltage gain of the Amp.


Sol:

$$g_m = 1 \text{ mA/V}$$

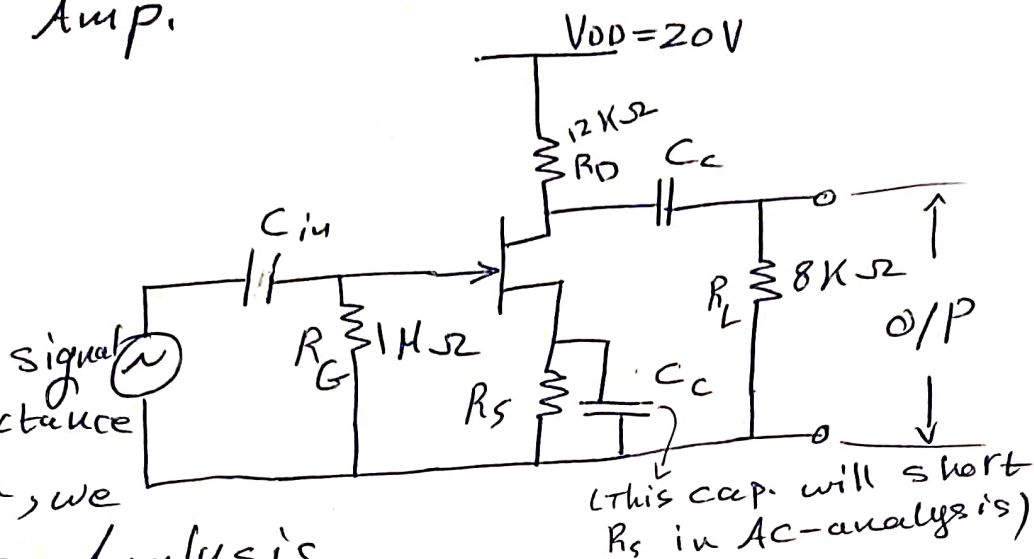So, the transconductance is already given, we don't need DC Analysis



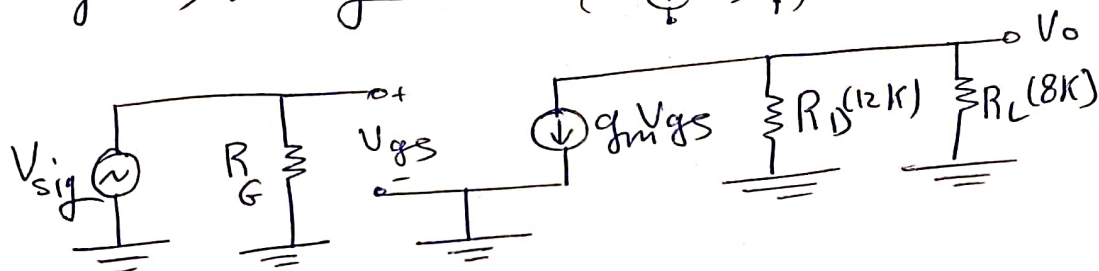AC (small-signal) Analysis : (short V_{DD} to ground) ($\infty \rightarrow 0$)



$$\Rightarrow A_v = \frac{V_o}{V_{sig}}$$

$$\because V_o = -g_m V_{gs} (R_D \parallel R_L)$$

$$\because V_{gs} = V_{sig}$$


$$\Rightarrow V_o = -g_m V_{sig} (R_D \parallel R_L)$$

$$\Rightarrow \frac{V_o}{V_{sig}} = A_v = -g_m (R_D \parallel R_L) = -(10^3) \left[\frac{12 \times 10^3 \times 8 \times 10^3}{(12 + 8) \times 10^3} \right] = -4.8$$


* If we need to get R_{in} & R_{out} :
 ↳ (not Required in this problem)

* R_{in} : (Replace the source by a test source)
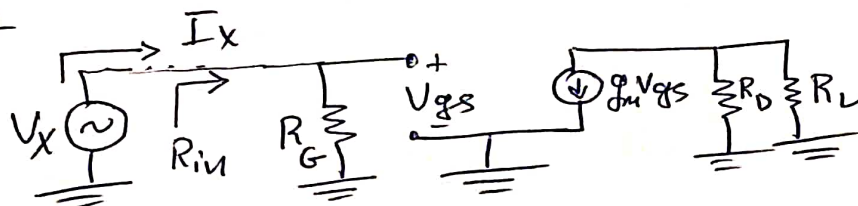
$$\Rightarrow R_{in} = \frac{V_x}{I_x} = R_G$$



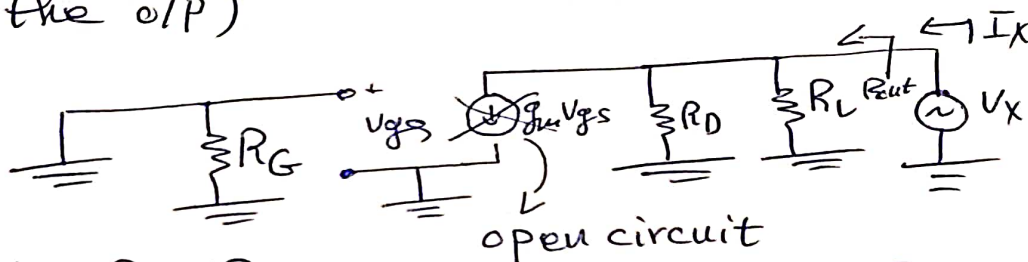* R_{out} : \rightarrow (short the source & add a test source at the o/p)




$$\Rightarrow R_{out} = \frac{V_x}{I_x} = R_L // R_D$$

open circuit
 ↳ since $V_{gs} = 0$.

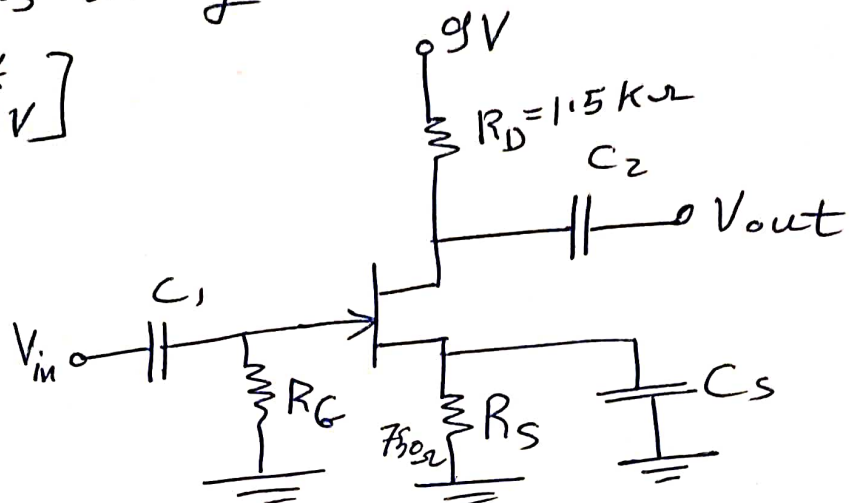7. For the JFET amplifier shown, calculate the voltage gain with i) R_S bypassed by a capacitor
ii) R_S un-bypassed.

[given: $I_{DSS} = 10 \text{ mA}$
 $V_{GS(off)} = -3.5 \text{ V}$]



Sol: First we need to do DC Analysis since

DC-Analysis :

$$\because I_g = 0$$

$$\Rightarrow V_G = 0$$

$$\Rightarrow V_{GS} = 0 - V_S$$

$$V_{GS} = -I_D R_S \quad (1)$$

$$\because I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right)^2$$

$$\Rightarrow I_D = 10 \times 10^{-3} \left(1 - \frac{V_{GS}}{(-3.5)}\right)^2$$

\Rightarrow From (1) :

$$I_D = -\frac{V_{GS}}{R_S}$$


$$\Rightarrow -\frac{V_{GS}}{R_S} = 10^{-2} \left[1 - 2 \frac{V_{GS}}{V_{GS(off)}} + \frac{V_{GS}^2}{V_{GS}^2}\right]$$

$$\Rightarrow -\frac{V_{GS}}{750} = 10^{-2} - \frac{2(10^{-2})}{(-3.5)} V_{GS} + \frac{V_{GS}^2}{(-3.5)^2} (10^{-2})$$

$$\Rightarrow 0.8163 \times 10^{-3} V_{GS}^2 + 0.0070476 V_{GS} + 10^{-2} = 0$$

$$\Rightarrow V_{GS} = -6.84 \text{ V} \quad V_{GS} = -1.79 > V_{GS(off)}$$

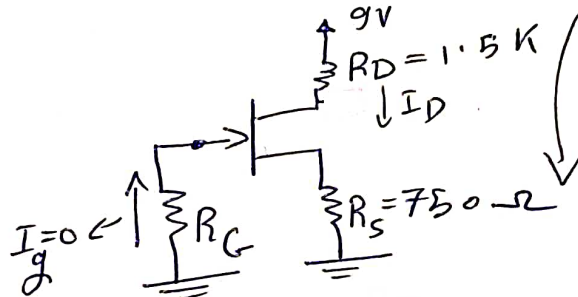
(Rejected) $\leftarrow (-6.8 < -3.5 \text{ } V_{GS(off)}) \leftarrow$ - 7 -



$$\begin{aligned}
 \Rightarrow g_m &= -\frac{2 I_{DSS}}{V_{GS(off)}} \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right) \\
 &= \frac{2 (10 \times 10^{-3})}{-3.5} \left(1 - \frac{(-1.7)}{(-3.5)}\right) \\
 &= 2.938 \times 10^{-3} \text{ A/V} \\
 &= 2.938 \text{ mA/V}
 \end{aligned}$$

AC Analysis: $\frac{1}{\text{capacitor}} = \text{open}$, $\frac{1}{\text{DC source}} = \text{short}$, $\text{AC source} = \text{circle with arrow}$

i) R_s bypassed:

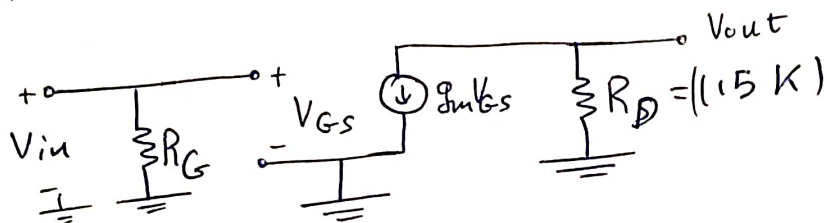


$$\Rightarrow V_o = -g_m V_{GS} R_D$$

$$V_{GS} = V_{in}$$

$$\Rightarrow V_o = -g_m V_{in} R_D$$

$$\Rightarrow A_v = \frac{V_o}{V_{in}} = -g_m R_D = -(2.938)(1.5K) = -4.407$$

ii) R_s unbypassed:

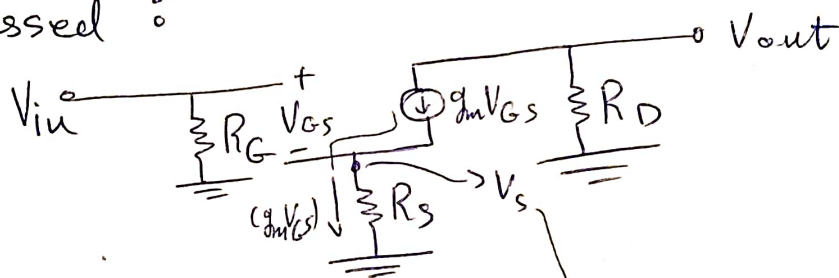

$$\Rightarrow V_{out} = -g_m V_{GS} R_D \quad (*) \quad V_s = (g_m V_{GS}) R_s$$

$$\Rightarrow V_{in} = V_{GS} + V_s = V_{GS} + g_m V_{GS} R_s$$

$$\Rightarrow V_{in} = V_{GS} (1 + g_m R_s)$$


$$\Rightarrow V_{GS} = \frac{V_{in}}{1 + g_m R_s} \Rightarrow \text{sub. in } (*) \Rightarrow V_{out} = \frac{-g_m R_D}{1 + g_m R_s} \cdot V_{in}$$

$$-8 - \Rightarrow A_v = \frac{V_{out}}{V_{in}} = \frac{-g_m R_D}{1 + g_m R_s} = 1.3756$$

* If we want to find R_{in} & R_{out} :

R_{in} :

$$\Rightarrow R_{in} = R_G$$

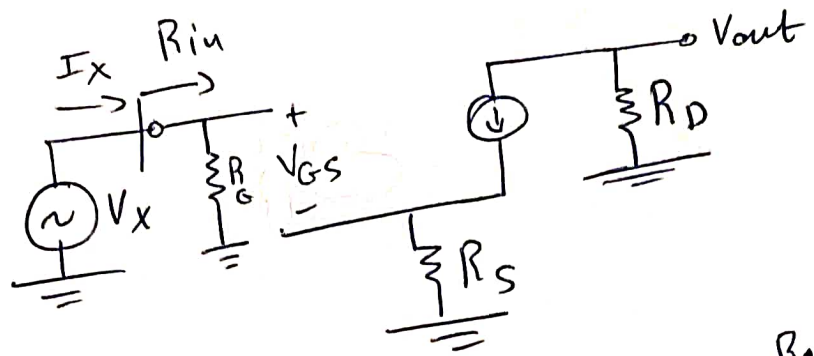

R_{out} :

$$\Rightarrow R_{out} = R_D$$

