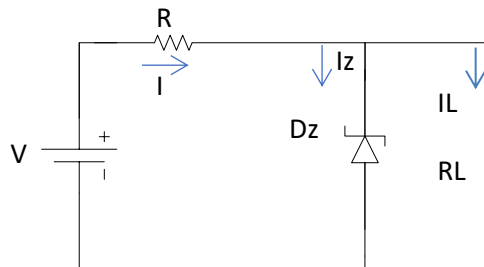



Electronic Devices

Sheet #4

1. In the shown figure, $V=300V$, $V_z=220V$, the value of the zener current is $15mA$, and the value of the load current is $25mA$.
 - (a) Calculate the value of R which must be used.
 - (b) If the load current decreases by $5mA$, what will be the zener current.
 - (c) The load is as in part (a). If the supply voltage changes to $340V$, what is I_z ?
 - (d) The normal operating range of the avalanche diode is from 3 to $50mA$. If $R=1.5K\Omega$ and $V=340V$, over what load current can output be varied?



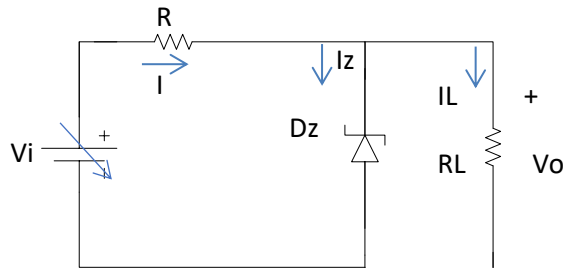2. For the voltage regulator shown, assume that $V_o = 20V$, $R=20\Omega$, $r_z=0$, and $R_L=200\Omega$. Voltage V_i varies between 24 and $30V$.
 - (a) Specify the maximum and minimum current rating for the zener diode.
 - (b) Determine the maximum power dissipated in resistance R and in zener diode.



3. For the circuit shown, Determine V_o for all voltage levels if $V_{z1}=5V$, $V_{z2}=6V$, $V_\gamma=0V$ and $V_i=20\sin\omega t$.

