

Electronic Systems

Active Filters


Lecture 6

Dr. Roaa Mubarak

The Active Filters Contents:

1. Introduction to Filters.
2. Low Pass Filter.
3. High Pass Filter.
4. Band Pass Filter.
5. Butterworth Filter.
6. Chebyshev Filter.
7. Bessel Filter.
- 8. KHN Biquad Filter.**
9. Multiple Feedback Filters.
10. State Variable Filters.

(KHN) Biquad filter (Summary)

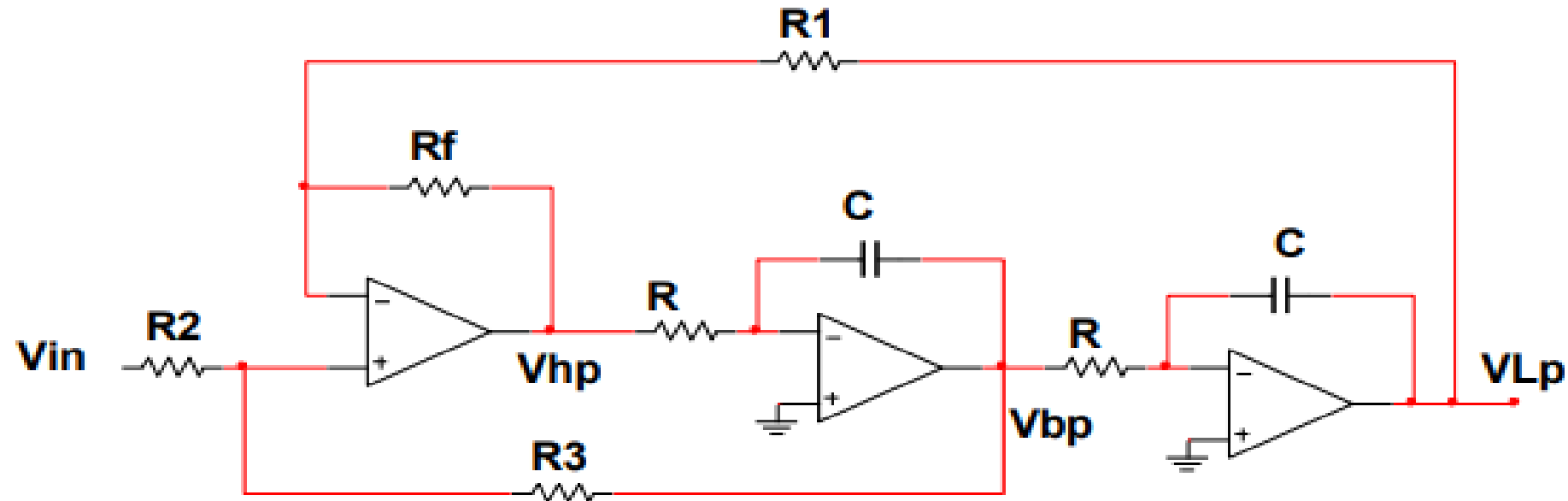

Design Equations

$$\times \boxed{\frac{R_F}{R_1} = 1}$$

$$\times \boxed{K = 2 - \frac{1}{Q}}$$

$$\times \boxed{\frac{R_3}{R_2} = 2Q - 1}$$

$$\times \boxed{f_o = \frac{1}{2\pi RC}}$$

\times For BPF

$$\boxed{Q = \frac{f_c}{B.W}}$$

$$f_L = f_o - \frac{B.W}{2}$$

$$f_H = f_o + \frac{B.W}{2}$$


(KHN) Biquad filter

Example 1:

Design a KHN Filter to realize a BPF with center frequency of 10 KHz and bandwidth of 100Hz.

Calculate the center frequency gain (A_m). Hint: use 1 nF capacitor.

Solution

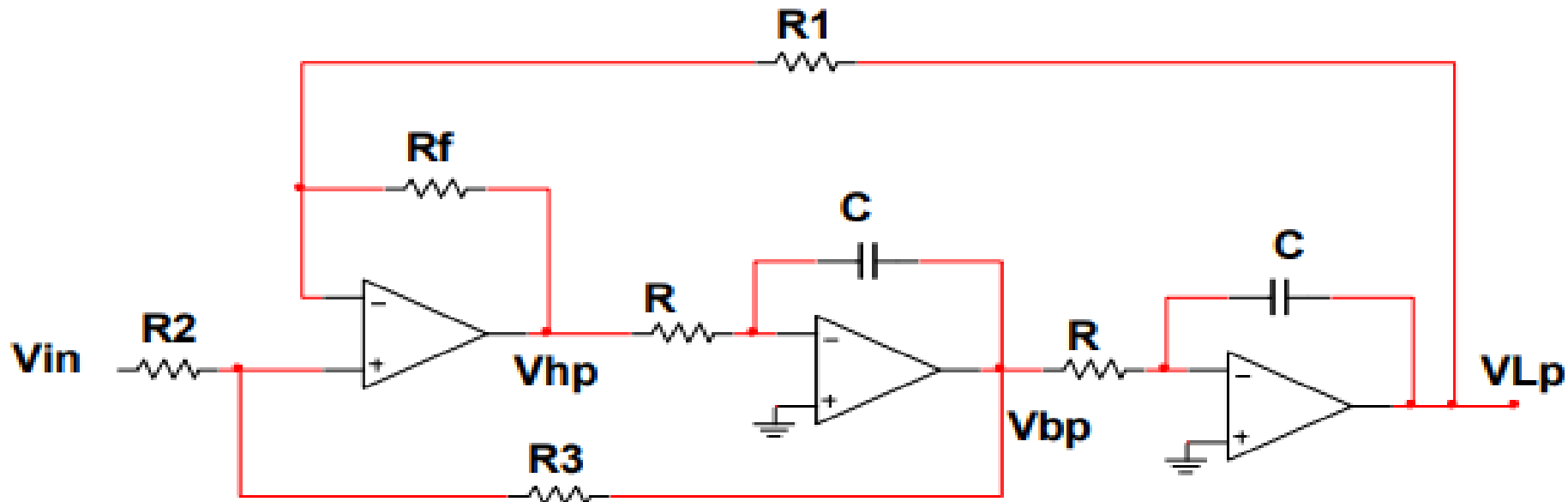

Solution:

$$* f_0 = 10 \times 10^3 = \frac{1}{2\pi RC}, \quad \boxed{C = 1nF}$$

$$\therefore R = \frac{1}{2\pi [10 \times 10^3] [1 \times 10^{-9}]} = 15920 \Omega$$

$$\boxed{R = 15.92 k\Omega}$$

$$* \frac{R_F}{R_1} = 1 \quad \checkmark \rightarrow \text{choose } \boxed{R_1 = 10k\Omega \quad \checkmark \rightarrow \therefore R_F = 10k\Omega}$$

$$* \text{Quality-Factor } Q = \frac{f_0}{B.W} = \frac{10 \times 10^3}{100} = 100$$
$$\boxed{Q = 100}$$

$$* K = 2 - \frac{1}{Q} = 2 - \frac{1}{100} \quad \checkmark \rightarrow \therefore \boxed{K = 1.99}$$

$$* \frac{R_3}{R_2} = 2Q - 1 = 2 \times 100 - 1$$

$$\frac{R_3}{R_2} = 199 \quad \checkmark \rightarrow \text{choose } \boxed{\begin{matrix} R_2 = 1k\Omega \\ R_3 = 199k\Omega \end{matrix}}$$

How to get the center Frequency gain (A_m)?

$$\frac{V_{hp}}{V_{in}} = \frac{k s^2}{s^2 + (\frac{\omega_0}{Q})s + \omega_0^2}$$

$$\therefore V_{hp} = \frac{k s^2}{s^2 + (\frac{\omega_0}{Q})s + \omega_0^2} V_{in}$$

$$\text{but } V_{bp} = -\frac{\omega_0}{s} V_{hp}$$

$$\therefore V_{bp} = \frac{k s^2}{s^2 + (\frac{\omega_0}{Q})s + \omega_0^2} \left(-\frac{\omega_0}{s}\right) V_{in}$$

$$\therefore \frac{V_{bp}}{V_{in}} = \frac{-k \omega_0 s}{s^2 + (\frac{\omega_0}{Q})s + \omega_0^2} = H_{bp} = T_{bp}$$

$$\therefore H_{bp}(j\omega) = \frac{-jk\omega_0\omega}{(j\omega)^2 + (\frac{\omega_0}{Q})j\omega + \omega_0^2}$$

$$T_{bp}(j\omega) = \frac{-jk\omega_0\omega}{-\omega^2 + j\frac{\omega_0\omega}{Q} + \omega_0^2}$$

$$T_{bp}(j\omega) = \frac{-jk\omega_0\omega}{[\omega_0^2 - \omega^2] + j\frac{\omega_0\omega}{Q}}$$


$$|T_{bp}| = \frac{k\omega_0\omega}{\sqrt{[\omega_0^2 - \omega^2]^2 + (\frac{\omega_0\omega}{Q})^2}}$$

$$\text{at } \omega = \omega_0, |T_{bp}| = A_m \quad \text{max. gain}$$

$$\therefore A_m = \frac{k\omega_0 \cdot \omega_0}{\sqrt{[\omega_0^2 - \omega_0^2]^2 + (\frac{\omega_0 \cdot \omega_0}{Q})^2}} = \frac{k\omega_0^2}{\frac{\omega_0^2}{Q}}$$

$$\boxed{A_m = k \cdot Q}$$

- Center Frequency gain(Max. gain)

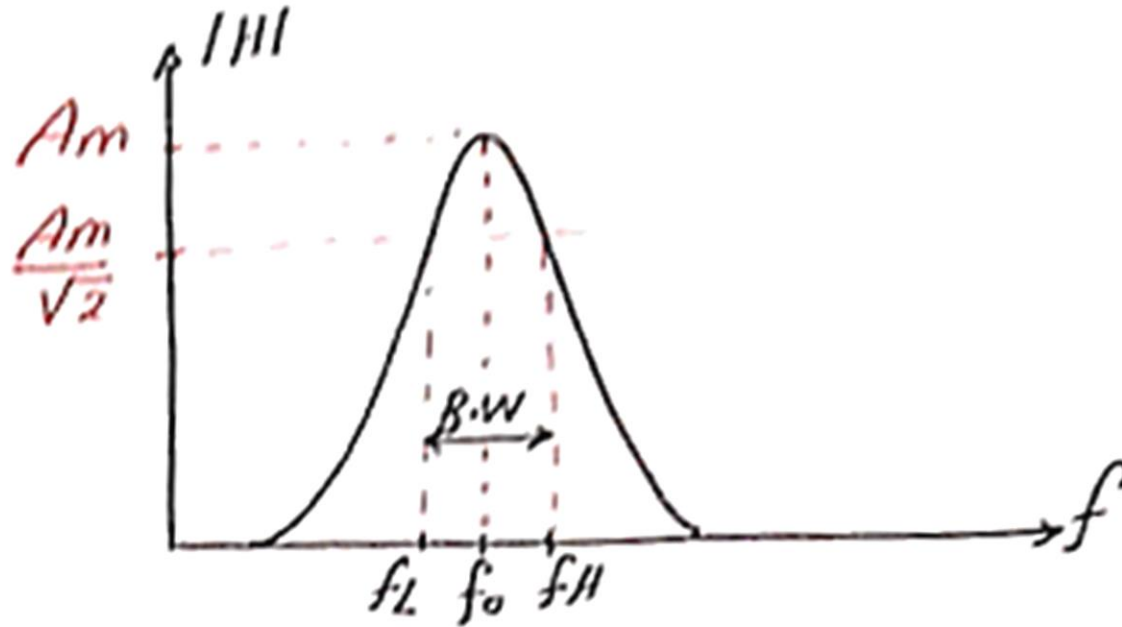

$$\times A_m = k.Q = 1.99 \times 10^3$$

$$\boxed{A_m = 199}$$

Example (2):

Design the KHN Filter to realize a HPF with a cut-off frequency 10KHz(Use C of 1 nF).

Solution:

$$H_{HP} = \frac{K s^2}{s^2 + s\left(\frac{\omega_0}{Q}\right) + \omega_0^2}$$

$$|T_{hp}| = \frac{K \omega^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + \left(\frac{\omega_0 \omega}{Q}\right)^2}}$$

$$\text{at } \omega = \omega_0 \quad |T_{hp}| = \frac{K \omega_0^2}{\frac{\omega_0^2}{Q}} = K \cdot Q$$



$$\frac{A_m}{\sqrt{2}} = K \cdot Q$$

$$\text{but } T_{hp} = \frac{K}{1 + \frac{\omega_0}{Q} \frac{1}{s} + \frac{\omega_0^2}{s^2}} \bigg|_{s=\infty} = A_m = K$$

$$\therefore \frac{K}{\sqrt{2}} = K \cdot Q \quad \therefore Q = \frac{1}{\sqrt{2}} = 0.707$$

$$K = 2 - \frac{1}{Q} = 0.586 \quad \therefore \frac{R_3}{R_1} = 2Q - 1 = 0.414$$

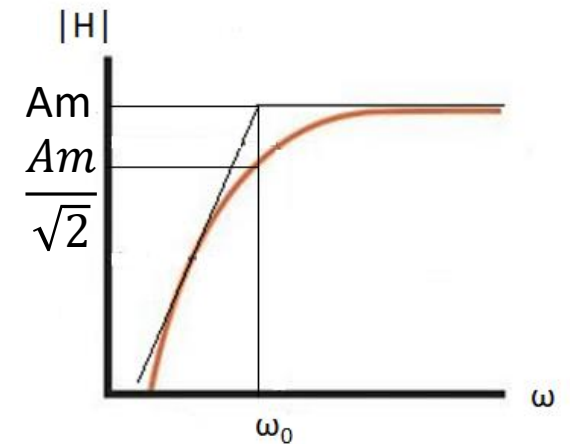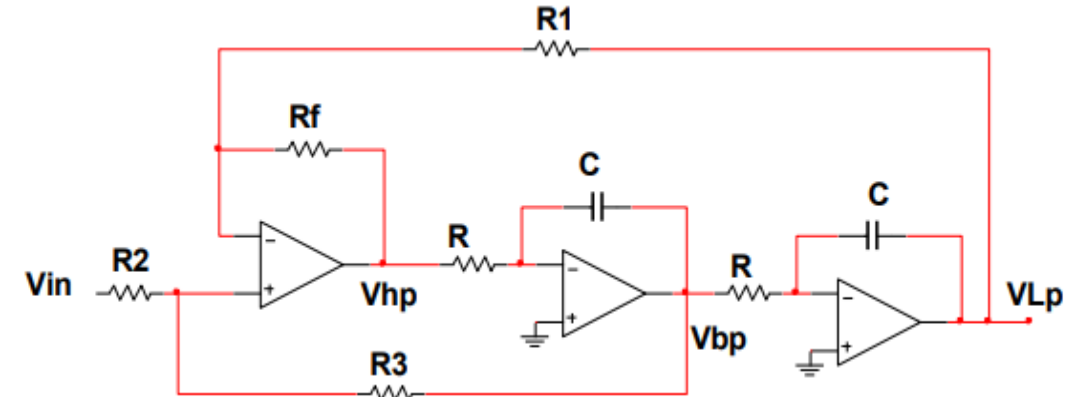Let $R_1 = 10k\Omega \therefore R_3 = 4.14k\Omega$



$$* f_c = 10^4 = \frac{1}{2\pi RC}$$

$$10^4 = \frac{1}{2\pi R(1 \times 10^{-9})}$$

$$R = 15.92k\Omega$$

$$* \frac{R_f}{R_1} = 1 \quad \text{Let } \begin{cases} R_1 = 10k\Omega \\ R_f = 10k\Omega \end{cases}$$

Example (3):

Design the KHN Filter to realize a LPF with a cut-off frequency 10KHz(Use C of 1 nF).

Solution:

$$* f_0 = 10^4 = \frac{1}{2\pi RC}$$

$$10^4 = \frac{1}{2\pi R(1 \times 10^{-9})}$$

$$\therefore R = 15.92 \text{ k}\Omega$$

$$* \frac{R_F}{R_i} = 1$$

$$\text{Let } \begin{cases} R_i = 10 \text{ k}\Omega \\ R_F = 10 \text{ k}\Omega \end{cases}$$

$$* Q = \frac{1}{\sqrt{2}} = 0.707$$

$$* k = 2 - \frac{1}{Q} = 0.586$$

$$* \frac{R_3}{R_2} = 2Q - 1 = 0.414$$

$$\text{Let } \begin{cases} R_2 = 10 \text{ k}\Omega \\ R_3 = 4.14 \text{ k}\Omega \end{cases}$$

Maximum gain

$$V_{LP} = \frac{\omega_o^2}{s^2} V_{hp}$$


$$V_{LP} = \frac{\omega_o^2}{s^2} \frac{k s^2}{s^2 + (\frac{\omega_o}{Q})s + \omega_o^2}$$

$$T_{LP} = \frac{V_{LP}}{V_i} = \frac{k \omega_o^2}{s^2 + (\frac{\omega_o}{Q})s + \omega_o^2}$$


Max. gain at $f=0 \therefore \omega=0$
 $\therefore s=0$

$$|T_{LP}| = \frac{k \omega_o^2}{\omega_o^2} = k$$



$$A_{in} = k = 0.586$$

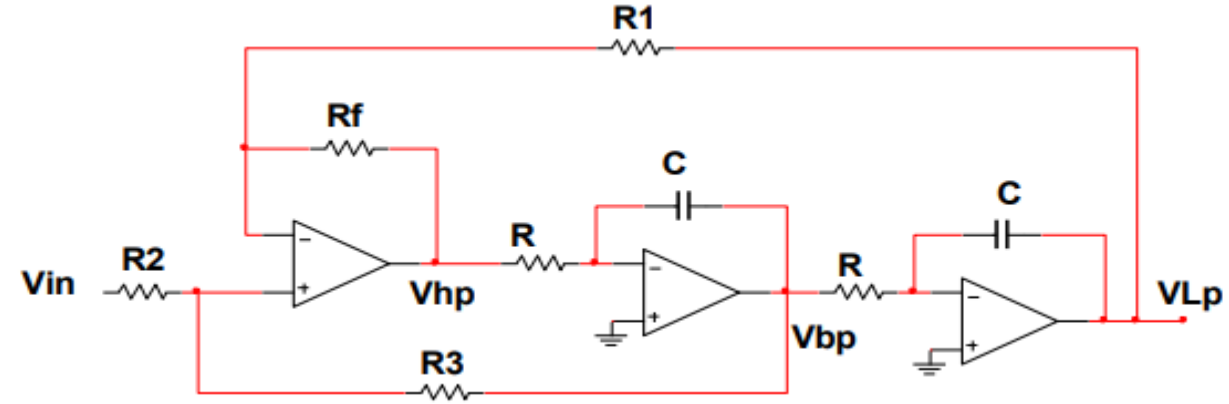
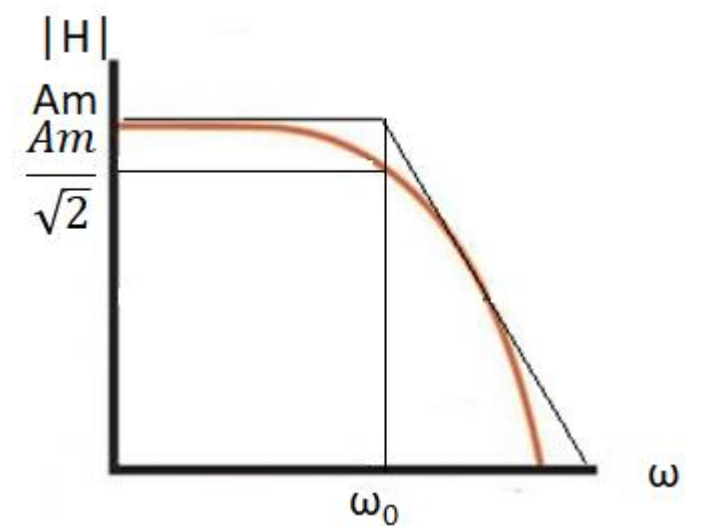
$$H_{LP} = \frac{a_0}{s^2 + s\left(\frac{\omega_o}{Q}\right) + \omega_o^2}$$



(KHN) Biquad All Pass Filter (APF)

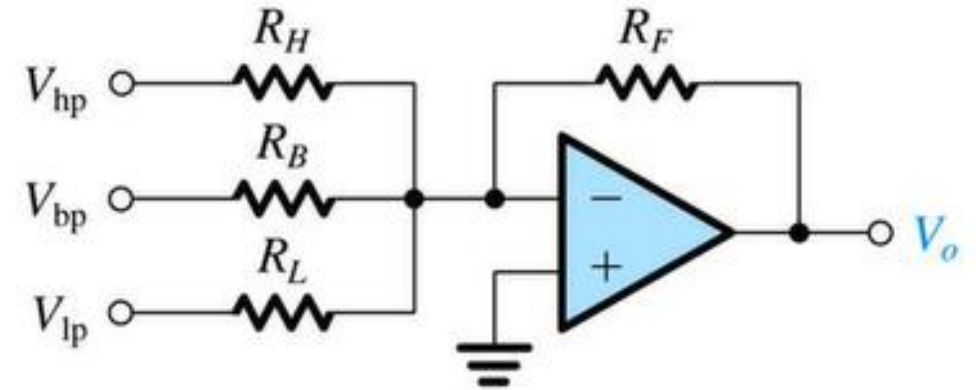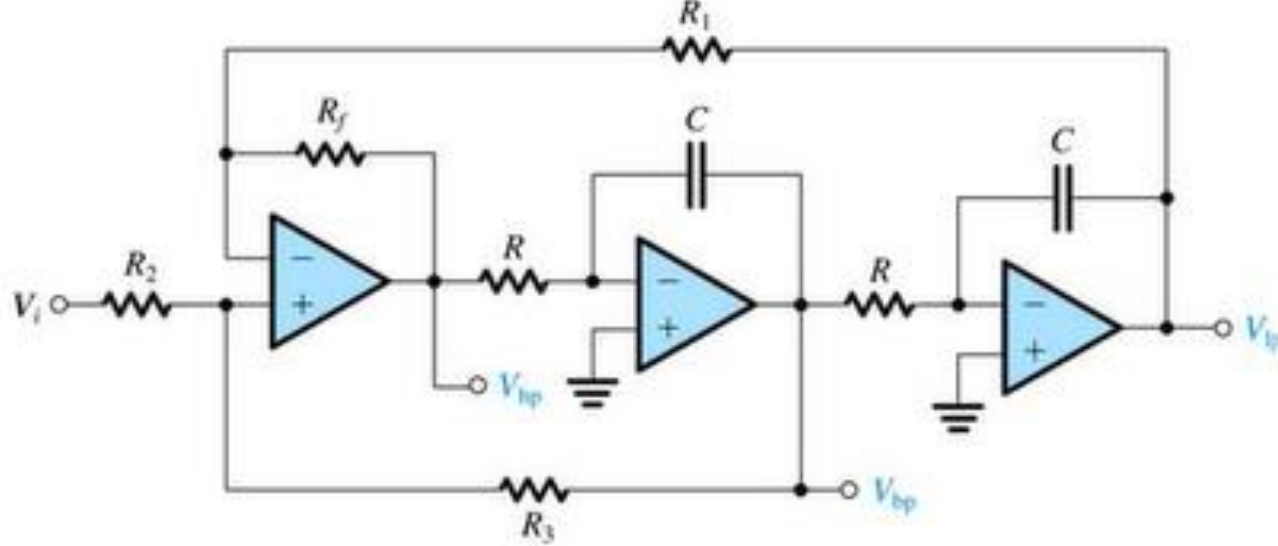

$$V_o = -\left(\frac{R_F}{R_H}V_{hp} + \frac{R_F}{R_B}V_{bp} + \frac{R_F}{R_L}V_{lp}\right)$$

$$= -V_i\left(\frac{R_F}{R_H}T_{hp} + \frac{R_F}{R_B}T_{bp} + \frac{R_F}{R_L}T_{lp}\right)$$

$$T_{bp} = \frac{V_{bp}}{V_i}$$

$$T_{lp} = \frac{V_{lp}}{V_i}$$

$$T_{hp} = \frac{V_{hp}}{V_i}$$

(KHN) Biquad All Pass Filter (APF)

$$V_o = -V_i \left(\frac{R_F}{R_H} T_{hp} + \frac{R_F}{R_B} T_{bp} + \frac{R_F}{R_L} T_{lp} \right)$$


$$T_{bp} = \frac{V_{bp}}{V_i} = - \frac{K \omega_0 s}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

$$T_{lp} = \frac{V_{lp}}{V_i} = \frac{K \omega_0^2}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

$$T_{hp} = \frac{V_{hp}}{V_i} = \frac{K s^2}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

$$\frac{V_o}{V_i} = -K \frac{(R_F/R_H)s^2 - s(R_F/R_B)\omega_0 + (R_F/R_L)\omega_0^2}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

(KHN) Biquad All Pass Filter (APF)

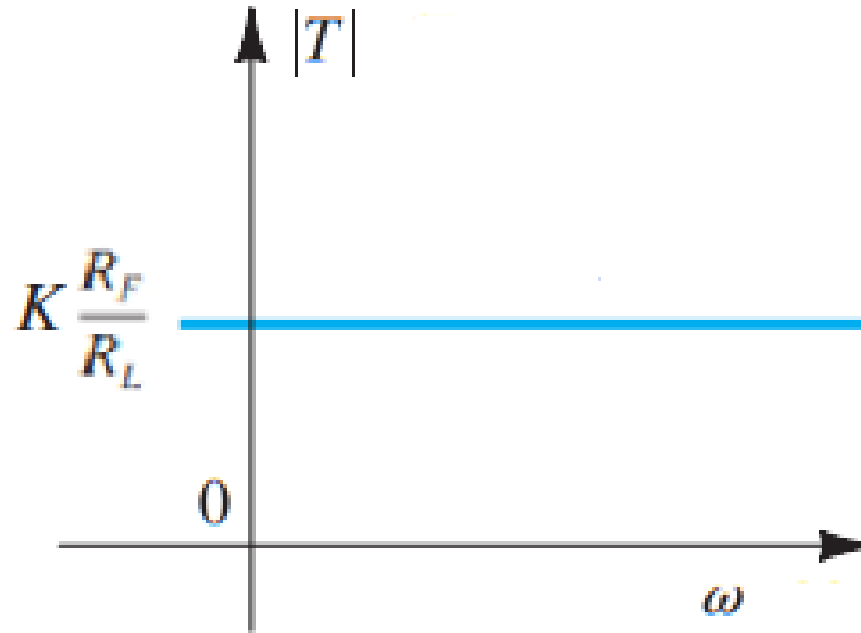

$$\text{Flat Gain} = A_m = |T_{AP}| = K \frac{R_F}{R_L}$$



KHN Biquad Notch Filter (BSF with narrow B.W)

- KHN Biquad Notch Filter is obtained by:

$$R_B = \infty$$

$$\frac{R_H}{R_L} = \left(\frac{\omega_n}{\omega_0} \right)^2$$

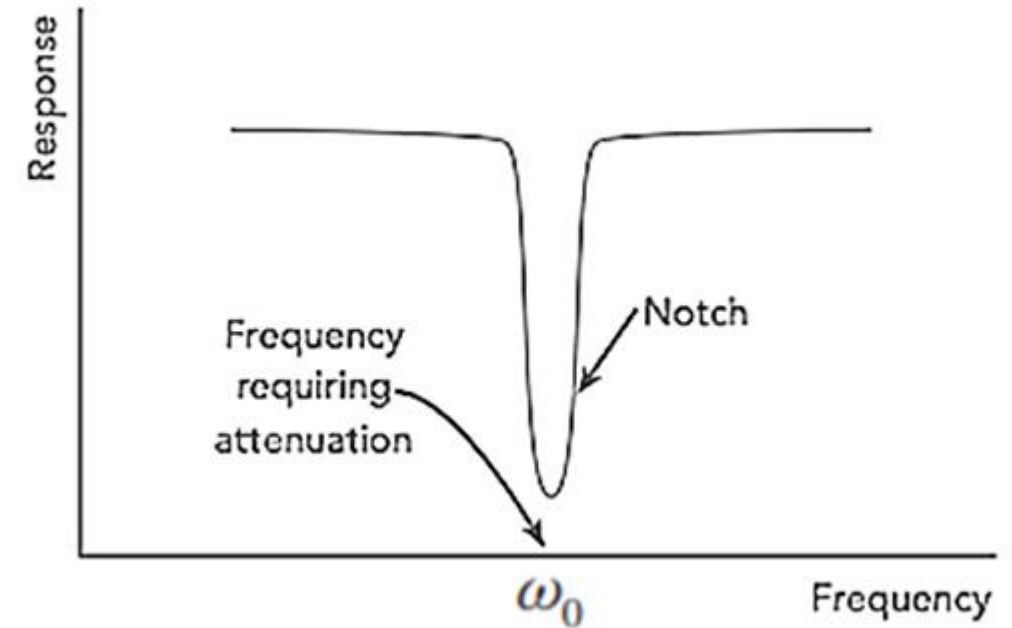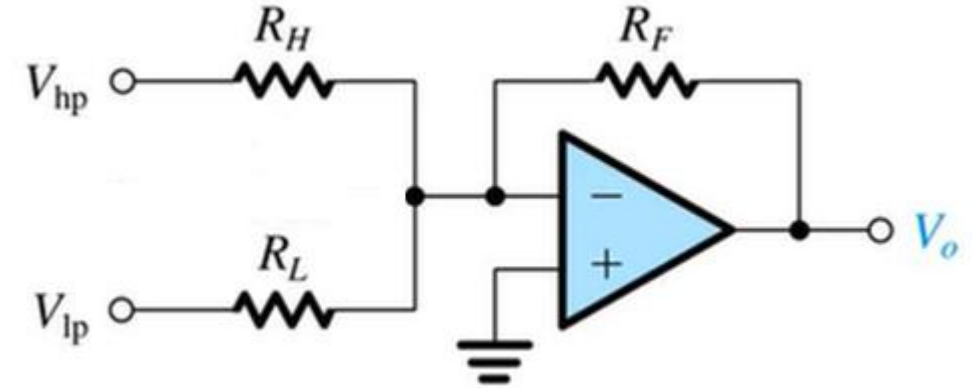
$$T_{NF} = \frac{V_o}{V_i} = -K \frac{(R_F/R_H)s^2 + (R_F/R_L)\omega_0^2}{s^2 + s(\omega_0/Q) + \omega_0^2}$$




Two-Thomas Biquad Filter

Two-Thomas Biquad Filter

- An alternative two-integrator-loop biquad circuit in which all three op amps are used in a single-ended mode can be developed as follows: Rather than using the input summer to add signals with positive and negative coefficients, we can introduce an additional inverter, as shown.
- Now all the coefficients of the summer have the same sign, and we can dispense with the summing amplifier altogether and perform the summation at the virtual-ground input of the first integrator.

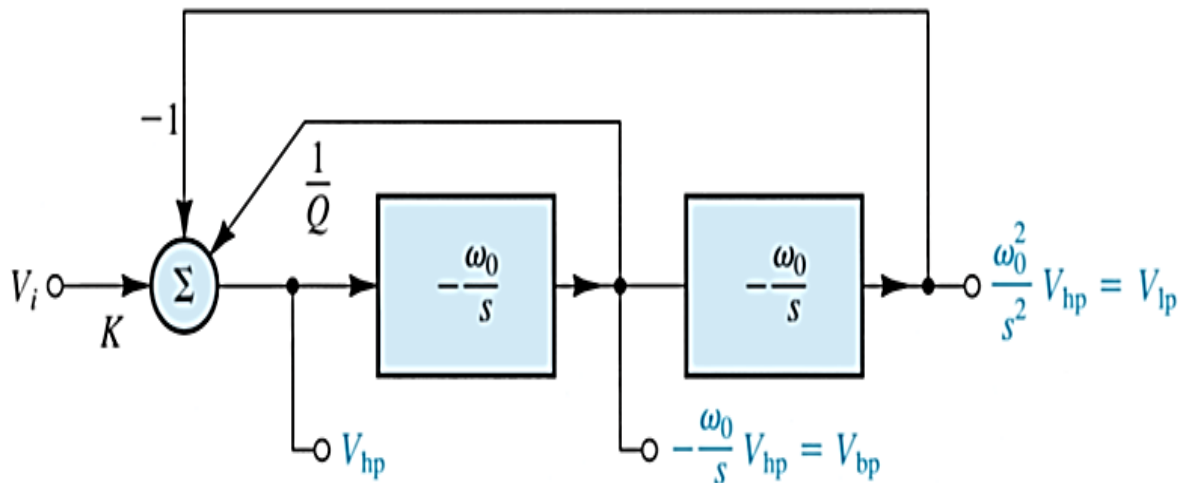



KHN Biquad Filter

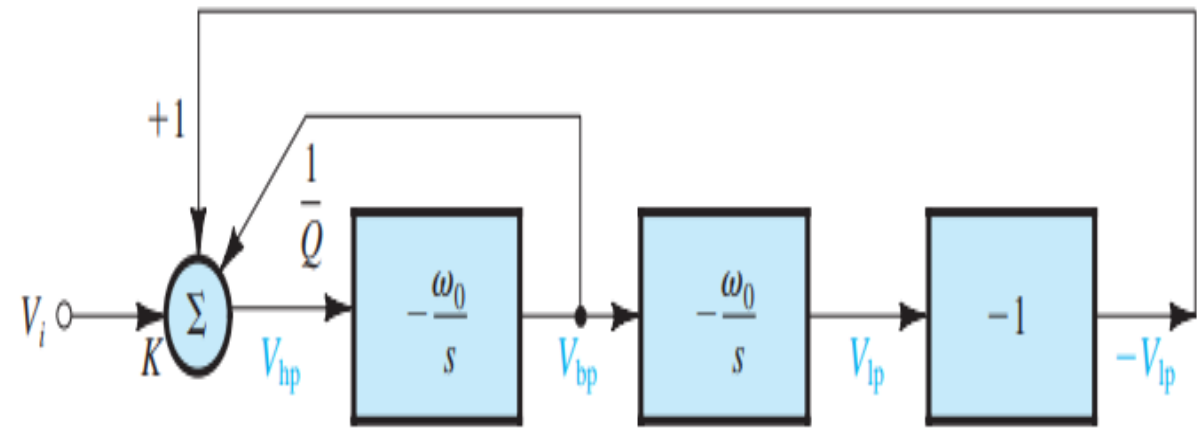



Two-Thomas Biquad Filter

Two-Thomas Biquad Filter

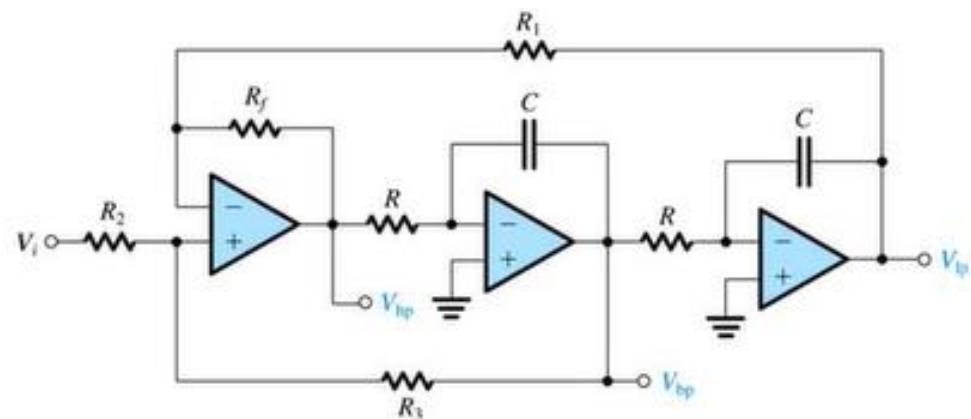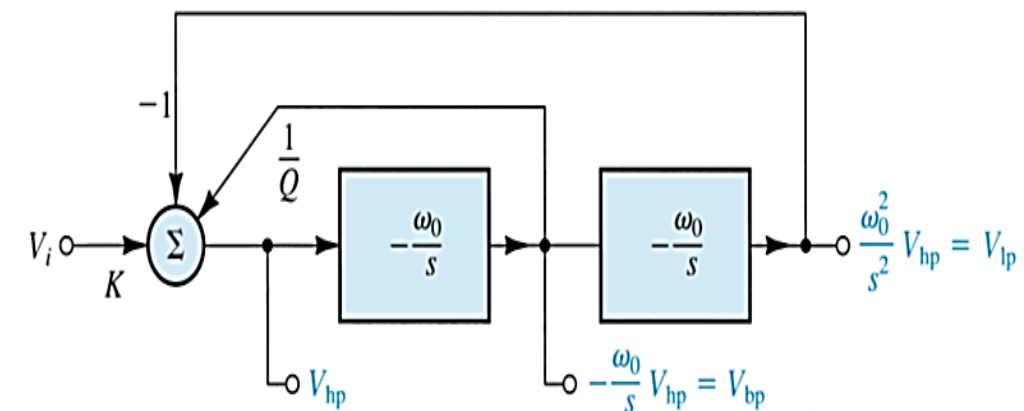Observe that the summing weights of 1, $1/Q$, and K are realized by using resistances of R , QR , and R/K , respectively. we observe that the high-pass function is no longer available!. The circuit is known as the Tow–Thomas biquad, after its originators.





KHN Biquad Filter

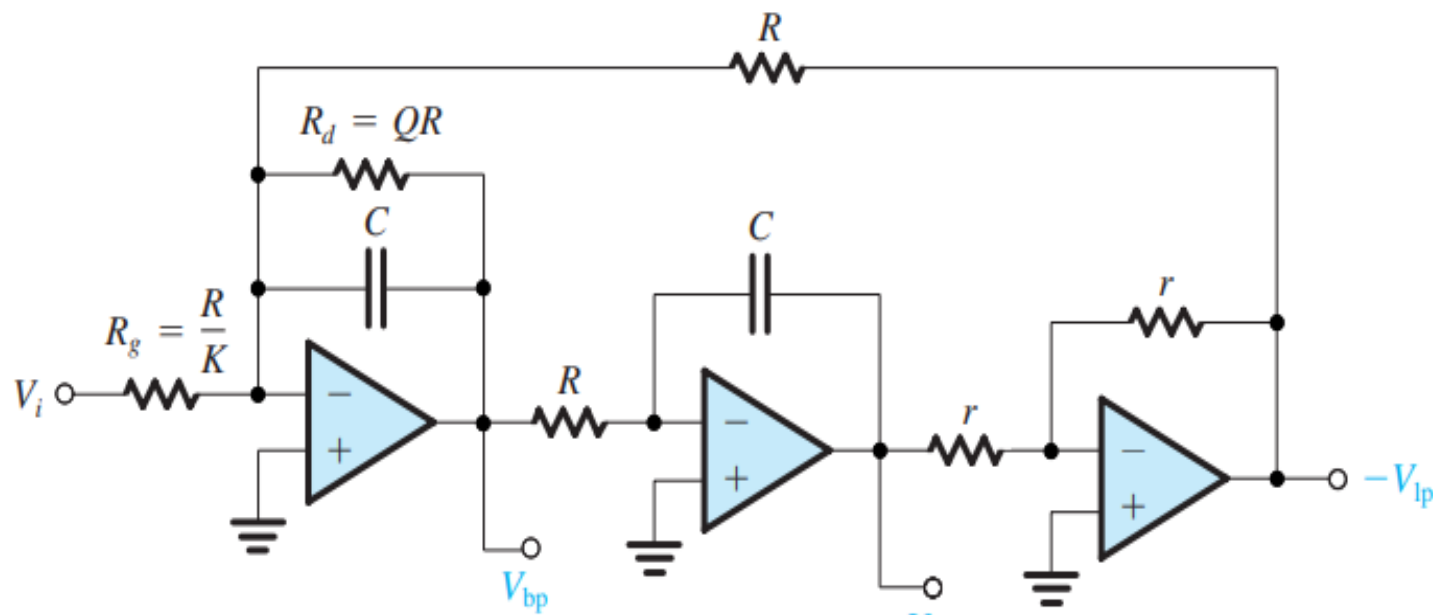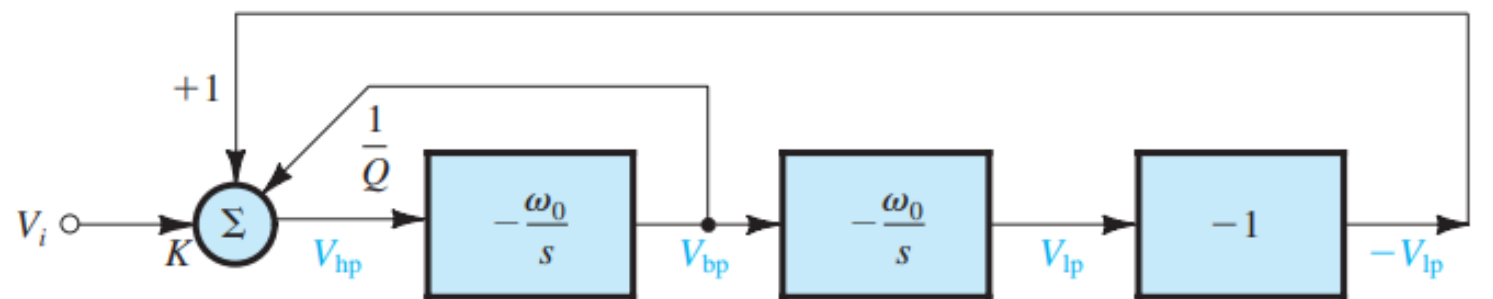


Two-Thomas Biquad Filter


Two-Thomas Biquad Filter

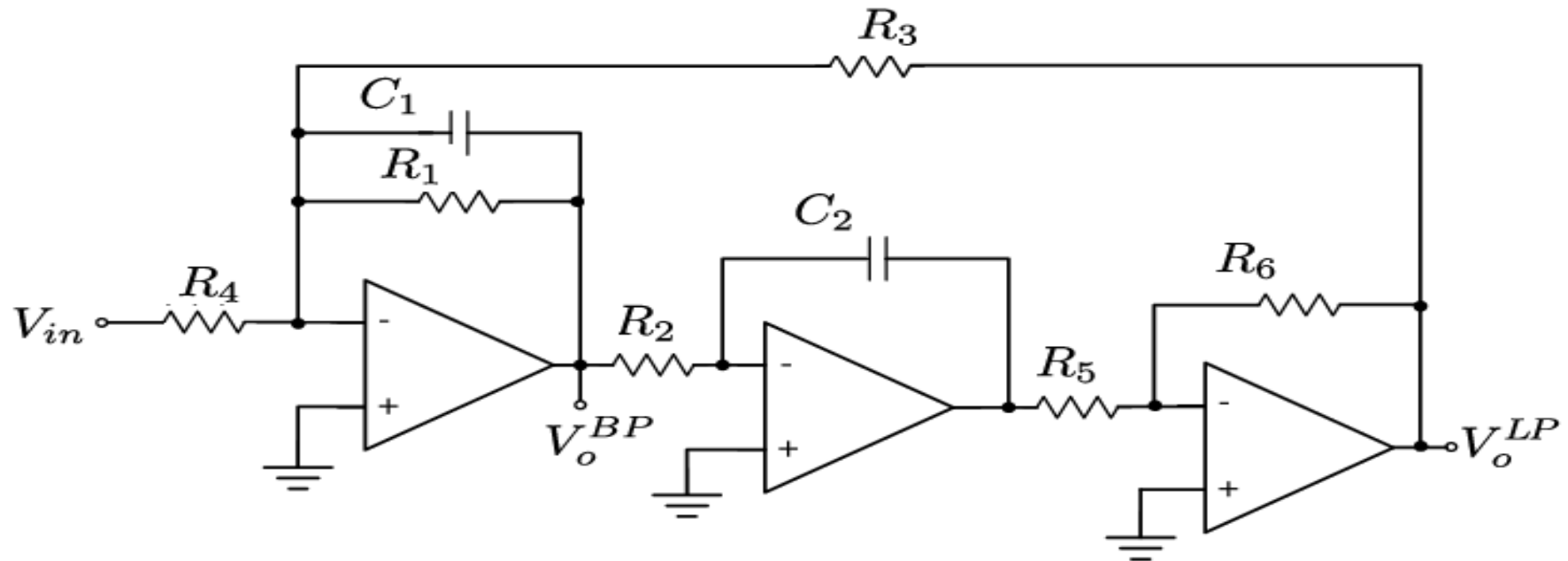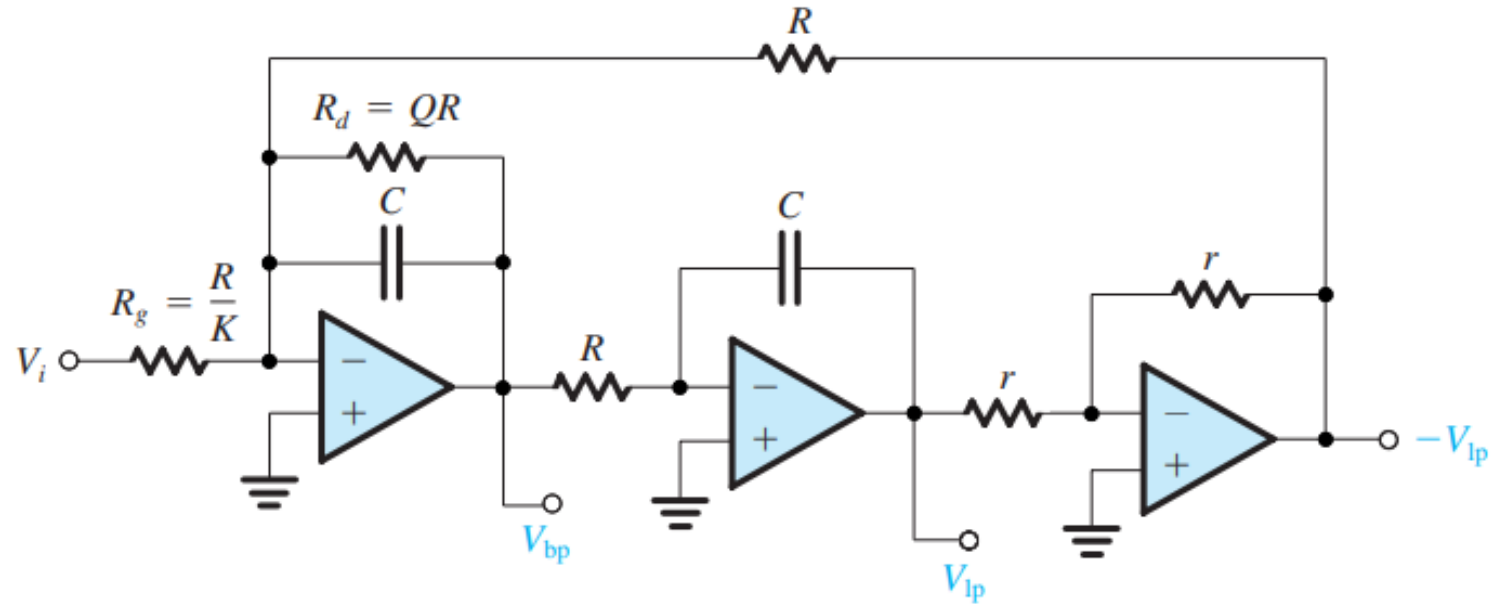

Two-Thomas Biquad Band Pass Filter

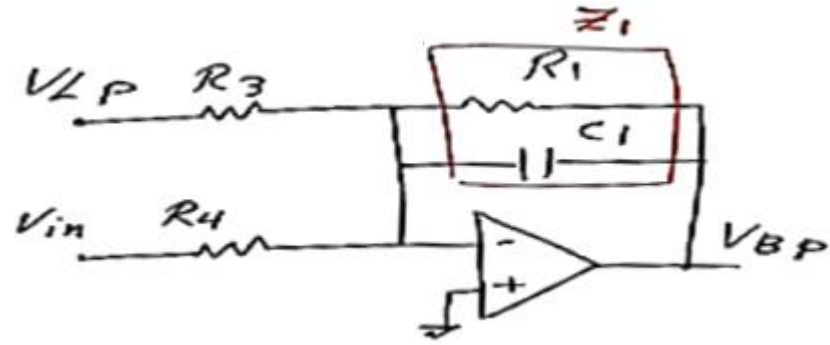
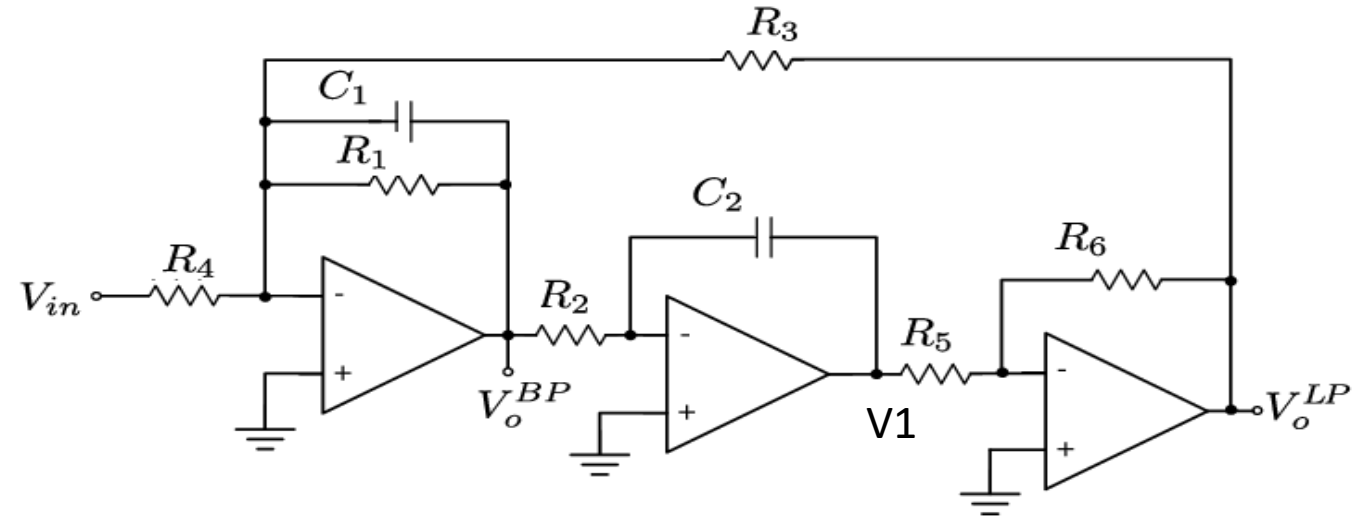
$$* Z_1 = \frac{R_1 \frac{1}{sC_1}}{R_1 + \frac{1}{sC_1}} = \frac{R_1}{sC_1 R_1 + 1}$$



① * Band-Pass Filter output (BPF)

$$V_{BP} = - \frac{Z_1}{R_3} V_{LP} - \frac{Z_1}{R_4} V_{in} \rightarrow \textcircled{1}$$

$$\text{but } V_1 = - \frac{1/sC_2}{R_2} V_{BP} = - \frac{1}{sC_2 R_2} V_{BP}$$

$$\text{and } V_{LP} = - \frac{R_6}{R_5} V_1 = - \frac{R_6}{R_5} \left[- \frac{1}{sC_2 R_2} V_{BP} \right]$$

$$\therefore V_{LP} = \frac{R_6}{R_5} \frac{1}{sC_2 R_2} V_{BP} \textcircled{2}$$

Two-Thomas Biquad Band Pass Filter


Sub. in to ①

$$\therefore V_{BP} = - \frac{Z_1}{R_3} \left[\frac{R_6}{R_5} \frac{1}{sC_2 R_2} V_{BP} \right] - \frac{Z_1}{R_4} V_i$$

$$V_{BP} \left[1 + \frac{Z_1}{R_3} \frac{R_6}{R_5} \frac{1}{sC_2 R_2} \right] = - \frac{Z_1}{R_4} V_{in}$$

$$V_{BP} \left[1 + \left(\frac{R_1}{sC_1 R_1 + 1} \right) \frac{1}{R_3} \frac{R_6}{R_5} \frac{1}{sC_2 R_2} \right] = - \frac{1}{R_4} \frac{R_1}{sC_1 R_1 + 1} V_{in}$$
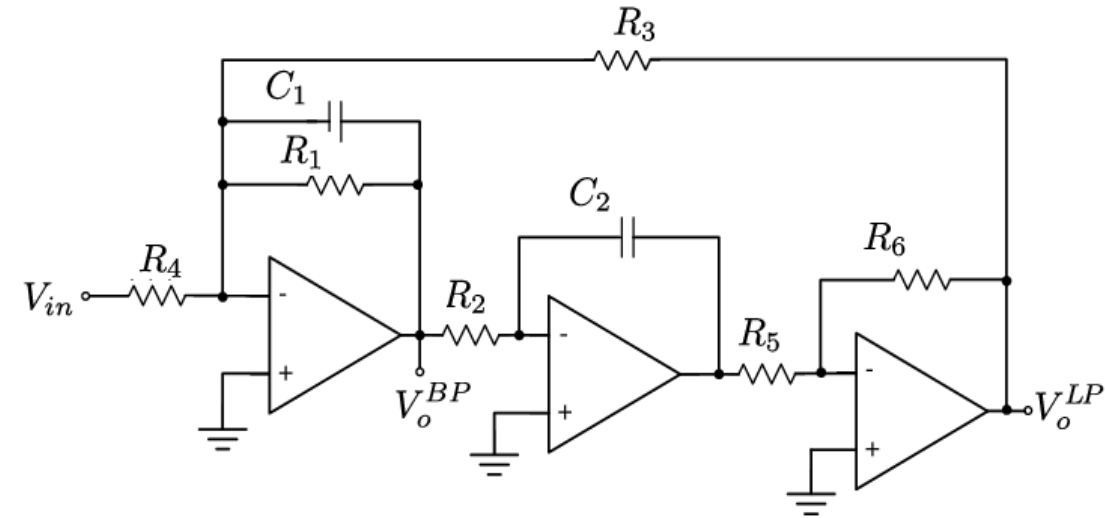
$$V_{BP} \left[\frac{(sC_1 R_1 + 1) R_3 R_5 sC_2 R_2 + R_1 R_6}{(sC_1 R_1 + 1) R_3 R_5 sC_2 R_2} \right] = \frac{-R_1}{R_4 (sC_1 R_1 + 1)} V_{in}$$



$$* Z_1 = \frac{R_1 \frac{1}{sC_1}}{R_1 + \frac{1}{sC_1}} = \frac{R_1}{sC_1 R_1 + 1}$$

Two-Thomas Biquad Band Pass Filter

$$\therefore \frac{V_{BP}}{V_{in}} = T_{BP} = \frac{-\frac{R_1}{R_4} R_3 R_5 s C_2 R_2}{(s C_1 R_1 + 1) R_3 R_5 s C_2 R_2 + R_1 R_6}$$

$$T_{BP} = \frac{-\frac{R_1}{R_4} R_3 R_5 s C_2 R_2}{s^2 R_1 R_2 C_1 C_2 R_3 R_5 + s R_2 R_3 R_5 C_2 + R_1 R_6}$$

$$T_{BP} = \frac{-\frac{R_1}{R_4} R_3 R_5 s C_2 R_2}{R_1 R_2 C_1 C_2 R_3 R_5 \left[s^2 + \frac{R_2 R_3 R_5 C_2}{R_1 R_4 C_1 C_2 R_3 R_5} s + \frac{R_1 R_6}{R_1 R_2 C_1 C_2 R_3 R_5} \right]}$$

$$T_{BP} = \frac{-\frac{1}{C_1 R_4} s}{s^2 + \frac{1}{R_1 C_1} s + \frac{(R_6 / R_5)}{R_2 R_3 C_1 C_2}} \quad \textcircled{I} = \frac{V_{B1}}{V_{in}}$$

$$T_{BP} = \frac{-a s}{s^2 + \left(\frac{\omega_0}{Q}\right) s + \omega_0^2} \quad \textcircled{II}$$

$Q \rightarrow$ quality - Factor

Two-Thomas Biquad Band Pass Filter

Comparing (I) and (II)

$$\omega_0^2 = \frac{R_6/R_5}{R_2 R_3 C_1 C_2}$$

$$\therefore \boxed{\omega_0 = \sqrt{\frac{R_6/R_5}{R_2 R_3 C_1 C_2}}}$$

and $f_0 = \frac{1}{2\pi} \sqrt{\frac{R_6/R_5}{R_2 R_3 C_1 C_2}}$

→ Center Frequency

Also, $\boxed{\frac{\omega_0}{Q} = \frac{1}{R_1 C_1}} \quad \text{III}$

$$\frac{\omega_0^2}{Q^2} = \frac{1}{R_1^2 C_1^2}$$

$$\therefore Q^2 = \omega_0^2 R_1^2 C_1^2$$

$$Q^2 = \frac{R_6/R_5}{R_2 R_3 C_1 C_2} \cdot R_1^2 C_1^2$$

$$Q^2 = \frac{R_1^2}{R_2 R_3} \cdot \frac{R_6}{R_5} \cdot \frac{C_1}{C_2}$$


$$\therefore Q = \frac{R_1}{\sqrt{R_2 R_3}} \cdot \sqrt{\frac{R_6}{R_5} \cdot \frac{C_1}{C_2}}$$

and the Band-width is

$$B.W = \frac{f_0}{Q}$$

$$f_L = f_0 - \frac{B.W}{2}$$

$$f_H = f_0 + \frac{B.W}{2}$$

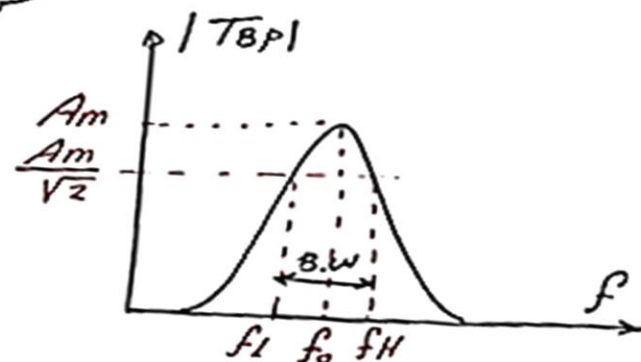

A_m = Center Frequency gain

Two-Thomas Biquad Band Pass Filter

The Center Frequency gain (A_m)

$$T_{BP} = \frac{-\frac{1}{C_1 R_4} s}{s^2 + \frac{1}{R_1 C_1} s + \frac{R_4 R_5}{R_2 R_3 C_1 C_2}}$$

$$T_{BP} = \frac{-a s}{s^2 + \left(\frac{\omega_0}{Q}\right)s + \omega_0^2}$$

$$T_{BP}(j\omega) = \frac{-j\omega a}{(j\omega)^2 + \left(\frac{\omega_0}{Q}\right)j\omega + \omega_0^2}$$

$$T_{BP}(j\omega) = \frac{-j\omega a}{[\omega_0^2 - \omega^2] + j\left(\frac{\omega_0 \omega}{Q}\right)}$$

$$|T_{BP}| = \frac{+a\omega}{\sqrt{[\omega_0^2 - \omega^2]^2 + \left(\frac{\omega_0 \omega}{Q}\right)^2}}$$

at $\omega = \omega_0 \rightarrow |T_{BP}| = A_m$

$$\therefore A_m = \frac{a\omega_0}{\sqrt{[\omega_0^2 - \omega_0^2]^2 + \left(\frac{\omega_0 \omega_0}{Q}\right)^2}} = \frac{a\omega_0}{\frac{\omega_0^2}{Q}}$$

$$\boxed{A_m = \frac{a}{\omega_0} \cdot Q} \quad (4) \quad \boxed{a = \frac{1}{C_1 R_4}} \quad (5)$$

but From III

$$\frac{\omega_0}{Q} = \frac{1}{R_1 C_1} \rightarrow \therefore \frac{Q}{\omega_0} = R_1 C_1$$

sub. into (4)

$$\therefore A_m = a \cdot \frac{Q}{\omega_0} = \frac{1}{R_4 C_1} \cdot R_1 C_1$$

$$\therefore \boxed{A_m = \frac{R_1}{R_4}}$$

Center Frequency gain

Two-Thomas Biquad Band Pass Filter

Special case:-

For $\boxed{R_5 = R_6}$ and $\boxed{C_1 = C_2 = C}$

$$* \left\{ f_0 = \frac{1}{2\pi C \sqrt{R_2 R_3}} \right\}$$

$$* \left\{ Q = \frac{R_1}{\sqrt{R_2 R_3}} \right\}$$

$$* \left\{ B.W = \frac{f_0}{Q} \right\}$$

$$* \left\{ A_m = \frac{R_1}{R_4} \right\}$$

Two-Thomas Biquad Band Pass Filter

Example 1:

Design a Two-Thomas Biquad Filter to realize a BPF with center frequency of 10 KHz and bandwidth of 100Hz. The center frequency gain (A_m) is required to be 200.

Hint: use 1 nF capacitor.

Two-Thomas Biquad Band Pass Filter

Solution:

* Assuming \rightarrow $R_5 = R_6 = 10\text{ k}\Omega$
 $C_1 = C_2 = C = 1\text{ nF}$

* $\therefore f_0 = \frac{1}{2\pi C \sqrt{R_2 R_3}} = 10^4\text{ Hz}$

$$\therefore (10^4)^2 = \frac{1}{(2\pi C)^2 R_2 R_3}$$

Assuming $R_2 = 10\text{ k}\Omega$

$$\therefore (10^4)^2 = \frac{1}{[2\pi \times 1 \times 10^{-9}]^2 (10 \times 10^3) R_3}$$

$$\therefore R_3 = 25330.3\ \Omega \approx 25.33\text{ k}\Omega$$

$$* Q = \frac{f_0}{B.W} = \frac{10^4}{100}$$

$$\therefore Q = 100 = \frac{R_1}{\sqrt{R_2 R_3}}$$

$$\therefore R_1 = Q \sqrt{R_2 R_3} = 100 \sqrt{10 \times 25.33}$$

$$\therefore R_1 = 1591.54\text{ k}\Omega \approx 1.591\text{ M}\Omega$$

* Center Frequency Gain (A_m)

$$A_m = \frac{R_1}{R_4} = 200$$

$$\therefore R_4 = \frac{R_1}{200} = \frac{1591.54}{200}$$

$$R_4 = 7.9577\text{ k}\Omega$$

Two-Thomas Biquad Low Pass Filter

[2] Low Pass Filter output: (LPF)

From (2)

$$V_{LP} = \frac{R_6}{R_5} \frac{1}{s C_2 R_2} V_{BP}$$

$$\therefore V_{LP} = \frac{R_6}{R_5} \frac{1}{s C_2 R_2} \left\{ \frac{-\frac{1}{C_1 R_4} s}{s^2 + \frac{1}{R_1 C_1} s + \frac{R_6/R_5}{R_2 R_3 C_1 C_2}} V_{in} \right\}$$

$$\therefore T_{LP} = \frac{V_{LP}}{V_{in}} = \frac{-\left(\frac{R_6/R_5}{R_2 R_4 C_1 C_2}\right)}{s^2 + \frac{1}{R_1 C_1} s + \frac{R_6/R_5}{R_2 R_3 C_1 C_2}}$$

but

$$T_{LP} = \frac{-a}{s^2 + \left(\frac{\omega_0}{Q}\right)s + \omega_0^2}$$

$$a = \frac{R_6/R_5}{R_2 R_4 C_1 C_2}$$

$$\omega_0 = \sqrt{\frac{R_6/R_5}{R_2 R_3 C_1 C_2}}$$

$$\therefore f_0 = \frac{1}{2\pi} \sqrt{\frac{R_6/R_5}{R_2 R_3 C_1 C_2}}$$

$$\frac{\omega_0}{a} = \frac{1}{R_1 C_1}$$

$$\therefore Q = \frac{R_1}{\sqrt{R_2 R_3}} \sqrt{\frac{R_6}{R_5} \cdot \frac{C_1}{C_2}}$$


Max. gain (D.C gain)

put $s = 0$

$$|T_{LP}| = A_m = \frac{a}{\omega_0^2}$$

$$A_m = \frac{R_6}{R_5} \frac{1}{R_2 R_4 C_1 C_2} \cdot \frac{R_2 R_3 C_1 C_2}{R_6/R_5}$$

$$A_m = \frac{R_3}{R_4}$$

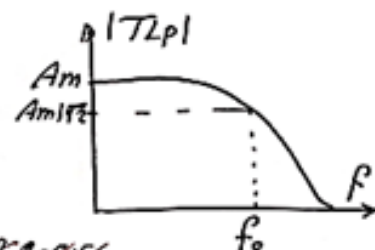

Two-Thomas Biquad Low Pass Filter

Example 2:

Design Two-Thomas Biquad Filter to realize a LPF with a cut-off Frequency 10KHz. (use 1 nF capacitors) The D.C gain is 100.

Two-Thomas Biquad Low Pass Filter

Solution:

* Assuming

$$[R_5 = R_6 = 10 \text{ k}\Omega]$$

$$[C_1 = C_2 = C = 1 \text{ nF}]$$

$$* f_0 = \frac{1}{2\pi C} \frac{1}{\sqrt{R_2 R_3}}$$

$$(10^4) = \frac{1}{2\pi(1 \times 10^{-9}) \sqrt{R_2 R_3}}$$

Assuming $[R_2 = 10 \text{ k}\Omega]$

$$\therefore [R_3 = 25.33 \text{ k}\Omega]$$

$$* Q = \frac{1}{\sqrt{2}} \quad (\text{LPF})$$

$$Q = 0.707 = \frac{R_1}{\sqrt{R_2 R_3}}$$

$$\therefore R_1 = Q \sqrt{R_2 R_3}$$

$$R_1 = 0.707 \sqrt{10 \times 25.33}$$

$$[R_1 = 11.254 \text{ k}\Omega]$$

* D.C. Gain (A_m)

$$A_m = \frac{R_3}{R_4}$$

$$100 = \frac{25.33 \text{ k}\Omega}{R_4}$$

$$\therefore \{ R_4 = 0.2533 \text{ k}\Omega \}$$
$$= 253.3 \Omega$$

~~≠~~