
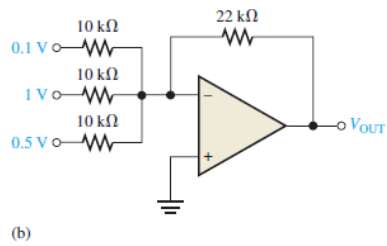

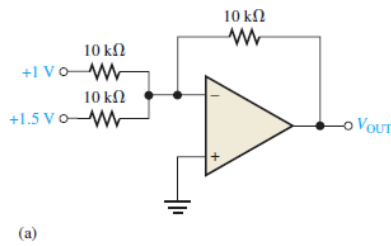
## Sheet P.1

Wednesday, November 16, 2022 1:19 PM

Determine the output voltage for each circuit shown.




$$a) V_o = 1V \times -\frac{10}{10} + 1.5V \times -\frac{10}{10} = -2.5V$$

$$b) V_o = -\left( \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$
$$= -3.52V$$
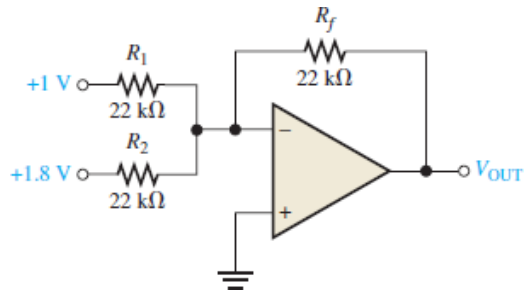
## Sheet P.2

Wednesday, November 16, 2022 1:21 PM

For the circuit shown, determine  $V_{out}$ . Also, find the value of  $R_f$  necessary to produce an output that is five times the sum of the inputs in the shown circuit.



$$V_{out} = -2.8 \text{ V}$$

$$V_{out} = -\frac{R_f}{R} (V_1 + V_2)$$


$$\frac{R_f}{R} = 5 \quad \therefore R = R_1 = R_2 = 22 \text{ k}\Omega$$

$$\therefore R_f = 110 \text{ k}\Omega$$
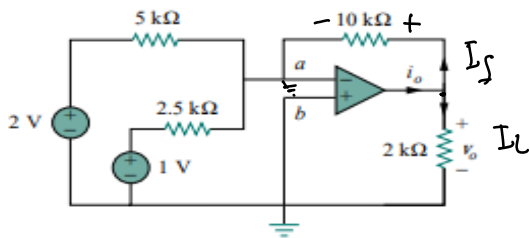
## Sheet P.3

Wednesday, November 16, 2022 1:21 PM

Calculate  $V_o$  and  $i_o$  for the following Op-amp circuit.



$$V_{out} = 2 * \frac{10k}{5k} + 1 * \frac{10k}{2.5k} = -8 V$$

using KCL at output node

$$I_o = I_f + I_L$$


$$I_f = \frac{V_o}{10k} \quad I_L = \frac{V_o}{2k}$$

$$I_o = -4.8 mA$$
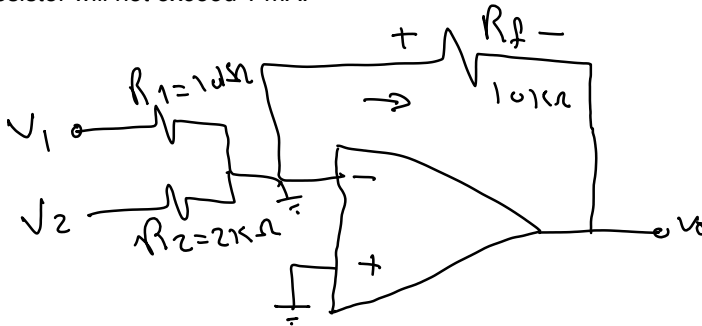
## Sheet P.4

Wednesday, November 16, 2022 1:22 PM

Design an inverting op-amp circuit to form the weighted sum  $V_o$  of two inputs  $V_1$  and  $V_2$ . It is required that  $V_o = -(V_1 + 5V_2)$ . Choose values for  $R_1$ ,  $R_2$ , and  $R_f$  so that for a maximum output voltage of 10V the current in the feedback resistor will not exceed 1 mA.



$$V_o = -(V_1 + 5V_2)$$

$$= -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2\right)$$

$$\frac{R_f}{R_1} = 1 \rightarrow R_f = R_1 \rightarrow \textcircled{1}$$

$$\frac{R_f}{R_2} = 5 \rightarrow R_f = 5R_2 \rightarrow \textcircled{2}$$

$$R_f = \left| \frac{0 - V_o}{I_f} \right| = \left| \frac{0 - 10}{1 \text{ mA}} \right| = 10 \text{ k}\Omega$$

from eq 1

$$R_1 = 10 \text{ k}\Omega$$


from eq 2

$$R_2 = 2 \text{ k}\Omega$$
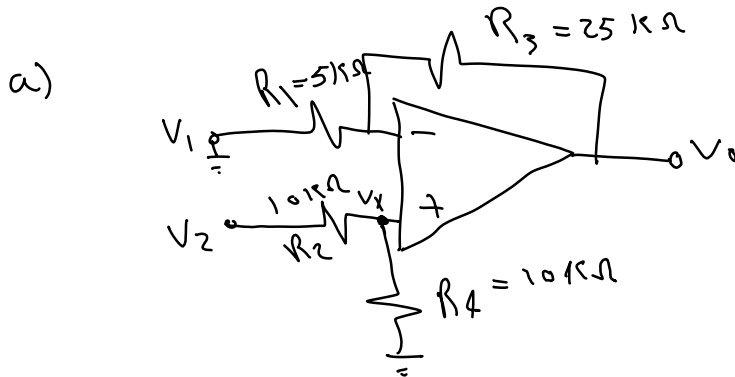
## Sheet P.5

Wednesday, November 16, 2022 1:22 PM

Design Op-amp circuit with inputs  $V_1$  and  $V_2$  such that  $V_o = -5V_1 + 3V_2$  using:  
 a. Only one Op-amp.                      b. More than one Op-amp.



$$V_o = V_{o1} + V_{o2}$$

$$= -\frac{R_3}{R_1} V_1 + V_x \left(1 + \frac{R_3}{R_1}\right)$$

using voltage divider

$$V_x = V_2 \frac{R_4}{R_2 + R_4}$$

$$V_o = -\frac{R_3}{R_1} V_1 + \underbrace{\frac{R_4}{R_2 + R_4} \left(1 + \frac{R_3}{R_1}\right)}_{\substack{\downarrow \\ -5}} V_2$$

$$= -5 V_1 + 3 V_2$$

$$\frac{R_3}{R_1} = 5 \rightarrow \textcircled{1}$$

$$\frac{R_4}{R_2 + R_4} (1 + 5) = 3$$

$$\frac{R_4}{R_2 + R_4} = \frac{1}{2} \rightarrow 2R_4 = R_2 \rightarrow R_4$$


$$\therefore R_4 = R_2 \rightarrow \textcircled{2}$$

$$\text{Let } R_1 = 5 \text{ k}\Omega$$

$$\therefore R_3 = 25 \text{ k}\Omega$$

$$\text{Let } R_2 = 10 \text{ k}\Omega$$

$$\therefore R_4 = 10 \text{ k}\Omega$$

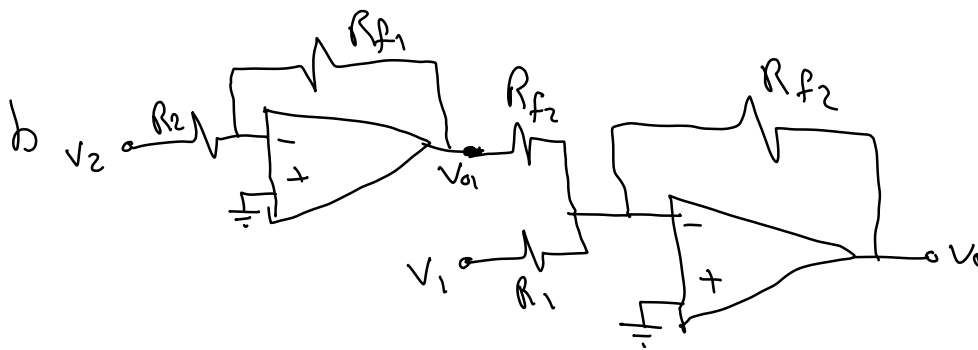

$$V_{01} = -\frac{R_{f1}}{R_2} V_2$$

$$V_0 = -\frac{R_{f2}}{R} V_{01} + \frac{-R_{f2}}{R_1} V_1$$

$$= +\frac{\cancel{R_{f2}}}{\cancel{R_{f2}}} \cdot \frac{R_{f1}}{R_2} V_2 - \frac{R_{f2}}{R_1} V_1$$

$$= +3V_2 - 5V_1$$

$$\frac{R_{f2}}{R_1} = 5 \rightarrow \textcircled{1}$$

$$\frac{R_{f1}}{R_2} = 3 \rightarrow \textcircled{2}$$

$$\text{Let } R_1 = 3 \text{ k}\Omega$$

$$\therefore R_{f2} = 15 \text{ k}\Omega$$

$$\text{Let } R_2 = 3 \text{ k}\Omega$$


$$\therefore R_{f1} = 9 \text{ k}\Omega$$

## Sheet P.6

Wednesday, November 16, 2022 1:23 PM

Consider the difference-amplifier shown, for the case  $R_1 = R_3 = 2 \text{ k}\Omega$  and  $R_2 = R_4 = 200 \text{ k}\Omega$ .

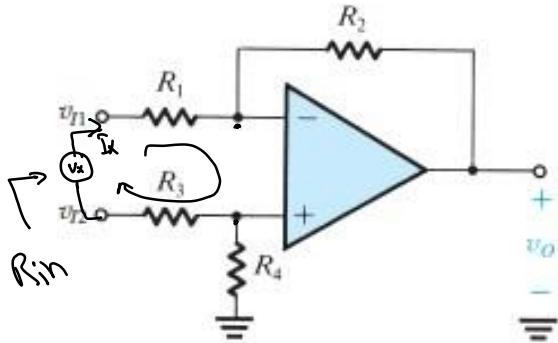- Find the value of the differential gain  $A_d$ .
- Find values for the resistances in the circuit so that the circuit behaves as a difference amplifier with an input resistance of  $20 \text{ k}\Omega$  and a gain of 10.



a)

$$V_o = (V_{i2} - V_{i1}) \underbrace{\frac{R_2}{R_1}}$$

$$A_d = \frac{R_2}{R_1} = \frac{200}{2} = 100$$

b) KVL

$$\begin{aligned} V_x &= I_x R_1 + I_x R_3 \\ &= I_x (R_1 + R_3) \end{aligned}$$

$$\frac{V_x}{I_x} = R_{in} = R_1 + R_3$$

$$20 \text{ k}\Omega + R_1 = R_3 \quad \text{and} \quad R_2 = R_4$$

$$R_{in} = 20 \text{ k}\Omega \rightarrow R_1 = R_3 = 10 \text{ k}\Omega$$


$$\frac{R_2}{R_1} = 10 \rightarrow R_2 = 100 \text{ k}\Omega = R_4$$


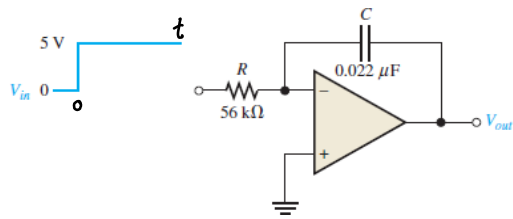
## Sheet P.7

Wednesday, November 16, 2022 1:24 PM

Determine the rate of change of the output voltage in response to the step input to the integrator shown in figure.



$$V_o = -\frac{1}{RC} \int V_i dt$$


$$= -\frac{1}{RC} \int_0^t 5 dt$$

$$V_o = -4058 t$$
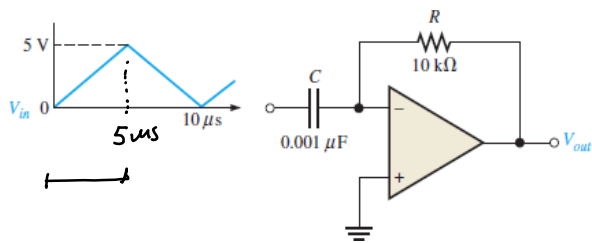
## Sheet P.8

Wednesday, November 16, 2022 1:25 PM

A triangular waveform is applied as an input to the circuit shown. Determine what the output should be and sketch its waveform in relation to the input.



$$V_{out} = -RC \frac{dV_{in}}{dt}$$

for  $0 < t < 5\mu s$

$$V_o = -RC \frac{5 - 0}{5\mu s - 0} = -10V$$

for  $5\mu s < t < 10\mu s$

$$V_o = -RC \frac{0 - 5}{10\mu s - 5\mu s} = 10V$$

