

Electronic Circuits



Operational Amplifier

Lecture 2


Dr. Roaa Mubarak

Operational Amplifier (Ideal vs. Actual)


Properties	Ideal	Actual (Real or Typical)
1. Open loop gain	∞	High $\geq 10^4$
2. Open loop bandwidth	∞	Very high
3. Input resistance	∞	High $\geq 10 \text{ M}\Omega$
4. Output resistance	0	Low $\leq 500 \Omega$
5. Input current	0	$< 0.5 \mu\text{A}$
6. Offset voltage & current	0	Low $< 10\text{mv}$, $< 0.2 \text{ nA}$

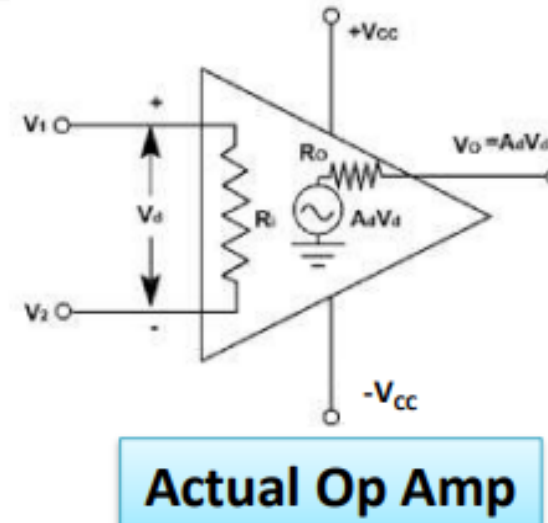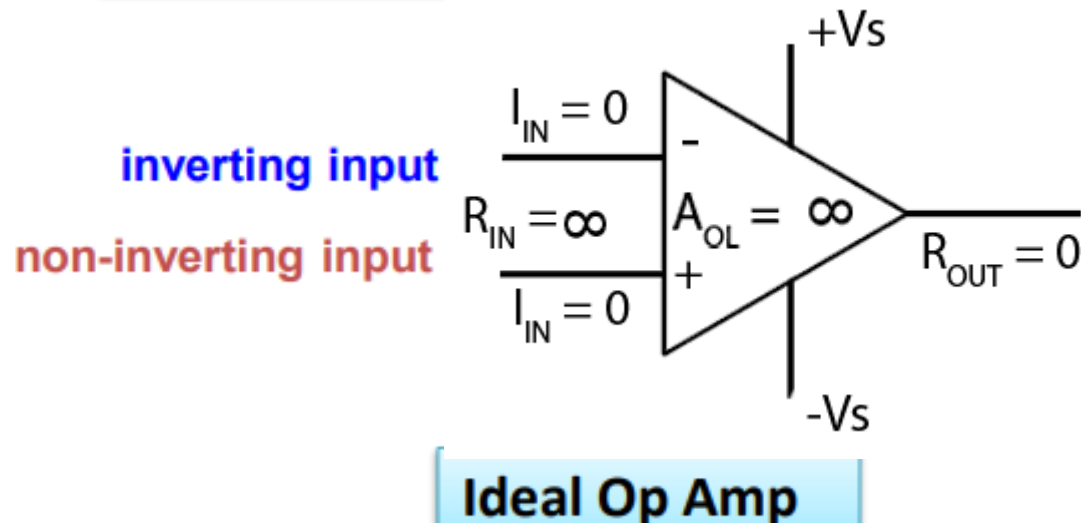


Actual Operational Amplifier

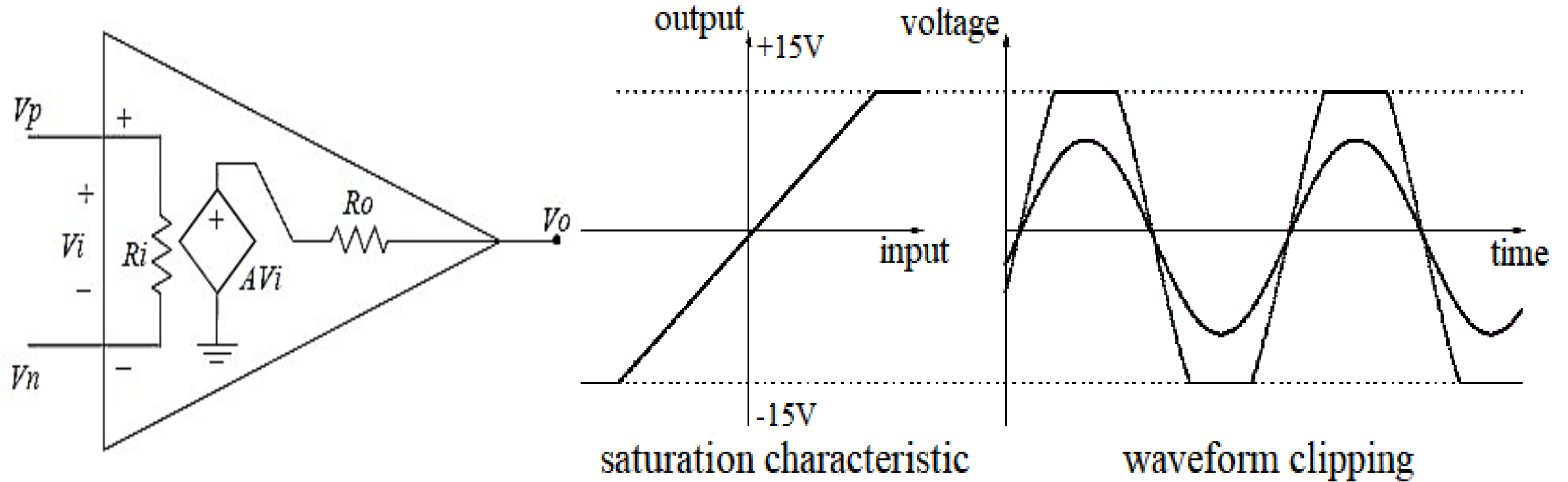

Ideal Operational Amplifier

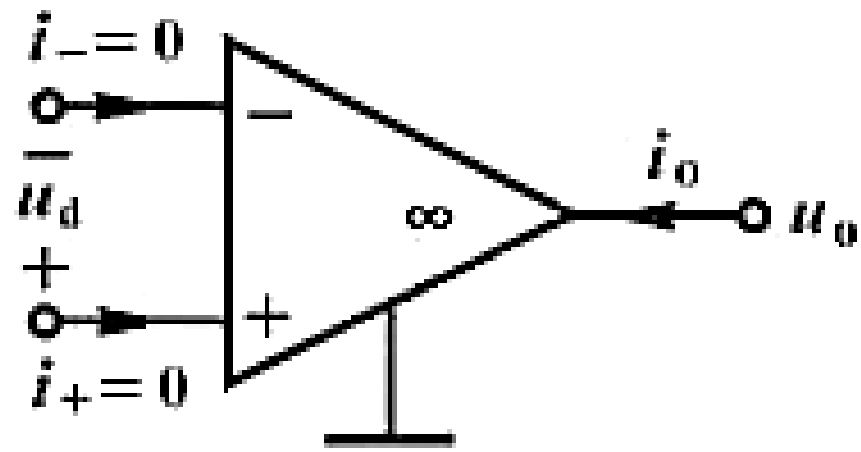


(a)

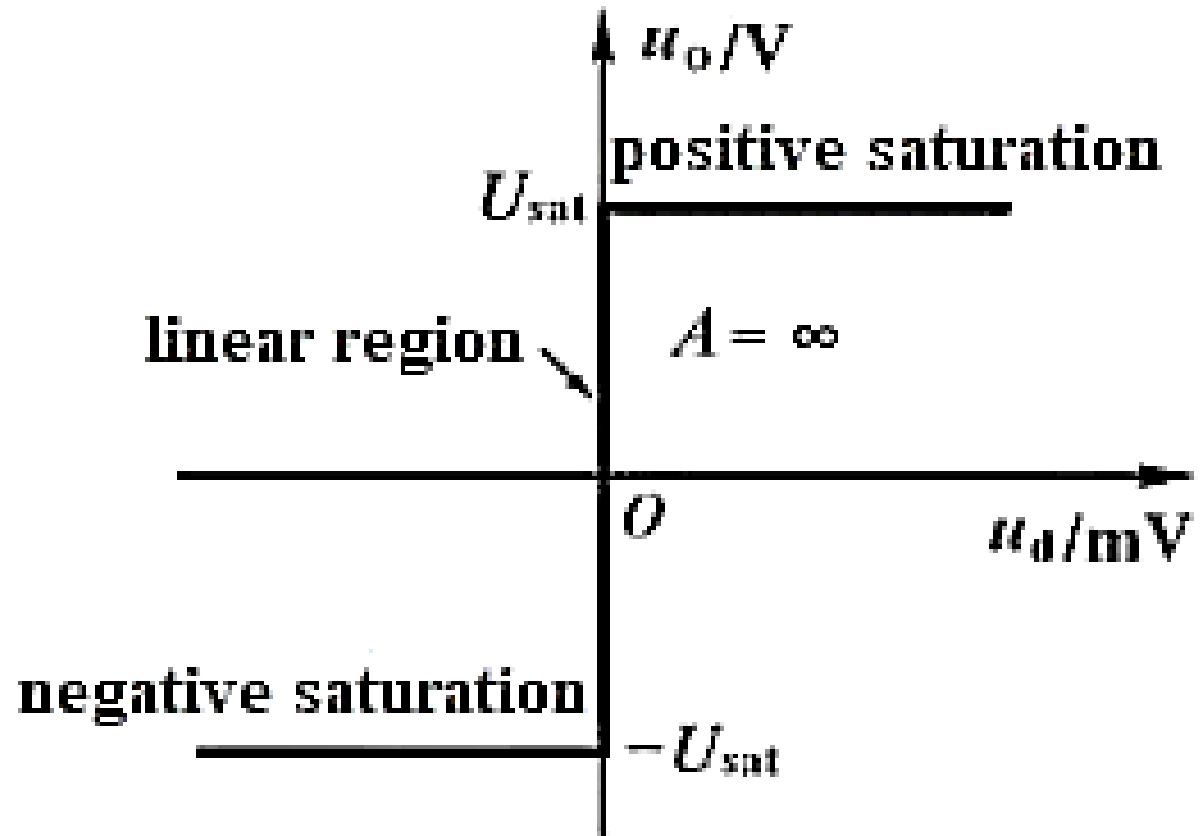

(b)

Ideal Op-Amp

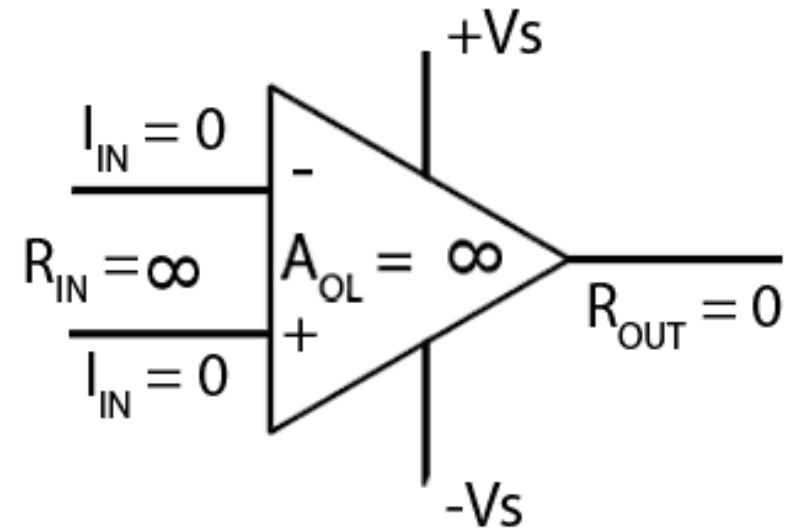
- The input Currents of Op-Amp $I_{in} = 0$ ($R_{in} = \infty$)
- Infinite Voltage gain $A = \infty$
- Zero Output Impedance ($R_{out} = 0$)



Gulden Rules of Op-Amp

- The inputs to the op-amp draw or source no current (true whether negative feedback or not)
- The output attempts to do whatever is necessary to make the voltage difference between the inputs zero
- The op-amp with negative feedback forces the two inputs v_+ and v_- to have the same voltage, even though no current flows into either input. This is sometimes called a “Virtual short”

Negative Feedback

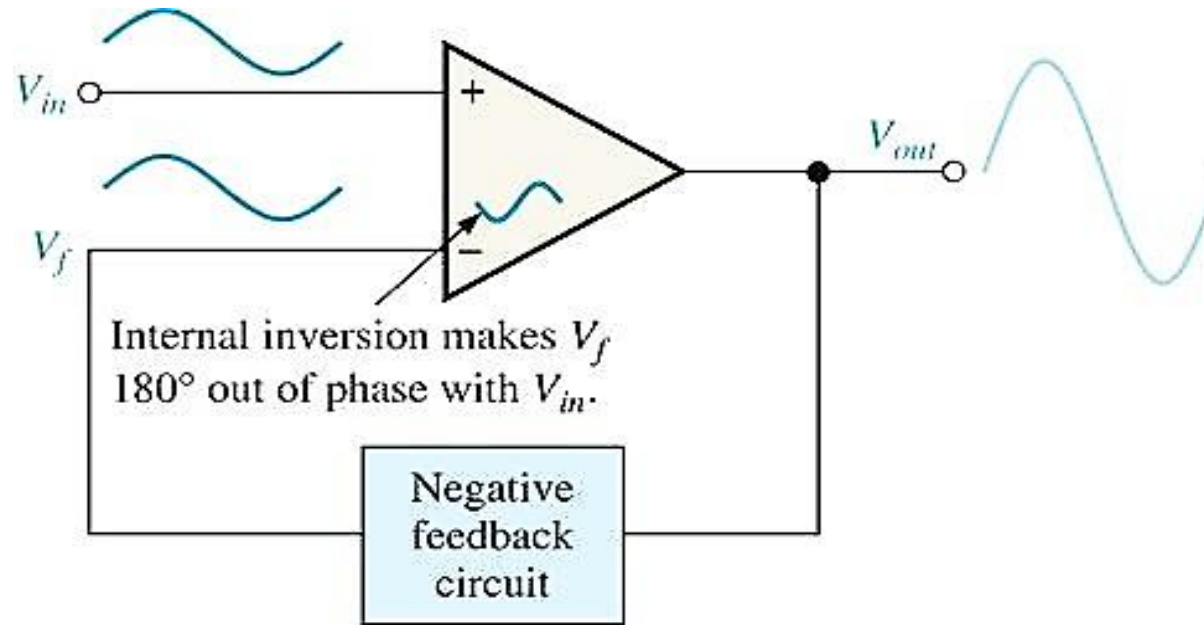

- Negative feedback is the process whereby a portion of the output voltage of an amplifier is returned to the input with a phase angle that is opposite to the input signal.
- The open-loop gain of an op-amp is usually very high (more than 100,000).
- With negative feedback the gain of op-amp (called close-loop gain A_{cl}) can be reduced and controlled so that an op-amp can function as a linear amplifier.

Op-Amp with Negative Feedback

- Close-Loop Voltage Gain, A_{cl}

- ❑ The close-loop voltage gain is the voltage of an op-amp with external feedback.
- ❑ The amplifier circuit consists of an op-amp and an external negative feedback circuit.
- ❑ The feedback from the output is connected to the inverting input of the op-amp.
- ❑ The negative feedback is determined and controlled by external components.

Op-Amp Applications

Linear Applications

- 1- The Inverting Amplifier
- 2-The Noninverting Amplifier
- 3- Summing Amplifier
- 4- Subtractor
- 5- Voltage Follower
- 6- Controlled Sources
- 7- Integrator
- 8- Differentiator

Op-Amp Applications

- Non linear Applications

9- Logarithmic Amplifier

10- Anti-Logarithmic Amplifier

11- Analog Multiplier

12- Analog Divider

13- Voltage Regulator

14- Comparator

15- Schmitt Trigger

16- Digital to Analog Converter


17- Rectifying using Op-Amp

18- Clipping using Op-Amp

19- Instrumentation Amplifier

Op-Amp Applications

1-Inverting Amplifier

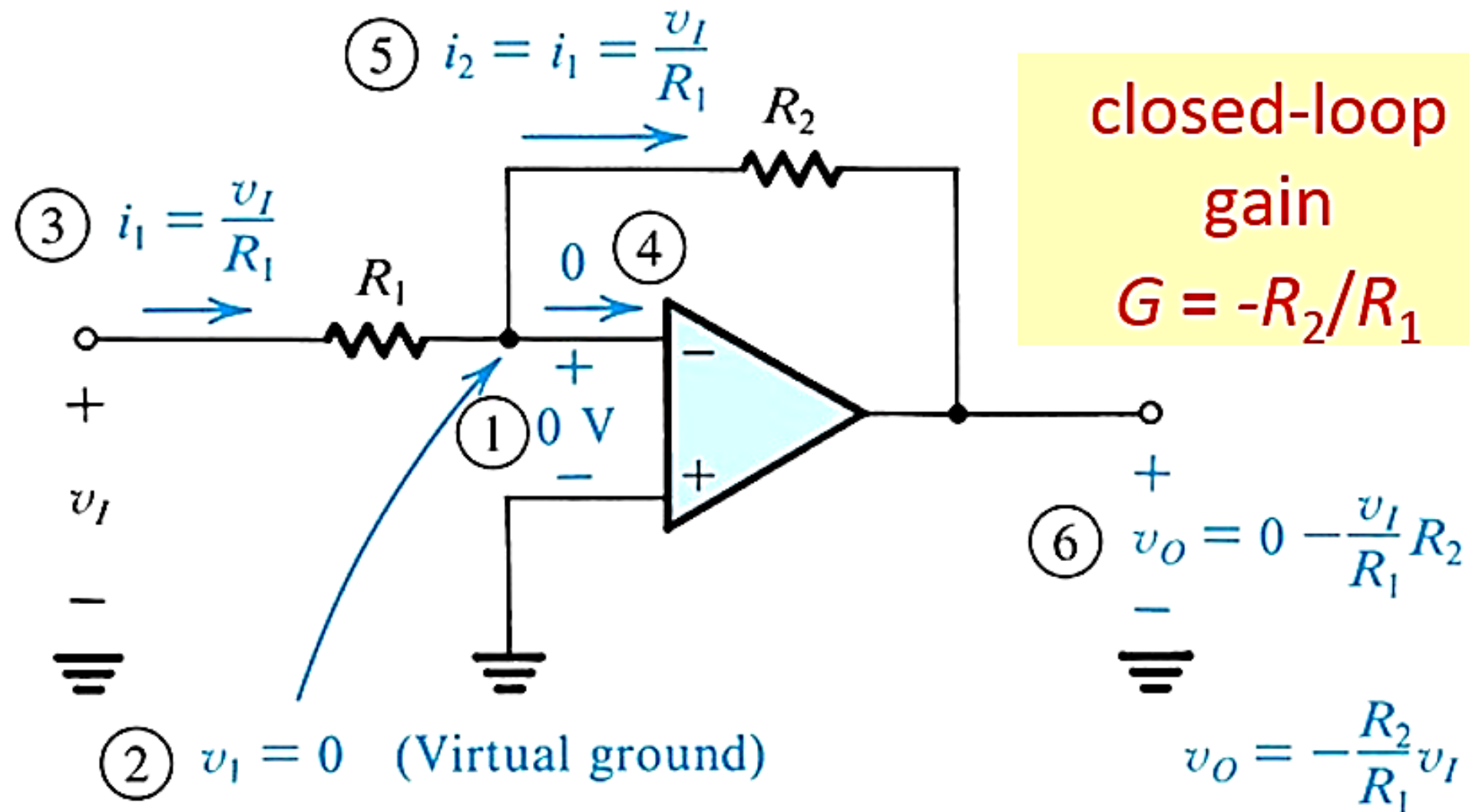

1-Inverting Amplifier

We Have

$$I_{in} = \frac{V_{in}}{R_i} \quad I_f = \frac{-V_{out}}{R_f}$$



Since $I_{in} = I_f$

$$\frac{V_{in}}{R_i} = \frac{-V_{out}}{R_f}$$


$$\frac{V_{out}}{V_{in}} = -\frac{R_f}{R_i}$$

The closed loop gain

$$A_{cl(I)} = -\frac{R_f}{R_i}$$

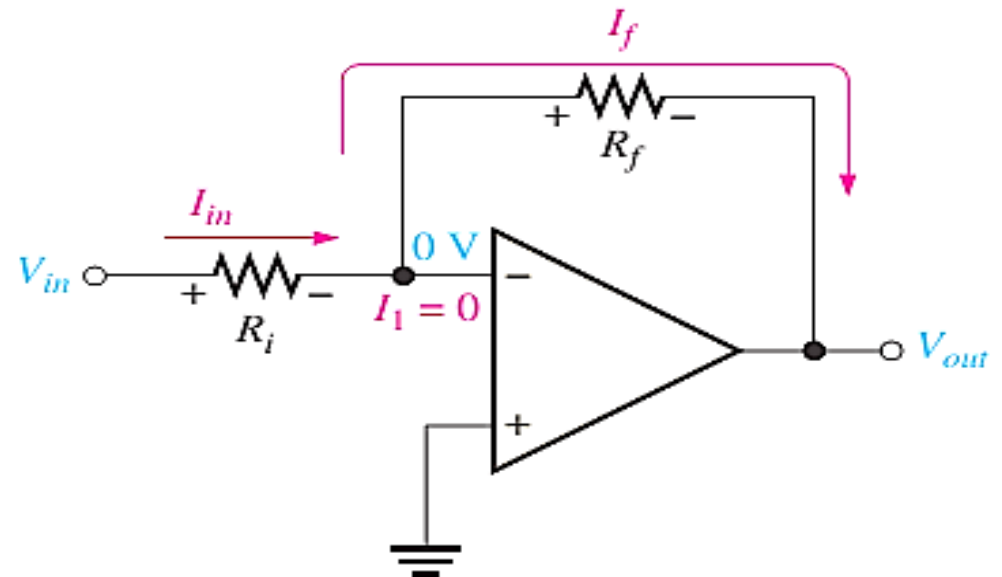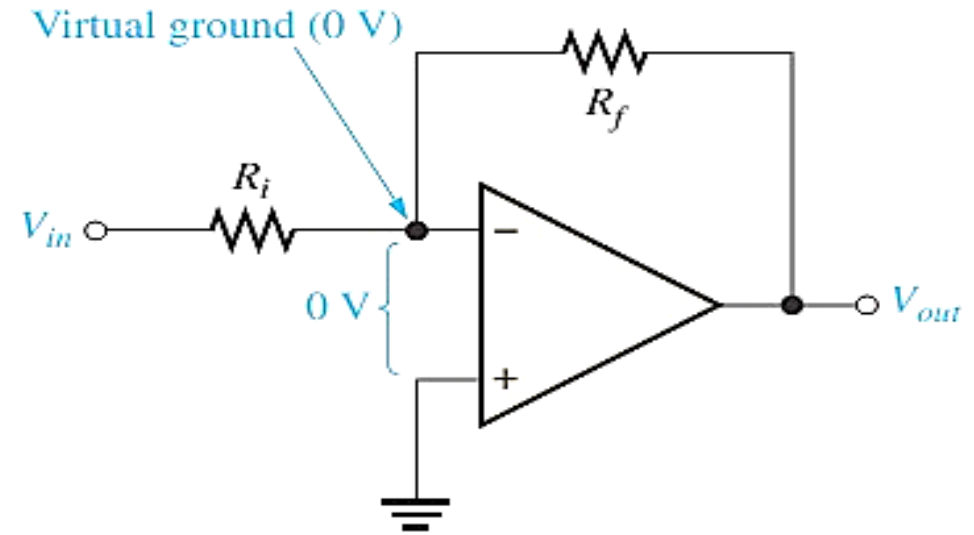

1-Inverting Amplifier

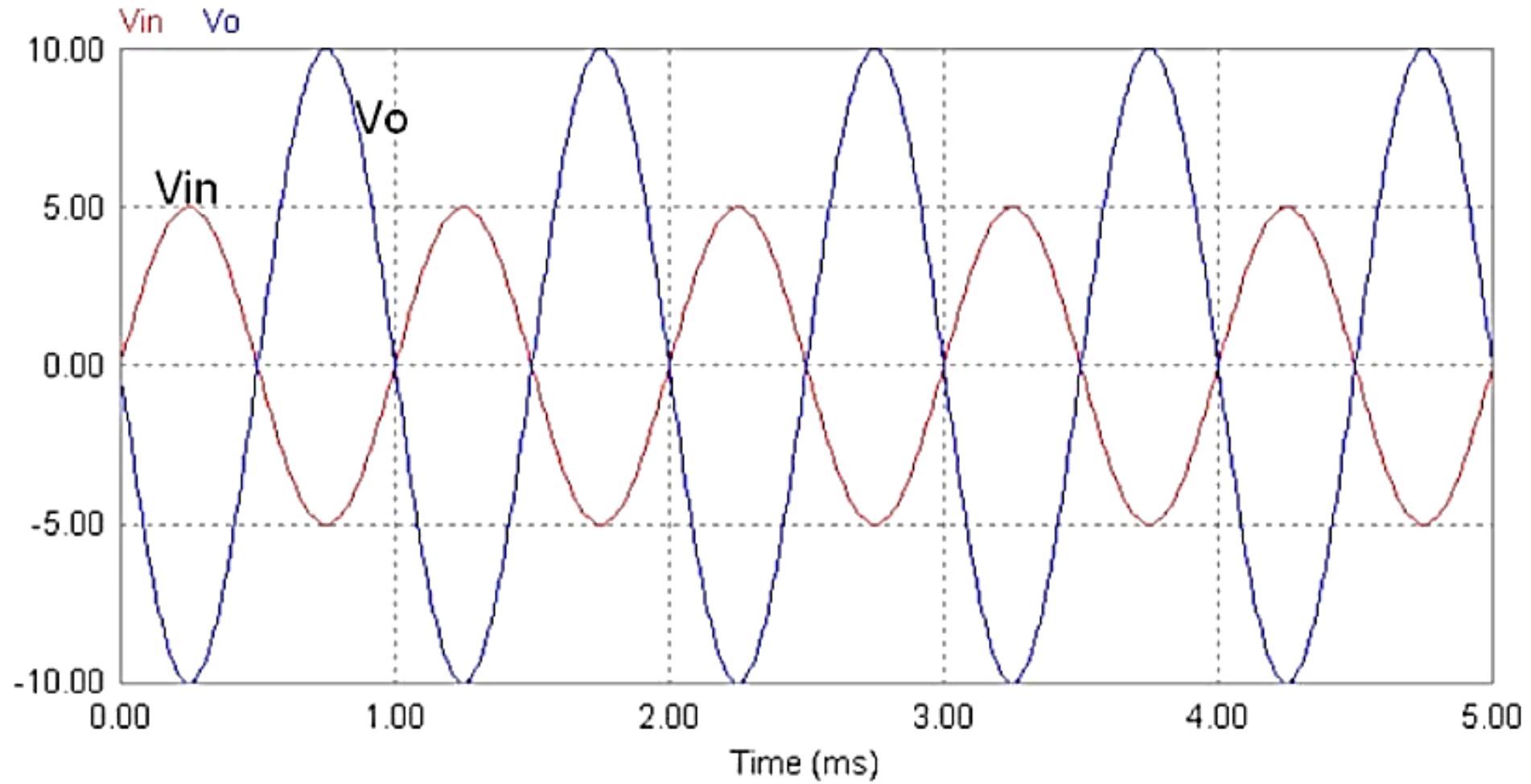


1-Inverting Amplifier example

Determine the gain of the inverting amplifier shown.

Solution:


$$\begin{aligned}A_{cl(I)} &= -\frac{R_f}{R_i} \\&= -\frac{82 \text{ k}\Omega}{3.3 \text{ k}\Omega} \\&= -24.8\end{aligned}$$

The minus sign
indicates inversion.


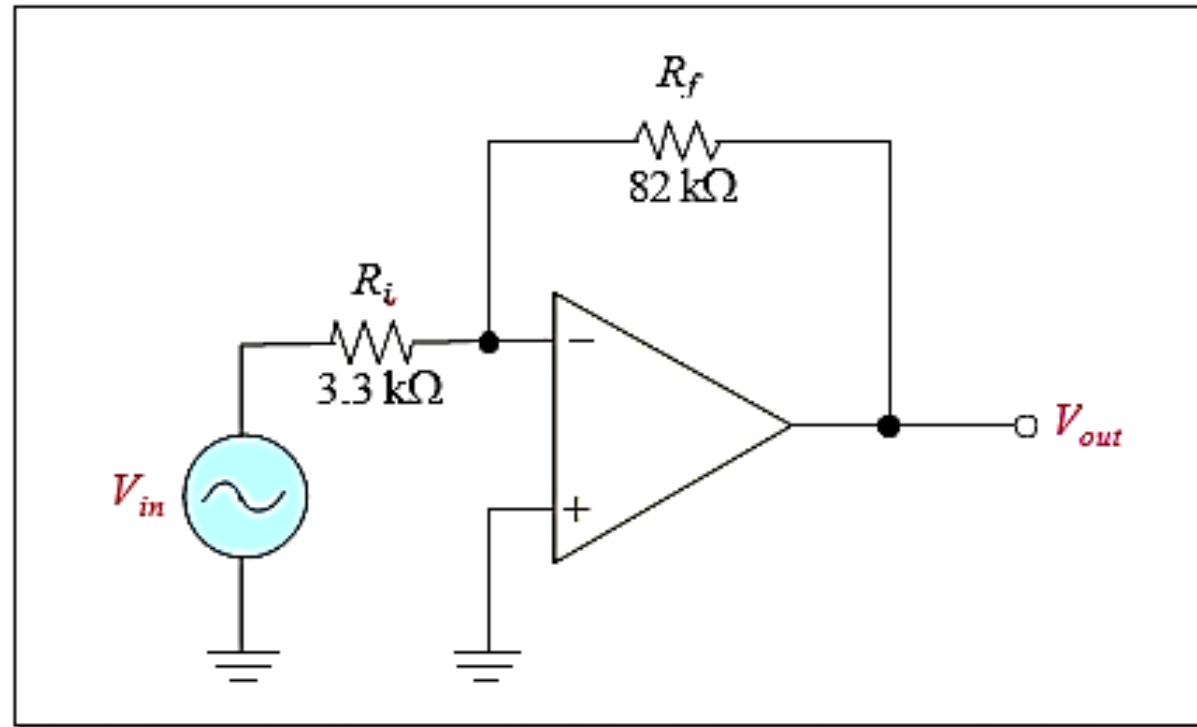


2- Noninverting Amplifier

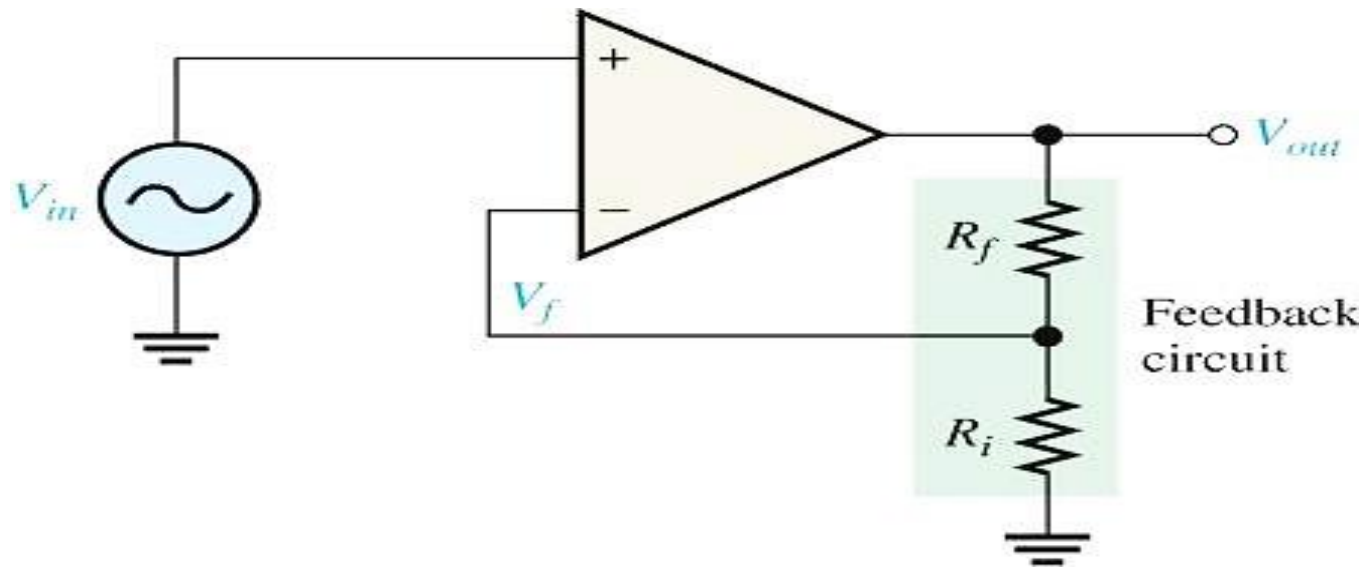- A **noninverting amplifier** is a configuration in which the signal is on the noninverting input and a portion of the output is returned to the inverting input.
- The feedback circuit is formed by input resistance R_i and feedback resistance R_f .
- This feedback creates a voltage divider circuit which reduces V_{out} and connects the reduced voltage V_f to the inverting input



2- Noninverting Amplifier

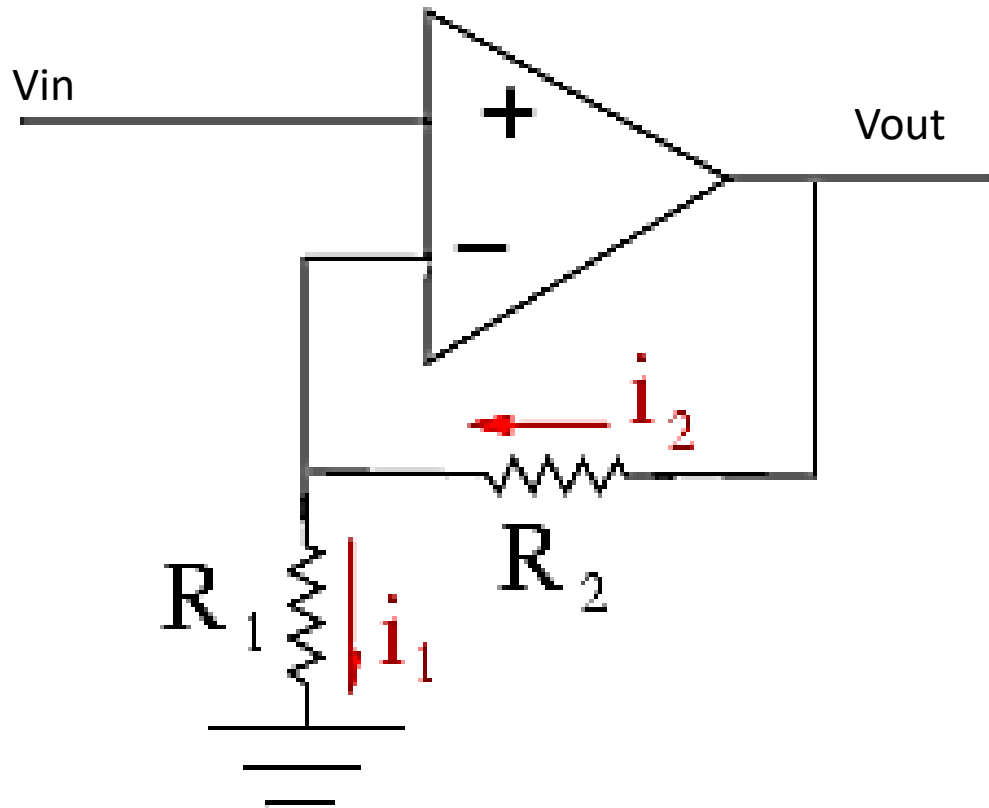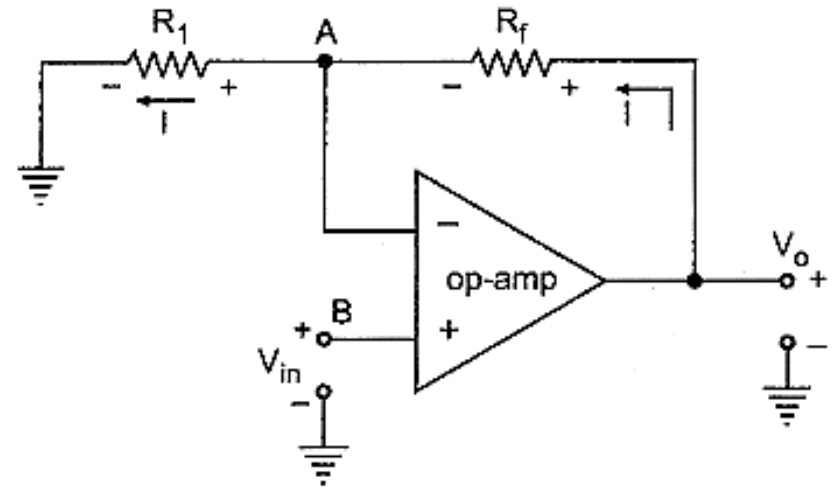


$$i_2 - i_1 = 0$$

$$\frac{V_{out} - V_{in}}{R_2} - \frac{V_{in}}{R_1} = 0$$

$$\frac{V_{out}}{V_{in}} = \frac{(R_1 + R_2)}{R_1}$$

2- Noninverting Amplifier

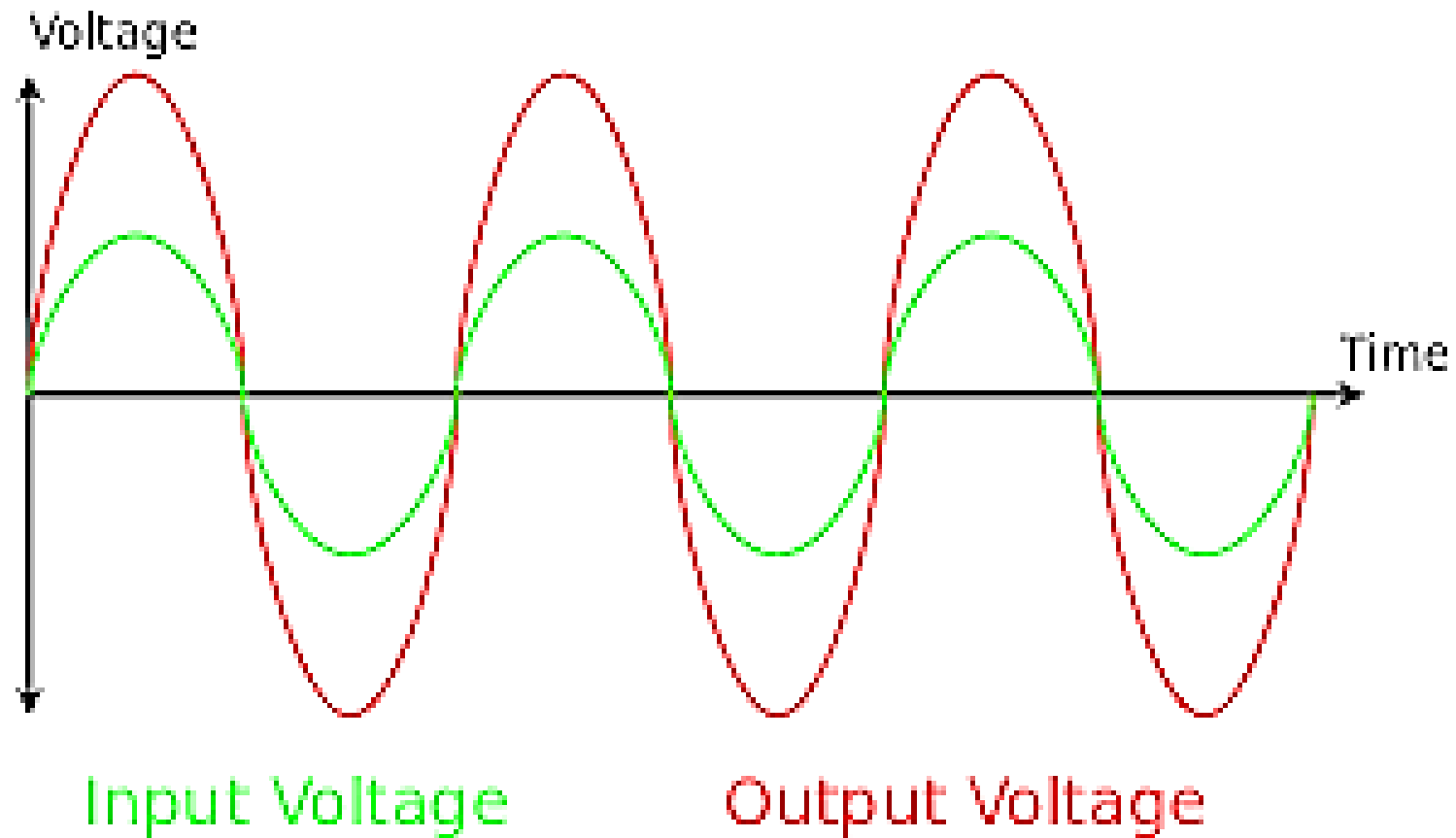

2-Noninverting Amplifier example

Determine the gain of the noninverting amplifier shown.

Solution:

$$\begin{aligned}A_{cl(NI)} &= 1 + \frac{R_f}{R_i} \\&= 1 + \frac{82 \text{ k}\Omega}{3.3 \text{ k}\Omega} \\&= 25.8\end{aligned}$$

