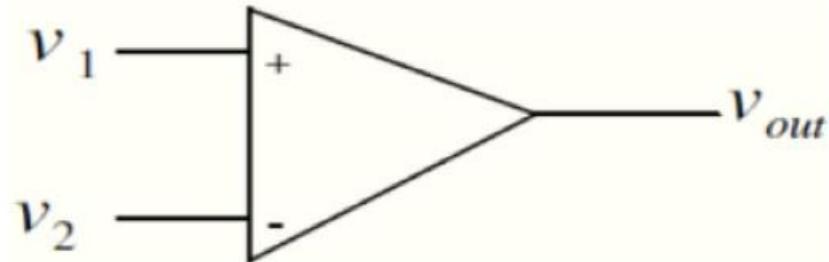


The Differential Amplifier

Introduction

- Differential Amplifiers are used extensively in IC
- They are more immune to Noise and Interference Signals
- No need for Bypass and coupling capacitors
- Example: the Voltage op-amp is a differential amplifier

$$V_{\text{Out}} = A_V(V_1 - V_2)$$




E. Sawires

- The Differential Amplifier amplifies the difference between its input terminals and rejects their average (Common Mode).
 - The differential input signal v_{Id} is simply the difference between the two input signals v_1 and v_2 ; that is,
- $$v_{Id} = (v_1 - v_2)$$
- The common-mode input signal v_{Icm} is the average of the two input signals v_1 and v_2 ; namely,
- $$v_{Icm} = \frac{(v_1 + v_2)}{2}$$
- The previous equations can be used to express the input signals v_1 and v_2 in terms of their differential and common-mode components as follows:

$$v_1 = \frac{v_{Id}}{2} + v_{Icm}$$

$$v_2 = -\frac{v_{Id}}{2} + v_{Icm}$$

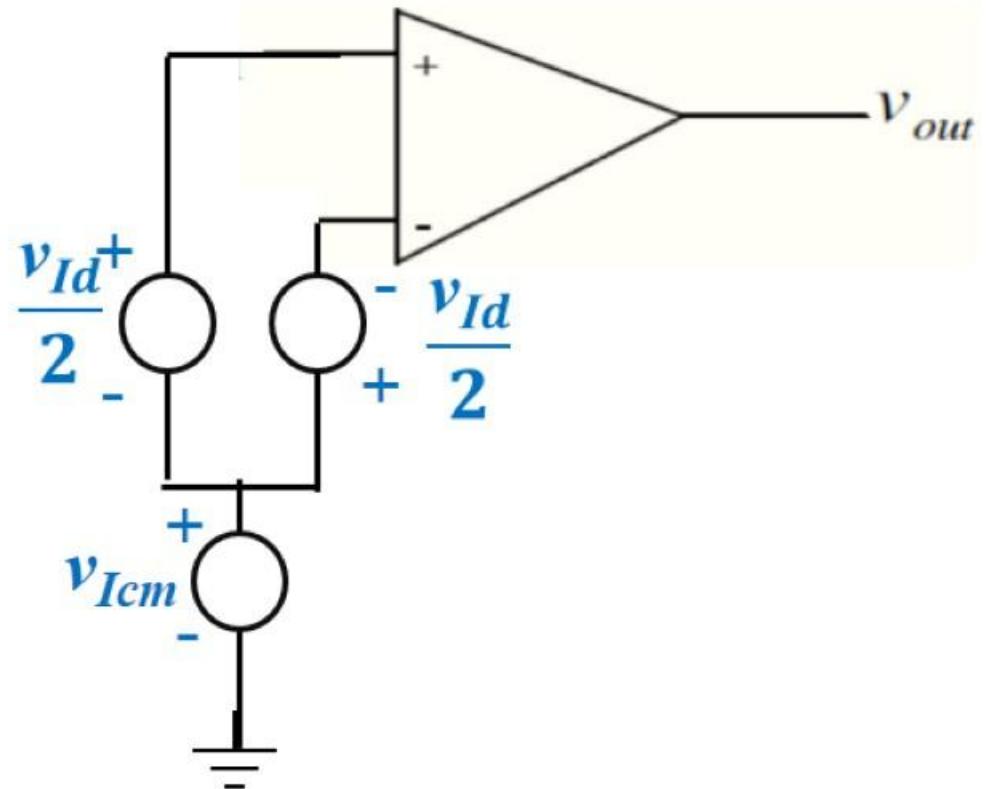

$$v_{out} = A_d v_{Id} + A_{cm} v_{Icm}$$

Objective


- Calculation of the Differential Mode Gain of the amplifier (**ideally tends to infinity**)
- Calculation of the Common Mode Gain of the amplifier (**ideally tends to ZERO**)
- Calculation of the Common Mode Rejection Ratio (CMRR) (**ideally tends to infinity**)

$$A_d = \frac{v_{out}}{v_{Id}}$$

$$A_{cm} = \frac{v_{out}}{v_{Icm}}$$

$$CMRR = \left| \frac{A_d}{A_{cm}} \right|$$

The BJT Differential Pair

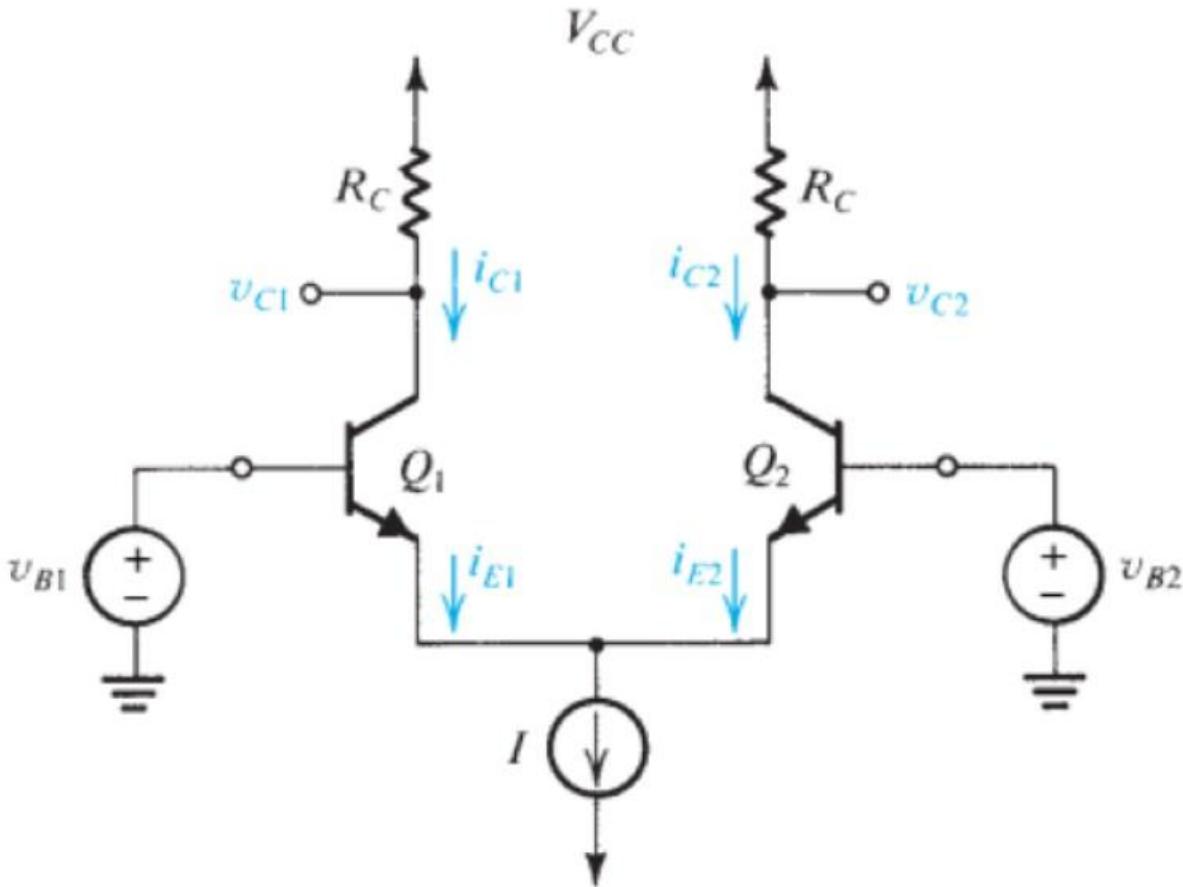

The basic BJT differential-pair configuration.


Large Signal Analysis for Differential Amplifier

Basic Operation

BJT Differential Amplifier/Pair

Emitter Coupled Circuit:

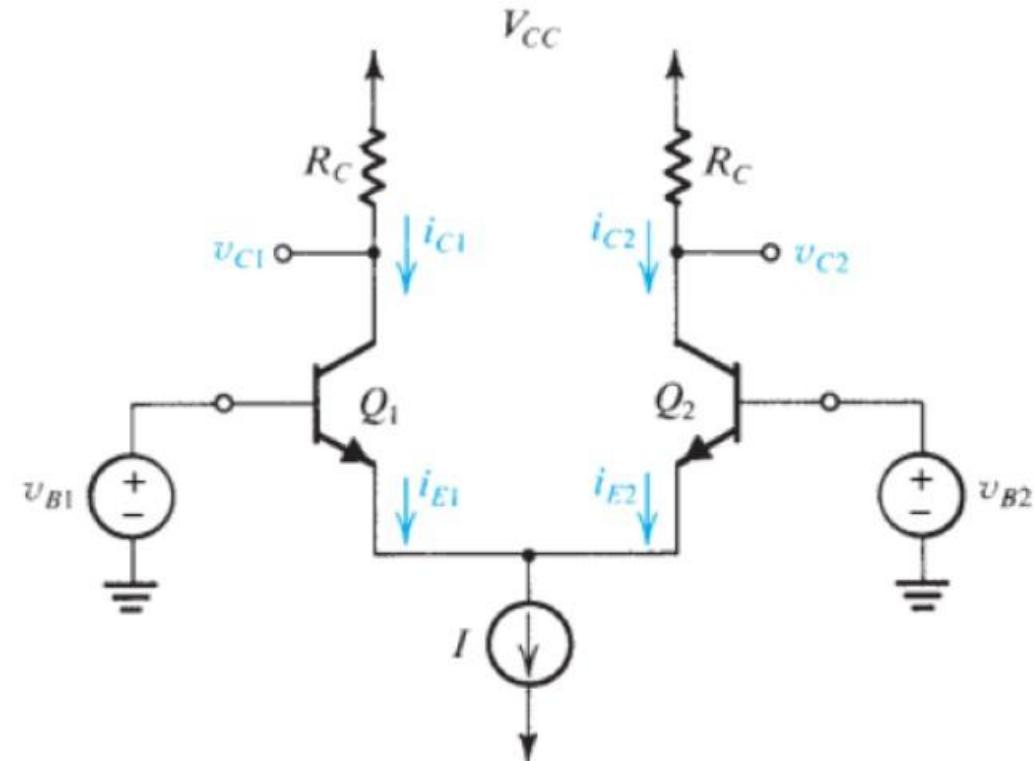- Two Identical BJTs (Same β and I_s).
- Their Emitters are connected together.
- The input signals are connected to the Q's Bases.
- A Constant DC biasing Current 'I' is used to set the DC operating point.



$$i_{E1} + i_{E2} = I$$

E. Sawires


BJT Differential Amplifier/Pair

- Emitter Coupled Circuit Large Signal Analysis (**Active Mode**)
- If Base 1 and Base 2 are connected together (Common mode signal), then the two emitter currents will be equal

$$v_{B1} = v_{B2} = v_{CM}$$

$$i_{E1} = i_{E2} = \frac{I}{2}$$

$$i_{C1} = i_{C2} = \frac{\alpha I}{2}$$

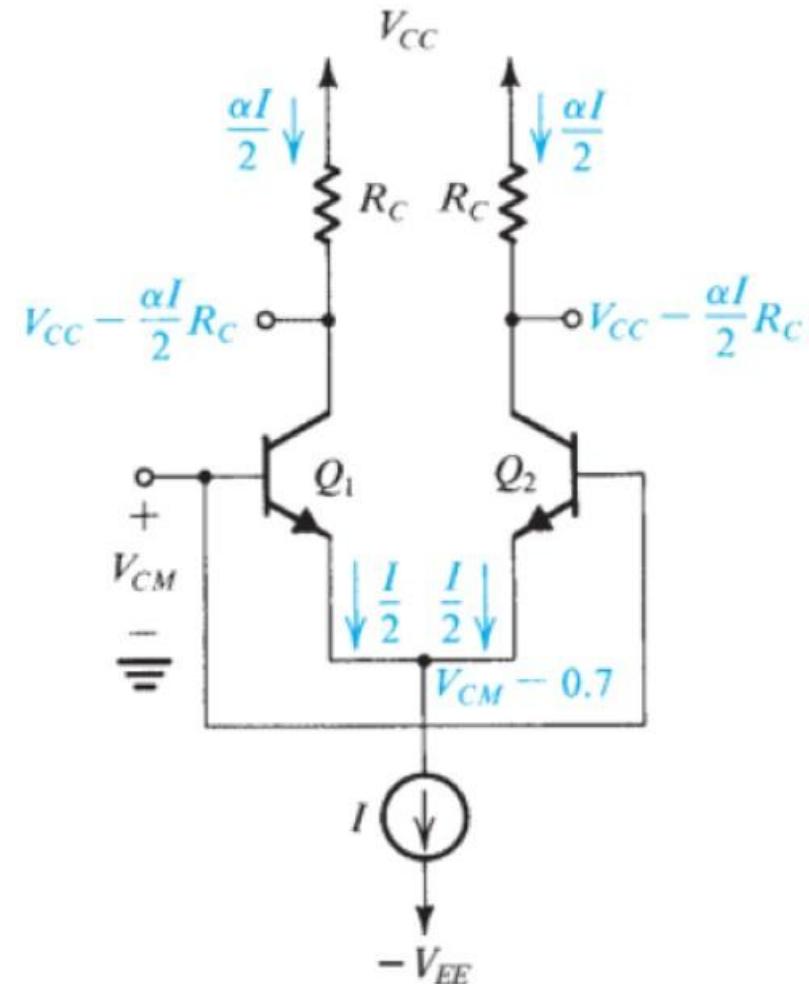


E. Sawires

BJT Differential Amplifier/Pair

- Emitter Coupled Circuit Large Signal Analysis (**Active Mode**)
- If Base 1 and Base 2 are connected together (Common mode signal), then the two emitter currents will be equal

$$v_{C1} = v_{C2} = v_{CC} - \frac{\alpha I}{2} R_C$$


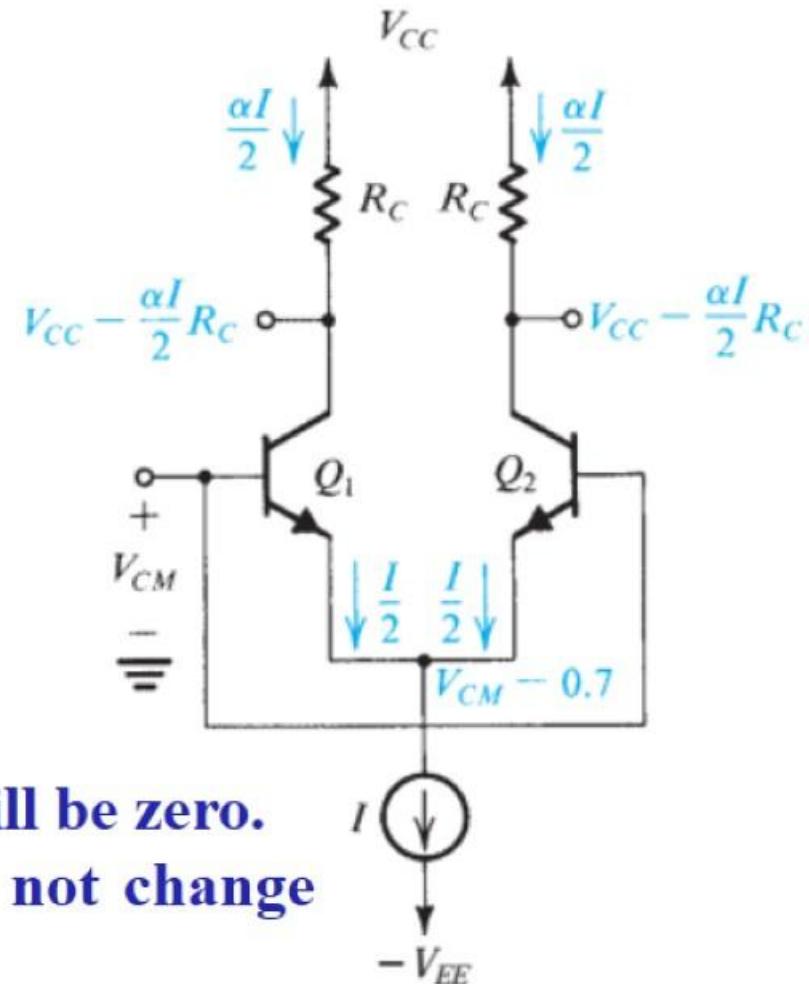
- The difference in voltage between the two collectors will be zero.
- Changing the value of the common mode signal will not change the transistors currents.
- Thus the differential pair does not respond to (i.e., it rejects) changes in the common-mode input voltage.



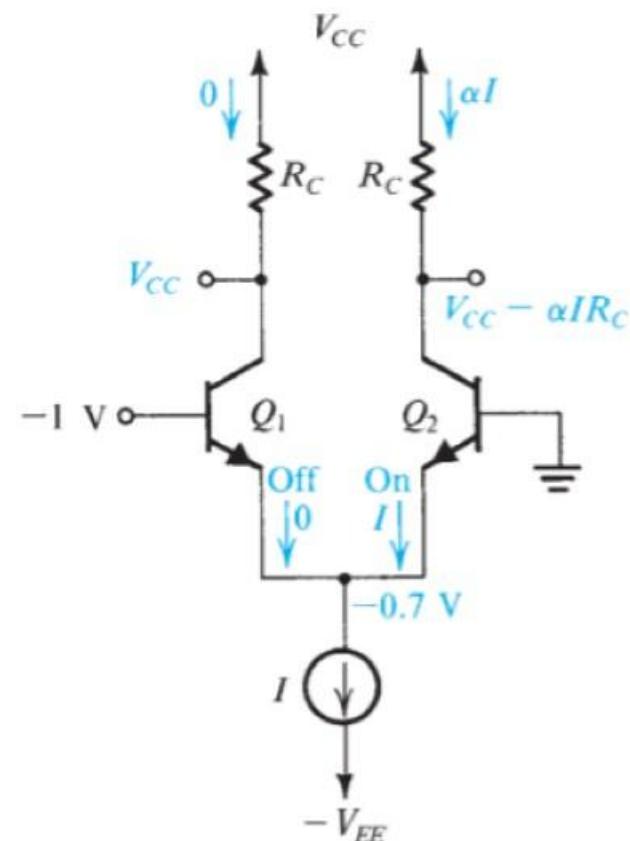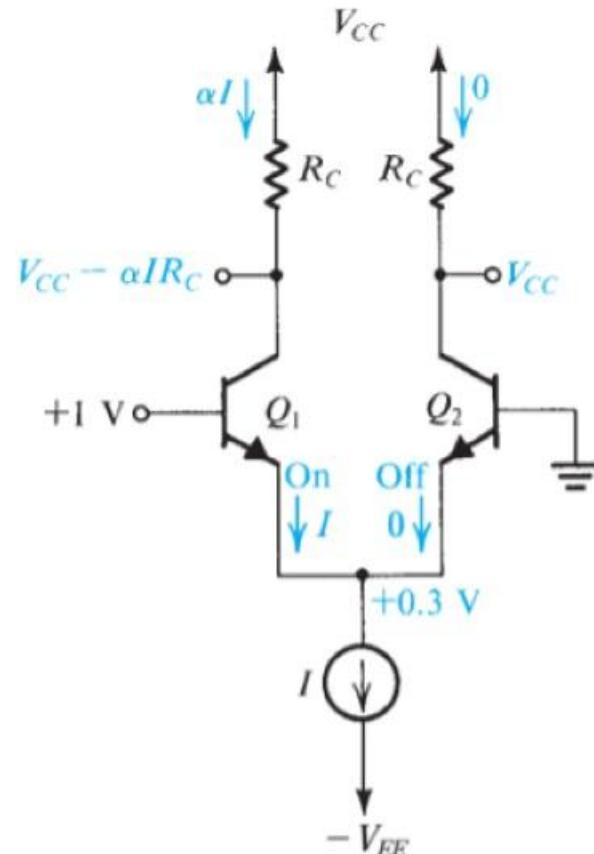E. Sawires


BJT Differential Amplifier/Pair

- Emitter Coupled Circuit Large Signal Analysis:
- If Base 1 and Base 2 are not connected together (**Differential signal**), then the two emitter currents will be equal.




BJT Differential Amplifier/Pair

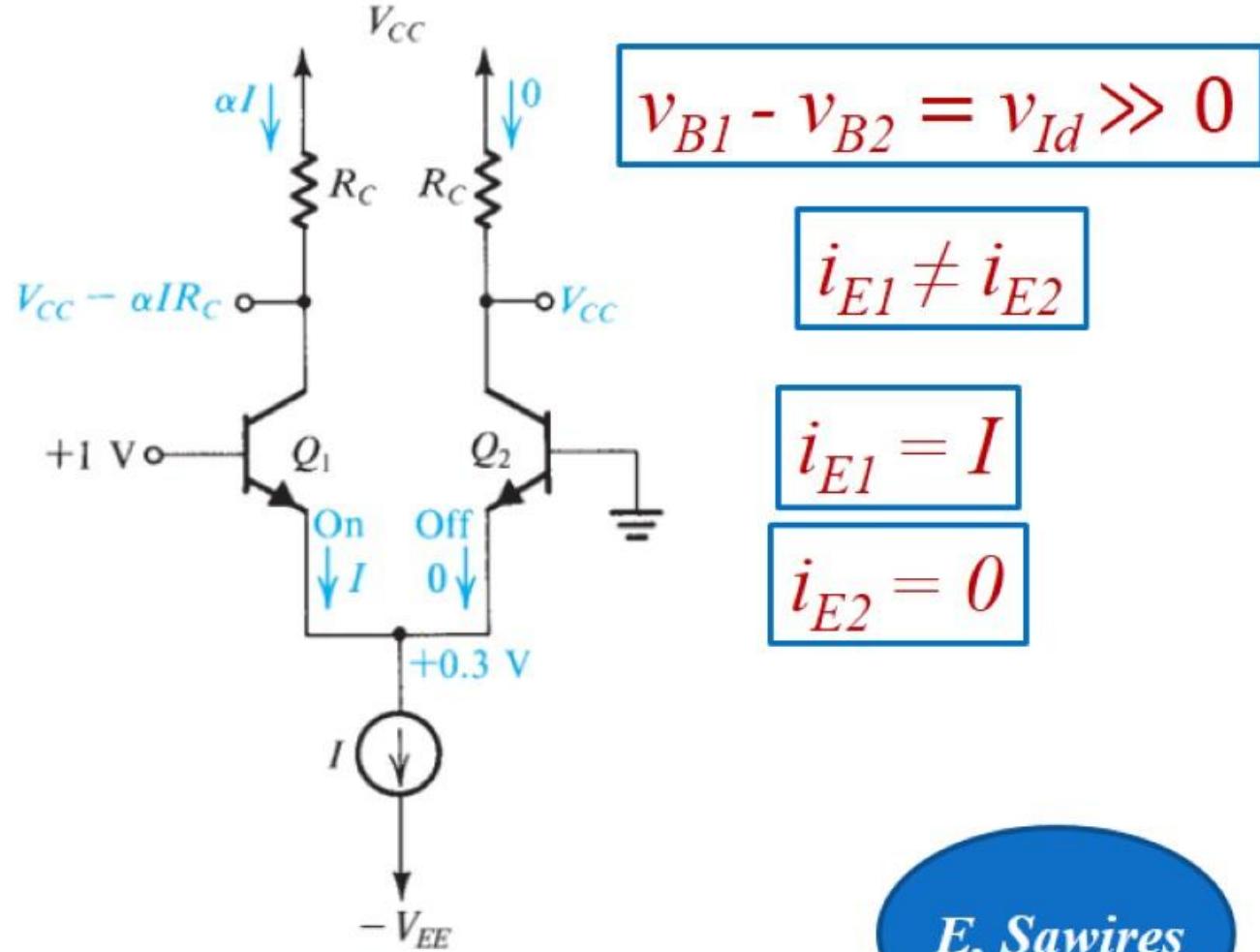- let the voltage v_{B2} be set to a constant value, say, zero (by grounding B2), and let $v_{B1} = +1$ V. With a bit of reasoning it can be seen that Q_1 will be on and conducting all of the current I and that Q_2 will be off. For Q_1 to be on (with $V_{BE1} = 0.7$ V), the emitter has to be at approximately +0.3 V, which keeps the EBJ of Q_2 reverse-biased.



E. Sawires

BJT Differential Amplifier/Pair

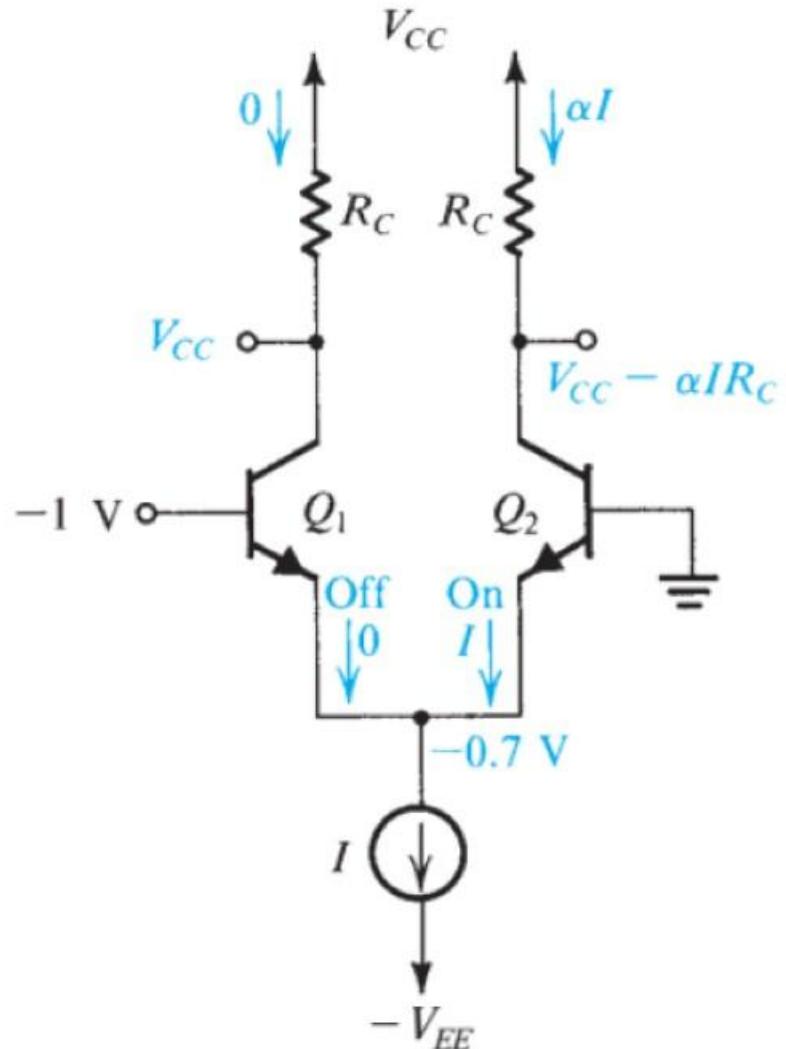

$$v_{B1} - v_{B2} = v_{Id} \ll 0$$

$$i_{E1} \neq i_{E2}$$


$$i_{E1} = 0$$

$$i_{E2} = I$$

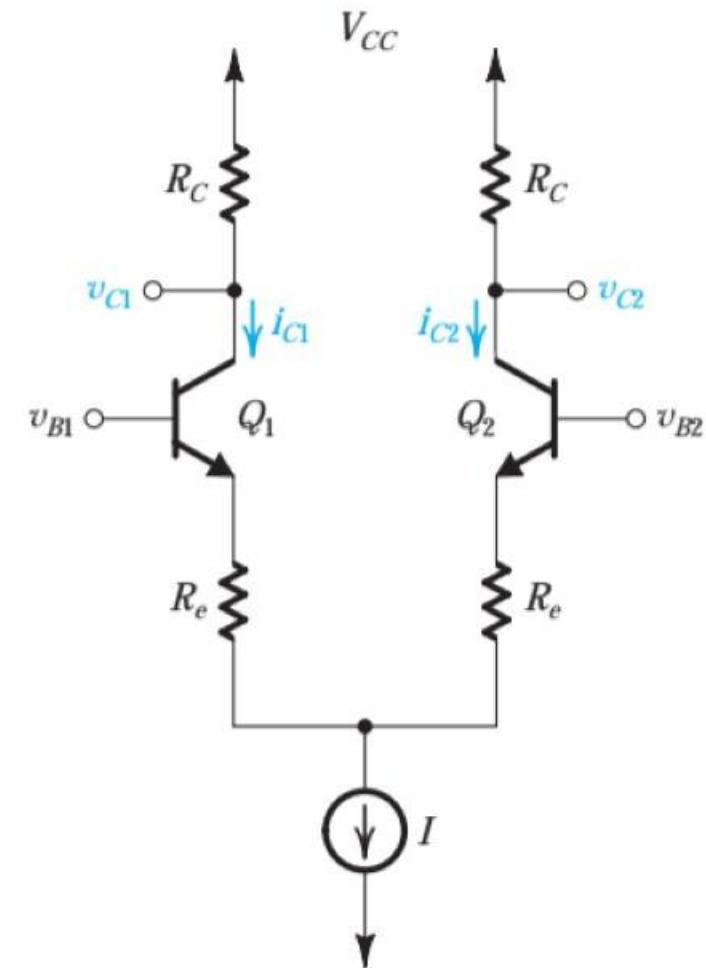E. Sawires

BJT Differential Amplifier/Pair

- Note: The linear range of operation can be extended by including resistances in the emitters.



E. Sawires

Small Signal Analysis for Differential Amplifier

Differential and Common Mode Gain for BJT

BJT Differential Amplifier/Pair


- We shall study the application of the BJT differential pair in small-signal amplification.
- The voltage at one of the input terminals will be $\frac{v_{id}}{2} + v_{cm}$ while that at the other input terminal will be $-\frac{v_{id}}{2} + v_{cm}$

BJT Differential Amplifier/Pair

➤ Small Signal Analysis Differential Mode Gain

DC Operating point is adjusted such that:

$$i_{C1} = i_{C2} = \frac{\alpha I}{2}$$

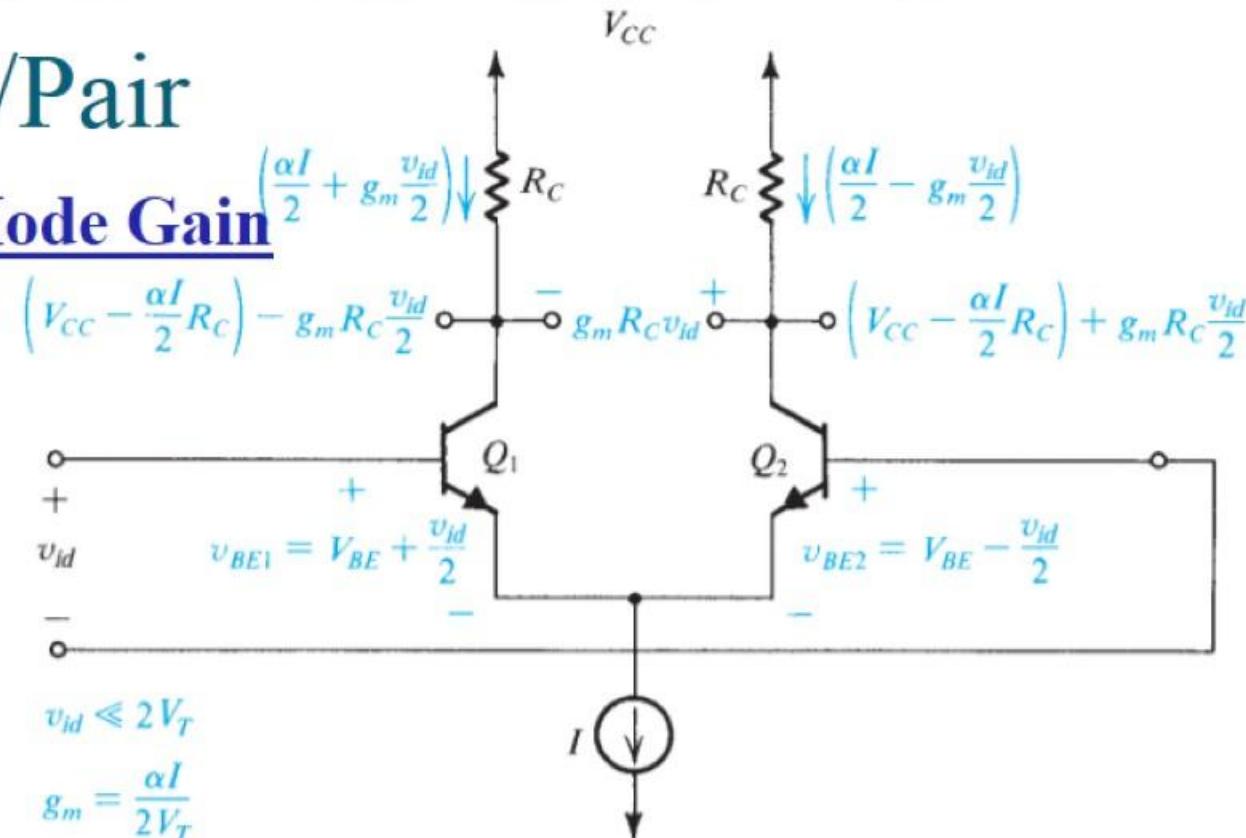

- The circuit is like two Common Emitters with the output taken as a difference between the two Collectors.

$$g_{m1} = g_{m2}$$

$$r_{\pi 1} = r_{\pi 2}$$



$$r_{o1} = r_{o2}$$

E. Sawires

BJT Differential Amplifier/Pair

➤ Small Signal Analysis Differential Mode Gain

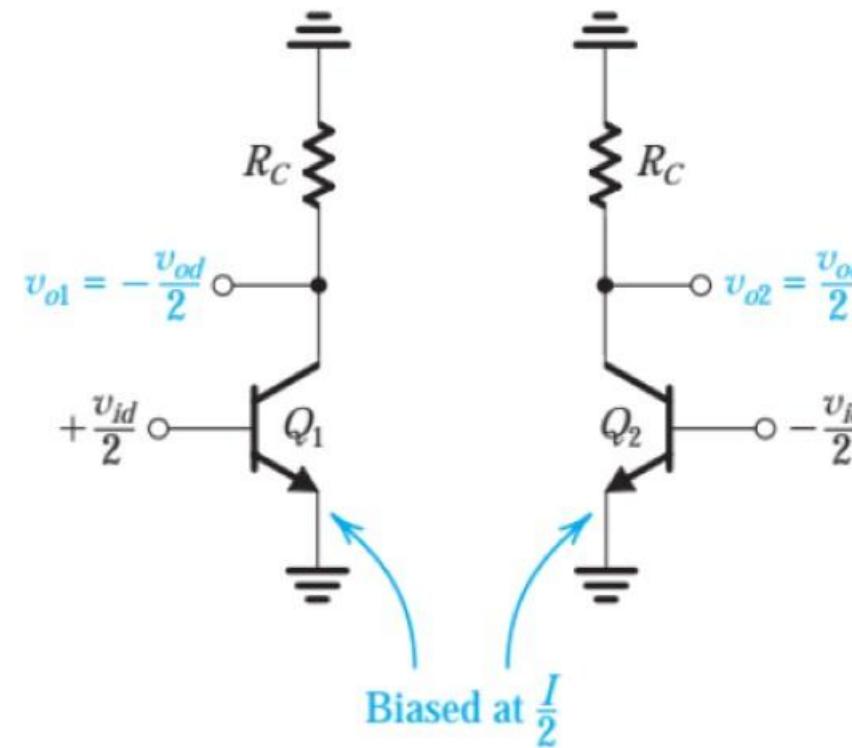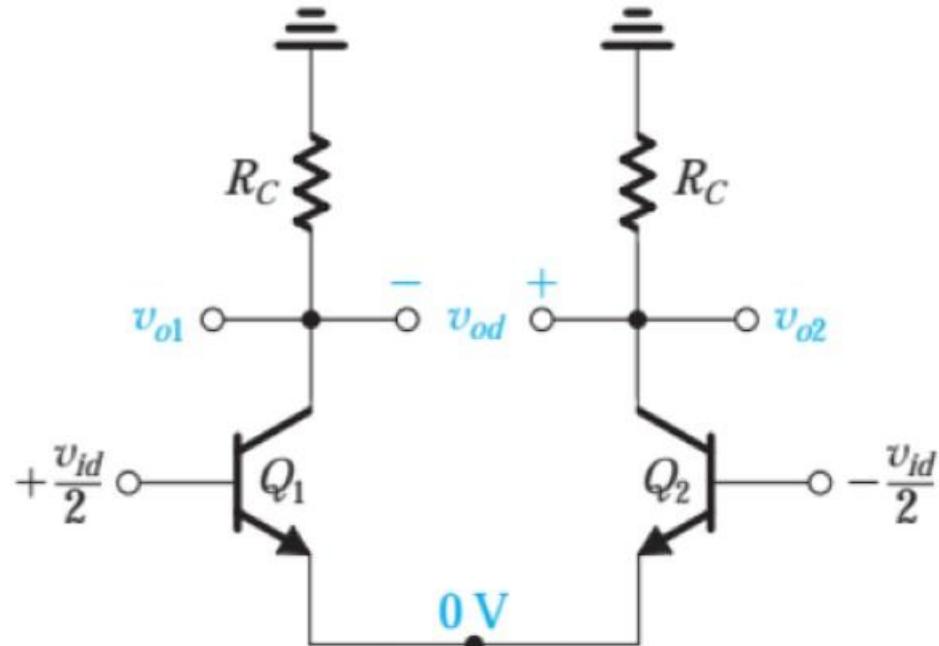
- We can use half Circuit Concept to calculate the gain




BJT Differential Amplifier/Pair

➤ Small Signal Analysis Differential Mode Gain

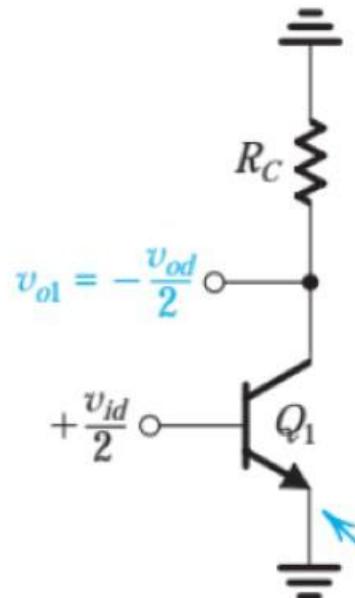- We can use half Circuit Concept to calculate the gain



$$R_{in} = 2r_\pi$$

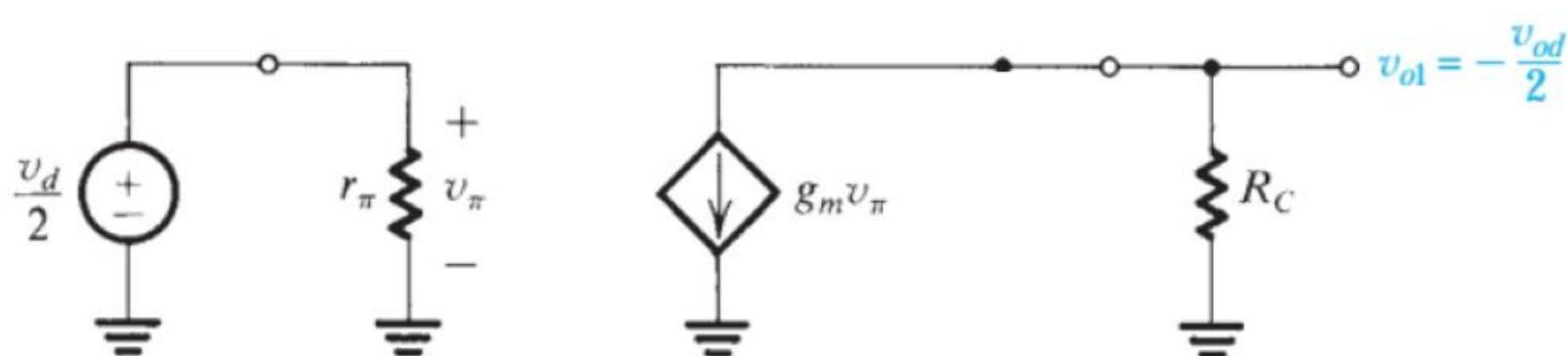

Equivalent-circuit model of the differential half-circuit formed by Q_1



$$A_d = \frac{v_{od}}{vi_d} = \frac{v_{o2} - v_{o1}}{vi_d} = \frac{v_{c2} - v_{c1}}{vi_d} = g_m R_C$$

E. Sawires

BJT Differential Amplifier/Pair

➤ Small Signal Analysis Differential Mode Gain

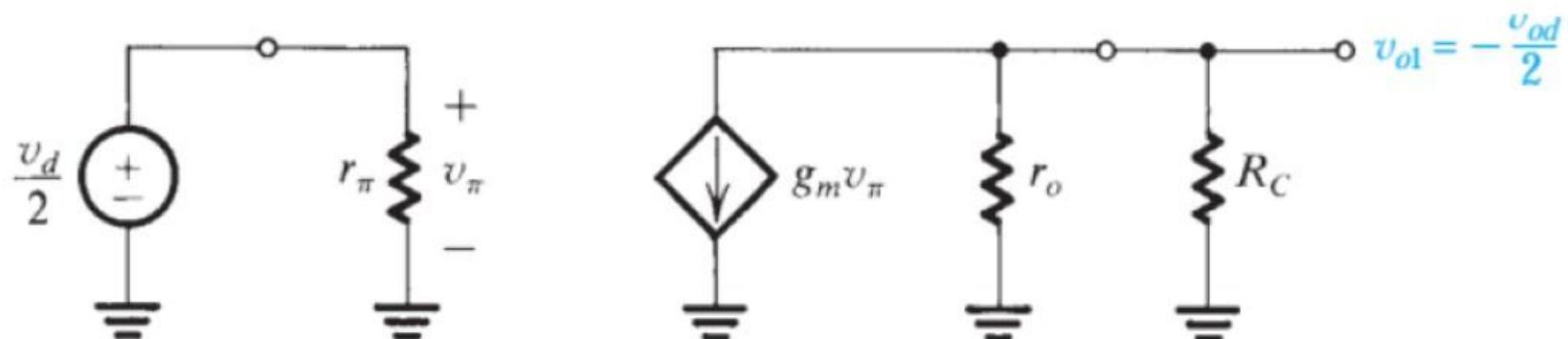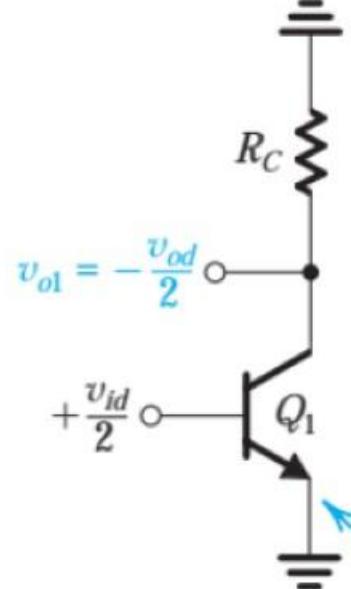- We can use half Circuit Concept to calculate the gain
- Notes: if r_o is taken into Consideration, then:



Equivalent-circuit model of the differential half-circuit formed by Q_1

$$A_d = \frac{v_{od}}{vi_d} = \frac{v_{o2} - v_{o1}}{vi_d} = \frac{v_{c2} - v_{c1}}{vi_d} = g_m (r_o // R_C)$$



E. Sawires

BJT Differential Amplifier/Pair

➤ Small Signal Analysis Differential Mode Gain

➤ R_{EE} is the Current Source Resistance.

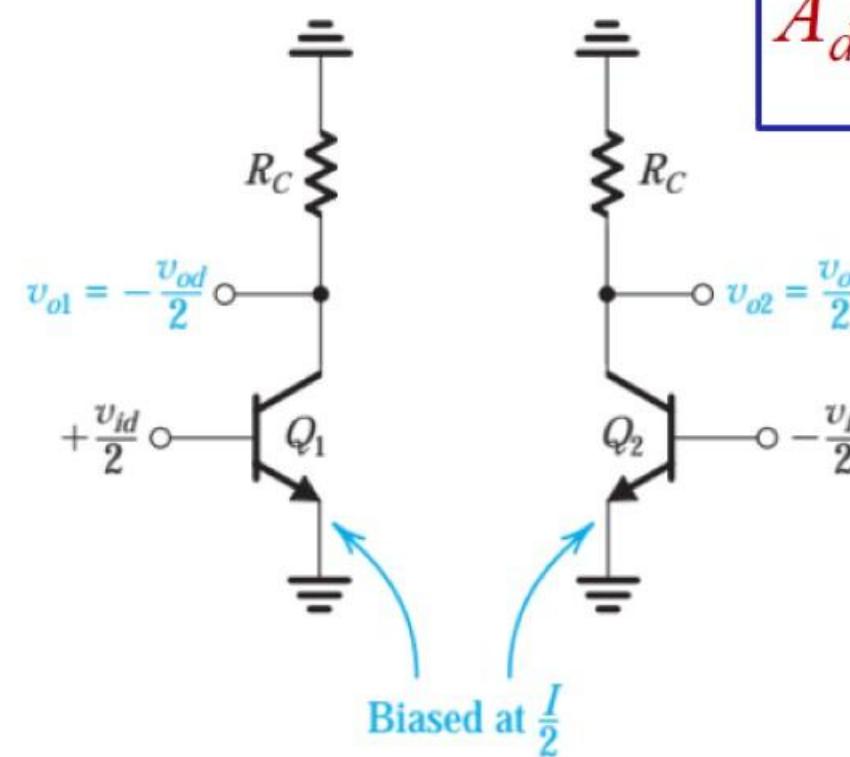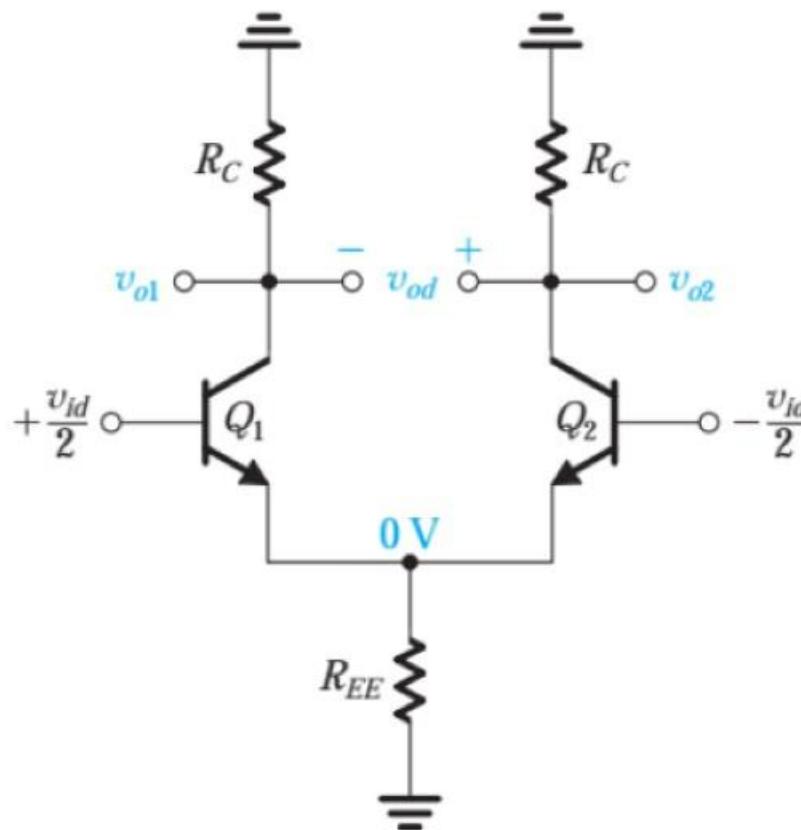➤ We can use half Circuit Concept to calculate the gain




$$A_d = \frac{v_{od}}{v_{id}} = g_m (r_o // R_C)$$

E. Sawires

BJT Differential Amplifier/Pair

➤ Small Signal Analysis Differential Mode Gain

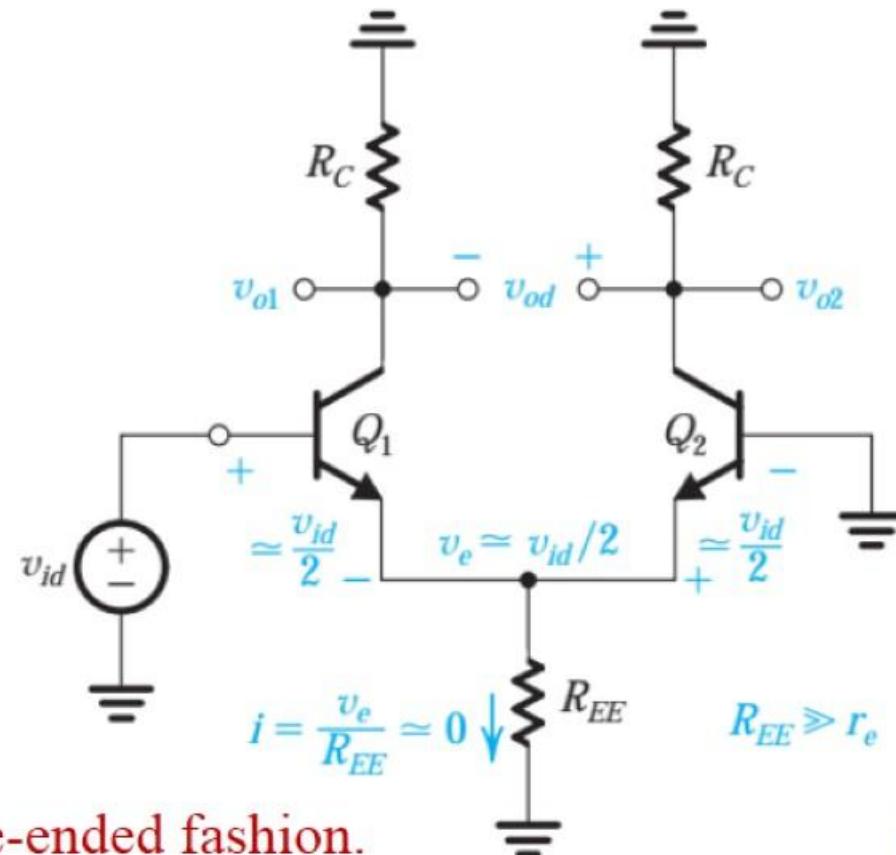- Notes: What if the signal is not applied fully differential? (Derive!)





The differential amplifier fed in a single-ended fashion.

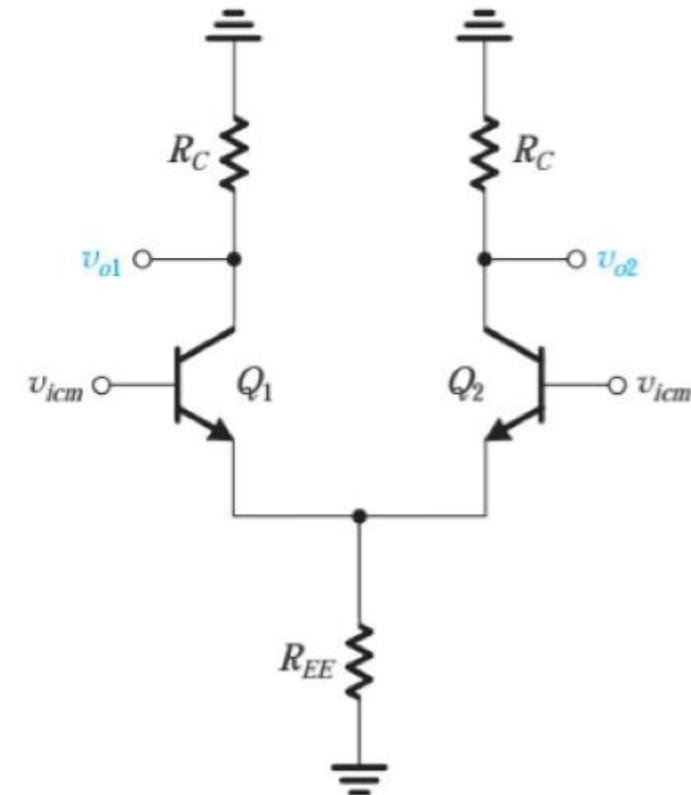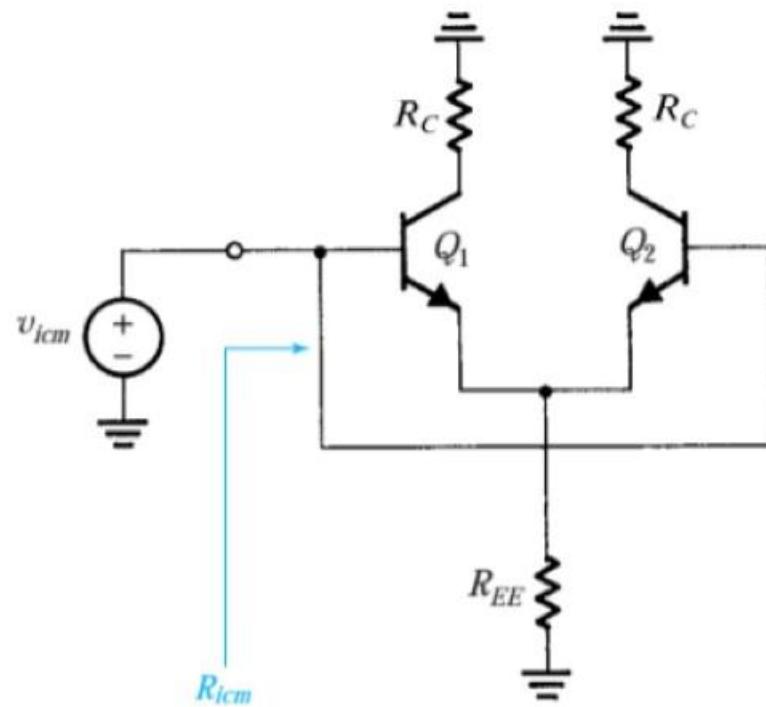E. Sawires




BJT Differential Amplifier/Pair

- Small Signal Analysis Common Mode Gain
- **R_{EE} is the Current Source Resistance (ve is not Zero in the common mode Case, why?)**



BJT Differential Amplifier/Pair

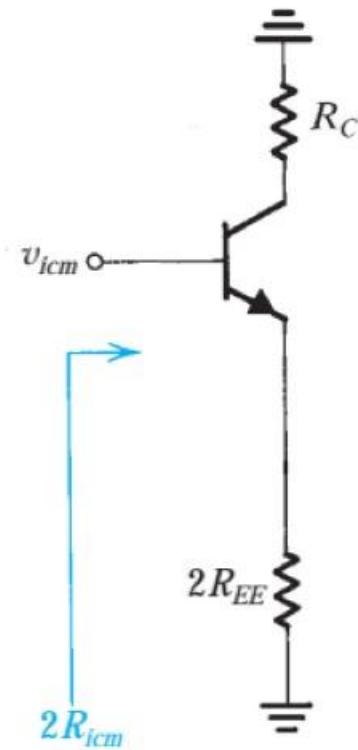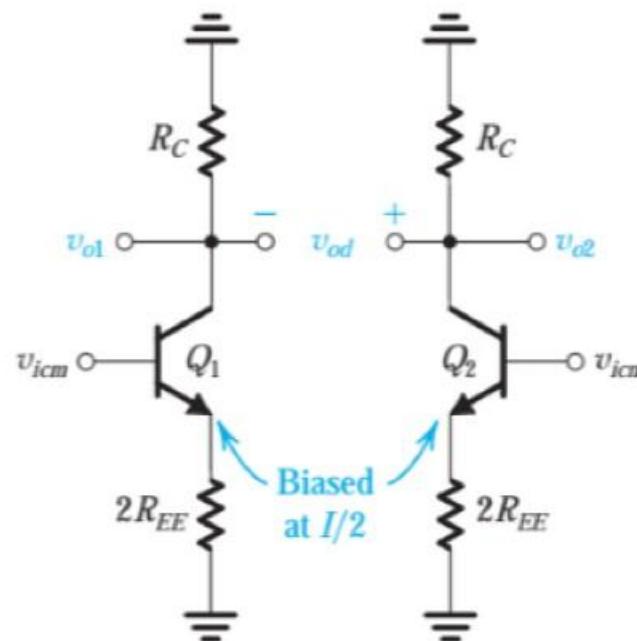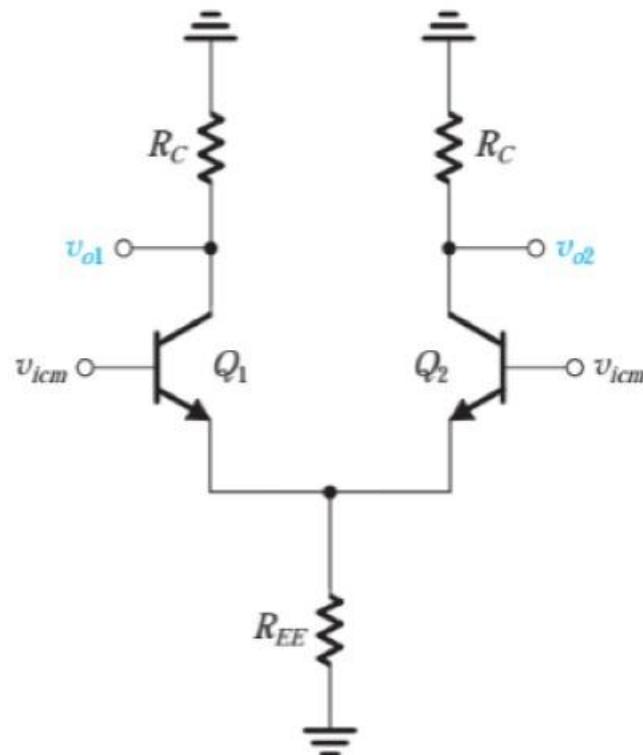
- Small Signal Analysis Common Mode Gain
- R_{EE} is the Current Source Resistance (ve is not Zero in the common mode Case, why?)



BJT Differential Amplifier/Pair

➤ Small Signal Analysis Common Mode Gain

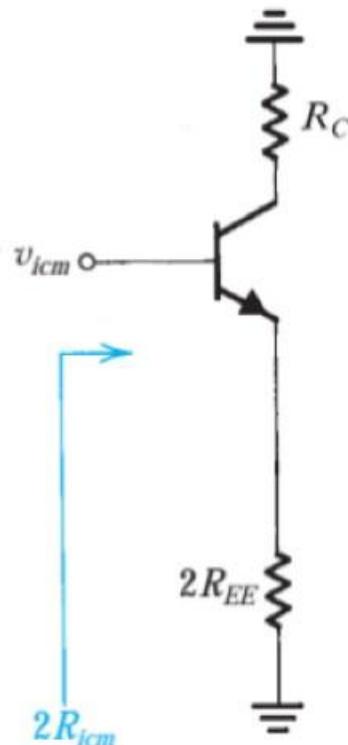- This condition, however, is based on the assumption of perfect matching between the two sides of the differential amplifier.



$$v_{o1} = -\frac{\alpha R_C}{r_e + 2R_{EE}} v_{icm}$$

$$v_{o2} = -\frac{\alpha R_C}{r_e + 2R_{EE}} v_{icm}$$

$$v_{od} = v_{o2} - v_{o1} = 0$$

E. Sawires

BJT Differential Amplifier/Pair

➤ Small Signal Analysis Common Mode Gain

➤ Any mismatch will result in v_{od} acquiring a component proportional to v_{Icm} . For example, consider the case of a mismatch ΔR_C between the two collector resistances: If the collector of has a collector resistance R_C ,

$$v_{o1} = -\frac{\alpha R_C}{2R_{EE} + r_e} v_{icm}$$

and the collector of has a collector resistance $(R_C + \Delta R_C)$

$$v_{o2} = -\frac{\alpha(R_C + \Delta R_C)}{2R_{EE} + r_e} v_{icm}$$

E. Sawires

BJT Differential Amplifier/Pair

➤ Small Signal Analysis Common Mode Gain

$$\begin{aligned}v_{od} &\equiv v_{o2} - v_{o1} \\&= -\frac{\alpha \Delta R_C}{2R_{EE} + r_e} v_{icm}\end{aligned}$$

$$A_{cm} \equiv \frac{v_{od}}{v_{icm}} = -\frac{\alpha \Delta R_C}{2R_{EE} + r_e}$$

- Since $\alpha \approx 1$, $r_e \ll 2R_{EE}$, Eq. can be approximated and written in the form

$$A_{cm} \simeq -\left(\frac{R_C}{2R_{EE}}\right)\left(\frac{\Delta R_C}{R_C}\right)$$

The common-mode rejection ratio can now be found from

$$\text{CMRR} = \frac{|A_d|}{|A_{cm}|}$$

$$\text{CMRR} = (2g_m R_{EE}) \left/ \left(\frac{\Delta R_C}{R_C} \right) \right.$$

E. Sawires


The MOS Differential Pair

MOS Differential Amplifier/Pair

Source Coupled Circuit:

- Two matched MOS-FET (Same K and V_T)
- Their Sources are connected together.
- The input signals are connected to the M's Gates
- A Constant DC biasing Current 'I' is used to set the DC operating point.

$$i_{D1} + i_{D2} = I$$

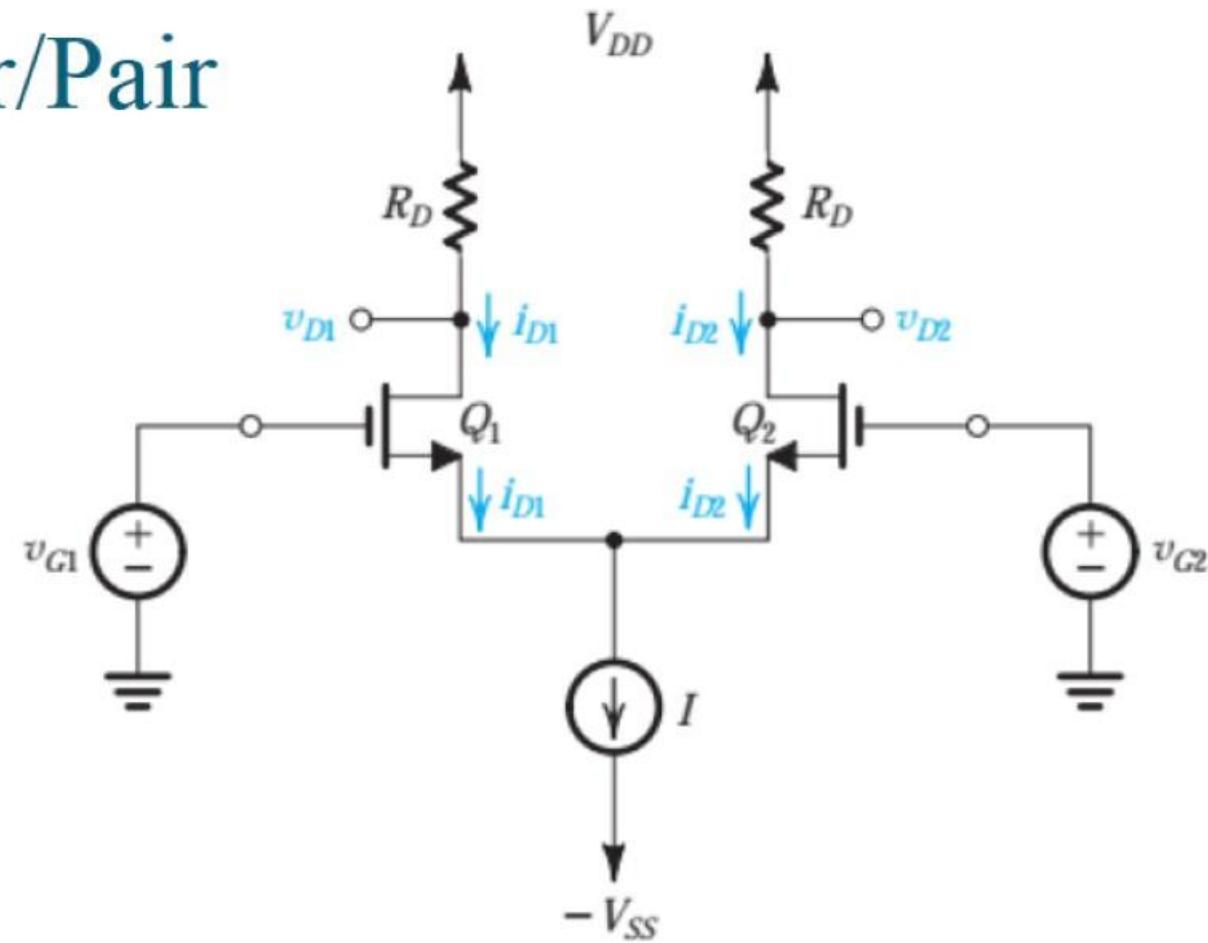

The basic MOS differential-pair configuration.

E. Sawires

MOS Differential Amplifier/Pair


Operation with a Common-Mode Input Voltage

- To see how the differential pair works, consider first the case when the two gate terminals are joined together and connected to a voltage V_{cm} , called the common-mode voltage.

$$v_{G1} = v_{G2} = V_{CM}$$

$$i_{D1} = i_{D2} = \frac{I}{2}$$
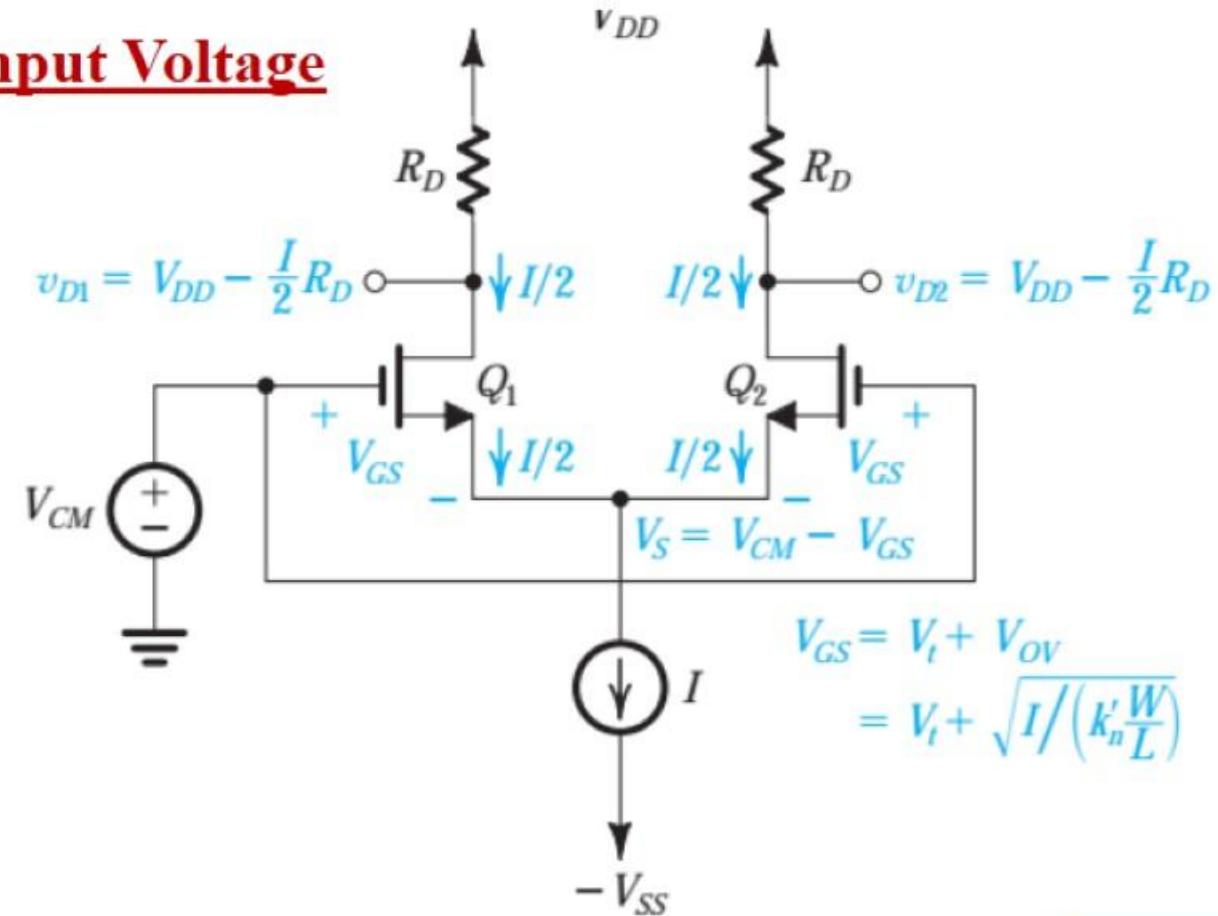
$$v_{D1} = v_{D2} = V_{DD} - \frac{I}{2}R_D$$



The MOS differential pair with a common-mode input voltage V_{cm} .

MOS Differential Amplifier/Pair

Operation with a Common-Mode Input Voltage

$$V_s = V_{CM} - V_{GS}$$


$$\frac{I}{2} = \frac{1}{2} K_n \frac{W}{L} (V_{GS} - V_t)^2$$

➤ The overdrive voltage

$$V_{OV} = V_{GS} - V_t$$

$$\frac{I}{2} = \frac{1}{2} K_n \frac{W}{L} V_{OV}^2$$



$$V_{OV} = \sqrt{I/k'_n(W/L)}$$

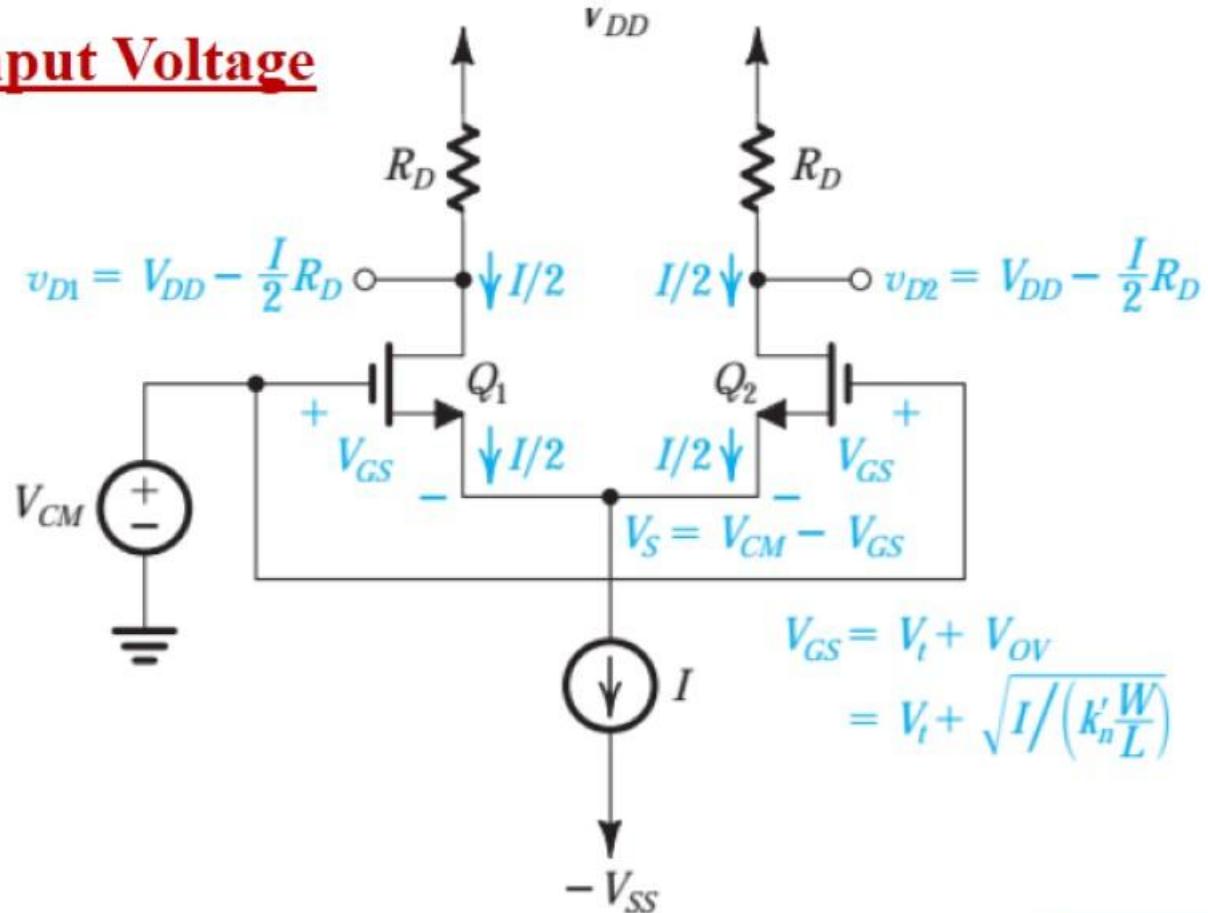

The MOS differential pair with a common-mode input voltage V_{cm}.


MOS Differential Amplifier/Pair

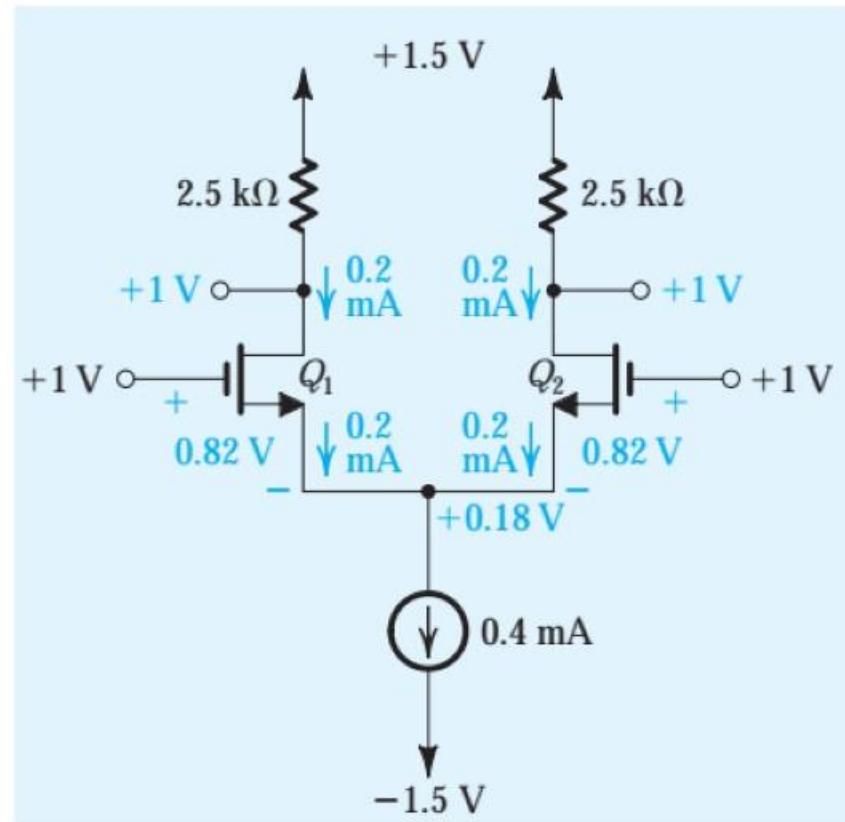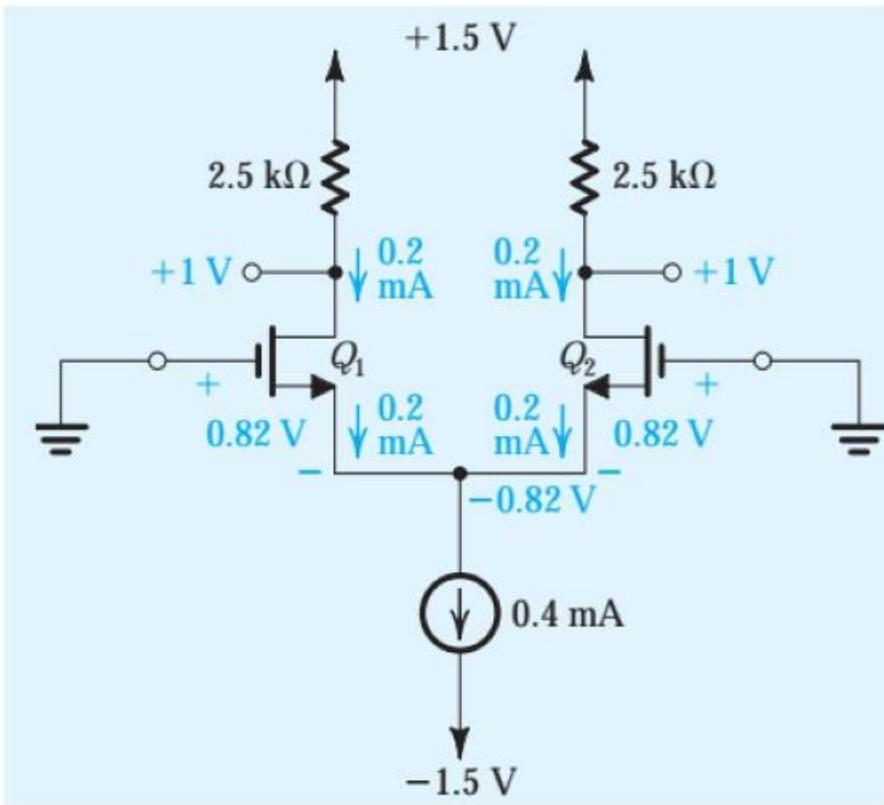- Changing the value of the common mode signal **will not change** the transistors currents.



MOS Differential Amplifier/Pair

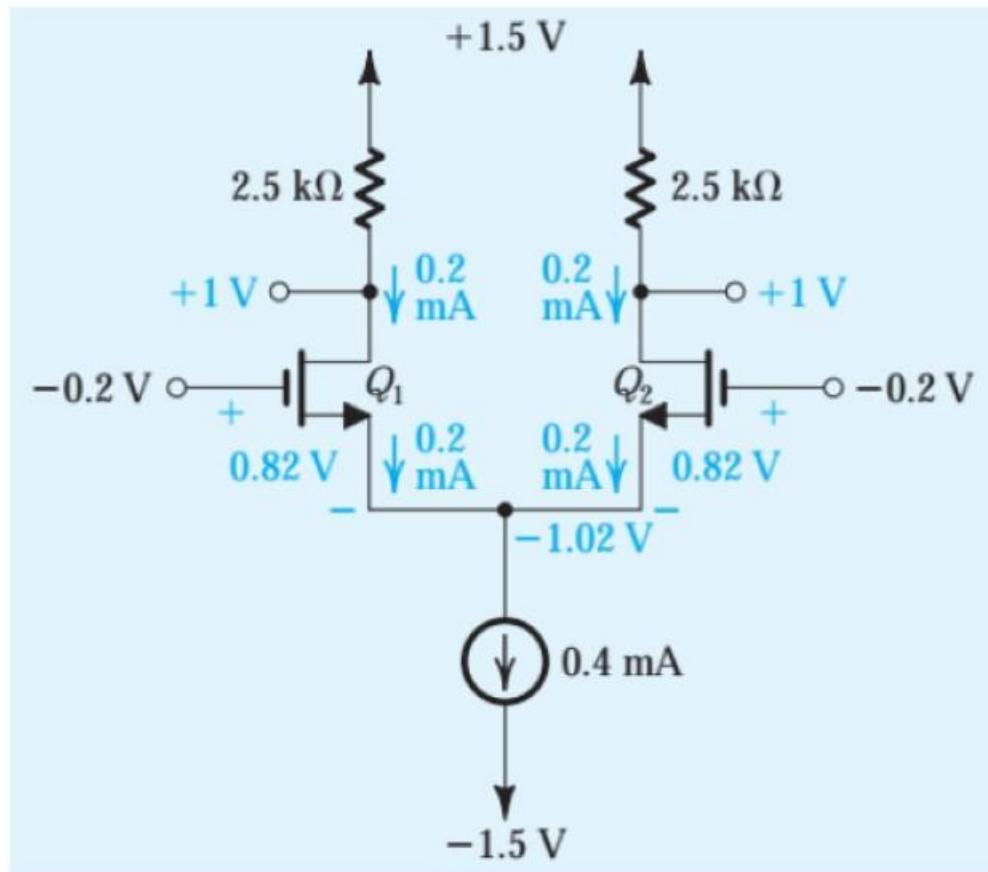- Changing the value of the common mode signal **will not change** the transistors currents.




E. Sawires

Small Signal Analysis for Differential Amplifier

Differential and Common Mode Gain for MOS-FET

MOSFET Differential Amplifier/Pair

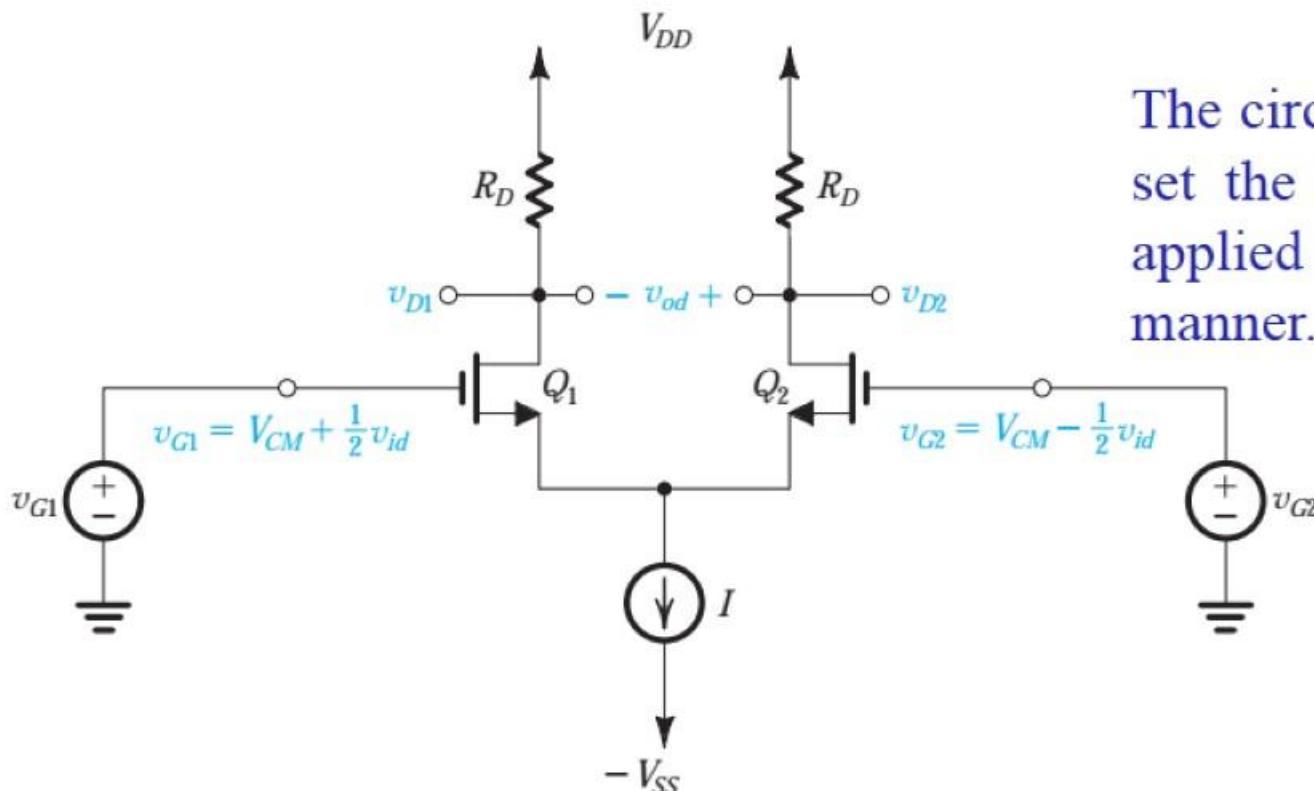- Small Signal Analysis Differential Mode Gain
- The circuit is like two Common Source Amplifiers, where the output is taken as a difference between the two Drains.




The circuit with a common-mode voltage applied to set the dc bias voltage at the gates and with v_{id} applied in a complementary (or balanced) manner.

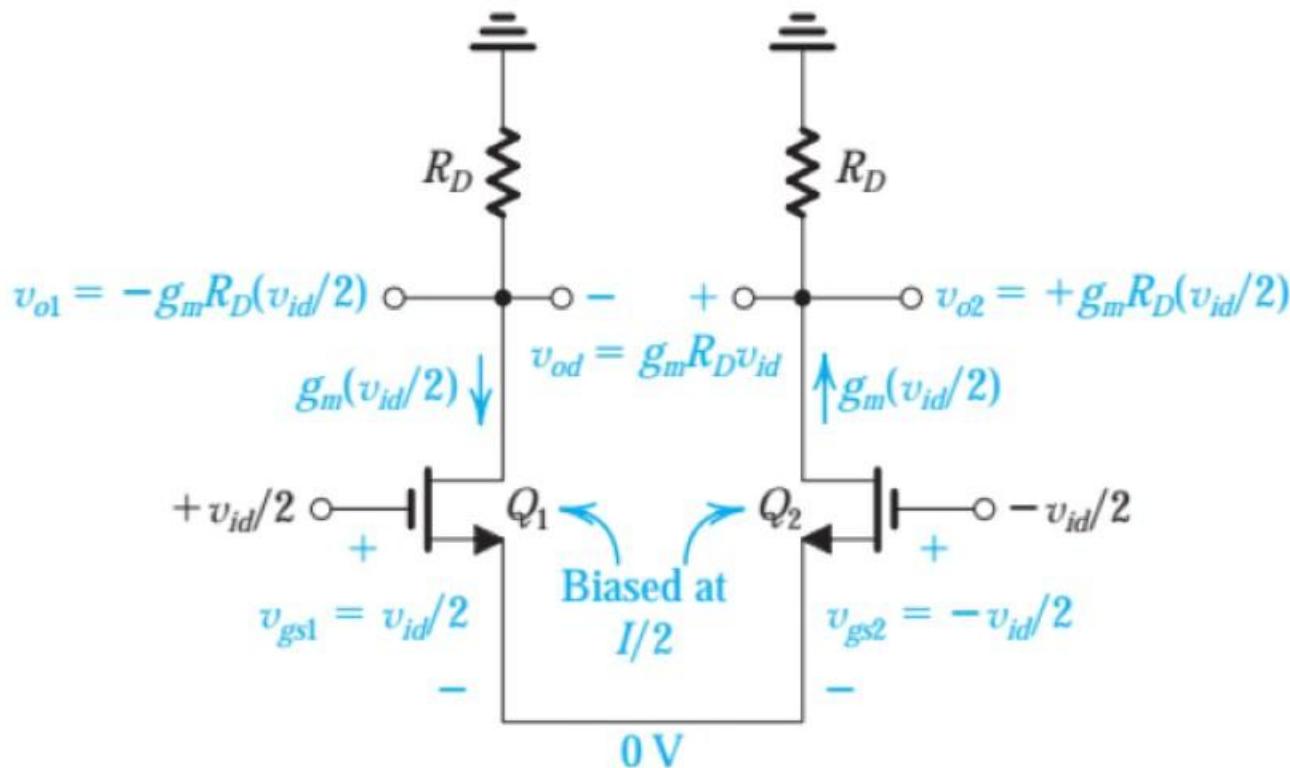E. Sawires

MOSFET Differential Amplifier/Pair

➤ Small Signal Analysis Differential Mode Gain



$$g_{m1} = g_{m2}$$

$$r_{o1} = r_{o2}$$


The circuit prepared for small-signal analysis.

E. Sawires

MOSFET Differential Amplifier/Pair

➤ Small Signal Analysis Differential Mode Gain

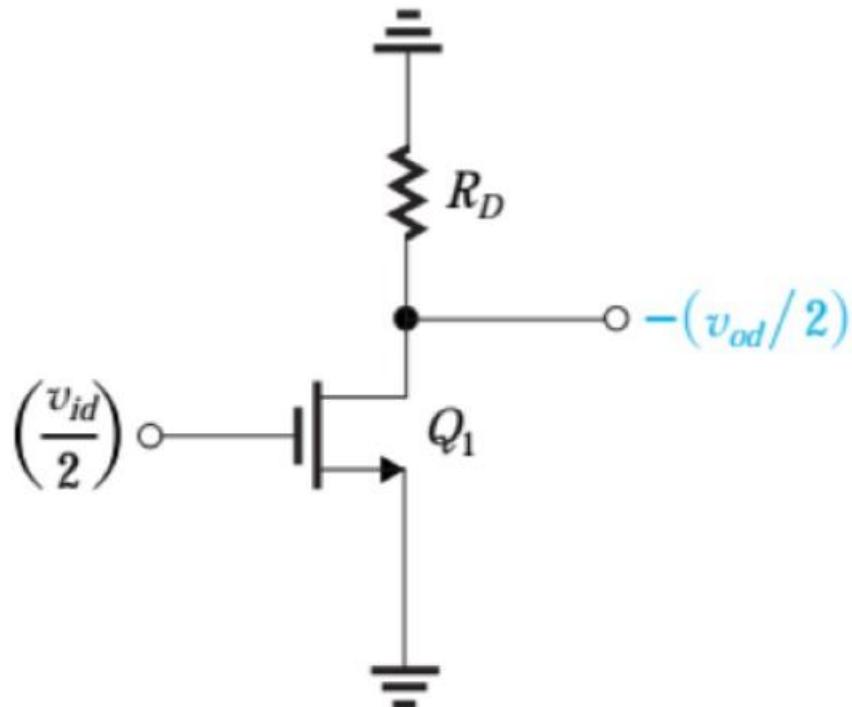- We can use half Circuit Concept to calculate the gain



$$v_{o1} = -g_m \frac{v_{id}}{2} R_D$$

$$v_{o2} = +g_m \frac{v_{id}}{2} R_D$$

$$\frac{v_{o1}}{v_{id}} = -\frac{1}{2} g_m R_D$$

$$\frac{v_{o2}}{v_{id}} = \frac{1}{2} g_m R_D$$

$$A_d = \frac{v_{od}}{vi_d} = \frac{v_{o2} - v_{o1}}{vi_d} = \frac{v_{D2} - v_{D1}}{vi_d} = g_m R_D$$


$$R_{in} = \infty$$

E. Sawires

MOSFET Differential Amplifier/Pair

➤ Small Signal Analysis Differential Mode Gain

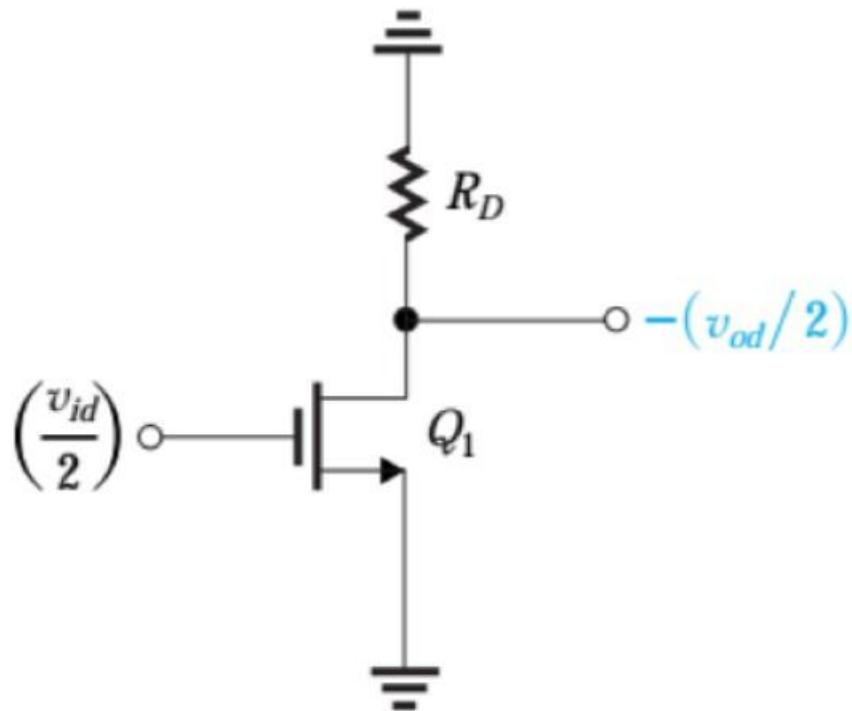- We can use half Circuit Concept to calculate the gain
- Notes: if r_o is taken into Consideration, then:



$$A_d = \frac{v_{od}}{vi_d} = \frac{v_{o2} - v_{o1}}{vi_d} = \frac{v_{D2} - v_{D1}}{vi_d} = g_m (r_o // R_D)$$


$$R_{in} = \infty$$

E. Sawires

MOSFET Differential Amplifier/Pair

➤ Small Signal Analysis Differential Mode Gain

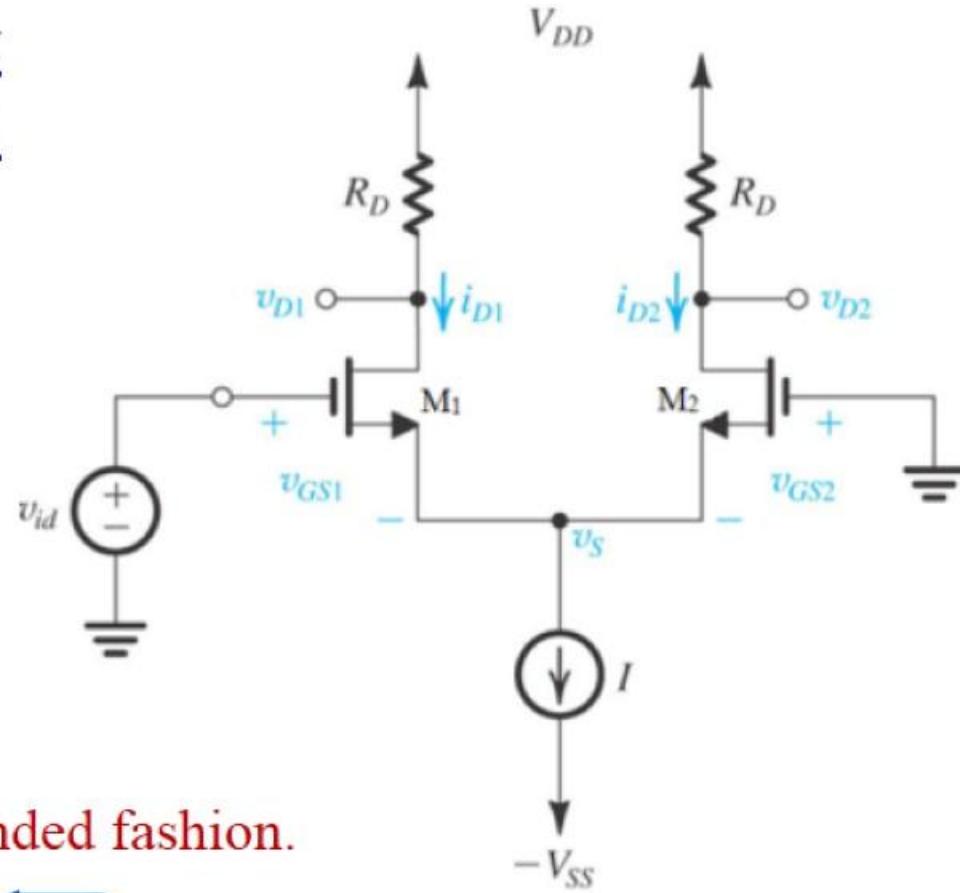- Notes: What if the signal is not applied fully differential? (Derive!)





The differential amplifier fed in a single-ended fashion.

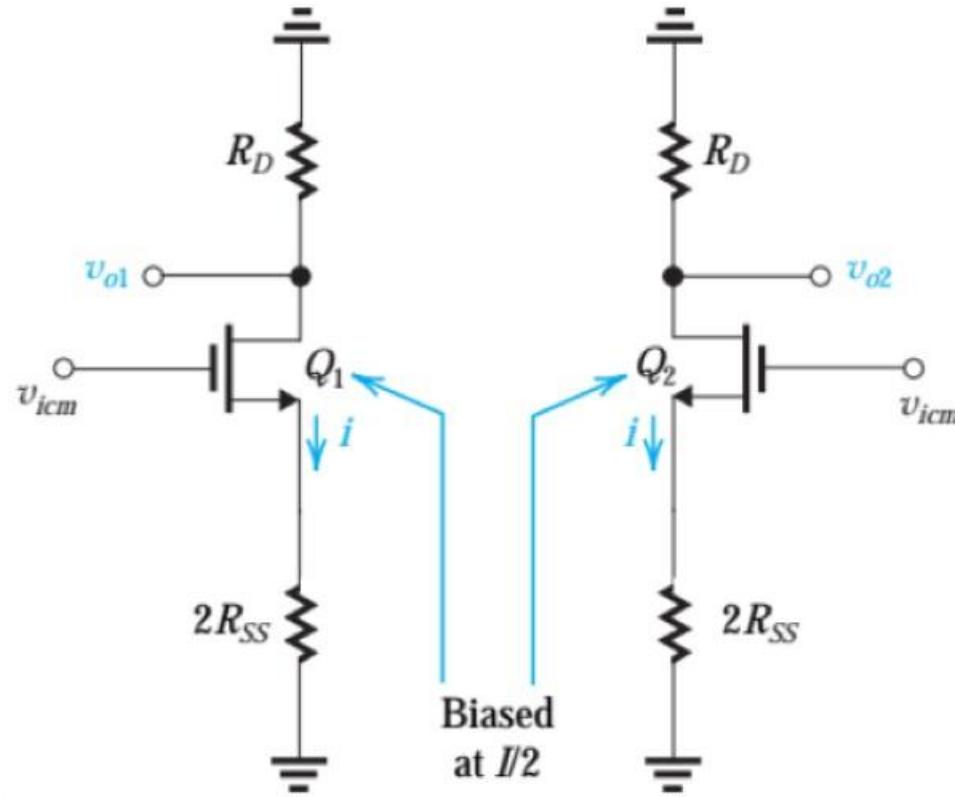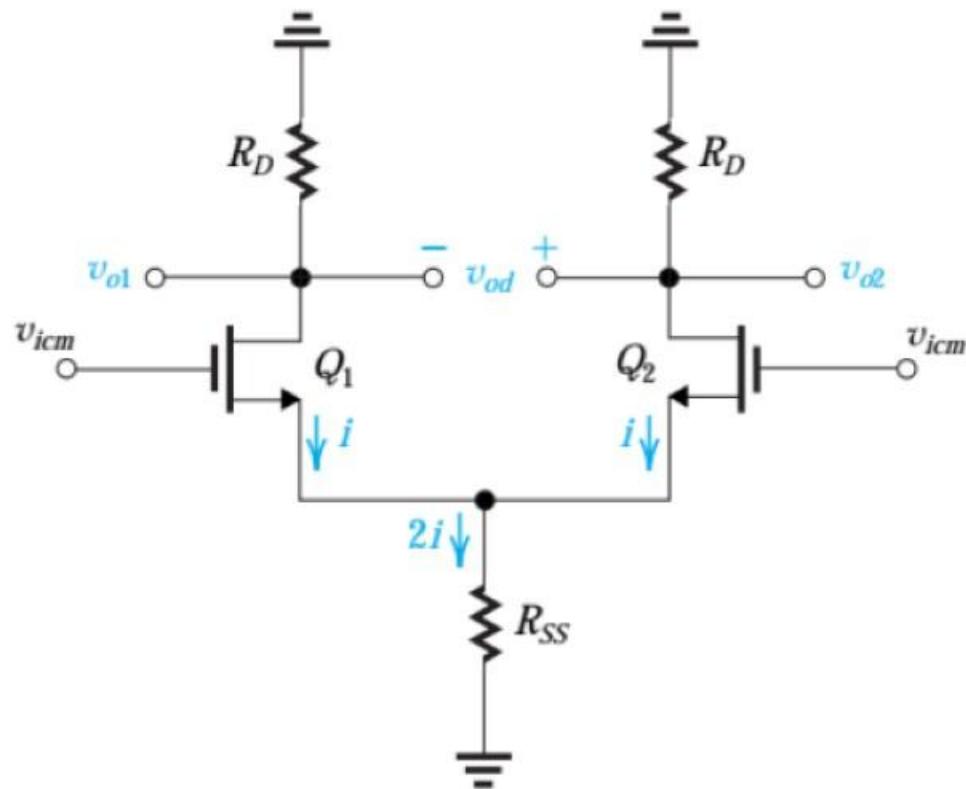E. Sawires


MOSFET Differential Amplifier/Pair

- Small Signal Analysis Common Mode Gain
- R_{SS} is the Current Source Resistance (vs is not Zero in the common mode Case, why?)



MOSFET Differential Amplifier/Pair

➤ Small Signal Analysis Common Mode Gain

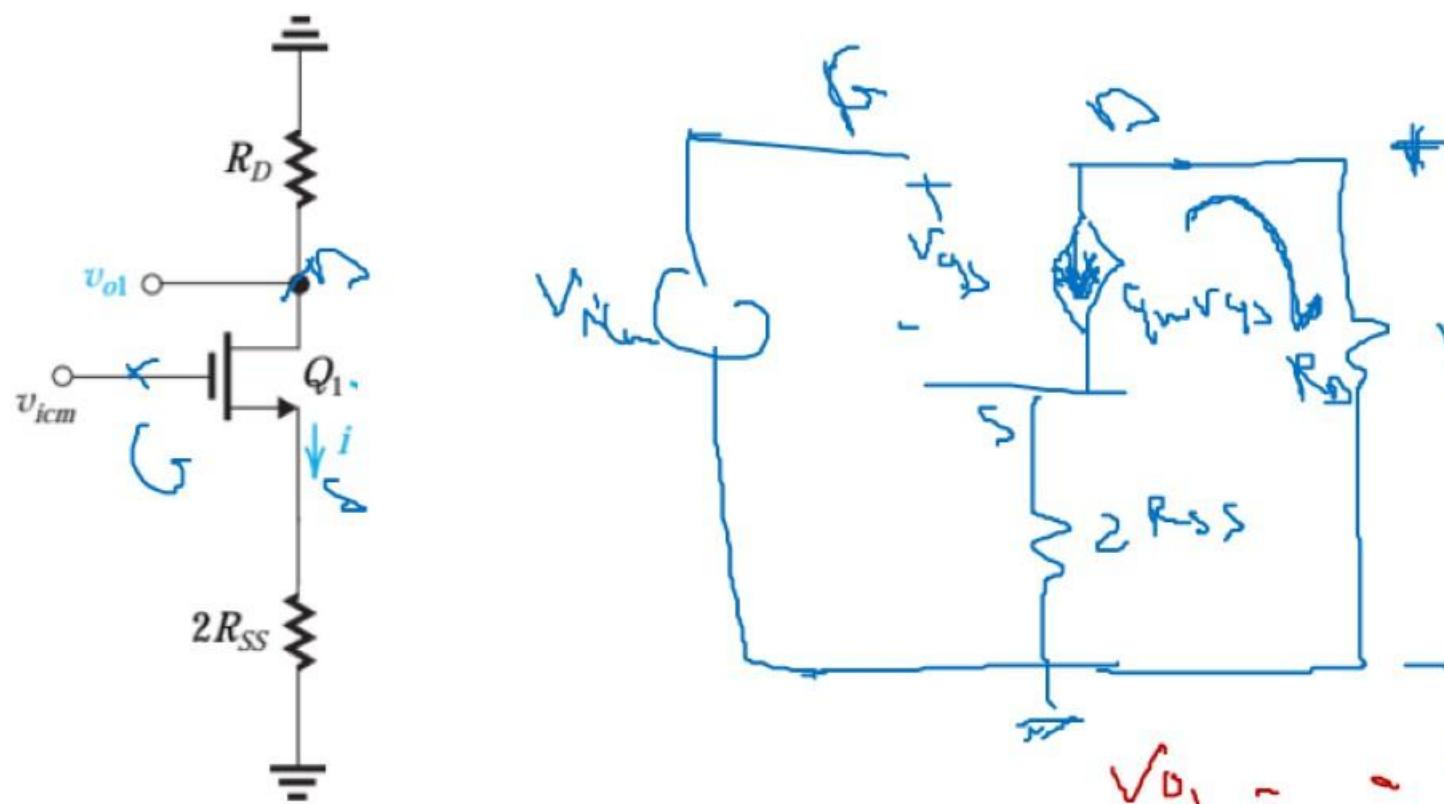

$$v_{o1} = -R_D g_m v_{gs}$$

$$v_{icm} = v_{gs} + 2R_{SS} g_m v_{gs}$$

$$= v_{gs} \left(1 + 2R_{SS} g_m \right)$$

$$\underline{v_{o1}} = v_{o2} = -\frac{1/g_m + 2R_{SS}}{1/g_m + 2R_{SS}} \underline{v_{icm}}$$

$$\frac{v_{o1}}{v_{icm}} = \frac{v_{o2}}{v_{icm}} \approx -\frac{R_D}{2R_{SS}}$$

$$\underline{v_{od}} = \underline{v_{o2}} - \underline{v_{o1}} = 0$$

$$v_{od} = -\frac{R_D g_m v_{icm}}{1 + 2R_{SS} g_m}$$

E. Sawires

MOSFET Differential Amplifier/Pair

➤ Small Signal Analysis Common Mode Gain

➤ Effect of R_D Mismatch

$$v_{o1} \approx -\frac{R_D}{2R_{SS}} v_{icm}$$

$$v_{o2} \approx -\frac{R_D + \Delta R_D}{2R_{SS}} v_{icm}$$

$$v_{od} = v_{o2} - v_{o1} = -\frac{\Delta R_D}{2R_{SS}} v_{icm}$$

$$A_{cm} \equiv \frac{v_{od}}{v_{icm}} = -\frac{\Delta R_D}{2R_{SS}}$$

E. Sawires

MOSFET Differential Amplifier/Pair

- It follows that a mismatch in the drain resistances causes the differential amplifier to have a finite common-mode gain.
- Thus, a portion of the interference or noise signal v_{icm} will appear as a component of v_{od} .
- A measure of the effectiveness of the differential amplifier in amplifying differential-mode signals and rejecting common-mode interference is the ratio of the magnitude of its differential gain $|A_d|$ to the magnitude of its common-mode gain $|A_{cm}|$.
- This ratio is termed common-mode rejection ratio (CMRR).

E. Sawires

MOSFET Differential Amplifier/Pair

- The common-mode rejection ratio can now be found from

$$\text{CMRR} = \frac{|A_d|}{|A_{cm}|} = \frac{g_m R_D}{\frac{2R_{SS}}{\Delta R_D}} = \frac{2g_m R_{SS}}{\Delta R_D / R_D}$$
$$\text{CMRR} = (2g_m R_{SS}) / (\Delta R_D / R_D)$$

E. Sawires

Thank You



Have a Wonderful Semester