

# **Electronic Systems**

## **Active Filters**

### **Lecture 7**

**Dr. Roaa Mubarak**


# The Active Filters Contents:

1. Introduction to Filters.
2. Low Pass Filter.
3. High Pass Filter.
4. Band Pass Filter.
5. Butterworth Filter.
6. Chebyshev Filter.
7. Bessel Filter.
8. KHN Biquad Filter.
- 9. State Variable Filters.**
10. Multiple Feedback Filters.

# State Variable Filter

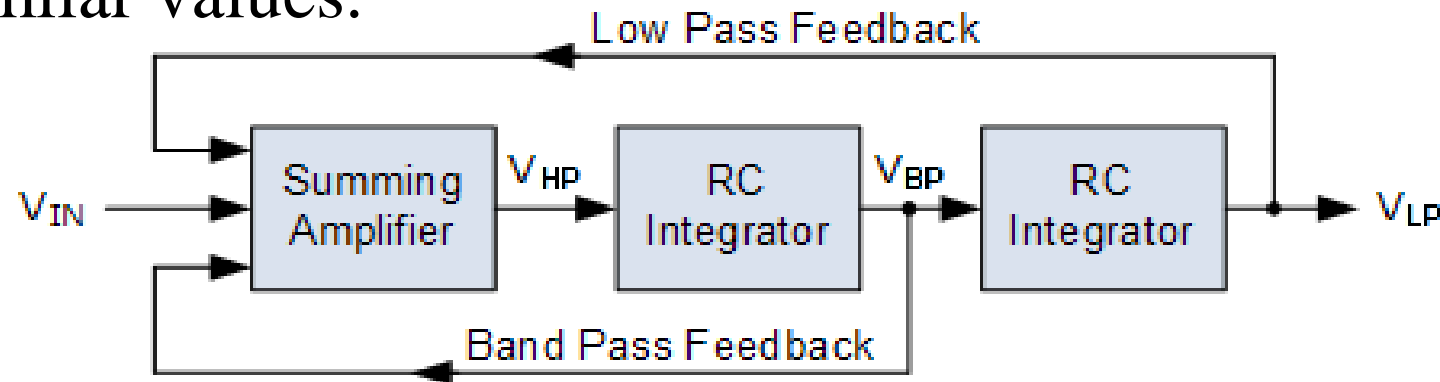
# State Variable Filter (Update for KHN Filter)

- The state variable is also called universal active filter is generally used for bandpass projects applications.
- It can be seen in the figure that it comprises a summing amplifier and 2 operational amplifier integrators which are attached in cascaded configuration to create 2nd order filter configuration.
- Though it is used as a bandpass filter the state variable arrangement also gives the low pass and high pass outputs. The mid-frequency is adjusted by the RC circuitry in these to integrators circuits.
- When it operates as a bandpass filter the critical frequency of the integrators are generally has similar values.


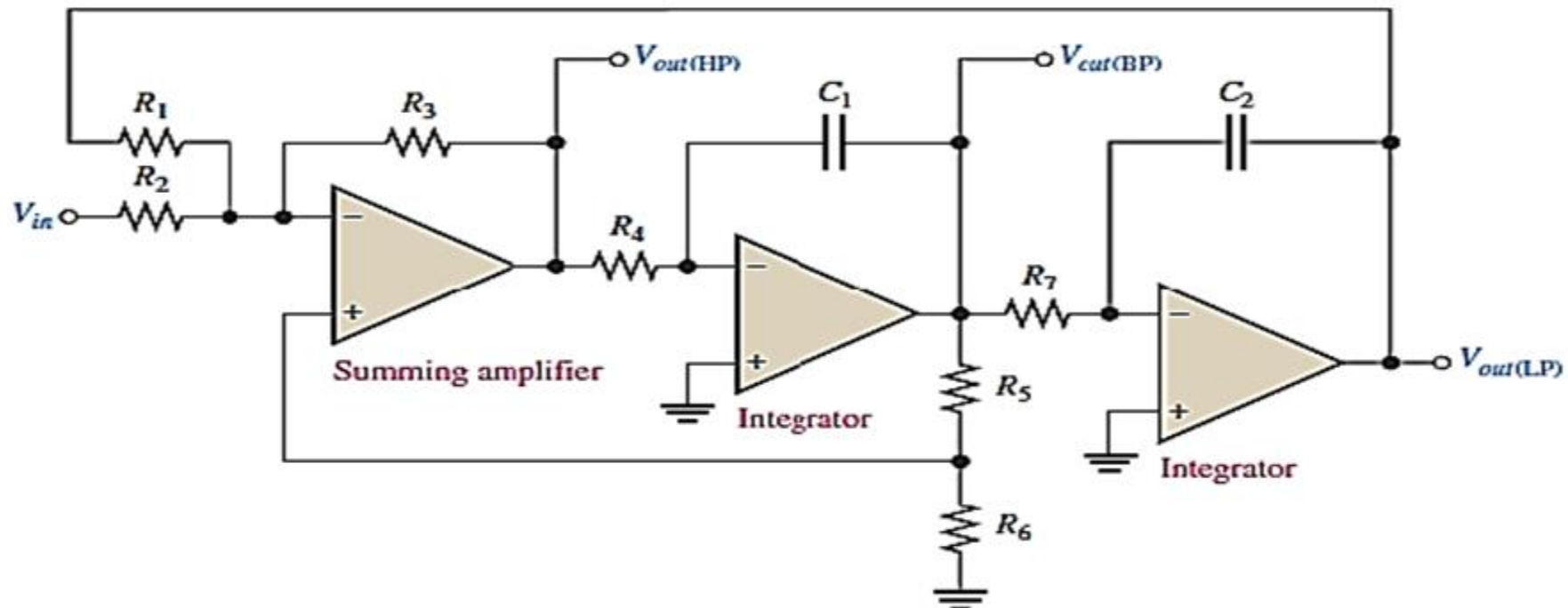
# State Variable Filter

- *State variable filters* are second-order RC active filters consisting of two identical op-amp integrators with each one acting as a first-order, single-pole low pass filter, a summing amplifier around which we can set the filters gain and its damping feedback network. The output signals from all three op-amp stages are fed back to the input allowing us to define the state of the circuit.




# State Variable Filter

- One of the main advantages of a state variable filter design is that all three of the filters main parameters, Gain (A), corner frequency  $f_C$ , and the quality factor Q can be adjusted or set independently without affecting the filters performance.
- In fact if designed correctly, the -3dB corner frequency, (  $f_c$  ) point for both the low pass amplitude response and the high pass amplitude response should be identical to the center frequency point of the band pass stage.
- That is  $f_{LP(-3dB)}$  equals  $f_{HP(-3dB)}$  which equals  $f_{BP(center)}$ .
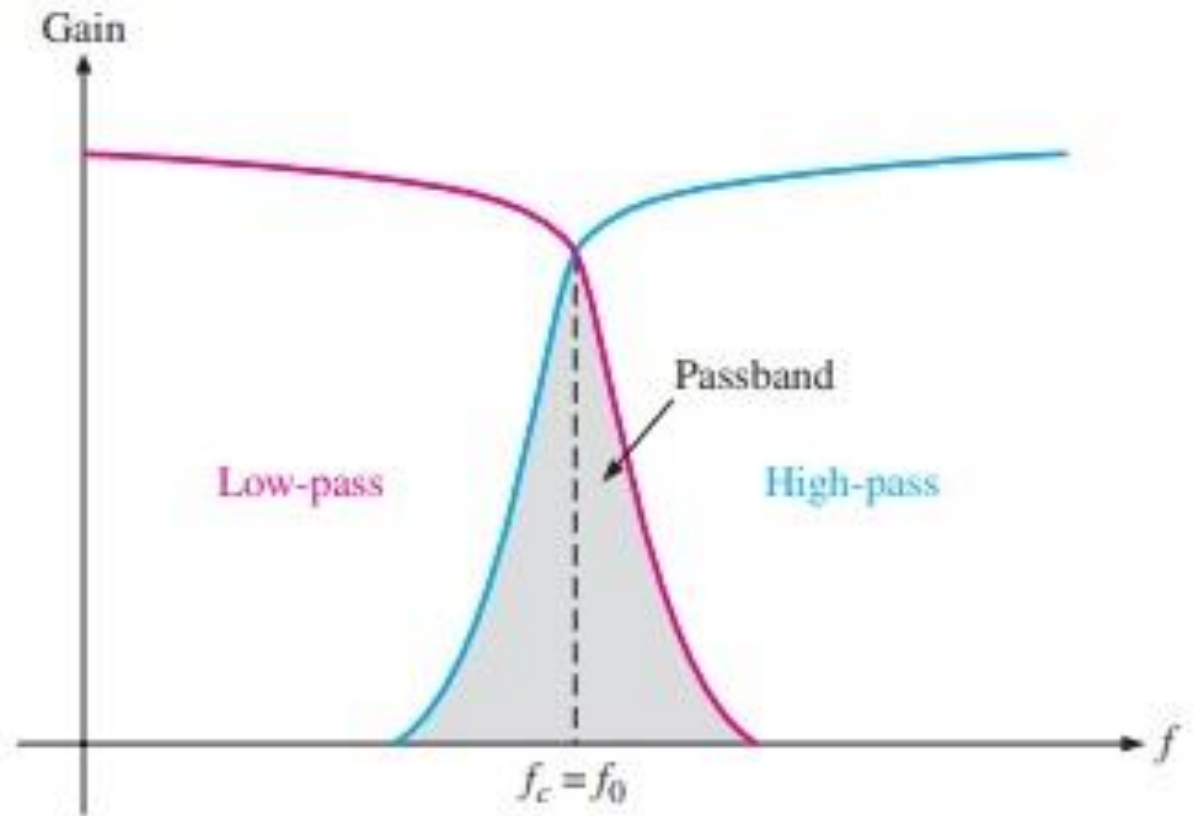
# State Variable Filter


- Over the  $f_c$  the low pass response diminishes so stopping the input signal from moving through the integrators. As a quencequence the bandpass filter results has a sharp peak at  $f_c$ .

$$f_c = \frac{1}{2\pi R_4 C_1} = \frac{1}{2\pi R_7 C_2}$$


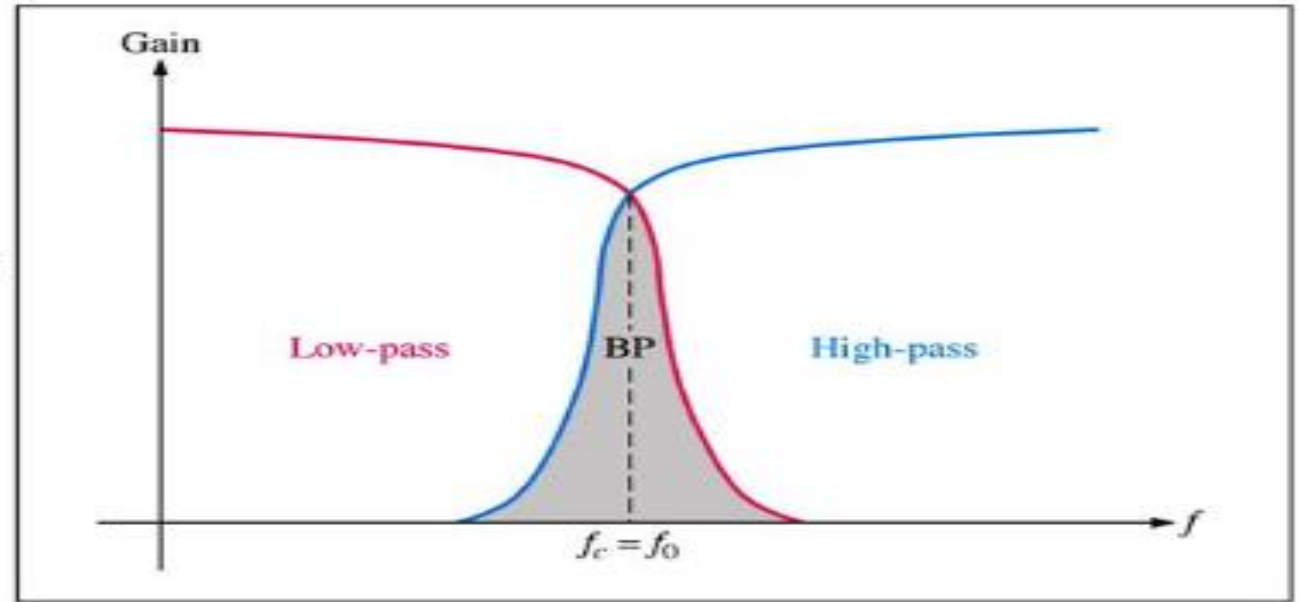
# State Variable Filter

- ❑ It consists of a **summing amplifier and two integrators**.
- ❑ It has outputs for low-pass, high-pass, and band-pass.
- ❑ The center frequency is set by the integrator RC circuits.
- ❑ The critical frequency of the integrators usually made equal
- ❑  $R_5$  and  $R_6$  set the  $Q$  (bandwidth).
- ❑ The band-pass output peaks sharply the center frequency giving it a high  $Q$ .
- ❑ The  $Q$  is set by the feedback resistors  $R_5$  and  $R_6$  according to the following equations :



$$Q = \frac{1}{3} \left( 1 + \frac{R_5}{R_6} \right)$$


$$f_c = \frac{1}{2\pi R_4 C_1} = \frac{1}{2\pi R_7 C_2}$$



# State Variable Filter (Update for KHN Filter)

- The KHN biquad filter is like to the state variable filter with the difference that it comprises of the integrator, with the inverting amplifier and another category of the integrator.
- Such differences in the arrangements among the KHN biquad and stable variable filter arrangement cause in some operation difference though both permit a large value of  $Q$ .
- In a KHN biquad filter, the  $Q$  is dependent on the critical frequency though in-state variable filter it is only the reverse the bandwidth is dependent and the  $Q$  is non-dependent on the critical frequency.

# State Variable Filter

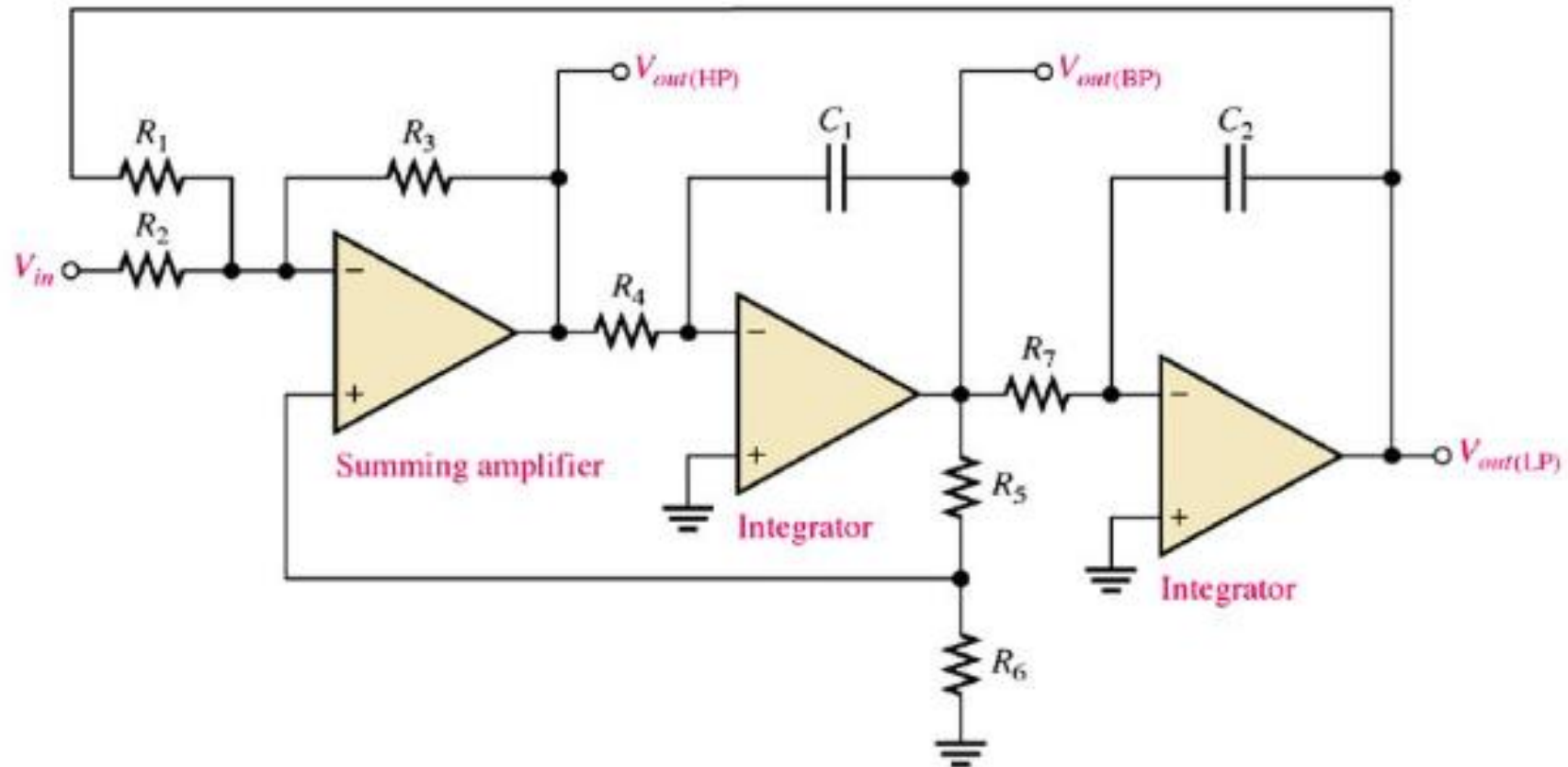

# State Variable Filter

$$* V_X = \left( \frac{V_{BP}}{R_5 + R_6} \right) \cdot R_6$$

$$\boxed{V_X = \frac{R_6}{R_5 + R_6} V_{BP} = K V_{BP}} \quad (1) \quad K = \frac{R_6}{R_5 + R_6}$$


$$* V_{HP} = - \frac{R_3}{R_1} V_{LP} - \frac{R_3}{R_2} V_{in} + \left( 1 + \frac{R_3}{R_1 \parallel R_2} \right) V_X$$

$$\boxed{V_{HP} = - \frac{R_3}{R_1} V_{LP} - \frac{R_3}{R_2} V_{in} + \left( 1 + \frac{R_3}{R_1 \parallel R_2} \right) K V_{BP}} \quad (2)$$

$$* \boxed{V_{BP} = - \frac{1}{s C_1 R_4} V_{HP}} \quad (3)$$

$$* V_{LP} = \left( - \frac{1}{s C_1 R_4} \right) \left( - \frac{1}{s C_2 R_7} \right) V_{HP}$$
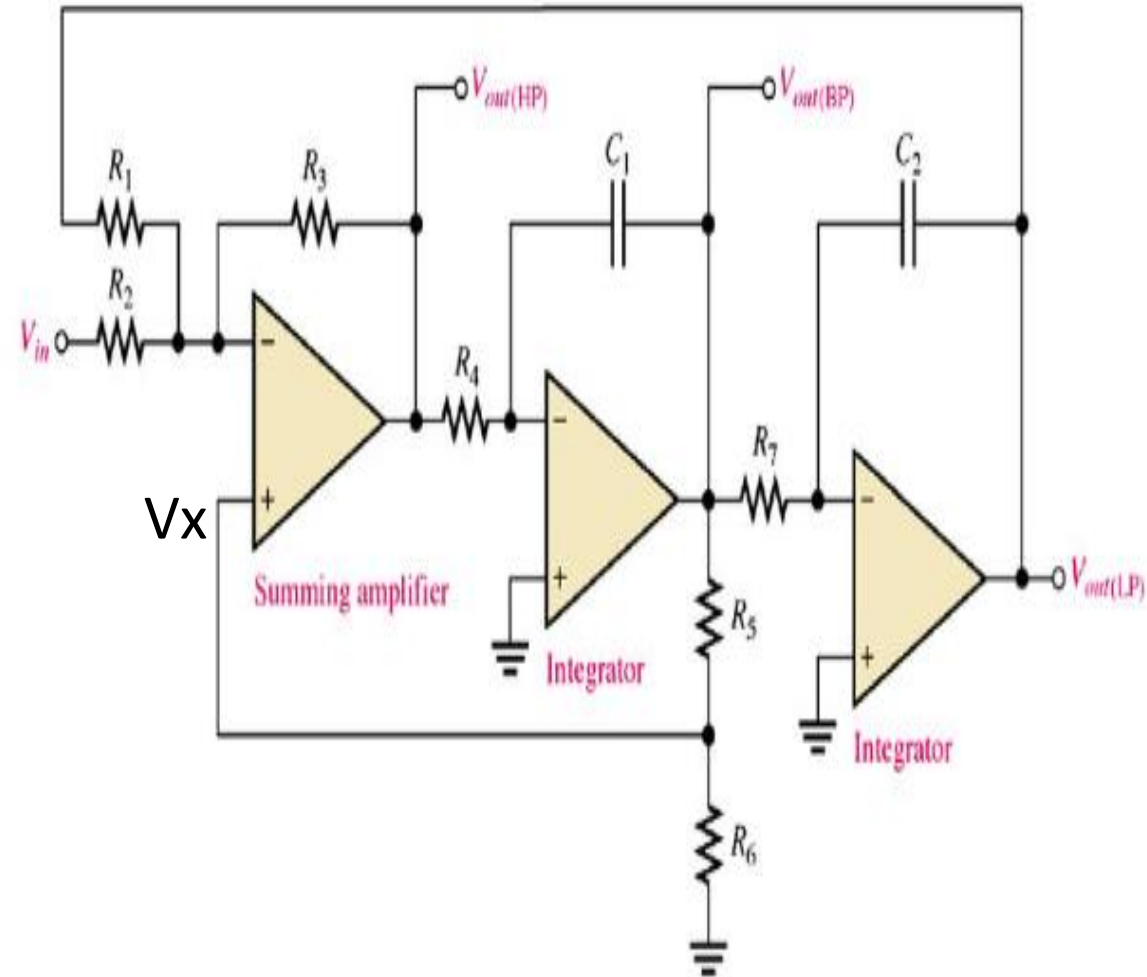
$$\boxed{V_{LP} = \frac{1}{s^2 C_1 C_2 R_4 R_7} V_{HP}} \quad (4)$$



# State Variable Filter

Sub. into (2)

$$\therefore V_{hp} = -\frac{R_3}{R_1} \frac{1}{s^2 C_1 C_2 R_4 R_7} V_{hp} - \frac{R_3}{R_2} V_{in}$$

$$+ \left(1 + \frac{R_3}{R_1 R_2}\right) K \frac{-1}{s C_1 R_4} V_{hp}$$

$$V_{hp} \left[ 1 + \frac{R_3 / R_1}{s^2 C_1 C_2 R_4 R_7} + \frac{K \left(1 + \frac{R_3}{R_1 R_2}\right)}{s C_1 R_4} \right] = -\frac{R_3}{R_2} V_{in}$$

$$V_{hp} \left[ \frac{s^2 C_1 C_2 R_4 R_7 + \frac{R_3}{R_1} + K \left[1 + \frac{R_3}{R_1 R_2}\right] s C_2 R_7}{s^2 C_1 C_2 R_4 R_7} \right] = -\frac{R_3}{R_2} V_{in}$$

$$\therefore THP = \frac{V_{hp}}{V_{in}} = \frac{-\frac{R_3}{R_2} s^2 C_1 C_2 R_4 R_7}{s^2 C_1 C_2 R_4 R_7 + K \left[1 + \frac{R_3}{R_1 R_2}\right] s C_2 R_7 + \frac{R_3}{R_1}}$$

$$THP = \frac{-\frac{R_3}{R_2} s^2 C_1 C_2 R_4 R_7}{C_1 C_2 R_4 R_7 \left[ s^2 + \frac{K \left(1 + \frac{R_3}{R_1 R_2}\right)}{C_1 C_2 R_4 R_7} s C_2 R_7 + \frac{R_3}{R_1} \frac{1}{C_1 C_2 R_4 R_7} \right]}$$

# State Variable Filter

$$T_{HP} = \frac{-\frac{R_3}{R_2} s^2}{s^2 + \frac{1}{C_1 R_4} k \left(1 + \frac{R_3}{R_1 \| R_2}\right) s + \frac{R_3}{R_1} \frac{1}{C_1 C_2 R_4 R_7}}$$

$$\frac{R_3}{R_1} = 1, \boxed{R_3 = R_1}$$

$$T_{HP} = \frac{-\frac{R_3}{R_2} s^2}{s^2 + \frac{1}{C_1 R_4} k \left(1 + \frac{R_3}{R_1 \| R_2}\right) s + \frac{1}{C_1 C_2 R_4 R_7}}$$

$$T_{HP} = \frac{-a s^2}{s^2 + \left(\frac{\omega_0}{Q}\right) s + \omega_0^2}$$

$$\therefore \omega_0 = \frac{1}{\sqrt{C_1 C_2 R_4 R_7}}$$

$$\boxed{f_0 = \frac{1}{2\pi \sqrt{C_1 C_2 R_4 R_7}}}$$

$$C_1 = C_2 = C, R_4 = R_7 = R, \omega_0 = \frac{1}{C_1 R_4} = \frac{1}{C_2 R_7}$$

$$\boxed{f_0 = \frac{1}{2\pi R C}} = \frac{1}{2\pi R_4 C_1} = \frac{1}{2\pi R_7 C_2}$$

# State Variable Filter

$$\frac{\omega_o}{Q} = \frac{1}{C_1 R_4} \frac{R_6}{R_5 + R_6} \left[ 1 + \frac{R_5}{\frac{R_1 R_2}{R_1 + R_2}} \right]$$

$$\frac{\omega_o}{Q} = \frac{1}{C_1 R_4} \frac{1}{\frac{R_5}{R_6} + 1} \left[ 1 + \frac{R_1 + R_2}{R_2} \right]$$

Choose  $R_1 = R_2$

$$\frac{\omega_o}{Q} = \frac{1}{C_1 R_4} \frac{1}{\frac{R_5}{R_6} + 1} [1 + 2]$$

$$\frac{\omega_o}{Q} = \frac{1}{C_1 R_4} \frac{3}{\frac{R_5}{R_6} + 1}$$

$$\therefore Q = C_1 R_4 \omega_o \frac{1}{3} \left[ 1 + \frac{R_5}{R_6} \right]$$


$$Q = C_1 R_4 \frac{1}{C_1 R_4} \frac{1}{3} \left[ 1 + \frac{R_5}{R_6} \right]$$

$$Q = \frac{1}{3} \left[ 1 + \frac{R_5}{R_6} \right]$$

# State Variable Filter

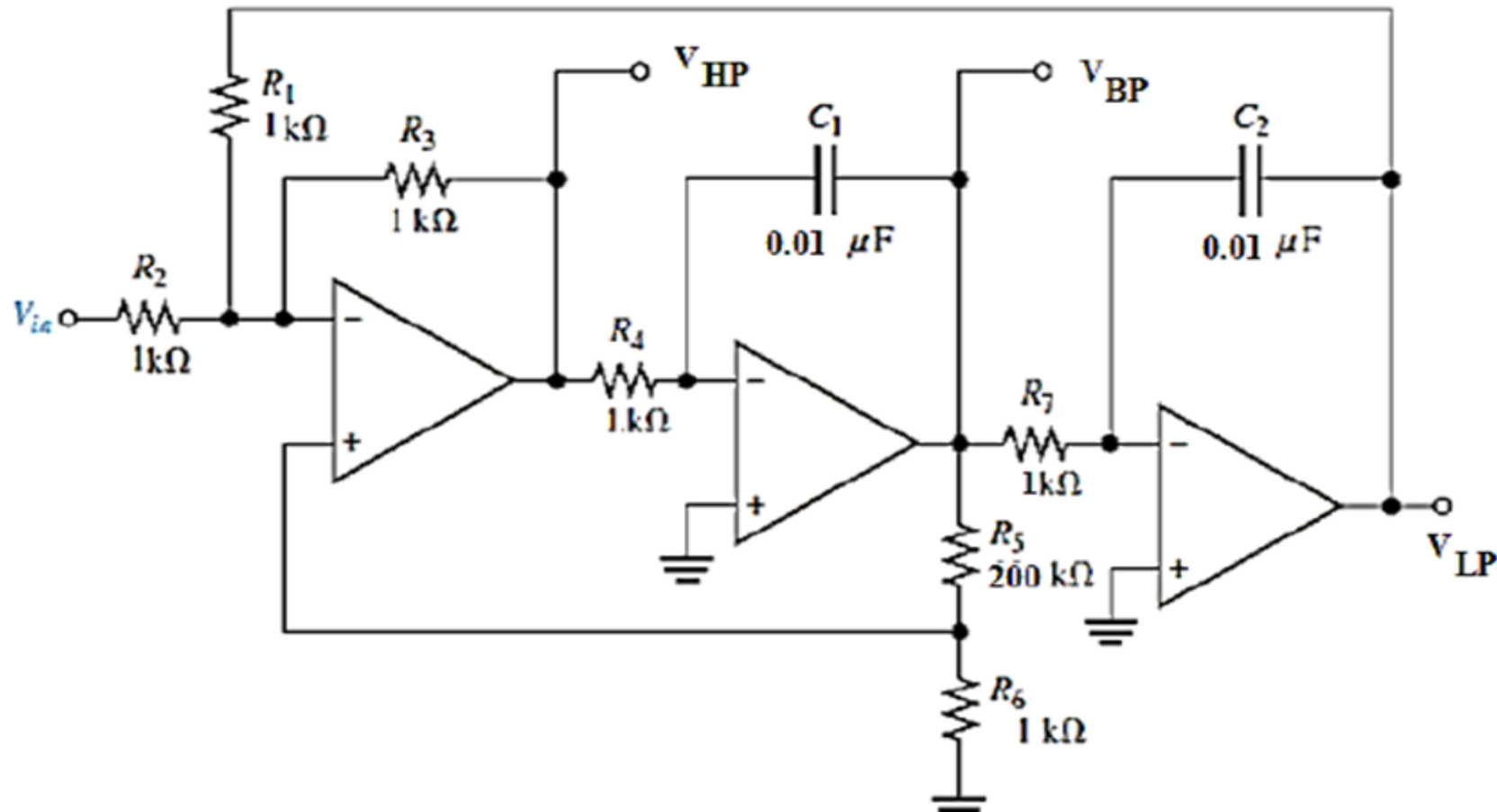- Example 1:

Determine the center frequency,  $Q$ , and BW for the state-variable filter shown.





# State Variable Filter

**Solution** For each integrator,

$$f_c = \frac{1}{2\pi R_4 C_1} = \frac{1}{2\pi R_7 C_2} = 15.92\text{KHz}$$

The center frequency is approximately equal to the critical frequencies of integrators.

$$f_0 = f_c = 15.92\text{KHz}$$


$$Q = \frac{1}{3} \left( \frac{R_5}{R_6} + 1 \right) = \frac{1}{3} \left( \frac{200\text{ k}\Omega}{1.0\text{ k}\Omega} + 1 \right) = 67$$

$$BW = \frac{f_0}{Q} = \frac{15.92\text{KHz}}{67} = 237.5\text{Hz}$$


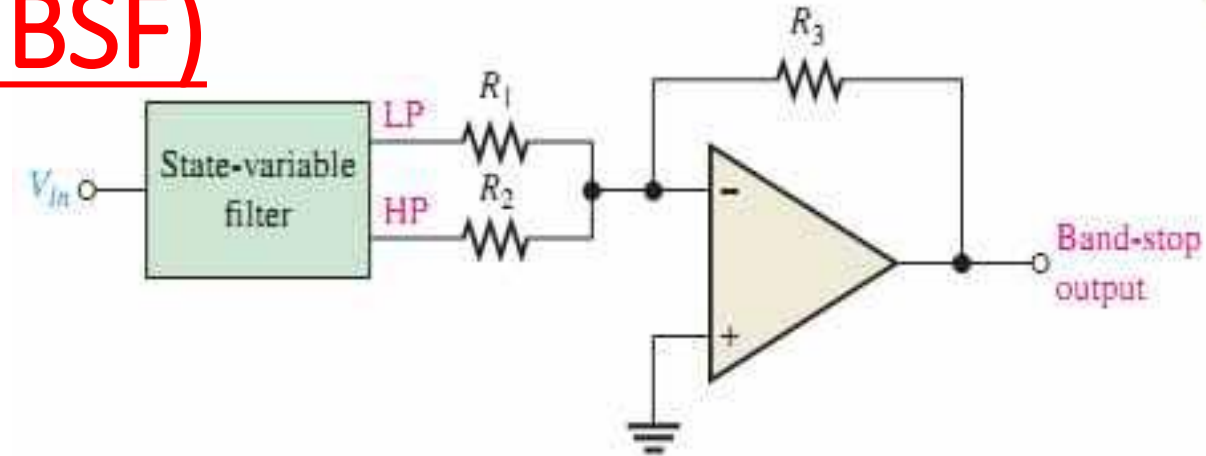
# State Variable Notch Filter (BSF)

- Summing the low-pass and the high-pass responses of the state-variable filter with a summing amplifier creates a band-stop filter.
- One important application of this filter is minimizing the 60 Hz "hum" in audio systems by setting the center frequency to 60 Hz.




$$H(s) = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + s\left(\frac{\omega_o}{Q}\right) + \omega_o^2}$$


$$H_{LP} = \frac{a_0}{s^2 + s\left(\frac{\omega_o}{Q}\right) + \omega_o^2}$$

$$H_{HP} = \frac{a_2 s^2}{s^2 + s\left(\frac{\omega_o}{Q}\right) + \omega_o^2}$$
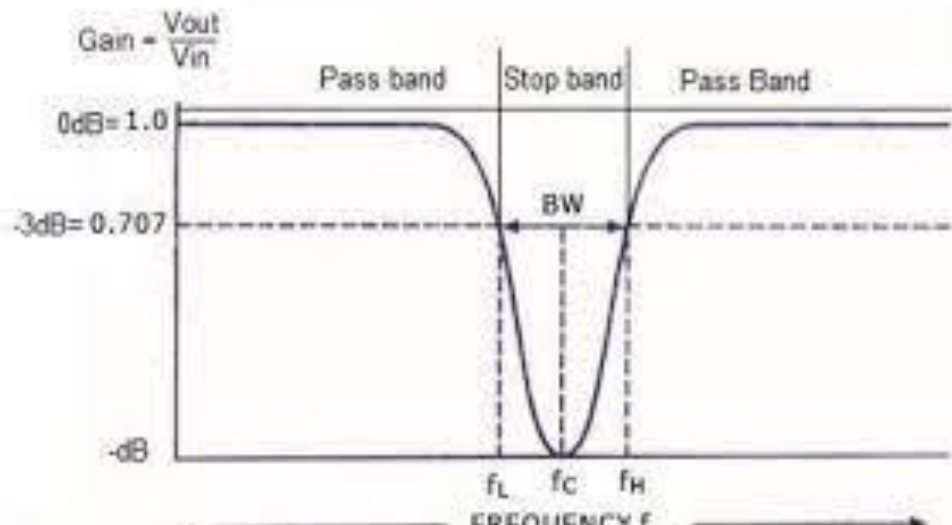
$$H_{BP} = \frac{a_1 s}{s^2 + s\left(\frac{\omega_o}{Q}\right) + \omega_o^2}$$



# State Variable Notch Filter (BSF)

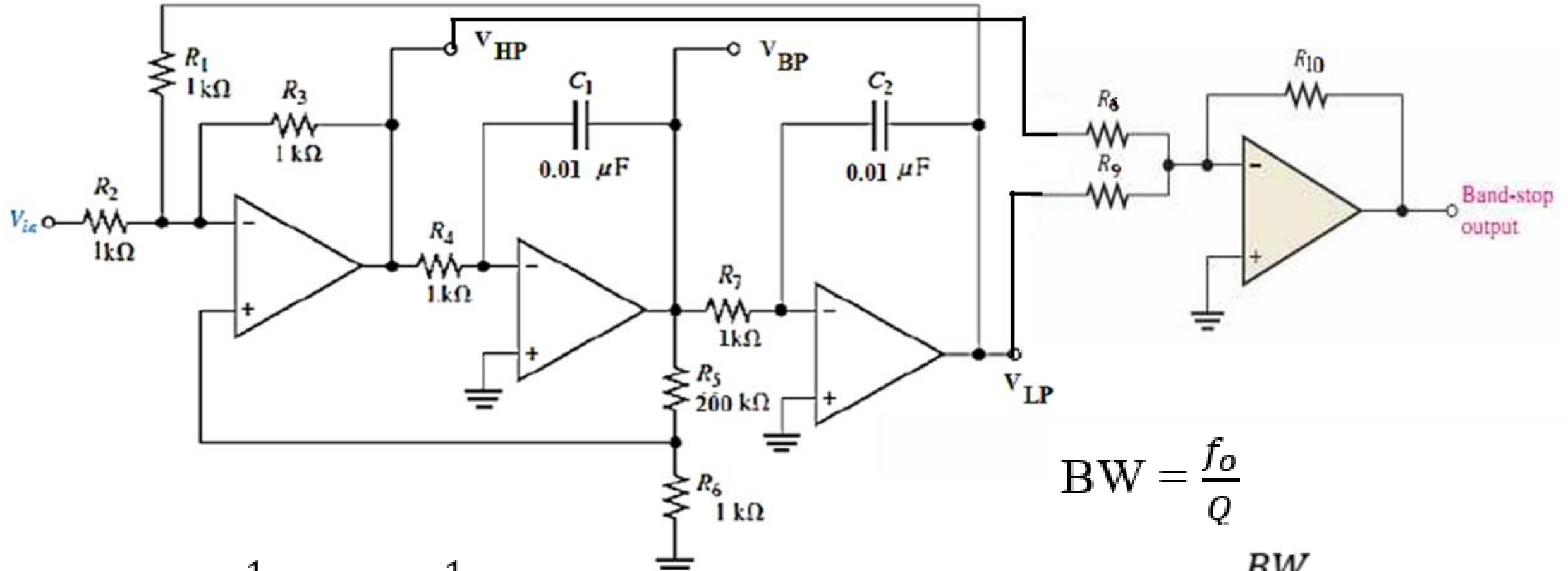

$$BW = \frac{f_o}{Q}$$

$$f_o = \frac{1}{2\pi R_4 C_1} = \frac{1}{2\pi R_7 C_2}$$

$$f_l = f_o - \frac{BW}{2}$$

$$f_H = f_o + \frac{BW}{2}$$

# State Variable Notch Filter (BSF)

- **Example2:**

For the state variable Notch filter shown in last slide:

- 1- Calculate the notch frequency  $f_o$ .
- 2- Design R5 and R6 for a quality factor Q of 20.
- 3- Calculate the lower and upper cut-off frequencies.

- Solution:

$$f_o = \frac{1}{2\pi R_4 C_1} = \frac{1}{2\pi R_7 C_2} = \frac{1}{2\pi (10^4)(0.1 \times 10^{-6})} = 159.15 \text{ Hz}$$

$$Q = 20 = \frac{1}{3} \left[ \frac{R_5}{R_6} + 1 \right]$$

$$\frac{R_5}{R_6} = 59 \quad \text{choose } R_6 = 1\text{K}\Omega, R_5 = 59$$

$$BW = \frac{f_o}{Q} = 8\text{Hz}$$

$$f_l = f_o - \frac{BW}{2} = 155.15\text{Hz} \quad f_H = f_o + \frac{BW}{2} = 163.15\text{Hz}$$