



Electronics and Communications Department

Analog Electronics


Lab 5

Differential Amplifier

Name	عبدالرحمن علي موسى علي
Section	4
Date	9/5/2023

- **Part I (DC measurements)**

❖ from the circuit shown in the figure.

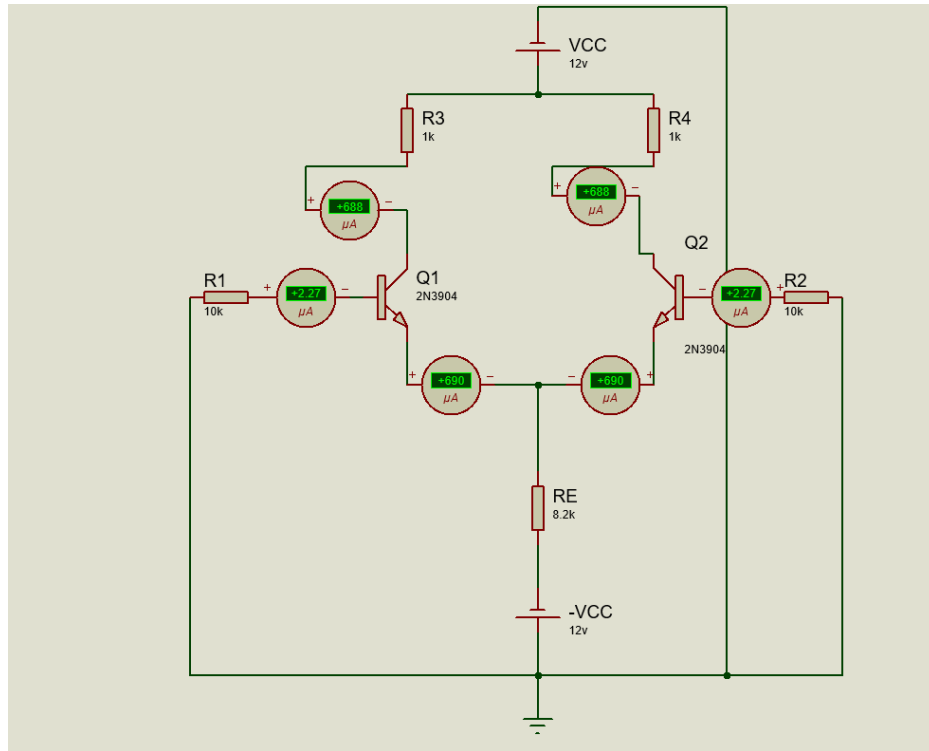


- we get the DC measurements as shown in the table below.

-Assume $V_T = 26\text{mV}$

I_{C1}	I_{E1}	I_{B1}	β	$r_e = \frac{V_T}{I_E}$	$g_m = \frac{I_C}{V_T}$
0.688mA	0.69mA	2.27μA	303	37.6Ω	26.4mA/V

- **Part II (AC)**

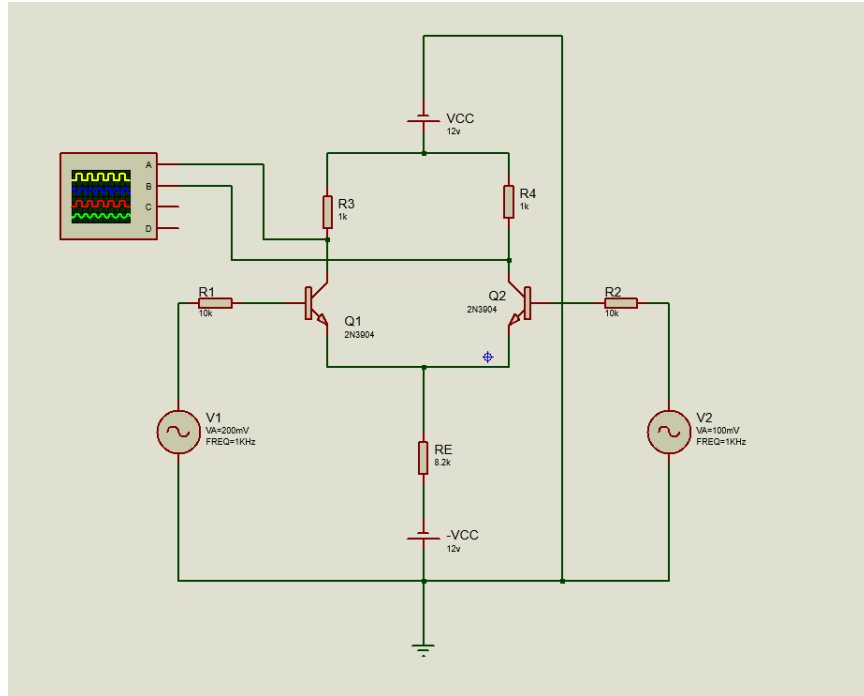❖ The circuit after connecting 2 AC sources.



$$r_{\pi} = \frac{V_T}{I_B} = 11.45 \text{ K}\Omega, \quad r_{ie} = \frac{R_B + r_{\pi}}{1 + \beta} + r_e = 108.16 \text{ }\Omega$$


$$A_{v_{dm}} = \frac{-R_C}{r_{ie}} = -9.24 \text{ V/V}, \quad A_{v_{cm}} = \frac{-R_C}{2R_E} = -0.05 \text{ V/V}$$

$$\text{CMRR} = \frac{A_{v_{dm}}}{A_{v_{cm}}} = 184.8 = 45.3 \text{ dB}$$

➤ Now we will see the three modes of the Differential Amplifier:


-Assume V_1 at 200mV in the three cases.

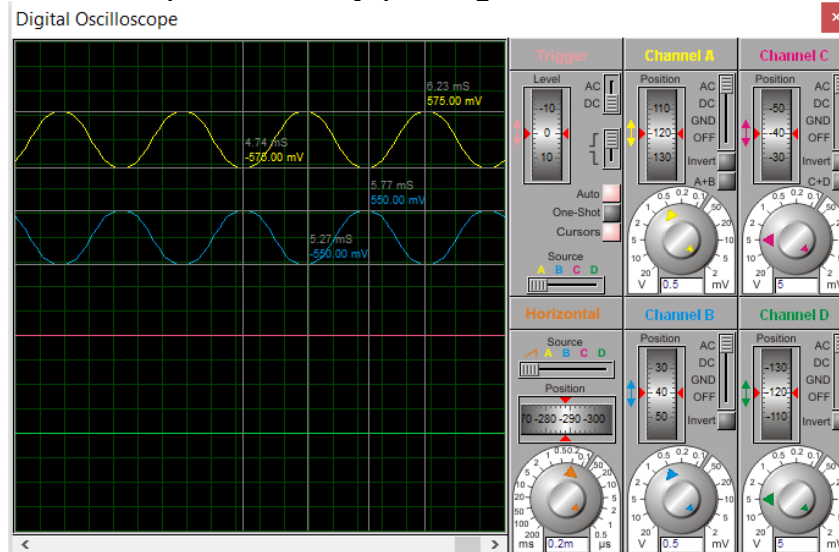a) Double input mode by putting V_2 at 100mV.




We get $V_{o1} = 575\text{mV}$, $V_{o2} = 550\text{mV}$

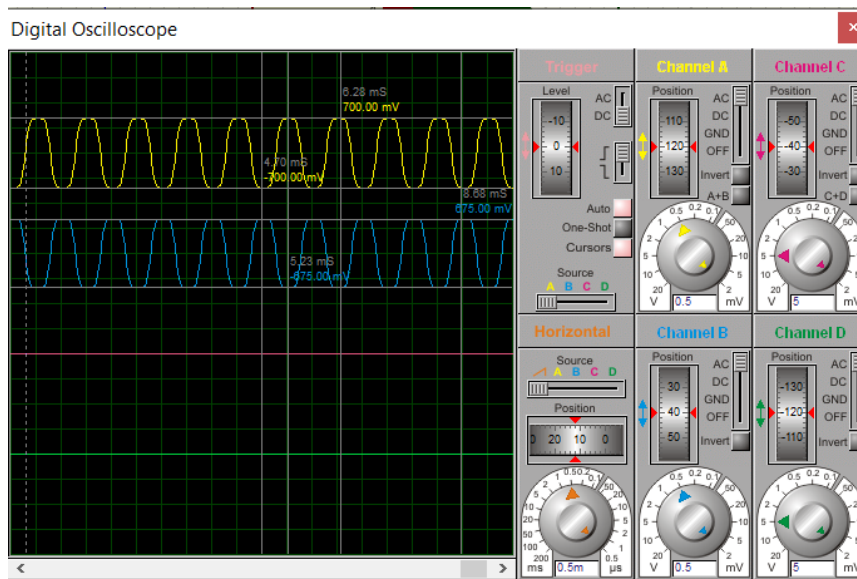b) Single input mode by deleting V_2 source and connecting R_2 to the ground.



We get $V_{o1} = 700\text{mV}$, $V_{o2} = 675\text{mV}$

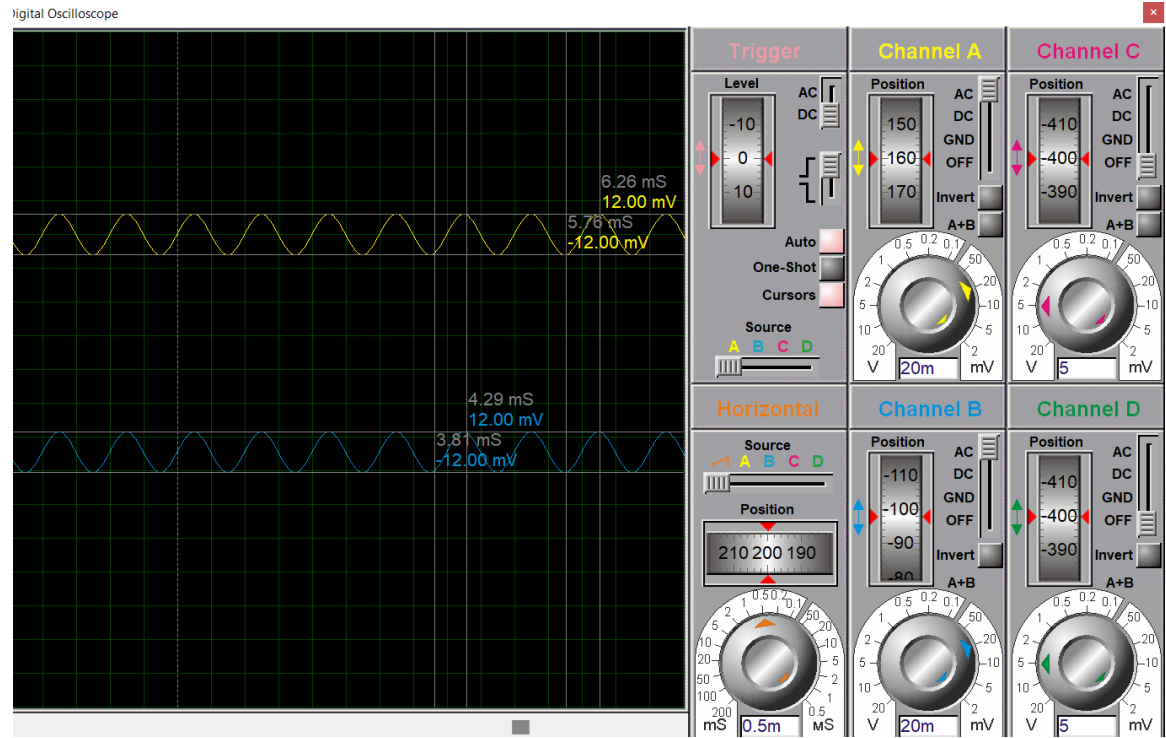- c) Common input mode by connecting R2 to V1 (the same source for 2 input).



We get $V_{o1} = 12\text{mV}$, $V_{o2} = 12\text{mV}$

V_1	V_2	V_{o1}	V_{o2}	$A_V = \frac{V_{o1} - V_{o2}}{V_1 - V_2}$
200mV	100mV	575mV	550mV	$A_{v_{dm}} = \frac{575 - (-550)}{200 - 100} = 11.25$
200mV	0	700mV	675mV	$A_{v_{dm}} = \frac{700 - (-675)}{200 - 0} = 6.875$
200mV	200mV	0	0	$A_{v_{cm}} = 0$