

# **Electronic Circuits Analysis III**

## **Oscillators**

### **Principles**

#### **RC Phase-Shift Oscillator**

**Fall 2020**

# Oscillators

- Oscillation:

an effect that repeatedly and regularly fluctuates about the mean value

- Oscillator:

circuit that produces oscillation

- Characteristics:

wave-shape, frequency, amplitude, distortion, stability



# Application of Oscillators

- ❑ Oscillators are used to generate signals, e.g.
  - ▣ Used as a local oscillator to transform the RF signals to IF signals in a receiver;
  - ▣ Used to generate RF carrier in a transmitter
  - ▣ Used to generate clocks in digital systems;
  - ▣ Used as sweep circuits in TV sets and CRO.



# Oscillators Classifications



---

- ❑ Oscillators are classified based on:
  - ❑ Output waveform
  - ❑ Circuit Components
  - ❑ Range of Operating Frequency



# Oscillators Classifications



- Oscillators are classified based on:
  - ▣ Output waveform
    - Sinusoidal Oscillators, pure Sinusoidal output waveform
    - Non-sinusoidal Oscillators, triangular, square, sawtooth output waveforms



# Oscillators Classifications



- Oscillators are classified based on:
  - ▣ Circuit Components
    - RC Oscillators, components Resistances and Capacitors
    - LC Oscillators, components Inductances and Capacitors



# Oscillators Classifications

□ Oscillators are classified based on:

▣ Range of Operating Frequency

■ Audio Frequency (A.F.) Oscillators,

■ Range: 20Hz to 100-200KHz

■ It's also called **Low Frequency (L.F.) Oscillators**

■ **RC Oscillators**

■ Radio Frequency (R.F.) Oscillators,

■ Range: More than 200-300KHz to xxxGHz

■ It's also called **High Frequency (H.F.) Oscillators**


■ **LC Oscillators**





# Sinusoidal Oscillators
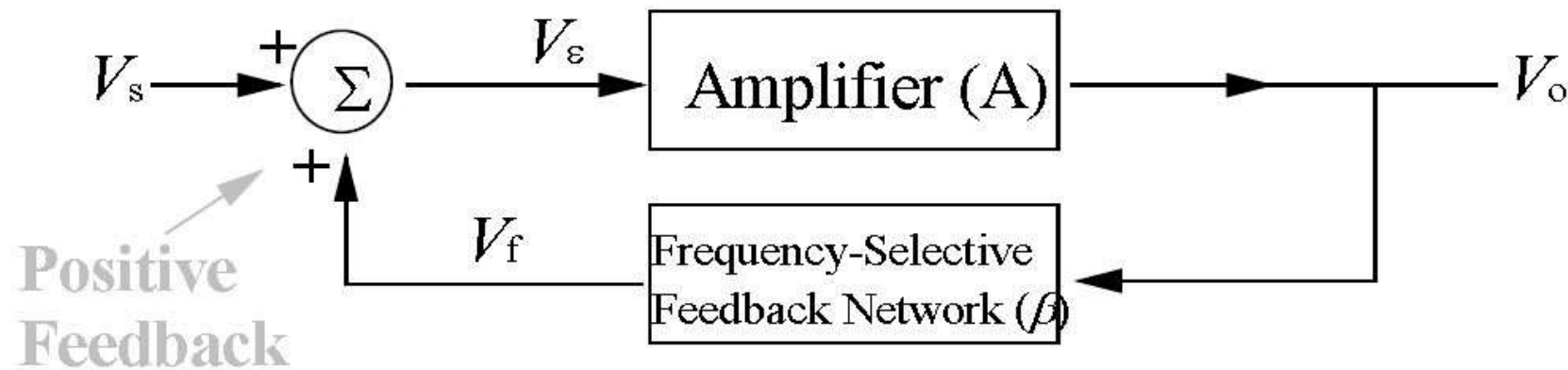
## □ Basic Principles of Linear Oscillators




## □ A linear oscillator contains:

- ▣ a frequency selection feedback network
- ▣ an amplifier to maintain the loop gain at **unity**



# Basic Linear Oscillator

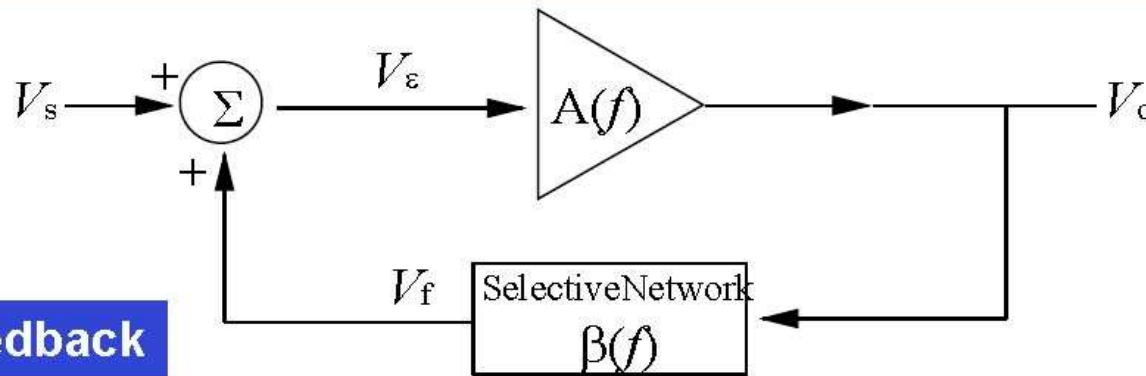

$$V_o = AV_\varepsilon = A(V_s + V_f) \quad \text{and} \quad V_f = \beta V_o$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{A}{1 - A\beta}$$

If  $V_s = 0$ , the only way that  $V_o$  can be nonzero is that **loop gain  $A\beta=1$**  which implies that

$$\begin{aligned} |A\beta| &= 1 \\ \angle A\beta &= 0 \end{aligned}$$


**(Barkhausen Criterion)**





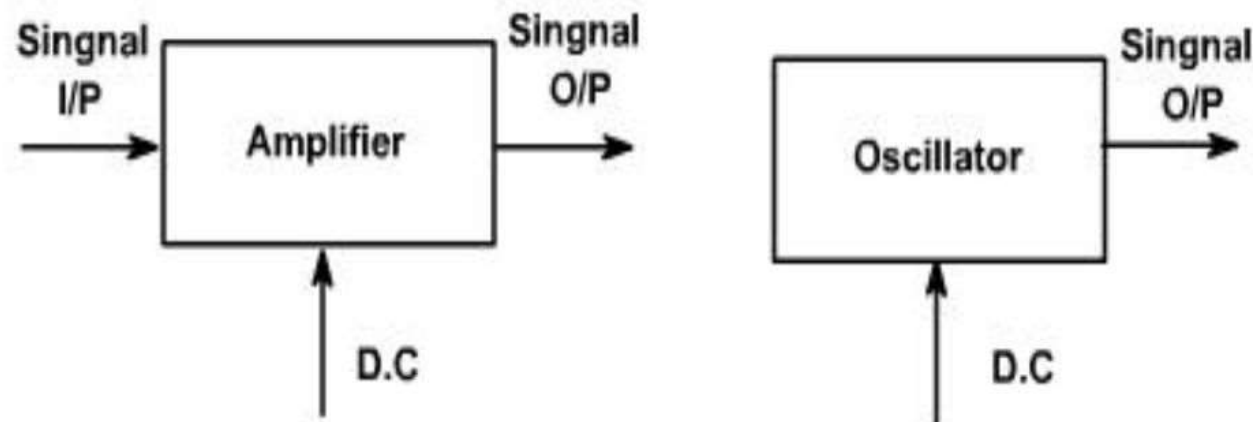
# Basic Linear Oscillator

- The oscillator, on the other hand, requires no external signal to initiate or maintain the energy conversion process.
- Instead an output signals is produced as long as source of DC power is connected.



# Oscillators: Basic Block Diagram

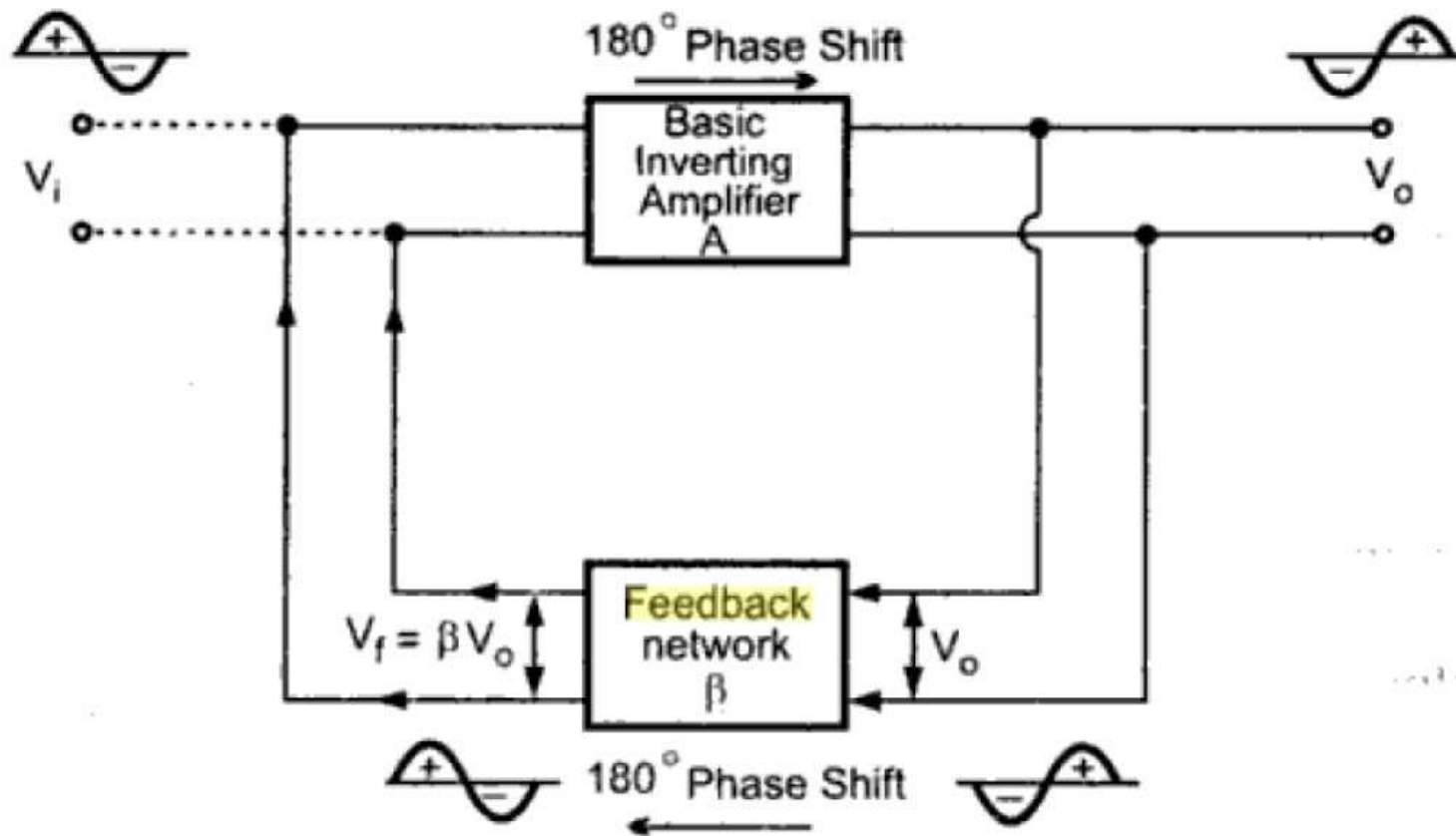

# Oscillators: Basic Block Diagram

## (Barkhausen Criterion)


1. The total phase shift around a loop, as the signal proceeds from input through amplifier, **feedback** network back to input again, completing a loop, is precisely  $0^\circ$  or  $360^\circ$ .
2. The magnitude of the product of the open loop gain of the amplifier ( $A$ ) and the magnitude of the **feedback** factor  $\beta$  is unity i.e.  $|A\beta| = 1$ .

$$|A\beta| = 1$$

$$\angle A\beta = 0 \quad \text{or} \quad 360$$

# Sinusoidal Oscillators

## □ Growing Type Oscillation

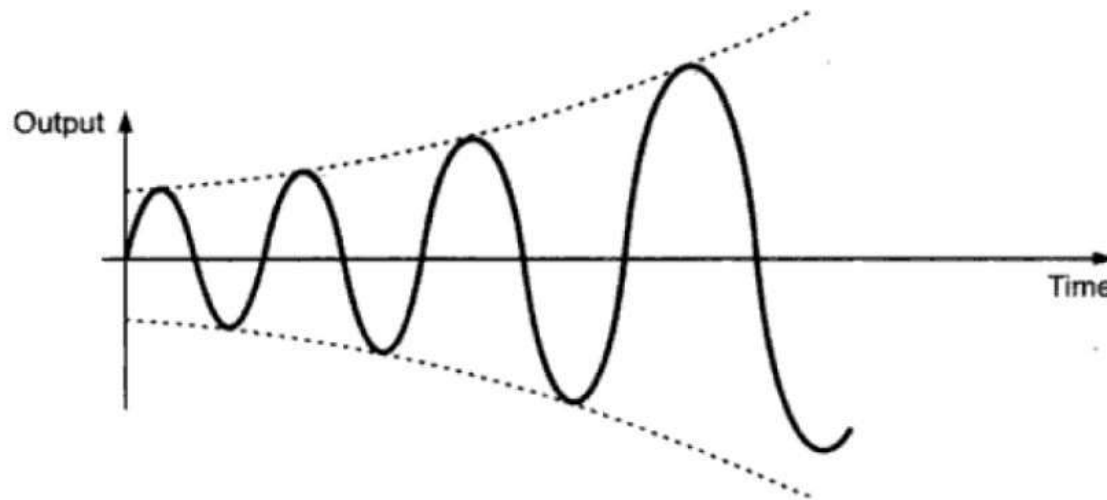


When the total phase shift around a loop is  $0^\circ$  or  $360^\circ$  and  $|A\beta| > 1$ , then the output oscillates but the oscillations are of growing type.



# Sinusoidal Oscillators

## □ Exponentially Decaying Oscillation

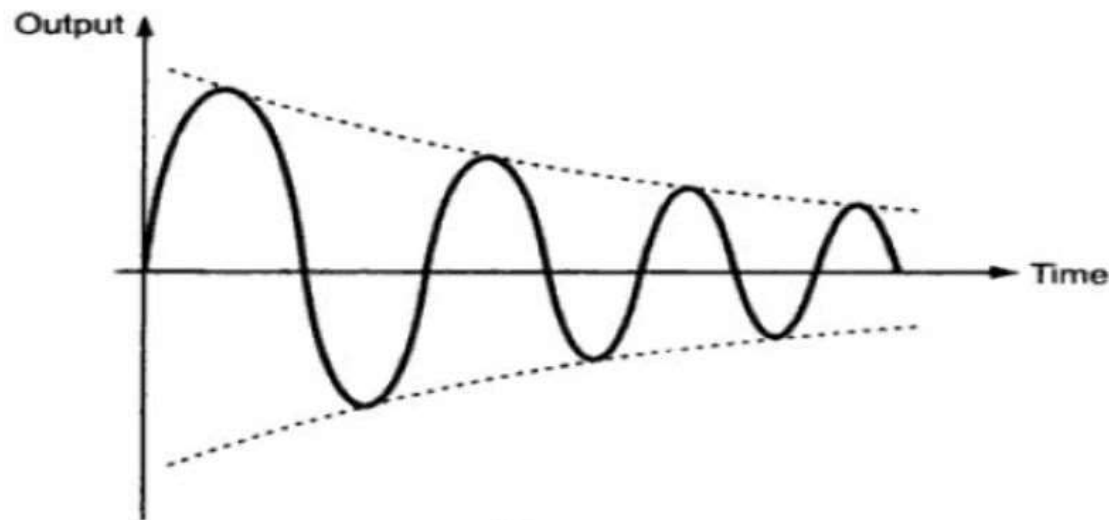

When total phase shift around a loop is  $0^\circ$  or  $360^\circ$  but  $|A\beta| < 1$  then the oscillations are of decaying type i.e. such oscillation amplitude decreases exponentially and the oscillations finally cease. Thus circuit works as an amplifier without oscillations.


# Linear Oscillators



1. RC Phase-Shift Oscillators
2. Wien Bridge Oscillators
3. LC Oscillators




# 1. RC Phase-Shift Oscillator

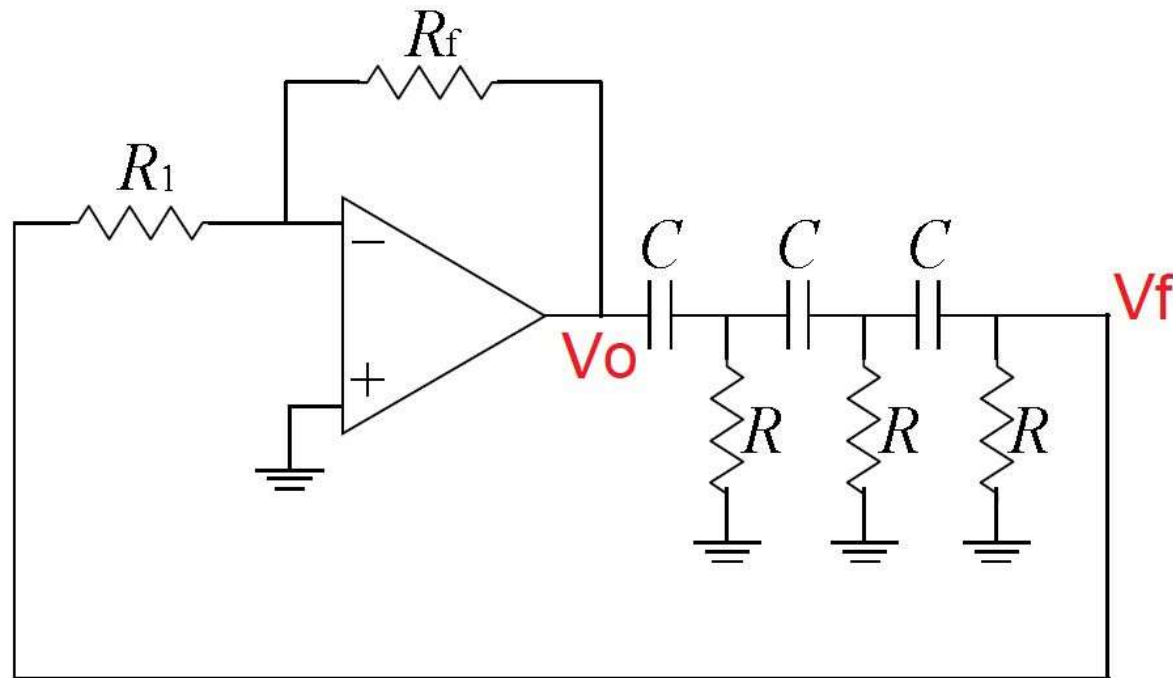

- **Using an inverting amplifier**  
180° phase shift  $V_i$  &  $V_o$
- The additional 180° phase shift is provided by an RC phase-shift network

$$A_v = -\frac{R_f}{R_1} \Rightarrow \angle A_v = 180$$
$$\Rightarrow \angle \beta = 180$$

# Feedback Network

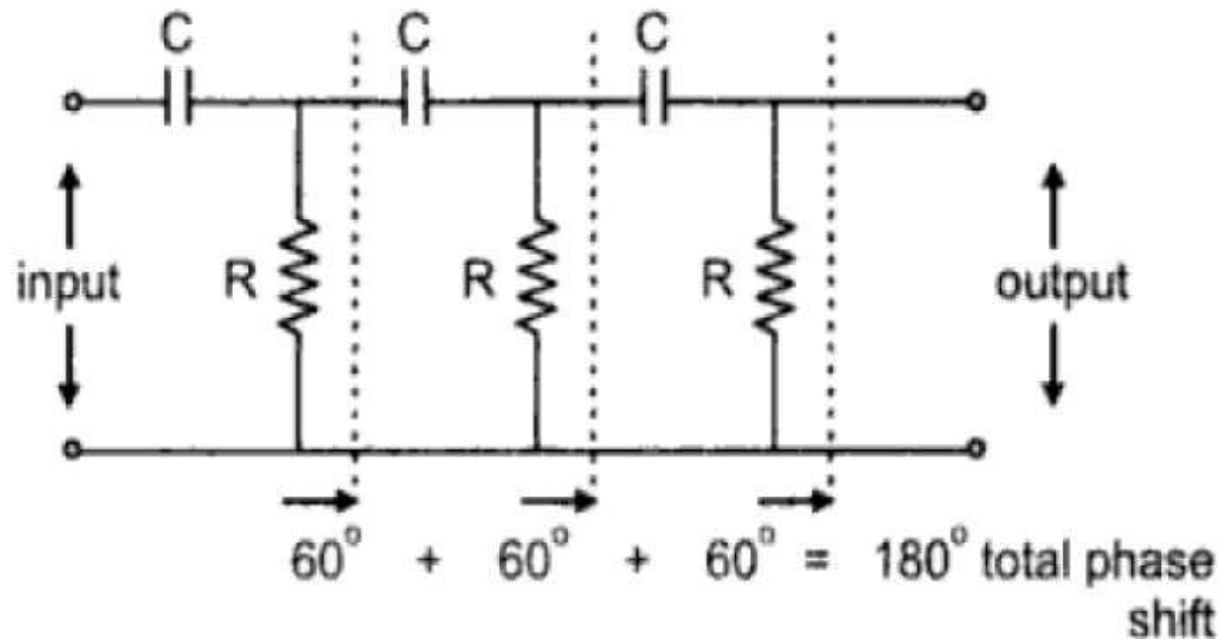


The network is also called the **ladder network**. All the resistance values and all the capacitance values are same, so that for a particular frequency, each section of R and C produces a phase shift of  $60^\circ$ .

Amplifier gain

$$A = \frac{V_o}{V_f} = -\frac{R_F}{R_i}$$

Feedback factor ( $\beta$ )

$\beta$  - network

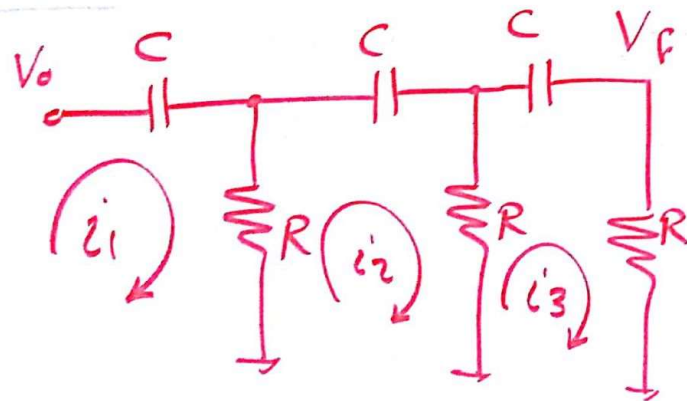

$$V_f = i_3 R \quad (1)$$

Loop ①

$$(R - jX_c) i_1 - R i_2 = V_o \quad (2)$$

Loop ②

$$(2R - jX_c) i_2 - R i_1 - R i_3 = 0$$

$$-R i_1 + (2R - jX_c) i_2 - R i_3 = 0 \quad (3)$$

Loop ③

$$(2R - jX_c) i_3 - R i_2 = 0$$

$$-R i_2 + (2R - jX_c) i_3 = 0 \quad (4)$$

$$\beta = \frac{V_f}{V_o}$$

$$C \rightarrow -jX_c, X_c = \frac{1}{\omega_c}$$

$$\Delta = \begin{vmatrix} \oplus & & \\ (R-jX_c) & -R & 0 \\ -R & (2R-jX_c) & -R \\ 0 & -R & (2R-jX_c) \end{vmatrix}$$

$$\Delta_3 = \begin{vmatrix} (R-jX_c) & -R & V_o \\ -R & (2R-jX_c) & 0 \\ 0 & -R & 0 \end{vmatrix}$$

$$\Delta = (R-jX_c) [(2R-jX_c)^2 - R^2] + R [-R(2R-jX_c) - 0]$$

$$\Delta = [R^3 - 5RX_c^2] + j[X_c^3 - 6R^2X_c]$$

$$\Delta_3 = V_o [R^2 - 0]$$

$$\Delta_3 = V_o R^2$$

$$\therefore I_3 = \frac{\Delta_3}{\Delta} = \frac{V_o R^2}{[R^3 - 5RX_c^2] + j[X_c^3 - 6R^2X_c]}$$

$$\therefore V_f = I_3 \cdot R = \frac{V_o R^3}{[R^3 - 5RX_c^2] + j[X_c^3 - 6R^2X_c]}$$

$$\beta = \frac{V_f}{V_o} = \frac{R^3}{[R^3 - 5RX_c^2] + j[X_c^3 - 6R^2X_c]}$$



$A \rightarrow \text{Real} \therefore \beta \rightarrow \text{Real}$

$$\therefore X_c^3 - 6R^2 X_c = 0$$

$$X_c^2 = 6R^2 \rightarrow X_c = \sqrt{6} R$$

$$\frac{1}{\omega_c} = \sqrt{6} R$$

$$\begin{cases} A\beta = 1 \\ -\frac{R_F}{R_i} \left(-\frac{1}{29}\right) = 1 \end{cases}$$

$$\frac{R_F}{R_i} = 29$$

$$\omega_0 = \frac{1}{\sqrt{6} RC}, \quad \omega_0 = 2\pi f_0$$


$$\therefore f_0 = \frac{1}{2\pi\sqrt{6} RC} \quad \text{oscillation frequency}$$

Oscillation Condition

$$\beta = \frac{R^3}{R^3 - sR X_c^2} = \frac{R^3}{R^3 - sR(6R^2)} = -\frac{1}{29}$$

## Summary

RC - phase-shift oscillator

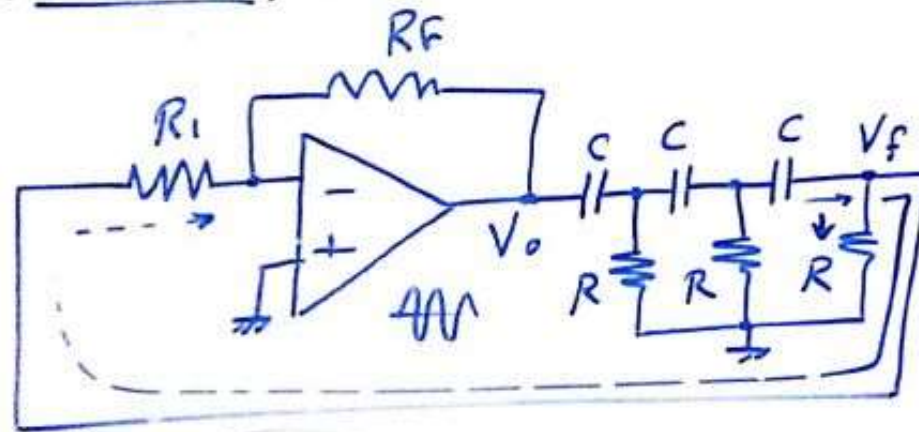

\*  $f_o = \frac{1}{2\pi\sqrt{6}RC}$  → Oscillation Frequency

\* Condition

$\frac{R_F}{R_1} = 29$ ,  $R_1 \gg R$   
 $\boxed{R_1 = 10R}$

## Example

Design RC-phase shift oscillator that generates a signal of 10 kHz frequency.

Sol.

$$* f_o = \frac{1}{2\pi\sqrt{6} RC}$$

Let  $C = 0.01 \text{ MF}$

$$10 \times 10^3 = \frac{1}{2\pi\sqrt{6} R \times 0.01 \times 10^{-6}}$$

$$R = \frac{1}{10^4 \times 2\pi \times \sqrt{6} \times 0.01 \times 10^{-6}}$$

$$R = 649.75 \Omega$$

$$* R_1 = 10R$$

$$R_1 = 6497.5 \Omega$$

$$R_1 = 6.4975 \text{ k}\Omega$$

$$\frac{R_F}{R_1} = 29$$

$$\therefore R_F = 29 R_1$$

$$R_F = 29 \times 6.4975$$

$$R_F = 188.43 \text{ k}\Omega$$

# RC Phase-Shift Oscillator

## Advantages

The advantages of R-C phase shift oscillator are,

1. The circuit is simple to design.
2. Can produce output over audio frequency range.
3. Produces sinusoidal output waveform.
4. It is a fixed frequency oscillator.

## Disadvantages

By changing the values of R and C, the frequency of the oscillator can be changed. But the values of R and C of all three sections must be changed simultaneously to satisfy the oscillating conditions. But this is practically impossible. Hence the phase shift oscillator is considered as a fixed frequency oscillator, for all practical purposes.

And the frequency stability is poor due to the changes in the values of various components, due to effect of temperature, aging etc.

