

Current sources

11

Introduction :-



Active Load :-

$$* V_o = (-g_m V_{\pi}) R_L$$

$$* V_{in} = V_{\pi}$$

\therefore Voltage gain is

$$A_v = \frac{V_o}{V_{in}} = -g_m R_L$$

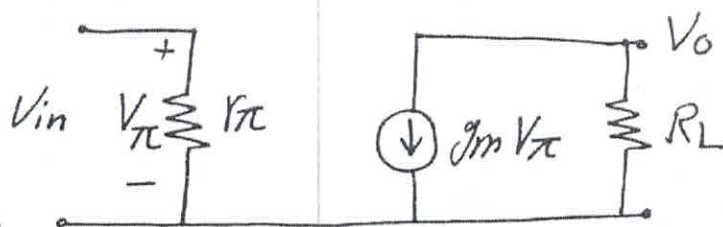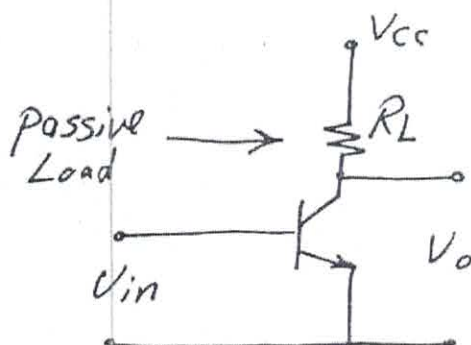

* To increase the voltage gain, we have to increase R_L .

Disadvantages of increasing R_L :-


- 1] Increase power dissipation
- 2] Large chip area required for R_L .
- 3] Unstable Q-point.

So, R_L is replaced by an Active Load


Diode Connected Transistor:-

2

NPN

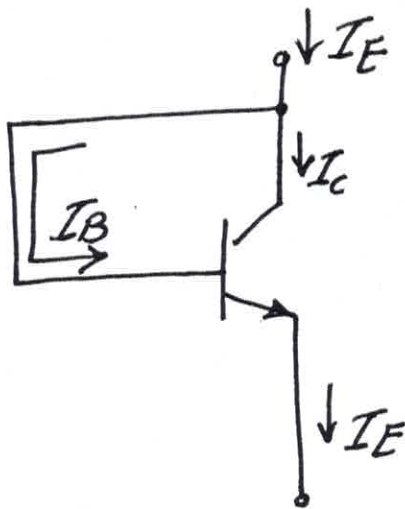

Active Load (NPN):-

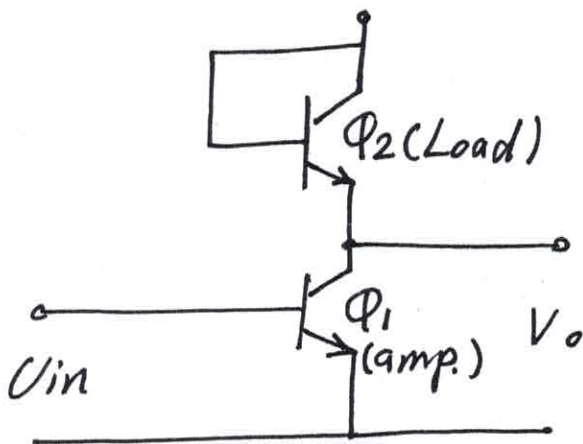

$$* R_{out}(\Phi_2) = \frac{r_\pi}{1+\beta} = R_L$$


$$* A_v = -g_m R_L$$

$$= -g_m r_\pi \frac{1}{1+\beta}$$


$$= -\frac{\beta}{1+\beta}$$

$$\boxed{A_v \approx -1} \text{ Low gain}$$

PNP

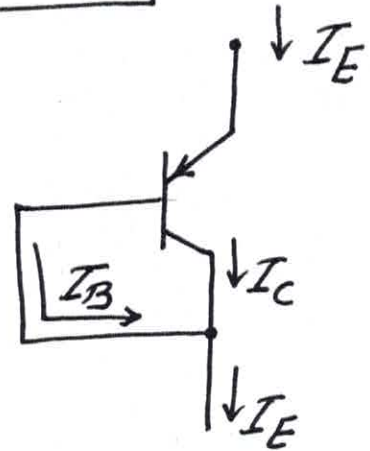

Active Load (PNP)

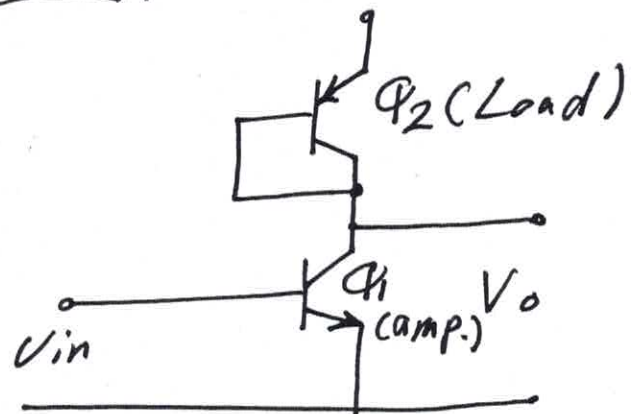

$$* R_{out}(\Phi_2) \approx r_o = \frac{V_A}{I_C} =$$

$$* \boxed{A_v = -g_m r_o}$$

$$r_o = 40 \text{ K}\Omega \rightarrow 100 \text{ K}\Omega$$

\therefore higher gain than (NPN)


where $r_o = \frac{V_A}{I_C}$

$V_A = \text{early voltage}$

Current - Sources :-

C.S \Rightarrow used For biasing amplifiers with active Load with Constant current and High output resistance.

[1] Current mirror :-

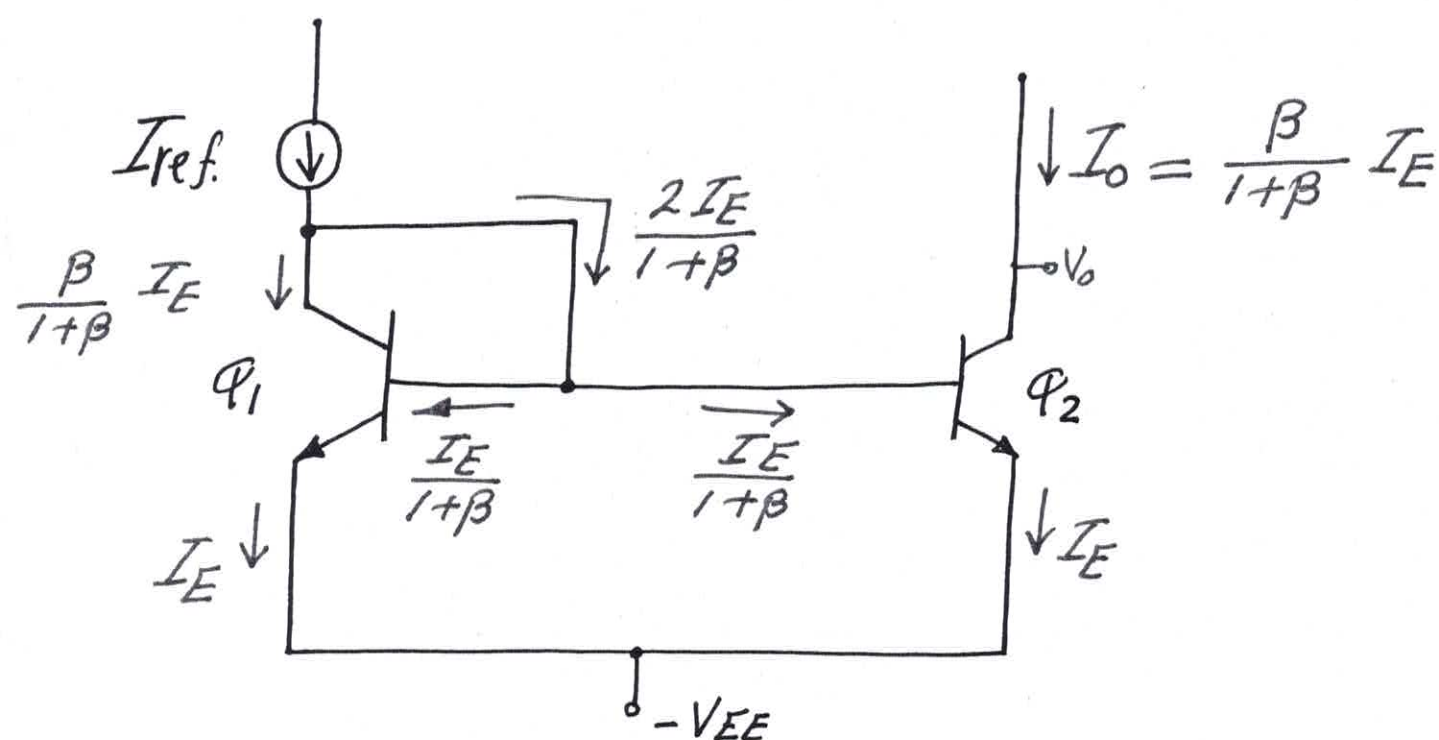

* Q_1 and Q_2 are matched (identical) and operating in the active mode.

Since $I_C = I_S e^{\frac{V_{BE}}{V_T}}$

and $V_{BE1} = V_{BE2} \therefore I_{C1} = I_{C2}$

$$\therefore V_{BE1} = V_{BE2}$$

$$* I_{B1} = I_{B2} = \frac{I_E}{1+\beta}$$

$$* I_{C1} = I_{C2} = \frac{\beta}{1+\beta} I_E$$

$$* \boxed{I_O = \frac{\beta}{1+\beta} I_E} \quad [1]$$

$$\text{but } I_{ref} = \frac{\beta}{1+\beta} I_E + \frac{2}{1+\beta} I_E$$

$$\boxed{I_{ref} = \left(\frac{\beta+2}{1+\beta} \right) I_E} \quad [2]$$

$$[1] \div [2] \therefore \frac{I_O}{I_{ref}} = \frac{\beta}{1+\beta} \cdot \frac{1+\beta}{\beta+2}$$

$$\frac{I_O}{I_{ref}} = \frac{\beta}{\beta+2} = \frac{1}{1+\frac{2}{\beta}}$$

$$\therefore \boxed{I_O = \frac{I_{ref}}{1+\frac{2}{\beta}}}$$


if β Large

$$\boxed{I_O \approx I_{ref}}$$

* With Early Effect (V_A)

$$\boxed{I_O = \frac{I_{ref}}{1+\frac{2}{\beta}} \left(1 + \frac{V_O + V_{EE} - V_{BE}}{V_A} \right)} \Rightarrow$$

Simple (mirror) Current Source :-

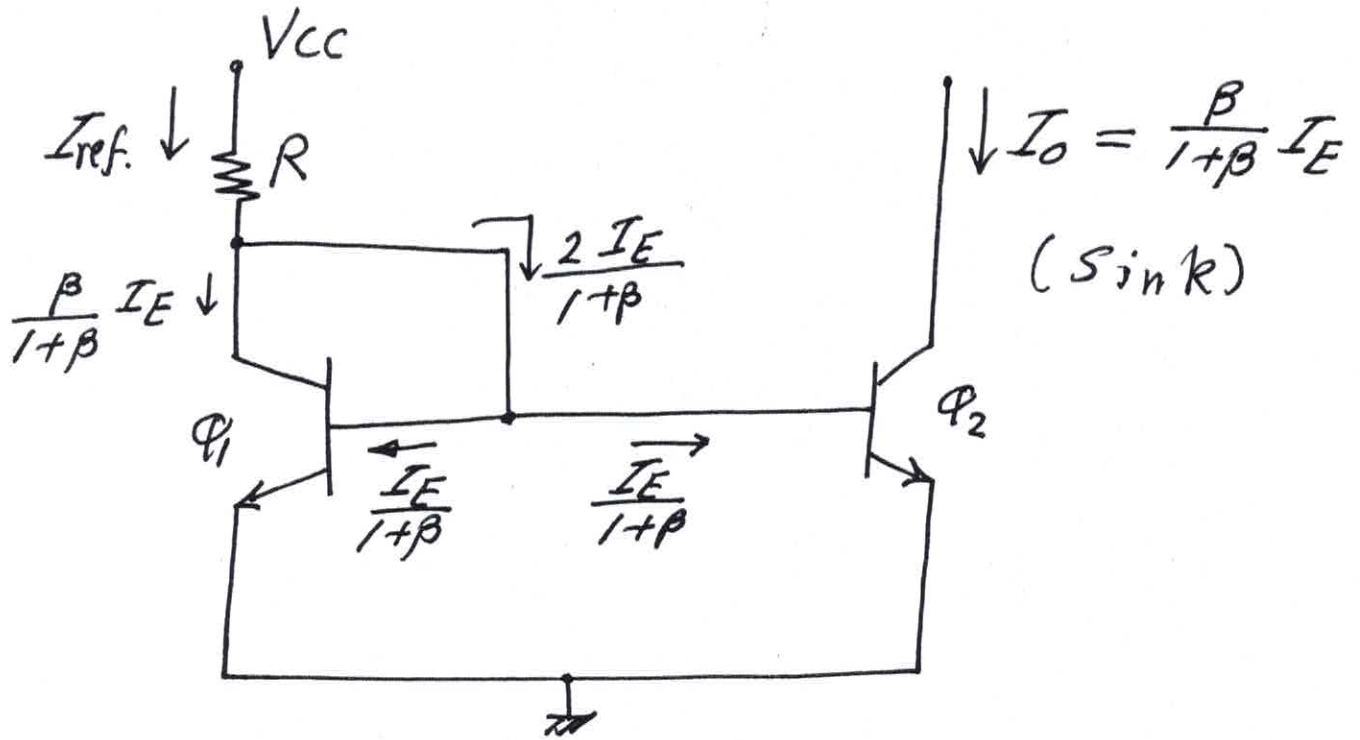


$$* \quad I_O = \frac{I_{ref}}{1 + \frac{2}{\beta}} = \frac{1}{1 + \frac{2}{\beta}} \frac{V_{CC} - V_{BE}}{R}$$

Disadvantages :-


- * Large chip area needed for R .
- * The dependence of I_O on the finite (β) of BJT.
- * The output resistance $r_o = \frac{V_A}{I_O}$ is limited by $40 \text{ k}\Omega \rightarrow 100 \text{ k}\Omega$
- * operating in the range of mA only.

Current Repeater (Multiple Current Source)

6

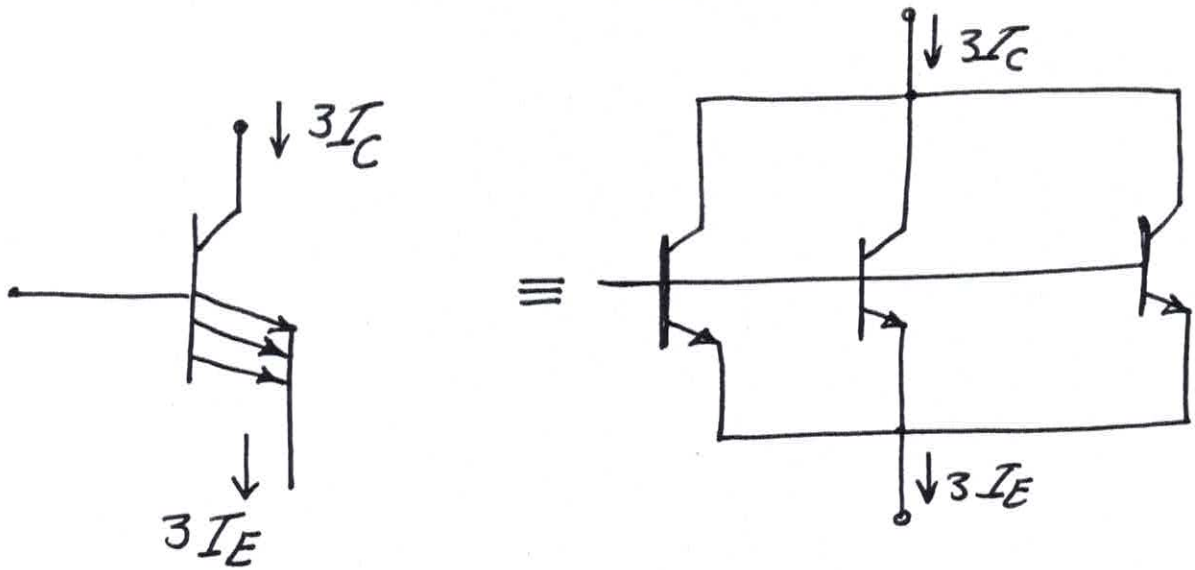


EX.

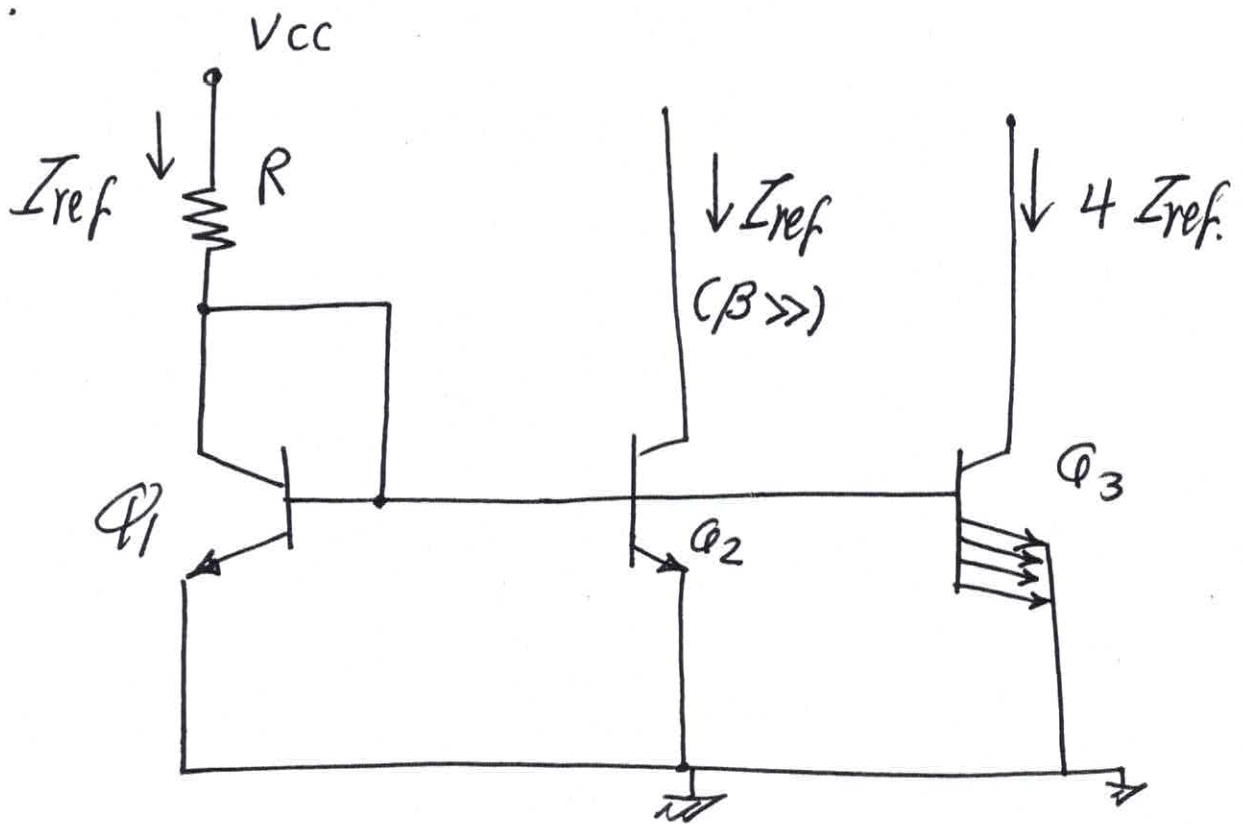

N-output Current Mirror:-

[7]

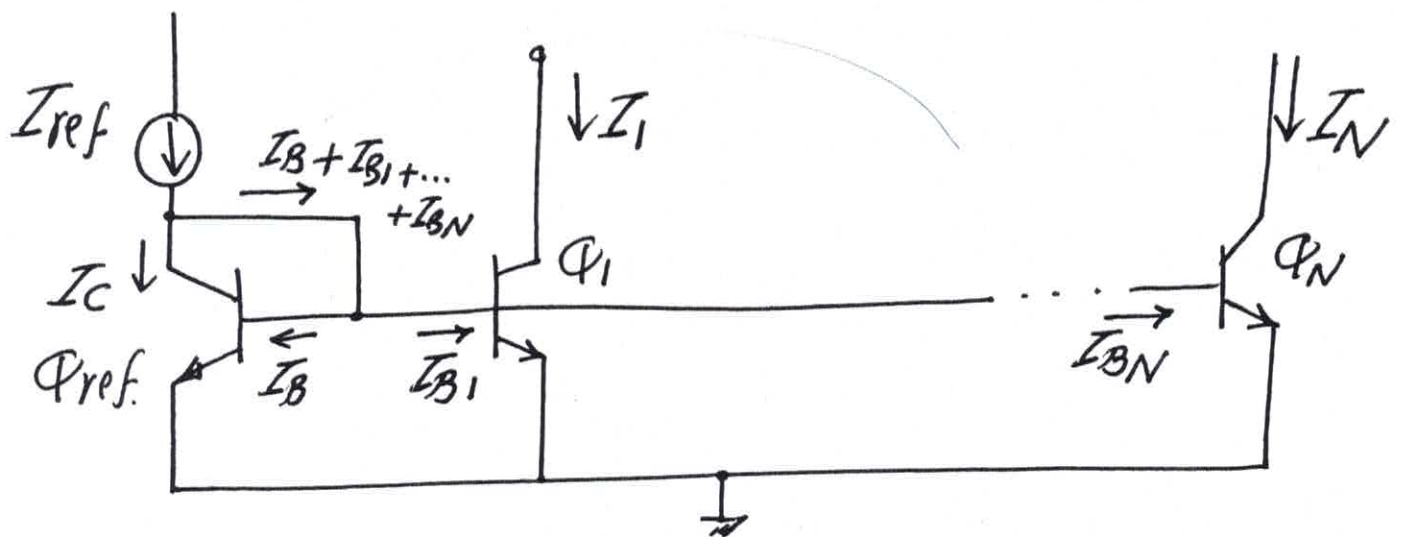

Q_1, Q_2, \dots, Q_N are matched (identical)

$$\therefore V_{BE} = V_{BE1} = V_{BE2} = \dots = V_{BEN}$$

$$\therefore I_C = I_{C1} = I_{C2} = \dots = I_N$$

$$I_B = I_{B1} = I_{B2} = \dots = I_{BN}$$

$$* I_{ref} = I_C + I_B + I_{B1} + I_{B2} + \dots + I_{BN}$$

$$I_{ref.} = I_C + (N+1) I_B$$


$$= I_C + (N+1) \frac{I_C}{\beta}$$

$$\therefore I_{ref} = \left[1 + \frac{N+1}{\beta} \right] I_C, \quad I_C = I_N$$

$$\therefore I_{ref} = \left[1 + \frac{N+1}{\beta} \right] I_N$$

$$\therefore I_N = \frac{I_{ref}}{1 + \frac{N+1}{\beta}} = I_1 = I_2 = \dots$$

Current Source with PNP Transistor :-

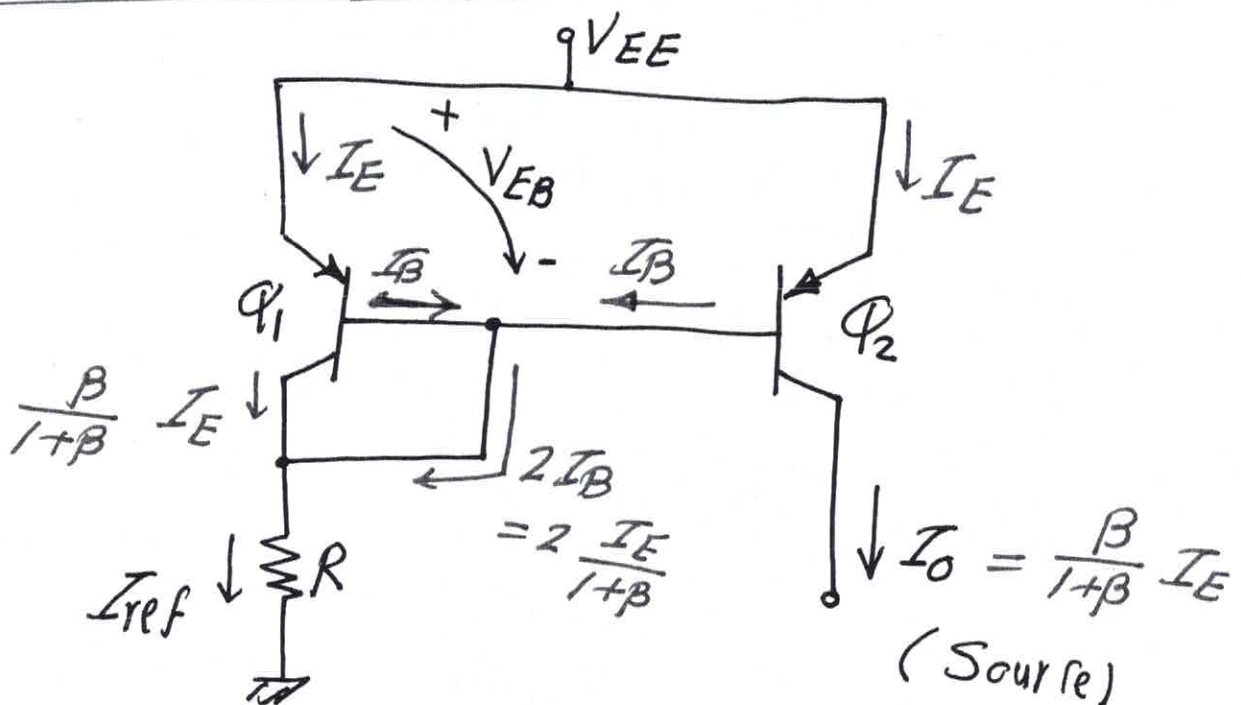


$$I_o = \frac{\beta}{1+\beta} I_E, \quad I_{ref} = \frac{2+\beta}{1+\beta} I_E$$

$$\therefore I_o = \frac{I_{ref}}{1 + \frac{2}{\beta}}, \quad I_{ref} = \frac{V_{EE} - V_{EB}}{R}$$

or

$$I_o = \frac{1}{1 + \frac{2}{\beta}} \frac{V_{EE} - V_{EB}}{R}$$

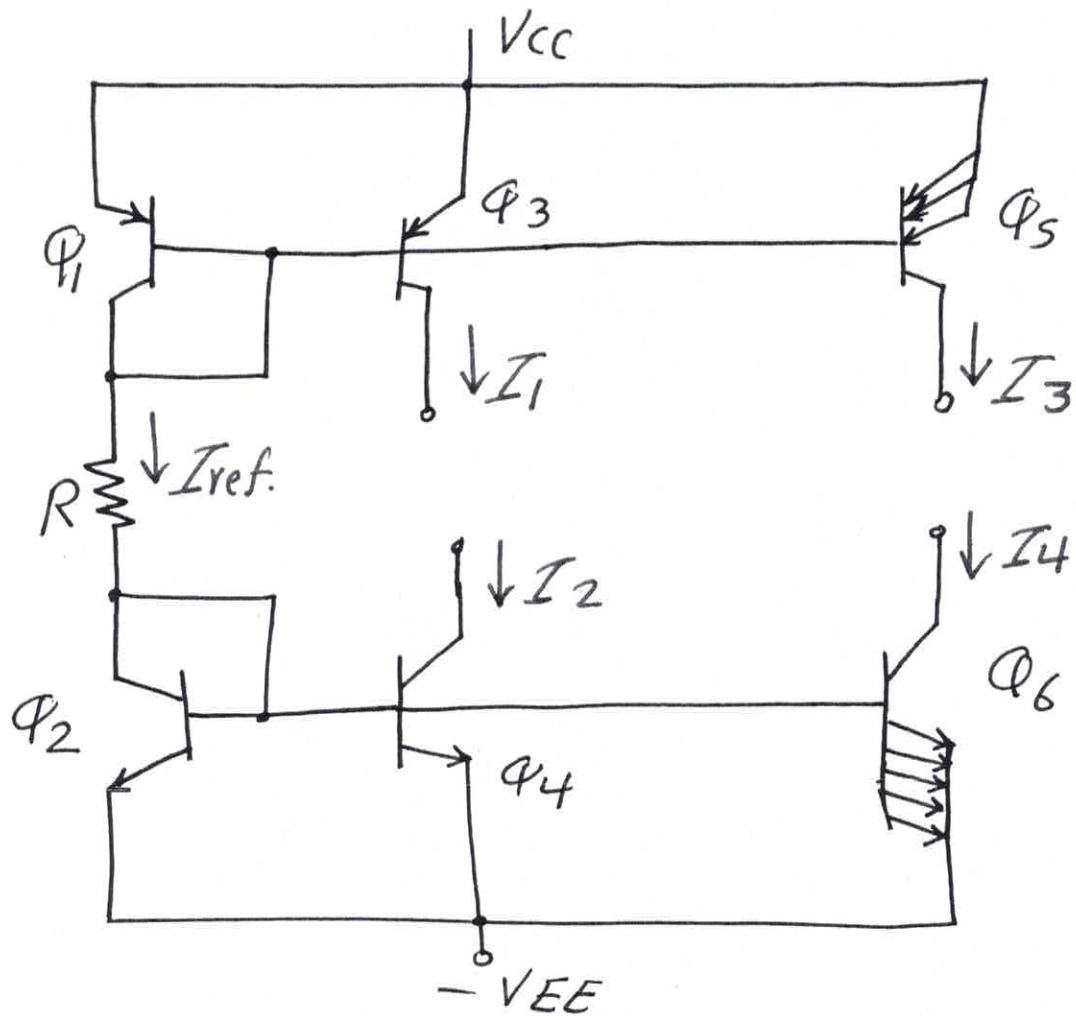Generation of a number of constant currents:- [9]



$$* I_1 = I_{ref} \quad (\beta \gg 1)$$

$$* I_2 = I_{ref}$$

$$* I_3 = 3I_1 = 3I_{ref}$$

$$* I_4 = 5I_2 = 5I_{ref}$$

$$* I_{ref} = \frac{V_{CC} + V_{EE} - V_{BE2} - V_{BE1}}{R}$$

Improved Current Source Circuit :-

[10]


Performance Parameters needed:-

- * I_0 independent of β
- * r_o (output resistance) is very high.

To obtain these parameters (improve C.S),
the following Circuits will be used:-

- [1] Current mirror with base-current Compensation.
- [2] Wilson Current Source.
- [3] Widler Current Source.

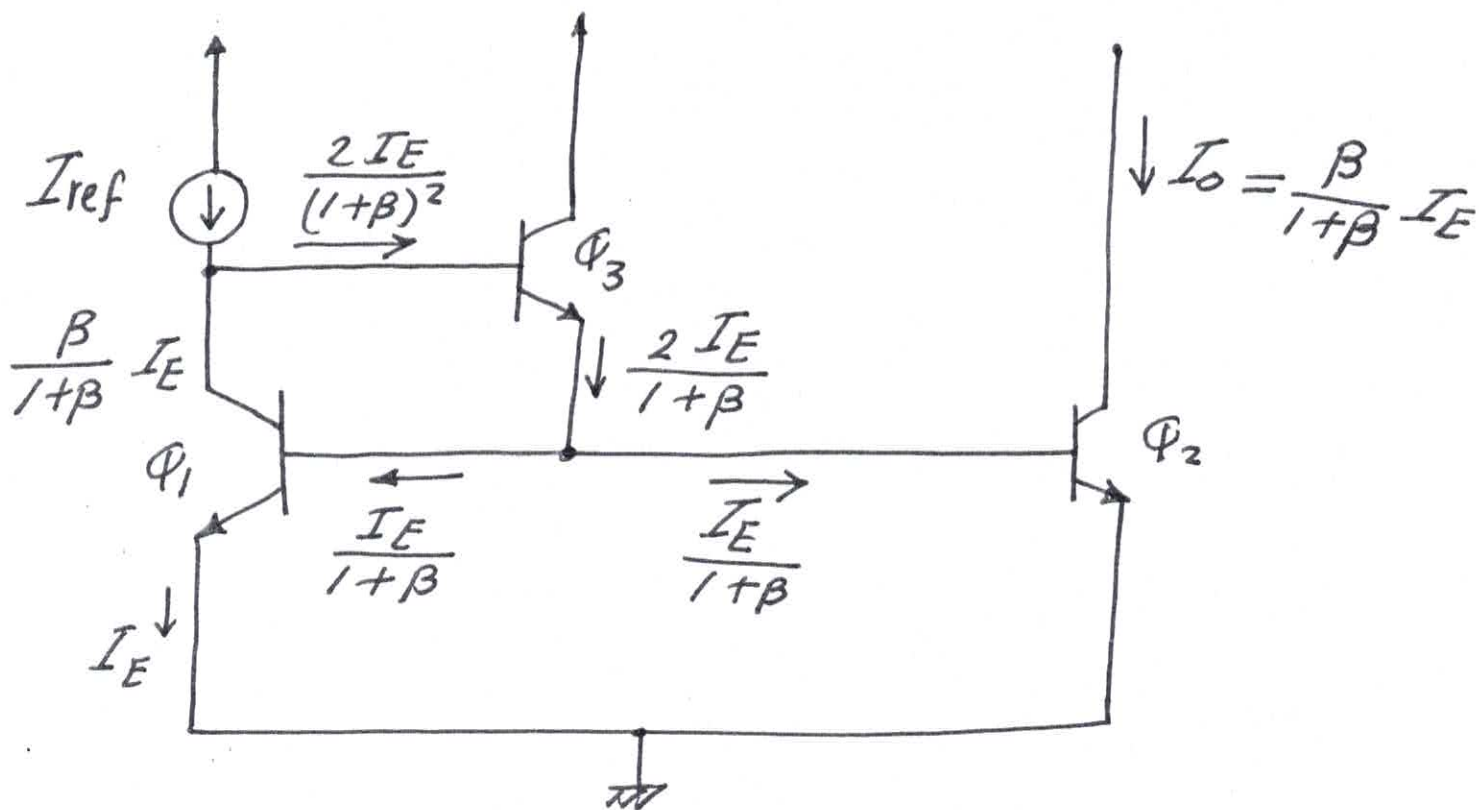1] Current mirror with base-current Compensation:-



$$* I_{ref} = \frac{\beta}{1+\beta} I_E + \frac{2 I_E}{(1+\beta)^2}$$

$$I_{ref} = \left[\frac{\beta}{1+\beta} + \frac{2}{(1+\beta)^2} \right] I_E \rightarrow [1]$$


$$* I_O = \frac{\beta}{1+\beta} I_E \rightarrow [2]$$

$$[2] \div [1] \quad \therefore \quad \frac{I_O}{I_{ref}} = \frac{\frac{\beta}{1+\beta}}{\frac{\beta}{1+\beta} + \frac{2}{(1+\beta)^2}}$$

$$\frac{I_o}{I_{ref}} = \frac{\beta}{\beta + \frac{2}{1+\beta}} = \frac{1}{1 + \frac{2}{\beta + \beta^2}}$$

$$\frac{I_o}{I_{ref}} = \frac{1}{1 + \frac{2}{\beta^2 + \beta}} \approx \frac{1}{1 + \frac{2}{\beta^2}}$$
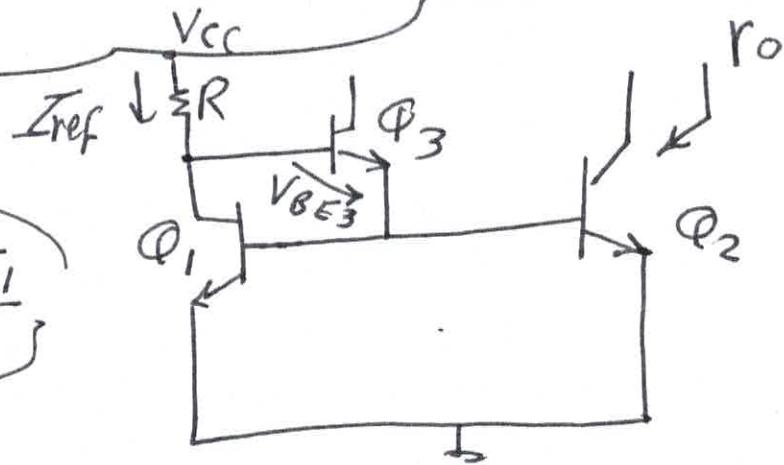
$$I_{ref} = \frac{V_{CC} - V_{BE3} - V_{BE1}}{R}$$



$$\therefore I_o = \frac{1}{1 + \frac{2}{\beta^2}} \cdot \frac{V_{CC} - V_{BE3} - V_{BE1}}{R}$$

Then, the error due to finite (β) has been reduced from $(\frac{2}{\beta})$ to $(\frac{2}{\beta^2})$.

Note $\frac{I_o}{I_{ref}} = \frac{1}{1 + \frac{2}{\beta^2}} \approx 1$


$$r_o = r_{o2} = \frac{V_A}{I_o}$$

[2] Wilson Current Source :-

[13]

Advantages:-

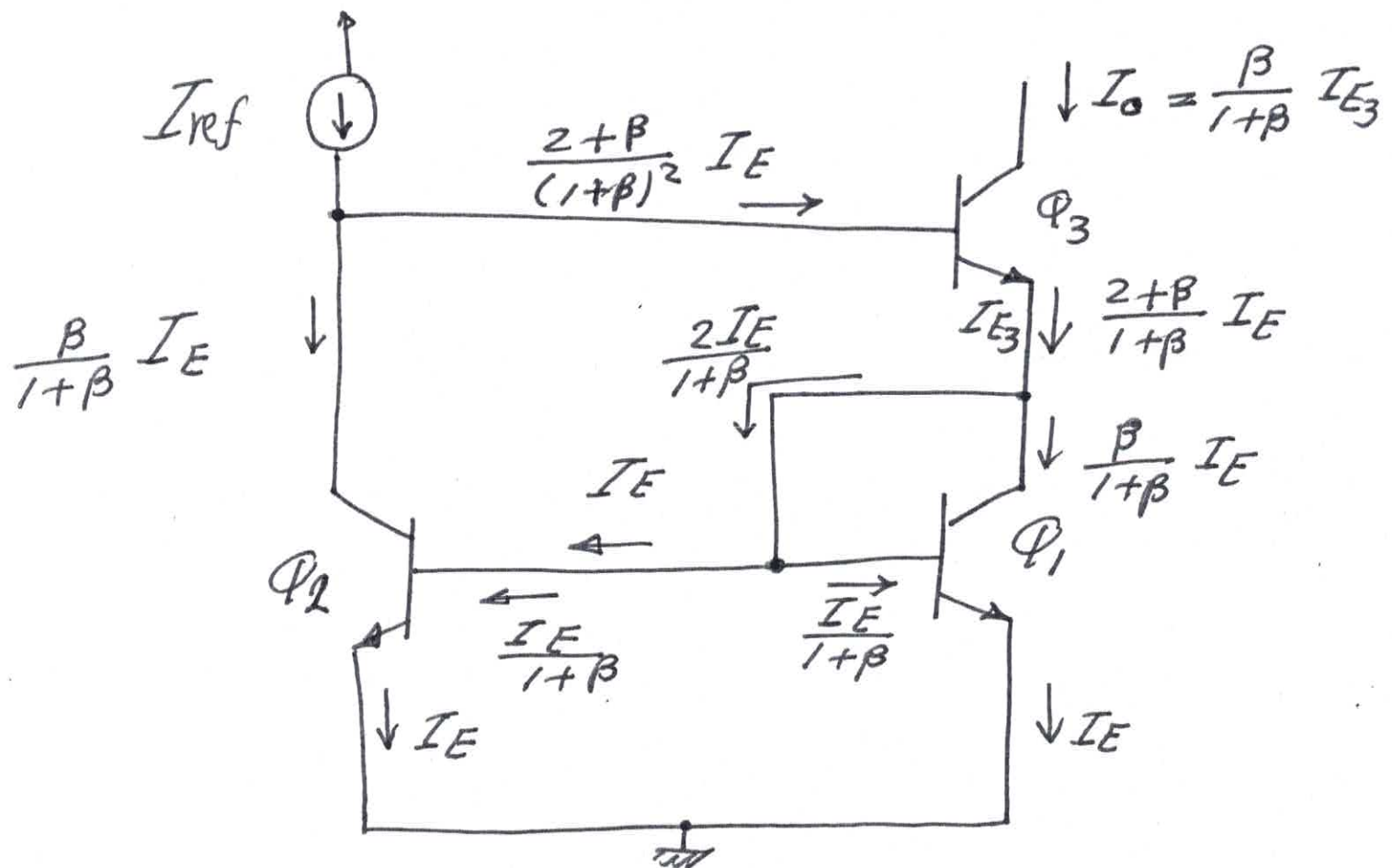- [1] Base-current Compensation.
- [2] Increasing the output resistance.



$$* I_O = \left(\frac{\beta}{1+\beta} \right) I_{E3} = \frac{\beta}{1+\beta} \left(\frac{2+\beta}{1+\beta} I_E \right)$$

$$I_O = \frac{\beta^2 + 2\beta}{(1+\beta)^2} I_E \rightarrow [1]$$

$$* I_{ref} = \frac{\beta}{1+\beta} I_E + \frac{2+\beta}{(1+\beta)^2} I_E$$

$$I_{ref} = \left[\frac{\beta}{1+\beta} + \frac{2+\beta}{(1+\beta)^2} \right] I_E \rightarrow [2]$$

$$\begin{aligned} \text{①} \div \text{②} \quad \therefore \frac{I_o}{I_{ref}} &= \frac{\frac{\beta^2 + 2\beta}{(1+\beta)^2}}{\frac{\beta}{1+\beta} + \frac{2+\beta}{(1+\beta)^2}} \\ &= \frac{\beta^2 + 2\beta}{\beta(1+\beta) + 2 + \beta} = \frac{(\beta^2 + 2\beta)}{(\beta^2 + 2\beta) + 2} \end{aligned}$$


$$\frac{I_o}{I_{ref}} = \frac{1}{1 + \frac{2}{\beta^2 + 2\beta}}$$

$$\therefore \boxed{I_o = \frac{I_{ref}}{1 + \frac{2}{\beta^2 + 2\beta}}}$$

The error due to finite (β) has been reduced from $(\frac{2}{\beta})$ to $(\frac{2}{\beta^2 + 2\beta})$

$I_F (I_{ref})$ is drawn from (V_{CC}) supply

15

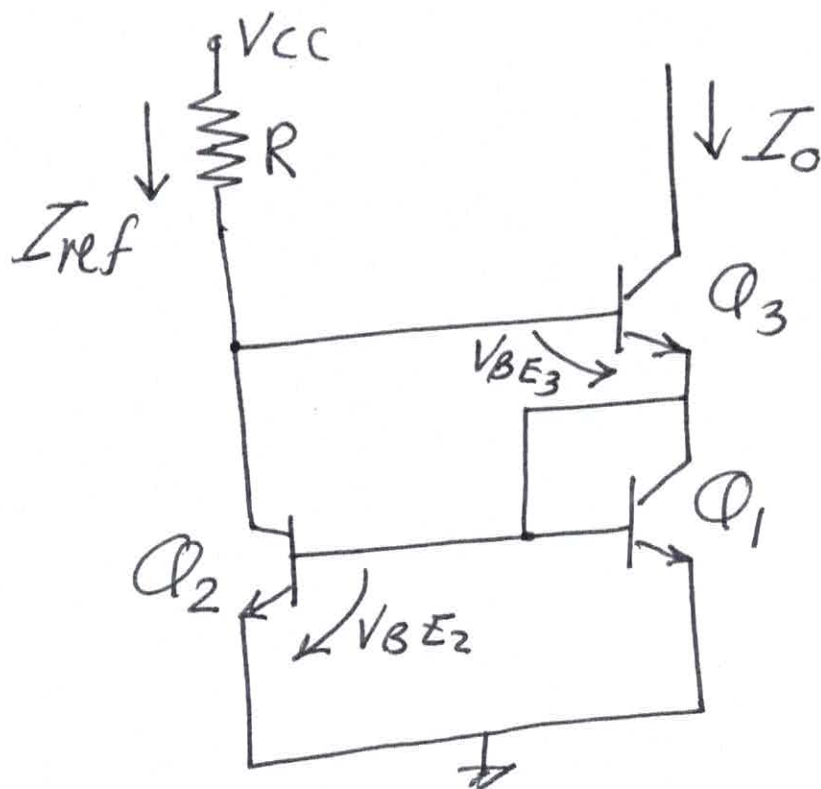

$$I_{ref} = \frac{V_{CC} - V_{BE3} - V_{BE2}}{R}$$

$$\therefore I_o = \frac{1}{1 + \frac{2}{\beta^2 + 2\beta}} \cdot \frac{V_{CC} - V_{BE3} - V_{BE2}}{R}$$



and

$$R_o = \frac{\beta r_o}{2} = \frac{\beta r_{o3}}{2}$$

$$r_{o3} = \frac{V_A}{I_o}$$

Wilson Current - Source output Resistance:-

16

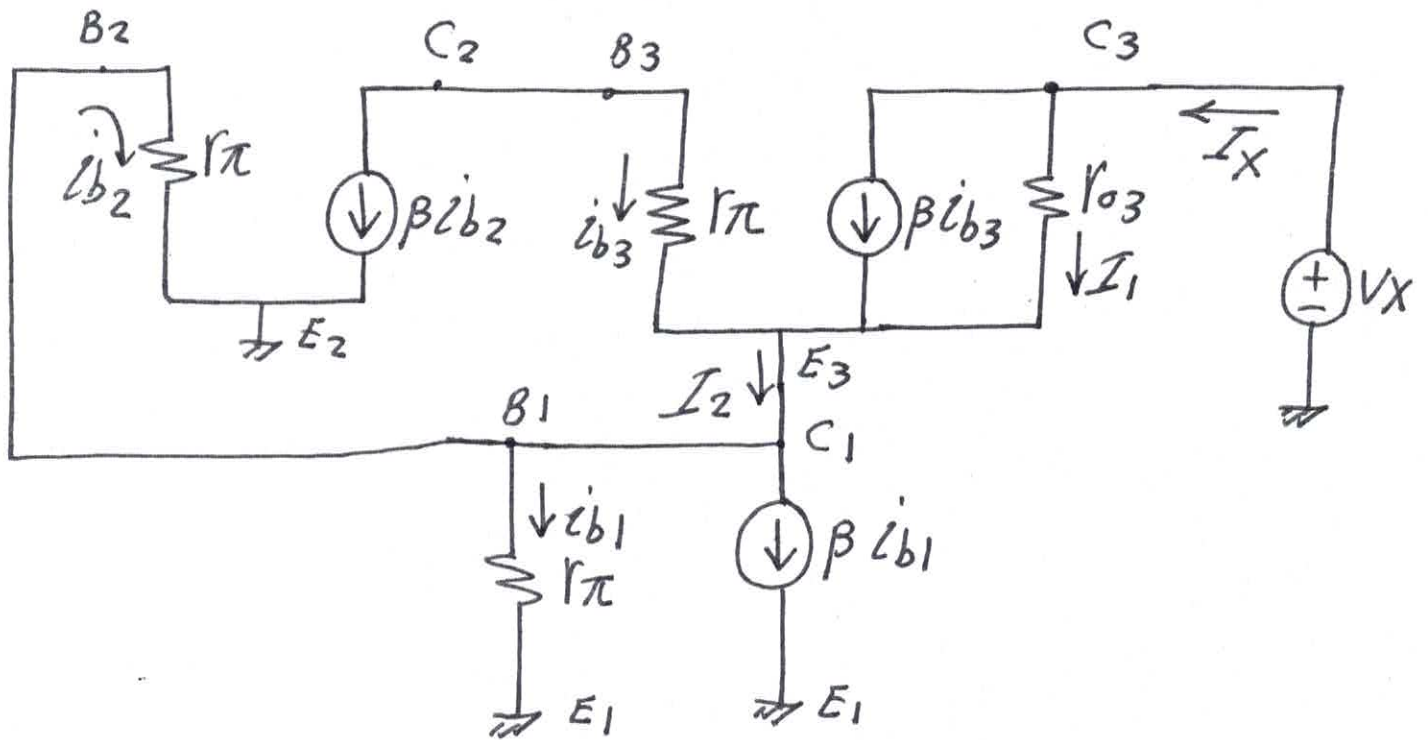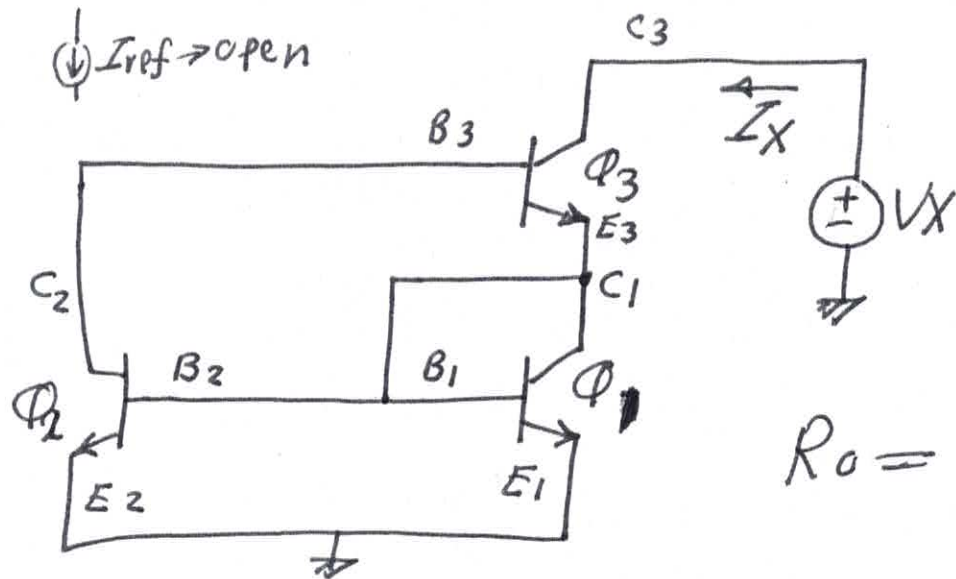

Q_1 and Q_2 are identical.

$$\therefore i_{b1} = i_{b2} = i_b$$

* $\beta i_{b2} = -i_{b3}$

$$i_{b3} = -\beta i_{b2} = -\beta i_b$$

$$* I_2 = \beta \dot{I}_{b1} + \dot{I}_{b1} + \dot{I}_{b2} \quad \boxed{17}$$

$$= (1+\beta) \dot{I}_{b1} + \dot{I}_{b2}, \quad \dot{I}_{b1} = \dot{I}_{b2} = \dot{I}_b$$

$$\boxed{I_2 = [2 + \beta] \dot{I}_b}$$

$$* I_1 + \beta \dot{I}_{b3} + \dot{I}_{b3} = I_2$$

$$I_1 + (1+\beta)(-\beta \dot{I}_b) = I_2$$

$$I_1 = \beta(1+\beta)\dot{I}_b + \underbrace{(2+\beta)}_{\downarrow} \dot{I}_b$$

$$I_1 = [\beta + \beta^2 + 2 + \beta] \dot{I}_b$$

$$\boxed{I_1 = [\beta^2 + 2\beta + 2] \dot{I}_b}$$

$$* I_X = I_1 + \beta \dot{I}_{b3} = I_1 + \beta(-\beta \dot{I}_b)$$

$$I_X = I_1 - \beta^2 \dot{I}_b = (\beta^2 + 2\beta + 2) \dot{I}_b - \beta^2 \dot{I}_b$$

$$\boxed{I_X = (2 + 2\beta) \dot{I}_b}$$

$$* V_X = V_{r03} + V_{B1} = I_1 r_{03} - \dot{I}_{b1} r_\pi$$

$$V_X = (\beta^2 + 2\beta + 2) \dot{I}_b r_{03} - \dot{I}_b r_\pi$$

$$\boxed{V_X = [(\beta^2 + 2\beta + 2) r_{03} - r_\pi] \dot{I}_b}$$

$$\therefore R_o = \frac{V_X}{I_X} = \frac{(\beta^2 + 2\beta + 2)r_{o3} - r_\pi}{2 + 2\beta}$$

$$(\beta^2 + 2\beta + 2)r_{o3} \gg r_\pi$$

$$R_o \approx \frac{\beta^2 + 2\beta + 2}{2 + 2\beta} r_{o3}$$

$$\beta^2 \gg 2\beta + 2$$

and $2\beta \gg 2$

$$\therefore R_o \approx \frac{\beta^2}{2\beta} r_{o3}$$

$$R_o \approx \frac{\beta r_{o3}}{2} = \frac{\beta r_o}{2}$$


For example, if $\beta = 100$, $r_o = 50 \text{ k}\Omega$

then, $R_o = 2.5 \text{ M}\Omega$

\therefore wilson c.s output resistance is very large

[3] Widler Current Source :-

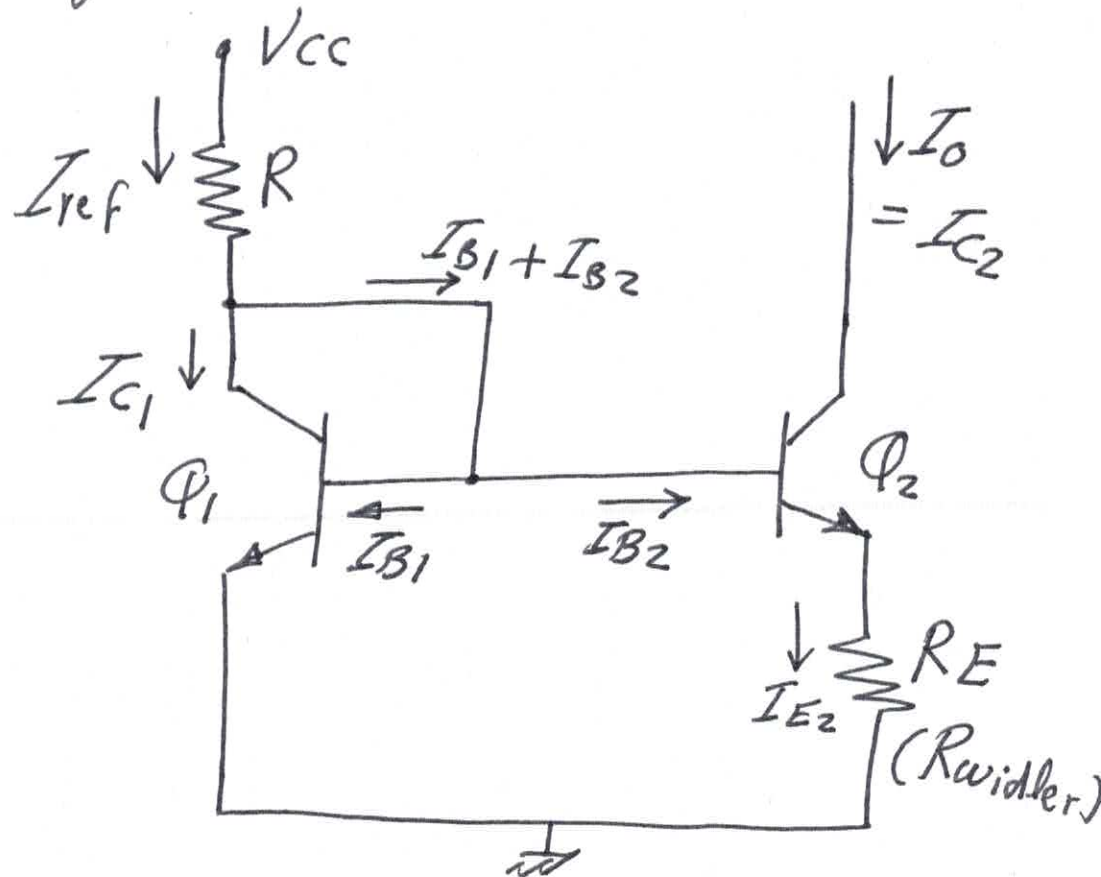Advantage Very high o/p Resistance (4-6 M Ω)



Q_1 and Q_2 are matched (identical)
but $V_{BE1} \neq V_{BE2}$

$$I_{ref} = I_{C1} + I_{B1} + I_{B2}$$

$$I_{ref} = I_{C1} + \frac{I_{C1}}{\beta} + \frac{I_{C2}}{\beta}$$

$$\text{but } V_{BE1} > V_{BE2}$$

$$\therefore I_{C1} > I_{C2}$$

$$\therefore \frac{I_{C1}}{\beta} > \frac{I_{C2}}{\beta}, \text{ neglect } \frac{I_{C2}}{\beta}$$

20

$$\therefore I_{ref.} \cong I_{C1} + \frac{I_{C1}}{\beta} = (1 + \frac{1}{\beta}) I_{C1}$$

$$I_{ref} \cong \frac{1+\beta}{\beta} I_{C1}$$

$$\therefore I_{C1} = \frac{\beta}{1+\beta} I_{ref.} = \frac{\beta}{1+\beta} \left(\frac{V_{CC} - V_{BE1}}{R} \right)$$

$$I_{C1} \cong \frac{V_{CC} - V_{BE1}}{R} \quad [1]$$

$$* V_{BE1} = V_{BE2} + I_{E2} R_E$$

$$\therefore \underbrace{V_{BE1} - V_{BE2}}_{\downarrow} = (I_{B2} + I_{C2}) R_E$$

$$\Delta V_{BE} = \left(\frac{I_{C2}}{\beta} + I_{C2} \right) R_E = \left(\frac{1}{\beta} + 1 \right) I_{C2} R_E$$

$$\therefore \Delta V_{BE} \cong I_{C2} R_E \quad [2]$$

$$* \text{ But } I_{C1} = I_S e^{V_{BE1}/V_T}$$

$$I_{C2} = I_S e^{V_{BE2}/V_T}$$

$$\therefore \frac{I_{C1}}{I_{C2}} = e^{\frac{V_{BE1} - V_{BE2}}{V_T}}$$

21

$$\ln\left(\frac{I_{C1}}{I_{C2}}\right) = \frac{V_{BE1} - V_{BE2}}{V_T} = \frac{\Delta V_{BE}}{V_T}$$

$$\therefore \boxed{\Delta V_{BE} = V_T \ln\left(\frac{I_{C1}}{I_{C2}}\right)} \quad [3]$$

From [2], [3]

$$\therefore I_{C2} R_E = V_T \ln\left(\frac{I_{C1}}{I_{C2}}\right)$$

but $I_{C1} = I_{ref}$, $I_{C2} = I_O$

$$I_O R_E = V_T \ln\left(\frac{I_{ref}}{I_O}\right)$$

$$I_O = \frac{V_T}{R_E} \ln\left(\frac{I_{ref}}{I_O}\right) \quad \text{ie}$$

($I_O < I_{ref}$)

where: R_E is the Widler Resistance.

- * IF I_O given \rightarrow substitute to Find R_E
- * IF R_E given \rightarrow solve For I_O using trial and

Widder output Resistance (R_o) :-


22

$$R_o = (1 + g_m R_E) r_o$$

$$R_E = R_E \parallel r_\pi \Rightarrow$$

* Widder o/p Resistance is very high (4-6 M Ω)

prove

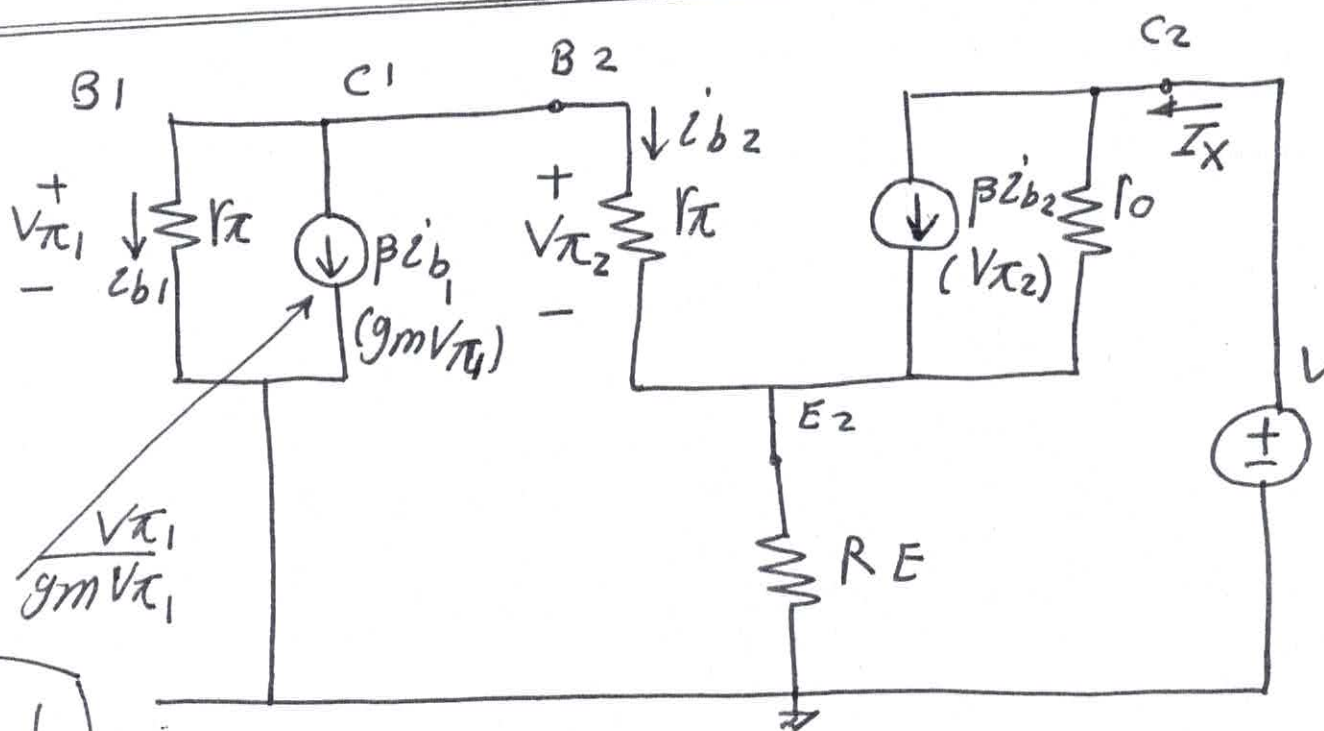

$$R = \frac{v_{\pi_1}}{g_m v_{\pi_1}}$$

$$R = \frac{1}{g_m}$$

$$* \frac{1}{g_m} \parallel r_\pi \cong \frac{1}{g_m} \quad \text{Since } \frac{1}{g_m} \ll r_\pi$$

$$* \frac{1}{g_m} + r_\pi \cong r_\pi$$