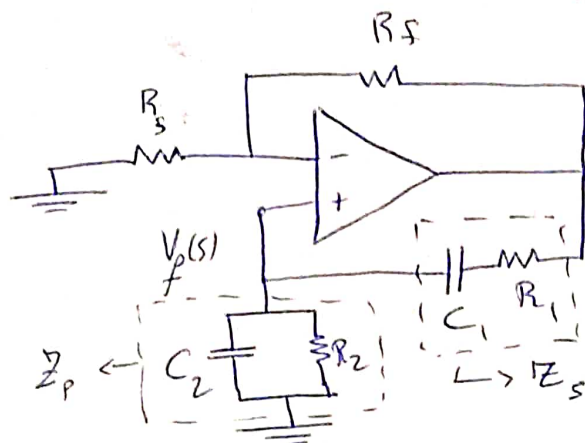


The Wien-Bridge oscillator :

1



non-inverting Amp. :

$$\Rightarrow A = 1 + \frac{R_F}{R}$$

$$\Rightarrow Z_S = R_1 - jX_{C_1}$$

$$Z_P = [R_2 // (-jX_{C_2})]$$

$$= \frac{-jR_2X_{C_2}}{R_2 - jX_{C_2}}$$

$$\Rightarrow V_f = \frac{V_o}{Z_P + Z_S} \cdot Z_P$$

$$\Rightarrow \beta = \frac{V_f}{V_o} = \frac{Z_P}{Z_P + Z_S}$$

$$\Rightarrow \beta = \frac{\frac{-jR_2X_{C_2}}{R_2 - jX_{C_2}}}{R_1 - jX_{C_1} + \frac{(-jR_2X_{C_2})}{R_2 - jX_{C_2}}}$$

$$= \frac{-jR_2X_{C_2}}{(R_1 - jX_{C_1})(R_2 - jX_{C_2}) - jR_2X_{C_2}}$$

$$= \frac{-jR_2X_{C_2}}{R_1R_2 - jR_1X_{C_2} - jR_2X_{C_1} - X_{C_1}X_{C_2} - jR_2X_{C_2}}$$

$$= \frac{R_2X_{C_2}}{j[R_1R_2 - jR_1X_{C_2} - jR_2X_{C_1} - X_{C_1}X_{C_2} - jR_2X_{C_2}]}$$

$$\Rightarrow \beta = \frac{R_2X_{C_2}}{R_1X_{C_2} + R_2X_{C_1} + R_2X_{C_2} + j(R_1R_2 - X_{C_1}X_{C_2})}$$

∴ $A \rightarrow$ pure Real & +ve \Rightarrow we need β to have 0 phase shift. \Rightarrow pure Real 2
 \hookrightarrow imaginary part = 0

$$\Rightarrow R_1 R_2 - X_{C_1} X_{C_2} = 0$$

$$\Rightarrow R_1 R_2 - \frac{1}{\omega_0 C_1} \cdot \frac{1}{\omega_0 C_2} = 0$$

$$\Rightarrow \frac{1}{\omega_0^2 C_1 C_2} = R_1 R_2$$

$$\Rightarrow \omega_0^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$\Rightarrow \boxed{\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}}$$

$$\text{if } R_1 = R_2 = R \text{ \& } C_1 = C_2 = C \Rightarrow \omega_0 = \frac{1}{RC}$$

$$\therefore |A\beta| = 1$$

at ω_0 :

$$\Rightarrow \beta = \frac{R_2 X_{C_2}}{R_1 X_{C_2} + R_2 X_{C_1} + R_2 X_{C_2}}$$

for $R_1 = R_2 = R$ & $C_1 = C_2 = C$


$$\Rightarrow \beta = \frac{\cancel{R} X_C}{3 \cancel{R} X_C} = \frac{1}{3}$$

$$\Rightarrow A = 3 \Rightarrow 1 + \frac{R_f}{R_3} = 3$$

$$\Rightarrow \boxed{\frac{R_f}{R_3} = 2}$$

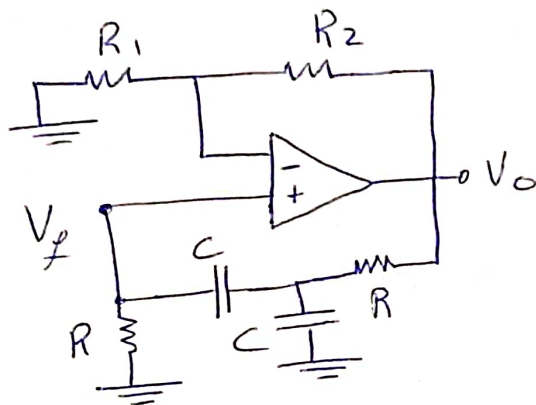1. [1] For the shown circuit :

- Find the frequency of oscillation.
- Define the condition of oscillation.
- What is the type of oscillator.




Sol:

$$A = 1 + \frac{R_2}{R_1} \quad (\text{non-inverting amplifier})$$

$$\beta = \frac{V_f}{V_o}$$

Applying KCL at node x:
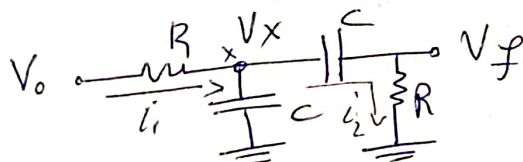
$$\Rightarrow \frac{V_o - V_x}{R} = \frac{V_x}{(-jX_c)} + \frac{V_x - V_f}{-jX_c}$$



$$\Rightarrow i_1 = \frac{V_o - V_x}{R}$$

$$\therefore \frac{V_f}{R} = \frac{V_x - V_f}{-jX_c} \Rightarrow \frac{V_x}{-jX_c} = V_f \left[-\frac{1}{jX_c} + \frac{1}{R} \right]$$

$$\Rightarrow V_x = V_f \left[1 - \frac{jX_c}{R} \right]$$

$$\frac{V_o}{R} = V_x \left[\frac{1}{R} + \frac{2}{-jX_c} \right] - \frac{V_f}{-jX_c}$$

$$\frac{V_o}{R} = V_f \left\{ \left[1 - \frac{jX_c}{R} \right] \left[\frac{1}{R} + \frac{2}{-jX_c} \right] - \frac{1}{-jX_c} \right\}$$

$$\Rightarrow \beta = \frac{V_f}{V_o} = \frac{1}{R \left[\left(\frac{1}{R} - \frac{2}{jX_c} - \frac{jX_c}{R^2} + \frac{2}{R} \right) + \frac{1}{jX_c} \right]}$$

$$\Rightarrow \beta = \frac{1}{R \left[\frac{3}{R} - \frac{1}{jX_c} - \frac{jX_c}{R^2} \right]} = \frac{1}{3 + j \left[\frac{R}{X_c} - \frac{X_c}{R} \right]}$$

* oscillation condition : $|A\beta| = 1$
 $\angle A\beta = 0$

$\because A \rightarrow$ pure Real
 $\rightarrow 0^\circ$ shift

$\Rightarrow \beta \rightarrow$ must be pure Real $\xrightarrow{\text{to achieve}} \angle A\beta = 0$

$$\Rightarrow \frac{R}{X_c} - \frac{X_c}{R} = 0$$

$$\Rightarrow \frac{R}{X_c} = \frac{X_c}{R}$$

$$\Rightarrow R(\omega_0) = \frac{1}{\omega_0 R C}$$

a) $\Rightarrow \omega_0^2 = \frac{1}{R^2 C^2} \Rightarrow \boxed{\omega_0 = \frac{1}{RC}}$


at $\omega_0 \Rightarrow \beta = \frac{1}{3} \because |A\beta| = 1$

$$\Rightarrow A = 3 \Rightarrow 1 + \frac{R_2}{R_1} = 3$$


b) $\Rightarrow \boxed{\frac{R_2}{R_1} = 2} \Rightarrow$ oscillation condition

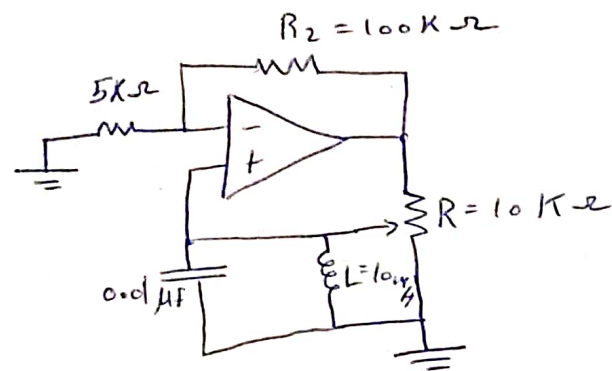c) \Rightarrow This is a wien Bridge oscillator

2] For the shown oscillator circuit, find the frequency of oscillation & min. value of R



Sol :

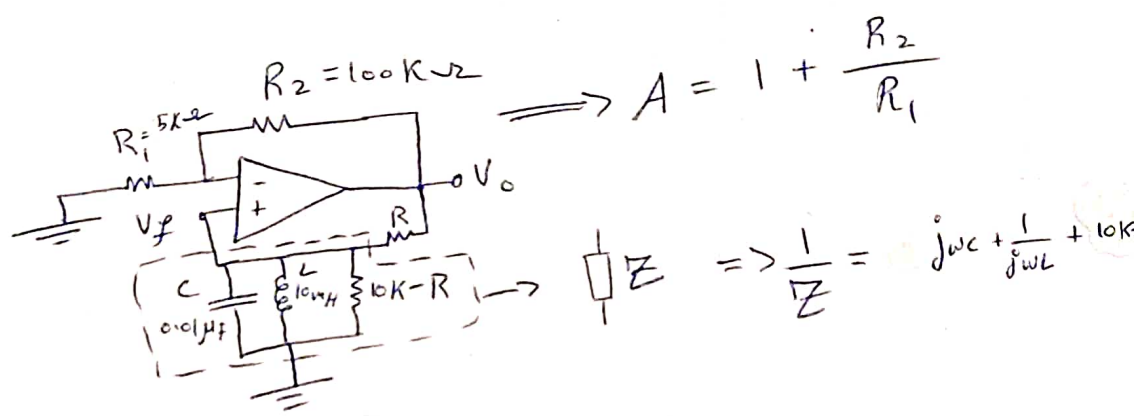

$$\Rightarrow \beta = \frac{V_f}{V_o} = \frac{Z}{R + Z}$$

\Rightarrow oscillation condition :

$$\therefore A\beta = 1$$

$$\Rightarrow A = \frac{1}{\beta} = \frac{R + Z}{Z}$$

$$\Rightarrow 1 + \frac{R_2}{R_1} = \frac{R}{Z} + 1$$

$$\Rightarrow \frac{R_2}{R_1} = \frac{R}{Z}$$

$$\Rightarrow \frac{R_2}{R_1} = R \left[j\omega C + \frac{1}{j\omega L} + \frac{1}{R} \right]$$

$$\frac{R_2}{R_1} = R \left[\frac{1}{10K - R} + j \left[\omega C - \frac{1}{\omega L} \right] \right]$$

* By comparing the imaginary parts in both sides \Rightarrow

$$\omega C - \frac{1}{\omega L} = 0 \Rightarrow \omega^2 = \frac{1}{LC} \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

$$\Rightarrow \boxed{\frac{R_2}{R_1} = \frac{R}{10K - R}} \Rightarrow \text{oscillation condition}$$

$$\therefore \frac{R_2}{R_1} = \frac{20}{\frac{100K}{5K_1}} = \frac{R}{10K - R}$$

61


$$\Rightarrow 20(10K - R) = R$$

$$\Rightarrow 200K - 20R = R$$

$$\Rightarrow \boxed{R = \frac{200K}{21} = 9.523 K \Omega} \rightarrow \text{min val. of } R \text{ to sustain oscillation}$$

3

7

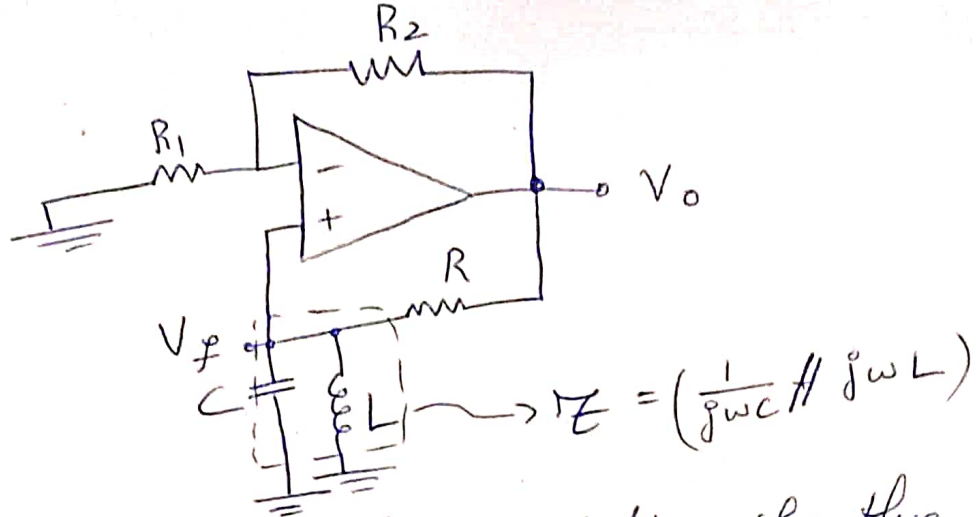

- Find the frequency of oscillation & the condition of oscillation.

sol:

$$\Rightarrow \frac{1}{Z} = \frac{1}{j\omega L} + j\omega C$$

$$A = 1 + \frac{R_2}{R_1}$$

$$B = \frac{V_p}{V_o} = \frac{Z}{R + Z}$$

\Rightarrow oscillation condition:

$$\because AB = 1$$

$$\Rightarrow A = \frac{1}{B} \Rightarrow 1 + \frac{R_2}{R_1} = \frac{R + Z}{Z}$$

$$\Rightarrow 1 + \frac{R_2}{R_1} = \frac{R}{Z} + 1$$

$$\Rightarrow \frac{R_2}{R_1} = R \left[j\omega C + \frac{1}{j\omega L} \right] = jR \left[\omega C - \frac{1}{\omega L} \right]$$

* equating: $R_L = R_C$ & $\text{imag} = \text{imag}$ for both sides

$$\Rightarrow \omega C - \frac{1}{\omega L} = 0 \Rightarrow \omega^2 = \frac{1}{LC}$$

$$\Rightarrow \omega_c = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow f_c = \frac{1}{2\pi\sqrt{LC}}$$

$$\Rightarrow \boxed{\frac{R_2}{R_1} = 0}$$

\Rightarrow This means we only need $A = 1$

\hookrightarrow since we don't have any resistance in the LC tank \rightarrow which is an ideal case