

Electronic Devices

Lecture 5 P-N Junction



Dr. Roaa Mubarak

Diode Models



The diode as a circuit elements:

- Ideal Diode Model
- Large Signal model
- Small Signal model

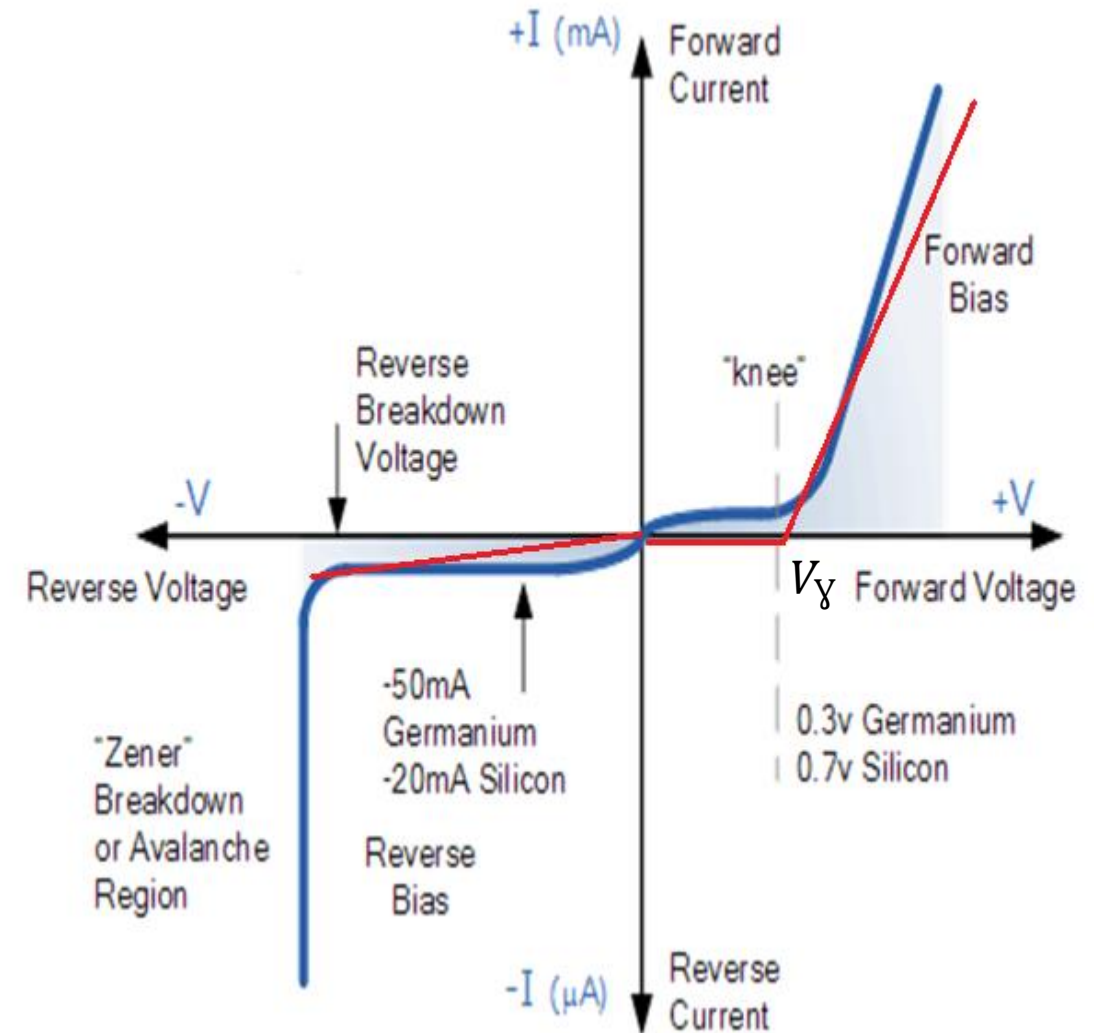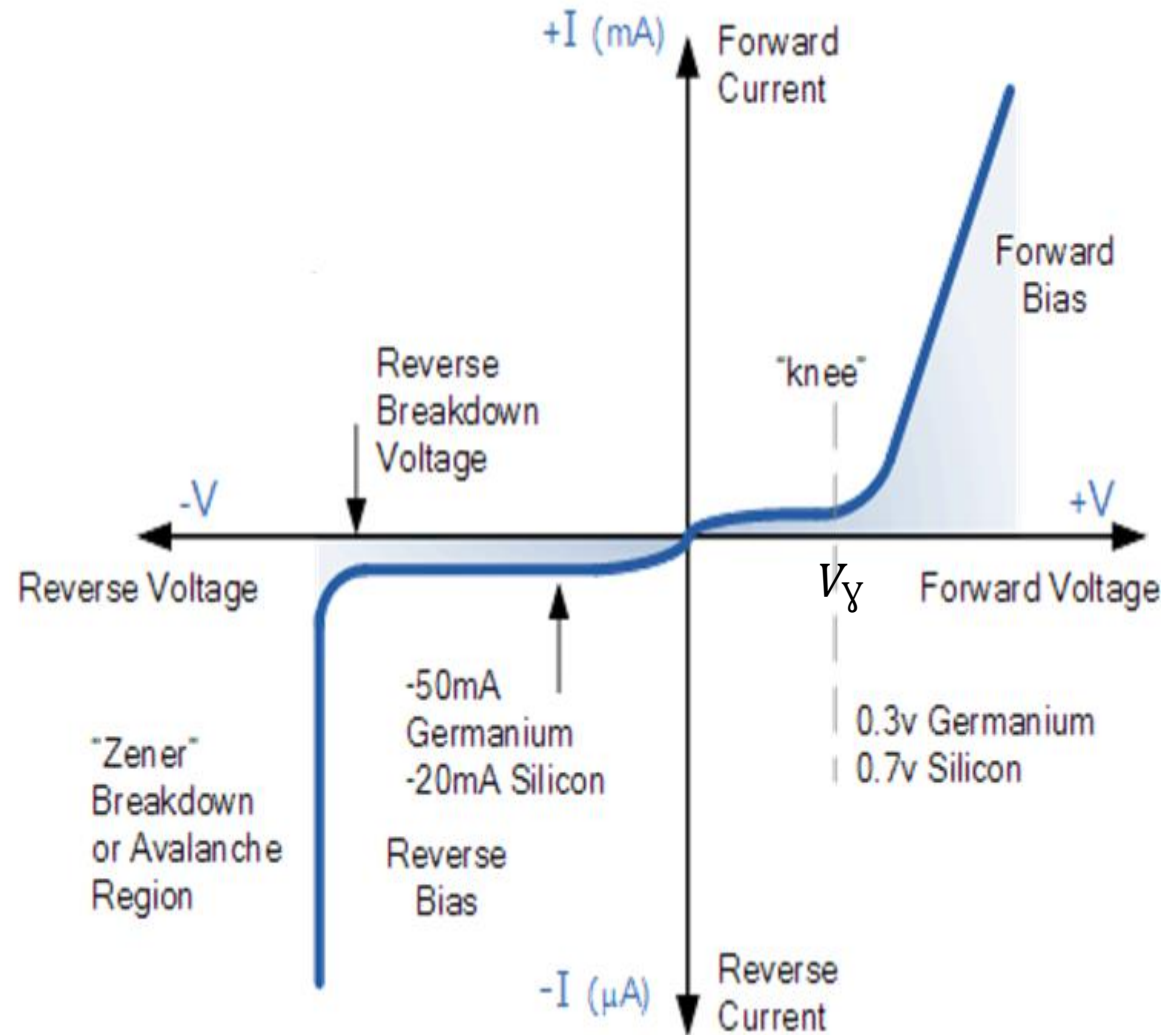Large Signal Diode Model “ Piecewise Linear Model”



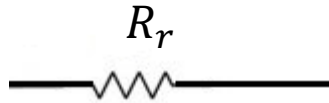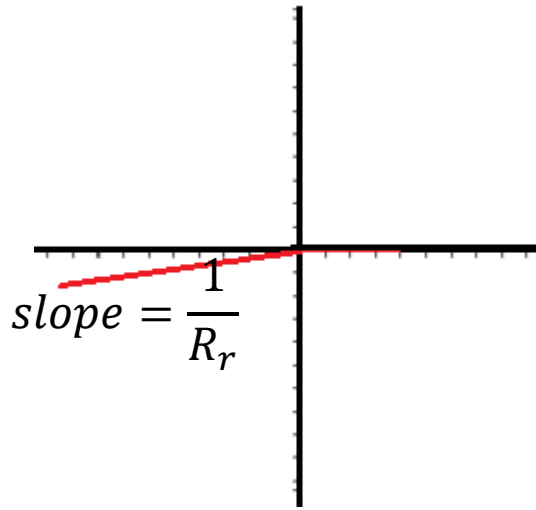Large Signal Diode Model “ Piecewise Linear Model”






Reverse biased

$$R_r \gg 100\text{K}\Omega \rightarrow \infty$$

Open Circuit

OFF

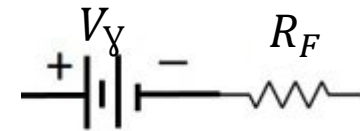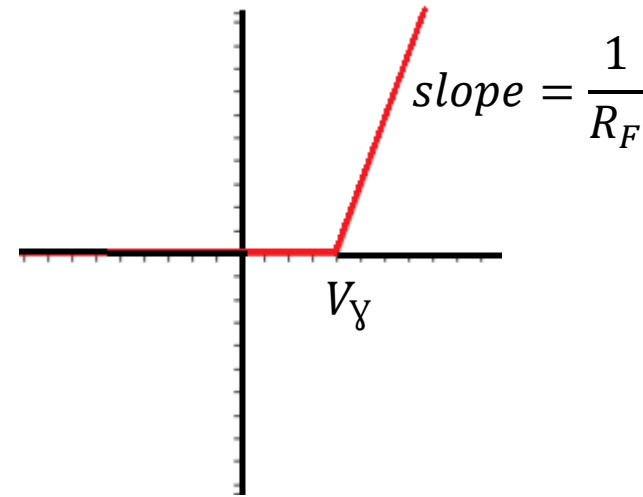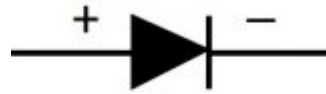

Forward biased

$$V_Y = 0.7\text{v Si or } = 0.3\text{v Ge}$$

$$R_F = 5 \rightarrow 50\Omega$$

ON



Example

- Determine the output voltage V_o in the circuit with silicon diodes have $R_F = 30\Omega$, $V_Y = 0.6\text{V}$, $R_r = \infty$ for the following values of inputs voltages.

a) $V_1 = V_2 = 5\text{V}$

b) $V_1 = 5\text{V}$, $V_2 = 0$

c) $V_1 = V_2 = 0$

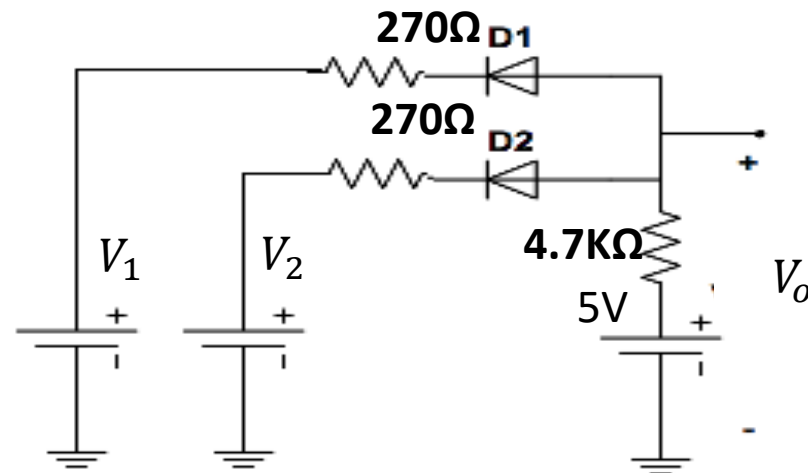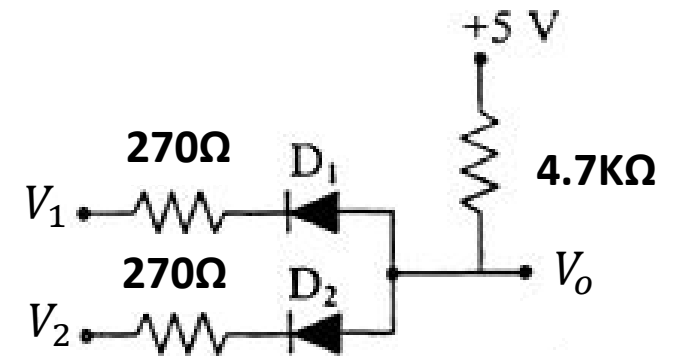


Solution:

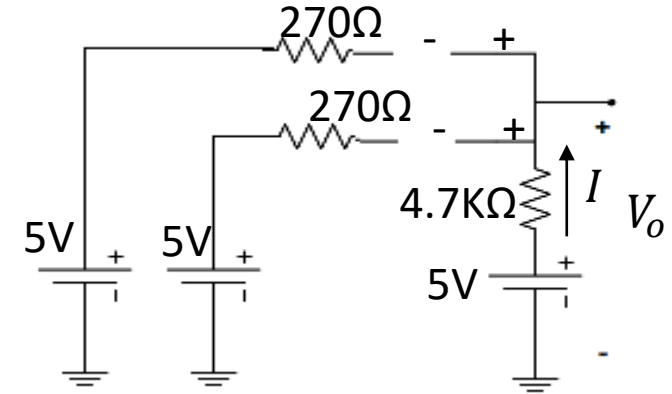a) $V_1 = V_2 = 5\text{V}$

Assume D1 & D2 are off replacing diode with $R_r = \infty$, means open circuit, the $V_o = 5\text{V}$

$V_{D1} \& V_{D2} = 0$ our assumption is true.



b) $V_1 = 5\text{V}$, $V_2 = 0$

Assume D1 is off & D2 is on


$V_o = 5 - 4700 I$

Applied KVL

$-5 + 4700I + 0.6 + 30I + 270I = 0$

$I = \frac{5 - 0.6}{4700 + 30 + 270} = 0.88 \text{ mA}$ ----- $I > 0$ our assumption is true.

$V_o = 5 - 4700 I = 0.864\text{V}$

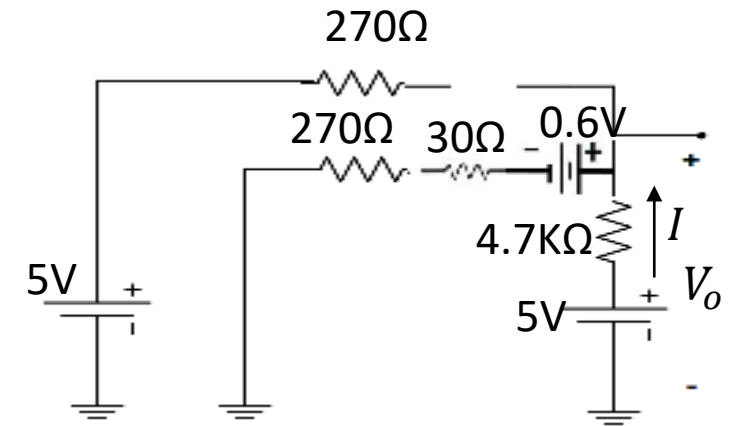

$$c) V_1 = V_2 = 0$$

Assume D1 & D2 are on


$$V_o = 5 - 4700(2I)$$

Applied KVL

$$-5 + 4700(2I) + 0.6 + 30I + 270I = 0$$

$$I = \frac{5 - 0.6}{4700(2) + 30 + 270} = 0.454 \text{ mA} \text{ ----- } I > 0 \text{ our assumption is true}$$


$$V_o = 5 - 4700(2I) = 0.736 \text{ V}$$

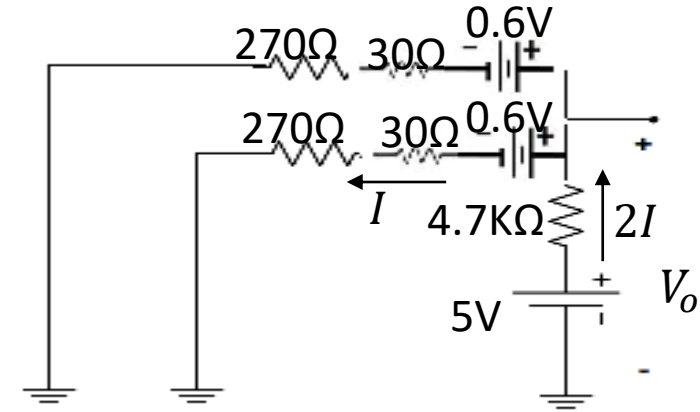

V1	V2	V _o
0	0	0.736
0	5	0.864
5	0	0.864
5	5	5

V1	V2	V _o
0	0	0
0	1	0
1	0	0
1	1	1

AND GATE

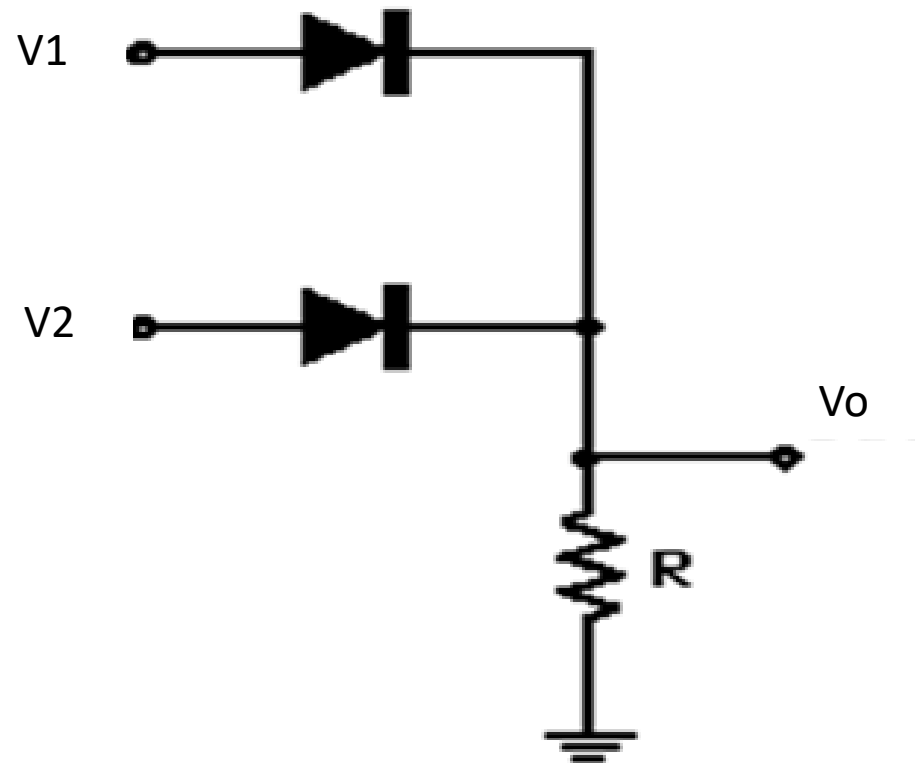

OR GATE

V1	V2	Vo
0	0	0
0	1	1
1	0	1
1	1	1

Load Line Concept (Graphical Analysis)

As shown in the circuit by applying KVL

$$-V_{DD} + I_D R + V_D = 0$$

$$I_D R + V_D = V_{DD}$$

$$I_D R = V_{DD} - V_D$$

$$I_D = -\frac{1}{R} V_D + \frac{V_{DD}}{R}$$

$$\text{At } V_D = 0 \rightarrow I_D = \frac{V_{DD}}{R}$$

$$\text{At } I_D = 0 \rightarrow V_D = V_{DD}$$

