


Differential Amplifiers

Problem (1)

The differential amplifier shown in Figures (1,2,3) are use two matched BJT's Q_1 and Q_2 with $\beta = 100$ and $V_A = \infty$.

Calculate:

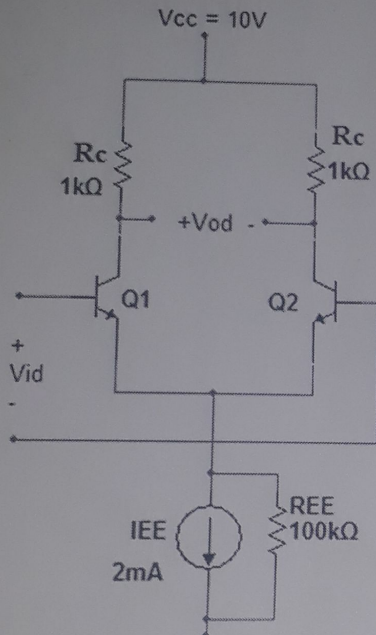1. The Value of collector current for Q_1 and Q_2 .
2. The differential mode gain A_{dm} .
3. The common mode gain A_{cm} .
4. The CMRR in decibel (dB).



Figure(1)

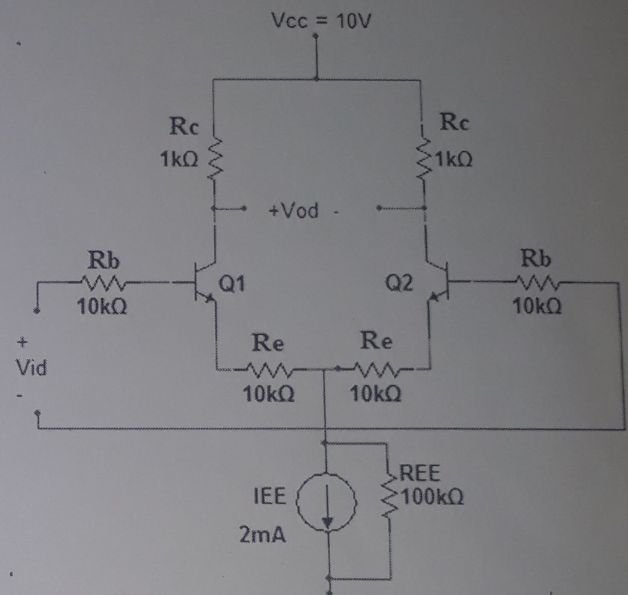


Figure (2)

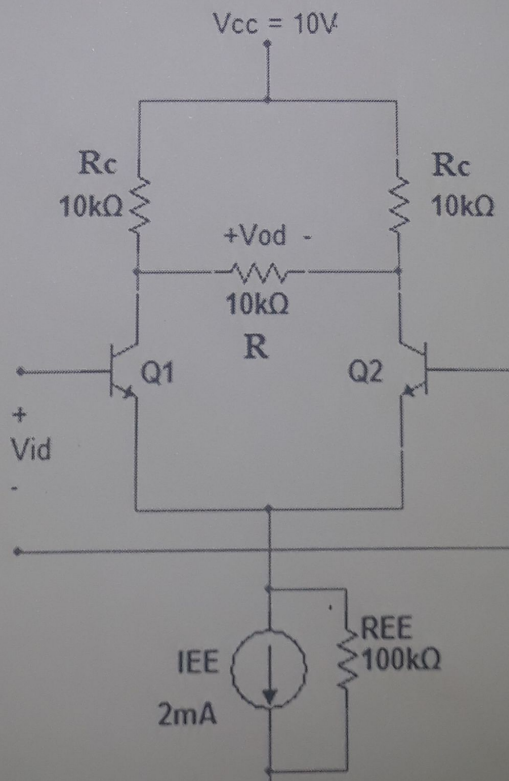


Figure (3)

Problem (2)

The differential amplifier shown in Figure (4) uses the current mirror current source Q3 and Q4 with $\beta = 200$ and $V_{A3} = V_{A4} = 120V$. If $V_{A1} = V_{A2} = \infty$, Calculate:

1. The Value of collector current for Q₁ and Q₂.
2. The differential mode gain A_{dm} .
3. The common mode gain A_{cm} .
4. The CMRR in decibel (dB).


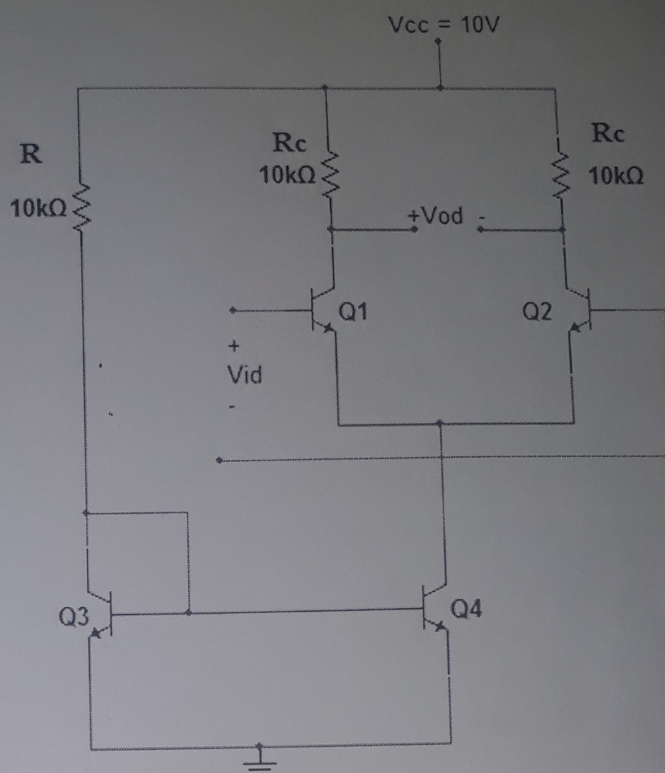


Figure (4)

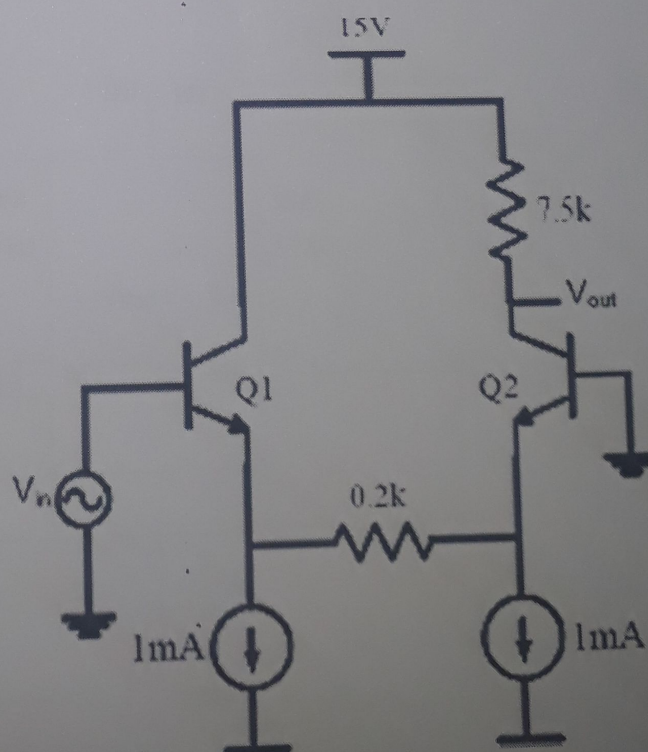Problem (3)

For the differential amplifier shown in Figure (5), calculate the voltage gain, input and output resistances. ($\beta=100$, $V_{A1} = V_{A2} = \infty$).



Figure(5)

Problem (4)

The MOS-differential amplifier shown in Figure (6,) uses two matched MOSFET's M_1 and M_2 with $K = 2\text{mA/V}^2$ and $V_A = \infty$.

Calculate:

1. The Value of the drain current for M_1 and M_2 .
2. The differential mode gain A_{dm} .
3. The common mode gain A_{cm} .
4. The CMRR in decibel (dB).

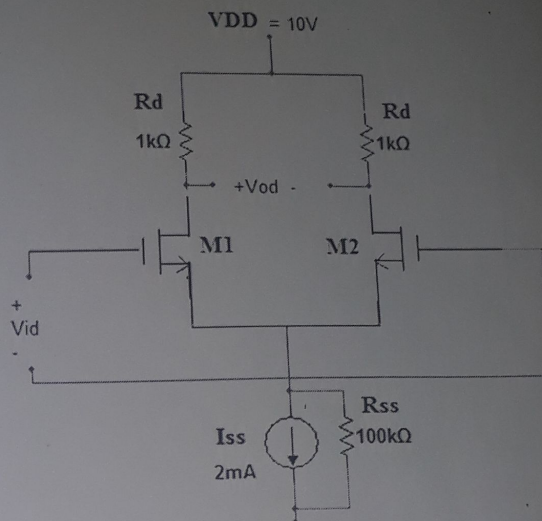


Figure (6)

Problem (5)

The differential amplifier shown in Figure (7) uses the current mirror current source M_3 and M_4 with $K = 0.5\text{mA/V}^2$ and $V_{A3} = V_{A4} = 120\text{V}$. If $V_{A1} = V_{A2} = \infty$, Calculate:

1. The differential mode gain A_{dm} .
2. The common mode gain A_{cm} .
3. The CMRR in decibel (dB).


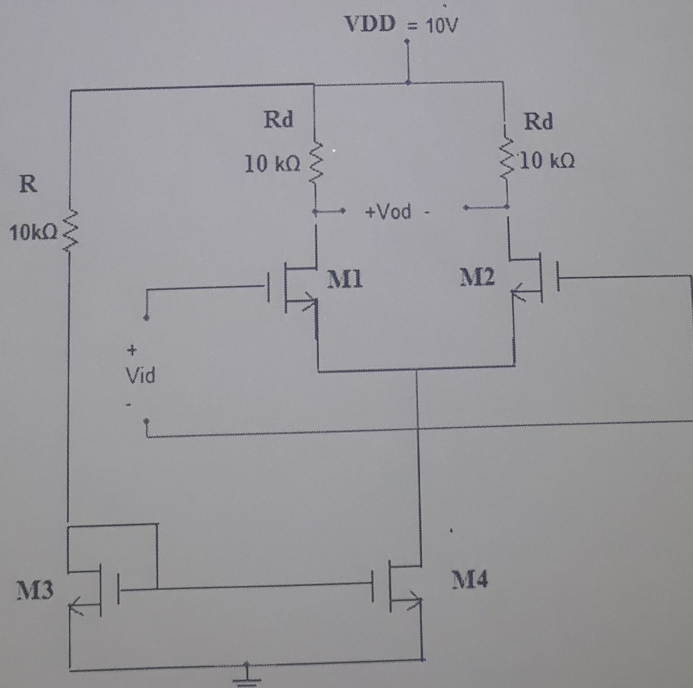


Figure (7)

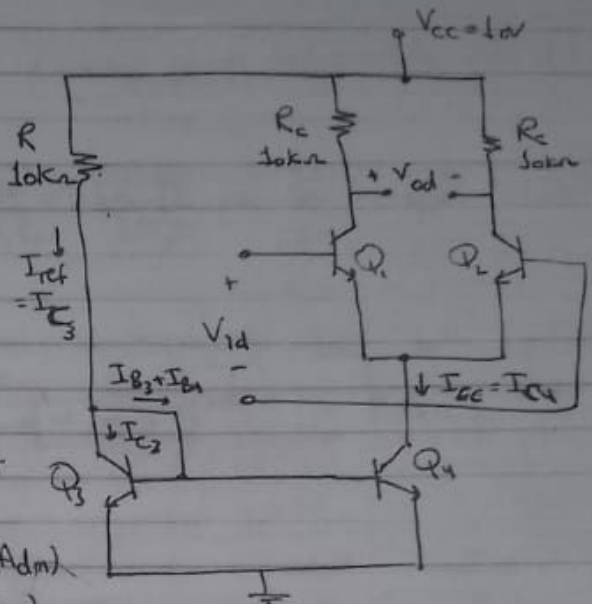Problem (2)

The differential amplifier shown in Figure (4) uses the current mirror current source Q_3 and Q_4 with $\beta = 200$ and $V_{A3} = V_{A4} = 120V$. If $V_{A1} = V_{A2} = \infty$, Calculate:



- 1) The value of collector current for Q_1 and Q_2
- 2) the differential mode gain (A_{dm})
- 3) The Common mode gain (A_{cm})
- 4) the CMRR in decibel (dB)

Figure (4)

Solution 1

$$① I_{ref} = \frac{V_{cc} - V_{CE3}}{R} = \frac{V_{cc} - V_{BE3}}{R} = \frac{10 - 0.7}{10} = \boxed{0.93 \text{ mA}}$$

$$I_{ref} = I_{C3} + I_{B3} + I_{B4}$$

$$V_{BE3} = V_{BE4} \quad ; \quad I_{C3} = I_{C4} \quad , \quad I_{B3} = I_{B4}$$

$$I_{ref} = I_{C4} + \frac{I_{C4}}{\beta} + \frac{I_{C4}}{\beta} = I_{C4} \left[1 + \frac{2}{\beta} \right]$$

$$I_{C4} = I_{EE} = \frac{I_{ref}}{1 + \frac{2}{\beta}} = \frac{0.93}{1 + 2/200} = \boxed{0.921 \text{ mA}}$$


$$I_{E1} = I_{E2} = \frac{I_{EE}}{2} = \frac{0.921}{2} = \boxed{0.46 \text{ mA}}$$

$$I_{C1} = I_{C2} = \frac{\beta}{1 + \beta} I_{E1} = \frac{200}{1 + 200} \cdot 0.46 = \boxed{0.458 \text{ mA}}$$



② The differential mode gain:

$$R_{EE} = r_{o4} = \frac{V_{A4}}{I_{C4}} = \frac{120}{0.921} = 130.29 \text{ k}\Omega$$
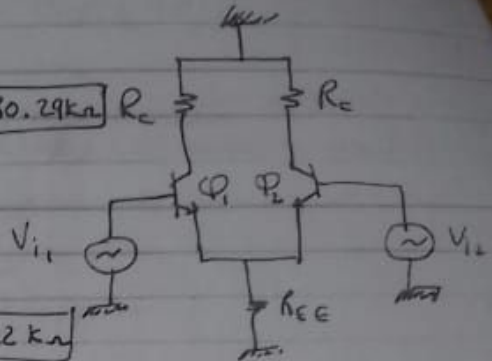
$$r_{\pi 1} = r_{\pi 2} = r_{\pi} = \beta \frac{V_T}{I_{C1}} = 200 \times \frac{0.025}{0.458} = 10.92 \text{ k}\Omega$$





Half - Circuit Concept

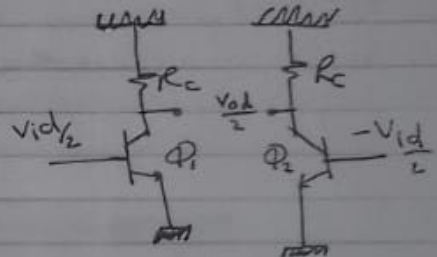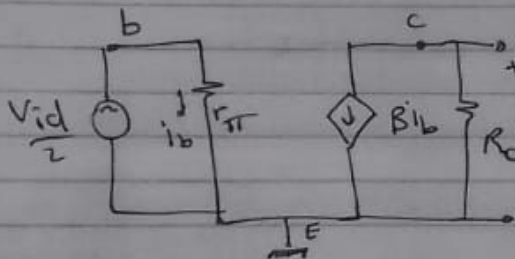

$$A_{dm} = \frac{V_{od1/2}}{V_{id1/2}} = \frac{V_{od}}{V_{id}} = \frac{-\beta i_b R_C}{i_b r_{\pi}} = \frac{-\beta R_C}{r_{\pi}}$$

$$A_{dm} = \frac{-200 \times 10 \times 10^3}{10.92 \times 10^3} = -183.15$$

③ The Common Mode gain:

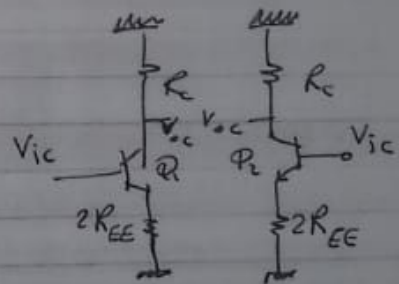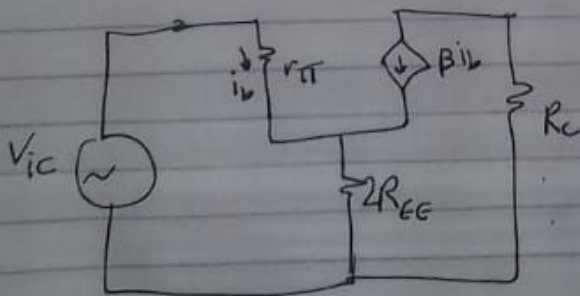

$$A_{CM} = \frac{V_{OC}}{V_{IC}} = \frac{-\beta \frac{1}{2} R_C}{\frac{1}{2} r_{\pi} + (1+\beta) \frac{1}{2} 2R_{EE}}$$

$$A_{CM} = \frac{-\beta R_C}{r_{\pi} + 2R_{EE}(1+\beta)} = \frac{-200 \times 10}{10.92 + 2(130.29)(1000)}$$

$$\boxed{A_{CM} = -0.038}$$

$$\textcircled{4} \quad CMRR = \left| \frac{A_{DM}}{A_{CM}} \right| = \left| \frac{183.15}{0.038} \right| = 4797.39$$

$$CMRR(dB) = 20 \log 4797.39 = \boxed{73.62 \text{ dB}}$$

... * ~~~~~ * ...

$$* I_{E1} = 1\text{mA}$$

$$, I_{E2} = 1\text{mA}$$

①

Note:- D.C Analysis

$$V_{E1} = -0.7\text{V}$$


$$V_{E2} = -0.7\text{V}$$

$$\therefore I = 0$$

$$\therefore I_{E1} = 1\text{mA} \approx I_{C1}$$

$$\therefore I_{E2} = 1\text{mA} \approx I_{C2}$$


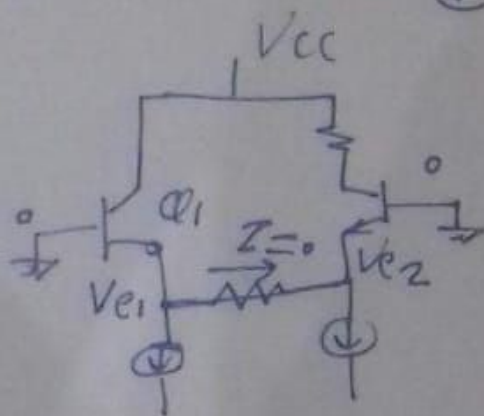
$$r_{\pi 1} = r_{\pi 2} = \beta \frac{V_T}{I_{C2}} = 100 \times \frac{0.025}{1\text{mA}} = 2.5\text{K}\Omega$$



A.C Analysis

$Q_1 \rightarrow$ Common-Collector

$Q_2 \rightarrow$ Common-Base

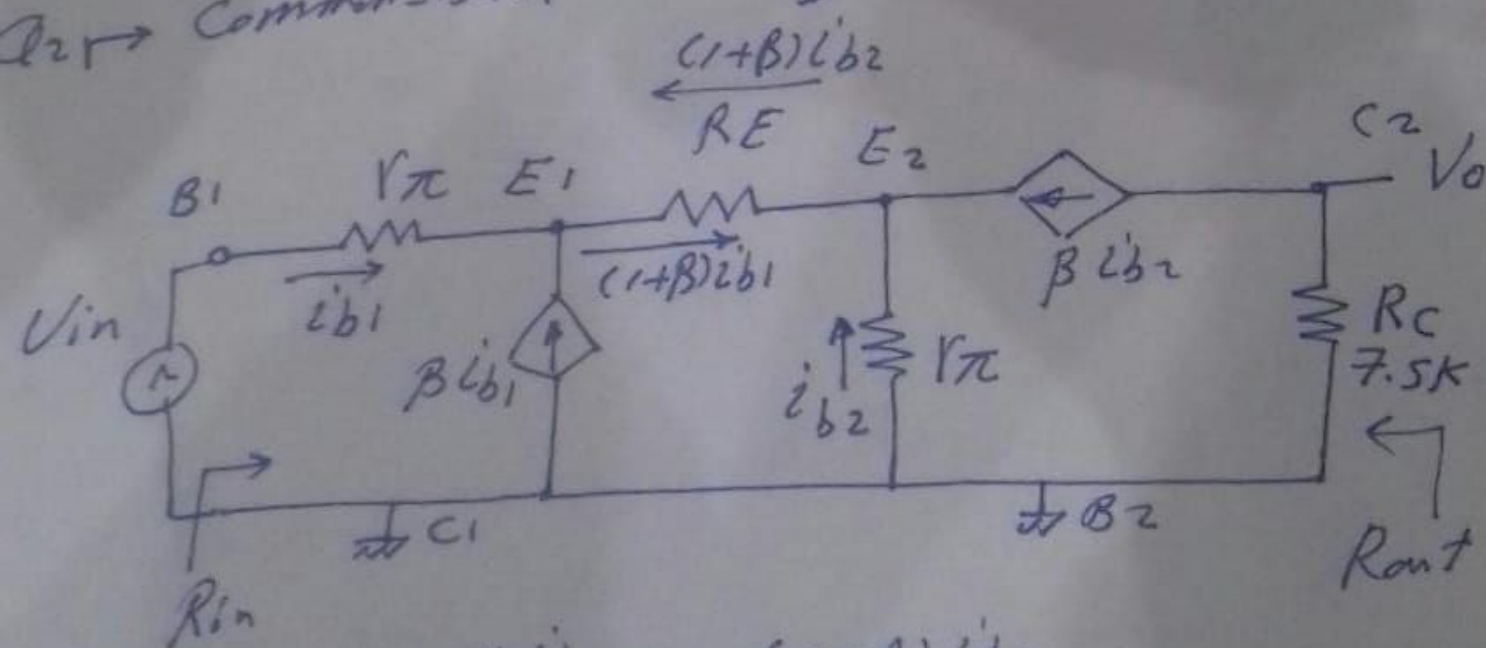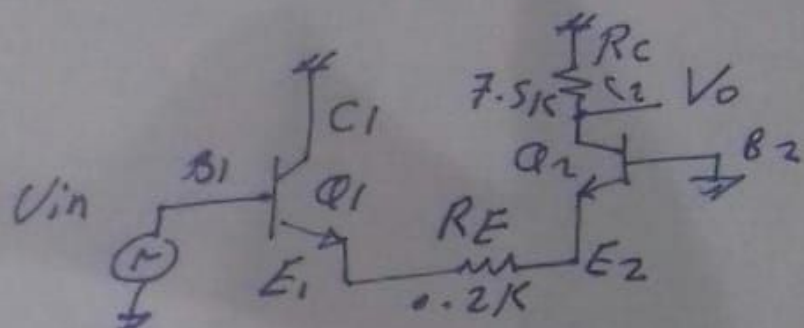

$$(1+\beta)i_{b2} = -(1+\beta)i_{b1}$$

$$\therefore \boxed{i_{b2} = -i_{b1}}$$

(2)

$$A_v = \frac{V_o}{V_{in}} \Rightarrow$$

$$V_o = -\beta i_{b2} R_c = +\beta i_{b1} R_c$$

$$\boxed{V_o = \beta i_{b1} R_c} \quad (1)$$

$$* V_{in} = i_{b1} r_{\pi} + (1+\beta) i_{b1} R_E - i_{b2} r_{\pi} \quad \leftarrow -i_{b1}$$

$$V_{in} = [r_{\pi} + (1+\beta) R_E + r_{\pi}] i_{b1}$$

$$\boxed{V_{in} = (2 r_{\pi} + (1+\beta) R_E) i_{b1}} \quad (2)$$

$$(1) \div (2) \quad A_v = \frac{V_o}{V_{in}} = \frac{\beta R_c}{2 r_{\pi} + (1+\beta) R_E}$$

$$A_v = \frac{100 \times 7.5}{2 \times 2.5 + 101 \times 0.2} = \frac{750}{5 + 20.2} = -$$

$$* R_{in} = \frac{V_{in}}{i_{b1}} \Rightarrow \text{from (2)}$$

$$R_{in} = \frac{2 r_{\pi} + (1+\beta) R_E}{1} = 2 \times 2.5 + 101 \times 0.2$$

= 20.2 k Ω

$$* R_{out} = R_c = 7.5 \text{ k}\Omega$$

As $V_{in} = 0 \quad i_{b1} = 0 \quad i_{b2} = 0$
 $\therefore \beta i_{b2} = 0 \quad (0 \text{ k}\Omega)$

Problem (5)

The differential amplifier shown in Figure (7) uses the current mirror current source M_3 and M_4 with $K = 0.5 \text{ mA/V}^2$ and $V_{A3} = V_{A4} = 120 \text{ V}$. If $V_{A1} = V_{A2} = \infty$, Calculate:

- 1) The differential mode gain A_{dm} .
- 2) The common mode gain A_{cm} .
- 3) The CMRR in decibel (dB).

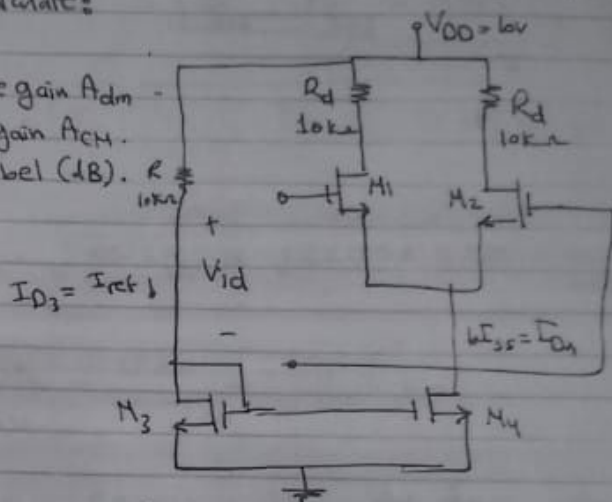


Figure (7)

① DC Analysis → Condition for Saturation $V_{DS} > V_{GS} - V_T$

For M_3 $V_{GS3} = V_{DS3} \Rightarrow \therefore M_3$ is in Saturation

K.V.L $10 = 10 I_{D3} + V_{DS3} = 10 I_{D3} + V_{GS3}$

$$\Rightarrow I_{D3} = \frac{10 - V_{GS3}}{10} = 1 - 0.1 V_{GS3} \quad \#1$$

[Known] $I_{D3} = \frac{K}{2} (V_{GS3} - V_T)^2$

$$1 - 0.1 V_{GS3} = \frac{0.5}{2} (V_{GS3} - 1)^2$$

$$4 - 0.4 V_{GS3} = V_{GS3}^2 - 2 V_{GS3} + 1$$

$$V_{GS3}^2 - 1.6 V_{GS3} - 3 = 0 \Rightarrow V_{GS3} = \begin{cases} 2.71 & \checkmark > V_T \\ -1.11 & \times \end{cases}$$

$$V_{GS3} = 2.71 \text{ V}$$

Sub in ①

$$I_{D3} = 1 - 0.1(2.71) = 0.729 \text{ mA}$$


$$\therefore V_{GS4} = V_{GS3} \Rightarrow I_{D4} = I_{D3} = 0.729 \text{ mA}$$

$$V_{GS1} = V_{GS2} \Rightarrow I_{D1} = I_{D2} = \frac{I_{ss}}{2} = \frac{0.729}{2} = 0.365 \text{ mA}$$

$$g_{m1} = g_{m2} = g_m = \sqrt{2K I_{D1}} = \sqrt{2 \times 0.5 \times 0.365} = 0.6041 \text{ mA/V}$$

$$R_{ss} = r_{ds4} = \frac{V_{A4}}{I_{D4}} = \frac{120 \text{ V}}{0.729 \text{ mA}} = 164.61 \text{ k}\Omega$$

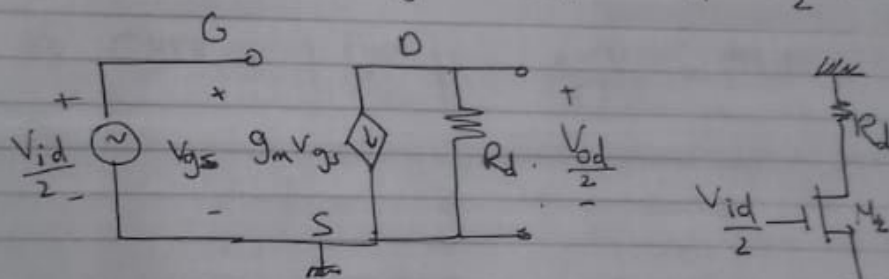
1) Differential mode gain (A_{dm}) . $V_{i1} = \frac{V_{id}}{2}$ & $V_{i2} = -\frac{V_{id}}{2}$



$$A_{dm} = \frac{V_{od}/2}{V_{id}/2} = \frac{V_{od}}{V_{id}} = \frac{-g_m V_{gs} R_d}{V_{gs}} = -g_m R_d$$

$$A_{dm} = -0.6041 \times 10 = -6.041$$

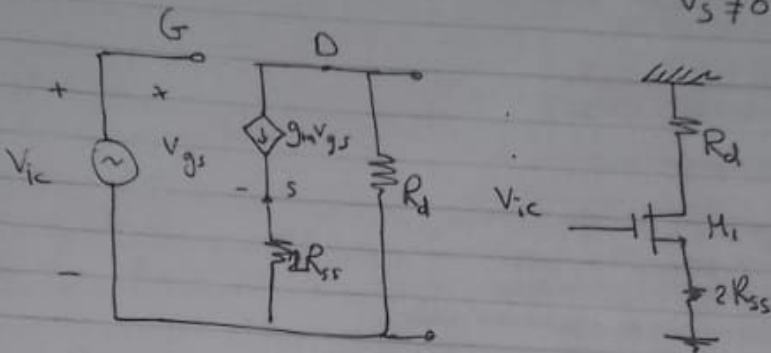2) Common mode gain (A_{CM}) , $V_{i1} = V_{ic}$, $V_{i2} = V_{ic}$
 $V_s \neq 0$



$$A_{CM} = \frac{V_{oc}}{V_{ic}} = \frac{-g_m V_{gs} R_d}{V_{gs} + 2R_{ss} g_m V_{gs}} = \frac{-g_m R_d}{1 + 2R_{ss} g_m}$$

$$A_{CM} = \frac{-0.6041 \times 10}{1 + 2(164.6)(0.6041)} = -0.0302$$

$$3) CMRR = \left| \frac{A_{DM}}{A_{CM}} \right| = \frac{6.041}{0.0302} = 199.88$$

$$CMRR(dB) = 20 \log 199.88 = 46.02 \text{ dB}$$

... * ~~~~~ *