
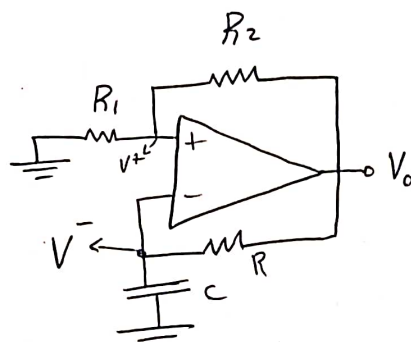


# # Astable Multivibrator :

1

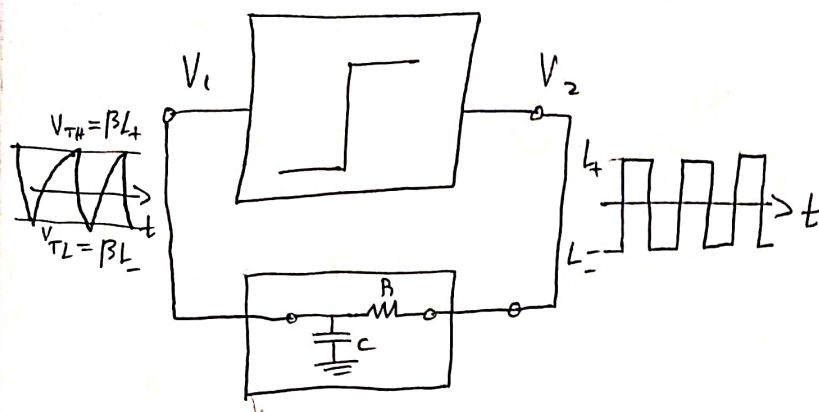

\* Ct. operation :

→ So, as  $V_0 = L^+$  → cap. starts to charge through R. until the  $V^- = V^+ \Rightarrow V_0$  switches to  $L^-$  & the cap. starts to discharge again through R. until  $V^-$  reach  $V^+$  again →  $V_0$  switches to  $L^+$  & so on.

$$\rightarrow \text{if } V_0 = L^+ \Rightarrow V^+ = \beta L^+, \beta = \frac{R_1}{R_1 + R_2}$$

for a capacitor :  $V_c = V_f + (V_{in} - V_f) e^{-t/\tau}$ ,  $\tau = RC$

$\downarrow$  Final Voltage     $\downarrow$  initial Voltage     $\downarrow$  final Voltage     $\downarrow$  Time constant


$$\Rightarrow V_c = L^+ + (\beta L^- - L^+) e^{-t/\tau}$$

$$\text{at } t = T_1 \Rightarrow V_c = \beta L^+$$

$$\Rightarrow \beta L^+ = L^+ + (\beta L^- - L^+) e^{-T_1/\tau}$$

$$\Rightarrow e^{\frac{T_1}{\tau}} = \frac{\beta L^- - L^+}{\beta L^+ - L^+}$$
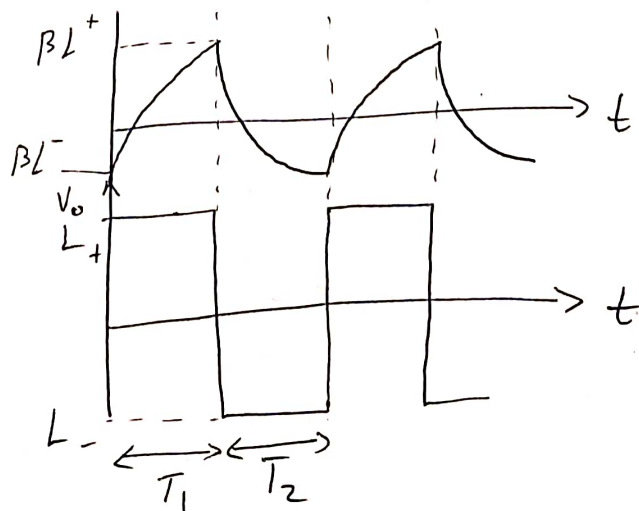
$$\Rightarrow \frac{T_1}{\tau} = \ln \left[ \frac{\beta L^- - L^+}{\beta L^+ - L^+} \right]$$



2

$$\Rightarrow \frac{T_1}{2} = RC \ln \left[ \frac{\beta L^- - L^+}{\beta L^+ - L^+} \right] \quad \because L^- = -L^+$$

$$\Rightarrow T_1 = RC \ln \left[ \frac{-\beta L^+ - L^+}{\beta L^+ - L^+} \right]$$


$$= RC \ln \left[ \frac{-L^+(1+\beta)}{L^+(1-\beta)} \right]$$

$$\Rightarrow \boxed{T_1 = RC \ln \left[ \frac{1+\beta}{1-\beta} \right]}$$

$$\because T_1 = T_2 \Rightarrow T_{\text{(periodic Time)}} = 2T_1 = 2RC \ln \left( \frac{1+\beta}{1-\beta} \right)$$

$$\Rightarrow f = \frac{1}{T}$$

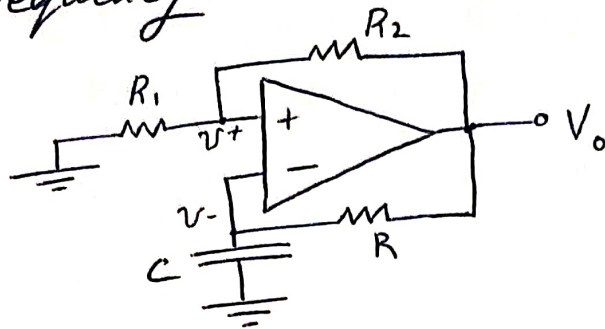Q1: For the shown circuit. let the op-amp saturation voltages be  $\pm 10V$ ,  $R_1 = 100\text{ K}\Omega$ ,  $R_2 = R = 1\text{ M}\Omega$  &  $C = 0.01\text{ }\mu\text{F}$ . Find the frequency of oscillation.



Sol:

$$\Rightarrow T = 2\tau \ln \left( \frac{1+\beta}{1-\beta} \right)$$

$$\tau = RC = 10^6 \times 0.01 \times 10^{-6} = 0.01 \text{ sec}$$

$$\beta = \frac{R_1}{R_1 + R_2} = \frac{100 \times 10^3}{(100 + 10^3) \times 10^3} = \frac{1}{11}$$


$$\Rightarrow T = 2(0.01) \ln \left( \frac{1 + (\frac{1}{11})}{1 - (\frac{1}{11})} \right)$$

$$= 3.646 \text{ msec}$$

$$\Rightarrow f = \frac{1}{T} = 274 \text{ Hz}$$

Q2: Consider the modification of the circuit in Q1. in which  $R_1$  is replaced by a pair of diodes connected in parallel in opposite directions. For  $L_+ = -L_- = 12V$ ,  $R_2 = R = 10k\Omega$ ,  $C = 0.1\mu F$ , & the diode voltage ( $V_D$ ) is constant, find an expression for the frequency as a function of  $V_D$ . if  $V_D = 0.7V$  at  $25^\circ C$  with  $T_c = -2mV/^\circ C$  find the frequency at  $0^\circ C$ ,  $25^\circ C$ ,  $50^\circ C$  &  $100^\circ C$ .

Sol:

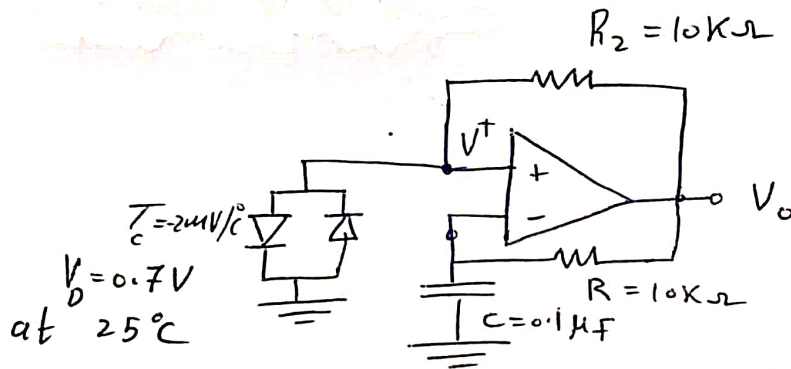

$V_f \rightarrow$  final voltage  
 $V_{in} \rightarrow$  initial voltage

\* for the capacitor  $C$ :  $V_c = (V_{in} - V_f) e^{-t/\tau} + V_f$ ,  $\tau = RC$

$\hookrightarrow$  this relation can be proved if you solved the diff. eq<sup>n</sup> for a simple RC ct.

So, assuming that  $V_c$  initially is  $-V_D$ .

$$\Rightarrow \text{at } T_1 \Rightarrow V_c = V_D$$

$$\Rightarrow V_D = L_+ + (-V_D - L_+) e^{-T_1/\tau}$$


$$\Rightarrow e^{-T_1/\tau} = \frac{-V_D - L_+}{V_D - L_+}$$

$$\Rightarrow \frac{T_1}{\tau} = \ln\left(\frac{-V_D - L_+}{V_D - L_+}\right)$$

$$\Rightarrow T_1 = \tau \ln\left(\frac{L_+ + V_D}{L_+ - V_D}\right)$$

$$\because T_1 = T_2 \Rightarrow T = 2T_1$$
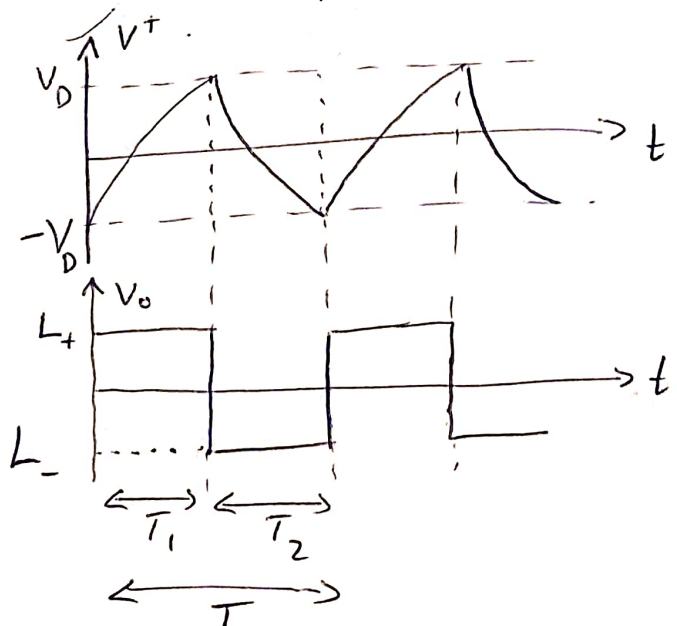
$$\Rightarrow T = 2\tau \ln\left(\frac{L_+ + V_D}{L_+ - V_D}\right)$$



$$\Rightarrow f = \frac{1}{T} = \frac{1}{2\tau \psi_u\left(\frac{L_+ + V_D}{L_+ - V_D}\right)}$$

$$\therefore \tau = RC = 10 \times 10^3 \times 0.1 \times 10^{-6} = 1 \text{ msec}$$

$$L_+ = 12 \text{ V}, L_- = -12 \text{ V}$$

$$\Rightarrow f = \frac{500}{\psi_u\left(\frac{12 + V_D}{12 - V_D}\right)} \text{ Hz}$$

$$\text{at } T = 25^\circ \text{C} \quad \therefore V_D = 0.7 = V_{D_0}$$

$$\Rightarrow f = \frac{500}{\psi_u\left(\frac{12 + 0.7}{12 - 0.7}\right)} = 4280.8 \text{ Hz}$$

$$\text{at } T = 0^\circ \text{C} \quad \therefore \Rightarrow V_D = V_{D_0} + T_c (\Delta T)$$

$$\Rightarrow \Delta T = -25, T_c = -2 \times 10^{-3} \text{ V/}^\circ \text{C}$$

$$\Rightarrow V_D = 0.7 + (25 \times 2 \times 10^{-3}) = 0.75 \text{ V}$$

$$\Rightarrow f = \frac{500}{\psi_u\left(\frac{12 + 0.75}{12 - 0.75}\right)} = 3994.7 \text{ Hz}$$

$$\text{at } T = 50^\circ \text{C} \quad \therefore \Rightarrow V_D = V_{D_0} + \underbrace{T_c}_{L > 25} (\Delta T)$$


$$\Rightarrow V_D = 0.7 - (25 \times 2 \times 10^{-3}) = 0.65 \text{ V}$$

$$\Rightarrow f = \frac{500}{\psi_u\left(\frac{12 + 0.65}{12 - 0.65}\right)} = 4610.8 \text{ Hz}$$

So, This Ct. can be used as a Temp. Meter.




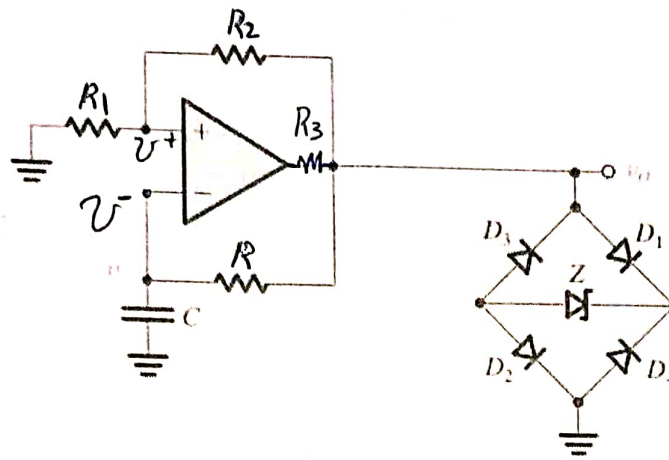
Q3- The astable multivibrator circuit in the shown circuit is augmented with an output limiter. Design the circuit to obtain an output square wave with 5-V amplitude and 1-kHz frequency using a 10 nF capacitor C. Use  $\beta = 0.462$ , and design for a current in the resistive divider approximately equal to the average current in the RC network over a half-cycle. Assuming  $\pm 13$ -V op-amp saturation voltages, arrange for the Zener to operate at a current of 1 mA.



sol<sup>n</sup>:

- for the limiter ct. : if  $V_o \rightarrow +ve$  :

if  $V_o \rightarrow -ve$  :

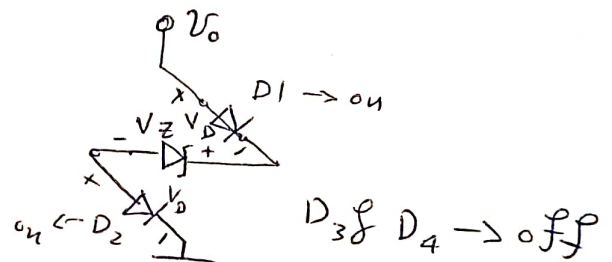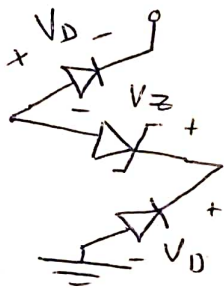

$$\Rightarrow V_o = -2V_D - V_Z \quad \Rightarrow V_o = 2V_D + V_Z$$

∴ if we need to limit o/p to  $\pm 5$  V :

$$\Rightarrow 2V_D + V_Z = 5 \text{ V}, \text{ let } V_D = 0.7$$

$$\Rightarrow \boxed{V_Z = 5 - 1.4 = 3.6 \text{ V}}$$

$$\therefore T = 2\tau \ln\left(\frac{1+\beta}{1-\beta}\right), \quad f = 1 \text{ kHz} \Rightarrow T = 10^{-3} \text{ sec}$$

$$\beta = 0.462, \quad \tau = RC$$

$$\Rightarrow 10^{-3} = 2R(10 \times 10^{-9}) \ln\left(\frac{1.462}{1-0.462}\right) \quad C = 10 \text{ nF}$$

$$\Rightarrow R = 50 \text{ k}\Omega$$

$$\therefore L_+ = 13V, L_- = -13V$$

7

$$\Rightarrow V_{TH} = L_+ \beta = 13(0.462) = 2.31V$$

$$\Rightarrow V_{TL} = L_- \beta = -13(0.462) = -2.31V$$

\* To get average current in R in  $\frac{1}{2}$  cycle:


> Voltage across R =  $V_R = V_o - v^-$

Taking +ve half cycle:

$v^-$  changes from  $-2.31V$

to  $2.31V$ .

&  $V_o = 5V$

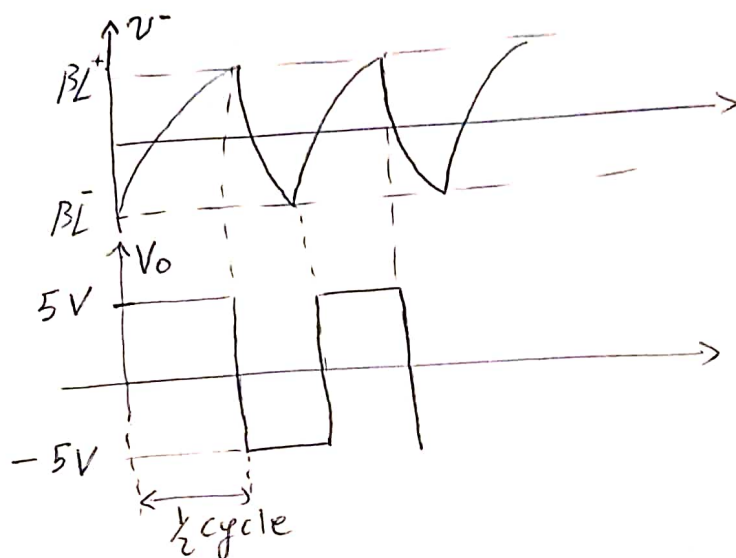

$$\Rightarrow V_R|_{avg \frac{1}{2} cycle} = \frac{(5 + 2.31) + (5 - 2.31)}{2} = 5V$$

$$\Rightarrow I_R|_{avg \frac{1}{2} cycle} = \frac{V_R|_{avg \frac{1}{2} cycle}}{R} = \frac{5}{R}$$

$$\therefore R = 50K \Rightarrow I_R|_{avg} = \frac{5}{50K} = 0.1mA$$

$\therefore$  current in  $R_1$  &  $R_2 = I_R|_{avg}$

$$\Rightarrow \boxed{\frac{5}{R_1 + R_2} = 0.1mA}$$


$$\Rightarrow \boxed{R_1 + R_2 = 50K\Omega}$$

$$\beta = \frac{R_1}{R_1 + R_2} = 0.462$$

$$\Rightarrow \boxed{R_1 = 0.462(50K) = 23.1K\Omega}$$

$$\Rightarrow \boxed{R_2 = 26.9K\Omega}$$

$$\therefore I_Z = 1mA$$

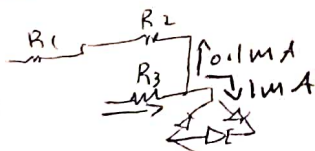

$$\Rightarrow \frac{13 - 5}{R_3} = 1mA + 0.1mA \Rightarrow \boxed{R_3 = 6.67K\Omega}$$