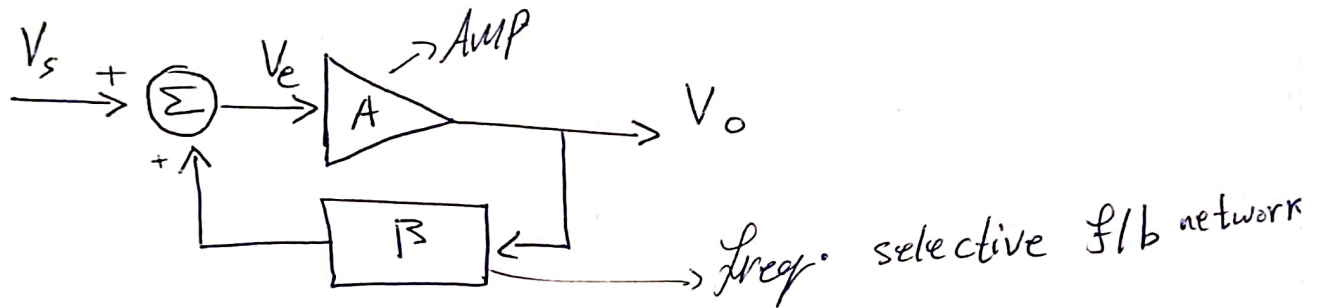


Oscillators

* Oscillators are cts that produce periodic waveform without having an i/p.

⇒ For a system to oscillate, it must satisfy the Barkhausen criterion.

Barkhausen criterion :



$$\Rightarrow V_o = [V_s + B V_o] A$$

$$\Rightarrow V_o [1 - AB] = V_s A$$


$$\Rightarrow \boxed{\frac{V_o}{V_s} = \frac{A}{1 - AB}} \rightarrow \text{closed loop gain}$$

$$\boxed{AB} \rightarrow \text{open loop gain}$$

$$\Rightarrow \boxed{\begin{array}{l} |AB| = 1 \\ \angle AB = 0^\circ \text{ or } 360^\circ \end{array}}$$

↳ so if we are using an inverting Amplifier $\Rightarrow \text{gain} = -A \rightarrow 180^\circ \text{ phase shift}$
↳ we need $B \rightarrow$ to add 180° phase shift

4 RC phase-shift oscillator:

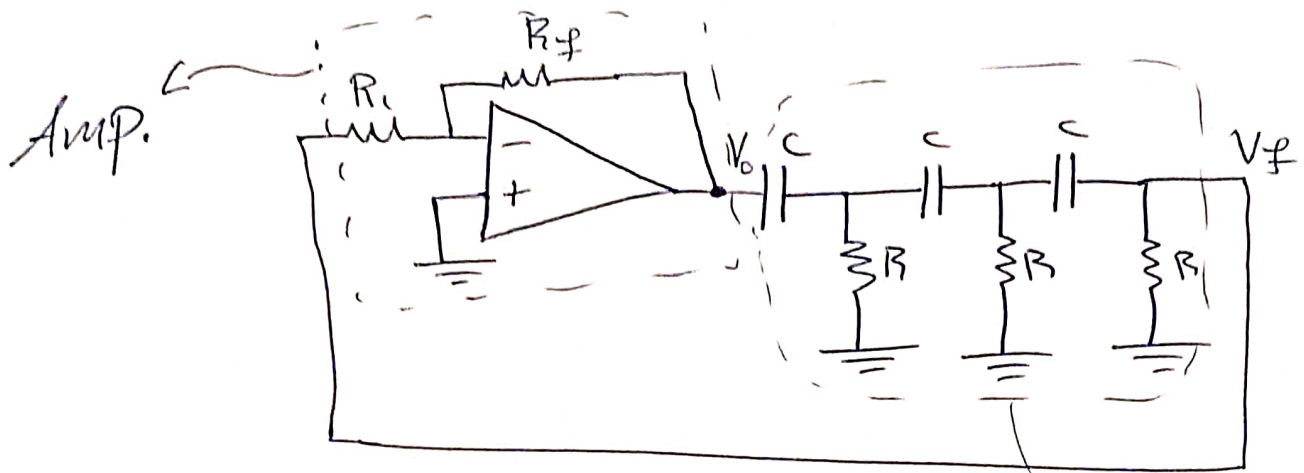

$$* A_v = -\frac{R_f}{R_1} \Rightarrow \angle A_v = 180^\circ$$


\Rightarrow we need to choose the values of R & C that make $\angle B = 180^\circ$ at ω_0 .

\hookrightarrow desired freq. of oscillation

$$\Rightarrow A = -\frac{R_f}{R_1} \Rightarrow \text{Real}$$

∴ Oscillation condition: $A B = 1$

\Rightarrow imaginary part = 0 at ω_0 .

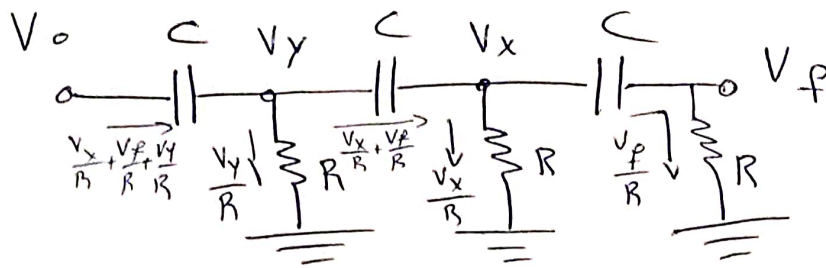

$$\Rightarrow V_x = V_f + \frac{V_f}{R} \cdot \frac{1}{sC}$$

$$V_x = V_f \left[1 + \frac{1}{sRC} \right]$$

$$\Rightarrow V_y = V_x + \left[\frac{V_x}{R} + \frac{V_f}{R} \right] \frac{1}{sC}$$

$$V_y = \frac{V_f}{sRC} + V_x \left[1 + \frac{1}{sRC} \right] = \frac{V_f}{sRC} + V_f \left[1 + \frac{1}{sRC} \right]^2 = V_f \left[\frac{1}{sRC} + \left(1 + \frac{1}{sRC} \right)^2 \right]$$

$$\Rightarrow V_o = V_y + \left[\frac{V_x}{R} + \frac{V_f}{R} + \frac{V_y}{R} \right] \frac{1}{sC}$$

$$\Rightarrow V_o = V_y \left[1 + \frac{1}{sRC} \right] + \frac{V_x}{sRC} + \frac{V_f}{sRC}$$

$$\Rightarrow V_o = \left[V_f \left(\frac{1}{sRC} + \left[1 + \frac{1}{sRC} \right]^2 \right) \right] \left[1 + \frac{1}{sRC} \right]$$

$$+ \frac{V_f}{sRC} \left[1 + \frac{1}{sRC} \right] + \frac{V_f}{sRC}$$

$$\Rightarrow \beta = \frac{V_f}{V_o} = \frac{1}{\left(\frac{1}{sRC} + \frac{1}{s^2 R^2 C^2} \right) + \left(1 + \frac{1}{sRC} \right)^3 + \left(\frac{1}{sRC} + \frac{1}{s^2 R^2 C^2} \right) + \frac{1}{sRC}}$$

$\left(1 + \frac{1}{sRC} \right)^3 = \left(1 + \frac{3}{sRC} + \frac{3}{s^2 R^2 C^2} + \frac{1}{s^3 R^3 C^3} \right)$
 at $s = j\omega_0$

$$\Rightarrow \beta = \frac{1}{\left(\frac{1}{j\omega_0 RC} - \frac{1}{\omega_0^2 R^2 C^2} \right) + \left(1 - \frac{3}{\omega_0^2 R^2 C^2} + \frac{3}{j\omega_0 RC} - \frac{1}{j\omega_0^3 R^3 C^3} \right) + \left(\frac{1}{j\omega_0 RC} - \frac{1}{\omega_0^2 R^2 C^2} \right) + \frac{1}{j\omega_0 RC}}$$

$\therefore A \rightarrow$ pure Real $\Rightarrow \beta \rightarrow$ Real \rightarrow imaginary part = 0

$$\Rightarrow \frac{6}{\omega_0 RC} - \frac{1}{\omega_0^3 R^3 C^3} = 0 \Rightarrow 6\omega_0^2 R^2 C^2 = 1$$

$$\Rightarrow \boxed{\omega_0 = \frac{1}{\sqrt{6} RC}}$$

$$\operatorname{Re}\{\beta\} = \frac{1}{-\frac{1}{\omega_0^2 R^2 C^2} + 1 - \frac{3}{\omega_0^2 R^2 C^2} - \frac{1}{\omega_0^2 R^2 C^2}}$$

$$= \frac{\omega_0^2 R^2 C^2}{-2 + \omega_0^2 R^2 C^2 - 3}$$

$$\because \omega_0^2 = \frac{1}{6R^2 C^2}$$

$$\Rightarrow \beta = \frac{\frac{1}{6R^2 C^2} R^2 C^2}{-5 + \frac{1}{6R^2 C^2} R^2 C^2} = \frac{\frac{1}{6}}{-5 + \frac{1}{6}} = -\frac{1}{29}$$

$$\Rightarrow |A\beta| = 1 \Rightarrow \beta = \frac{1}{A}$$

$$\Rightarrow \boxed{A = 29}$$

gain must be at least 29
for the phase-shift oscillator.

* You may do the same analysis using Mesh analysis

In an RC phase shift oscillator, if $R_1 = R_2 = R_3 = 200 \text{ K}\Omega$ & $C_1 = C_2 = C_3 = 100 \text{ pF}$. Find the frequency of oscillation

Sol:

$$\therefore f = \frac{1}{2\pi RC\sqrt{6}}$$

$$\Rightarrow f = \frac{1}{2\pi (200 \times 10^3)(100 \times 10^{-12}) \times \sqrt{6}}$$

$$\Rightarrow f = 3.248 \text{ KHz}$$

Given a BJT-based RC phase shift oscillator, if $R = 10 \text{ K}\Omega$, $C = 0.01 \mu\text{F}$ & $R_c = 2.2 \text{ K}\Omega$. Find the frequency of oscillation & the minimum current gain (β) needed to achieve the oscillation condition.

Sol:

$$\Rightarrow f = \frac{1}{2\pi RC \sqrt{6 + 4 \frac{R_c}{R}}}$$


$$= \frac{1}{2\pi (10 \times 10^3)(0.01 \times 10^{-6}) \sqrt{6 + 4 \left(\frac{2.2}{10}\right)}}$$

$$= 606.7 \text{ Hz}$$

$$\Rightarrow \beta_{\min} = 23 + 4 \frac{R_c}{R} - \frac{29R}{R_c}$$

$$= 23 + 4 \left(\frac{2.2}{10}\right) - 29 \left(\frac{10}{2.2}\right) = 155.7$$

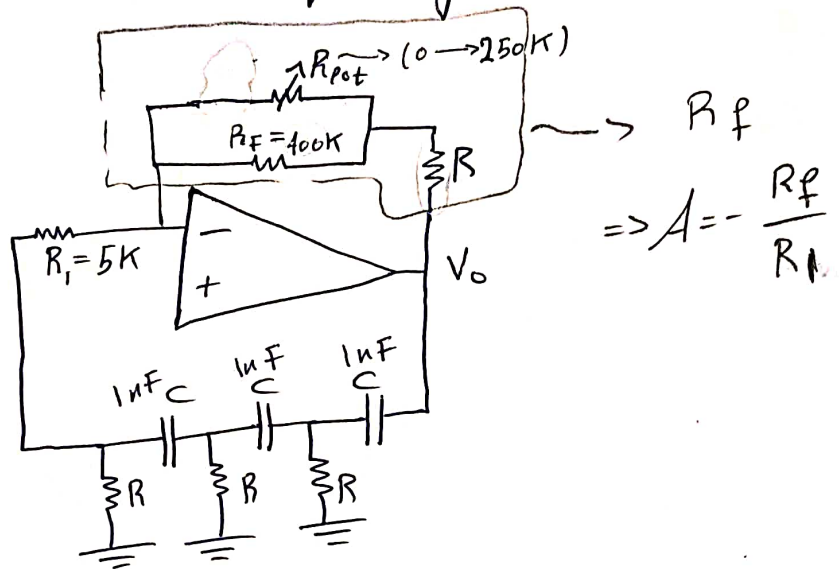For the given RC-phase shift oscillator,
Find the value of R & R_{pot} that results
in the minimum frequency of oscillation
(note that $R_1 \geq 10R$ must be satisfied), then
Find the value of this frequency.



Sol :

$$\because R_1 \geq 10R$$

$$\Rightarrow R_{max} = \frac{R_1}{10} = 500 \Omega$$

$$\because f_o = \frac{1}{2\pi\sqrt{6}RC} \Rightarrow f_{o_{min}} \xrightarrow{\text{for } R_{max}}$$

$$\Rightarrow \text{for phase-shift oscillator: } A \geq 29$$

$$\Rightarrow 500 + \left(\frac{R_{pot}(400k)}{R_{pot} + 400k} \right) = 29(5k) \Rightarrow \frac{(R + R_{pot} // R_F)}{R_1} \geq 29$$

$$\Rightarrow 500(R_{pot} + 400k) + R_{pot}(400k) = 29(5k)R_{pot} + (400k)(29)(5k)$$

$$\Rightarrow R_{pot} = 226.2 k\Omega$$

$$\Rightarrow f_{o_{min}} = \frac{1}{2\pi \underbrace{(5 \times 29 \times 10^3)}_{R_{\text{feedback (Total)}}} (1 \times 10^{-9}) \sqrt{6}} = 448.1 \text{ Hz}$$