

# **Electronic Systems**

## **Active Filters**

### **Lecture 4**

**Dr. Roaa Mubarak**

# The Active Filters Contents:

1. Introduction to Filters.
2. Low Pass Filter.
3. High Pass Filter.
4. Band Pass Filter.
- 5. Butterworth Filter.**
6. Chebyshev Filter.
7. Bessel Filter.
8. KHN Biquad filter.
9. Multiple Feedback Filters.
10. State Variable Filters.

# 3. Butterworth Band Pass Filter (BBF)



- $f_L$  is the lower Cut-off Frequency
- $f_H$  is the Higher Cut-off Frequency
- B.W is the Band-Width
  - $B.W = f_H - f_L$
- Condition:  $f_H (f_{c(LPF)}) > f_L (f_{c(HPF)})$

The Center Frequency (Tuned Freq.)

$$f_o = \sqrt{f_L \cdot f_H}$$

The Quality Factor  
(How Sharp is the response)

$$Q = \frac{f_o}{B.W}$$

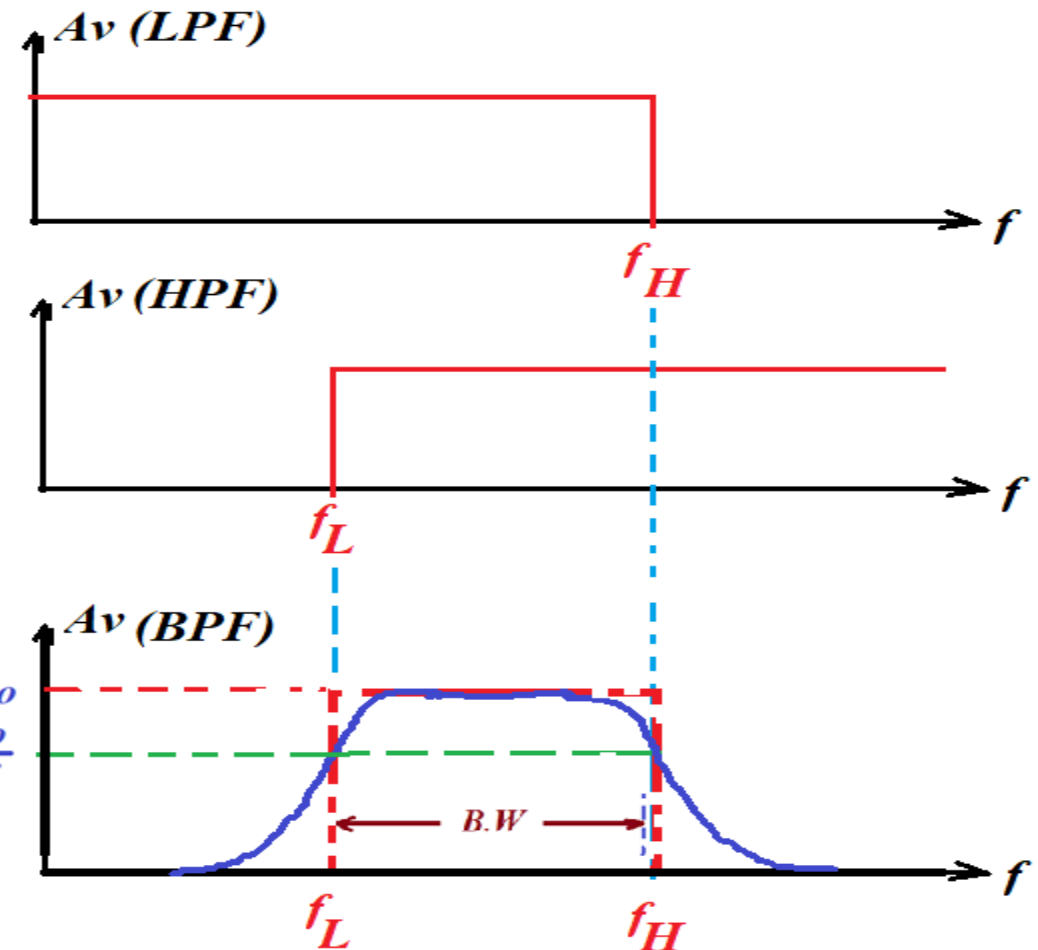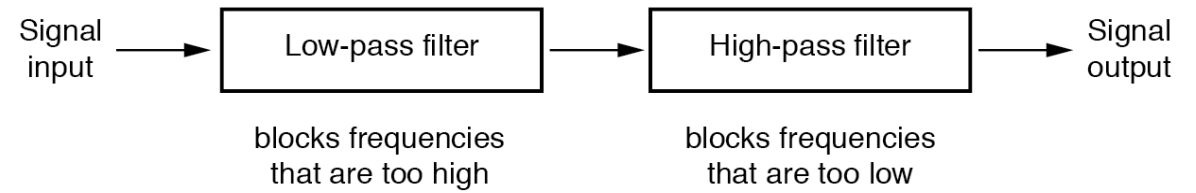

### 3. Butterworth Band Pass Filter (BBF)

#### Example 1:



**Design a 3<sup>rd</sup> order Butterworth Band-Pass-Filter (BPF) for the audio frequency band from 20 Hz to 20 KHz. The Butterworth polynomial for  $n = 3$  is  $(S+1)(S^2 + S + 1)$ .**

- (a) Draw the Block- diagram for the filter.**
- (b) Draw the Circuit- diagram for the filter.**
- (c) Calculate the values of the circuit components.**

# 3. Butterworth Band Pass Filter (BBF)


**Solution:**

**(a) Block Diagram**

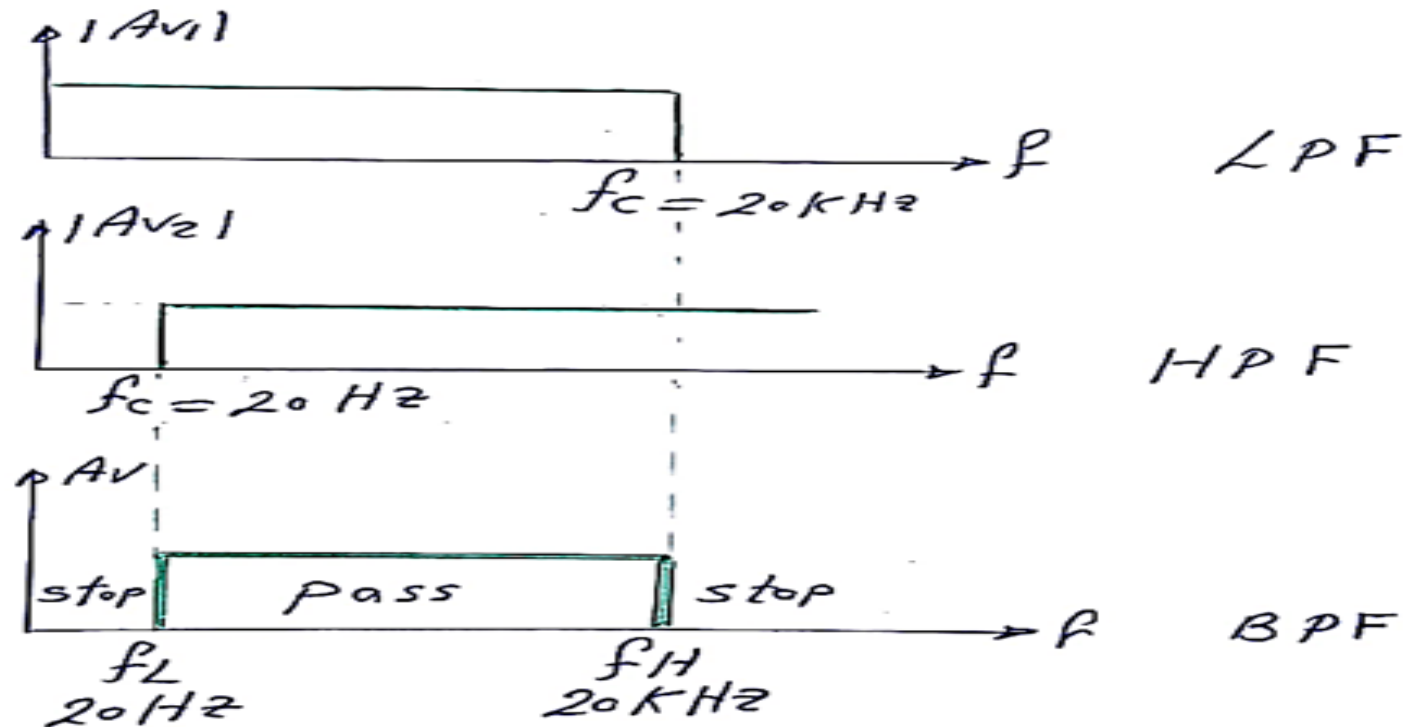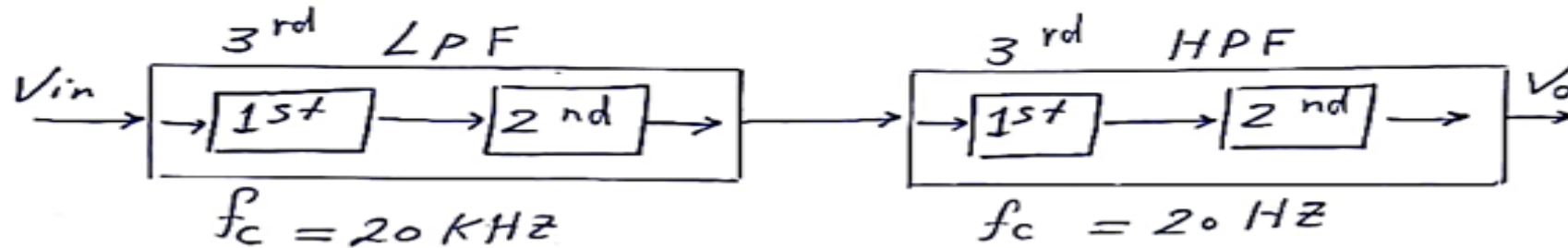

# 3. Butterworth Band Pass Filter (BBF)

## (b) Circuit Diagram

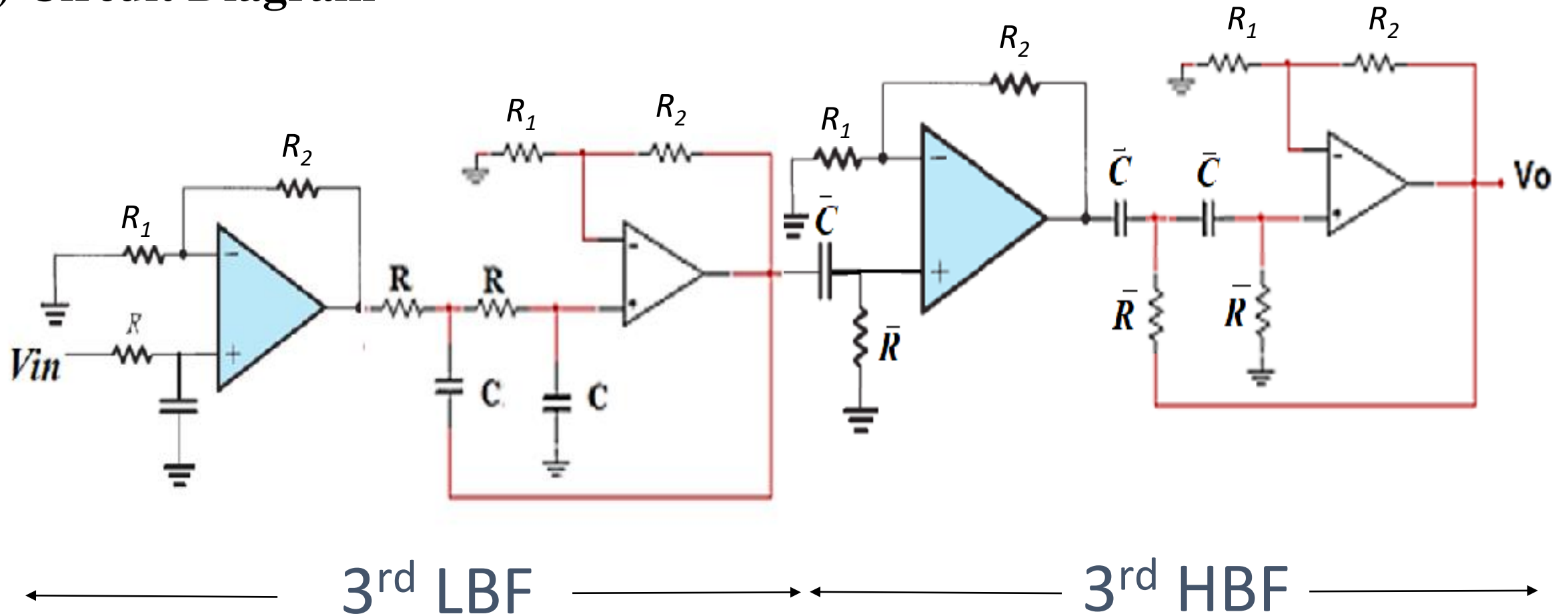

# 3. Butterworth Band Pass Filter (BBF)

## (c) Circuit Components Calculations

□ For LPF :-

$$* f_o = f_c = \frac{1}{2\pi RC} \rightarrow 20 \times 10^3 = \frac{1}{2\pi RC}$$

$$\text{Choose } \boxed{C = 0.01 \mu F} \rightarrow \therefore \boxed{R = 795.77 \Omega}$$

\* For HPF :-

$$* f_o = f_c = \frac{1}{2\pi \bar{R} \bar{C}} \rightarrow 20 = \frac{1}{2\pi \bar{R} \bar{C}}$$

$$\text{Choose } \boxed{\bar{C} = 0.01 \mu F} \rightarrow \therefore \boxed{\bar{R} = 795.775 K\Omega}$$

---

For  $n = 3 \rightarrow$  polynomial is  $(s+1)(s^2+s+1)$

$$\boxed{2K=1} \leftarrow \therefore A_o = 3 - 2K = 3 - 1 = 2$$

$$\boxed{A_o = 2} = 1 + \frac{R_2}{R_1} \rightarrow \therefore \frac{R_2}{R_1} = 1$$

$$\text{Let } \boxed{\begin{matrix} R_1 = 10 K\Omega \\ R_2 = 10 K\Omega \end{matrix}}$$

### 3. Butterworth Band Pass Filter (BBF)

#### Example2:

**Design a 4<sup>th</sup> order Butterworth Band-Pass-Filter (BPF) for the audio frequency band from 20 Hz to 20 KHz. The Butterworth polynomial for  $n = 4$  is  $(S^2+0.765S+1)(S^2+ 1.848S +1)$**


- (a) Draw the Block- diagram for the filter.**
- (b) Draw the Circuit- diagram for the filter.**
- (c) Calculate the values of the circuit components.**



# 3. Butterworth Band Pass Filter (BBF)


**Solution:**

**(a) Block diagram**

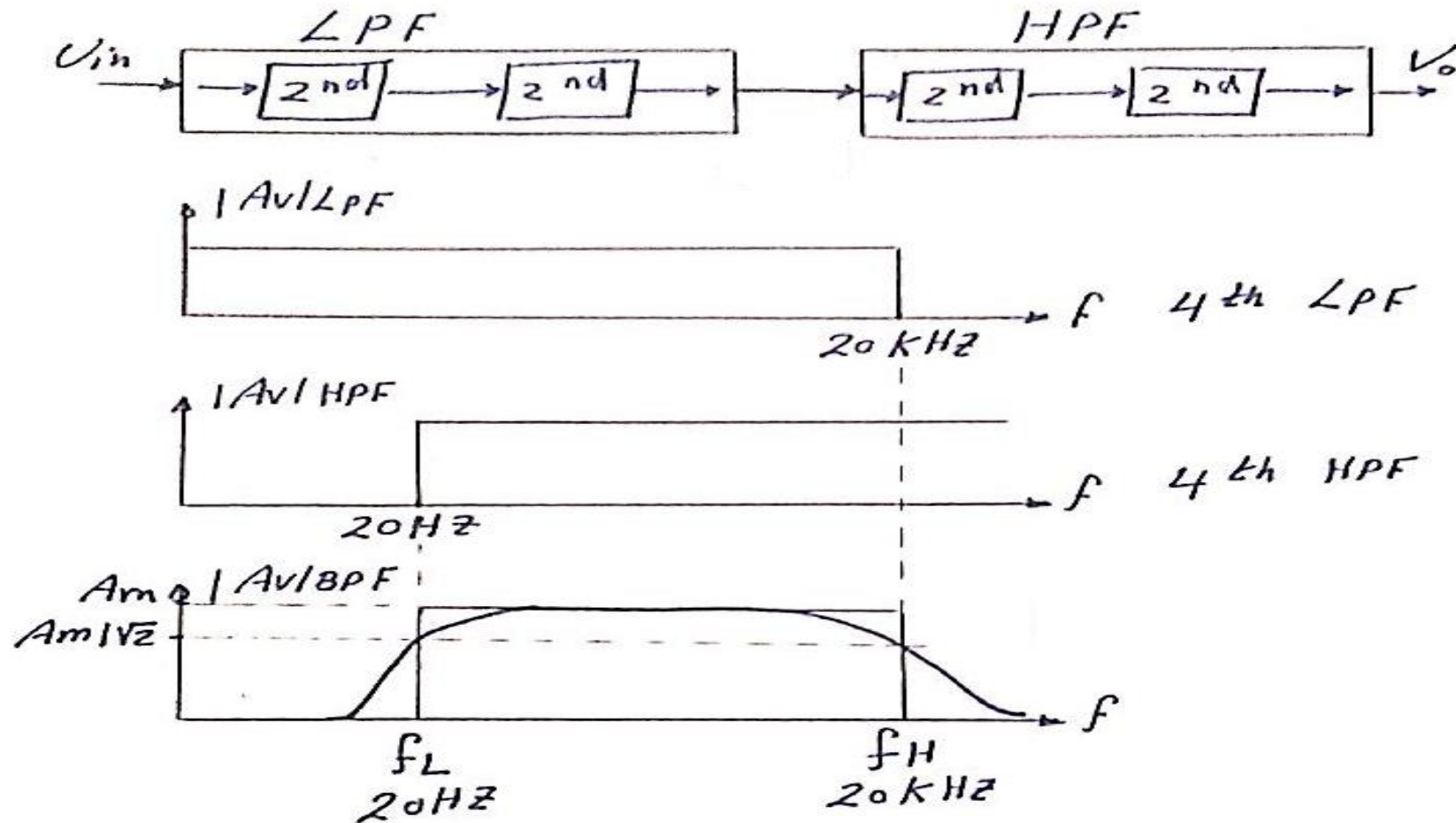

### 3. Butterworth Band Pass Filter (BBF)

#### (b) Circuit- diagram

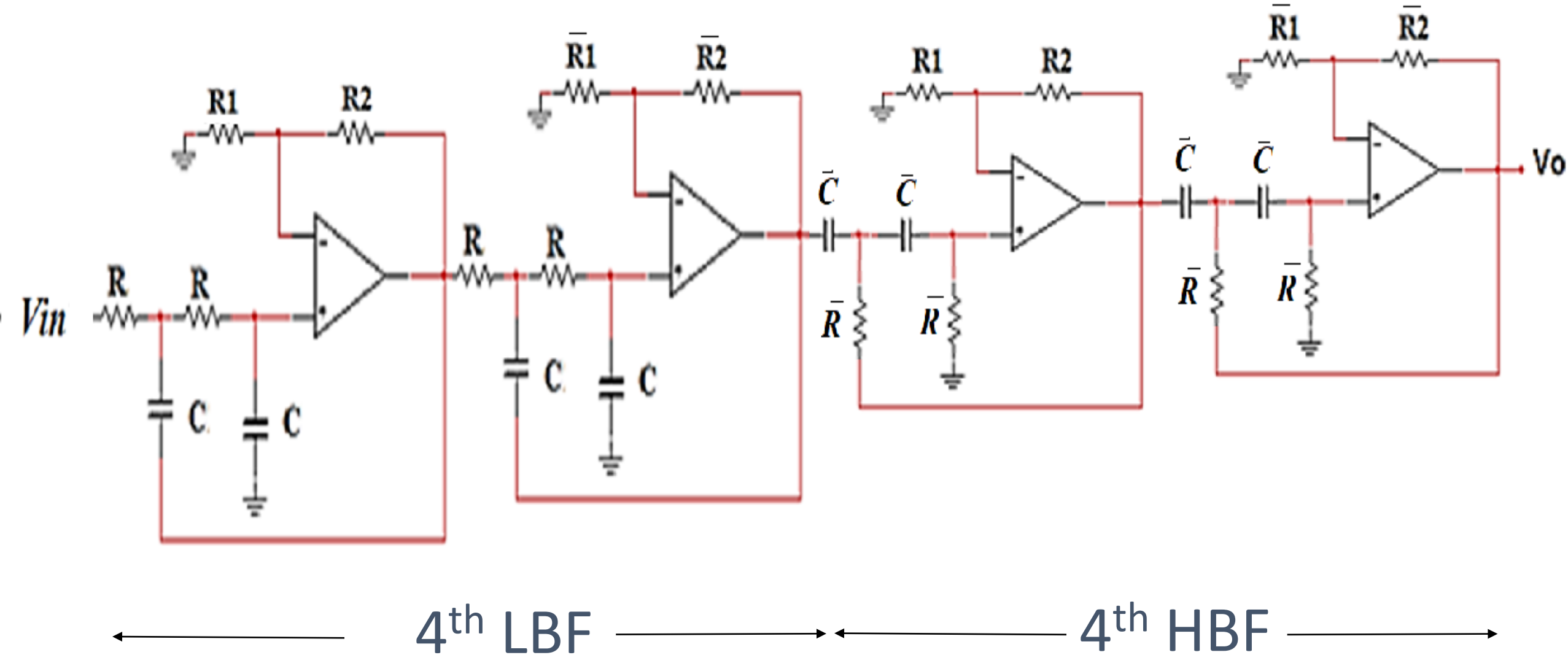

### 3. Butterworth Band Pass Filter (BBF)

#### (b) Circuit Components Calculations:

For LPF:-

$$f_0 = \frac{1}{2\pi RC} = 20 \times 10^3 \text{ Hz}$$

choose  $C = 0.01 \mu\text{F}$   $\rightarrow \therefore R = 795.775 \Omega$

For HPF:-

$$f_0 = \frac{1}{2\pi R' C'} = 20 \text{ Hz}$$

choose  $C = 0.01 \mu\text{F}$   $\rightarrow \therefore R = 795.775 \text{ k}\Omega$

$$Bn(s) = (s^2 + 0.765s + 1)(s^2 + 1.848s + 1)$$

$$2K_1 = 0.765$$

$$\therefore Am_1 = 3 - 2K_1 = 2.235$$

$$Am_1 = 1 + \frac{R_2}{R_1} = 2.235$$

$$\frac{R_2}{R_1} = 1.235$$

Let  $\rightarrow R_1 = 10 \text{ k}\Omega$   
 $\therefore R_2 = 12.35 \text{ k}\Omega$

$$2K_2 = 1.848$$



$$\therefore Am_2 = 3 - 2K_2 = 1.152$$

$$Am_2 = 1 + \frac{R_2'}{R_1'} = 1.152$$

$$\frac{R_2'}{R_1'} = 0.152$$

Let  $\rightarrow R_1' = 10 \text{ k}\Omega$   
 $\therefore R_2' = 1.52 \text{ k}\Omega$
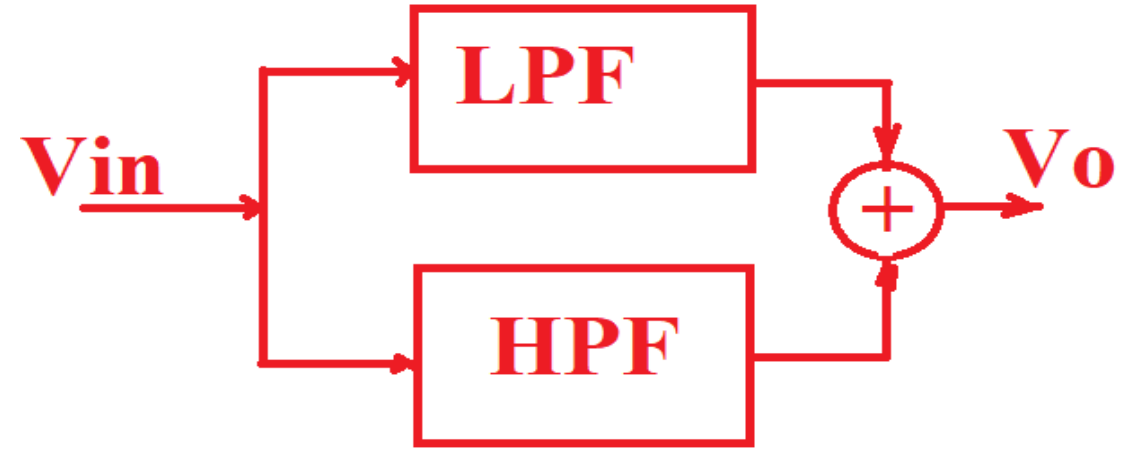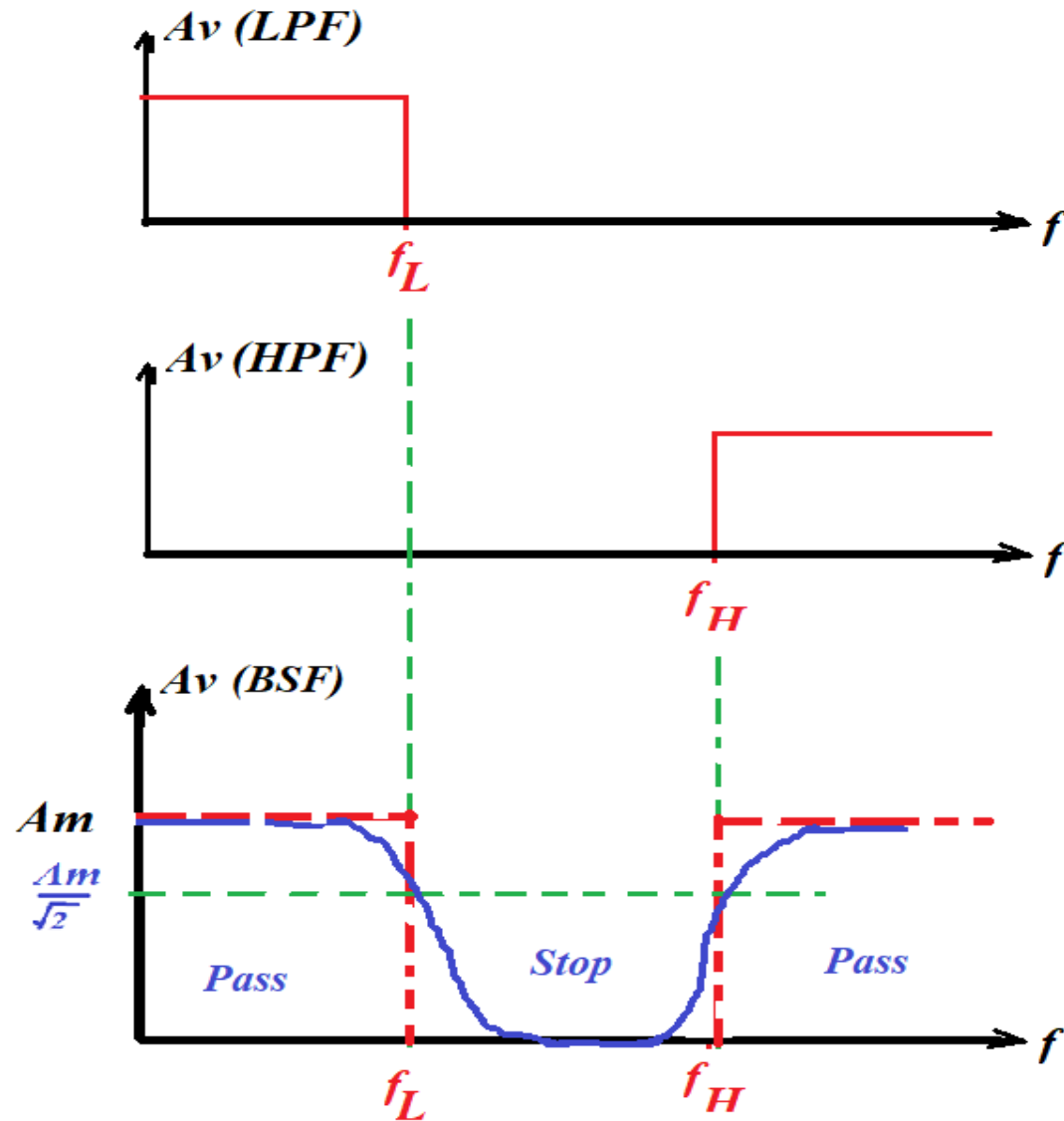
## 4. Butterworth Band Stop Filter (BSF) (BRF)



□ Condition:  $f_L (f_{c(LPF)}) < f_H (f_{c(HPF)})$

## 4. Butterworth Band Stop Filter (BSF) (BRF)

### Example3:


**3rd order Butterworth BSF to reject the frequency band from 10 KHz to 40 KHz. The Butterworth polynomial for  $n = 3$  is  $(S + 1)(S^2 + S + 1)$ .**

- 1. Draw the block diagram for the filter.**
- 2. Draw the circuit diagram.**
- 3. Calculate all circuit components values.**

# 4. Butterworth Band Stop Filter (BSF) (BRF)


**Solution:**

**(a) Block Diagram:**

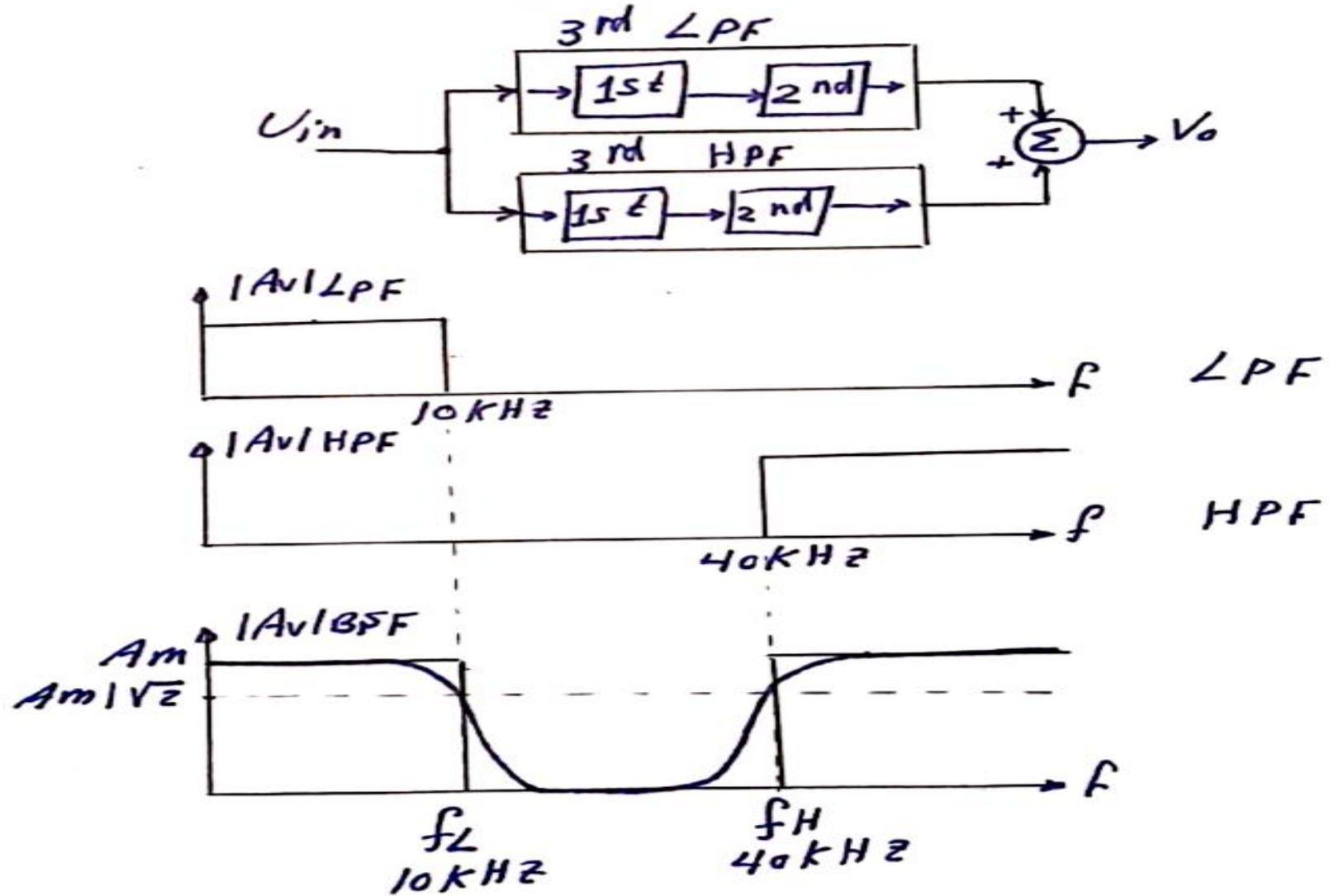

# 4. Butterworth Band Stop Filter (BSF) (BRF)

## (b) Circuit- diagram

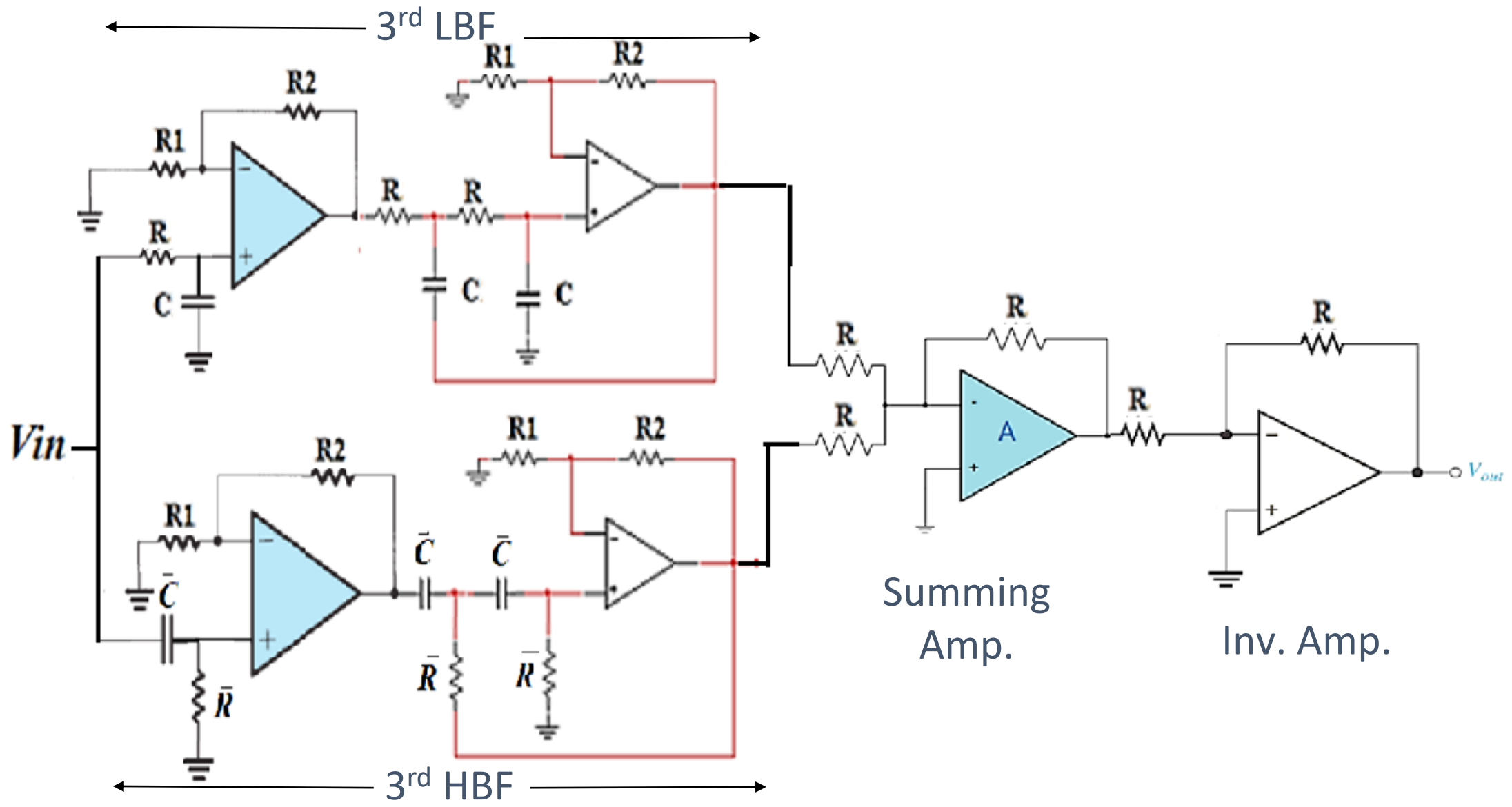



# 4. Butterworth Band Stop Filter (BSF) (BRF)

## (C) Components Calculations

For LPF:-

$$f_0 = \frac{1}{2\pi RC} = 10^4 \text{ Hz}$$

choose  $C = 0.01 \mu\text{F}$   $\rightarrow \therefore R = 1591.55 \Omega \approx 1.59 \text{ k}\Omega$

For HPF:-

$$f_0 = \frac{1}{2\pi R'C'} = 40 \times 10^3 \text{ Hz}$$

choose  $C' = 0.01 \mu\text{F}$   $\rightarrow \therefore R' = 397.89 \Omega \approx 398 \Omega$

$$B_n(s) = (s+1)(s^2 + s + 1)$$

\* For the second-order

$$A_m = 3 - 2k = 3 - 1 = 2 = 1 + \frac{R_2}{R_1}$$

$$\therefore \frac{R_2}{R_1} = 1$$

Let  $R_1 = 10 \text{ k}\Omega \rightarrow \therefore R_2 = 10 \text{ k}\Omega$

Assuming the gain of the first-order part is equal to that of the second-order part.



## 4. Butterworth Band Stop Filter (BSF) (BRF)



### Example 4:

**Design a 4<sup>th</sup> order Butterworth BSF to reject the frequency band from 2 KHz to 10 KHz. The Butterworth polynomial for  $n = 4$  is  $(S^2 + 1.848 S + 1)(S^2 + 0.765 S + 1)$ .**

- 1. Draw the block diagram for the filter.**
- 2. Draw the circuit diagram.**
- 3. Calculate all circuit components values.**


# 4. Butterworth Band Stop Filter (BSF) (BRF)

## (a) Block diagram

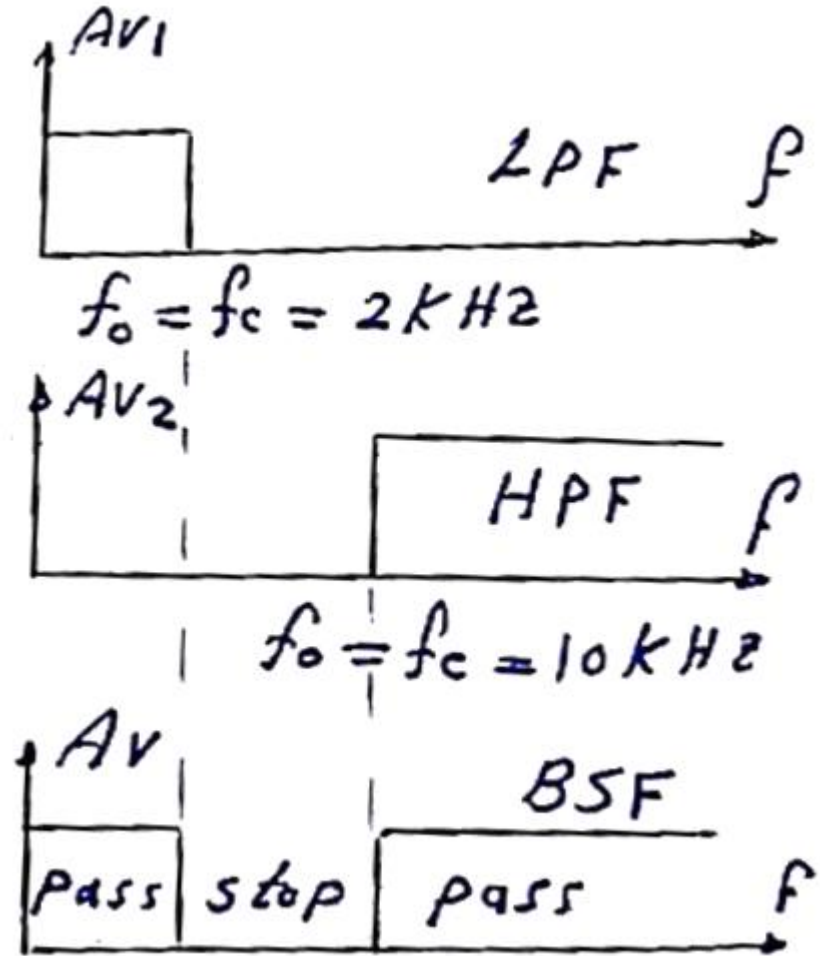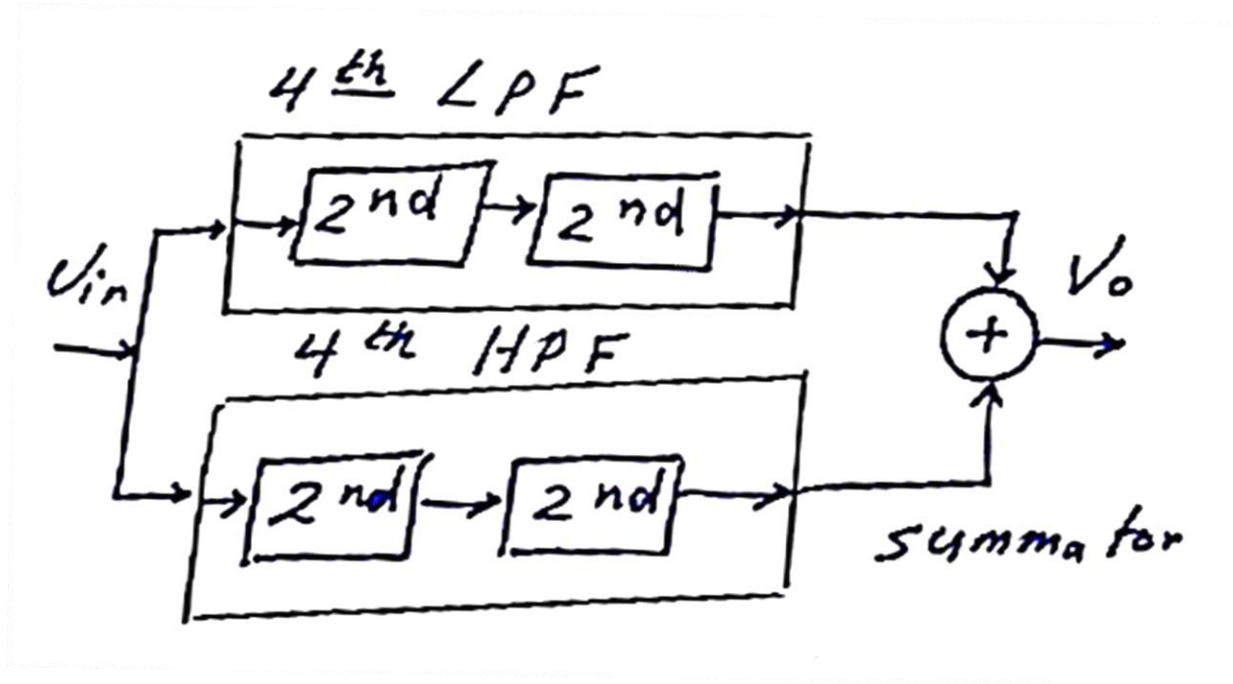

## 4. Butterworth Band Stop Filter (BSF) (BRF)

**(b) Circuit diagram**

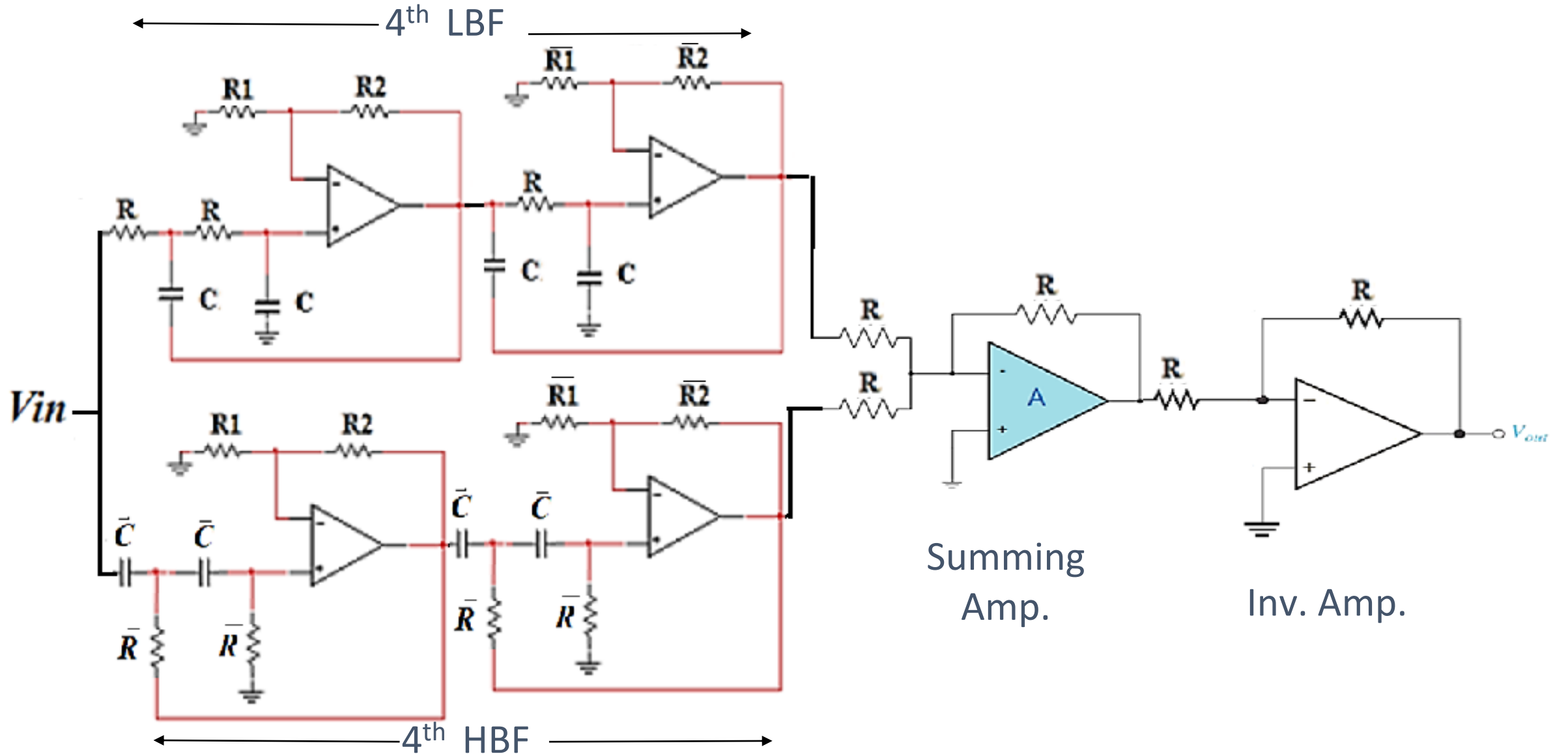

## 4. Butterworth Band Stop Filter (BSF) (BRF)

For L.P.F

$$f_c = 2 \times 10^3 = \frac{1}{2\pi RC}, \text{ choose } \boxed{C = 0.01 \mu F}$$

$$\therefore R = \frac{1}{2\pi \times 2 \times 10^3 \times 0.01 \times 10^{-6}} \checkmark \boxed{R \cong 7.96 \text{ k}\Omega}$$

For H.P.F

$$f_c = 10 \times 10^3 = \frac{1}{2\pi R' \bar{C}}, \text{ choose } \boxed{\bar{C} = 0.01 \mu F}$$

$$\therefore \bar{R} = \frac{1}{2\pi \times 10 \times 10^3 \times 0.01 \times 10^{-6}} \checkmark \boxed{\bar{R} = 1.59 \text{ k}\Omega}$$

$$\text{For } n=4 \checkmark (s^2 + 1.848s + 1) \cdot (s^2 + 0.765s + 1)$$

$$2K = 1.848$$

$$A_0 = 3 - 2K = 1.152 = 1 + \frac{R_2}{R_1}$$

$$\therefore \boxed{\frac{R_2}{R_1} = 0.152}$$

$$\text{choose } \boxed{R_1 = 10 \text{ k}\Omega}$$
$$\therefore \boxed{R_2 = 1.52 \text{ k}\Omega}$$

$$2K' = 0.765$$

$$A_0 = 3 - 2K' = 2.235 = 1 + \frac{\bar{R}_2}{\bar{R}_1}$$

$$\therefore \boxed{\frac{\bar{R}_2}{\bar{R}_1} = 1.235}$$

$$\text{choose } \boxed{\bar{R}_1 = 10 \text{ k}\Omega}$$
$$\therefore \boxed{\bar{R}_2 = 12.35 \text{ k}\Omega}$$

# Unity Gain Filter ( $A_m=1$ )

## 1. First Order LPF:

*Transfer Function*

$$A_V(S) = \frac{1}{1 + \frac{S}{W_c}}$$


*The maximum gain  $A_m$  is unity*

$$W_c = 2\pi f_c$$

*$f_c$  Is the cut-off frequency*
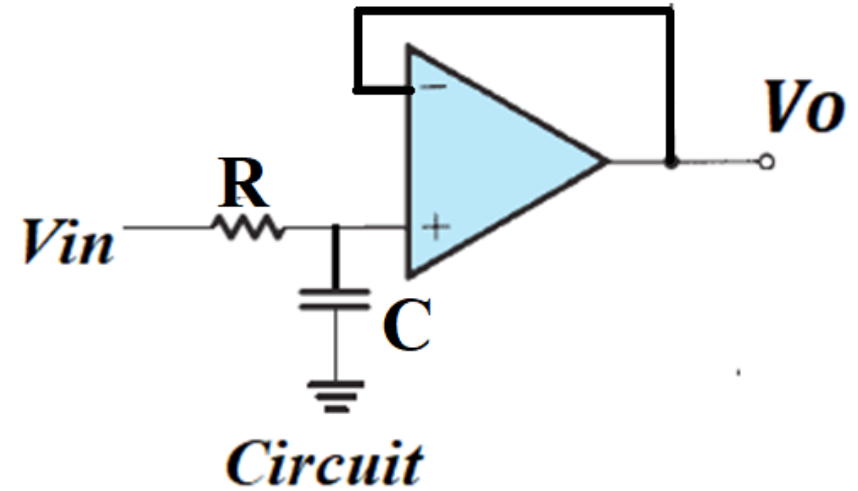
## Design Rules:

- ❑ *Maximum gain  $A_m = 1$*
- ❑ *Cut-Off Frequency  $f_c = \frac{1}{2\pi R C}$*



# Unity Gain Filter ( $A_m=1$ )

## 2. second Order LPF:

**Transfer Function:**

$$A_v(S) = \frac{V_o}{V_{in}} = \frac{1}{\left(\frac{S}{W_c}\right)^2 + 2K\left(\frac{S}{W_c}\right) + 1}$$

**The maximum gain  $A_m$  is unity**

$$W_c = 2\pi f_c$$

**$f_c$  is the cut-off frequency**

**$K$  is the damping ratio**


**$(2K)$  is the coefficient of  $(S)$  in the table**

## Design Rules:

❑ **Maximum gain  $A_m = 1$**

❑ **Cut-Off Frequency  $f_c = \frac{1}{2\pi R C}$**

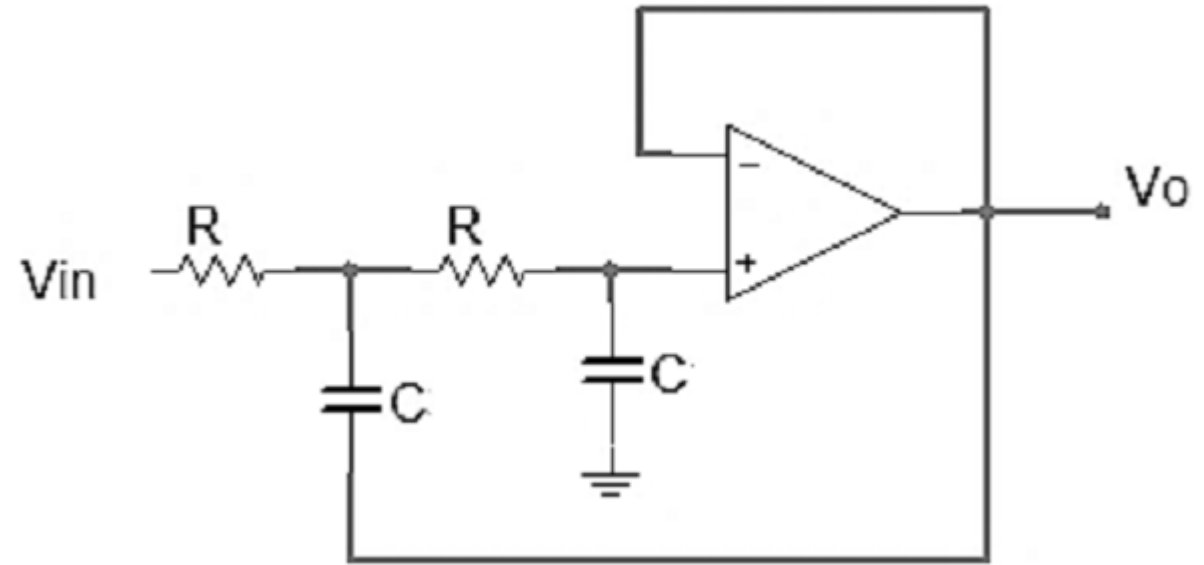❑ **Damping Ratio  $2K = \text{Coefficient of } (S) \text{ in the polynomial } B_n(S).$**




# Unity Gain Filter ( $A_m=1$ )

## Example:

Analyze the unity gain filter shown :

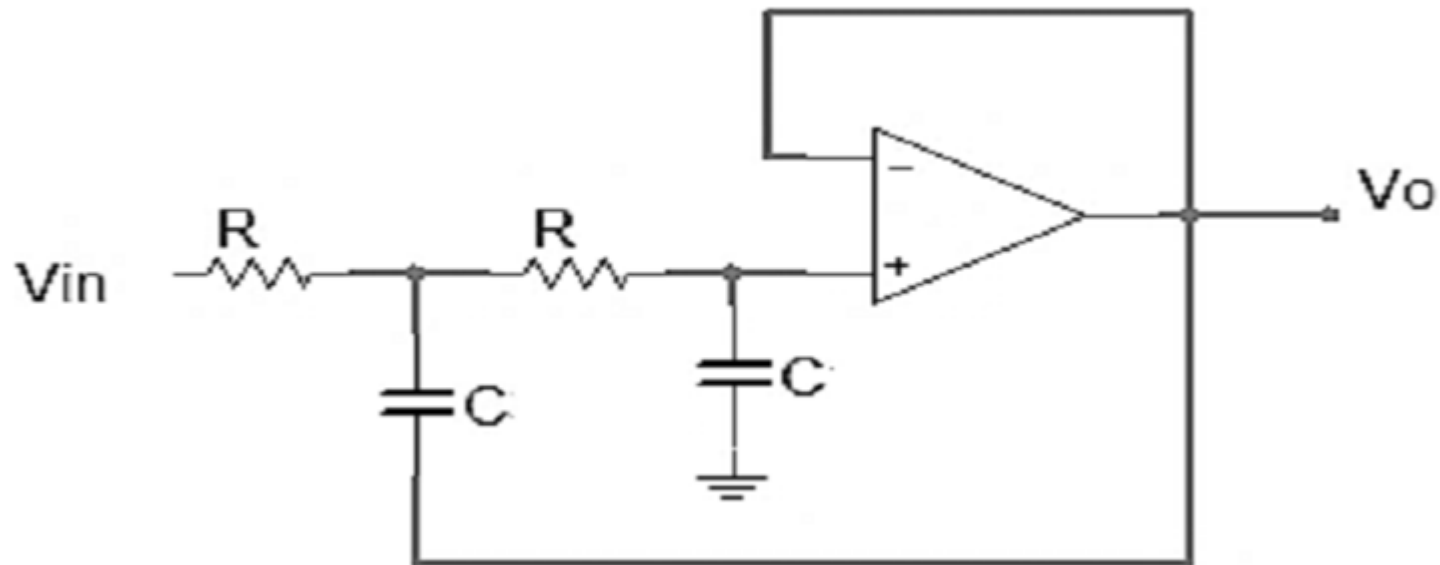1. Derive an expression for the filter transfer function.
2. What is the order and type of the filter?
3. Design the filter cut-off frequency of 100Hz



# Unity Gain Filter ( $A_m=1$ )

## Solution:


1. Derive an expression for the filter transfer function ( $V_o/V_{in}$ ).

$$V_o = I_3 \cdot \frac{1}{sC}$$

$$V_o = \left[ \frac{V_1}{R + \frac{1}{sC}} \right] \cdot \frac{1}{sC}$$

$$\therefore V_o = \frac{V_1}{sCR + 1}$$
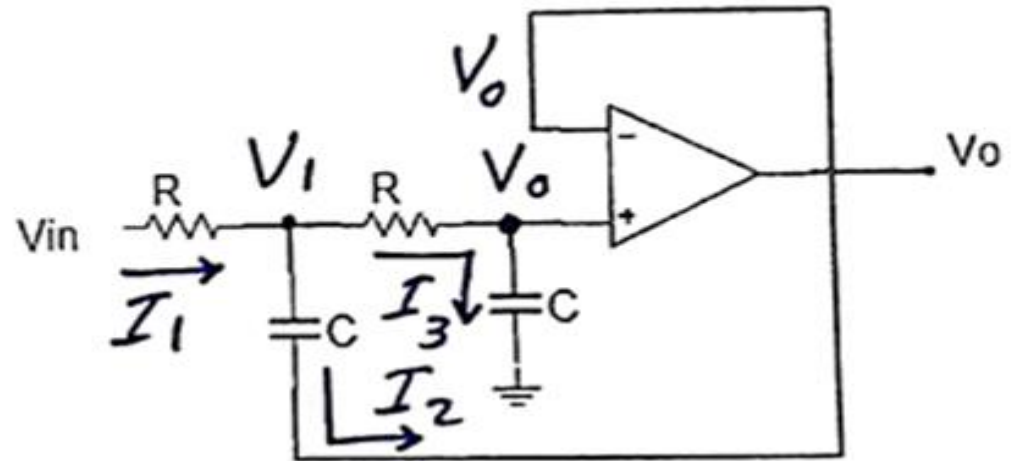
$$\therefore \boxed{V_1 = (sCR + 1) V_o} \quad [1]$$





# Unity Gain Filter ( $A_m=1$ )

$$\frac{V_{in} - V_1}{R} = \frac{V_1 - V_o}{1/sC} + \frac{V_1}{R + \frac{1}{sC}}$$

$$\frac{V_{in} - V_1}{R} = sC V_1 - sC V_o + \frac{sC V_1}{sCR + 1} \quad \times R$$


$$V_{in} - V_1 = sCR V_1 - sCR V_o + \frac{sCR}{sCR + 1} V_1$$

$$V_{in} = [sCR + 1 + \frac{sCR}{sCR + 1}] V_1 - sCR V_o$$

$$V_{in} = [sCR + 1 + \frac{sCR}{sCR + 1}] (sCR + 1) V_o - sCR V_o$$

$$V_{in} = [s^2 C^2 R^2 + 2sCR + 1] V_o - sCR V_o$$
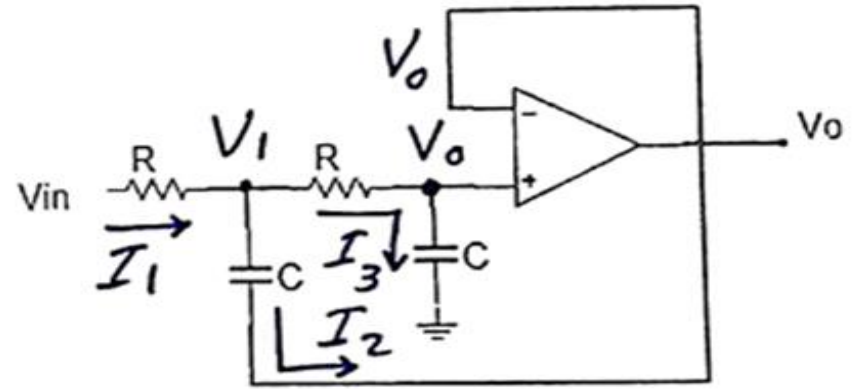
$$V_{in} = [s^2 C^2 R^2 + 2sCR + 1 + sCR - sCR] V_o$$



$$\therefore \frac{V_o}{V_{in}} = \frac{1}{s^2 C^2 R^2 + 2sCR + 1}$$

$$\frac{V_o}{V_{in}} = \frac{1}{\left(\frac{s}{1/RC}\right)^2 + 2\left(\frac{s}{1/RC}\right) + 1}$$

$$\frac{V_o}{V_{in}} = \frac{1}{\left(\frac{s}{\omega_o}\right)^2 + 2\left(\frac{s}{\omega_o}\right) + 1}$$

# Unity Gain Filter ( $A_m=1$ )

(b) What is the order and type of the filter?

Second-Order

LPF

(c) Design the filter for a cut-off frequency of 100KHz.

$$\omega_0 = \frac{1}{RC} = 2\pi f_0$$

$$\therefore f_0 = \frac{1}{2\pi RC}$$

choose  $C = 0.01 \mu F$  →

$$\therefore R = \frac{1}{2\pi (100 \times 10^3) (0.01 \times 10^{-6})}$$

$$R = 159.155 \Omega \rightarrow$$