

Summary of laws for Sheet 5 BJT Trs

Email

nPn transistors

① active mode

$$\rightarrow I_C = \alpha I_E$$

$$\rightarrow I_C = \beta I_B \quad \text{Common emitter Current gain}$$

$$\rightarrow I_E = (1 + \beta) I_B$$

$$\rightarrow I_B = \frac{I_E}{1 + \beta} = \frac{I_C}{\beta}$$

$$\rightarrow I_E = I_B + I_C$$

$$\rightarrow \beta = \frac{\alpha}{1 - \alpha} = \frac{I_C}{I_B} \quad \text{Common base Current gain}$$

$$\alpha = \frac{\beta}{1 + \beta} = \frac{I_C}{I_E}$$

to check active mode

$$V_{CE} > V_{BE} (0.7)$$

② Saturation mode

$$V_{CE} = 0.2$$

$$V_{BE} = 0.7$$

حسب التيار في ال circuit ولهاش قوانين

to check Saturation

$$I_{B \text{ sat}} > I_{B \text{ min (active)}}$$

PnP transistors

① active mode

$$\rightarrow I_C = \alpha I_E = \beta I_B$$

$$\rightarrow I_E = (1 + \beta) I_B$$

$$\rightarrow I_E = I_B + I_C$$

$$\rightarrow I_B = \frac{I_E}{1 + \beta} = \frac{I_C}{\beta}$$

$$\rightarrow \beta = \frac{\alpha}{1 - \alpha} = \frac{I_C}{I_B}$$

$$\rightarrow \alpha = \frac{\beta}{1 + \beta} = \frac{I_C}{I_E}$$

to check active mode

$$V_{EC} > V_{EB} (0.7)$$

② Saturation mode

$$V_{EC} = 0.2$$

$$V_{EB} = 0.7$$

to check Saturation

$$I_{B \text{ sat}} > I_{B \text{ min (active)}}$$

Cut off

$$V_{BE} \text{ or } V_{EB} < 0 (-V_E)$$

من اكانه لا تستعمل في انه off

"Sheet 5"

Eman
①

1. Consider NPN transistor whose base-emitter voltage is 0.76 V at a collector current equals 10 mA. Determine:
- The current will it conduct at $V_{BE} = 0.70$ V.
 - The base-emitter voltage for $I_C = 10 \mu A$.

Sol:-

$$a) I_B = I_S \left(e^{\frac{V_{BE}}{\eta V_T}} - 1 \right)$$

assume $\eta = 1$ $V_T = 0.026$

$$I_C = \beta I_B$$

$$I_C = \beta I_S \left(e^{\frac{V_{BE}}{\eta V_T}} - 1 \right)$$

$$I_{C1} = 10 \text{ mA} \rightarrow V_{BE1} = 0.76$$

$$I_{C2} = ? \rightarrow V_{BE2} = 0.7$$

$$\frac{I_{C1}}{I_{C2}} = \frac{\beta I_S \left(e^{\frac{V_{BE1}}{\eta V_T}} - 1 \right)}{\beta I_S \left(e^{\frac{V_{BE2}}{\eta V_T}} - 1 \right)} = \frac{e^{\frac{0.76}{0.026}} - 1}{e^{\frac{0.7}{0.026}} - 1}$$


$$I_{C2} = \frac{(10^{-2}) \left(e^{\frac{0.76}{0.026}} - 1 \right)}{\left(e^{\frac{0.7}{0.026}} - 1 \right)} = 0.995 \text{ mA}$$

b)

$$\frac{I_{C1}}{I_{C2}} = \frac{e^{\frac{0.7}{0.026}} - 1}{e^{\frac{V_{BE2}}{0.026}} - 1}$$

$$\frac{10 \times 10^{-3}}{10 \times 10^{-6}} = \frac{e^{\frac{0.7}{0.026}} - 1}{e^{\frac{V_{BE2}}{0.026}} - 1}$$

$$V_{BE2} = 0.52 \text{ V}$$

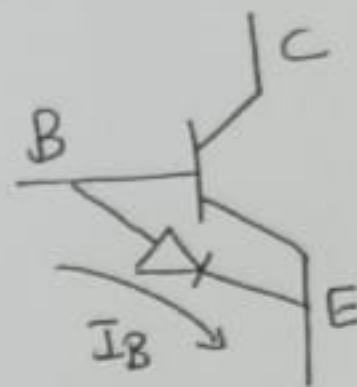

2. In a BJT, the base current is $10\ \mu\text{A}$, and the collector current is $600\ \mu\text{A}$. Find β and α for this transistor.

Sol:-

$$I_B = 10\ \mu\text{A} \quad , \quad I_C = 600\ \mu\text{A}$$

$$\beta = \frac{I_C}{I_B} = \frac{600}{10} = 60$$

$$\alpha = \frac{\beta}{1+\beta} = \frac{60}{61} \approx 0.9836$$

3. Measurement of npn BJT in a particular circuit shows the base current to be $14.46 \mu\text{A}$, the emitter current to be 1.460 mA , and the base-emitter voltage to be 0.7 V . For these conditions, calculate α and β .

Soln -

$$I_B = 14.46 \mu\text{A}$$

$$I_E = 1.460 \text{ mA}$$

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = I_C + I_B$$


$$I_E = (1 + \beta) I_B$$

$$1.460 = (1 + \beta) 14.46 \times 10^{-3}$$

$$\beta \approx 99.968$$

$$\alpha = \frac{\beta}{1 + \beta} = 0.99$$

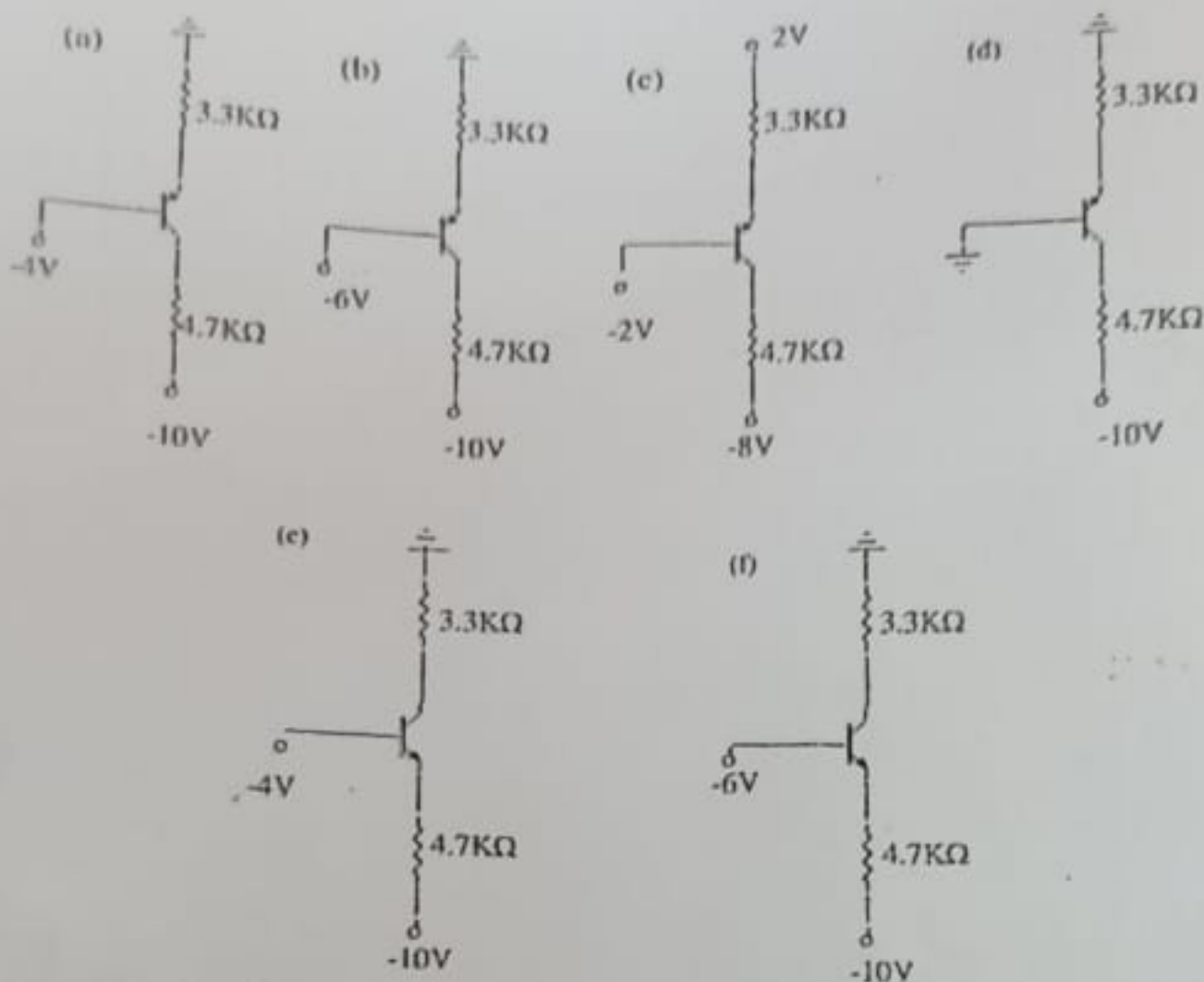4. For the following circuits, find node voltages, V_B , V_C , and currents I_B , I_C , I_E . Use V_{BE} (or V_{EB} for PNP transistor) = 0.7 V and $\beta = 50$.



Sol:-

a] assume the PNP transistor is active

$$V_B = -4 \text{ V}$$

$$V_{EB} = V_E - V_B = 0.7 \text{ V}$$


$$\begin{aligned} V_E &= V_B + 0.7 \\ &= -4 + 0.7 = -3.3 \text{ V} \end{aligned}$$

$$I_E = \frac{0 - V_E}{3.3 \text{ k}} = \frac{3.3}{3.3 \text{ k}} = 1 \text{ mA}$$

$$I_B = \frac{I_E}{1 + \beta} = \frac{1 \text{ mA}}{51} = 19.6 \mu\text{A}$$

$$I_C = \beta I_B = 50 * 19.6 \mu\text{A} = 0.98 \text{ mA}$$
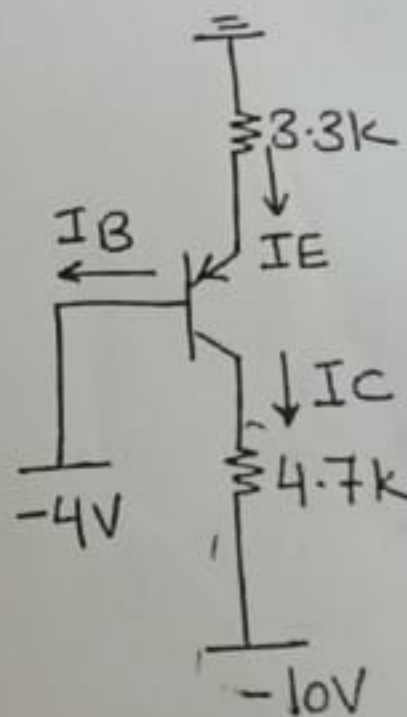
$$V_C = 4.7 \text{ k} * I_C - 10 = -5.392 \text{ V}$$



$$V_{EC} = V_E - V_C$$

$$V_{EC} = -3.3 + 5.392 = 2.1V$$

$V_{EC} > V_{BE}$ assumption true
Tr active

b] assume the PNP tr is active

$$V_B = -6V$$

$$V_{EB} = V_E - V_B = 0.7V$$

$$\begin{aligned} V_E &= V_B + 0.7 \\ &= -6 + 0.7 = -5.3V \end{aligned}$$

$$I_E = \frac{0 - V_E}{3.3k} = \frac{5.3}{3.3k} = 1.606mA \approx 1.61mA$$

$$I_B = \frac{I_E}{1 + \beta} = \frac{1.61mA}{51} = 31.49 \mu A$$

$$I_C = \beta I_B = 50 * 31.49 \mu A = 1.575mA$$

$$V_C = 4.7k * I_C - 10 = -2.59V$$


$$\begin{aligned} V_{EC} &= V_E - V_C \\ &= -5.3 + 2.59 = -2.71V \end{aligned}$$

$V_{EC} < V_{BE}$ then assumption not true
Tr working in Saturation Region

$$\therefore V_{EC} = 0.2$$

$$V_C = V_E - 0.2 = -5.3 - 0.2 = -5.5V$$
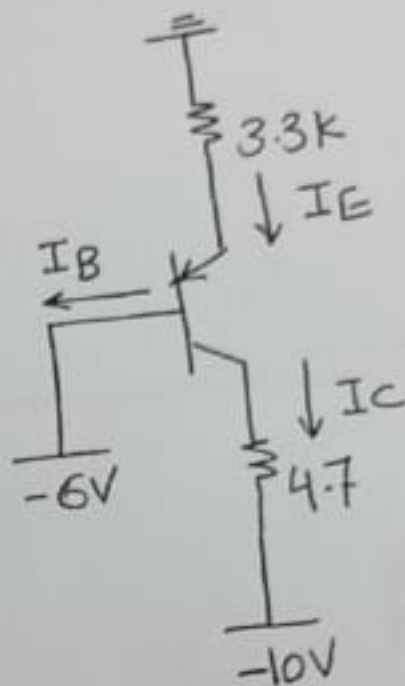
$$I_C = \frac{V_C - (-10)}{4.7k} = \frac{-5.5 + 10}{4.7} = 0.957mA$$



$$I_B = I_E - I_C = 0.648 \text{ mA}$$

Eman
⑥

$$\because I_C < \beta I_B \quad \rightarrow 50 * 0.648$$

$$0.957 \text{ mA} < 32.4 \text{ mA} \quad \text{assumption true}$$

or

$$I_{B_{\text{sat}}} > I_{B_{\text{act}}}$$

$$0.648 \text{ mA} > 31.49 \mu\text{A}$$

X C] assume PNP Tr is active
 $V_B = -2\text{V}$

$$V_{EB} = V_E - V_B = 0.7\text{V}$$

$$\bullet V_E = V_B + 0.7 = -2 + 0.7 = -1.3\text{V}$$

$$\bullet I_E = \frac{2 - V_E}{3.3\text{k}} = \frac{2 + 1.3}{3.3} = 1\text{mA}$$

$$\bullet I_B = \frac{I_E}{1 + \beta} = \frac{1\text{mA}}{51} = 19.6 \mu\text{A}$$


$$\bullet I_C = \beta I_B = 50 * 19.6 \mu\text{A} = 0.98 \text{ mA}$$

$$\bullet V_C = 4.7 \text{ k } I_C - 8 = -3.394\text{V}$$

$$V_{EC} = V_E - V_C = -1.3 + 3.394 = 2.094\text{V}$$

$$V_{EC} > V_{BE}$$

assumption true Tr in active mode

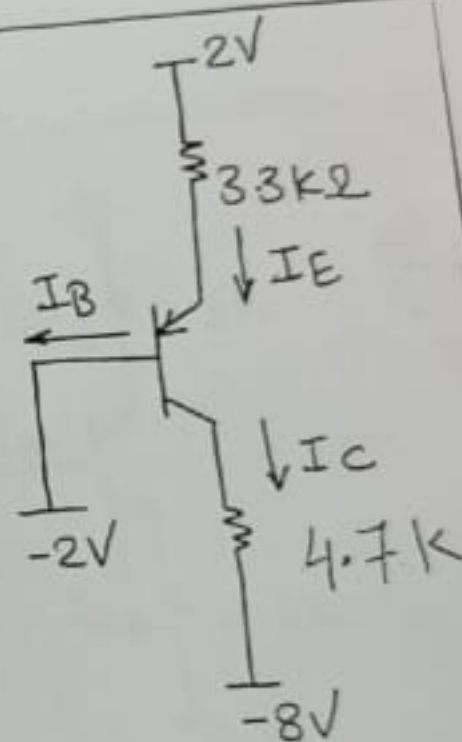


d] $V_B = 0V$

V_E is negative

then EB and CB junction will be off thus the transistor will operate in off mode

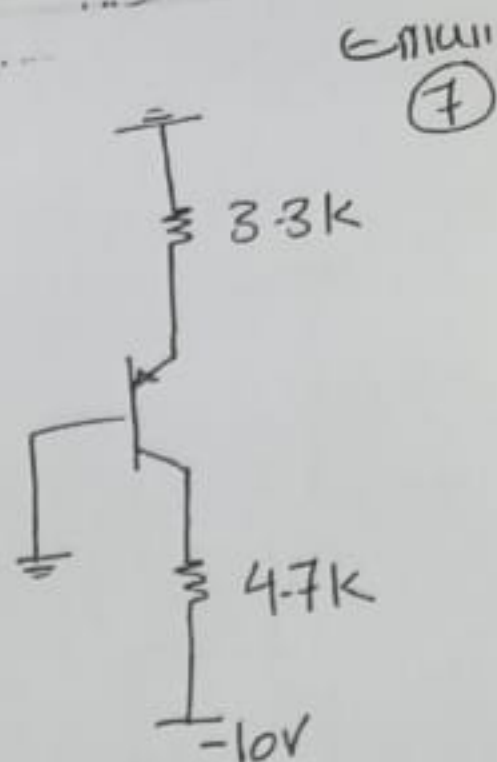- $I_E = 0A$
- $I_B = 0A$
- $I_C = 0A$
- $V_C = -10V$
- $V_E = 0V$



e] Assume NPN Tr is active

$V_B = -4V$

$V_{BE} = V_B - V_E = 0.7V$

• $V_E = V_B - 0.7 = -4 - 0.7 = -4.7V$

• $I_E = \frac{-4.7 + 10}{4.7k} = 1.128mA$


• $I_B = \frac{I_E}{1 + \beta} = \frac{1.128}{51} = 22.11\mu A$

• $I_C = \beta I_B = 50 * 22.11\mu A = 1.106mA$

• $V_C = -3.3k * I_C = -3.65V$

$V_{CE} = -3.65 + 4.7 = 1.05V > V_{BE}$

assumption true Tr active

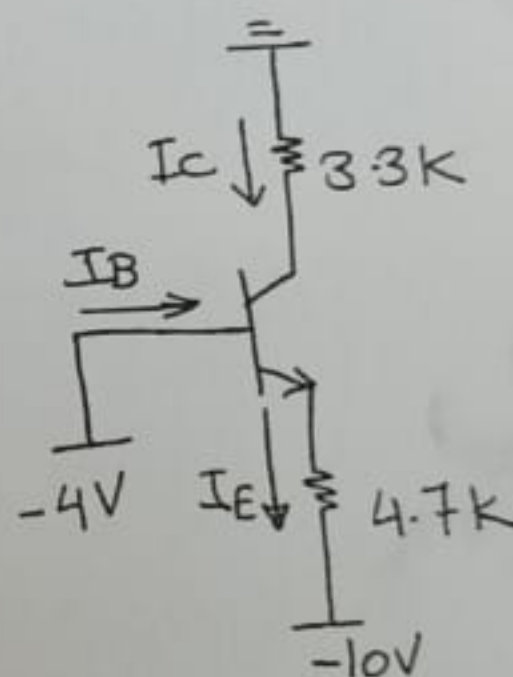

f) assume NPN transistor is active

Eman
⑧

$$V_B = -6V$$

$$V_{BE} = V_B - V_E = 0.7V$$

$$\bullet V_E = V_B - 0.7 = -6 - 0.7 = -6.7V$$

$$\bullet I_E = \frac{-6.7 + 10}{4.7k} = 0.702mA$$


$$\bullet I_B = \frac{I_E}{1+\beta} = \frac{0.702mA}{51} = 13.77\mu A$$

$$\bullet I_C = \beta I_B = 50 \times 13.77 = 0.688mA$$


$$\bullet V_C = -3.3k \times I_C = -2.272V$$

$$V_{CE} = -2.272 + 6.7 = 4.428V$$

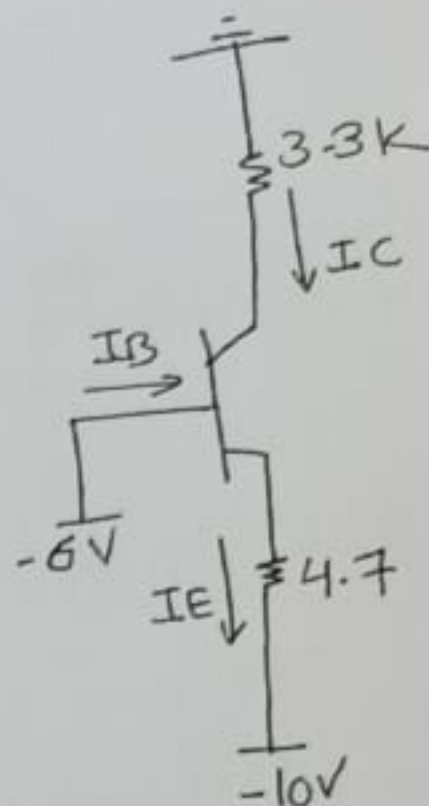$V_{CE} > V_{BE}$ assumption true
Tr active



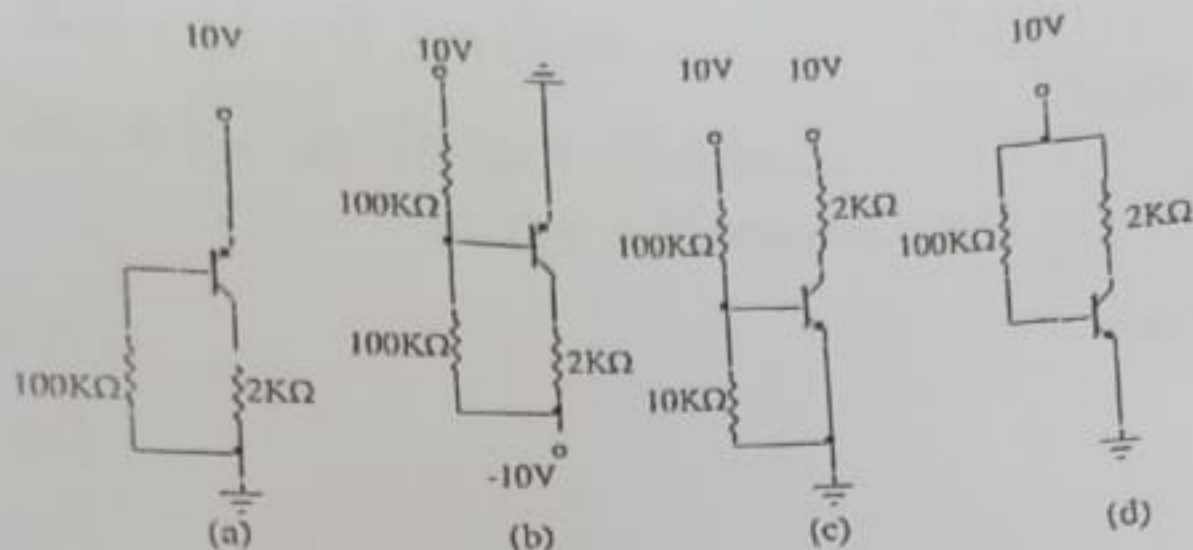5. For the following circuits in which V_{BE} (V_{EB} for PNP transistor) = 0.7 V and $\beta = 10$. Find the transistor's DC operating point?



Soln-

a] assume PNP Tr is active

$$V_E = 10V$$

$$V_{EB} = V_E - V_B = 0.7V$$

$$V_B = V_E - 0.7 = 10 - 0.7 = 9.3V$$

$$I_B = \frac{9.3}{100k} = 93\mu A$$


$$I_C = \beta I_B = 10 * 93\mu A = 0.93mA$$

$$I_E = I_B (1 + \beta) = 93\mu A * 11 = 1.023mA$$

$$V_C = 2k * I_C = 1.86V$$


$$V_{EC} = 10 - 1.86 = 8.14V > V_{BE}$$

assumption true Tr active

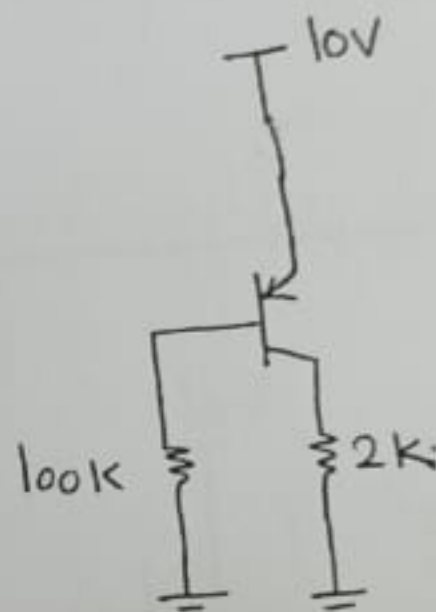

- b] $V_E = 0V$
 V_B is +ve
 the EB and CB junction
 will be off \therefore Tr will operate
 in Cut off mode

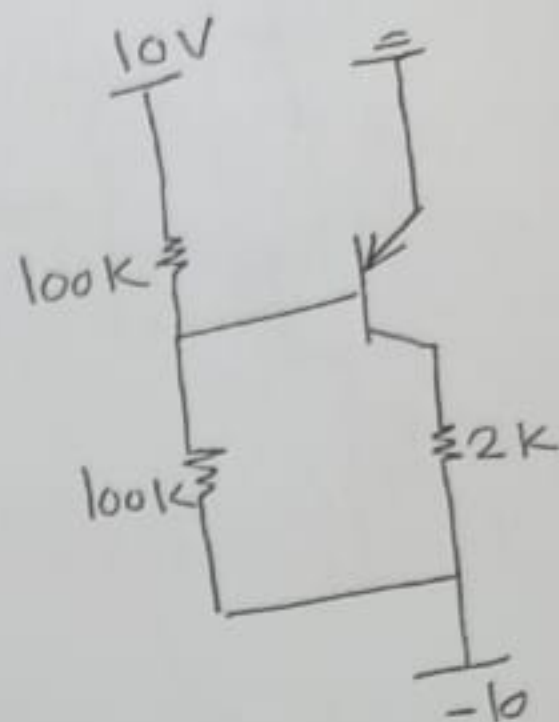- $I_E = 0A$
- $I_B = 0A$
- $I_C = 0A$
- $V_C = -10V$
- $V_E = 0V$



c] assume the NPN Tr is active

• $V_E = 0V$

$V_{BE} = V_B - V_E = 0.7V$

• $V_B = 0.7V$

$I_2 = \frac{0.7}{10k} = 0.07mA$

$I_1 = \frac{10 - 0.7}{100k} = 0.093mA$


• $I_B = I_1 - I_2 = 0.093 - 0.07 = 23\mu A$

• $I_C = \beta I_B$

$= 10 * 23\mu A = 0.023mA$

$V_C = 10 - 2k * I_C = 9.54V$

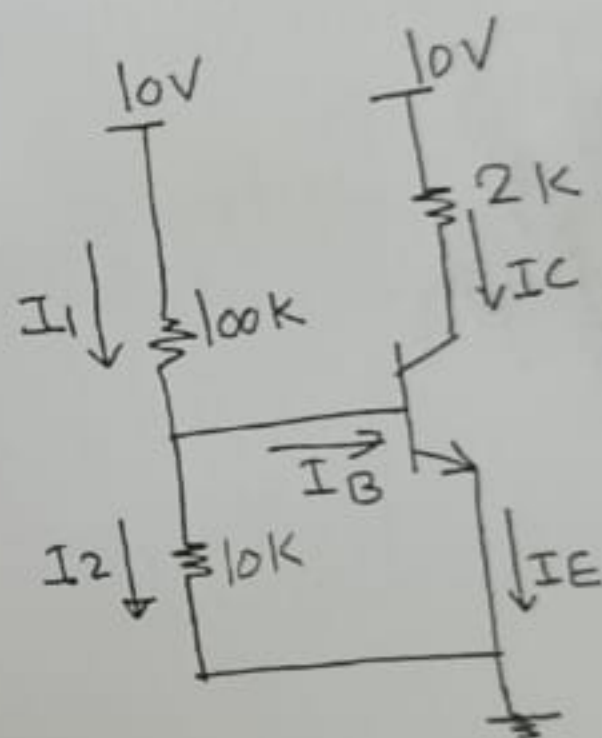$V_{CE} = 9.54 - 0 = 9.54V > V_{BE}$
 assumption true



d] assume NPN Tr is active

$$V_E = 0 \text{ V}$$

$$V_{BE} = V_B - V_E = 0.7 \text{ V}$$

$$V_B = 0.7 \text{ V}$$

$$I_B = \frac{10 - 0.7}{100 \text{ k}} = 93 \mu\text{A}$$


$$I_C = \beta I_B = 0.93 \text{ mA}$$

$$I_E = (1 + \beta) I_B = 1.023 \text{ mA}$$

$$V_C = 10 - 2 \text{ k} \times I_C = 8.14 \text{ V}$$


$$V_{CE} = 8.14 - 0 = 8.14 \text{ V} > V_{BE}$$

assumption true

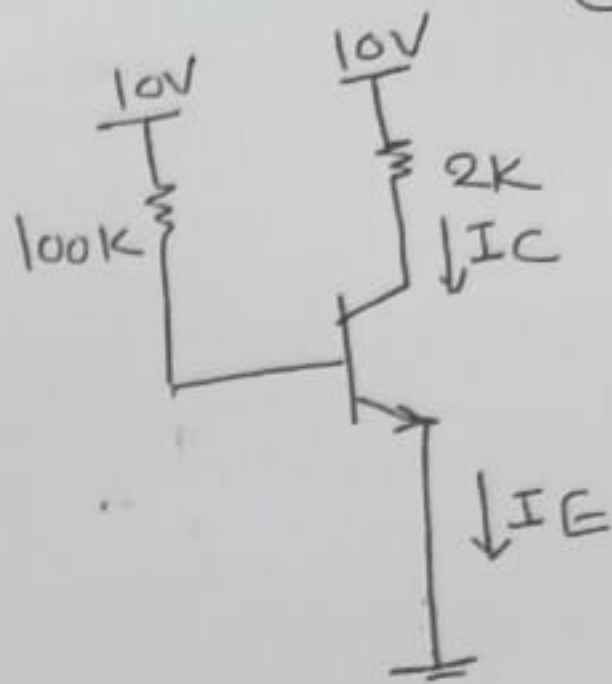

Eman
11

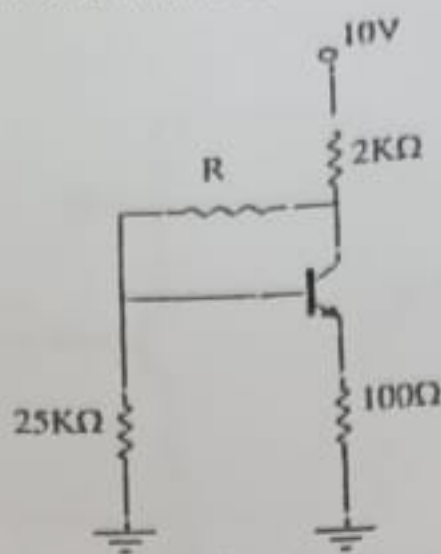6. If $\alpha = 0.97$ and $V_{BE} = 0.7V$, find R in the circuit shown if $I_E = 2mA$.



Sol:-

x assume tr in active mode

$$I_C = \alpha I_E = 0.97 \times 2 = 1.94mA$$

$$I_B = I_E - I_C = 2 - 1.94 = 0.06mA$$

$$V_E = I_E R_E = 100 \times 2 \times 10^{-3} = 0.2V$$

$$V_B = V_{BE} + V_E = 0.7 + 0.2 = 0.9V$$

$$I_2 = \frac{V_B}{25K\Omega} = 0.036mA$$

$$I_R = I_B + I_2 = 0.06 + 0.036 = 0.096mA$$


$$I_1 = I_R + I_C = 0.096 + 1.94 = 2.036mA$$

$$V_C = V_{CC} - I_1(2) = 10 - (2.036 \times 2) = 5.928V$$


$$V_{CE} = V_C - V_E = 5.928 - 0.2 = 5.728V > V_{BE}$$

assumption true
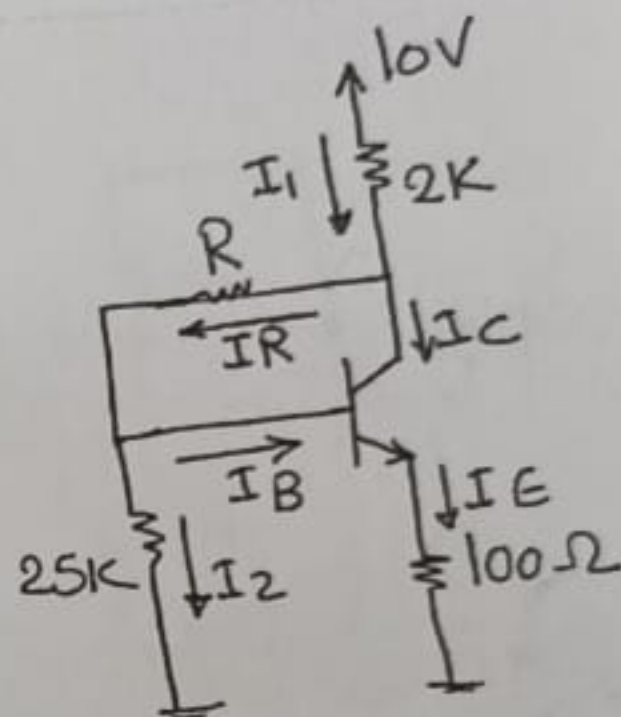
$$R = \frac{V_C - V_B}{I_R} = \frac{5.028}{0.096} = 52.375 k\Omega$$



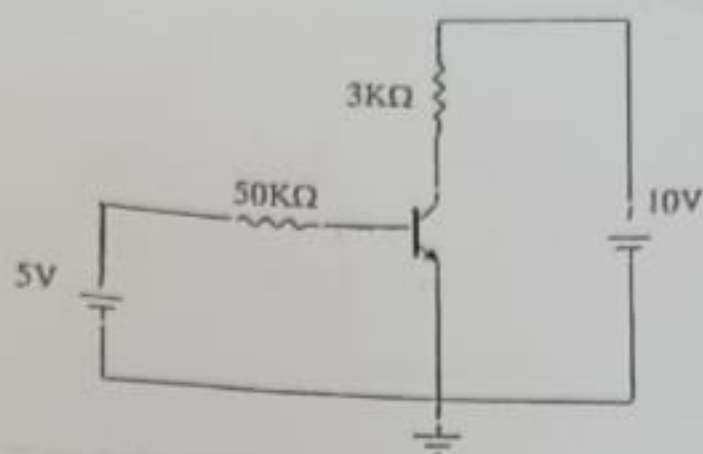7. In the figure show below, if $\beta=100$, determine whether or not the silicon transistor is in saturation and find I_B and I_C . Repeat with the $2K\Omega$ emitter resistance is added.



Solⁿ-

assume Tr in Saturation


$$V_{CE} = 0.2V$$

$$V_{BE} = 0.7V$$

i/p 100P

$$5 = I_B(50) + V_{BE}$$
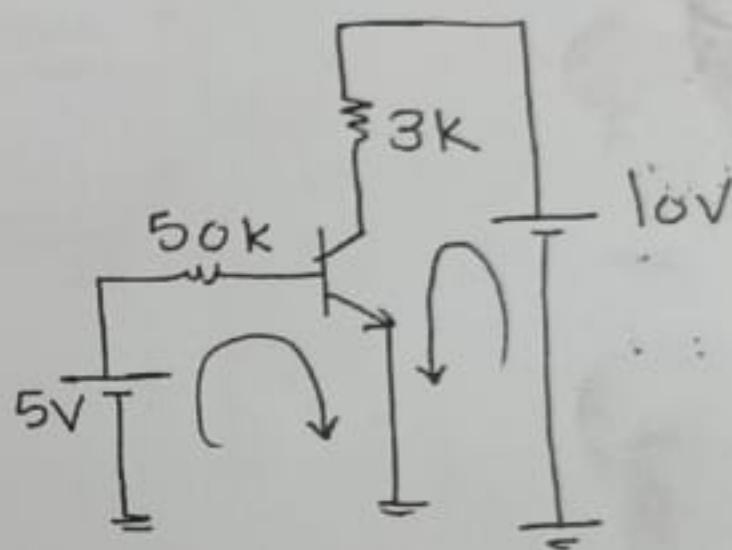
$$I_{B(sat)} = \frac{5 - 0.7}{50 \times 10^3} = 8.6 \times 10^{-5} A = 86 \mu A = 0.086 mA$$



o/p 100P

$$10 - I_C(3) - V_{CE} = 0$$

$$I_C = \frac{10 - 0.2}{3 \times 10^3} = 3.26 \times 10^{-3} = 3.26 mA$$


$$I_{B(min)} = \frac{I_{C(sat)}}{\beta} = \frac{3.26}{100} = 0.0326 mA$$

$$I_{B(min) \text{ active}} < I_{B(sat)}$$

assumption true
Tr in saturation

اقل نیاز
بجایه نیاز
act نیاز

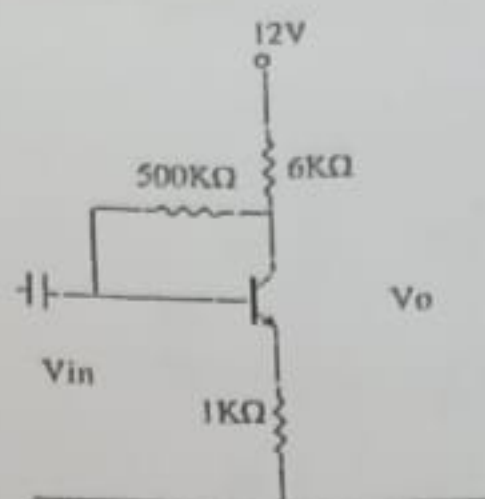8. In the collector base bias circuit shown in figure, calculate the quiescent collector voltage when $\beta=100$.



Solⁿ - assume tr active

i/p loop

$$12 - 6 I_E - 500 I_B - 0.7 - 1 I_E = 0$$

$$12 - 0.7 = 7 I_E + 500 I_B$$

$$= 7 (1 + \beta) I_B + 500 I_B$$

$$11.3 = [7 (101) + 500] I_B$$

$$I_B = 9.36 \mu A$$

$$I_C = \beta I_B = 100 \times 9.36 = 0.936 mA$$


$$I_E = (1 + \beta) I_B = 0.946 mA$$

o/p loop


$$12 - (6 + 1) I_E = V_{CE}$$

$$= 5.38 V > V_{BE} \text{ assumption true}$$
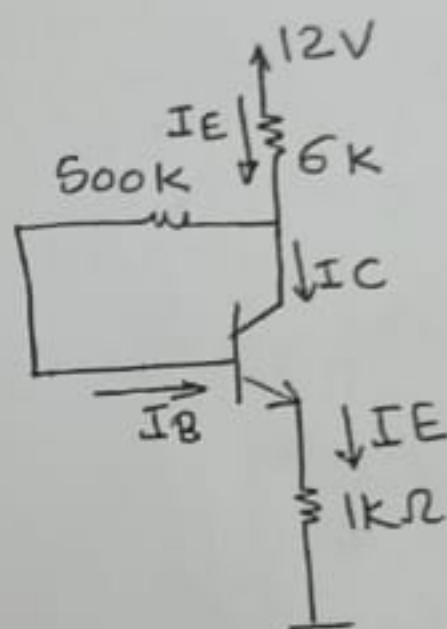
$$V_C = V_{CE} + I_E R_E = 5.38 + 0.946 = 6.32 V$$



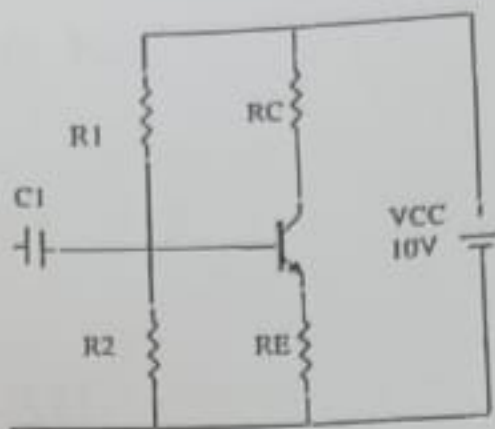9. In the circuit shown in figure, determine the unknown parameters that satisfy the bias condition to be $V_{CE} = 5V$ and $I_C = 1mA$ with $\beta = 50$.



Solⁿ—

$$I_B = \frac{I_C}{\beta} = \frac{1mA}{50} = 0.02mA$$

$$I_E = I_B + I_C = 1.02mA$$

O/P loop

$$10 - 5 - I_C R_C - I_E R_E = 0$$

$$5 = R_C + 1.02 R_E$$

i/P loop

$$V_{th} - 0.7 = R_{th}(0.02) + R_E(1.02)$$



$$R_E = 0.5k$$

$$R_{th} = 100k$$

O/P loop

$$5 = R_C + 1.02 \times 0.5$$

$$R_C = 4.5k\Omega$$

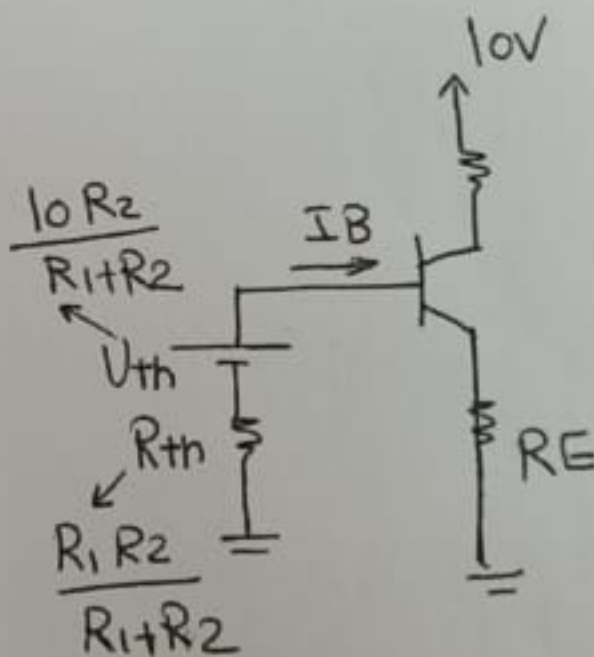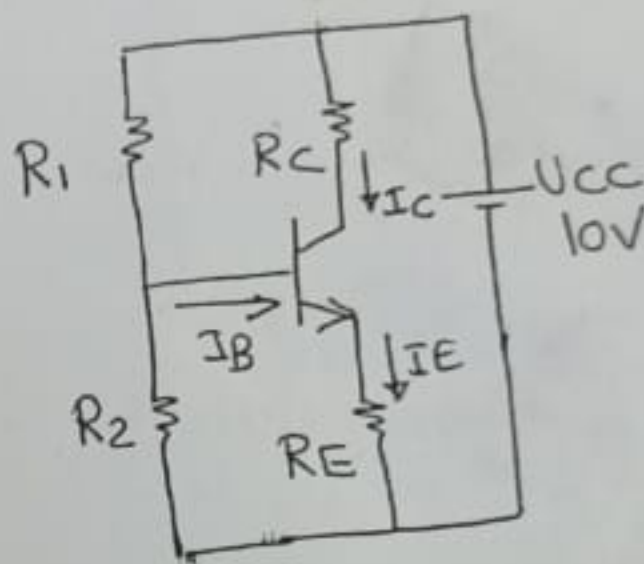

i/P 100 p

(16)

$$\frac{10 R_2}{R_1 + R_2} - 0.7 = 100 \times 0.02 + 0.5 \times 1.02$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = 100 \text{ k}$$

$$V_{th} = \frac{10 R_2}{R_1 + R_2} = 3.21 \text{ V}$$

$$\frac{R_2}{R_1 + R_2} = 0.321$$

$$R_{th} = 0.321 R_1 = 100 \text{ k}$$


$$R_1 = 311.5 \text{ k}\Omega$$

$$0.321(R_1 + R_2) = R_2$$

$$0.321(311.5 + R_2) = R_2$$

$$R_2 = 147.3 \text{ k}\Omega$$

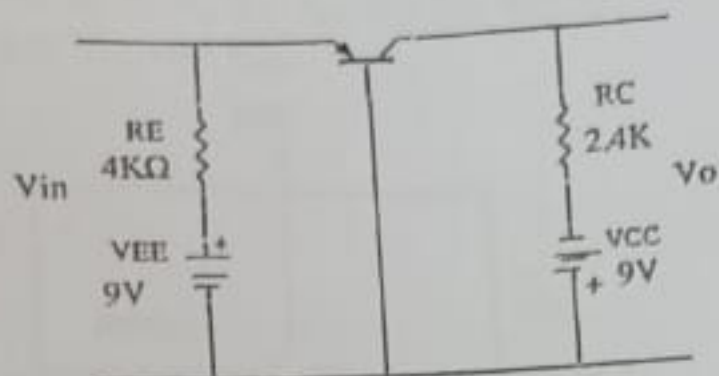10. Calculate the currents I_E and I_C for the circuit shown in figure, if $\beta = 150$.



Sol:-

assume Tractive

i/P loop

$$9 - 0.7 = 4 I_E$$

$$I_E = 2.075 \text{ mA}$$

$$I_B = \frac{I_E}{1 + \beta} = 0.014 \text{ mA}$$


$$I_C = \beta I_B = 2.061 \text{ mA}$$

o/P loop

$$9 - 2.4 I_C = V_{CB}$$


$$V_{CB} = 4.053 > V_{BE} \text{ active}$$
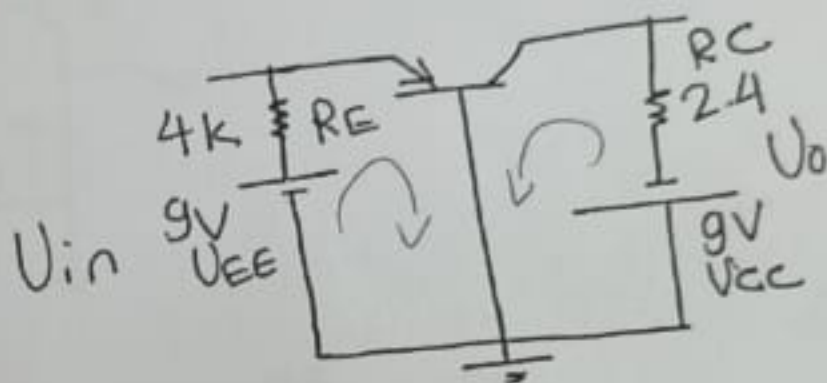
$$\therefore I_C = 2.061, \quad I_E = 2.075 \text{ mA}$$



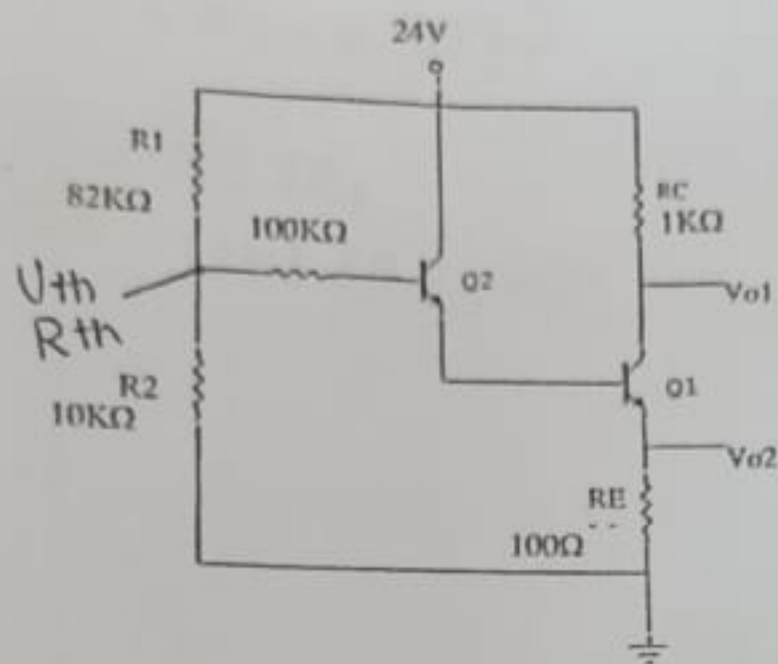11. For the circuit shown, transistor Q1 and Q2 operate in the active region with $V_{BE1} = V_{BE2} = 0.7V$, $\beta_1 = 100$, $\beta_2 = 50$.

- Find the currents I_{B2} , I_{B1} , I_{C2} , I_{C1} , I_{E1} , and I_{E2} .
- Find the voltages V_{O1} and V_{O2} .



Solve-

$$V_{th} = \frac{24 \times 10}{10 + 82} = 2.61V$$

$$R_{th} = \frac{82 \times 10}{82 + 10} = 8.91k$$

i/P loop

$$V_{th} - I_{B2}(100 + 8.91) - 0.7 - 0.7 - 101 \times 51 \times 0.1 \times I_{B2} = 0$$

$$I_{B2} = 1.94 \mu A$$


$$I_{C2} = \beta_2 I_{B2} = 0.097 mA$$

$$I_{E2} = (1 + \beta_2) I_{B2} = 0.099 mA$$

$$(1 + \beta_1) I_{B1} = I_{E1}$$

$$(1 + \beta_1)(1 + \beta_2) I_{B2} = (1 + \beta_1) I_{E2}$$

$$I_{E2} = I_{B1} = 0.099 mA$$

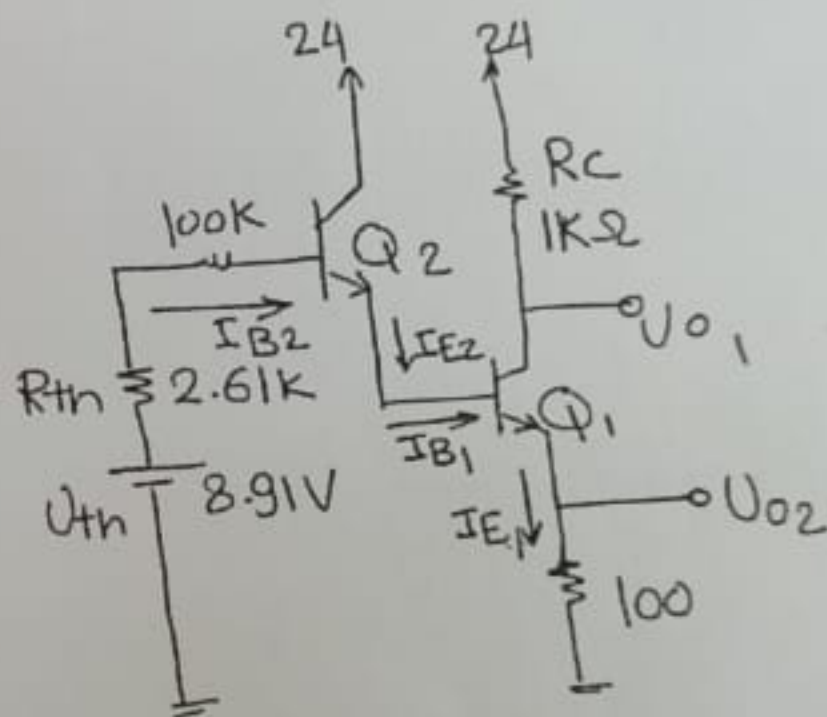

$$I_{C1} = \beta_1 I_{B1} = 9.89 \text{ mA}$$


$$I_{E1} = (1 + \beta_1) I_{B1} = 9.99 \text{ mA}$$

$$V_{O2} = I_{E1} \times 100 = 0.999 \text{ V}$$

$$\begin{aligned} V_{O1} &= 24 - R_C I_{C1} \\ &= 24 - (1\text{k}) (9.89 \text{ mA}) = 14.11 \text{ V} \end{aligned}$$

Eman
(19)

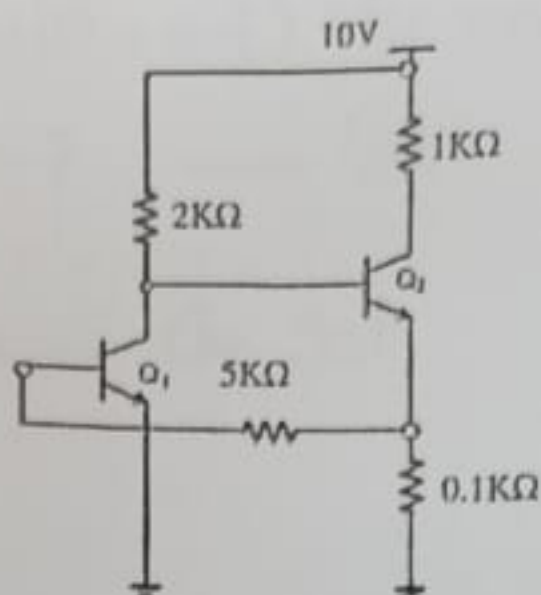12. Evaluate the voltages at all nodes and the currents through all branches. What is the DC mode of operation for the transistors? Assume: $V_{BE} = 0.7 \text{ V}$ $\beta = 50$.



Sol/g-

$$\rightarrow I_2 = I_{C1} + I_{B2} \\ = \beta I_{B1} + I_{B2}$$

$$\rightarrow I_{E2} = I_1 + I_{B1} \\ = (1 + \beta) I_{B2}$$

loop ①

$$10 - (\beta I_{B1} + I_{B2})(2) - 0.7 - (I_{E2} - I_{B1})(0.1) = 0$$

$$10 - (\beta I_{B1} + I_{B2})(2) - 0.7 - ((\beta + 1)I_{B2} - I_{B1})(0.1) = 0$$

$$10 - 2\beta I_{B1} - 2I_{B2} - 0.7 - (0.1)\beta I_{B2} - (0.1)I_{B2} + (0.1)I_{B1} = 0$$


$$9.3 + (-2\beta + 0.1)I_{B1} + (-2 - 0.1\beta - 0.1)I_{B2} = 0$$

$$99.9 I_{B1} - 7.1 I_{B2} = -9.3 \rightarrow \text{①}$$

loop ②

$$0.7 + 5 I_{B1} - 0.1 I_1 = 0$$
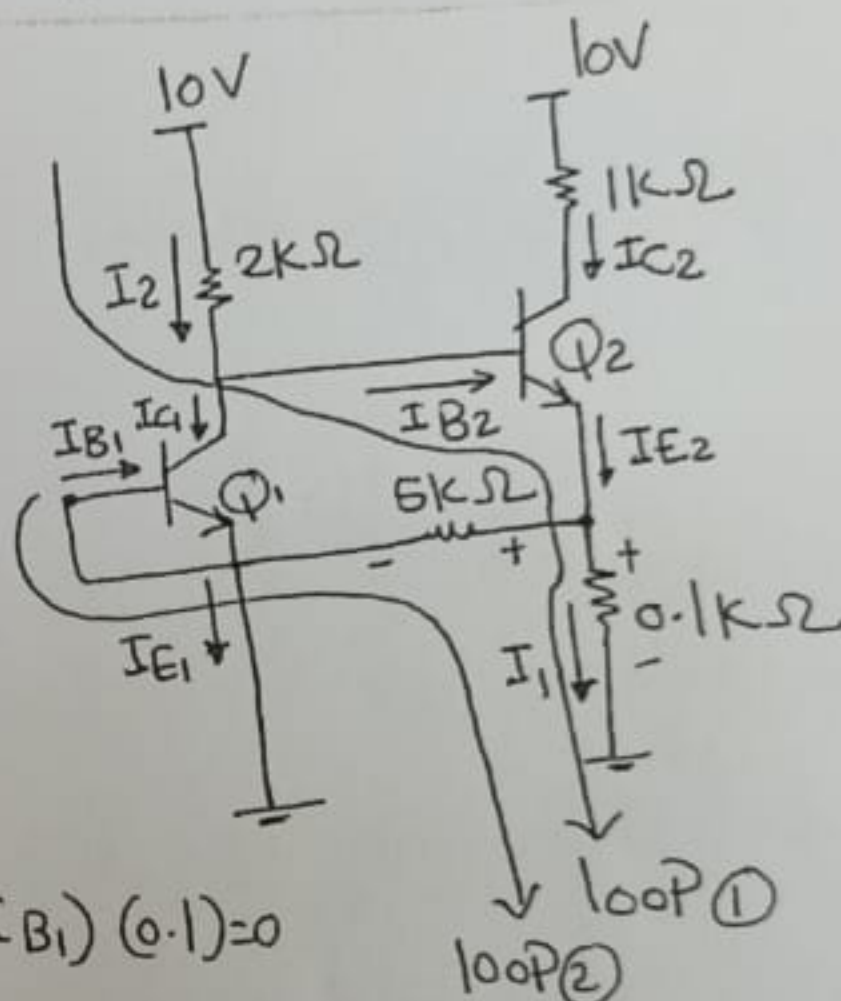
$$0.7 + 5 I_{B1} - 0.1((\beta + 1)I_{B2} - I_{B1}) = 0$$



$$0.7 + 5I_{B1} - 0.1\beta I_{B2} - 0.1I_{B2} + 0.1I_{B1} = 0$$

$$0.7 + (5 + 0.1)I_{B1} + (-0.1\beta - 0.1)I_{B2} = 0$$

$$5.1I_{B1} - 5.1I_{B2} = -0.7 \rightarrow (2)$$

Solving (1) and (2) we can get

$$I_{B1}, I_{B2}$$

$$I_{E1} = (\beta + 1)I_{B1}$$

$$I_{C1} = (\beta)I_{B1}$$

$$I_{E2} = (\beta + 1)I_{B2}$$

$$I_{C2} = (\beta)I_{B2}$$

$$I_1 = I_{E2} - I_{B1}$$

$$I_2 = I_{C1} + I_{B1}$$

$$V_{C1} = 10 - 2I_2$$

$$V_{B1} = V_{BE}$$

$$V_{E1} = \text{Zero}$$

$$V_{C2} = 10 - 2I_{C2}$$

$$V_{B2} = V_{BE} + 0.1I_1$$

تم بحمد الله