
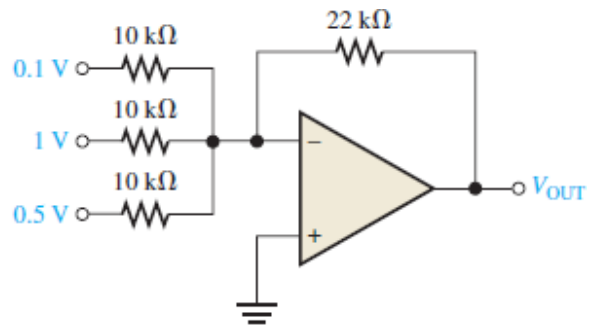


Electronic Circuits


Op- Amp

Sheet 2

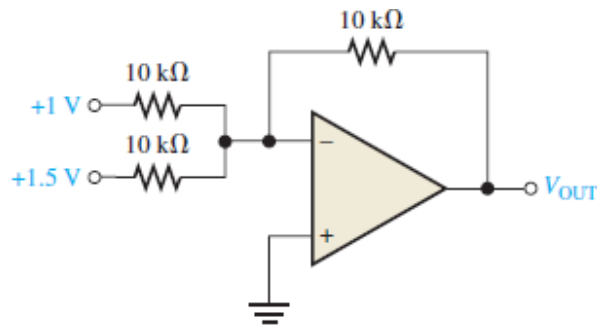
1. Determine the output voltage for each circuit shown.



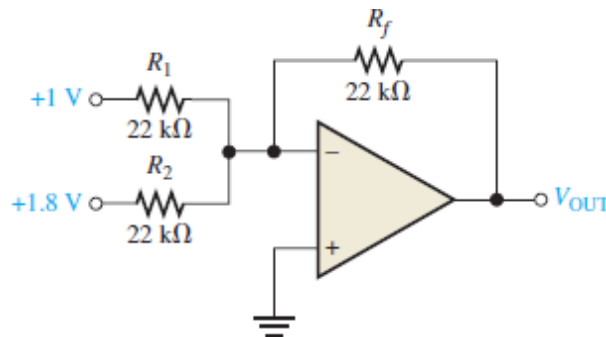2. For the circuit shown, determine V_{out} . Also, find the value of R_f necessary to produce an output that is five times the sum of the inputs in the shown circuit.




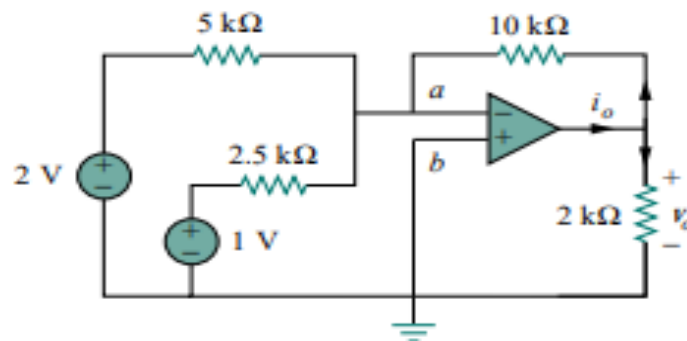3. Calculate V_o and i_o for the following Op-amp circuit.




4. Design an inverting op-amp circuit to form the weighted sum V_o of two inputs V_1 and V_2 . It is required that $V_o = -(V_1 + 5V_2)$. Choose values for R_1 , R_2 , and R_F so that for a maximum output voltage of 10V the current in the feedback resistor will not exceed 1 mA.

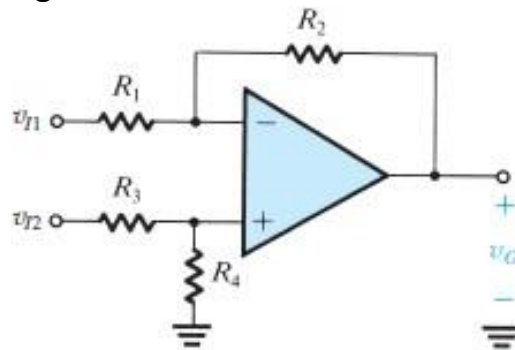5. Design Op-amp circuit with inputs V_1 and V_2 such that $V_o = -5V_1 + 3V_2$ using:
- Only one Op-amp.
 - More than one Op-amp.
6. Consider the difference-amplifier shown, for the case $R_1 = R_3 = 2 \text{ k}\Omega$ and $R_2 = R_4 = 200 \text{ k}\Omega$.
- Find the value of the differential gain A_d .
 - Find values for the resistances in the circuit so that the circuit behaves as a difference amplifier with an input resistance of $20 \text{ k}\Omega$ and a gain of 10.



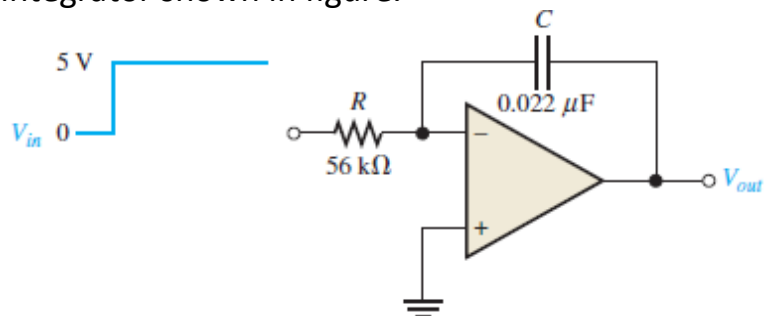7. Determine the rate of change of the output voltage in response to the step input to the integrator shown in figure.



8. A triangular waveform is applied as an input to the circuit shown. Determine what the output should be and sketch its waveform in relation to the input.

