
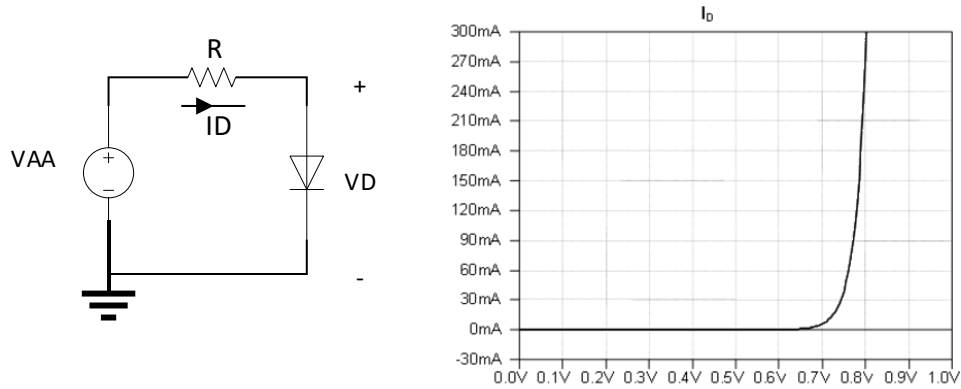


**Electronic Devices**  
**Sheet #2**

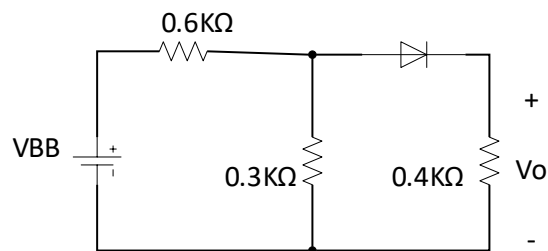1. (a) The resistivities of two sides of a step-graded germanium diode are  $2\Omega\cdot\text{cm}$  (p side) and  $1\Omega\cdot\text{cm}$  (n side). Calculate the value  $V_o$  the potential barrier at room temperature.  
(b) Repeat part a for a silicon p-n junction.
2. (a) Sketch the linear plots of carrier concentration vs. distance for an abrupt silicon junction if  $N_D=10^{15}$  atoms/ $\text{cm}^3$  and  $N_A=10^{16}$  atoms/ $\text{cm}^3$ . Give numerical values for the ordinates. Label the n, p, and depletion region.  
(b) Sketch the potential barrier as a function of a function of distance for this case.
3. (a) Consider a step graded germanium p-n junction with  $N_D=10^3 N_A$ , Corresponding to 1 acceptor atom per  $10^8$  germanium atoms. Calculate the contact difference of potential  $V_o$  at room temperature.  
(b) Repeat part (a) for a silicon p-n junction.
4. If the reverse saturation current in a p-n junction silicon diode is  $1\text{nA}$ , what is the applied voltage for a forward current of  $2.5\mu\text{A}$ ?
5. (a) Calculate the factor by which the reverse saturation current of a germanium diode is multiplied when the temperature is increased from  $25$  to  $80^\circ\text{C}$ .  
(b) Repeat part (a) for silicon diode over the range  $25$  to  $125^\circ\text{C}$ .
6. Reverse biased diodes are frequently employed as electrically controllable variable capacitors. The junction capacitance of an abrupt junction diode is  $20\text{pf}$  at  $5\text{V}$  compute the decrease in capacitance for  $1.0\text{V}$  increase in bias, assuming that potential barrier =  $0.65\text{V}$ .
7. (a) A silicon diode at room temperature conducts  $1\text{mA}$  at  $0.7\text{V}$ . Given that voltage increase to  $0.8\text{V}$ , calculate the diode current. Assume  $\eta = 2$ .  
(b) Calculate the reverse saturation current.  
(c) Repeat (a) for  $\eta = 1$ .
8. A silicon diode with shown volt-ampere characteristic used in the following circuit with  $V_{AA}=6\text{V}$  and  $R=100\Omega$ .  
(a) Determine the diode current and voltage.  
(b) If  $V_{AA}$  is decreased to  $3\text{V}$  what must the new value of  $R$  be if the diode current is to remain at the value in (a)?




9. The circuit shown uses an ideal diode. Find  $V_o$  given  $V_{BB}=9V$ .



10. For the circuit shown, the cut-in voltage of the diode is  $0.6\text{ V}$  and the drop across a conducting diode is  $0.7\text{ V}$ . Calculate  $V_o$  for the following input voltages and indicate the state of each diode (ON or OFF). Justify your assumptions about the state of each diode.

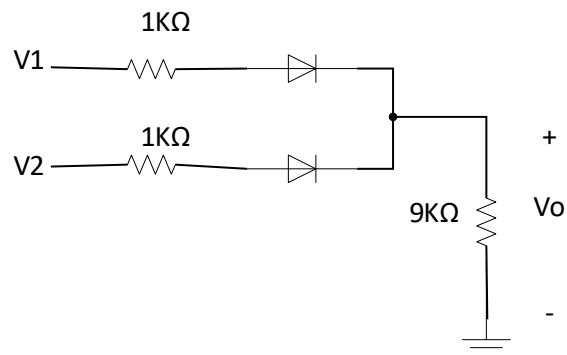- (a)  $V_1=0\text{ V}$ ,  $V_2=0\text{ V}$ .
- (b)  $V_1=5\text{ V}$ ,  $V_2=0\text{ V}$ .
- (c)  $V_1=0\text{ V}$ ,  $V_2=5\text{ V}$ .
- (d)  $V_1=5\text{ V}$ ,  $V_2=5\text{ V}$ .



11. In the shown circuit, the diode  $D_1$  is germanium with offset voltages  $0.3\text{ V}$  and an incremental resistance  $30\text{ ohms}$  whereas  $D_2$  is silicon with offset voltage  $0.6\text{ V}$  and incremental resistance  $18\text{ ohms}$ . Find the diode current if  $R=10\text{ k-ohms}$ .

