


Sheet P.1.1

Sunday, November 6, 2022 9:21 AM

The differential amplifiers shown in the following three figures use two matched BJT's Q_1 and Q_2 with $\beta = 100$ and $V_A = \infty$.

Calculate:

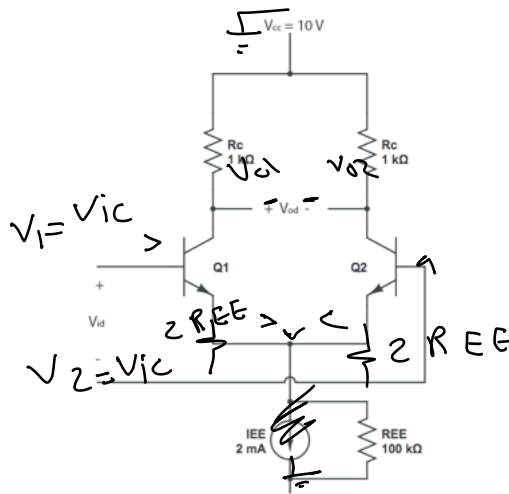
- The value of collector current for Q_1 and Q_2 .
- The differential mode gain A_{dm} .
- The common mode gain A_{cm} .
- The CMRR in decibel (dB).



$$I_{E1} = I_{E2} = 1 \text{ mA}$$

$$I_{C1} = I_{C2} = I_{E1} \frac{\beta}{1+\beta} = \checkmark \quad I_b = \frac{I_c}{\beta} = \checkmark$$

for the left Half of the Circuit

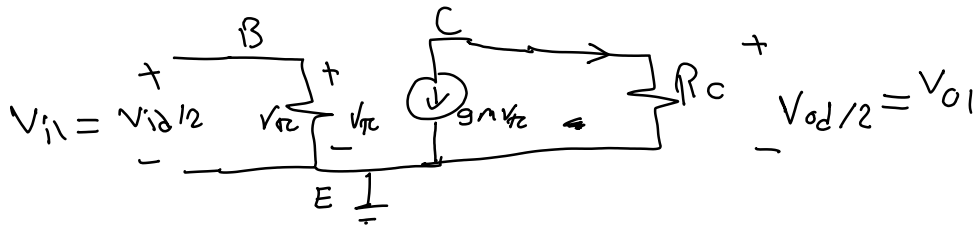

$$\frac{V_{o1}}{V_{i1}} = ??$$

$$r_{\pi} = \frac{V_T}{I_b} = \frac{26 \text{ mV}}{I_b} = \checkmark$$

$$g_m = \frac{\beta}{r_{\pi}} \checkmark \rightarrow \beta = g_m r_{\pi}$$

$$r_o = \frac{V_A}{I_C} = \infty$$

$$V_{o1} = -g_m V_{\pi} R_C \rightarrow (1)$$

$$V_{\pi} = V_{i1} \rightarrow (2)$$

$$V_{o1} = -g_m V_{i1} R_C$$

$$\frac{V_{o1}}{V_{i1}} = -g_m \underline{(R_C)} = \frac{V_{od} R_C}{V_{id} R_C} = \frac{V_{od}}{V_{id}} = A_{dm}$$


$$V_{od} = V_{o1} - V_{o2}$$


$$= \frac{V_{id}}{2} A - \left(-\frac{V_{id}}{2}\right) A$$

$$= \left(\frac{V_{id}}{2} + \frac{V_{id}}{2}\right) A$$

$$V_{od} = V_{id} A$$

$$A = \frac{V_{od}}{V_{id}}$$

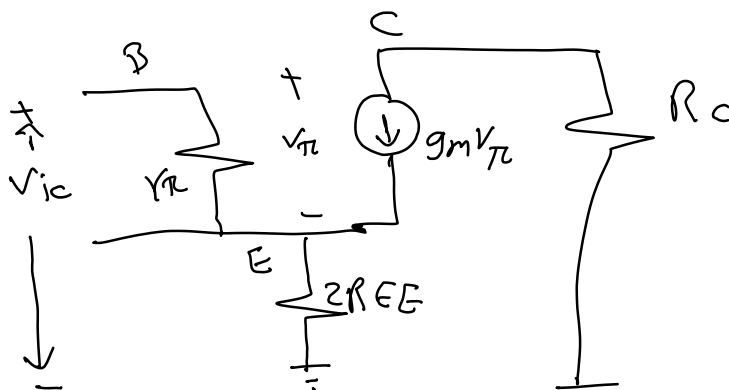

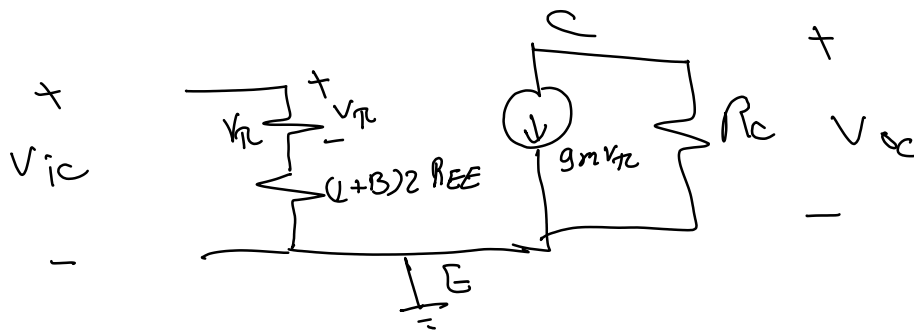

$$V_{oc} = -g_m V_{\pi} R_c$$

$$V_{\pi} = V_{ic} \frac{r_{\pi}}{r_{\pi} + 2R_{EE}(1+B)}$$

$$V_{oc} = -g_m R_c V_{ic} \frac{r_{\pi}}{r_{\pi} + 2R_{EE}(1+B)}$$

$$\frac{V_{oc}}{V_{ic}} = \frac{-g_m R_c r_{\pi}}{r_{\pi} + 2R_{EE}(1+B)} = A_{cm} = \frac{-R_c}{2R_{EE}}$$

$$= \frac{-\frac{B R_c}{B}}{\frac{r_{\pi}}{B} + \frac{2R_{EE}(1+B)}{B}}$$

$$\therefore 2R_{EE} \gg \frac{r_{\pi}}{B}$$

$$A_{cm} = \frac{-R_c}{2R_{EE}} \uparrow$$

$$CMRR|_{dB} = 20 \log \left(\frac{A_{cm}}{A_{cm}} \right)$$



Sheet P.1.2

Sunday, November 6, 2022 9:23 AM

The differential amplifiers shown in the following three figures use two matched BJT's Q_1 and Q_2 with $\beta = 100$ and $V_A = \infty$.


Calculate:

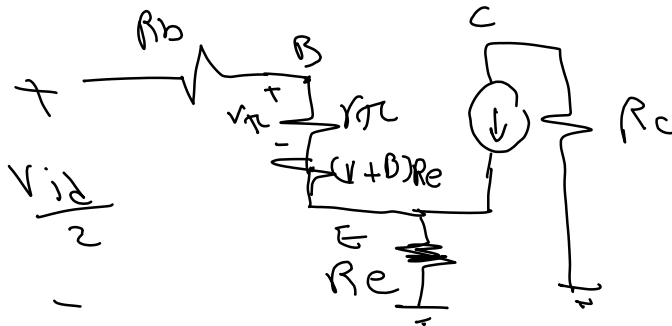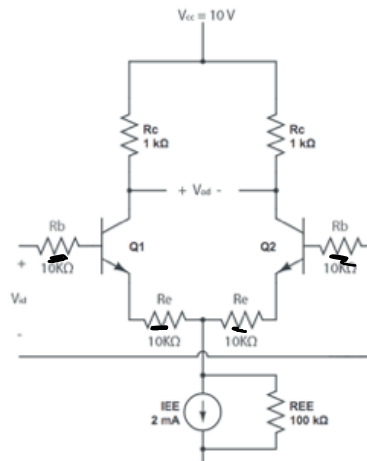- The value of collector current for Q_1 and Q_2 .
- The differential mode gain A_{dm} .
- The common mode gain A_{cm} .
- The CMRR in decibel (dB).



$$\frac{V_{out}}{2} = -g_m R_c v_{be}$$
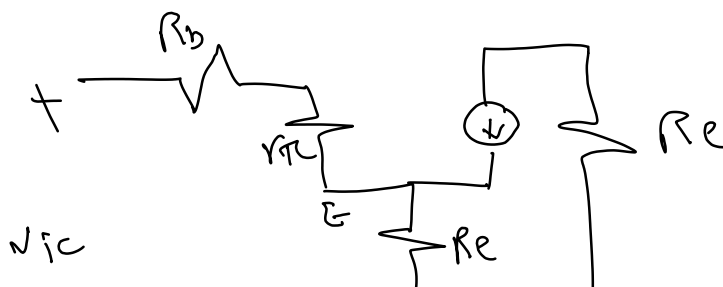
$$v_{be} = \frac{V_{id}}{2} \frac{r_{\pi}}{r_{\pi} + R_b + (1 + \beta) R_e}$$



2 E E I

,



Sheet P.1.3

Sunday, November 6, 2022 9:24 AM

The differential amplifiers shown in the following three figures use two matched BJT's Q_1 and Q_2 with $\beta = 100$ and $V_A = \infty$.

Calculate:

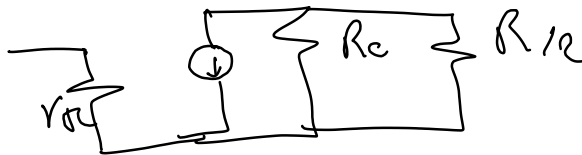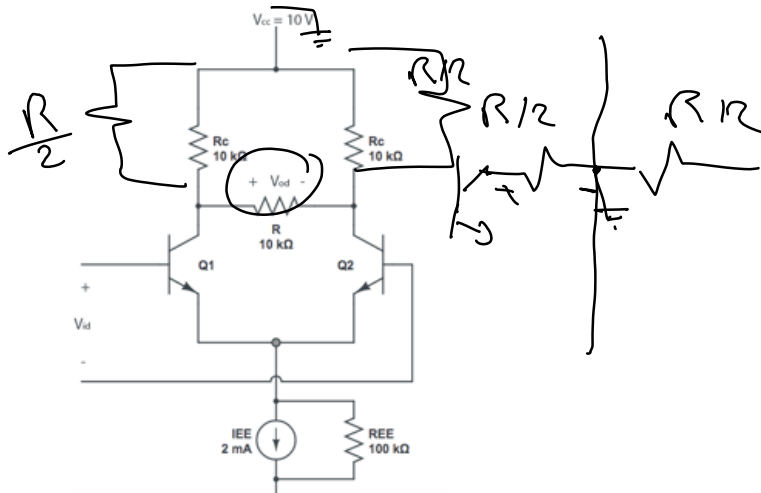- The value of collector current for Q_1 and Q_2 .
- The differential mode gain A_{dm} .
- The common mode gain A_{cm} .
- The CMRR in decibel (dB).




Sheet P.2

Sunday, November 6, 2022 9:26 AM

The differential amplifier shown in the following figure uses the current mirror current source Q_3 and Q_4 with $\beta = 200$ and $V_{A3} = V_{A4} = 120 \text{ V}$.

If $V_{A1} = V_{A2} = \infty$, Calculate:

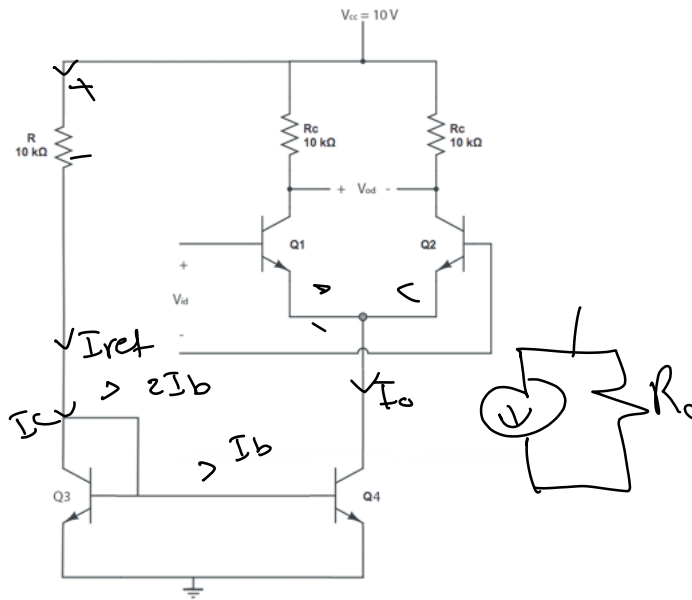- The value of collector current for Q_1 and Q_2 .
- The differential mode gain A_{dm} .
- The common mode gain A_{cm} .
- The CMRR in decibel (dB).



$$I_{ref} = \frac{10 - 0.7}{R} = \checkmark = 0.93 \text{ mA}$$

$$I_o = I_{ref} \Rightarrow$$

$$I_o = I_{ref} \frac{\beta}{\beta + 2} = \checkmark$$


$$I_{E1} = I_{E2} = \frac{I_o}{2}$$

$$R_o = r_o = \frac{V_A}{I_c} \Rightarrow r_{o4} = \frac{120}{I_o} = \checkmark$$

Sheet P.3

Saturday, November 12, 2022 6:56 PM

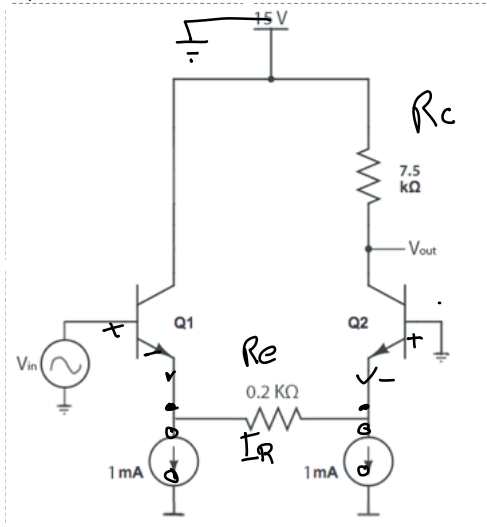For the differential amplifier shown in the following figure, calculate the voltage gain, input and output resistances. ($\beta = 100$, $V_{A1} = V_{A2} = \infty$)




$$V_{E1} = -V_{BE1}$$


$$V_{E2} = -V_{BE2}$$

$$I_R = \frac{V_{E1} - V_{E2}}{R} = 0$$

$$I_{E1} = I_{E2} = 1 \text{ mA}$$
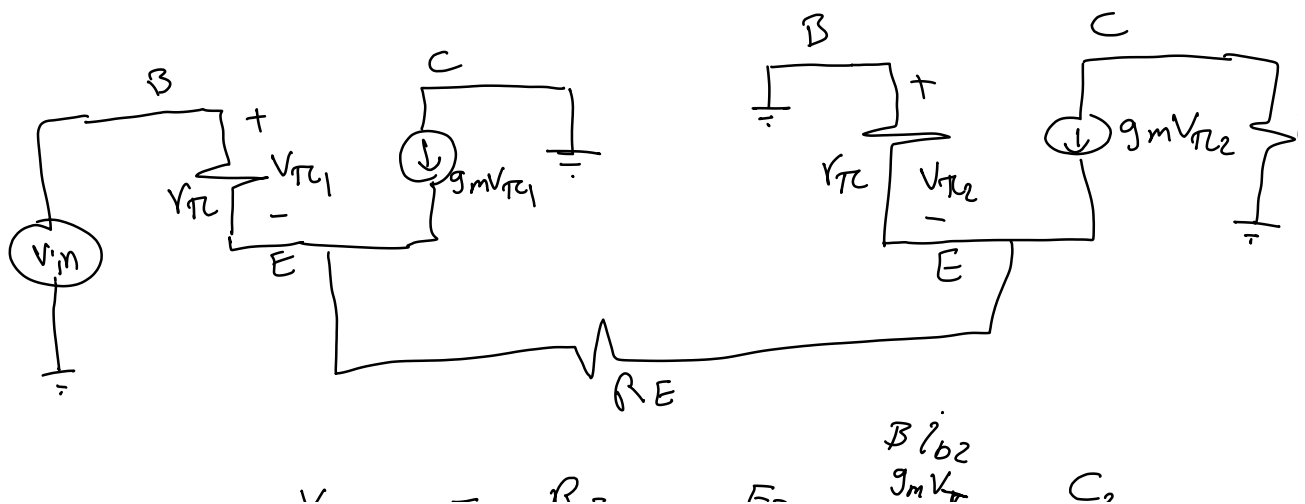
$$I_C = \checkmark \quad I_B = \checkmark$$



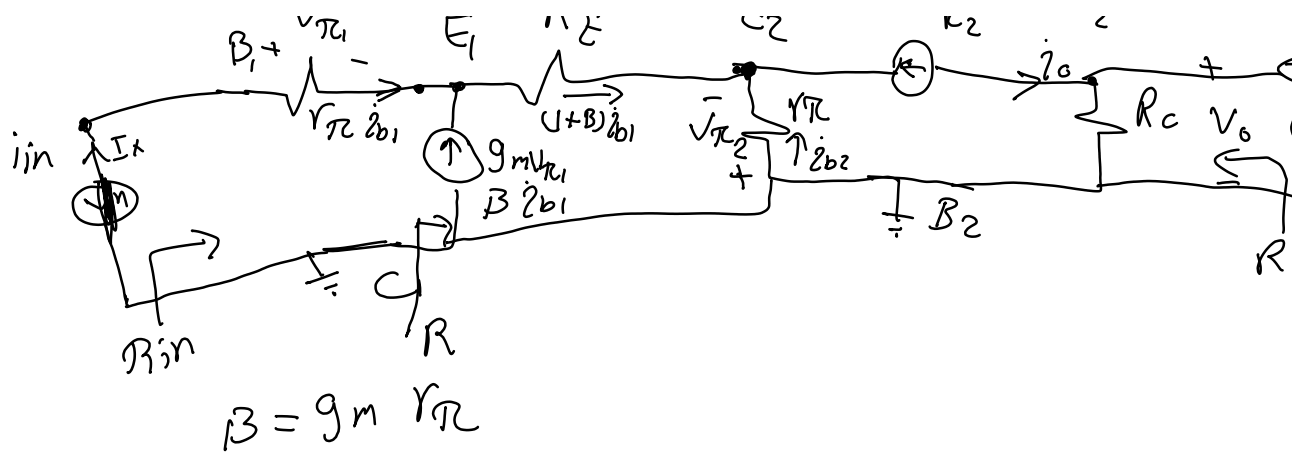

Apply KCL at E_2

$$\beta \dot{i}_{b2} + \dot{i}_{b2} + (1 + \beta) \dot{i}_{b1} = 0$$

$$(1 + \beta) \dot{i}_{b2} = -(1 + \beta) \dot{i}_{b1}$$

$$\boxed{\dot{i}_{b2} = -\dot{i}_{b1}}$$

$$V_o = -\beta \dot{i}_{b2} R_C$$

$$V_o = \beta \dot{i}_{b1} R_C \rightarrow (1)$$

$$V_{in} = \dot{i}_{b1} r_{\pi} + (1 + \beta) R_E \dot{i}_{b1} + (-\dot{i}_{b2} r_{\pi})$$

$$= \dot{i}_{b1} r_{\pi} + (1 + \beta) R_E \dot{i}_{b1} + \dot{i}_{b1} r_{\pi}$$

$$V_{in} = \dot{i}_{b1} (2 r_{\pi} + (1 + \beta) R_E)$$

$$\dot{i}_{b1} = \frac{V_{in}}{2 r_{\pi} + (1 + \beta) R_E} \rightarrow (2)$$

from ② \rightarrow ①

$$\frac{V_o}{V_{in}} = \frac{\beta R_C}{2 r_{\pi} + (1 + \beta) R_E} = \checkmark$$

$$I_R = i_{b1}$$

$$V_R = (1 + \beta) i_{b1} R_E + i_{b1} r_{\pi}$$

$$R = \frac{V_R}{I_R} = (1 + \beta) R_E + r_{\pi}$$

$$R_{in} = 2 r_{\pi} + (1 + \beta) R_E$$

$$R_{out} = R_C$$


Sheet P.4

Saturday, November 12, 2022 6:58 PM


The MOS differential amplifier shown in the following figure uses two matched MOSFET's M_1 and M_2 with $K = 2 \text{ mA/V}^2$ and $V_A = \infty$.

Calculate:

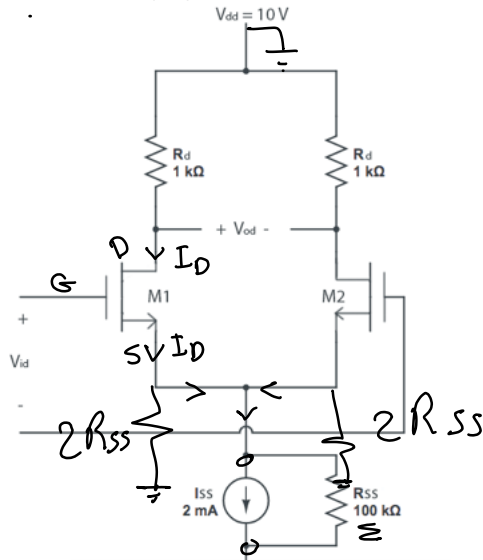- The value of drain current for M_1 and M_2 .
- The differential mode gain A_{dm} .
- The common mode gain A_{cm} .
- The CMRR in decibel (dB).



$$I_{D2} = I_{D1} = 1 \text{ mA}$$

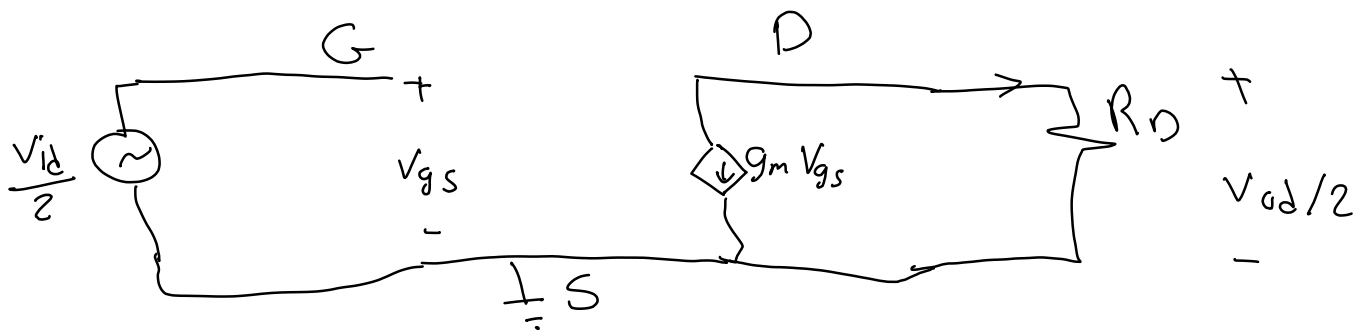

$$g_m = \sqrt{2K I_D} = \checkmark$$


$$r_{ds} = \frac{V_A}{I_D} = \infty$$

$$\frac{V_{od}}{2} = -g_m V_{gs} R_D$$

$$\therefore V_{id}/2 = V_{gs}$$

$$\therefore \frac{V_{od}}{2} = -g_m R_D \frac{V_{id}}{2}$$
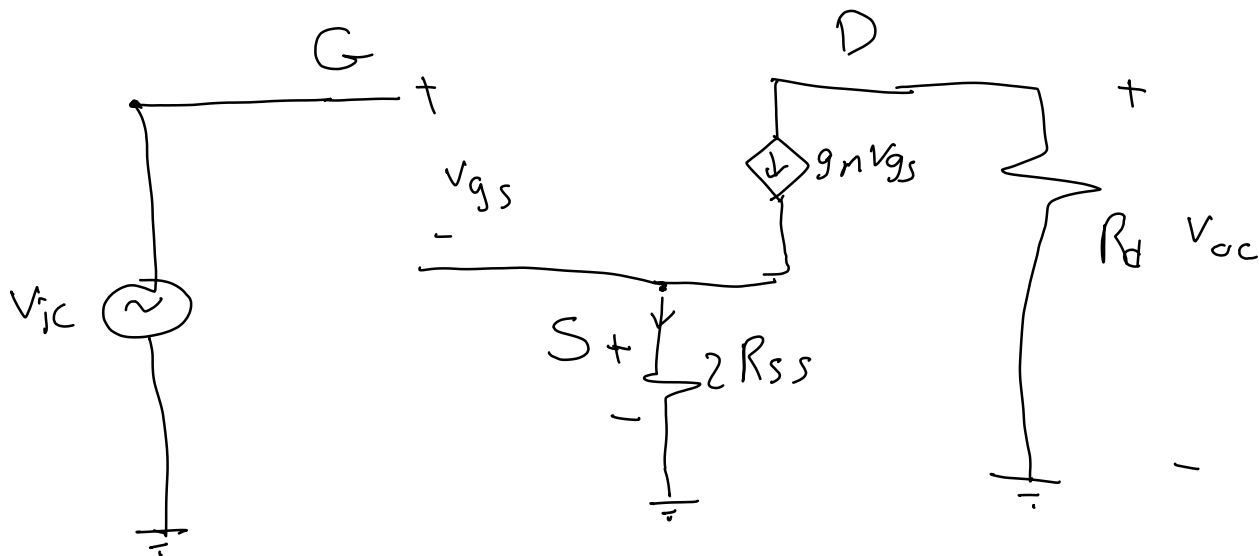
$$\frac{V_{od}}{V_{id}} = -g_m R_D = A_{dm}$$



$$V_{oc} = -g_m V_{gs} R_d$$

$$V_{ic} = V_{gs} + g_m V_{gs} 2R_{ss}$$

$$\frac{V_{oc}}{V_{ic}} = \frac{-g_m \cancel{V_{gs}} R_d}{(1 + g_m 2R_{ss}) \cancel{V_{gs}}} = \frac{-g_m R_d}{1 + 2g_m R_{ss}} = A_{cm}$$

$$C_{mRR} = 20 \log \left| \frac{A_{dm}}{A_{cm}} \right| = \checkmark$$


Sheet P.5

Saturday, November 12, 2022 7:00 PM

The differential amplifier shown in the following figure uses the current mirror current source M_3 and M_4 with $K = 0.5 \text{ mA/V}^2$ and $V_{A3} = V_{A4} = 120 \text{ V}$.

If $V_{A1} = V_{A2} = \infty$, Calculate:

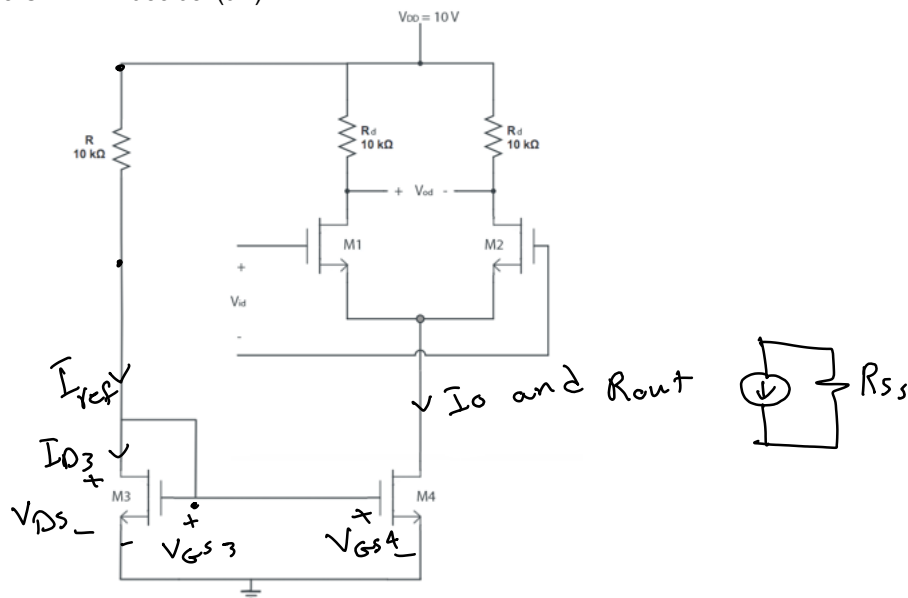- The differential mode gain A_{dm} .
- The common mode gain A_{cm} .
- The CMRR in decibel (dB).



$$I_{ref} = \frac{10 - V_{GS3}}{10k} = I_{D3} = 1 - 0.1 V_{GS3} \rightarrow \textcircled{1}$$

M_3 is in saturation region

$$V_{DS} > V_{GS} - V_T$$

$$\therefore V_{DS} = V_{GS}$$

$$\therefore M_3 \rightarrow \text{sat.}$$

$$I_{D3} = \frac{K}{2} (V_{GS3} - V_T)^2 \rightarrow \textcircled{2}$$

$$\text{Where } K = K_n = K_n' \cdot \frac{W}{L} \text{ and } K_n' = \mu_n C_{ox}$$

$$V_{GS3} \begin{cases} \rightarrow 2.71 \text{ V } \checkmark \\ \hookrightarrow -1.11 \text{ V } \times \end{cases} \quad V_T = 1 \text{ V}$$

$$V_{GS3} = 2.71 \text{ V}$$

$$I_{D3} = 1 - 0.1 \times 2.71 = 0.729 \text{ mA}$$

$\therefore m_3$ and m_4 are matched

$$\therefore I_{D3} = I_{D4} = I_G = 0.729 \text{ mA}$$

$$R_{out} = r_{ds4} = \frac{V_{A4}}{I_4} = \frac{120}{0.729} = 164.61 \text{ k}\Omega$$

$$g_{m1} = g_{m2} = \sqrt{2 \times I_D} = \checkmark$$