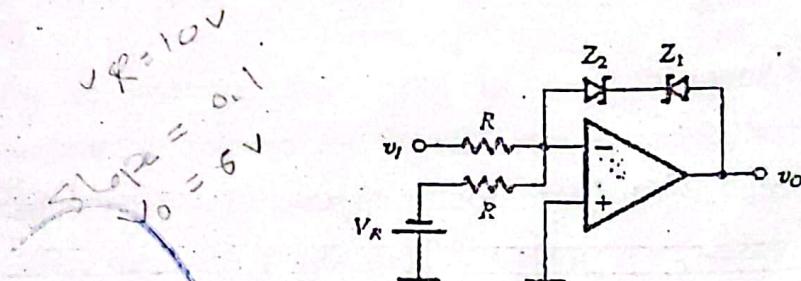



(1)

PROBLEMS

- X 1- Consider the circuit of Fig. 3(a) with R_f removed so as to realize the comparator function. Find suitable values for all resistors so that the comparator output levels are ± 6 V and so that the slope of the limiting characteristic is 0.1. Use power supply voltages of ± 10 V and assume the voltage drop of a conducting diode to be 0.7 V.



(a)

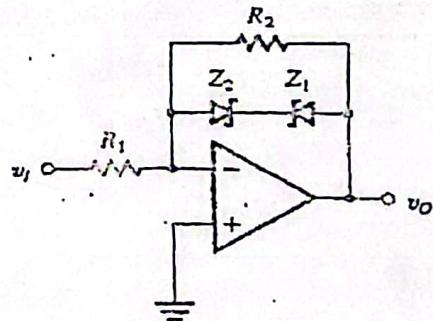

(b)

Fig. P2

- X 2- Denoting the zener voltages of Z_1 and Z_2 by V_{z1} and V_{z2} and assuming that in the forward direction the voltage drop is approximately 0.7 V, sketch and clearly label the transfer

(2)

characteristics $v_o - v_i$ of the circuits in Fig. P12.8. Assume the op amps to be ideal.

X 3-For the Wien-bridge oscillator circuit in Fig. 4, show that the transfer function of the feedback network $[V_o(s) / V_i(s)]$ is that of a bandpass filter. Find W_0 and Q of the poles, and find the center-frequency gain.

X 4-For the Wien-bridge oscillator of Fig. 4, let the closed-loop amplifier (formed by the op amp and the resistors R_1 and R_2) exhibit a phase shift of -0.1 rad in the neighborhood of $W = 1/CR$. Find the frequency at which oscillations can occur in this case, in terms of CR .

X 5- For the circuit in Fig. P5 find $L(s)$, $L(j\omega)$, the frequency for zero loop-phase, and R_2/R_1 for oscillation.

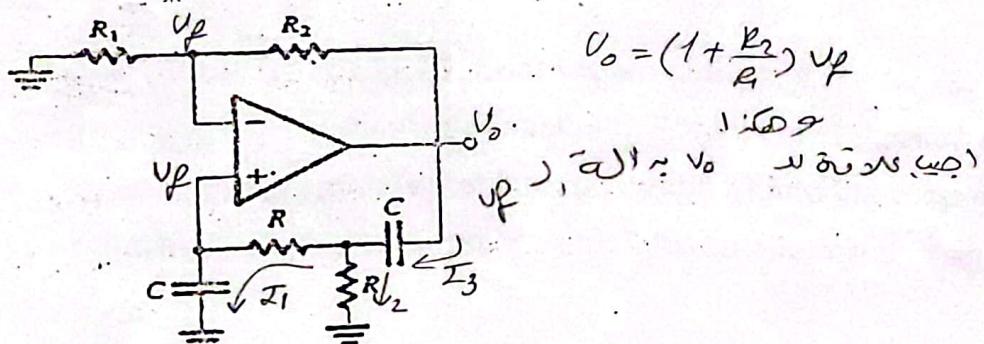


Fig. P5

(3)

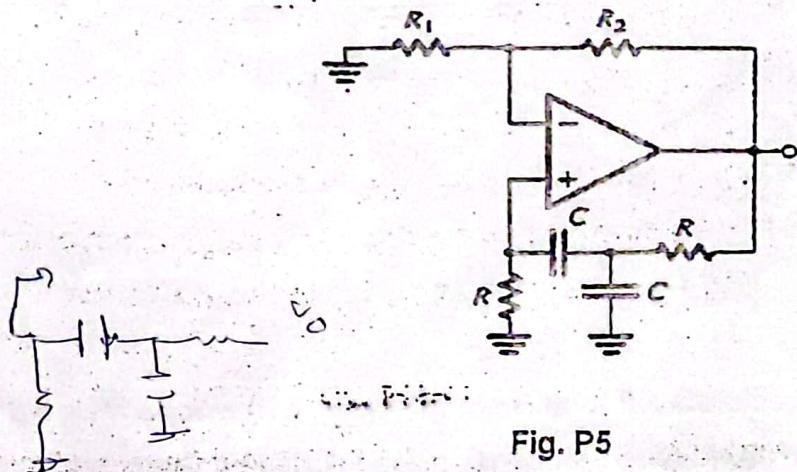


Fig. P5

✓ 6- Redesign the circuit of Fig. 6 for operation at 10 kHz using the same values of resistance. If at 10 kHz the op amp provides an excess phase shift (lag) of 5.7°, what will be the frequency of oscillation? (Assume that the phase shift introduced by the op amp remains constant for frequencies around 10 kHz.) To restore operation to 10 kHz, what change must be made in the shunt resistor of the Wien bridge? Also, to what must R_2/R_1 be changed?"

✓ 7- For the circuit of Fig. P7, connect an additional $R = 10 \text{ k}\Omega$ resistor in series with the rightmost capacitor C. For this modification (and ignoring the amplitude stabilization circuitry) find the loop gain $A\beta$ by breaking the circuit at node X. Find R_f for oscillation to begin, and find f_o

(4)


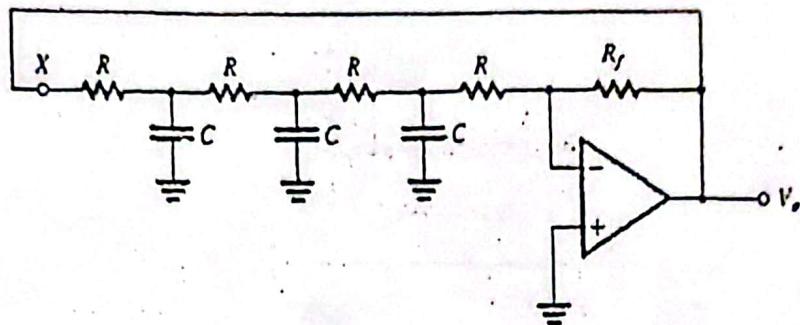


Fig. P7



- 8- Figure P8 shows four oscillator circuits of the Colpitts type, complete with bias detail. For each circuit derive an equation governing circuit operation, and find the frequency of oscillation and the gain condition that ensures that oscillations start.

$$\text{Ans} = 1$$

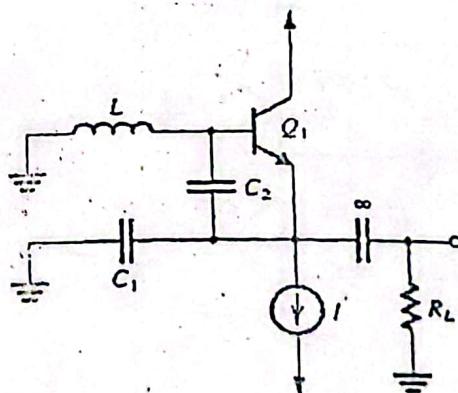

(a)

(5)

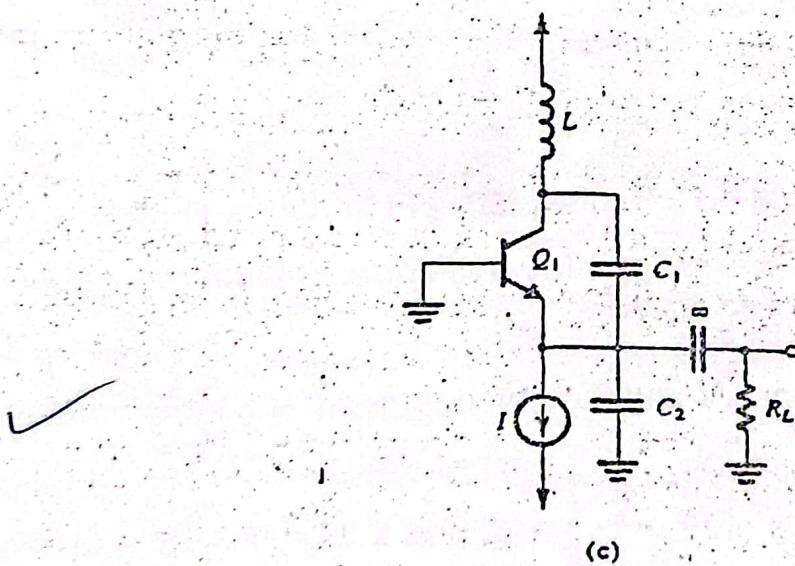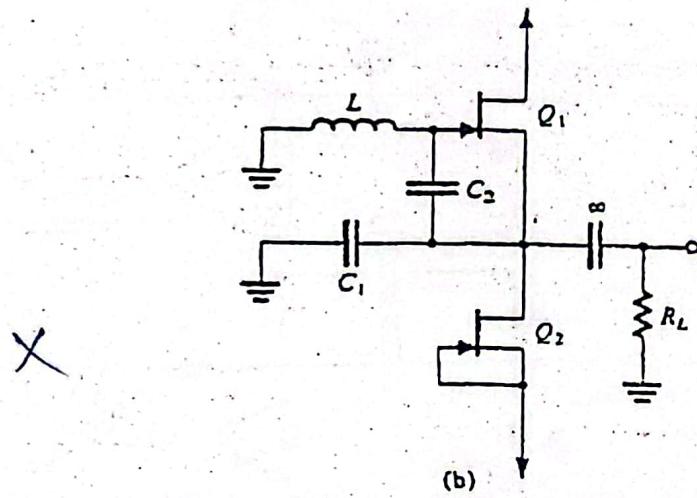

(6)

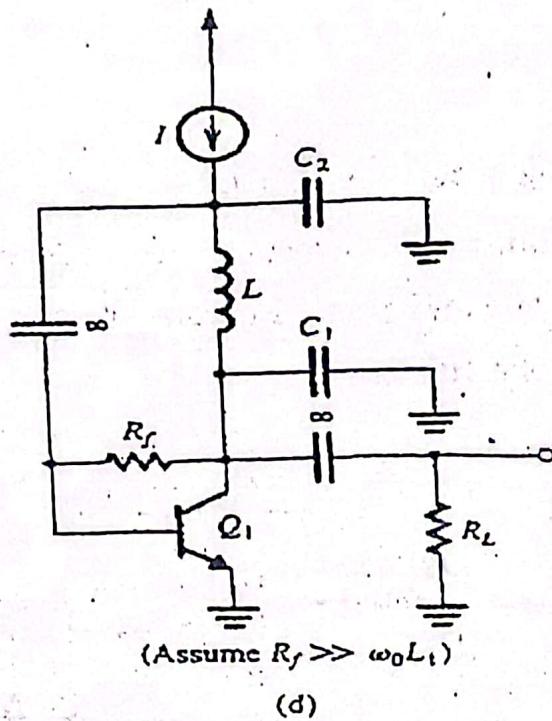


Fig. P8

~~X~~ 9-Consider the bistable circuit of Fig. 13(a) with the op amp's positive input terminal connected to a positive voltage source V through a resistor R_3 .

(a) Derive expressions for the threshold voltages V_{TL} and V_{TH} in terms of the op amp's saturation levels $L+$ and $L-$, R_1 , R_2 , R_3 , and V .

(b) Let $L_+ = -L_- = 13$ V, $V = 15$ V and $R_1 = 10$ k Ω . Find the values of R_2 and R_3 that result in $V_{TL} = +4.9$ V and $V_{TH} = +5.1$ V.

~~X~~ 10-Consider the bistable circuit of Fig. 14(a) with the op amp's negative input terminal disconnected from ground and connected to a reference voltage V_R .

(a) Derive expressions for the threshold voltages V_{TL} and V_{TH} in terms of the op amp's saturation levels $L+$ and $L-$, R_1 , R_2 , and V_R .

(7)

- (b) Let $L_+ = -L_- = V$ and $R_1 = 10 \text{ k}\Omega$. Find R_2 and V_R that result in threshold voltages of 0 and $V/10$.

- ✓ 11-For the circuit in Fig. P11; sketch and label the transfer characteristic $v_o - v_i$. The diodes are assumed to have a constant 0.7-V drop when conducting, and the op amp saturates at $\pm 12 \text{ V}$. What is the maximum diode current?

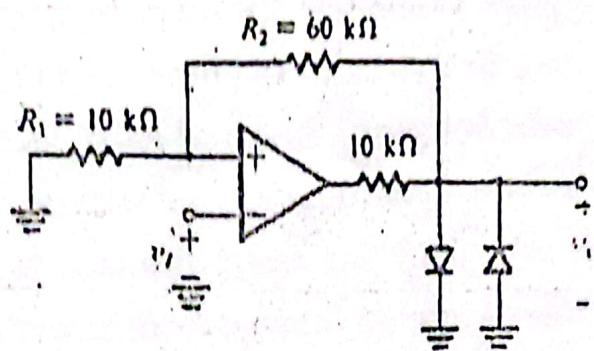


Fig. P11

- ✓ 11-Consider the circuit of Fig. P11 with R_1 eliminated and R_2 short circuited. Sketch and label the transfer characteristic $v_o - v_i$. Assume that the diodes have a constant 0.7-V drop when conducting and that the op amp saturates at $\pm 12 \text{ V}$.

- ✓ 12-Consider a bistable circuit having a noninverting transfer characteristic with $L_+ = L_- = 12 \text{ V}$, $V_{IL} = -1 \text{ V}$, and $V_{IH} = +1 \text{ V}$.
- (a) For a 0.5-V-amplitude sine-wave input having zero average, what is the output?

(8)

(b) Describe the output if a sinusoid of frequency f and amplitude of 1.1 V is applied at the input. By how much can the average of this sinusoidal input shift before the output becomes a constant value?

13-Find the frequency of oscillation of the circuit in Fig. 15(b) for the case $R_1 = 10 \text{ k}\Omega$, $R_2 = 16 \text{ k}\Omega$, $C = 10 \text{ nF}$, and $R = 62 \text{ k}\Omega$.

14-The circuit of Fig. P14 consists of an inverting bistable multivibrator with an output limiter and a noninverting integrator. Using equal values for all resistors except R_4 , and a 0.5-nF capacitor, design the circuit to obtain a square wave at the output of the bistable multivibrator of 15-V peak-to-peak amplitude and 10-kHz frequency. Sketch and label the waveform at the integrator output. Assuming ± 13 -V op amp saturation levels, design for a minimum zener current of 1 mA. Specify the zener voltage required, and give the values of all resistors.

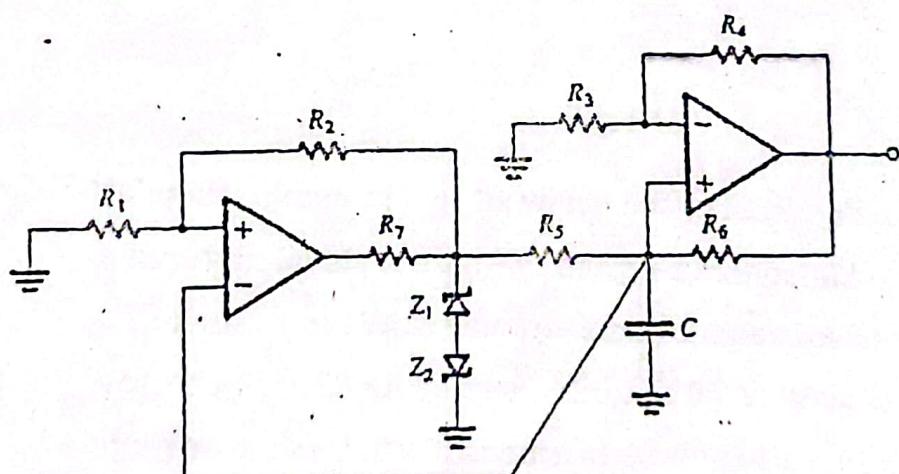


Fig.P14

(9)

15-Figure Pi5 shows a monostable multivibrator circuit. In the stable state $v_o = L+$, $v_A = 0$, and $v_B = -V_{ref}$. The circuit can be triggered by applying a positive input pulse of height greater than V_{ref} . For normal operation, $C_1R_1 \ll CR$. Show the resulting waveforms of v_o and v_A . Also, show that the pulse generated at the output will have a width T given by

$$T = RC \ln(L+ - L-) / V_{ref}$$

Note that this circuit has the interesting property that the pulse width can be controlled by changing V_{ref} .

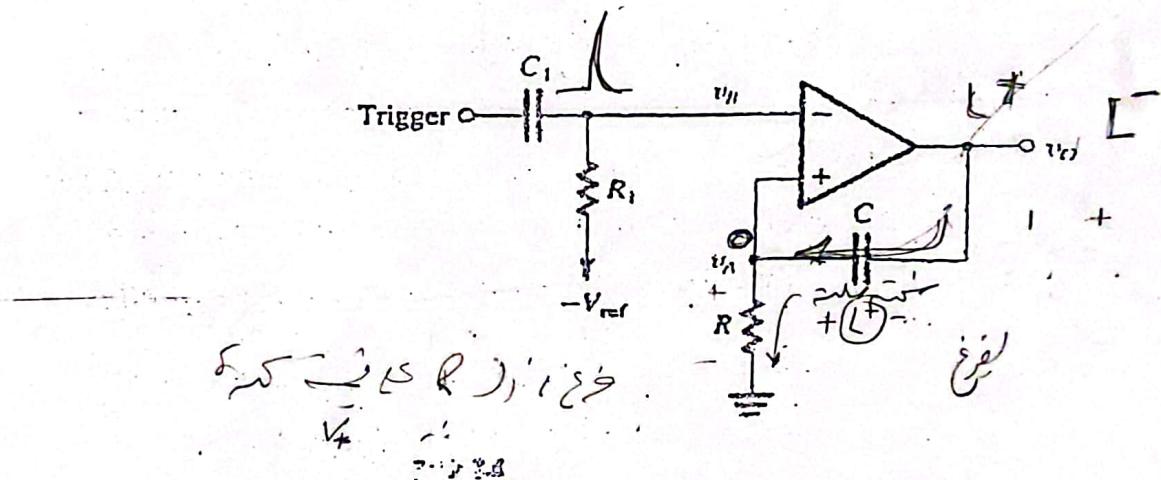


Fig. P15


16-Using the circuit of Fig. 19, with a nearly ideal op amp for which the saturation levels are ± 13 V, design a monostable multivibrator to 0.1 nF and 1 nF. Wherever possible, choose resistors of 100 kΩ in your design. Diodes have a drop of 0.7 V. What is the minimum input step size that will ensure triggering? How long does the circuit take to recover to a state in which retriggering is possible with a normal output?

~~sheet~~
~~analog~~

sheet oscillators

W_i

P. ⑥ :

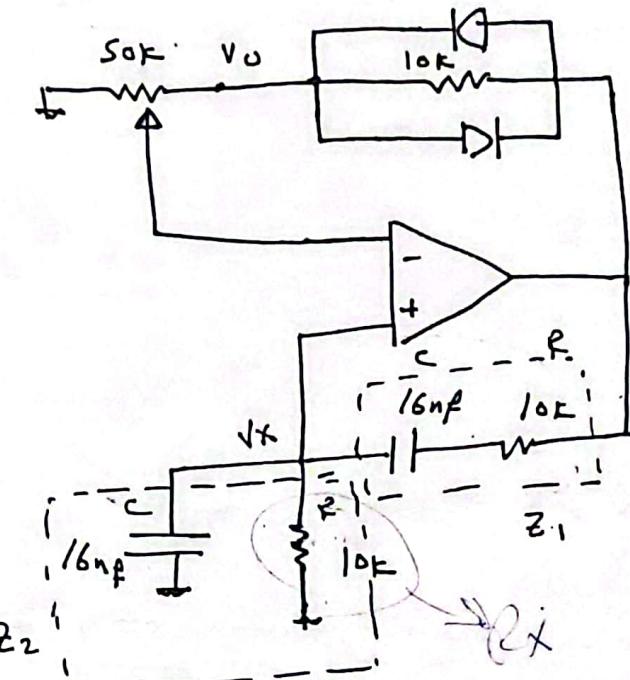

$$f_0 = 10 \text{ kHz} = 10^4 \text{ Hz}$$

$$\omega_0 = 2\pi f_0 = \frac{1}{RC}, \quad R = 10k\Omega = 10^4 \Omega$$

$$\Rightarrow 2\pi \times 10^4 = \frac{1}{10^4 \times C}$$

$$C = \frac{1}{2\pi \times 10^4} = \underline{\underline{1.6 \text{ nF}}}$$

⇒

$$\boxed{f = 10 \text{ kHz}}$$
$$, C = 1.6 \text{ nF}$$

Wien bridge oscillator

$$z_1 = R + \frac{1}{sc} = \frac{Rsc + 1}{sc}$$

$$z_2 = \frac{R \cdot \frac{1}{sc}}{R + \frac{1}{sc}} = \frac{R}{1 + scR}$$

$$V_x = \frac{V_o z_2}{z_1 + z_2}$$

$$\frac{V_x}{V_o} = \beta = \frac{z_2}{z_1 + z_2}$$


$$\begin{aligned} \sqrt{\beta} &= \frac{z_1 + z_2}{z_2} = 1 + \frac{z_1}{z_2} \\ &= 1 + \frac{\frac{scR + 1}{sc}}{\frac{R}{scR + 1}} = \end{aligned}$$

$$= 1 + \frac{(scR + 1)^2}{scR}$$

$$= 1 + \frac{s^2C^2R^2 + 2scR + 1}{scR}$$

$$= 1 + scR + 2 + \frac{1}{scR}$$

$$= 3 + scR + \frac{1}{scR}$$

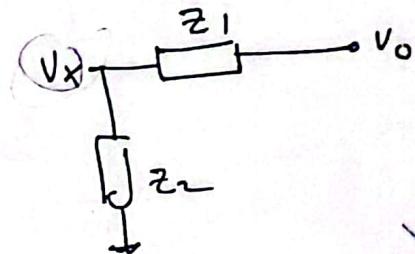

$$\beta = \frac{V_f}{V_i}$$

Page 2

#3

$$\beta = \left[3 + sCR + \frac{1}{sCR} \right]^{-1}$$

$$\beta(j\omega) = \left[3 + j\omega CR + \frac{1}{j\omega CR} \right]^{-1}$$

$$\beta(j\omega) = \left[3 + j(\omega CR - \frac{1}{\omega CR}) \right]^{-1}$$

$$\phi(\omega) = -\tan^{-1} \left(\frac{\omega CR - \frac{1}{\omega CR}}{3} \right)$$

↙ real part ↘ imag part

*(مکانیکی اوریئنٹیشن
کے لئے
تباہی کا
لگائیں)*

*کا نو
سچی*

$$\frac{\partial \tan^{-1} y}{\partial \omega} = \frac{1}{1+y^2} \cdot \frac{\partial y}{\partial \omega}$$



Ghar

$$y = \frac{\omega CR - \frac{1}{\omega CR}}{3}$$

$$\frac{\partial y}{\partial \omega} = \frac{R_C + \frac{1}{\omega^2 R_C}}{3}$$

$$\therefore \boxed{\frac{\partial \phi(\omega)}{\partial \omega}} = -\frac{\partial \tan^{-1} y}{\partial \omega} = -\frac{1}{1+y^2} \cdot \frac{\partial y}{\partial \omega}$$

~~ω₀~~

$$\therefore \frac{\partial \phi(\omega)}{\partial \omega} = \frac{-1}{1 + \left(\frac{\omega_{CR} - \frac{1}{\omega_{CR}}}{3} \right)^2} \cdot \left(\frac{R_C + \frac{1}{\omega^2 R_C}}{3} \right)$$

at $\omega = \omega_0 = \frac{1}{R_C}$

$$\therefore \frac{\partial \phi(\omega)}{\partial \omega} = \frac{-1}{1 + \left(\frac{1-1}{3} \right)^2} \cdot \frac{R_C + \frac{1}{\frac{1}{R_C} \cdot R_C}}{3}$$

$$\boxed{\frac{\partial \phi(\omega)}{\partial \omega}} = \boxed{-\frac{2}{3} R_C}$$



$$\partial \phi = \underline{5.7^\circ} = \frac{5.7 \times \pi}{180} = \boxed{0.1 \text{ rad}} \quad (\text{lag})$$

$$\therefore \Delta \omega = \Delta \omega_0 = \frac{\partial \phi}{-2/3 R_C} = \frac{\cancel{\Delta} 0.1}{-2/3 R_C}$$

$$= 0.15 \frac{1}{R_C} = 0.15 \omega_0$$

at $\omega_0 = 2\pi f_0 = 2\pi \times 10^4 \text{ Hz}$

$$\Delta \omega_0 = 0.15 \omega_0 = 0.15 \times 2\pi \times 10^4 =$$

$$= 9.4 \text{ kHz}$$


Then the new frequency of oscillation

$$\text{rs } \omega_0 - \Delta \omega_0 = 10 - \cancel{9.4} \div 2\pi \quad \cancel{9.4} \quad \boxed{8.5 \text{ kHz}}$$

$$= 0.6 \text{ kHz} = 600 \text{ Hz}$$

ω_s

To restore operation at 10 kHz

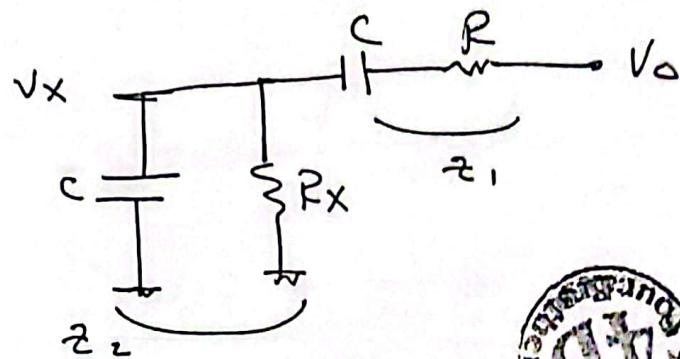

$$\frac{V_o}{z_1 + z_2} = V_x$$

$$\beta = \frac{V_x}{V_o} = \frac{z_2}{z_1 + z_2} = \frac{\frac{R_x}{sC}}{\frac{R_x}{sC} + \frac{R}{R_x} + \frac{1}{s^2 C^2}}$$

$$= \frac{\frac{R_x}{sC}}{\frac{R_x}{sC} + R R_x + \frac{R_x}{sC} + \frac{R}{sC} + \frac{1}{s^2 C^2}} \quad \leftarrow \frac{\frac{sC}{R_x}}{\frac{sC}{R_x}}$$

$$= \frac{1}{2 + R sC + \frac{R}{R_x} + \frac{1}{s^2 C^2 R_x}}$$

$$\therefore \beta(s) = \frac{1}{2 + R sC + \frac{R}{R_x} + \frac{1}{s^2 C^2 R_x}}$$

$$= \frac{1}{\left(2 + \frac{R}{R_x}\right) + \left(R sC + \frac{1}{s^2 C^2 R_x}\right)}$$

$\xrightarrow{\text{real}}$ $\xrightarrow{\text{imag}}$

$$\phi = -\tan^{-1} \frac{\omega_c R - \frac{1}{\omega R_{xc}}}{2 + \frac{R}{R_x}}$$

To restore operation then

$$\tan(-s_7) = \frac{\omega_c R - \frac{1}{\omega_0 R_{xc}}}{2 + \frac{R}{R_x}}$$

$$\omega_0 = \frac{1}{R_c}$$



$$\Rightarrow 1 - \frac{1}{\frac{1}{s_7} R_{xc}} = \left(2 + \frac{R}{R_x}\right) (-0.1)$$

$$1 - \frac{R}{R_x} = \left(2 + \frac{R}{R_x}\right) (-0.1)$$

$$1 + 0.2 = -0.1 R/R_x + \frac{R}{R_x}$$

$$1.2 = 0.9 \frac{R}{R_x}$$


$$\frac{R}{R_x} = \frac{1.2}{0.9} = \frac{12}{9} = \frac{4}{3}$$

$$\text{For } R = 10 \text{ k}\Omega = 10^4 \Omega$$

$$\therefore R_x = \frac{R}{4} * 3 = 7.5 \text{ k}\Omega$$

$$\boxed{R_x = 7.5 \text{ k}\Omega}$$

for restore operation

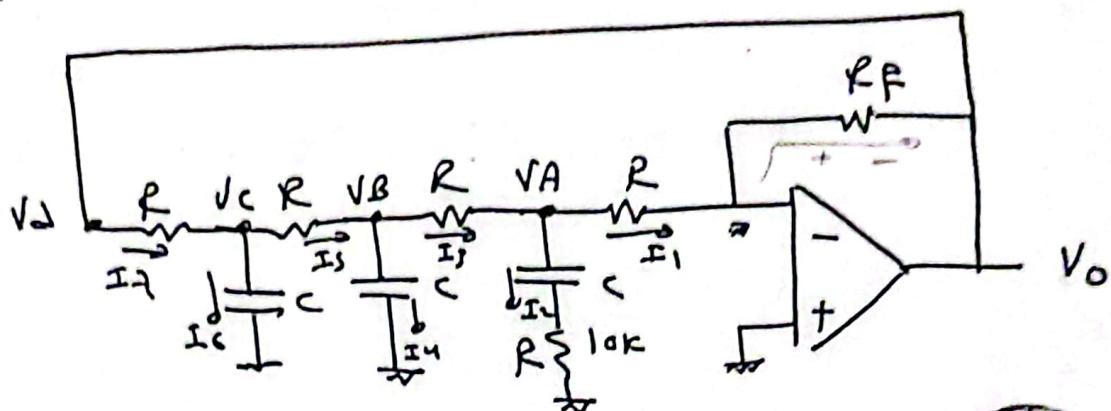P(7)

$$R = 10k\Omega$$



$$V_o = - \frac{R_f}{R} V_A$$

$$A = \frac{V_o}{V_A} = - R_f / R \rightarrow ①$$

$$I_1 = V_A / R$$

$$I_2 = \frac{V_A}{s_c C + R}$$

$$I_3 = I_1 + I_2 = \frac{V_A}{R} + \frac{V_A}{s_c C + R}$$

$$= \left(\frac{1}{R} + \frac{1}{s_c C + R} \right) V_A$$

$$= \left[\frac{1}{R} + \frac{1}{s_c C + R} \right] V_A$$

$$= \left(\frac{1}{R} + \frac{s_c C}{1 + s_c C R} \right) V_A$$

W8

$$V_B = I_3 R + V_A$$

~~90% correct~~

$$= \left(\frac{1}{R} + \frac{s_c}{1+s_c R} \right) V_A * R + V_A$$

$$= \left(1 + 1 + \frac{s_c R}{1+s_c R} \right) V_A$$

$$= \left(2 + \frac{s_c R}{1+s_c R} \right) V_A$$

$$I_4 = \frac{V_B}{s_c} = s_c \left(2 + \frac{s_c R}{1+s_c R} \right) V_A$$

$$= \left(2s_c + \frac{s^2 c^2 R}{1+s_c R} \right) V_A$$

$$I_S = I_3 + I_4$$

$$= \left(\frac{1}{R} + \frac{s_c}{1+s_c R} \right) V_A + \left(2s_c + \frac{s^2 c^2 R}{1+s_c R} \right) V_A$$

$$= \left[\frac{1}{R} + 2s_c + \frac{s_c + s^2 c^2 R}{1+s_c R} \right] V_A$$

$$V_C = I_S R + V_B$$

Correct

مجهول مجهول
مجهول مجهول
مجهول مجهول
مجهول مجهول
مجهول مجهول

W9

$$V_C = \left(1 + 2sCR + \frac{sCR + s^2C^2R^2}{1+sCR} \right) V_A + \left(2 + \frac{sCR}{1+sCR} \right) V_A$$

$$= \left(3 + 2sCR + \frac{2sCR + s^2C^2R^2}{1+sCR} \right) V_A$$

$$I_6 = \frac{V_C}{Y_{SC}} = SC \left[3 + 2sCR + \frac{2sCR + s^2C^2R^2}{1+sCR} \right] V_A$$
$$= \left(3SC + 2s^2C^2R + \frac{2s^2C^2R + s^3C^3R^2}{1+sCR} \right) V_A$$



$$I_7 = I_6 + IS$$

$$= \left[3SC + 2s^2C^2R + \frac{2s^2C^2R + s^3C^3R^3}{1+sCR} + \right.$$
$$\left. \frac{1}{R} + 2SC + \frac{SC + s^2C^2R}{1+sCR} \right] V_A$$
$$= \left[\frac{1}{R} + 3SC + 2SC + 2s^2C^2R + \right.$$
$$\left. + \frac{3s^2C^2R + SC + s^3C^3R^3}{1+sCR} \right] V_A$$

$$V_d = V_o = I_7 R + V_C$$

W₁

$$V_d = V_0 = \left[1 + \frac{3sCR}{1+sCR} + \frac{2s^2C^2R^2}{1+sCR} + \right. \\ \left. + \frac{3s^2C^2R^2 + sCR + s^3C^3R^4}{1+sCR} + \right. \\ \left. + 3 + \frac{2sCR}{1+sCR} + \frac{2sCR + s^2C^2R^2}{1+sCR} \right] \sqrt{A}$$



$$= \left[4 + \frac{7sCR + 2s^2C^2R^2}{1+sCR} + \right. \\ \left. + \frac{4s^2C^2R^2 + 3sCR + s^3C^3R^4}{1+sCR} \right] \sqrt{A}$$

$$\boxed{B = \frac{\sqrt{A}}{V_0}}$$

$$\Rightarrow \frac{1}{B} = \frac{V_0}{\sqrt{A}} = \left(4 + \frac{7sCR + 2s^2C^2R^2}{1+sCR} + \frac{4s^2C^2R^2 + 3sCR + s^3C^3R^4}{1+sCR} \right)$$

$$\boxed{A = -\frac{RF}{R}} \quad \text{from ①}$$

The condition of oscillation is

$$AB = 1$$

$$\text{or } A = \frac{1}{B}$$

WII

$$-\frac{RF}{R} = 4 + 7sCR + 2s^2C^2R^2 + \frac{4s^2C^2R^2 + 3sCR + 3C^3R^4}{1+sCR}$$

mul both sides by $(1+sCR)$

$$\begin{aligned} -\frac{RF}{R}(1+sCR) &= 4(1+sCR) + (7sCR)(1+sCR) + \\ &+ 2s^2C^2R^2(1+sCR) + 4s^2C^2R^2 + 3sCR + 3C^3R^4 \end{aligned}$$

$$\begin{aligned} -\frac{RF}{R} - \frac{RF}{R}sCR &= 4 + \underline{4sCR} + \underline{7sCR} + \underline{7s^2C^2R^2} + \\ &+ \underline{2s^2C^2R^2} + \underline{2s^3C^3R^3} + \underline{4s^2C^2R^2} + \underline{3sCR} + \underline{3C^3R^4} \end{aligned}$$

$$\begin{aligned} -\frac{RF}{R} - 4 &= sCR \left(\frac{RF}{R} + 4 + 7 \right) + s^2C^2R^2(7+2+4) + \\ &+ 2s^3C^3R^3 + 3C^3R^4 \end{aligned}$$

$$\begin{aligned} -\frac{RF}{R} - 4 &= sCR \left(\frac{RF}{R} + 11 \right) + 16s^2C^2R^2 + \\ &+ 2s^3C^3R^3 + 3C^3R^4 \end{aligned}$$

Real part :

$$-\frac{RF}{R} - 4 = 16s^2C^2R^2 \quad S = j\omega$$



٢٢/٢

$$-\frac{R_F}{R} - 4 = -16 \omega^2 c^2 R^2 \times R$$

$$+ R_F + 4R = +16 \omega^2 c^2 R^3$$

$$\omega^2 = \frac{R_F + 4R}{16 c^2 R^3}$$

$$\boxed{\omega = \sqrt{\frac{R_F + 4R}{16 c^2 R^3}}}$$



Imaginary part

$$o = \left(\frac{R_F}{R} + 11 \right) j \omega c R + j \omega^2 \times 2 c^2 R^2 - j \omega^3 c^3 R^4 -$$

$$o = \left(\frac{R_F}{R} + 11 \right) - \omega^2 \times 2 c^2 R^2 - \omega^2 c^2 R^3$$

$$\omega^2 (2 c^2 R^2 + c^2 R^3) = \frac{R_F}{R} + 11$$

$$\frac{R_F + 4R}{16 c^2 R^3} (2 c^2 R^2 + c^2 R^3) = \frac{R_F}{R} + 11$$

$$R_F + 4R \left(\frac{1}{8R} + \frac{1}{16} \right) = \frac{R_F}{R} + 11 \quad \times 16R$$

$$(R_F + 4R) (2 + R) = 16 R_F + 176 R$$

$$2R_F + R_F R + 8R + \frac{4R^2}{16} = 16 R_F + 176 R$$


$$\boxed{4R^2 - 168R = 14R_F - R_F^2}$$

مختصر: ماردا نجاتی (معادل مختصر)



ایسا ہے مختصر لبع ایسا ہے

1/3

P. (8)
⑨

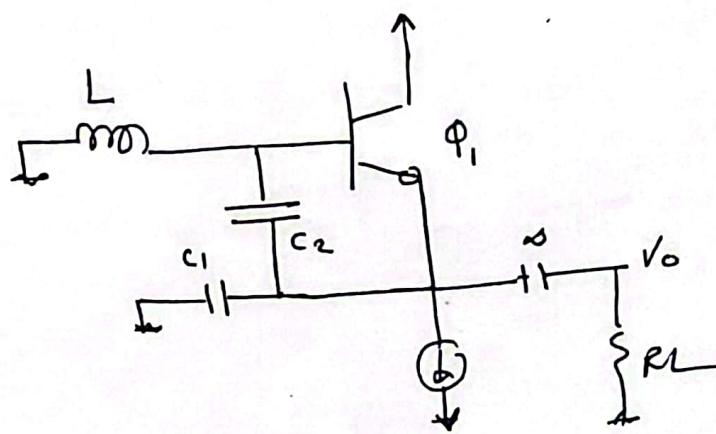

$\sqrt{\pi} \omega$

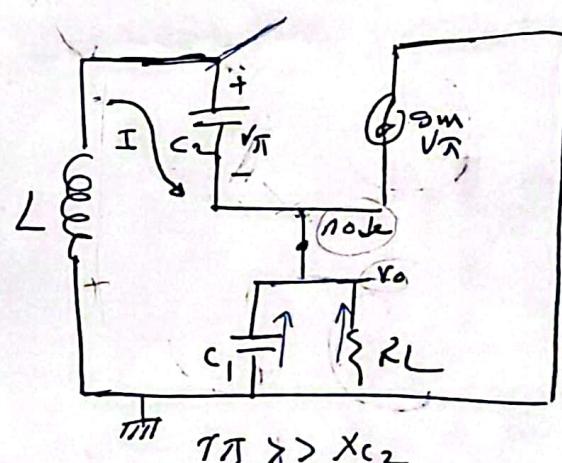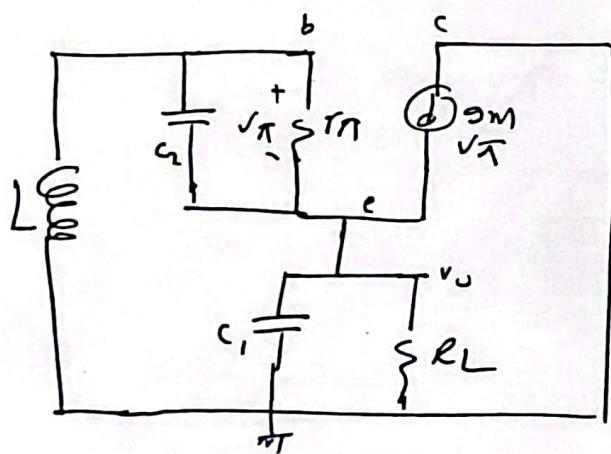

$$I = \sqrt{\pi} \cdot s c_2 = -\frac{[V_0 + \sqrt{\pi}]}{sL} \quad \textcircled{1}$$

$$V_0 = \sqrt{\pi} s c_2 \cdot sL - \sqrt{\pi}$$

$$V_0 = (s^2 c_2 L - 1) \sqrt{\pi} \quad \textcircled{1}$$

$$\therefore I = -\frac{\sqrt{\pi}}{s c_2}$$

Node:

$$V_o / V_{sc}$$

$$(1) + \omega_m v_{\pi} + \frac{V_o}{RL} + V_o \cdot sc_1 = 0$$

$$v_{\pi} sc_2 + \omega_m v_{\pi} = -V_o \left(\frac{1}{RL} + sc_1 \right) = 0$$

From ① :

$$\underline{v_{\pi} sc_2 + \omega_m v_{\pi}} = - \left[(s^2 c_2 L - 1) v_{\pi} \right] \left[\frac{1}{RL} + sc_1 \right]$$

$$\cancel{v_{\pi} sc_2 + \omega_m v_{\pi}} = (1 - s^2 c_2 L) \cancel{v_{\pi}} \left(\frac{1}{RL} + sc_1 \right)$$

$$sc_2 + \cancel{\omega_m R} = \frac{1}{RL} + sc_1 - \frac{s^2 c_2 L}{RL} \xrightarrow{s^3 c_1 c_2 L}$$

imaginary part :

$$sc_2 = sc_1 - s^3 c_1 c_2 L \quad s = j\omega$$

$$s^2 = -\omega^2$$

$$j\omega c_2 = j\omega c_1 + j\omega^3 c_1 c_2 L \quad s^3 = -j\omega^3$$

$$c_2 = c_1 + \omega^2 c_1 c_2 L$$

$$\omega^2 = \frac{c_2 - c_1}{c_1 c_2 L}$$

$$\omega = \sqrt{\frac{c_2 - c_1}{c_1 c_2 L}}$$



ω_{ls}

Real part:

$$\omega_m = \frac{1}{RL} - \frac{\omega^2 C_2 L}{RL}$$

$$\omega_m = \frac{1}{RL} + \frac{\omega^2 C_2 L}{RL}$$



$$\omega_m = \frac{1}{RL} + \frac{1}{RL} \cdot \frac{C_2 - C_1}{C_1 C_2} \cdot \cancel{f_2 K}$$

$$= \frac{1}{RL} \left(1 + \frac{C_2 - C_1}{C_1} \right) = \frac{1}{RL} \left(1 + \frac{C_2}{C_1} - 1 \right)$$


$$\omega_m = \frac{C_2}{C_1 RL}$$

$$RL = \frac{C_2}{\omega_m C_1}$$



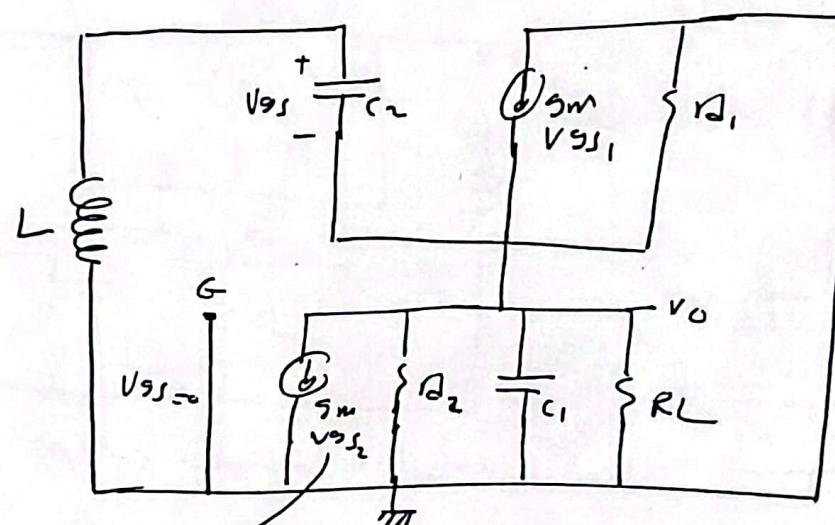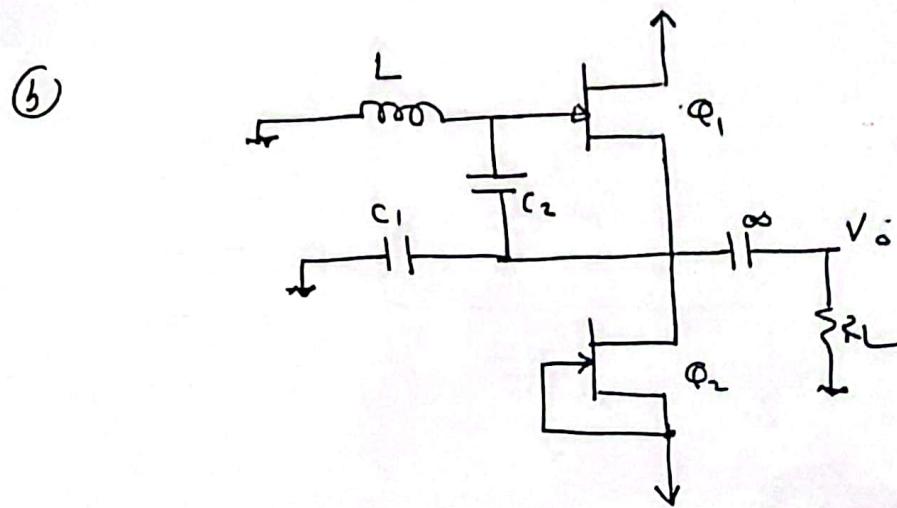



$V_{GS} = 0 \sim \text{open circuit}$

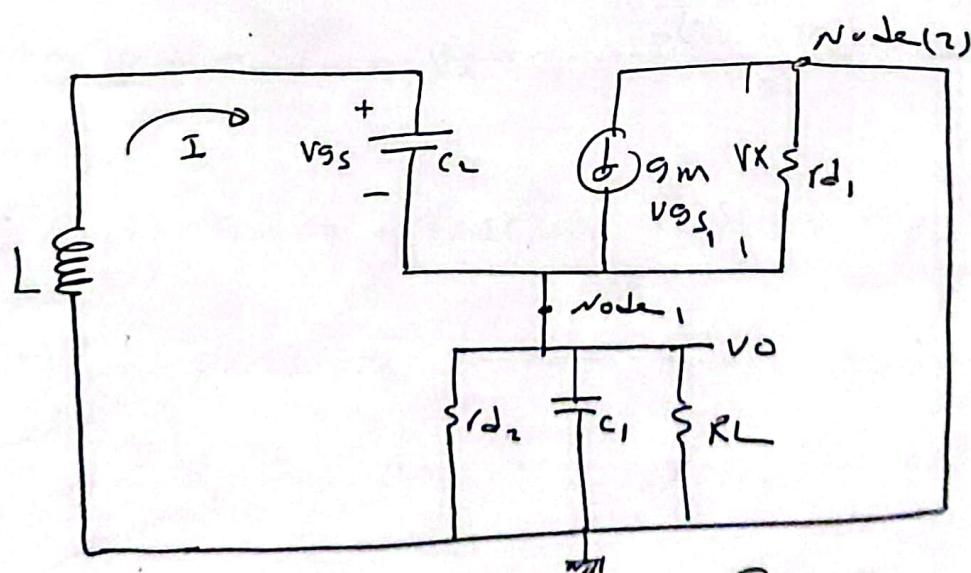


$$V_X = -V_O$$

مثبت میں اکا میں سلسلہ

(c)

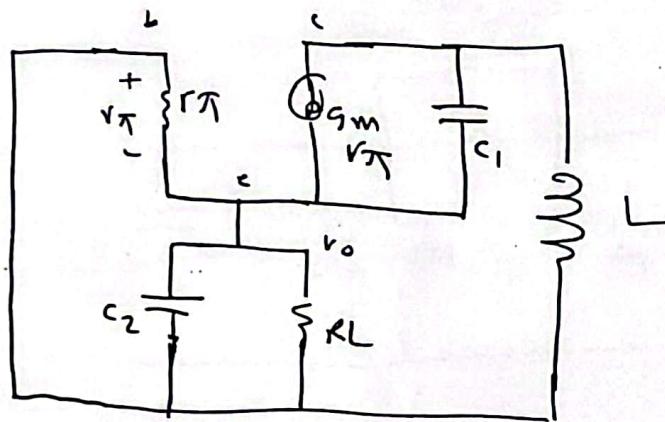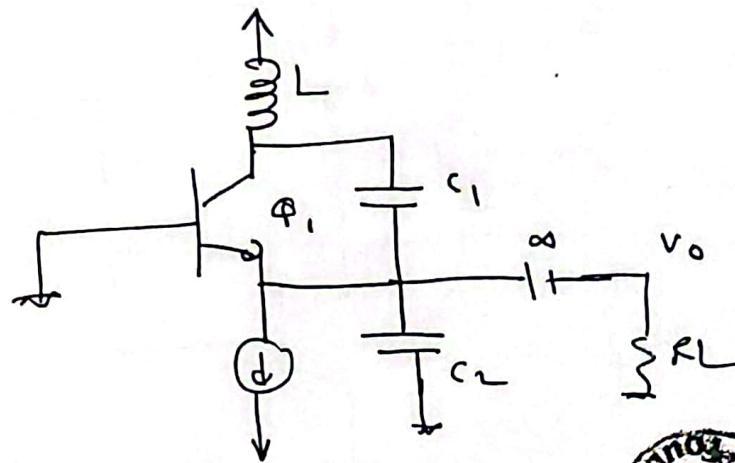

$r_\pi \gg$ Can be neglected

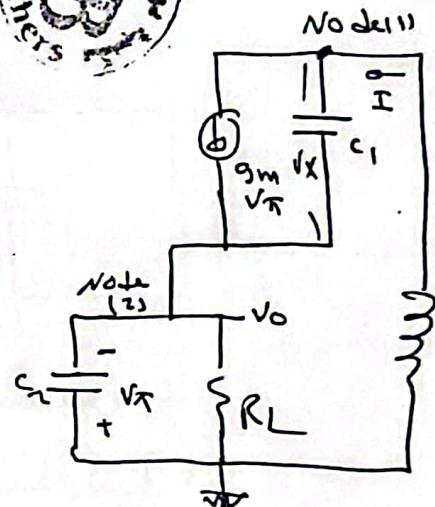


$$v_o = -v_\pi$$

$$\text{Node 11: } j\omega v_\pi + v_x s C_1 = -\frac{(v_x + v_o)}{sL} \rightarrow ①$$

$$\text{Node 12: } g_m v_\pi + v_x s C_1 = v_o s C_L + v_o / R_L \rightarrow ②$$

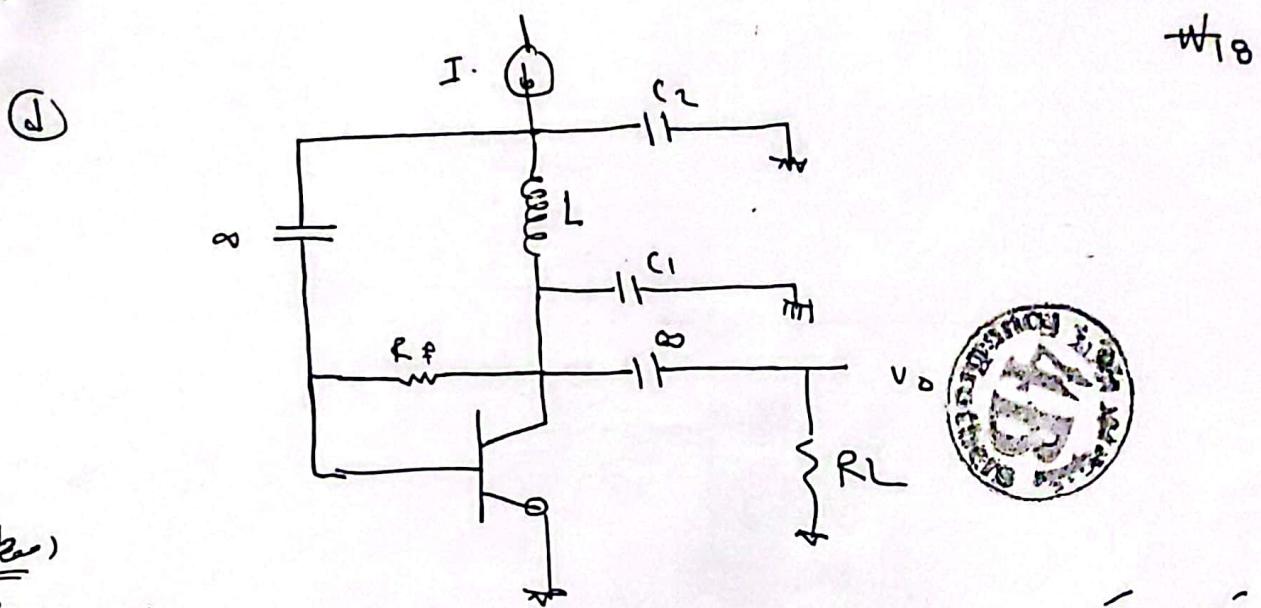
Now solve { find v_x in both sides and equal
 answer } { the two terms you can determine (w)



(مکار)


$$R_F \gg \omega_0 L$$

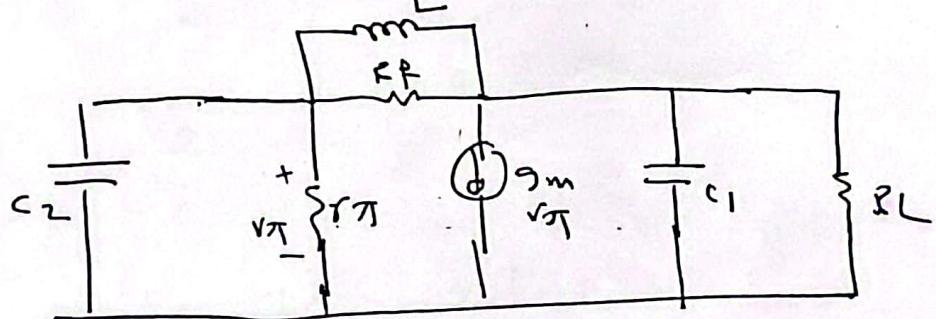Short cct $\sim \frac{1}{\omega_0^2} \propto$ میں ایک سلسلہ بی علیہ کھلے کھلے



$$r_\pi \gg C_2 \quad \text{can be neglected}$$

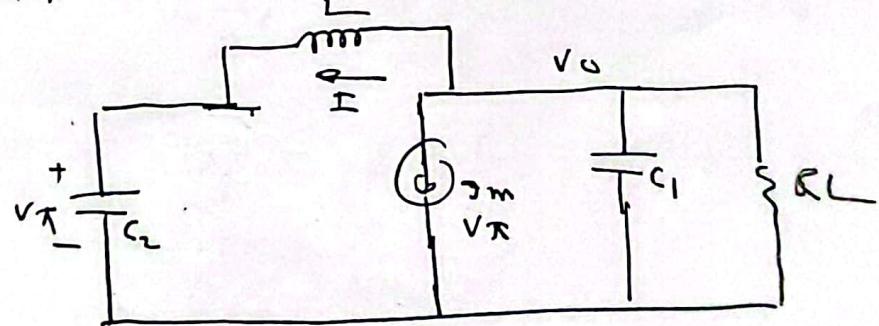also $R_F \gg \omega_0 L$ can be neglected



$$I = \frac{V_o - V_\pi}{sL} = V_\pi s C_2$$


$$C I + g_m V_\pi + V_o s C_1 + \frac{V_o}{R_L} = 0$$

(W) \rightarrow سمجھو جیا

(4)

Prob(5)

Find $L(s) = A : B$
and $L(j\omega)$

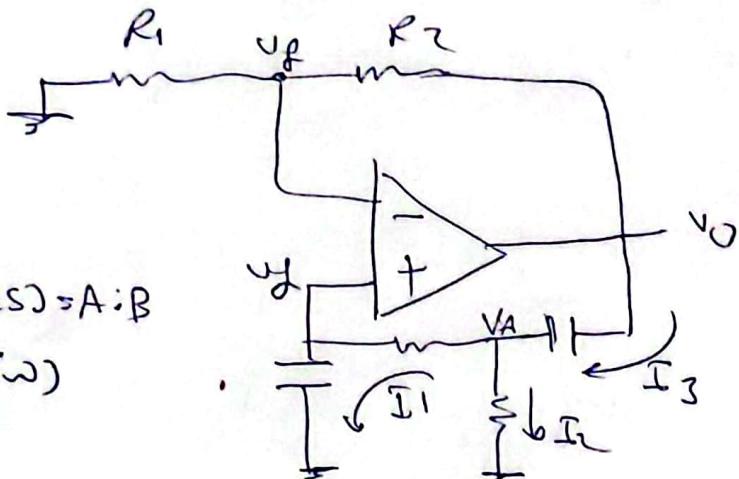

$$v_o = \left(1 + \frac{R_2}{R_1}\right) v_f$$

$$A = \frac{v_o}{v_f} = 1 + \frac{R_2}{R_1}$$

$$I_3 = (v_o - v_A) sC \rightarrow I_2 + I_1$$

$$I_2 = v_A / R$$

$$I_1 = \frac{v_A - v_f}{R} = v_f sC$$

$$\therefore v_A - v_f = v_f R sC$$

$$\boxed{v_A = (1 + R sC) v_f}$$

$$(v_o - v_A) sC = \frac{v_A}{R} + v_f sC$$

$$v_o sC - v_A sC \rightarrow \frac{v_A}{R} + v_f sC$$

$$v_o sC \rightarrow v_A (sC + \frac{1}{R}) + v_f sC$$

(5)

$$V_o SC = (1 + R_{SC})(SC + \frac{1}{R_C}) V_f + V_f SC$$

$$V_o SC = (3SC + R_S^2 C^2 + \frac{1}{R_C}) V_f$$

$$V_o = (3 + R_{SC} + \frac{1}{R_{SC}}) V_f$$

$$L(s) = A \cdot B$$

$$\beta = \frac{V_o}{V_f} = (3 + R_{SC} + \frac{1}{R_{SC}})$$

$$A = (1 + \frac{R_2}{R_1})$$

$$\therefore A \cdot B = L(s) = (3 + R_{SC} + \frac{1}{R_{SC}}) (1 + \frac{R_2}{R_1})$$


$$L(j\omega) = \left(3 + j\omega R_C - \frac{1}{j\omega C} \right) \left(1 + \frac{R_2}{R_1} \right)$$

P

#19

P. ⑨


a)

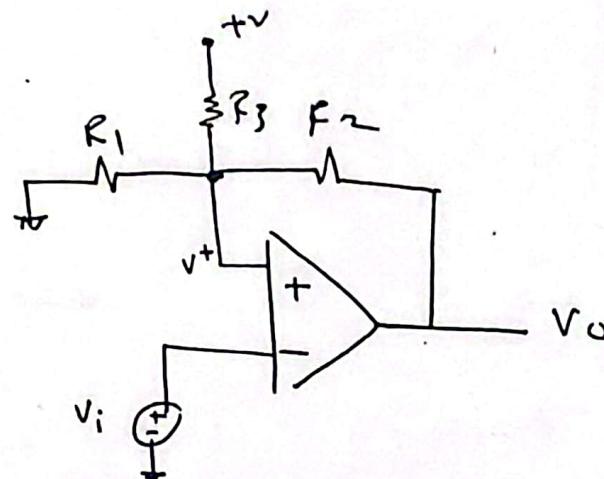

طريق التوصيب

$$(a) * \text{ when } V^+ = V_{TH} \rightarrow V_o = L^+$$
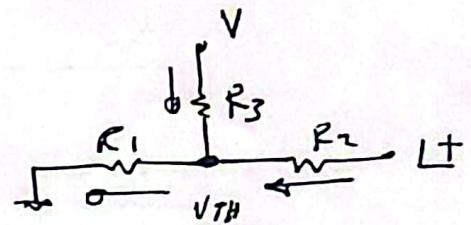
$$\frac{V_{TH}}{R_1} = \frac{V - V_{TH}}{R_3} + \frac{L^+ - V_{TH}}{R_2}$$



$$V_{TH} \left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_2} \right) = \frac{V}{R_3} + \frac{L^+}{R_2}$$

$$V_{TH} \left(\frac{1}{R_T} \right) = \frac{V}{R_3} + \frac{L^+}{R_2}, \quad R_T = R_1 \parallel R_2 \parallel R_3$$

$$V_{TH} = R_T \left(\frac{V}{R_3} + \frac{L^+}{R_2} \right)$$

$$* \text{ when } V^+ = V_{TL} \rightarrow V_o = L^-$$

in the same way

$$V_{TL} = R_T \left(\frac{V}{R_3} + \frac{L^-}{R_2} \right), \quad R_T = R_1 \parallel R_2 \parallel R_3$$

$$\textcircled{5} \quad L^+ = -L^- = 13 \text{ V} \quad V = 15 \text{ V}$$

$$R_1 = 10 \text{ k}\Omega \quad R_2, R_3 ? ?$$

$$V_{TL} = 4.9 \text{ V} \quad V_{TH} = 5.1 \text{ V}$$



$$V_{TH} * \left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_2} \right) = \frac{V}{R_3} + \frac{L^+}{R_2}$$

$$5.1 \left(\frac{1}{10} + \frac{1}{R_3} + \frac{1}{R_2} \right) = \frac{15}{R_3} + \frac{13}{R_2}$$

$$0.51 = \frac{7.9}{R_2} + \frac{9.9}{R_3} \quad \rightarrow \textcircled{1}$$

$$V_{TL} = \left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_2} \right) = \frac{15}{R_3} - \frac{13}{R_2}$$

$$0.49 = \frac{-17.9}{R_2} + \frac{10.1}{R_3} \quad \rightarrow \textcircled{2}$$


From \textcircled{1} - \textcircled{2}

$$R_2 = 856.8 \text{ k}\Omega$$

$$R_3 = 19.8 \text{ k}\Omega$$

P. (16)

ω_{22}

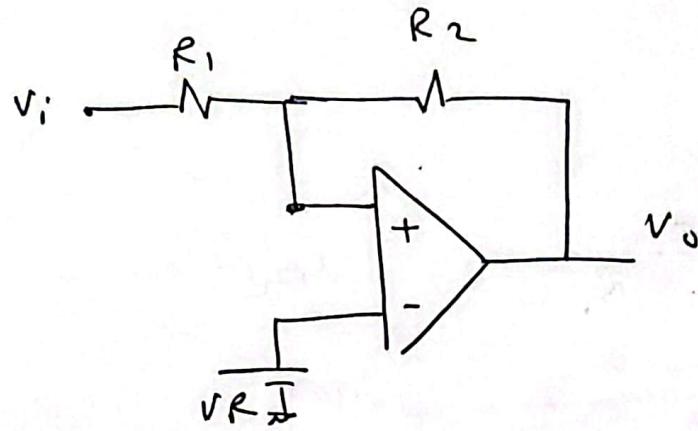

a) at $V_{TL} \rightarrow V_o = L^+ , V^+ = VR$
 و لذلک $VR \rightarrow$ مفهومی کوئی سپ جائی نی نہیں $V^+ \rightarrow L^+$
 لذلک $L^- \rightarrow V_o \rightarrow$ نہیں

$$V_i = V_{TL} \xrightarrow{R_1} \frac{L^+ - VR}{R_2} = \frac{VR - V_{TL}}{R_1}$$

$$\frac{V_{TL}}{R_1} = \frac{VR}{R_1} + \frac{VR}{R_2} - \frac{L^+}{R_2}$$



$$V_{TL} = VR + \frac{R_1}{R_2} VR - \frac{R_1}{R_2} L^+$$

$V_i > V_{TL}$
 $V^+ > VR$
 $V_o = L^+$

$$\boxed{V_{TL} = VR \left(1 + \frac{R_1}{R_2}\right) - \frac{R_1}{R_2} L^+}$$

$V_i < V_{TL}$
 $V^+ < VR$
 $V_o = L^-$

→ (1)

$$\frac{L^+ - VR}{R_2} = \frac{VR - V_{TL}}{R_1}$$


$$\frac{V_{TL}}{R_1} = VR \left(\frac{1}{R_1} + \frac{1}{R_2}\right) - \frac{L^+}{R_2}$$

$$V_{TL} = VR \left(1 + \frac{R_1}{R_2}\right) - \frac{L^+}{R_2}$$

also:

$$\text{at } V_{TH} \longrightarrow V_0 = L^- , V^+ = VR$$

L^-

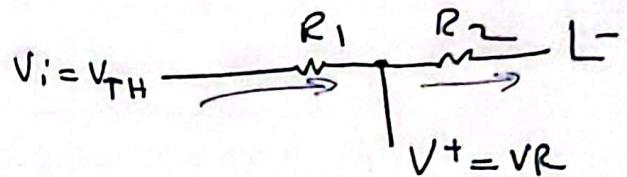

$$\frac{L^- - VR}{R_2} = \frac{VR - V_{TH}}{R_1}$$



$$\frac{V_{TH}}{R_1} = \frac{VR}{R_1} + \frac{VR}{R_2} - \frac{L^-}{R_2} \quad V_{TH} - \frac{VR}{R_1} = \frac{V_R - L^-}{R_2}$$

$$\boxed{V_{TH} = VR \left(1 + \frac{R_1}{R_2} \right) - \frac{R_1}{R_2} L^-} \rightarrow \textcircled{2}$$

$$\textcircled{5} \quad L^+ = -L^- = v , \quad f_1 = 10k$$

$$V_{TL} = 0 \quad V_{TH} = \frac{V}{I_0}$$

From \textcircled{1}:

$$0 = VR \left(1 + \frac{10}{R_2} \right) - \frac{10}{R_2} v \rightarrow \textcircled{1}$$

From \textcircled{2}:

$$\frac{v}{I_0} = VR \left(1 + \frac{10}{R_2} \right) + \frac{10}{R_2} v$$

ω_{24}

From ② - ① :

$$\frac{10}{R_2} V + \frac{10}{K_2} V = \frac{V}{10} - 0$$

$$\frac{Z_0}{R_2} = \frac{1}{10} \quad \boxed{R_2 = 20 \Omega}$$

From ① :

$$0 = V_R \left(1 + \frac{10}{200} \right) - \frac{10}{200} V$$

$$V_R \left(\frac{21}{20} \right) = \frac{1}{20} V$$

$$\boxed{V_R = \frac{V}{21}}$$




$$R_2 = 6\text{ k}\Omega$$

P. 11

sketch $V_o - V_i$

$$V_o = 0.7v$$

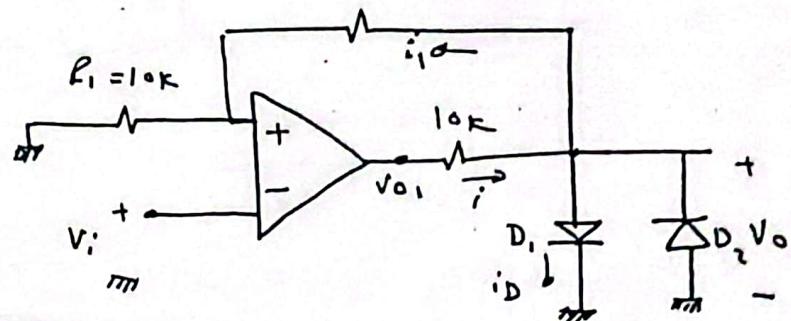

$$V_o = L^+, L^- = \pm 0.7v \quad \text{لذة} V_o \text{ على ديدون}$$

عنة مایلیو $\rightarrow V_o$ موجب فا $\sim D_{1m}$ $\sim 0.7v$

عنة مایلیو $\rightarrow V_o$ سالب فا $\sim D_{2m}$ $\sim -0.7v$

$$\Rightarrow V_{T_L} = \frac{-0.7}{10 + 60} \times 10 = -0.1v$$

$$V_{TH} = \frac{+0.7}{10 + 60} \times 10 = +0.1v$$




$$i = \frac{12 - 0.7}{10} = \frac{11.3}{10} = 1.13 \text{ mA}$$

$$i_1 = \frac{0.7}{10 + 60} = 0.01 \text{ mA}$$


$$i_{D_{max}} = i_{D_1} = i - i_1 = 1.13 - 0.01$$

$$= 1.12 \text{ mA}$$

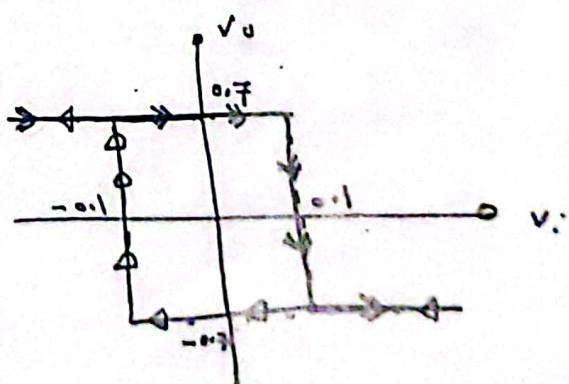


٢٦

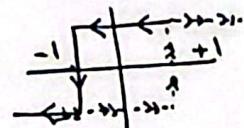P. 12 a bistable Circuit having an non inverting transfer char



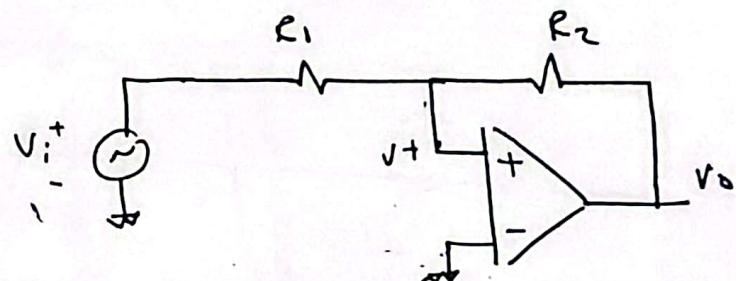
$$L^+ = L^- = 12V \quad V_{TL} = -1V \quad V_{TH} = +1V$$



non-inv. bistable


$$\textcircled{a} \quad V_{in} = 0.5V$$

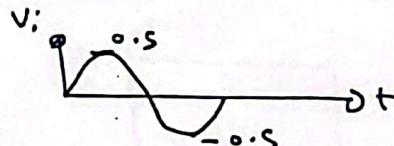

هذا вход لا يكفي لتبديل حالة المايكرو مزنت اتى من

$$(-12V, 12V) \quad V_o = \pm 12V$$
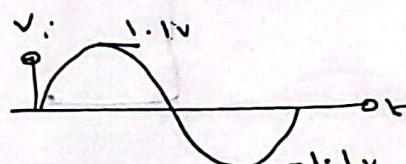
$$\textcircled{b} \quad V_i = 1.1 \sin \theta$$



$$\therefore V_{TH} = \underline{\underline{1V}}$$

.. عندما يصل V_i الى ١١ فولت تاتر يما $V^+ > 0$ و يما $V^- < 0$


$$\therefore V_o = L^+$$

و عندما يصل V_i الى -١١ فولت تاتر يما $V^+ < 0$ و يما $V^- > 0$


$$\therefore V_o = L^-$$

$$I = 1.1 \sin \theta$$
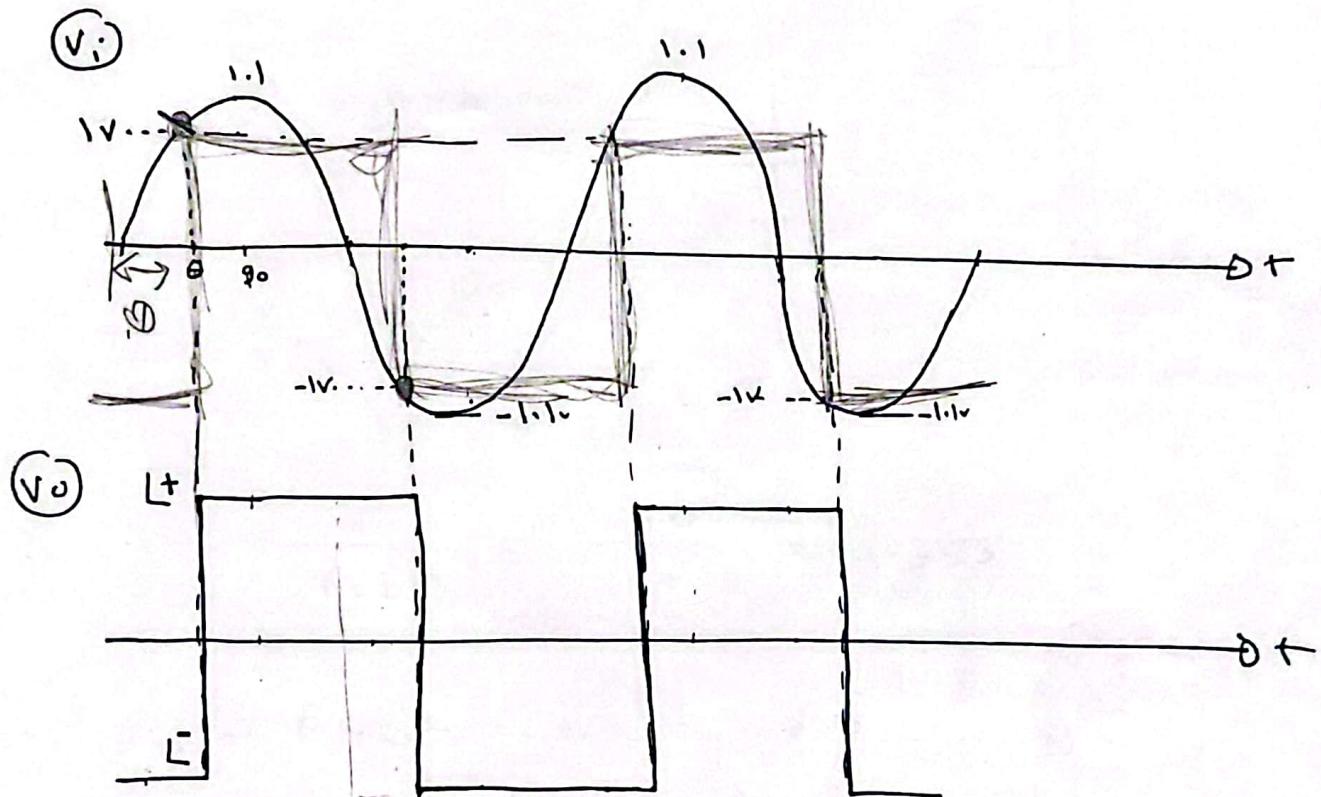
$$\sin \theta = \frac{1}{1.1} \quad \theta = \underline{65.4^\circ}$$


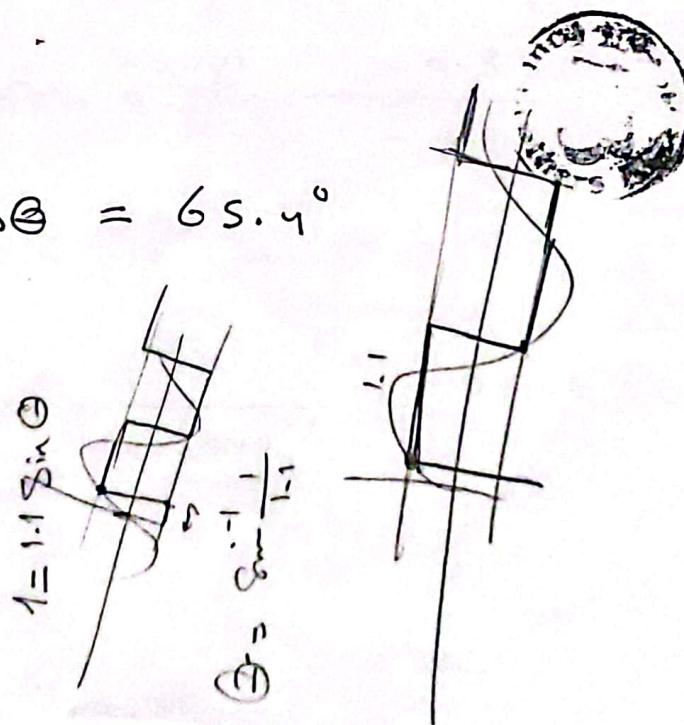
$$\text{shift} = \Delta \theta = 65.4^\circ$$




P. (13)

موجات مربعية متذبذبة

Square wave generator

موجات متذبذبة متعددة
multivibrators J1

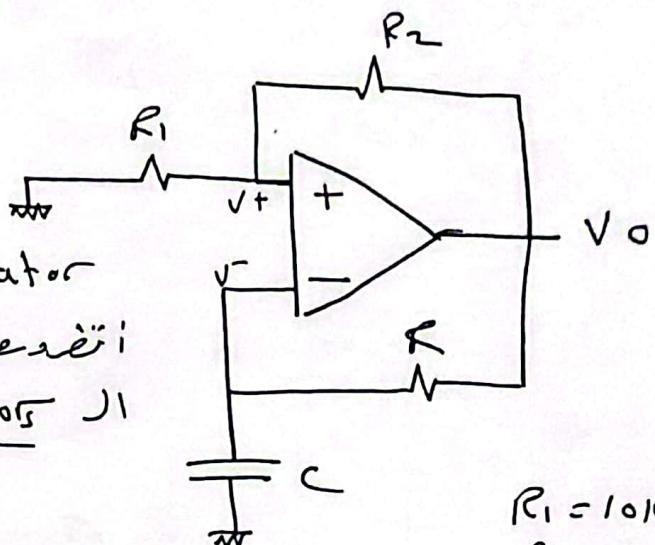

$$\begin{aligned}R_1 &= 10\text{k}\Omega \\R_2 &= 16\text{k}\Omega \\C &= 10\text{nF} \\R &= 62\text{k}\Omega\end{aligned}$$

$$T = 2\pi \ln \frac{1+B}{1-B}$$

$$B = \frac{R_1}{R_1 + R_2} = \frac{10}{10 + 16} = 0.385$$

$$\begin{aligned}\tau &= RC = 62 \times 10^3 \times 10 \times 10^{-9} \\&= 6.2 \times 10^{-5} \text{ sec}\end{aligned}$$


$$\therefore T = 2 \times 6.2 \times 10^{-5} \ln \frac{1 + 0.385}{1 - 0.385}$$

$$T = 1.006 \times 10^{-3} \text{ sec}$$

$$f = \frac{1}{T} = \frac{1}{1.006 \times 10^{-3}} = 994.04 \text{ Hz}$$

P. (14) inv. bistable multivibrator

W₂₉

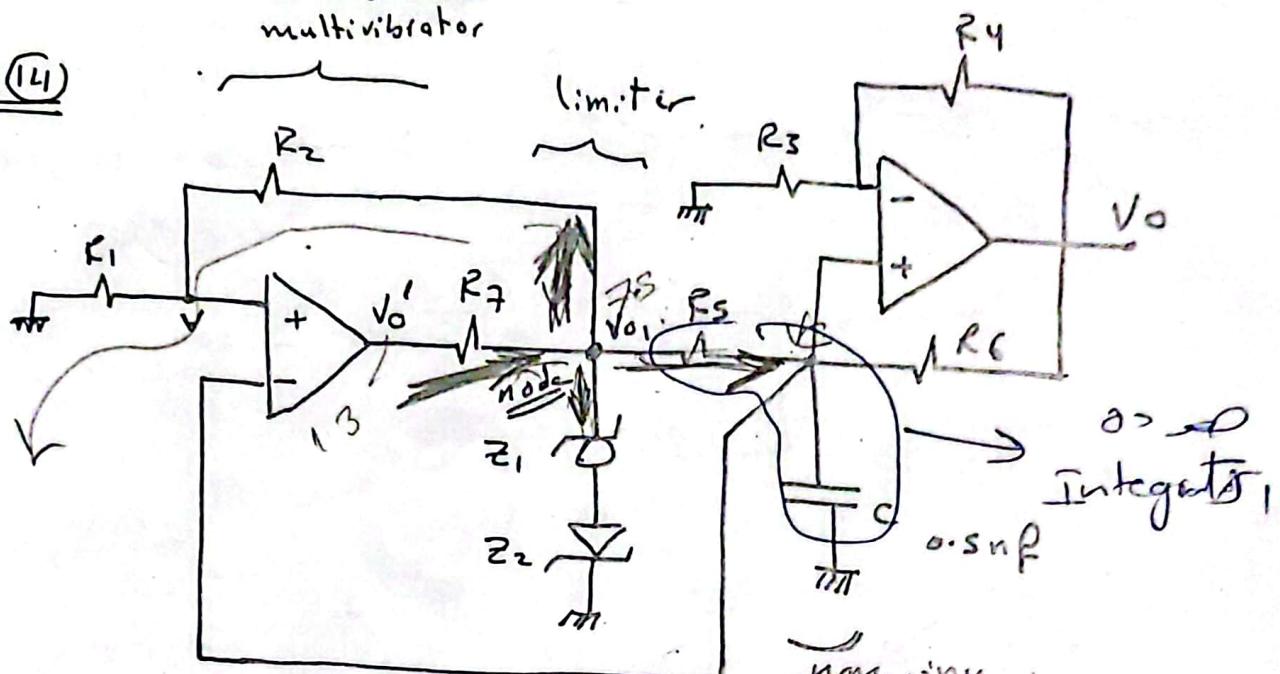

$$V_{O_1} = \pm 15V, f = 10\text{kHz} \text{ (square-wave)}$$

$$R_i \rightarrow R_6 = R$$

$$L^+, L^- = \pm 13V$$



$$I_{Z_{\min}} = 1mA \quad V_{O_{1\max}} = \frac{\pm 15}{2} = \underline{\underline{\pm 7.5V}} = V_p$$

when $V_{O_1} = +7.5V$ (Z_1 break, Z_2 forward) $V_{O_{1\max}}$ peak

$$V_{O_1} = V_{Z_1} + V_{Z_2}$$

$$V_{Z_1} = V_{O_1} - V_{Z_2} = \left(\frac{15}{2} \right) - (-0.7) \\ = 6.8V$$

Also when $V_{O_1} = -7.5V$ (Z_1 forward, Z_2 break)

$$V_{Z_2} = -7.5 - (-0.7) = -6.8V$$

$$|V_{Z_2}| = 6.8V$$

$$V_{Z_1} = V_{Z_2} = 6.8 \text{ V} ; V_X = 0.7 \text{ V}$$


$$V = \frac{V_{O_1} R}{R + R}$$

$$V = \frac{V_{O_1}}{2}$$


$$= \pm 7.5/2$$

نلاحظ في عند ما يمتحن
الـ V_{O_1} من $+7.5$ نحو -7.5 ص

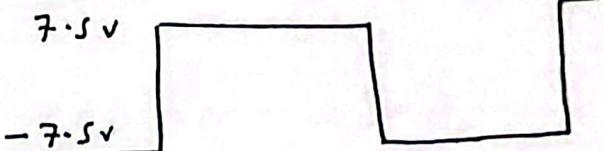يصل $V^+ = V$ \rightarrow V^- نحو $-7.5/2$!



V_C

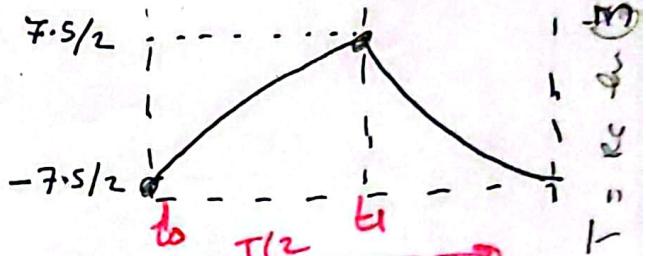

لذلك $-7.5 \leq V_{O_1} \leq 7.5$

$V_C(t_1) = \left(\frac{1}{RC} \int_{t_0}^{t_1} (V_{O_1} dt) \right) + V_C(t_0)$

$$\frac{7.5}{2} = \frac{1}{RC} (t_1 - t_0) (7.5 - (-7.5)) - \frac{7.5}{2}$$

$$t_1 - t_0 = \frac{T}{2}$$

$$\therefore 7.5 = \frac{1}{RC} \frac{T}{2} \quad (15)$$

$$R = \frac{T}{C}$$

$T = R_f \ln(3)$

$$f = \frac{1}{RC}$$

T_f

$$T_f = \frac{7.5}{7.5 + 0.7} = \frac{7.5}{8.2} = 0.902 \text{ s}$$

$$T_f = \frac{7.5}{7.5 + 0.7} = \frac{7.5}{8.2} = 0.902 \text{ s}$$

$$T_f = 7.5 - (7.5 + \frac{7.5}{2}) e^{-\frac{7.5}{7.5 + 0.7}}$$

w31

$$R = \frac{1}{10^4 (0.5 \times 10^{-9}) (2)} = 200 \text{ k}\Omega \quad \begin{array}{l} \text{1} \\ \text{2 ln}(3) \text{ P.C.} \\ \ln(3) \approx 1 \end{array}$$

$$\therefore R_1 \rightarrow R_C = 200 \text{ k}\Omega \quad \cancel{\text{look}}$$


$$R_1 \rightarrow R_L$$

For minimum zero Current = 1mA

node: $V_o' = \pm 13$

$$\frac{13 - 7.5}{R_7} = 1 + \frac{7.5}{R_1 + R_2} + \frac{7.5 - V_C}{R_S}$$

The maximum Current in the integrator is

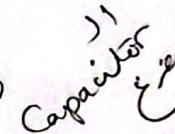when $V_C = -\frac{7.5}{2}$ 


$$\frac{5.5}{R_7} = 1 + \frac{7.5}{400} + \frac{11.25}{200}$$

$$\therefore R_7 = 5.12 \text{ k}\Omega$$



$$\frac{5.5}{R_7} = 1 + \frac{7.5}{200} + \frac{15}{100}$$

$$0.025 \quad 0.01525 \quad 0.025$$

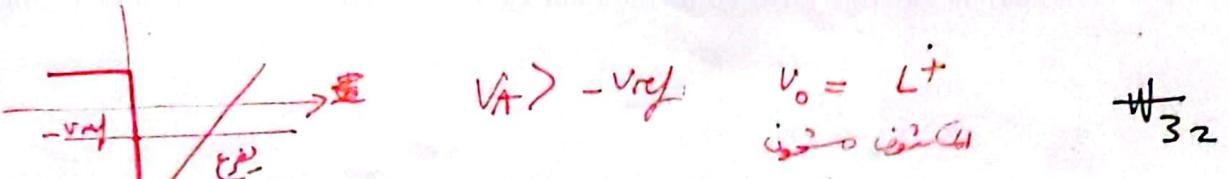

P. 15


$$V_A > -V_{ref} \quad V_o = L^+$$

اللکٹن سخنے

#32

$$V_A < -V_{ref} \quad V_o = L^-$$

اللکٹن بیسخ

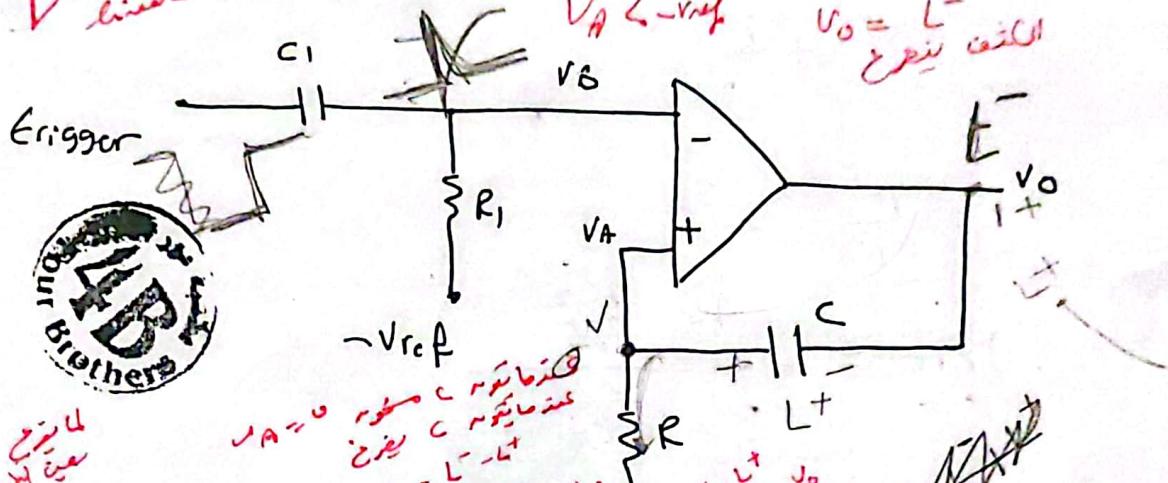

لایخ : بندی مخصوص
و $V_B = 0$
 $V_o = 0$

$$V_o = L^+, \quad V_A = 0, \quad V_B = -V_{ref}$$

لکٹن سخنے کا داد L^+ وعند نقطہ $V_A = 0$ بقیے

$$V_A = -L^+ + L^+ = 0$$

$$V_B \text{ میلوں سے بستولت ہے}$$

$$V_A \xrightarrow[-]{L^+} L^+$$

Trigger

$$V_o = L^- \xrightarrow[-]{L^+} V_A = 0 \xrightarrow[-]{L^-} \text{ میلوں سے اعلان مدد، } L^- \text{ میلوں سے آخر جو}$$

$$\text{ہو}$$

$$V_A \xrightarrow[-]{L^+} L^- \text{ (Trigger سے رخصی لے) }$$

$$V_A = -L^+ + L^- \text{ ہو } V_A \rightarrow -L^+ \\ = -(L^+ - L^-) = 2L^-$$

وھر لنتھے لئے یہ سدھا لکٹن سخنے سخنے (L^+)

و کلام خر عالم کا ملتا ہے (+) الہ سخنے سخنے و بدلہ تعلق فہمیہ
ال V_A ہو سہ دشوار اس ترتیب قیاس بے لازمی کرنا یہ سابھ

$V_A \rightarrow R$ فہمیہ لے


ترندر

عند يصل المدخل من V_A نخرج $-V_{ref}$

الـ L^+ صرارة أخذ ورحلة ...

$$V_o = L^- \rightarrow \text{التذييل}$$

ويخرج بـ L^+ مخزن تلو ... بـ L^+ لـ L^-

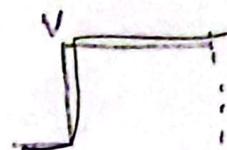

$$V_c = V_p + (V_i - V_p) e^{-t/\tau}$$

$$V_p = 0$$


$$V_i = -(L^+ - L^-) = L^- - L^+$$

$$V_c = -(L^+ - L^-) e^{-t/\tau} + L^+$$

$$\text{at } t = T \quad V_c = -V_{ref}$$

$$V_c = -V_{ref}$$

$$-V_{ref} = -(L^+ - L^-) e^{-T/\tau}$$

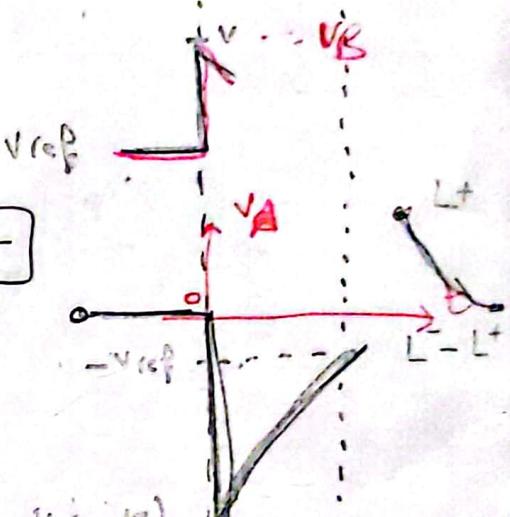

$$-T = \tau \ln \frac{V_{ref}}{L^+ - L^-}$$



$$T = \tau \ln \frac{L^+ - L^-}{V_{ref}} \quad \tau = RC$$

$$\therefore T' = RC \ln \frac{L^+ - L^-}{V_{ref}}$$

المدة التي يستغرقها
نحو L^+

$$L^- - L^+ = -(L^+ - L^-)$$

$$-L^+$$