

Contents

Experiments

- 1- Phase Shift Oscillator
- 2- Wien Bridge Oscillator
- 3- Astable Multivibratos
- 4- Colpitt Oscillator

Experiment (1)

Phase Shift Oscillator

Objective:

This experiment is demonstrated the operation of RC sine wave phase shift oscillator.

The required components and Equipment:

- 1- Three resistance 10 K ohm
- 2- Three Capacitors of 2.2 nF
- 3- LM 741
- 4- Power Supply of 12 and -12 volt
- 5- Wight Board
- 6- Oscilloscope

Procedures:

- Connect the circuit as shown in Fig.1.1 by using the 741 datasheet in Fig. 1.2.
- Connect channel 1 of the oscilloscope with the output of the op-amp.
- Measure the frequency of oscillations.

Circuit Diagram:

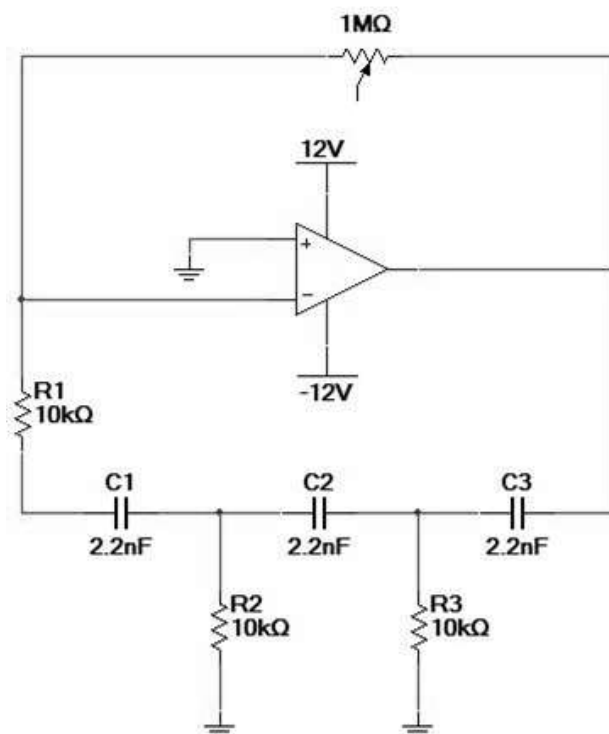


Figure 1.1: Phase Shift Oscillator Circuit


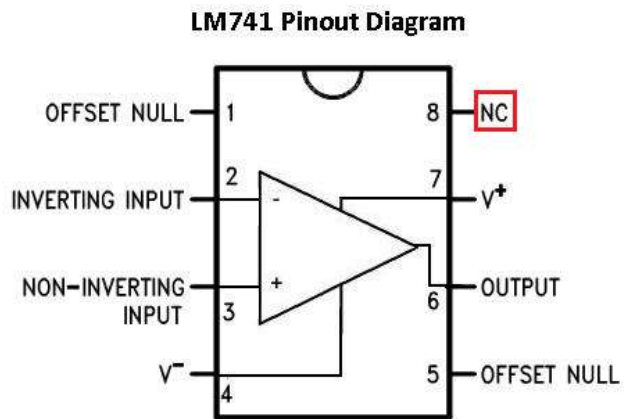


Figure 1.2: 741 Op-Amp Datasheet

Results:

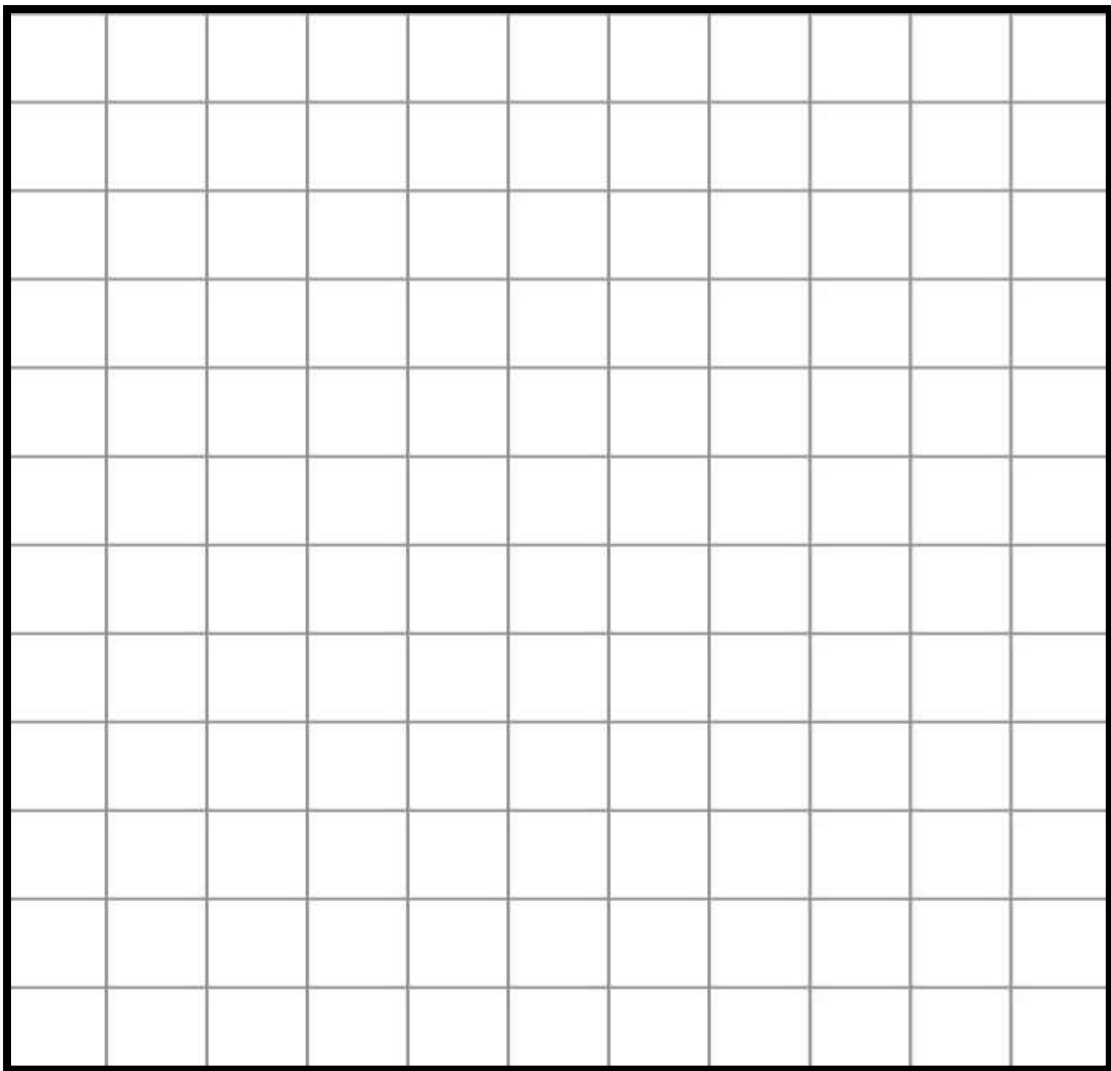- Sketch the output wave form and record the measured frequency.
- Compare between the calculated and measured frequency.



Experiment (2)

Wien Bridge Oscillator

Objective:

The experiment is intended to familiarize the student with the operation of RC sine wave Wien bridge oscillator.

The required components and Equipment:

- 1- Variable resistor 1 M ohm
- 2- Two Capacitors 16 nF
- 3- Two resistor of 10 Kohm
- 4- One 47 K ohm
- 5- Power Supply of 12 and -12 volt
- 6- Oscilloscope
- 7- LM741
- 8- Wight Board

Procedures:

- Connect the circuit as shown in Fig.2.1 by using the 741 datasheet in Fig. 2.2.
- Adjust the variable resistance 1 M ohm to 106Kohm.
- Connect the output voltage to the oscilloscope channel.
- Compare the measurement with calculation and the results from oscilloscope.

Circuit Diagram:

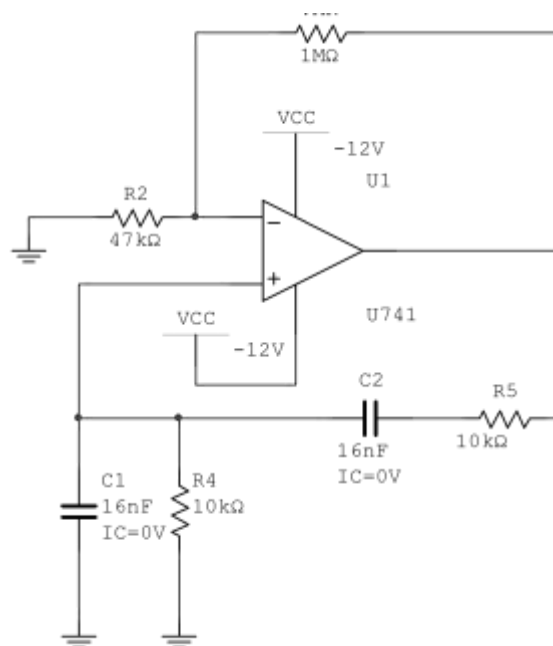


Figure 2.1: Wien Bridge Oscillator Circuit

LM741 Pinout Diagram


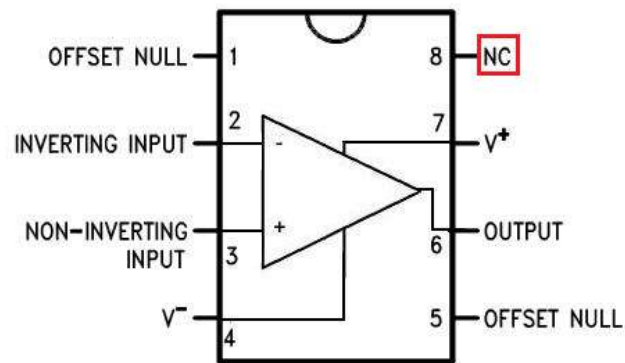


Figure 2.2: 741 Op-Amp Datasheet

Results:

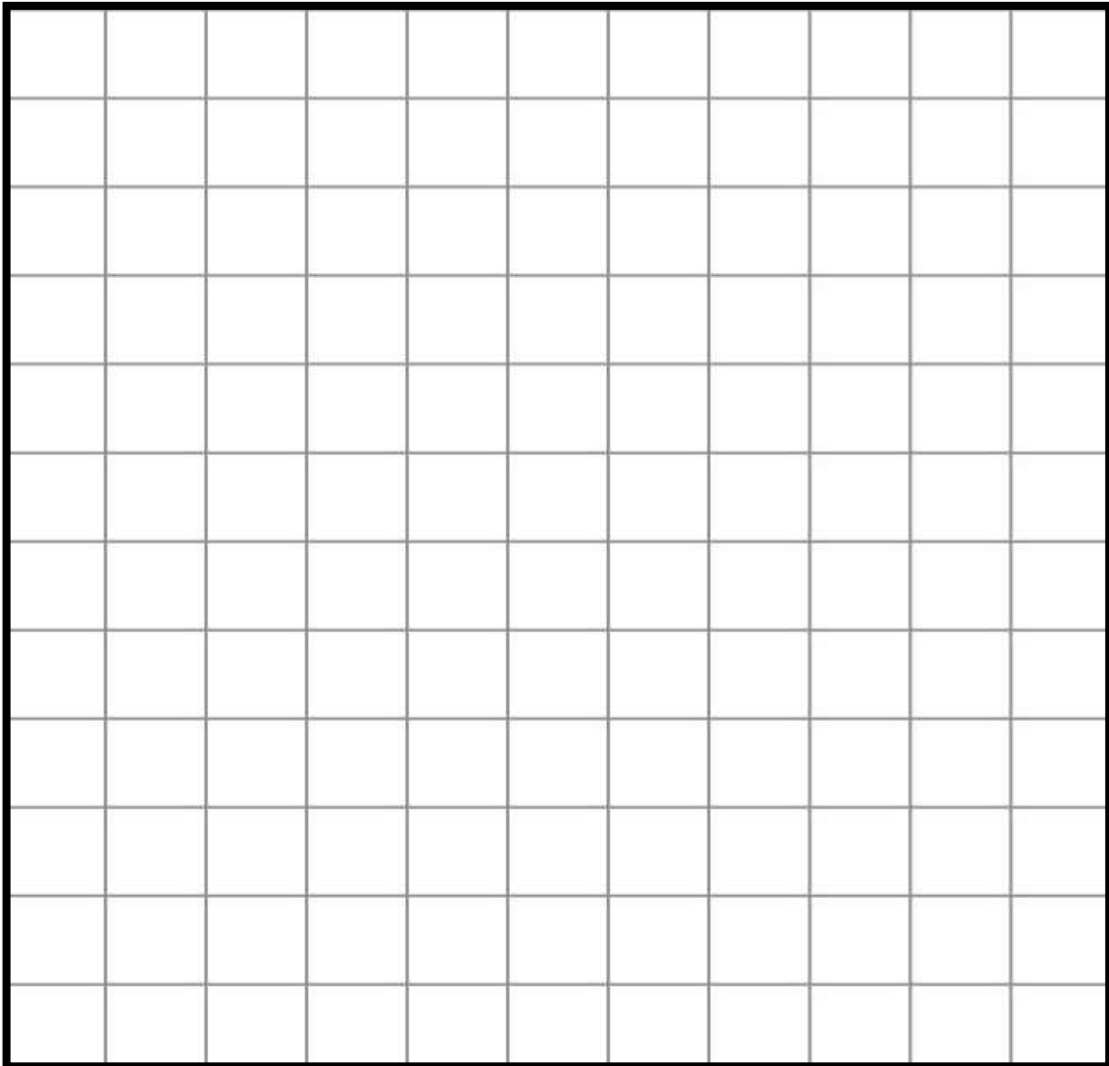- Sketch the output waveform and record the measured frequency.
- Compare your frequency measured with the calculated frequency and $f = \frac{1}{2\pi RC}$



Experiment (3)

Astable Multivibrators

Objective:

The experiment is intended to design and implement Astable Multivibrator with IC 555 as shown in figure.

The required components and Equipment:

- 1- Function Generator
- 2- One chip LM555
- 3- One capacitor 1 μF
- 4- Two resistances 1 K ohm
- 5- Oscilloscope
- 6- Multimeter
- 7- Supply 15V

Procedures:

- Study the operation of the circuit shown in Fig.3.1.
- Connect the component.
- Connect this circuit with oscilloscope and measure and draw the output wave shaping.

Circuit Diagram:

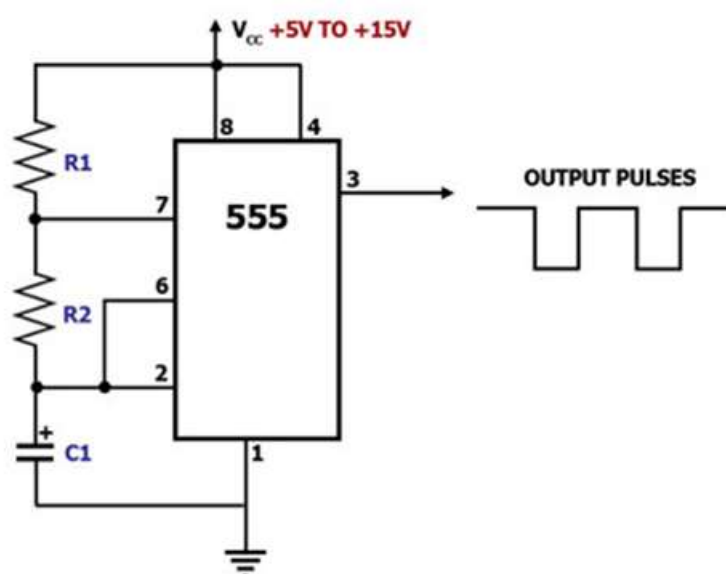


Figure 3.1: 555 Astable Multivibrator Circuit

Results:

- Calculate the output frequency and state the design equations .

Experiment (4)

Colpitts Oscillator

Objective:

This experiment is demonstrated the operation of Colpitts sine wave phase shift oscillator.

The required components and Equipment:

- 1- Variable Resistance 1M ohm
- 2- Resistance 1Kohm
- 3- Two Capacitors of 2.2 nF
- 4- LM741
- 5- Power Supply of 12V and -12V
- 6- Inductor 105 mH
- 7- Wight Board
- 8- Oscilloscope

Procedures:

- Connect the circuit as shown in Fig.4.1 by using the 741 datasheet in Fig. 4.2.
- Connect channel 1 of the oscilloscope with the output of the op-amp.
- Measure the frequency of oscillations.

Circuit Diagram:

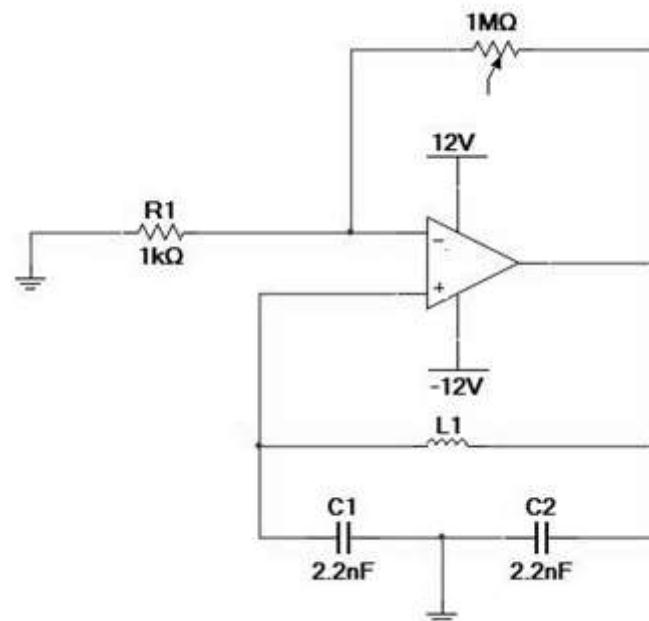


Figure 4.1: Colpitts Oscillator Circuit

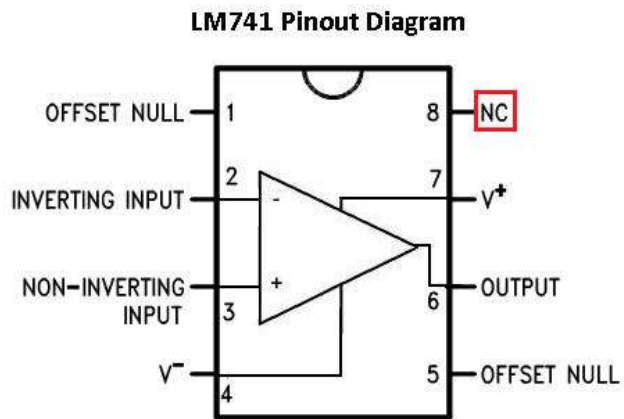


Figure 4.2: 741 Op-Amp Datasheet

Results:

- Sketch the output wave form and record the measured frequency.
- Compare between the calculated and measured frequency.

