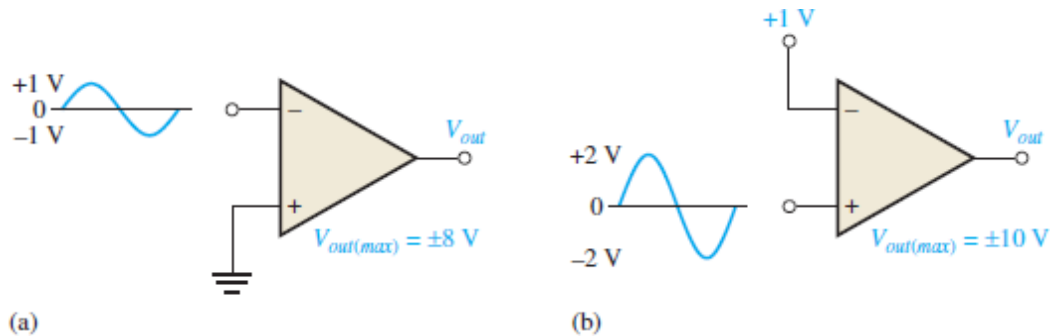


Electronic Circuits


Op- Amp

Sheet 3


1. Draw the output voltage waveform for each circuit shown with respect to the input. Show voltage levels.



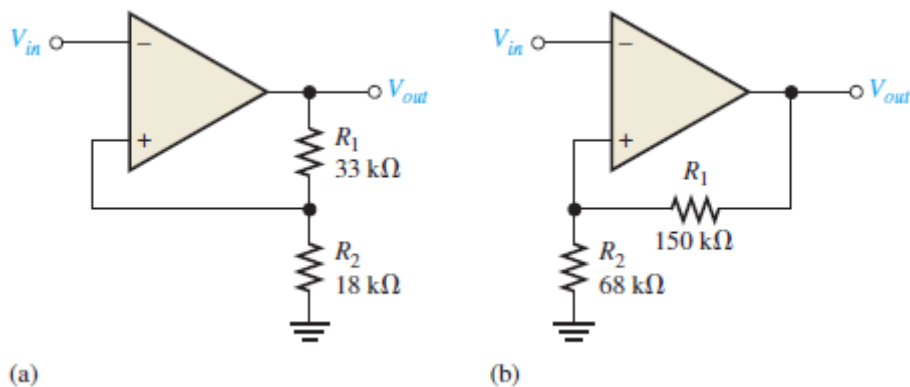
2. Determine the hysteresis voltage for each comparator shown. The maximum output levels are $\pm 11 \text{ V}$.



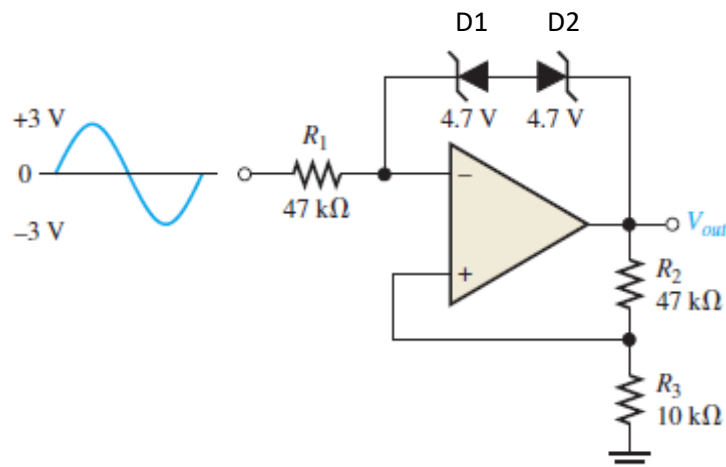
3. Determine the output voltage waveform in the following figure.



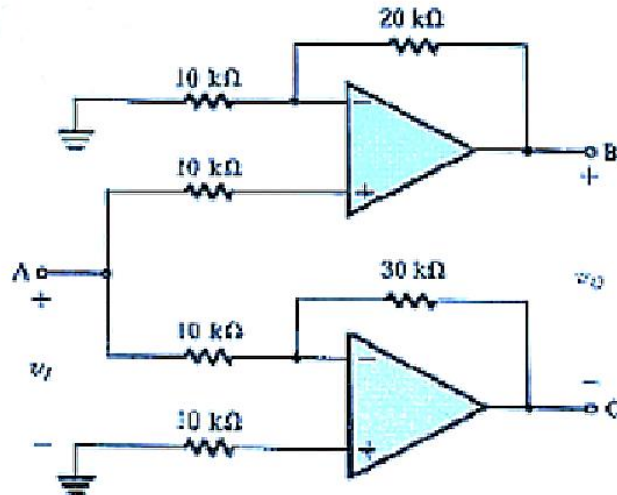4. Design a noninverting amplifier with the gain of 2. At the maximum output voltage of 10V the current in the voltage divider is to be $10\ \mu\text{A}$.
5. Calculate V_B , V_C and the voltage gain ($V_{\text{out}}/v_{\text{in}}$) for the circuit shown



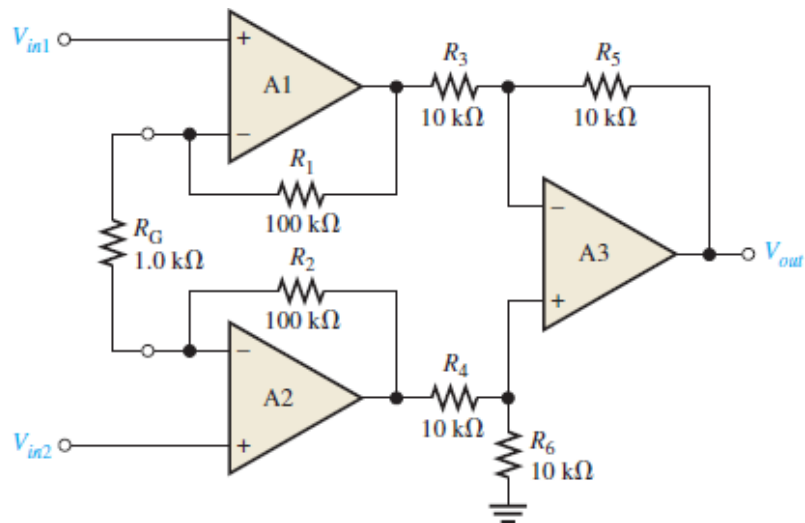6. For the instrumentation amplifier configuration shown in figure.
 - a) Find the voltage gains of op-amps A_1 and A_2 .
 - b) Find the overall voltage gain of the instrumentation amplifier
 - c) The following voltages are applied to the instrumentation amplifier: $V_{in1} = 5\text{mV}$, $V_{in2} = 10\text{mV}$, $V_{cm} = 225\text{mV}$. Determine the final output voltage.
 - d) What value of R_G must be used to change the gain of the instrumentation amplifier to 1000?



7. For instrumentation amplifier shown, derive an expression for i_o

