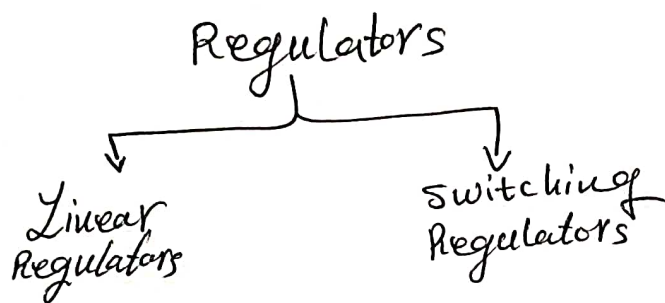



Voltage Regulators

* A Voltage Regulator circuit is a ct. that provides a constant DC o/p voltage independent of i/p Voltage, o/p load current & Temperature.




Linear Regulators :

1 Series-Regulator :

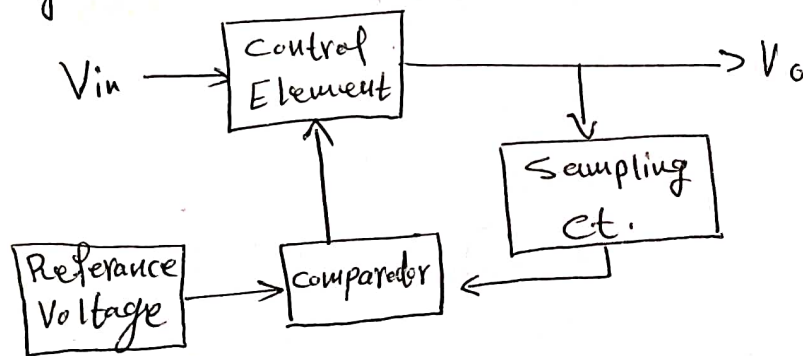

* Transistor series Voltage Regulator :

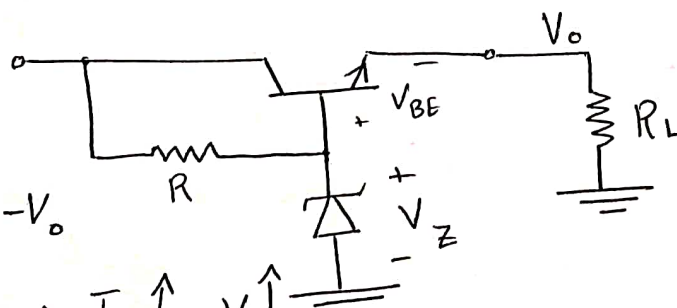


$$\Rightarrow V_{BE} = V_Z - V_o$$

* if $V_o \downarrow \Rightarrow V_{BE} \uparrow \Rightarrow I_E \uparrow \Rightarrow V_o \uparrow$
 $(V_o = I_E R_L)$

* if $V_o \uparrow \Rightarrow V_{BE} \downarrow \Rightarrow I_E \downarrow \Rightarrow V_o \downarrow$
 $I_E = I_s e^{\frac{V_{BE}}{V_T}}$

Ex:

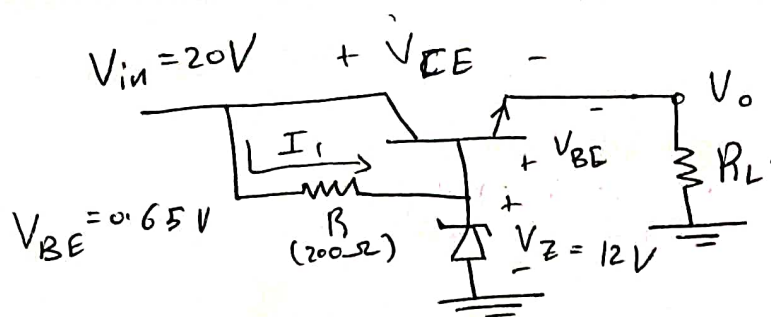


Find:

- 1) V_o
- 2) V_{CE}
- 3) I_1

Sol:

- 1) $V_o = V_Z - V_{BE} = 12 - 0.65 = 11.35 \text{ V}$
- 2) $V_{CE} = \underbrace{20}_{(V_{in})} - V_o = 20 - 11.35 = 8.65 \text{ V}$ (Active Mode)
- 3) $I_1 = \frac{V_{in} - V_Z}{R} = \frac{20 - 12}{200} = 40 \text{ mA}$

* Improved series Regulator

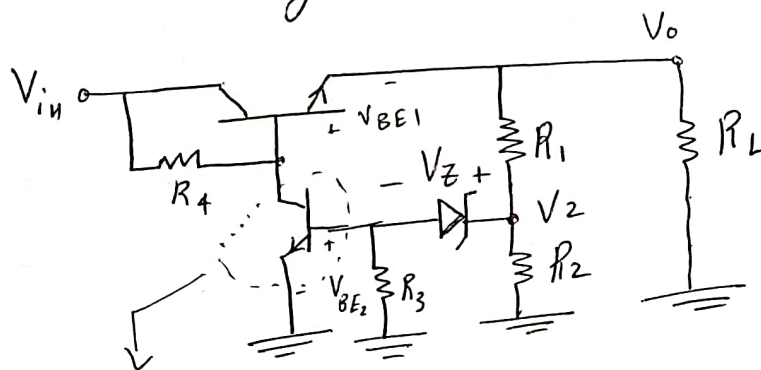

Adding An Amplifier in the feedback path increases feedback gain \rightarrow detects smaller changes in $V_o \rightarrow$ Retains more stable o/p Voltage.

* Assuming the Zener is not loading the divider ($R_1 - R_2$):

$$\Rightarrow V_2 = \frac{V_o}{R_1 + R_2} \cdot R_2, \quad V_2 = V_{BE2} + V_Z$$

$$\rightarrow \text{if } V_o \downarrow \rightarrow V_2 \downarrow \rightarrow V_{BE2} \downarrow \rightarrow V_{CE2} \uparrow \rightarrow V_{BE1} \uparrow \rightarrow V_o \uparrow$$

$V_{CE2} = V_{in} - I_1 R_4$
 $\approx V_{in} - I_{L2} R_4$

EX: For an improved series Regulator:

$$R_1 = 50 \text{ k}\Omega, R_2 = 43.75 \text{ k}\Omega, V_Z = 6.3 \text{ V}$$

$V_o = 15 \text{ V}$ drops by 0.1 V load change

in V_{BE2} . Let $V_o = 15 \text{ V}$, $V_o' = 15 - 0.1 = 14.9 \text{ V}$

Sol:

$$V_2 = \frac{R_2}{R_1 + R_2} (V_o) = \frac{43.75}{93.75} (15) = 7 \text{ V}$$


$$V_2' = \frac{R_2}{R_1 + R_2} (V_o') = \frac{43.75}{93.75} (14.9) = 6.953 \text{ V}$$

$$V_{BE2} = V_2 - V_Z = 7 - 6.3 = 0.7 \text{ V}$$

$$V_{BE2}' = 6.953 - 6.3 = 0.653 \text{ V}$$

$$\Rightarrow \Delta V_{BE2} = 0.7 - 0.653 = 0.047 \text{ V}$$

* OP-Amp series Regulator :

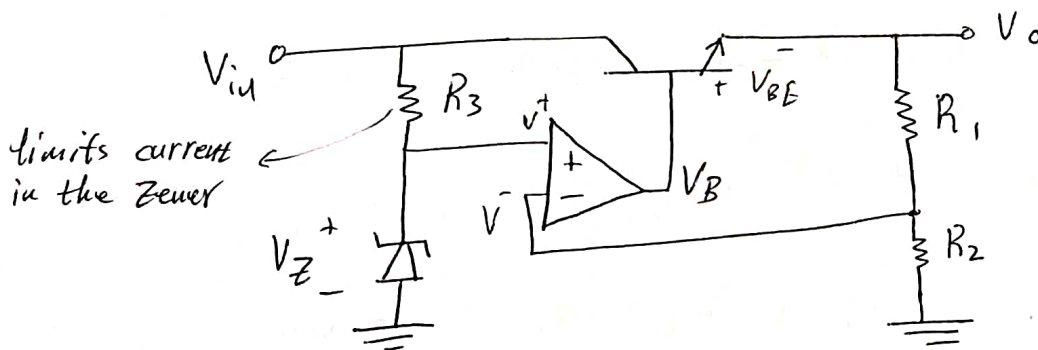

$$\Rightarrow V^+ = V_Z$$

$$V^- = \frac{V_o}{R_1 + R_2}, \quad V_B \propto (V_Z - V^-)$$

$$\text{As } V_o \downarrow \rightarrow V^- \downarrow \rightarrow V_B \uparrow \rightarrow V_{BE} \uparrow \rightarrow I_E \uparrow \rightarrow V_o \uparrow$$


* To find V_o : op-Amp here is acting as non-inverting Amplifier. [neglecting effect of V_{BE}]

$$V_o = \left(1 + \frac{R_1}{R_2}\right) V_Z$$

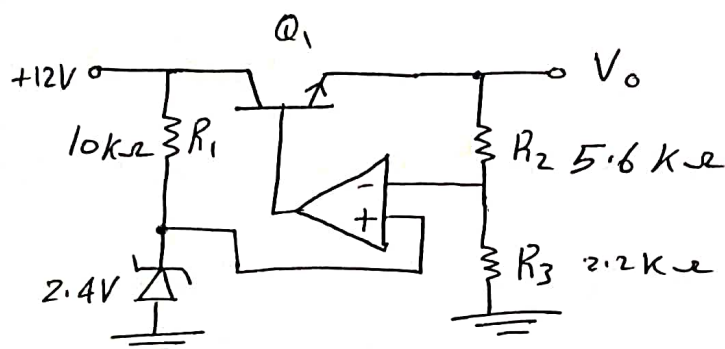Q4 - For the shown series Regulator

4

- Find the output Voltage (V_o).
- if R_3 increased to $4.7K$, what happens to V_o .
- if the Zener Voltage is $2.7V$ instead of $2.4V$ what will V_o be?




Sol:

$$\begin{aligned} a - V_o &= \left(1 + \frac{R_2}{R_3}\right) V_Z \\ &= \left(1 + \frac{5.6}{2.2}\right) (2.4) = 8.5 V \end{aligned}$$

$$b - V_o = \left(1 + \frac{5.6}{4.7}\right) (2.4) = 5.26 V$$

$$c - V_o = \left(1 + \frac{5.6}{2.2}\right) (2.7) = 9.57 V$$

* Short-circuit or overload protection:

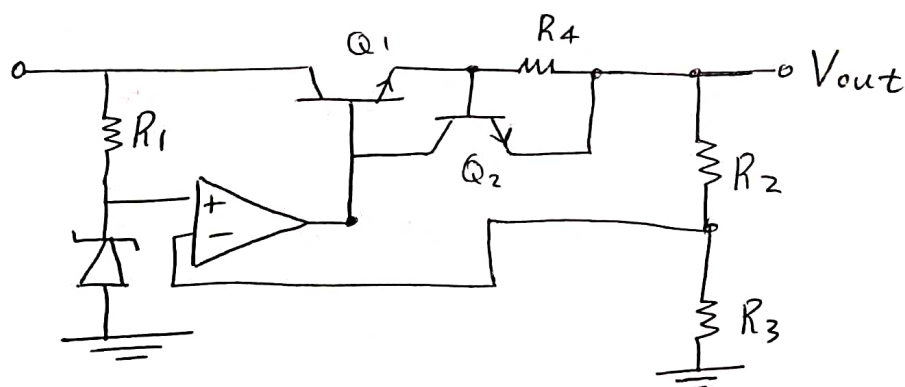

* if the current passing through R_4 is small that $I_{out} R_4 < 0.7V$
 $\rightarrow Q_2$ is cut-off & has no-effect.

* if the o/p current is high enough that $I_{out} R_4 = 0.7V$
 $\rightarrow Q_2$ switches on \rightarrow decreasing I_{B1} & hence limiting the o/p current at:

$$\boxed{I_{L(max)} = \frac{0.7}{R_4}}$$


Q2 - A series voltage regulator with constant-current limiting is shown.

a - Find the value of R_4 if the load current to be limited to max. value of 250 mA.

b - What power rating must R_4 have.

c - if R_4 is halved, what is the max. load current.

Sol:

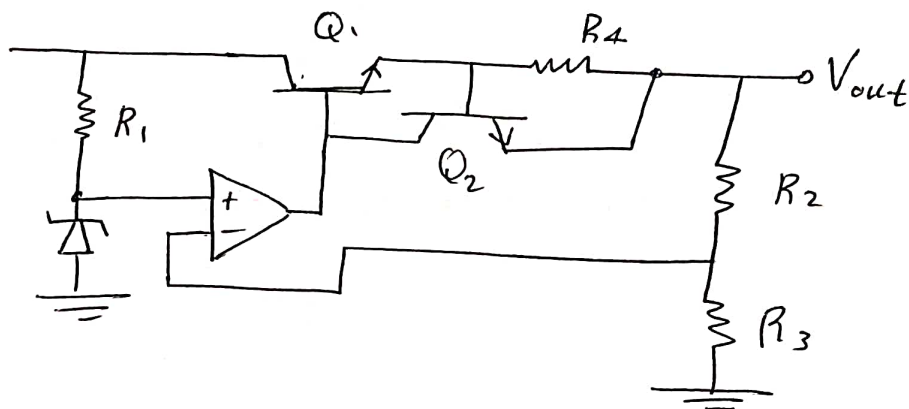

$$a - I_{L_{max}} = \frac{0.7}{R_4}$$

$$\Rightarrow R_4 = \frac{0.7}{0.25} = 2.8 \Omega$$

$$b - P = I^2 R$$


$$\Rightarrow P_{rated} = (I_{L_{max}})^2 R_4 = (2.8)(0.25)^2 = 0.175 W$$

$$c - \text{if } R_4' = \frac{R_4}{2} = 1.4 \Omega$$

$$\Rightarrow I_{L_{max}} = \frac{0.7}{1.4} = 500 mA$$

OP-Amp shunt voltage Regulator :

6

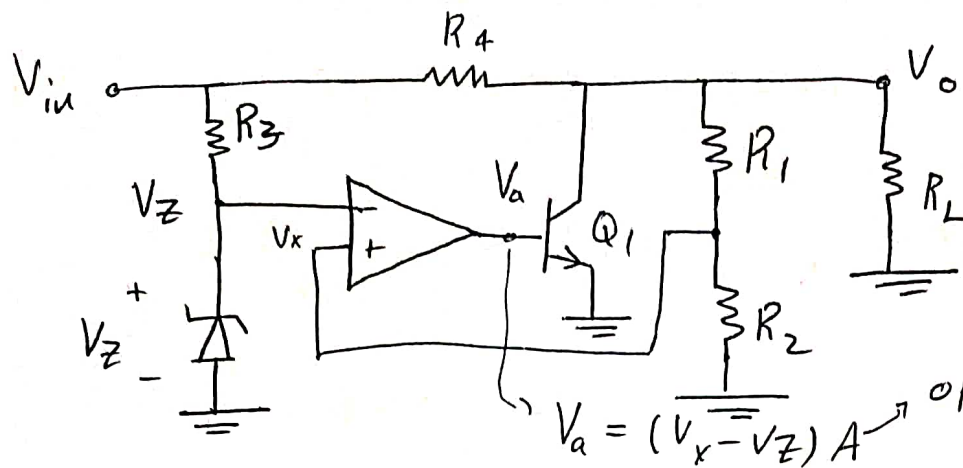

$$V_a = (V_x - V_Z) A \quad \text{OP-Amp gain}$$

as $V_o \uparrow \rightarrow V_x \uparrow \Rightarrow V_a \uparrow \Rightarrow Q_1$ conducts higher current
 \hookrightarrow less current through R_L ($I_L \downarrow$)
 $\hookrightarrow V_o \downarrow$

$$V_x = \frac{R_2}{R_1 + R_2} V_o$$

\hookrightarrow loop will try to eliminate difference between V_x & V_Z .

$$\text{at } V_x = V_Z \Rightarrow V_Z = \frac{R_2}{R_1 + R_2} V_o$$

$$\Rightarrow V_o = \left(1 + \frac{R_1}{R_2}\right) V_Z$$

$$* I_{s.c} = \frac{V_{in}}{R_4} \quad (\text{short ct. current})$$

Q3 - For an op-Amp shunt Regulator if

$$R_4 = 100 \Omega, \quad R_3 = 12 K\Omega, \quad R_1 = 10 K\Omega, \quad R_2 = 3.9 K\Omega$$

$$V_Z = 5.1 V$$

a - Assume I_L remains constant & V_{in} changes by 1V
 what change in collector current of Q_1 will take place?

b - with constant V_{in} if R_L changed from $1 K\Omega$ to $1.2 K\Omega$
 (neglecting change in V_o) find change in shunt current through Q_1 .

a- $\because V_o$ is constant $\rightarrow I_L \rightarrow$ constant

$$\Rightarrow \Delta I_c = \frac{\Delta V_{in}}{R_A} = \frac{1V}{100} = 10mA$$

$$b- V_o = \left(1 + \frac{R_1}{R_2}\right) V_z = \left(1 + \frac{10}{3.9}\right) (5.1) = 18.2V$$

$$I_{L1} = \frac{18.2}{1K} = 18.2mA$$

$$I_{L2} = \frac{18.2}{1.2K} = 15.2mA$$


$$\Rightarrow \Delta I_L = \Delta I_c = 3mA$$

Switching Regulators :


* By switching the opp voltage we can get different equivalent DC Voltage (current)
(using PWM)

Duty cycle

$$\Rightarrow D = \frac{T_H}{T}$$

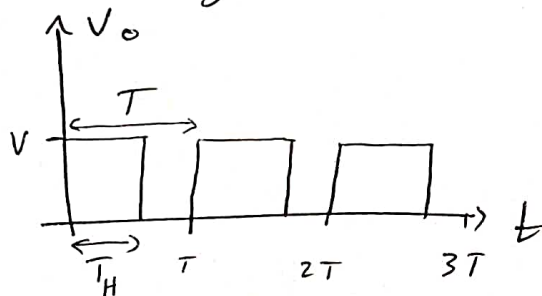

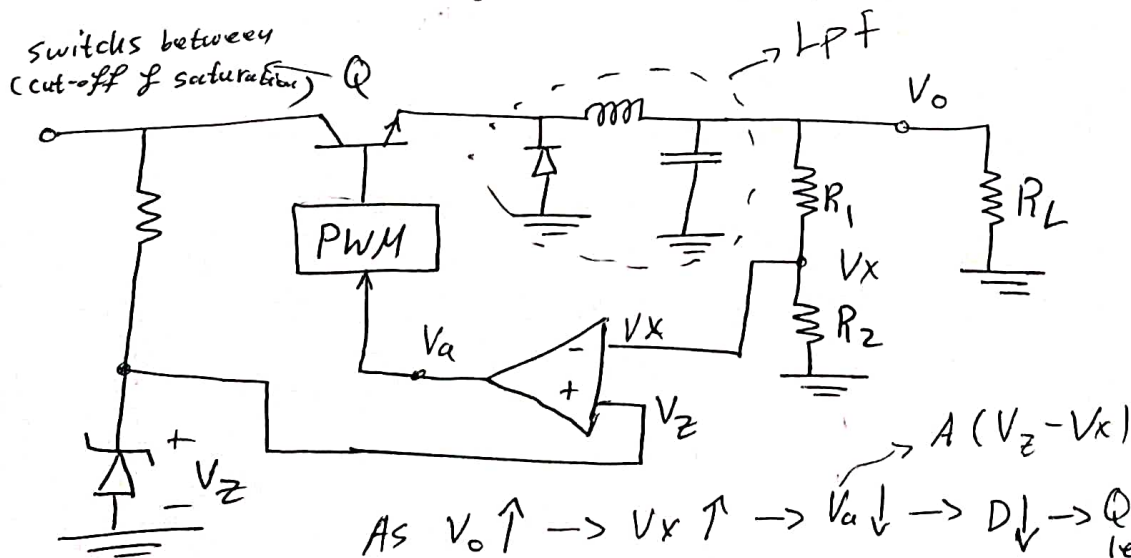
$$\Rightarrow V_{d.c} = \frac{1}{T} \int_0^T V_o dt = \frac{1}{T} \int_0^{T_H} V_H dt = V_H \left(\frac{T_H}{T}\right) = V_H \cdot D$$



As $V_o \uparrow \rightarrow V_x \uparrow \rightarrow V_a \downarrow \rightarrow D \downarrow \rightarrow Q$ conducts less current
 $V_o \downarrow$

Q₄ - For the Shown Regulator, if the switching frequency is 10 KHz & off-Time is 60 μ s [8]

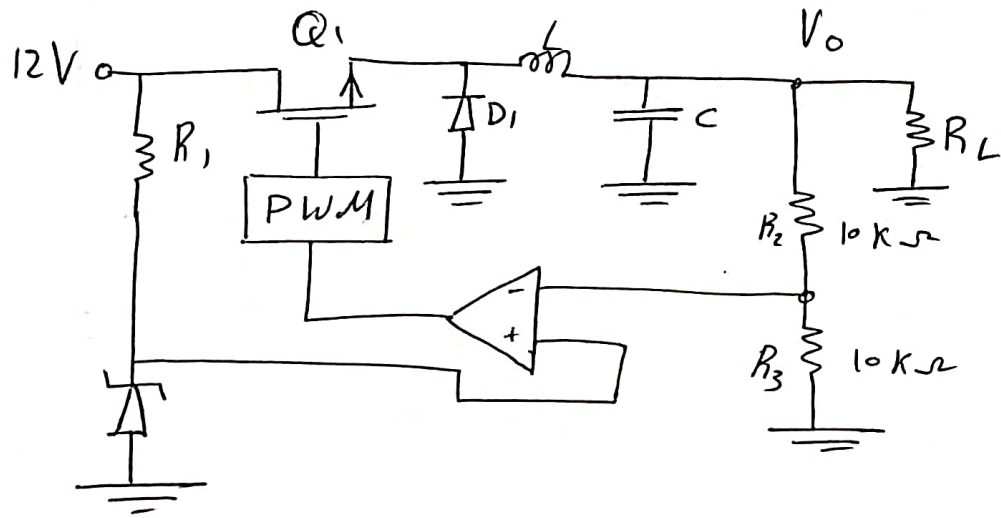a) What is the o/p Voltage? (Neglect V_{DS} drop).



b) Find the percent duty cycle

c) when does the diode D_1 turns on (forward-biased)?

50%:

$$a) \quad V_o = V_{in} \left(\frac{T_H}{T} \right) \quad , \quad \frac{T_H}{T} = 60 \mu s$$

$$T = \frac{1}{f} \quad , \quad f = 10 \text{ KHz} \quad \left\{ \begin{array}{l} T_{off} = 60 \mu s \\ T_{on} = 100 - 60 = 40 \mu s \end{array} \right.$$

$$= \frac{1}{10^4} = 10^{-4} = 100 \mu s$$

$$\Rightarrow V_o = 12 \left(\frac{40}{100} \right) = 4.8 \text{ V}$$

$$b) \quad D = \frac{40}{100} \times 100\% = 40\%$$

c) D_1 will be forward biased when Q_1 Turns-off