



Electronic Systems

Active Filters

Sheet 2

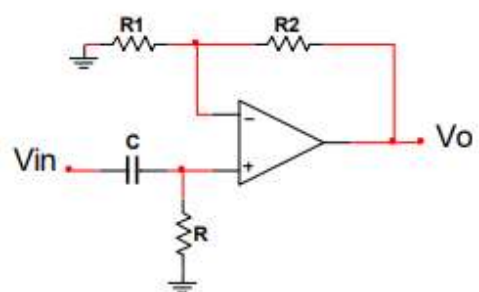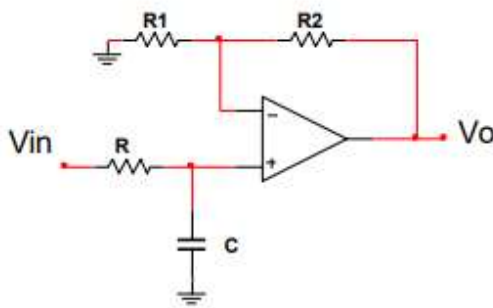1. For the circuits shown:



- Derive the Circuit transfer function $A_v(S)$.
- Determine the maximum gain (A_m) and cutoff frequency f_c .
- Determine the unity gain frequency f_T .
- Design the circuit for maximum gain of 20 and cutoff freq. of 20 KHz.
- What is the type of the filter?



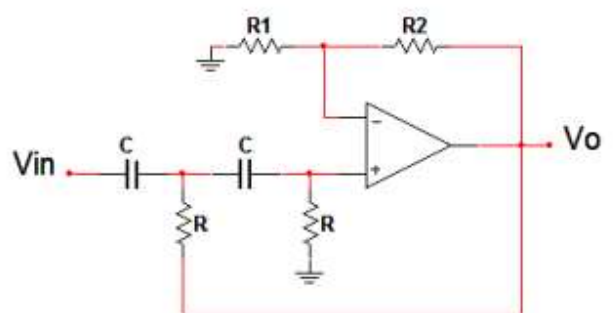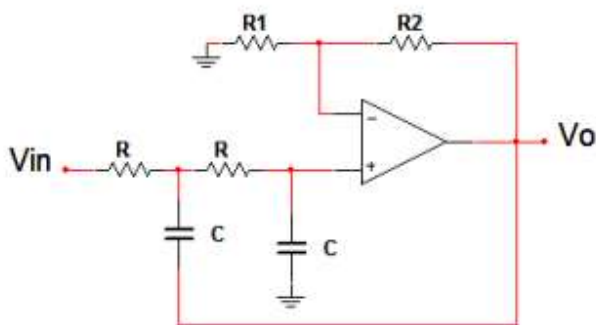2. For the circuits shown:

- Derive the Circuit transfer function $A_v(S)$.
- Determine the maximum gain (A_m) and cutoff frequency (f_c).
- Design the circuit for cutoff frequency of 10 KHz.

Given: for $n=2$ the Butterworth polynomial $B_n(S)$ is $(S^2 + 1.414S + 1)$.



3. Design a 3rd order Butterworth LPF with a cut-off frequency 30 KHz.
For $n = 3$, $B_n(S) = (S+1)(S^2 + S+1)$.
4. Design a 5th order Butterworth LPF with a cut-off frequency of 50 KHz.
For $n = 5$, $B_n(S) = (S+1)(S^2 + 0.618S+1)(S^2 + 1.618S+1)$.
5. Design a 5th order Butterworth BPF with an operating frequency band from 10 KHz to 50 KHz. For $n = 5$, $B_n(S) = (S+1)(S^2 + 0.618S+1)(S^2 + 1.618S+1)$.
6. Design a 6th order Butterworth BSF with a rejection frequency band from 20 KHz to 60 KHz. For $n = 6$, $B_n(S) = (S^2 + 0.517638S+1)(S^2 + 1.414214S+1)(S^2 + 1.931852S+1)$.