

- 1- Consider an amplifier circuit using a BJT having $I_S = 10^{-15} \text{ A}$, a collector resistance $R = 6.8 \text{ k}\Omega$, and a power supply $V_{CC} = 10 \text{ V}$. Determine the value of the bias voltage V_{BE} required to operate the transistor at $V_{CE} = 3.2 \text{ V}$. What is the corresponding value of I_C ?
- 2- The transistor in Fig. 1 is biased with a constant current source $I = 1 \text{ mA}$ and has $\beta = 100$ and $V_A = 100 \text{ V}$.
 - (a) Find the dc voltages at the base, emitter, and collector.
 - (b) Find g_m , r_π , and r_o .
 - (c) If terminal Z is connected to ground, X to a signal source v_{sig} with a source resistance $R_{sig} = 2 \text{ k}\Omega$, and Y to an 8-k Ω load resistance, use the hybrid- π model, to draw the small-signal equivalent circuit of the amplifier. Calculate the overall voltage gain v_y / v_{sig} .

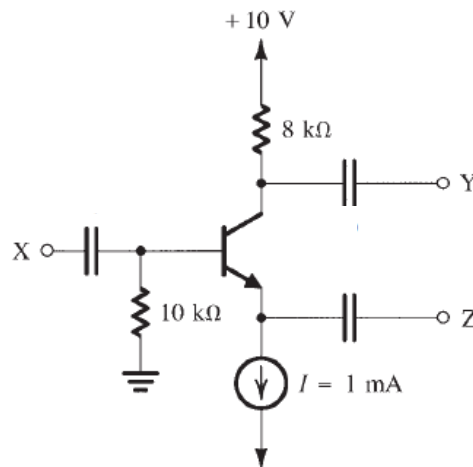


Fig.1

- 3- The amplifier circuit in Fig. 2 has the following parameters: $R_C = 1 \text{ k}\Omega$, $R_2 = R_{F1} = R_{F2} = 20 \text{ k}\Omega$, $R_S = 10 \text{ k}\Omega$, $r_\pi = 1 \text{ k}\Omega$, $\beta = 100$, and $r_o = \infty$.
 - a) Draw the small-signal equivalent circuit.
 - b) Determine the voltage gain.

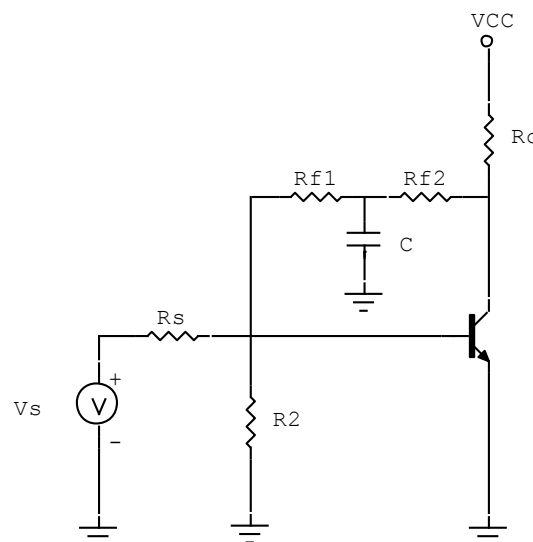


Fig.2

- 4- For the common-emitter amplifier shown in Fig. 3, let $V_{CC} = 15\text{ V}$, $R_1 = 27\text{ k}\Omega$, $R_2 = 15\text{ k}\Omega$, $R_E = 2.4\text{ k}\Omega$, and $R_C = 3.9\text{ k}\Omega$. The transistor has $\beta = 100$. Calculate the dc bias current I_C . If the amplifier operates between a source for which $R_{sig} = 2\text{ k}\Omega$ and a load of $2\text{ k}\Omega$, replace the transistor with its hybrid- π model, and find the values of R_{in} , R_o , A_{vo} , A_v and the overall voltage gain G_v (v_o/v_{sig}).

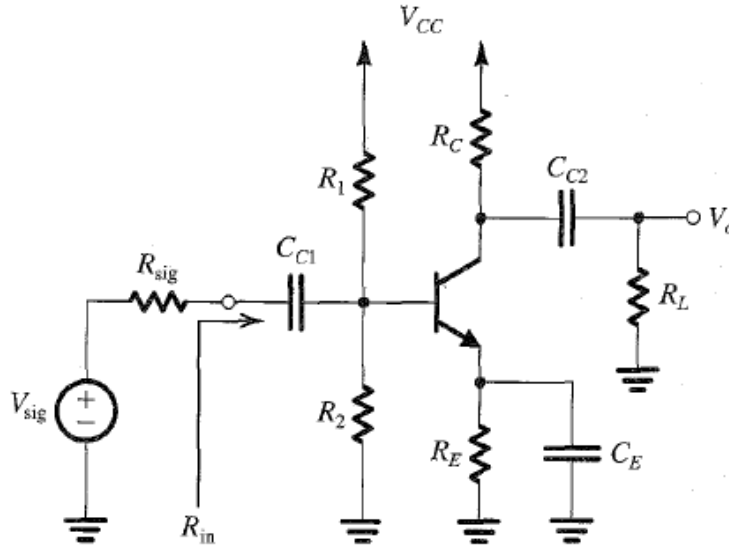


Fig. 3

- 5- For the common-emitter amplifier with an Emitter resistance shown in Fig. 4. Find the equations of R_{in} , R_o , A_{vo} , A_v and the overall voltage gain G_v (v_o/v_{sig}).

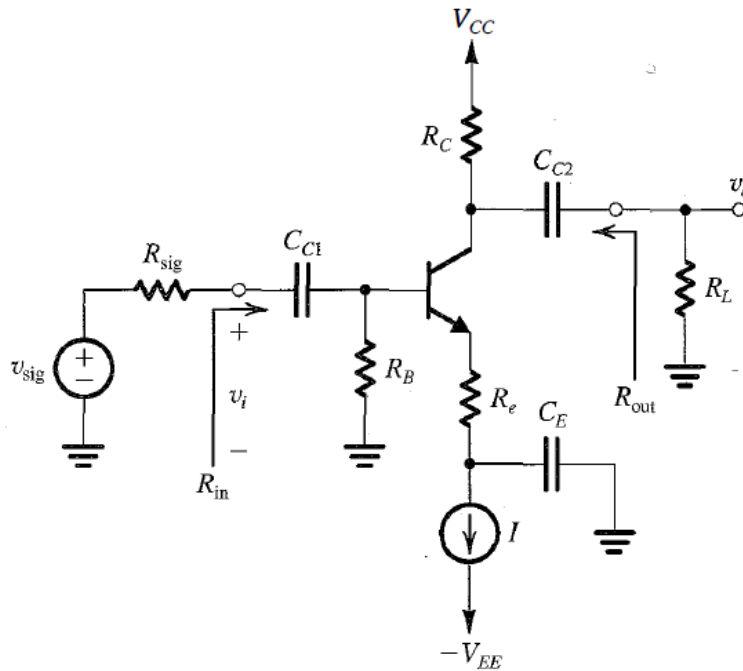


Fig. 4

- 6- In the circuit shown in Fig. 5, the transistor has a β of 200. What is the dc voltage at the collector? Find the values of R_{in} , R_o , and the overall voltage gain (v_o/v_{sig}). For an output signal of ± 0.4 V, what value of v_{sig} is required?

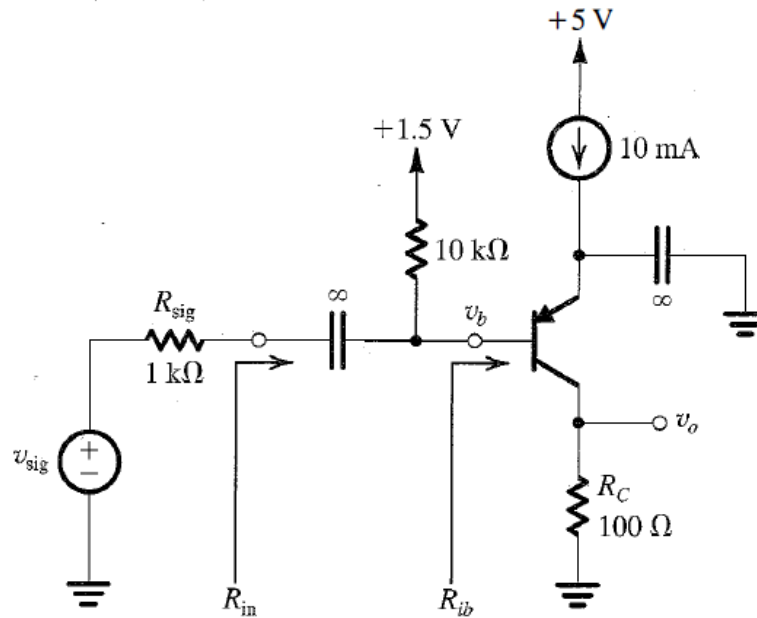


Fig. 5

- 7- For the Common-Base (CB) amplifier shown in Fig. 6, if $R_S = 100 \Omega$, $R_E = 4.3 K\Omega$, $R_C = 2.2 K\Omega$, $R_L = 51 K\Omega$ and $\beta = 100$. What are the overall voltage gain v_o/v_{sig} , input resistance and output resistance of the amplifier if the DC operating collector current ($I_C = 1$ mA).

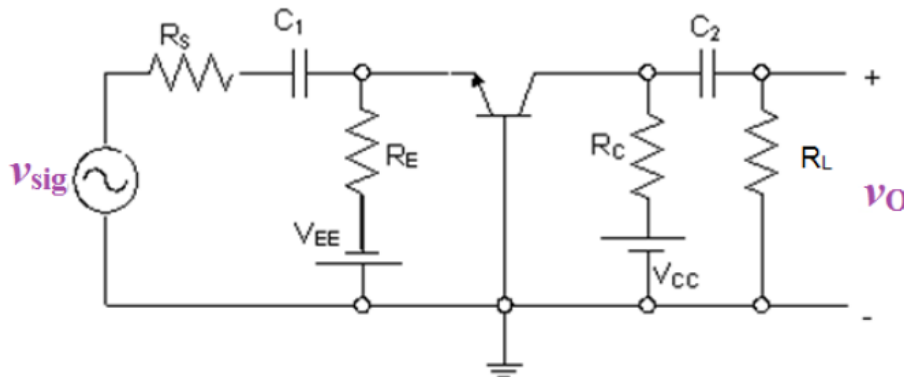


Fig. 6

- 8- For the Common-Collector amplifier shown in Fig. 7:
 $R_S = 2 K\Omega$, $R_1 = 100 K\Omega$, $R_2 = 300 K\Omega$, $R_3 = 13 K\Omega$, $R_4 = 100 K\Omega$, $\beta = 100$ and $I_C = 0.25$ mA. Find the input resistance, output resistance and the overall voltage gain v_{out}/v_{sig} ?


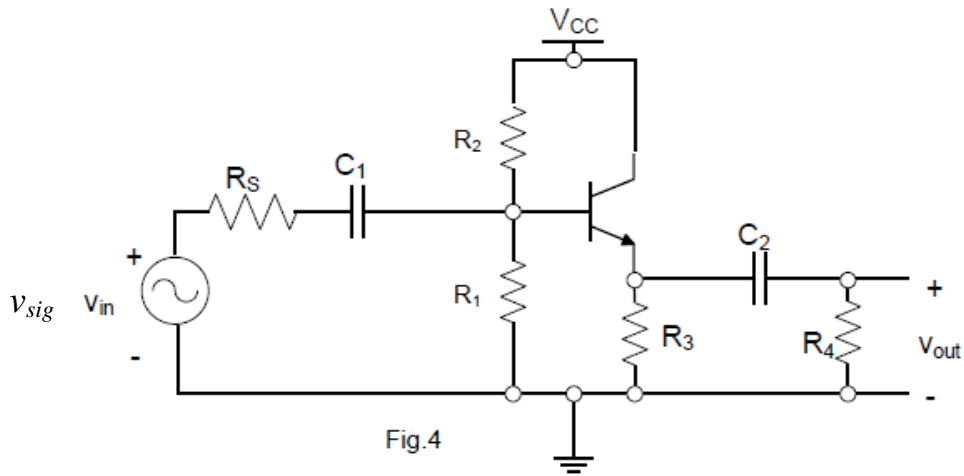


Fig. 7

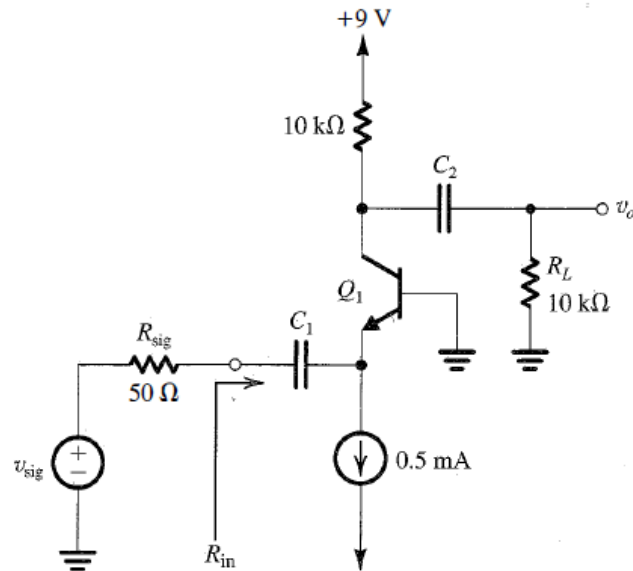- 9- For the circuit shown in Fig. 8, draw a complete small-signal equivalent circuit utilizing an appropriate T model for the BJT (use $\alpha = 0.99$). Your circuit should show the values of all components, including the model parameters. What is the input resistance R_{in} ? Calculate the voltage gain (v_o / v_{sig}).



Best Wishes

Dr. Eman F. Sawires

..... End