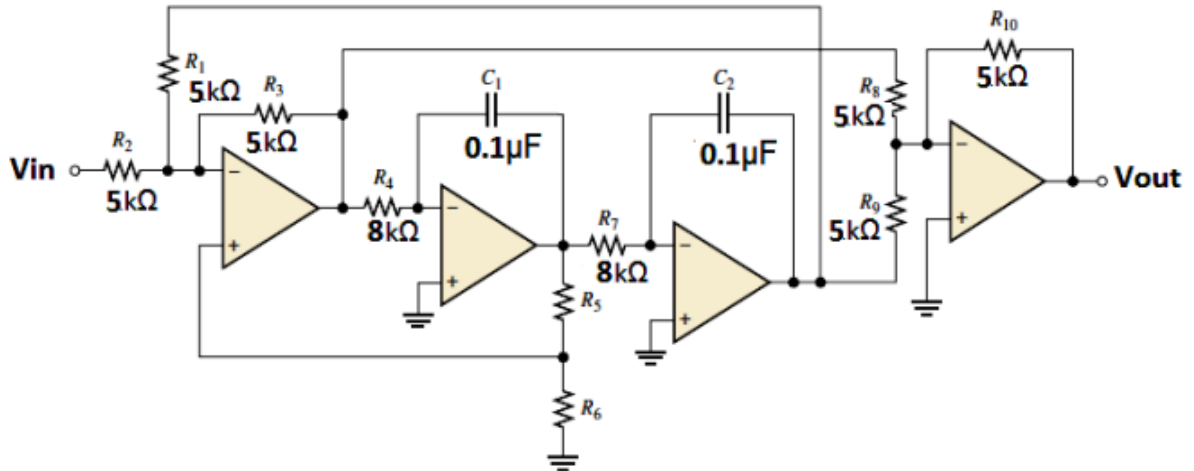


Electronic Systems
Active Filters
Sheet 4

1. For the state variable Band-Stop-Filter (BSF) shown in the following Figure.
 - Calculate the center frequency (f_0).
 - Design the value of R_5 and R_6 for a quality factor (Q) of 20.



2. For the multiple feedback BPF shown,
 - Derive an expression for the Filter Transfer Function (V_{out}/V_{in}).
 - Prove that the center frequency is expressed by:

$$f_0 = \frac{1}{2\pi \sqrt{(R_1 \parallel R_3) R_2 C_1 C_2}}$$

- Show that:

$$R_1 = \frac{Q}{2\pi f_0 C A_0}$$

$$R_2 = \frac{Q}{\pi f_0 C}$$

$$R_3 = \frac{Q}{2\pi f_0 C (2Q^2 - A_0)}$$

- Show that the center frequency gain is given by:

$$A_0 = \frac{R_2}{2R_1}$$

