
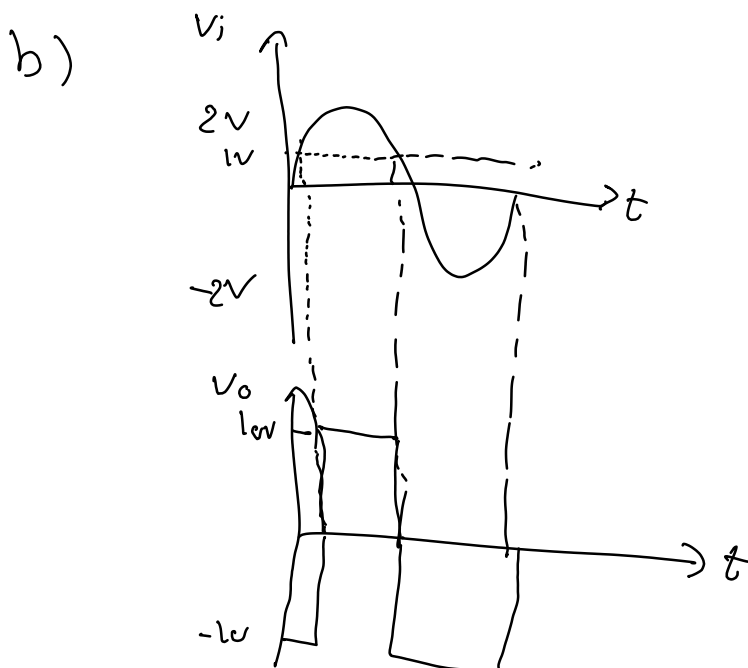
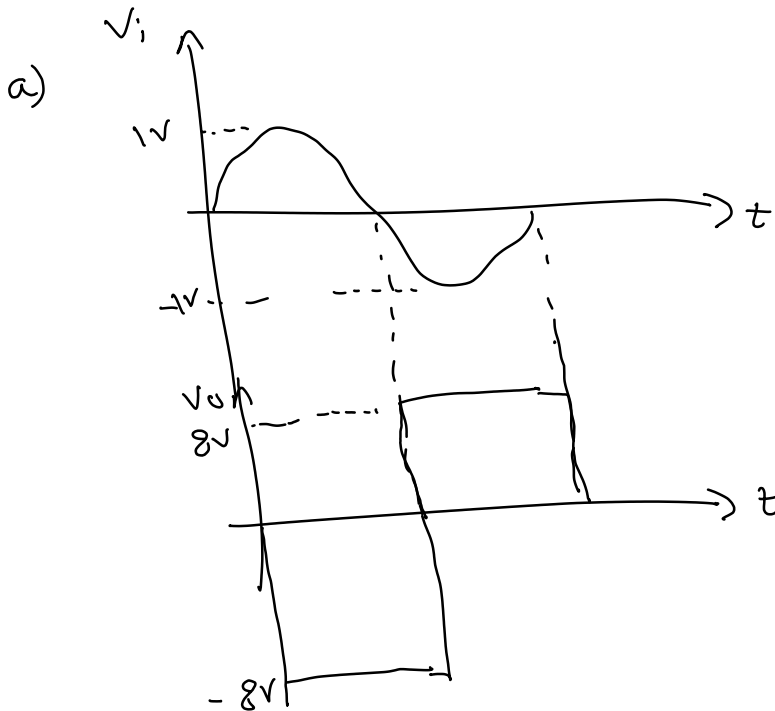
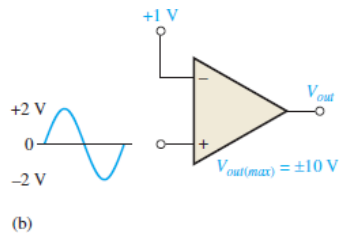



## Op Amp Sheet 3

Tuesday, December 27, 2022 7:22 PM

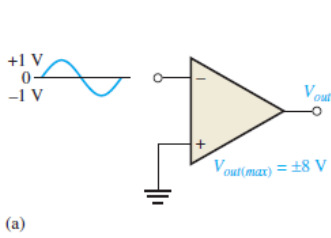1. Draw the output voltage waveform for each circuit shown with respect to the input. Show voltage levels.



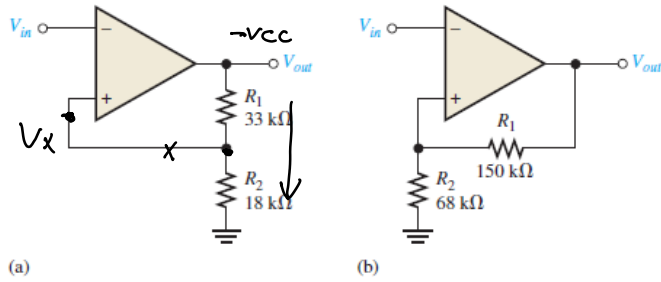2. Determine the hysteresis voltage for each comparator shown. The maximum output levels are  $\pm 11$  V.




at  $V_{in} < V_x$

$$V_x = V_{cc} \frac{R_2}{R_1 + R_2} = \beta V_{cc}$$

at  $V_{in} > V_x$

$$V_o = -V_{cc}$$
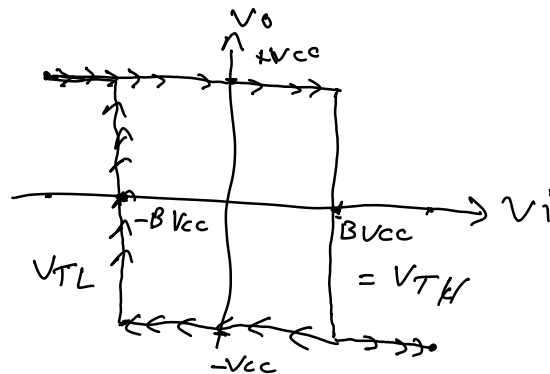
$$V_x = -V_{cc} \frac{R_2}{R_1 + R_2} = -\beta V_{cc}$$



$$V_H = 2\beta V_{cc}$$

a)  $V_H = 2\beta V_{max}$



$$= 2 \frac{R_2}{R_1 + R_2} 11$$

$$= 2 \frac{18}{33 + 18} 11 = 7.76 \text{ V}$$

$$b) \quad V_H = 2\beta V_{max}$$

$$= 2 \frac{68}{68 + 150} = 6.86V$$

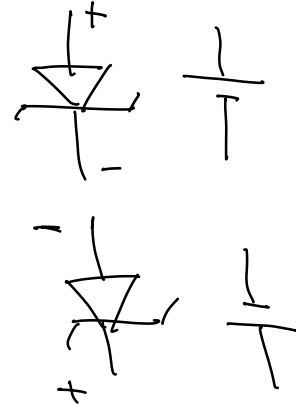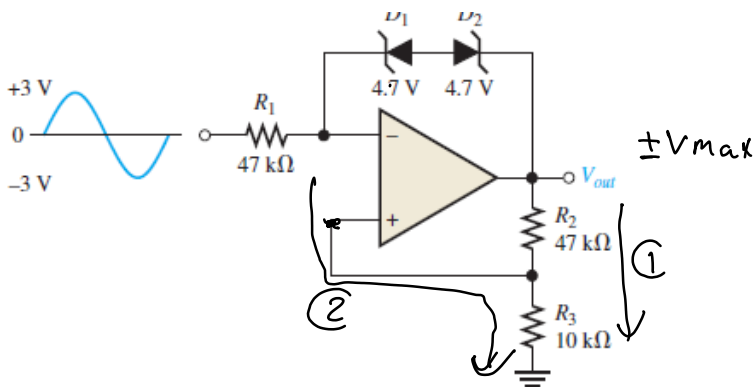3. Determine the output voltage waveform in the following figure.



at  $V_o = +V_{max}$

$$V_{ZS} = 4.7 + 0.7 = 5.4V$$

at  $V_o = -V_{max}$

$$V_{ZS} = -4.7 - 0.7 = -5.4V$$

$$V_{ZS} = \pm 5.4V$$

for Loop ①

$$V_o = V_{R2} + V_{R3} \rightarrow \text{①}$$

for Loop ②

$$V_o = V_{ZS} + V_{R3} \rightarrow \text{②}$$

$$\text{eq ①} - \text{eq ②}$$

$$0 = V_{R2} - V_{ZS}$$

$$V_{R2} = V_{ZS} = \pm 5.4V$$

rule - 5)




$$I_{R2} = \frac{V_{R2}}{R_2} = \frac{\pm 5.4}{4K} = \pm 114.89 \mu A$$

$$\begin{aligned} V_o &= V_{R2} + V_{R3} \\ &= \pm 5.4 + \pm 114.89 \mu A \times 10K \\ &= \pm 6.55 V \end{aligned}$$

$$V_{TL} = -B V_{max} = -1.15 V$$

$$V_{TH} = B V_{max} = 1.15 V$$

$$B = \frac{R_3}{R_2 + R_3}$$

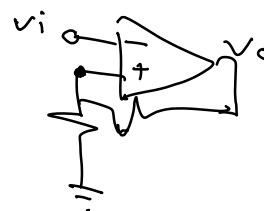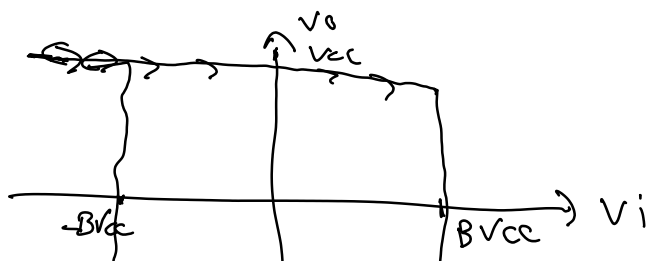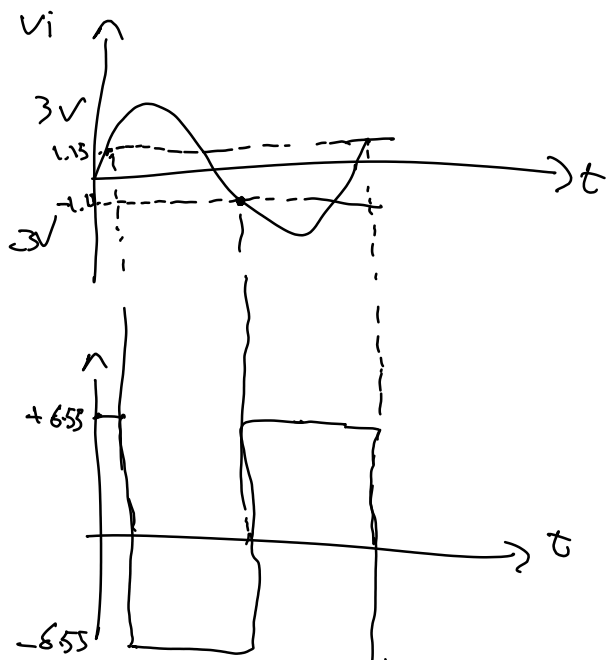




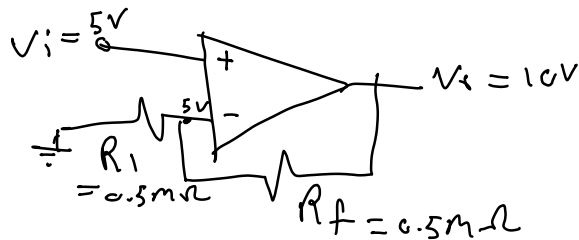4. Design a non-inverting amplifier with the gain of 2. At the maximum output voltage of 10V the current in the voltage divider is to be 10  $\mu$ A.

$$\text{Gain} = 2$$

$$V_{\text{max}} = 10\text{V} \rightarrow I = 10\mu\text{A}$$




$$G = 1 + \frac{R_f}{R_1} = 2 \rightarrow \frac{R_f}{R_1} = 1 \rightarrow R_f = R_1$$

$$V_o = G V_i \rightarrow V_i = \frac{V_o}{G} = \frac{10}{2} = 5\text{V}$$

$$R_f = \frac{V_o - V_i}{I} = \frac{10 - 5}{10\mu\text{A}} = 0.5\text{ m}\Omega$$

$$R_1 = R_f = 0.5\text{ m}\Omega$$

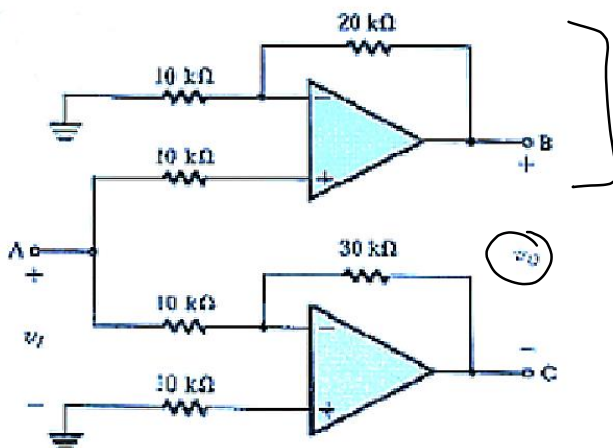5. Calculate  $V_B$ ,  $V_C$  and the voltage gain ( $V_{\text{out}}/V_{\text{in}}$ ) for the circuit shown



$$V_B = V_A \left(1 + \frac{20}{10}\right) = 3V_A$$

$$V_C = V_A - \frac{30}{10} = -3V_A$$

$$V_o = V_B - V_C$$

$$V_o = 3V_A - (-3V_A)$$

$$V_o = 6V_i \rightarrow \frac{V_o}{V_i} = 6$$


6. For the instrumentation amplifier configuration shown in figure.

a) Find the voltage gains of op-amps A<sub>1</sub> and A<sub>2</sub>.

b) Find the overall voltage gain of the instrumentation amplifier

c) The following voltages are applied to the instrumentation amplifier:  $V_{in1} = 5\text{mV}$ ,  $V_{in2} = 10\text{mV}$ ,  $V_{cm} = 225\text{mV}$ . Determine the final output voltage.

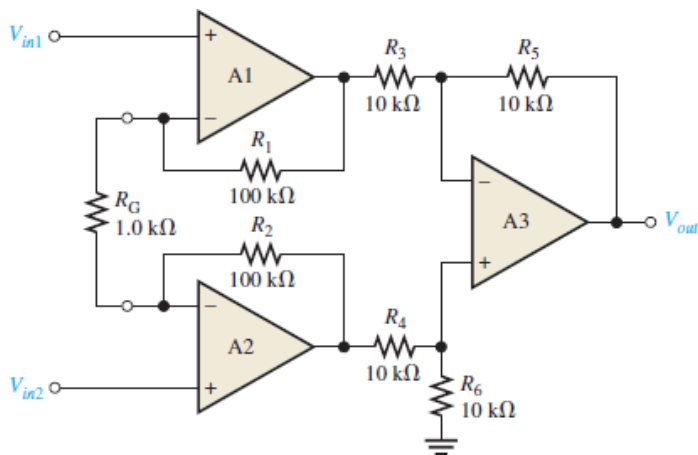d) What value of  $R_G$  must be used to change the gain of the instrumentation amplifier to 1000?



Gain for A<sub>1</sub>, A<sub>2</sub>      $R_1 = R_2 = R$

$$G = 1 + \frac{2R}{R_G} = 201$$

$$\text{Overall Gain} = \left(1 + \frac{2R}{R_G}\right) \frac{R_6}{R_4} = 201$$

$$V_{out} = \left(1 + \frac{2R}{R_G}\right) \frac{R_6}{R_4} * (V_{in2} - V_{in1})$$

$$= 201 ((10 + 2/25) - (5 + 2/25))$$


$$V_{out} = 1005 \text{ mV}$$

$$\text{overall Gain} = \left(1 + \frac{2R}{R_G}\right) \frac{R_6}{R_4}$$

$$1000 = \left(1 + \frac{2 \times 1000}{R_G}\right)$$

$$R_G = 4.99 \text{ k}\Omega$$

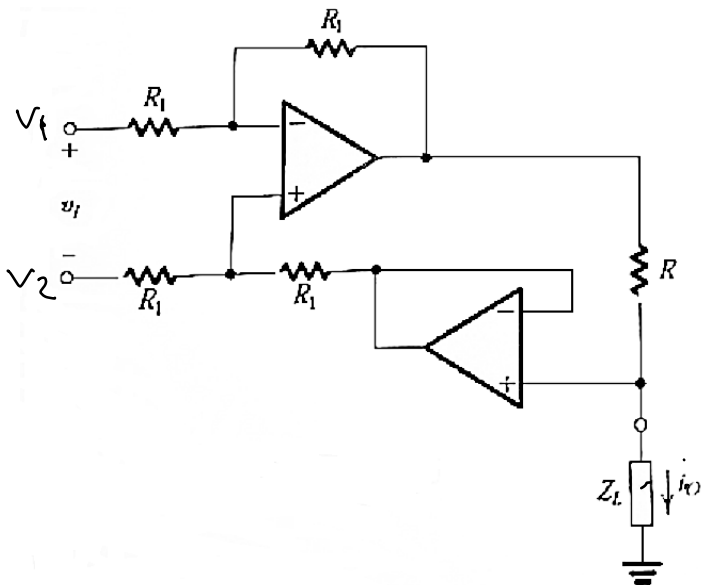
7. For instrumentation amplifier shown, derive an expression for  $i_o$




$$V_i = V_1 - V_2$$

using super position

for  $V_1$

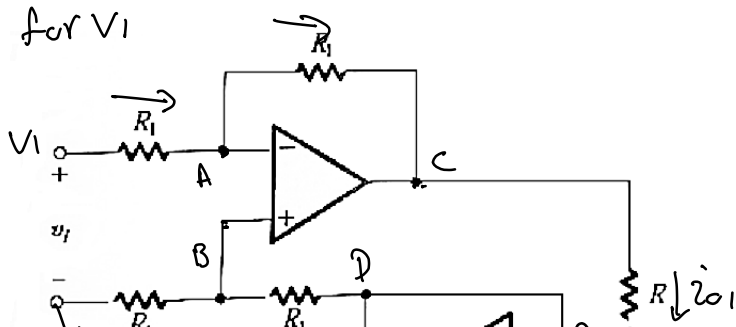

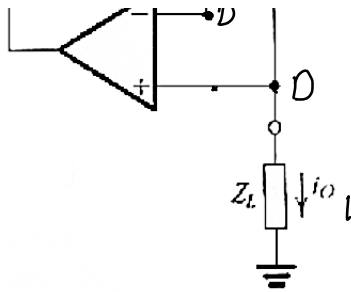

$$V_D = \hat{i}_1 Z_L$$

$$V_B = V_D \frac{R_1}{R_1 + R_1} = \frac{V_D}{2} = \frac{\hat{i}_1 Z_L}{2}$$

$$V_A = V_B$$


$$V_C = \hat{i}_1 (R + Z_L)$$

$$\frac{V_1 - V_A}{R_1} = \frac{V_A - V_C}{R_1}$$

$$V_1 - \frac{\hat{i}_1 Z_L}{2} = \frac{\hat{i}_1 Z_L}{2} - \hat{i}_1 (R + Z_L)$$

$$V_1 = \cancel{\hat{i}_1 Z_1} - \hat{i}_1 R - \cancel{\hat{i}_1 Z_L}$$
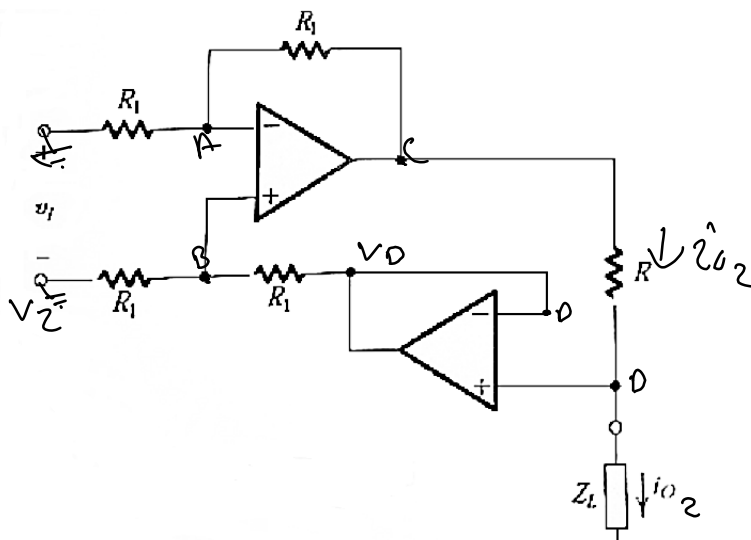
$$V_1 = -\hat{i}_1 R \rightarrow \hat{i}_1 = \frac{-V_1}{R}$$







$$V_B = \frac{V_2}{2} + \frac{V_D}{2}$$

$$V_D = i_{o2} Z_L$$

$$V_B = \frac{V_2}{2} + \frac{i_{o2} Z_L}{2}$$

$$V_E = i_{o2} (R + Z_L)$$

$$V_A = \frac{V_C}{2} = \frac{i_{o2} (R + Z_L)}{2}$$

$$V_A = V_B \rightarrow \frac{i_{o2} (R + Z_L)}{2} = \frac{V_2}{2} + \frac{i_{o2} Z_L}{2}$$

$$V_2 = i_{o2} R + \cancel{i_{o2} Z_L} - \cancel{i_{o2} Z_L}$$

$$V_2 = i_{o2} R \rightarrow i_{o2} = \frac{V_2}{R}$$

$$\dot{i}_O = \dot{i}_{O1} + \dot{i}_{O2}$$

$$= -\frac{V_1}{R} + \frac{V_2}{R}$$

$$= -\left(\frac{V_1 - V_2}{R}\right)$$

$$\dot{i}_O = -\frac{V_i}{R}$$