


# Electronic Devices

## **Lecture 11** **Bipolar Junction Transistor**


**Dr. Roaa Mubarak**
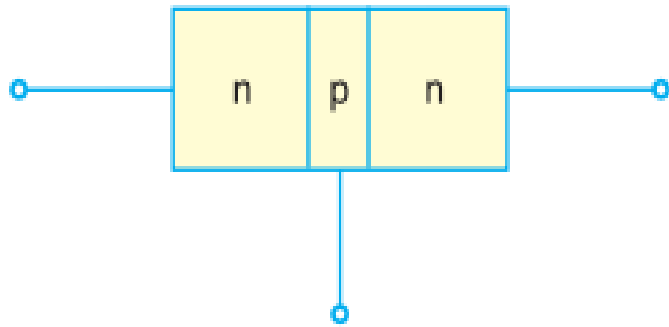
# The Bipolar Junction Transistor

- It is a three terminal element device formed from 2 junctions which share a common semiconductor layer.
- There are two junction, so transistor can be considered as two diode connected back to back.
- The middle section is thin than other.



NPN Transistor

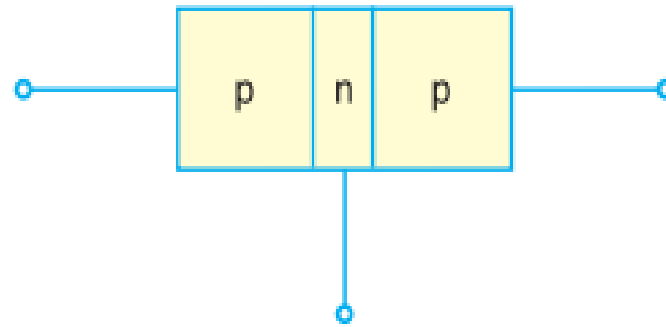


PNP Transistor

- BJT is very important electronic device because we use it as:  
Amplifier-Switch-logic circuits
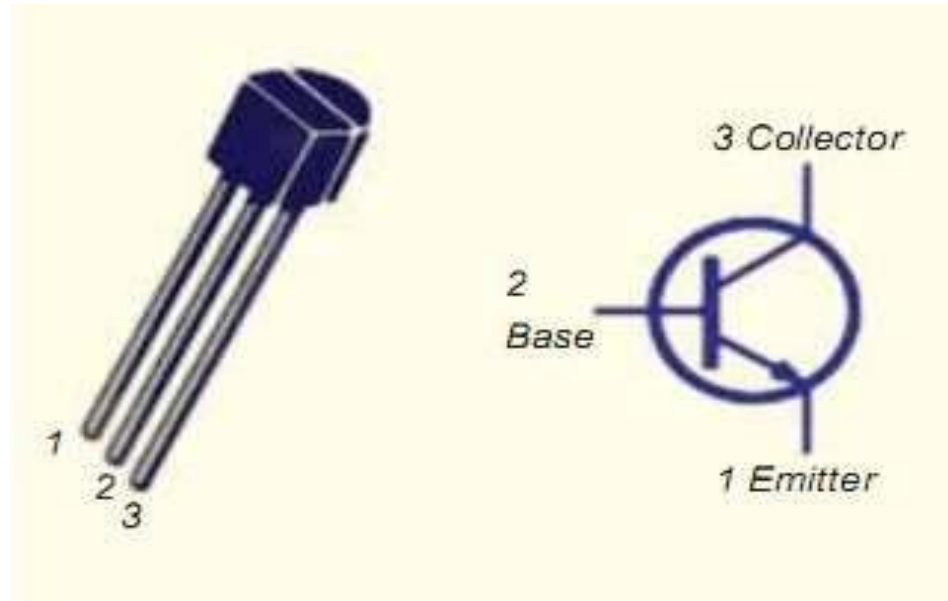
# The Bipolar Junction Transistor

- Transistor has three section of doped semiconductor.
- The section one side is called “Emitter” and the opposite side is called “Collector”.
- The middle section is called “Base”.



# The Bipolar Junction Transistor

- **Emitter:**

- The section of one side that supplies carriers is called emitter.
- Emitter is heavily doped so it can inject large amount of carriers into the base.
- Emitter is always forward biased to base so it can supply carrier.
- For “NPN transistor” emitter supply electrons to its junction.
- For “PNP transistor” emitter supply holes to its junction.

# The Bipolar Junction Transistor


- **Collector:**

- The section on the other side that collects carrier is called collector.
- For “NPN transistor” collector receives electrons to its junction.
- For “PNP transistor” collector receives holes to its junction.
- Collector is moderately doped.

- **Base:**

- The middle section which forms two P-N junction between emitter and collector is called Base.
- The Base is much thinner than other region.
- Base is lightly doped so it can pass most of the carrier to the collector.


# Physical Structure of BJT

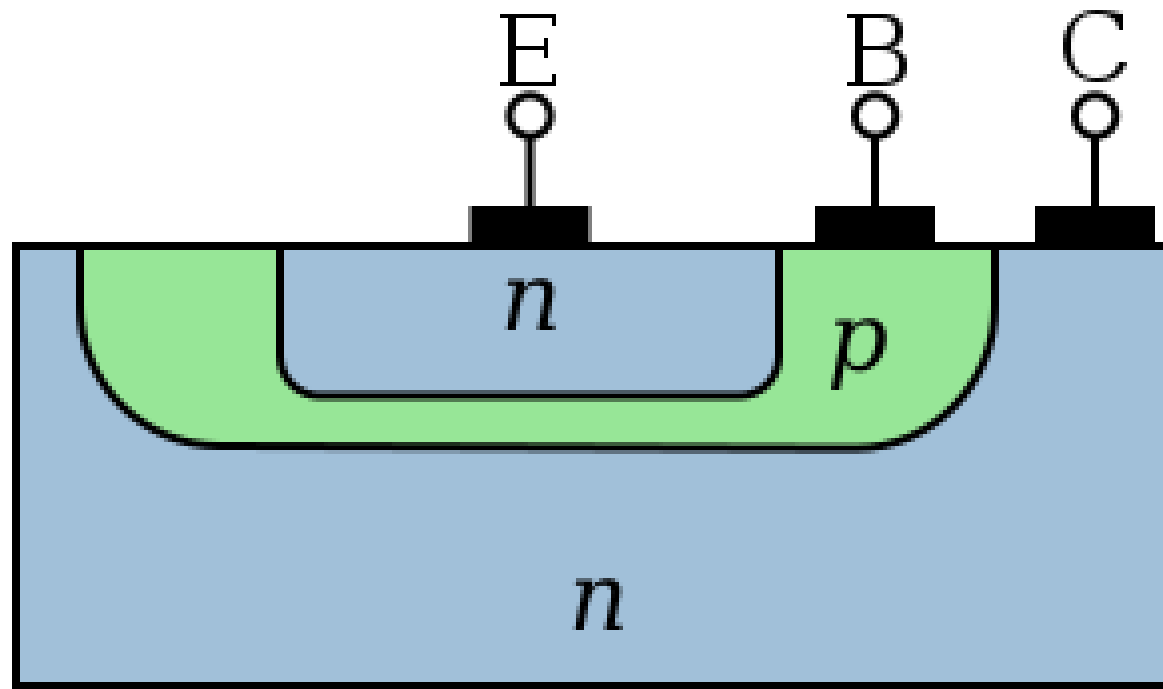

Cross-section of an NPN BJT

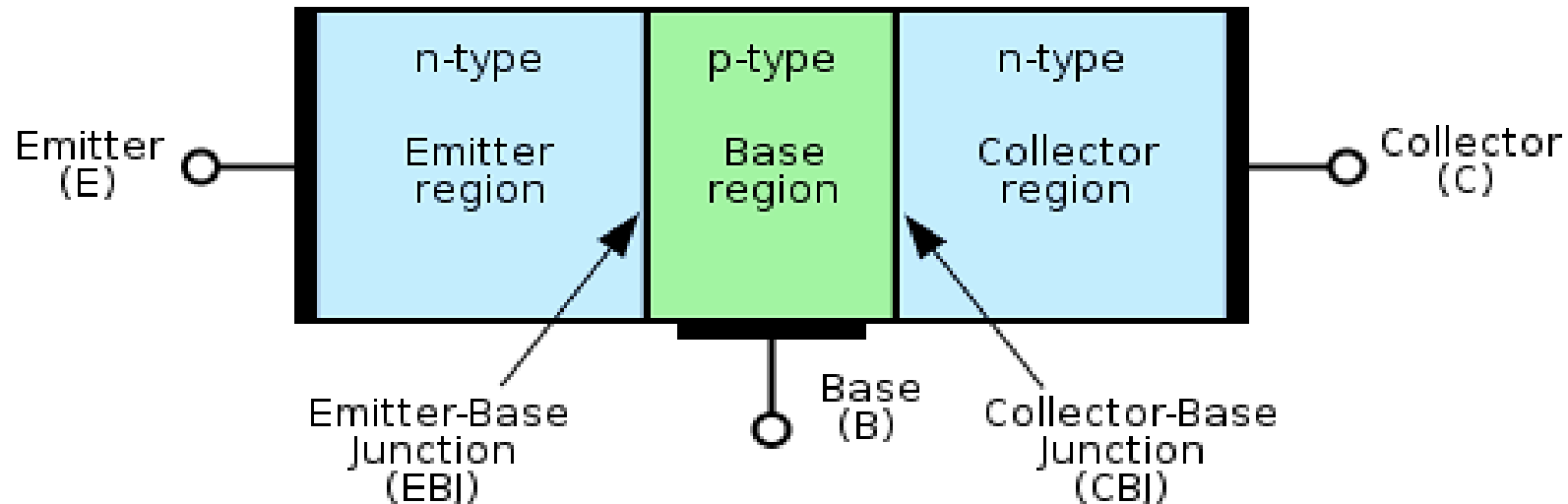
# The Bipolar Junction Transistor

- The junction between emitter and base is called emitter-base junction(emitter diode) and junction between base and collector is called collector-base junction(collector diode).
- The emitter diode is always forward biased and collector diode is reverse biased ( Active/ Amplifier).
- The resistance of emitter diode is very small (forward) and resistance of collector diode is high (reverse).




# The Bipolar Junction Transistor

## ➤ Unbiased NPN Transistor

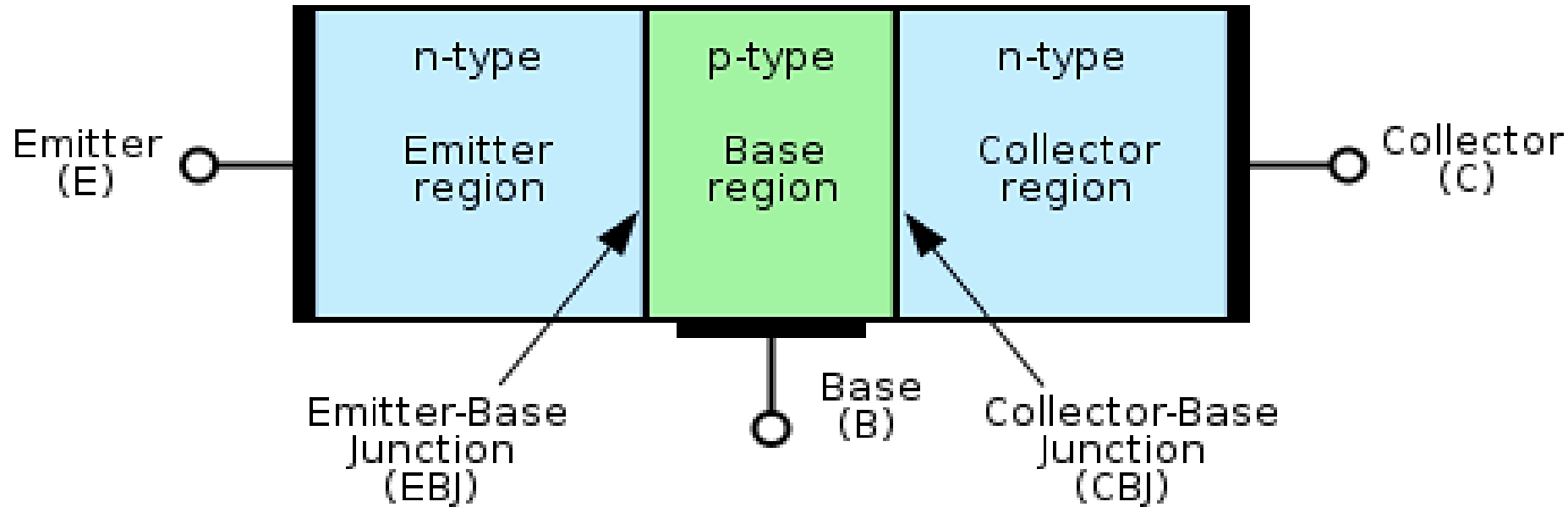

## ➤ Unbiased PNP Transistor

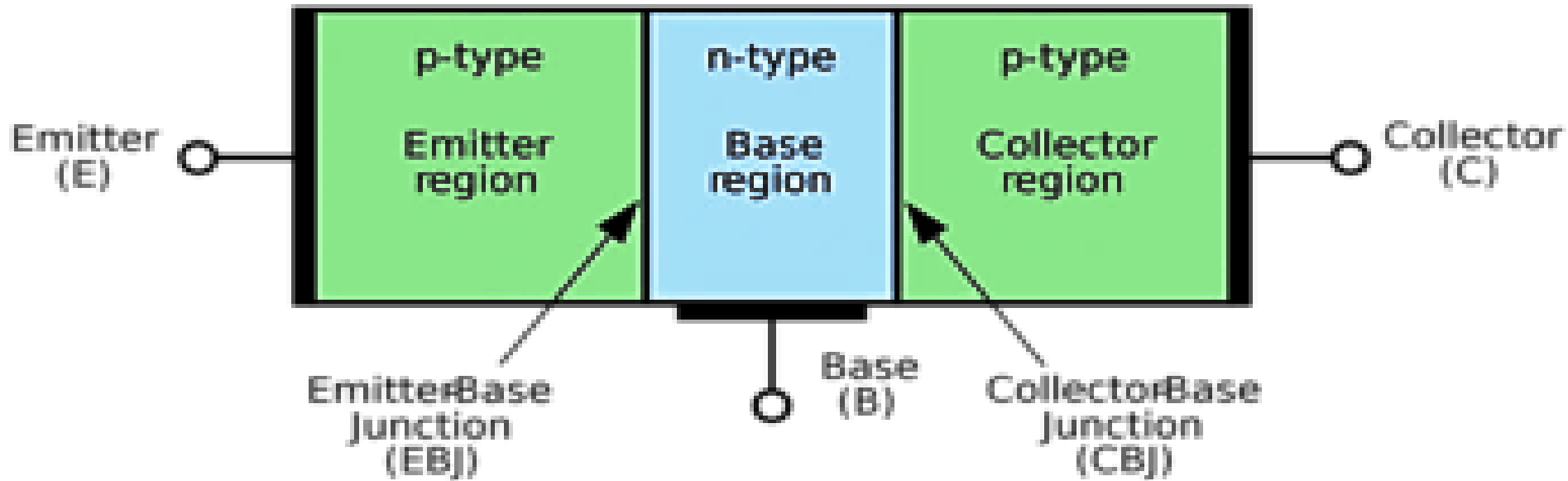




# The Bipolar Junction Transistor

- Depending upon the bias condition (Forward or Reverse) of each of the two junction ( E-B or C-B) different modes of operation of the BJT are obtained.



Mode	EBJ	CBJ
Cutoff	Reverse	Reverse
Active	Forward	Reverse
Reverse Active	Reverse	Forward
Saturation	Forward	Forward

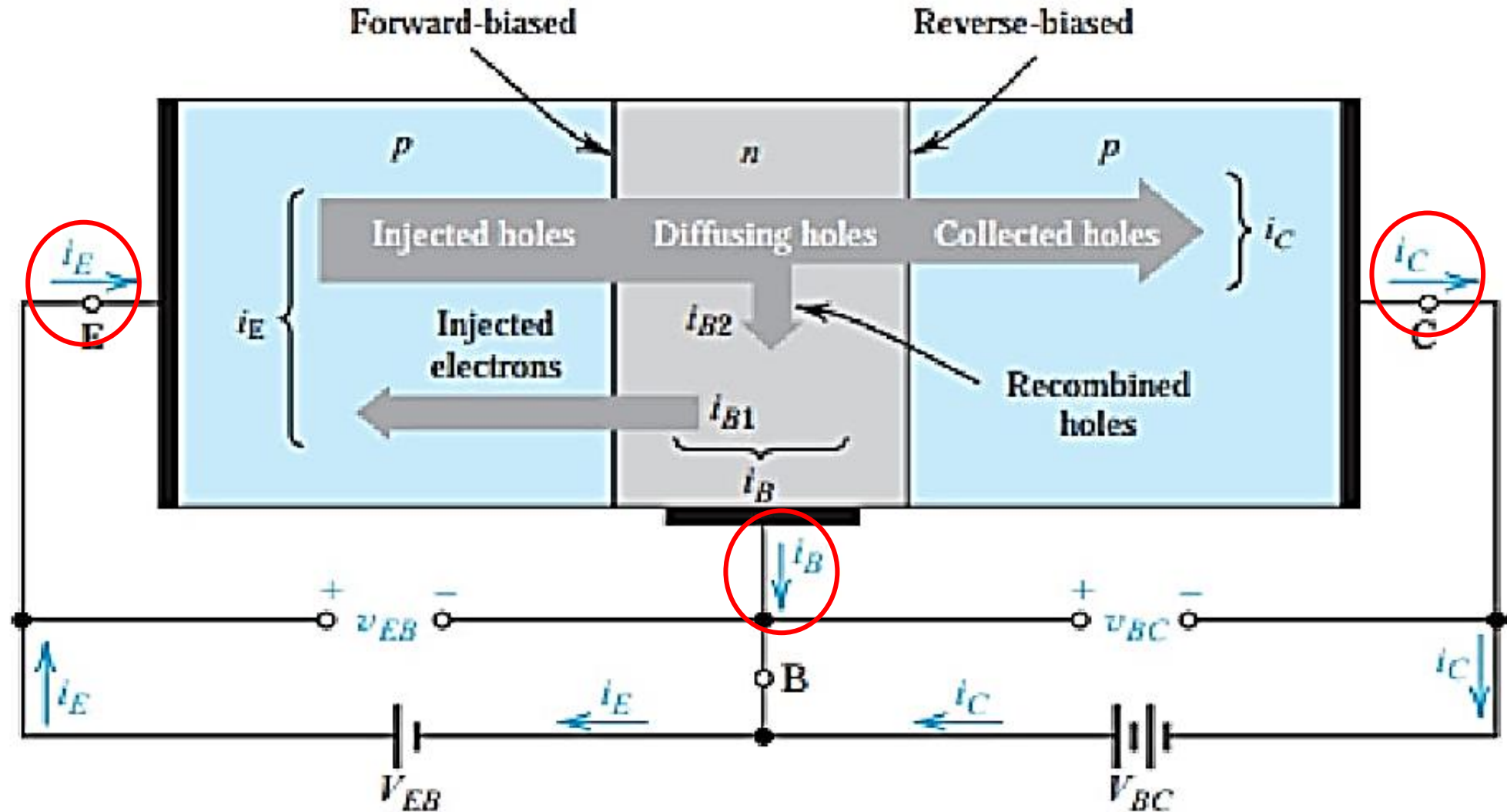
# Operation of Transistor in the Active Mode (PNP)



# Operation of Transistor in the Active Mode (PNP)







- Forward bias is applied to emitter- base junction and reverse bias is applied to collector- base junction.
- The forward bias in the emitter-base junction causes holes to move toward base. This constitute emitter current,  $I_E$ .
- As this holes flow toward n-type base, they try to recombine with electrons. As base is lightly doped only few holes recombine with electrons within the base.
- These recombined holes constitute small base current.
- The remainder holes crosses base and constitute collector current.
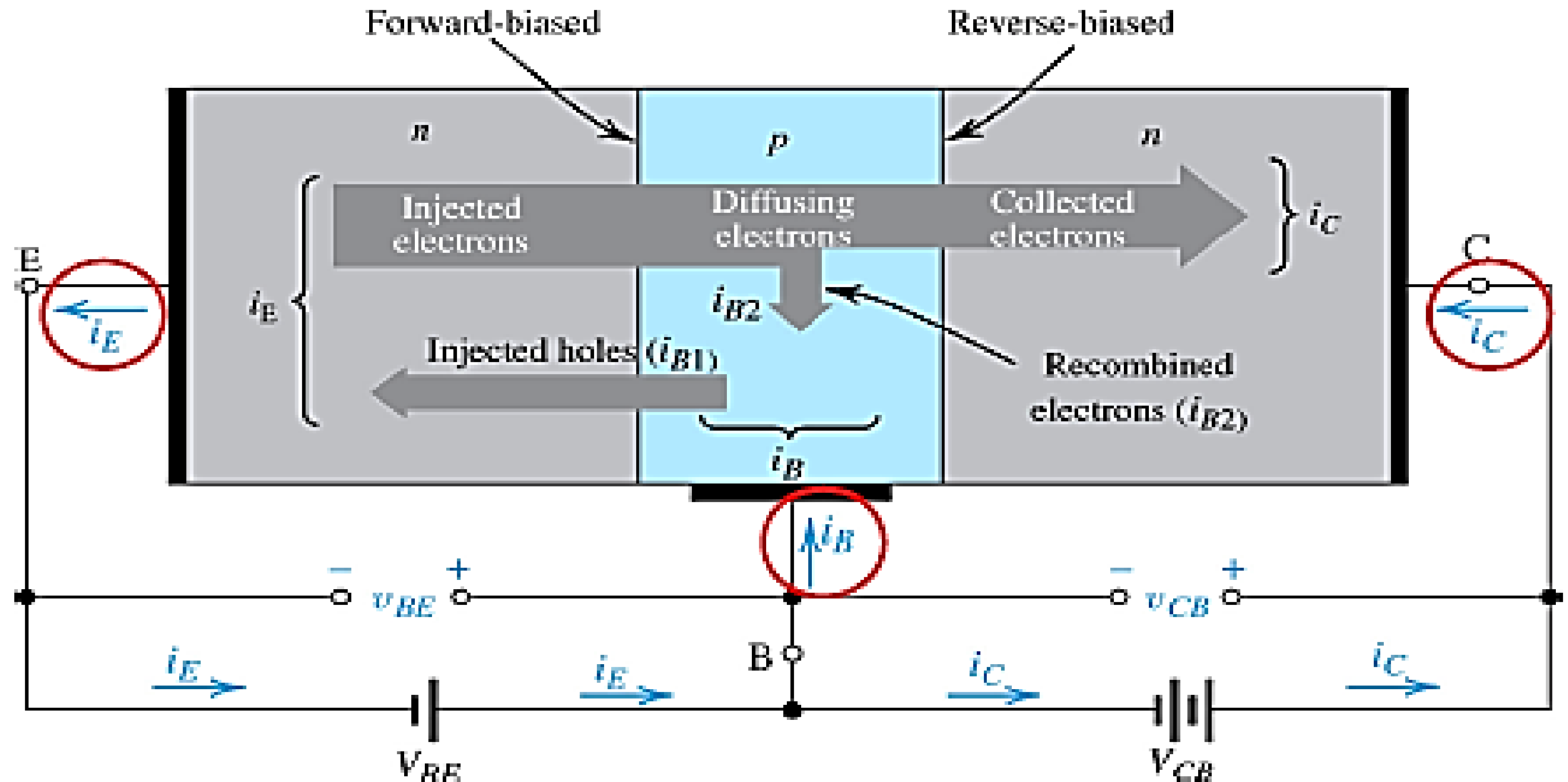
# Operation of Transistor in the Active Mode (NPN)


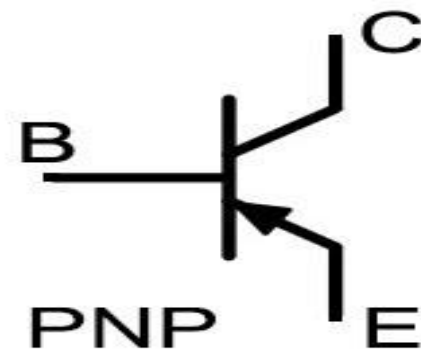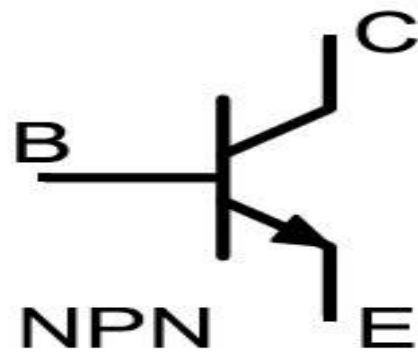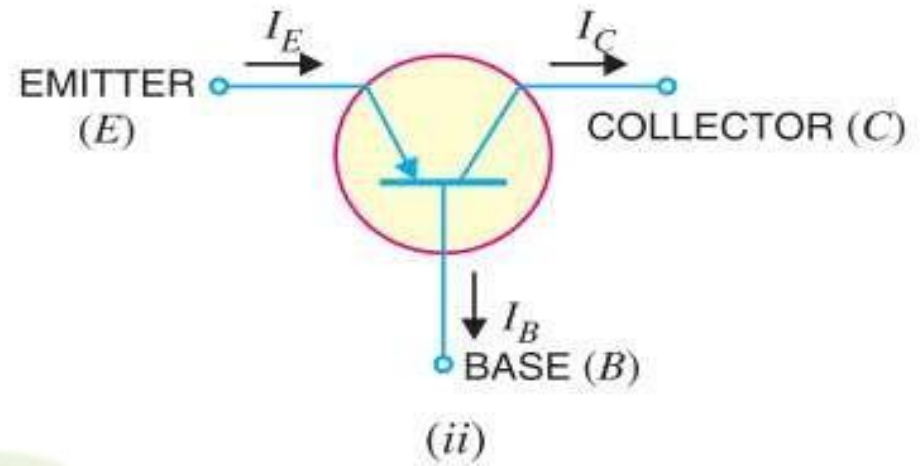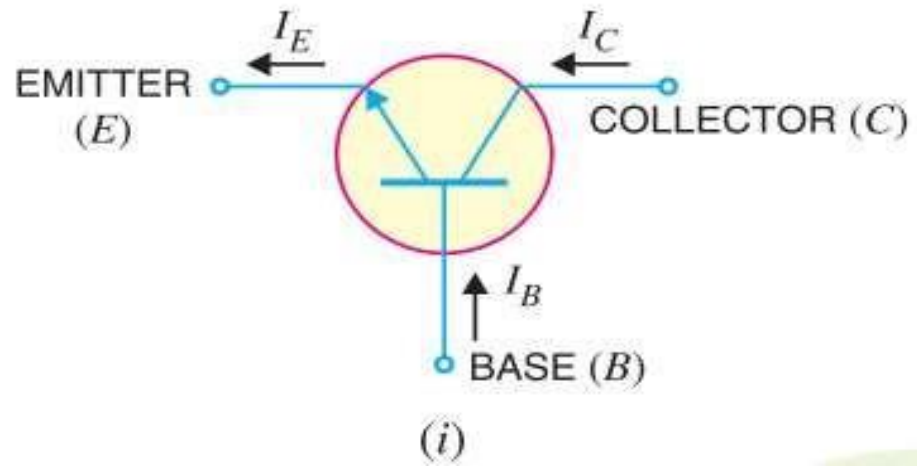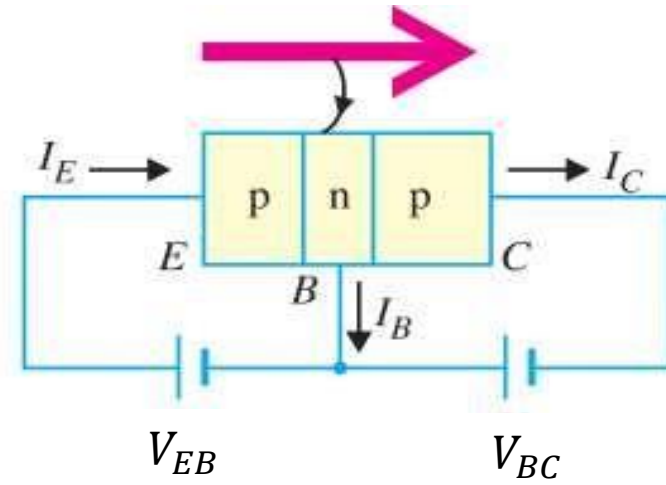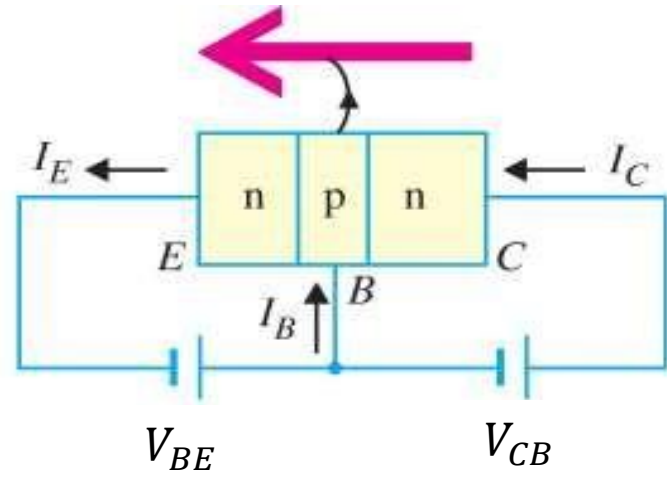
# Operation of Transistor in the Active Mode (NPN)

- Forward bias is applied to emitter-base junction and reverse bias is applied to collector-base junction.
- The forward bias in the emitter-base junction causes electrons to move toward base. This constitutes emitter current,  $I_E$ .
- As these electrons flow toward p-type base, they try to recombine with holes. As base is lightly doped only few electrons recombine with holes within the base.
- These recombined electrons constitute small base current.
- The remainder electrons cross base and constitute collector current.



# BJT Current Equations

$$I_E = I_B + I_C$$

Active  
Mode

$$I_C = \beta I_B$$

$$I_E = (1 + \beta) I_B$$

$$I_C = \frac{\beta}{(1 + \beta)} I_E$$

$$I_C = \alpha I_E$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$\beta$  Common Emitter Current Gain  $50 < \beta < 300$




$\alpha$  Common Base Current Gain  $\alpha < 1$ ,  $\alpha = 0.95: 0.99$

# Different BJT Configurations


- Common Base
- Common Emitter
- Common Collector




# Different BJT Configurations

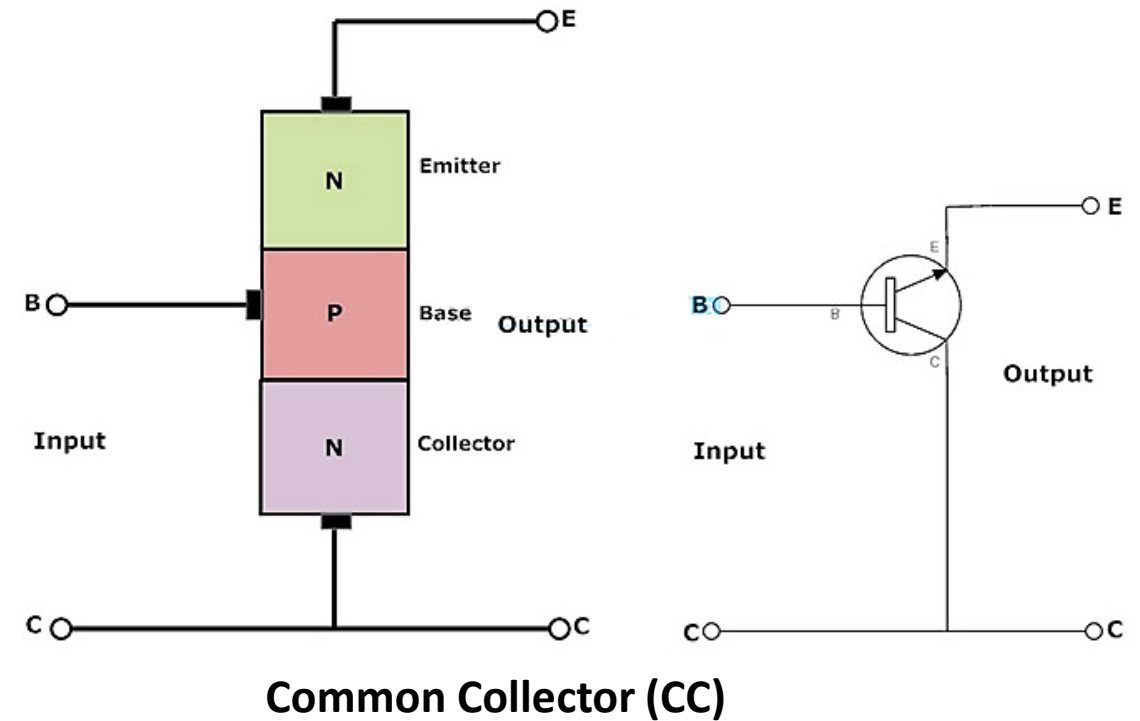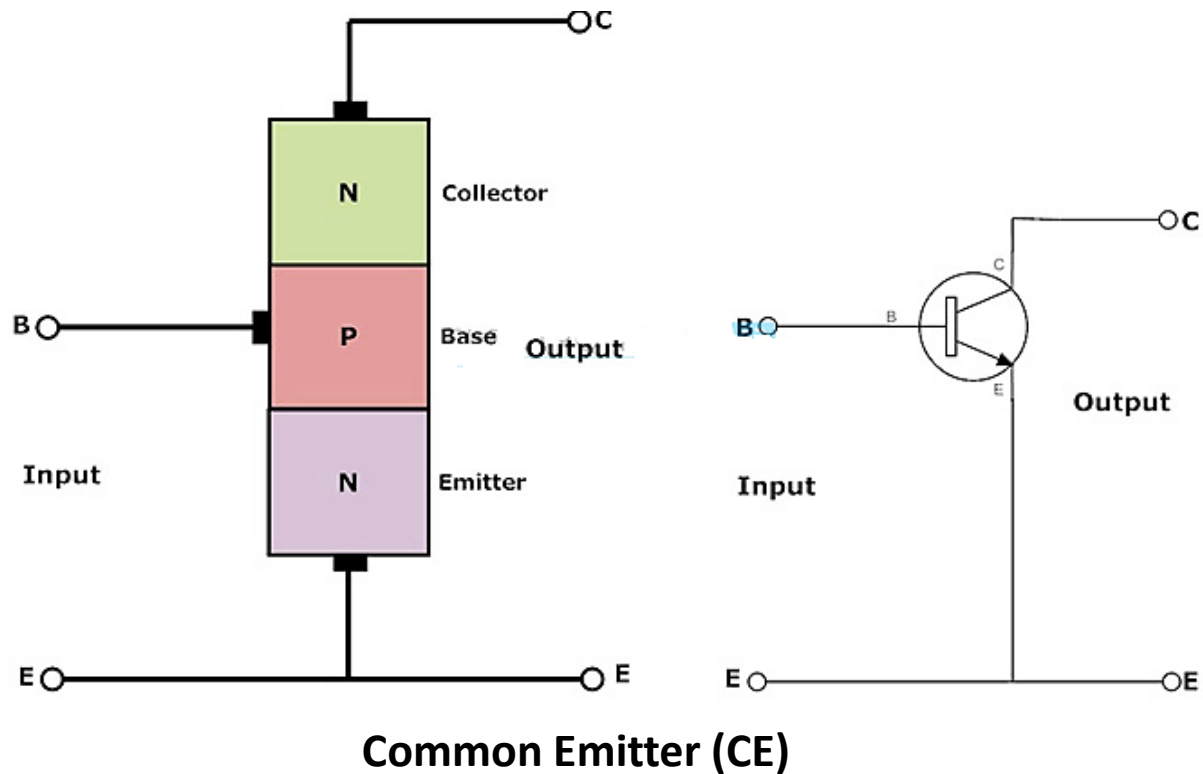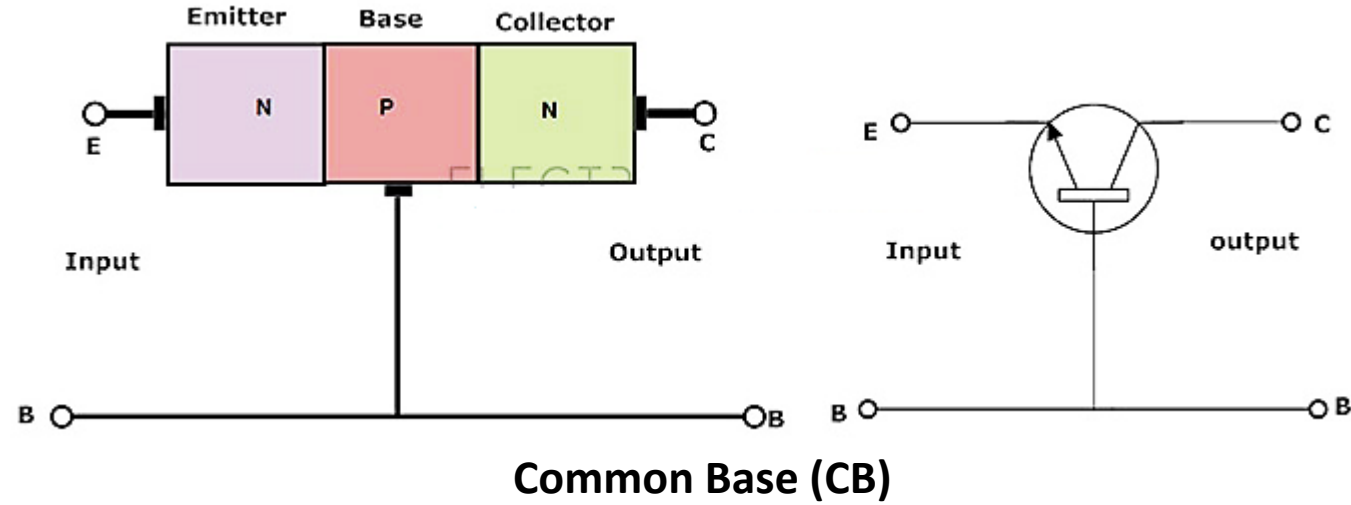

# Common Base "CB"

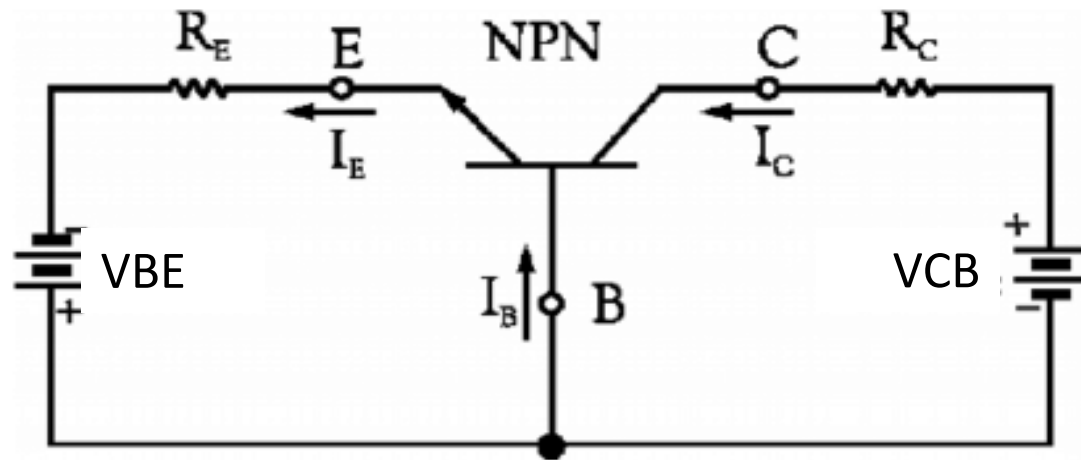

(a) Common-base NPN transistor circuit.

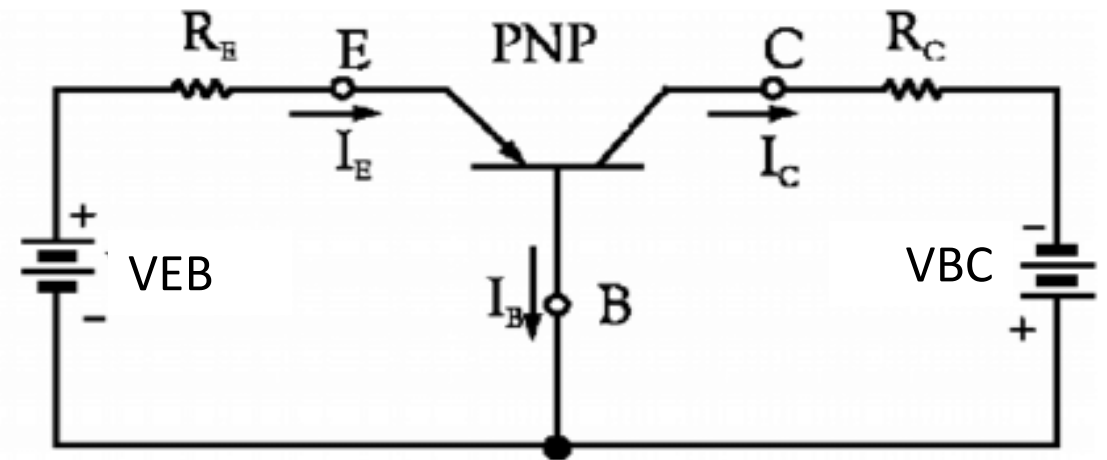

(b) Common-base PNP transistor circuit.

- The common-base terminology is derived from the fact that the base is common to both the input and output sides of the configuration.
- Active mode: E-B junction (Forward) , C-B junction ( Reverse)
  - NPN:  $V_{BE}$ ,  $V_{CB}$
  - PNP:  $V_{EB}$ ,  $V_{BC}$

## Common Base “CB”

- Current amplifier Factor  $\alpha$ :

The ratio of change in collector current to the change in emitter current at constant VCB is known as current amplification factor (Current gain)  $\alpha$ .

$$I_C = \alpha I_E \qquad \alpha = \frac{\Delta I_C}{\Delta I_E}$$

- Practical value of  $\alpha$  is less than unity, but in the range of 0.95 to 0.99.
- Total emitter current does not reach the collector terminal, because a small portion of it constitute base current. So,

$$I_E = I_B + I_C$$

# Common Base “CB”

- Also, collector diode is reverse biased, so very few minority carrier passes the collector-base junction which actually constitute leakage current,  $I_{CBO}$ .
- So, collector current constitute of portion of emitter current  $\alpha I_E$  and leakage current  $I_{CBO}$ .

$$I_C = \alpha I_E + I_{CBO}$$


$$I_C = \alpha (I_C + I_B) + I_{CBO}$$

$$I_C (1 - \alpha) = \alpha I_B + I_{CBO}$$


$$I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{I_{CBO}}{1 - \alpha}$$
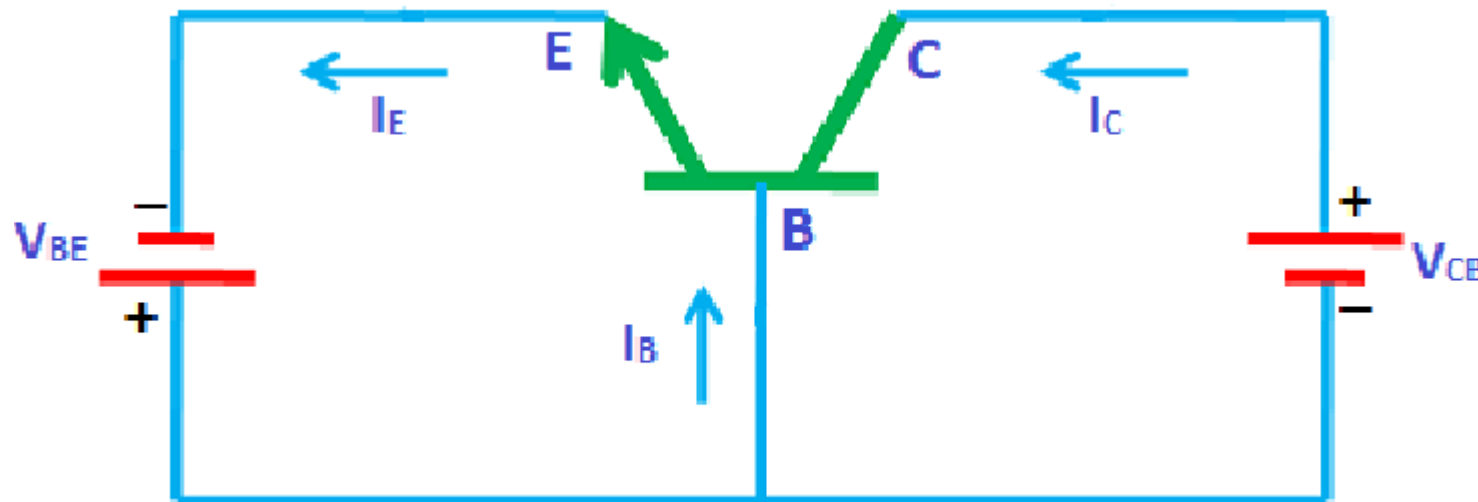
# Input Characteristics of Common Base Configuration (NPN)

- $V_{BE}$  vs  $I_E$  characteristics is called input characteristics.
- $I_E$  increases rapidly with  $V_{BE}$ .  
It means input resistance is very small.
- $I_E$  almost independent of  $V_{CB}$ .





Input Characteristics

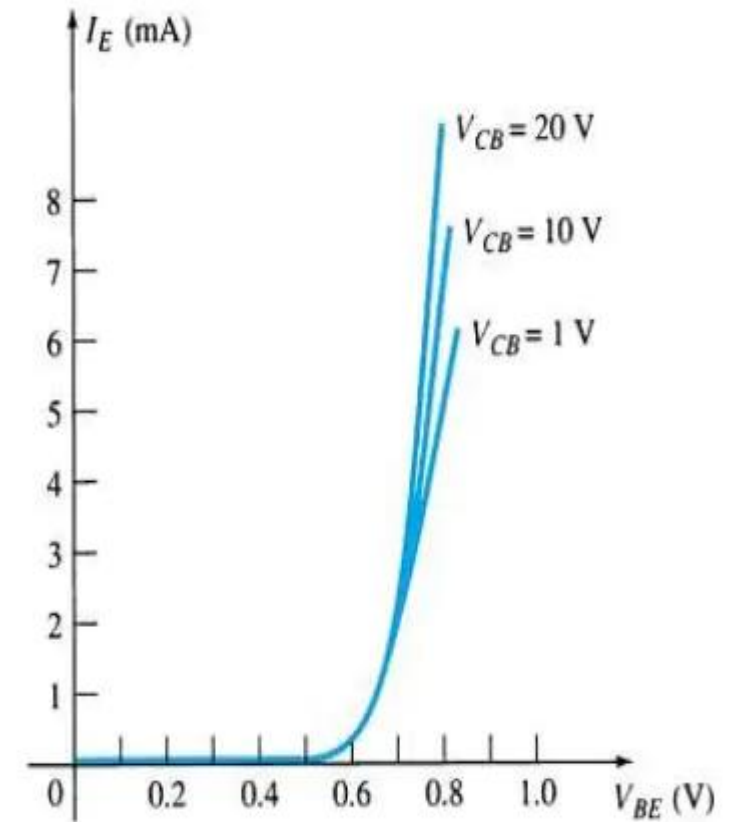
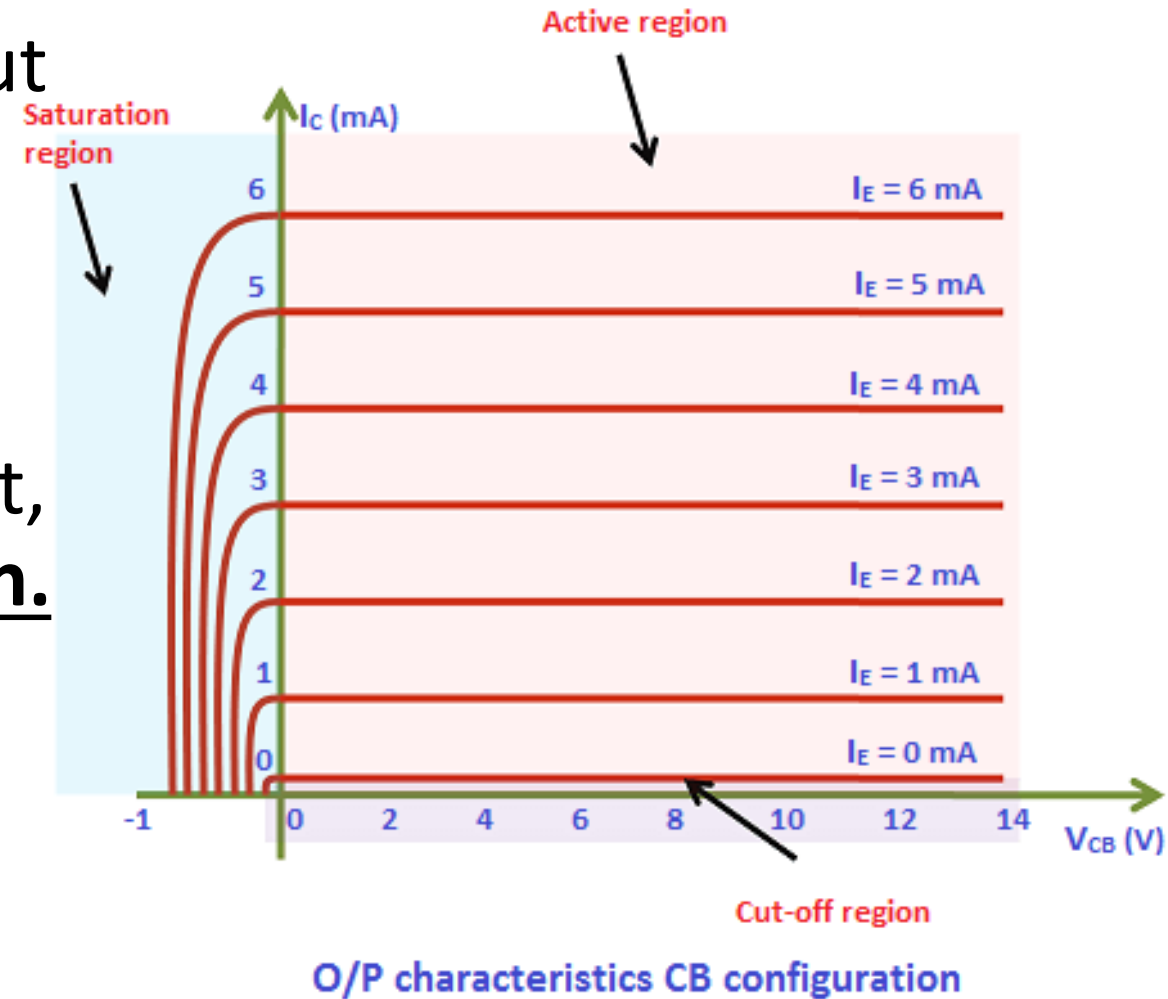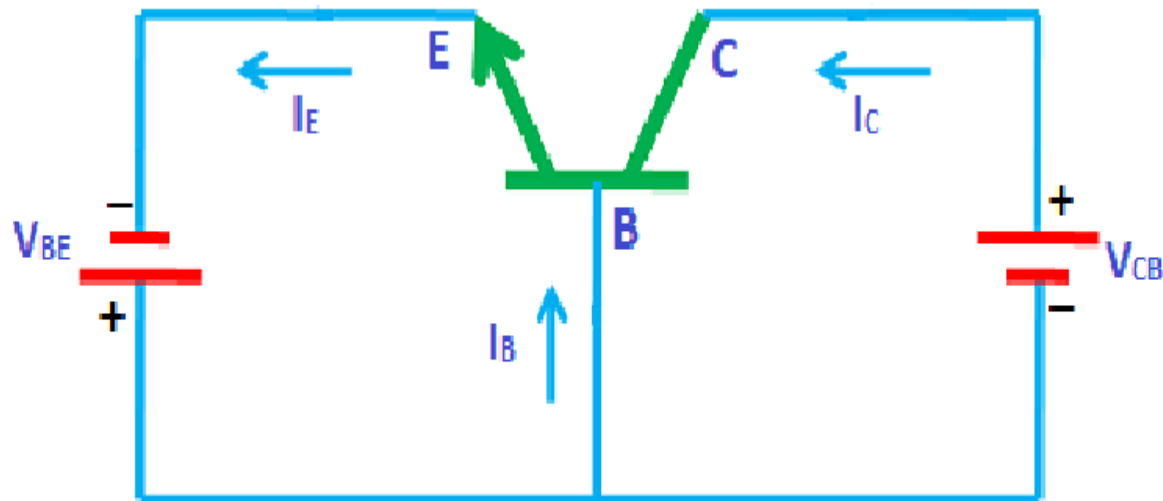
# Output Characteristics of Common Base Configuration(NPN)

- $V_{CB}$  vs  $I_C$  characteristics is called output characteristics.
- $I_C$  varies linearly with  $V_{CB}$ , only when  $V_{CB}$  is very small.
- As,  $V_{CB}$  increases,  $I_C$  becomes constant, It means **output resistance is very high.**



# Input, Output Resistance and gain of CB

- **Input Resistance**: The ratio of change in emitter-base voltage to the change in emitter current is called Input Resistance.

$$r_i = \frac{\Delta V_{BE}}{\Delta I_E} \quad (\text{Low})$$

- **Output Resistance**: The ratio of change in collector-base voltage to the change in collector current is called Output Resistance.

$$r_o = \frac{\Delta V_{CB}}{\Delta I_C} \quad (\text{High})$$

- **Current gain**:

$$A_i = \alpha = \frac{\Delta I_C}{\Delta I_E} \quad (\text{low less than unity})$$

- **Voltage gain**:

$$A_v = \frac{I_C \mathcal{X} r_o}{I_E \mathcal{X} r_i} \quad (\text{High})$$