
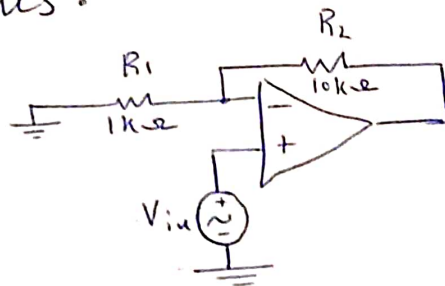


Active Filters

sheet 1

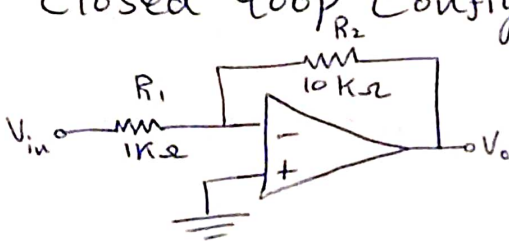
1. The circuits shown represent an op-amp inverting & non-inverting amplifiers respectively. op-amp finite open-loop DC gain $A_o = 10^5$ & open-loop Bandwidth $\omega_b = 10 \text{ rad/s}$

- Derive an expression for the closed-loop Bandwidth ω_c .
- Calculate the closed loop DC gain A_m & closed-loop Bandwidth ω_c .
- Calculate the Gain-BW product (GBP) for open & closed loop configurations.



Sol:-

For inverting Amplifier

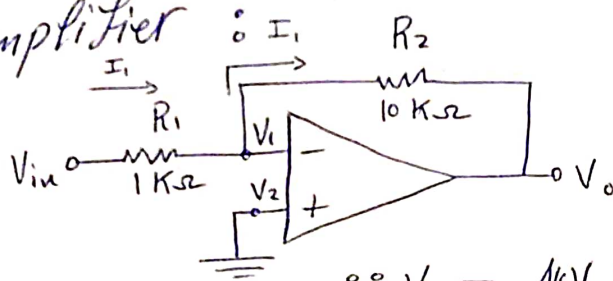

$$\Rightarrow I_1 = \frac{V_{in} - V_1}{R_1} = \frac{V_1 - V_o}{R_2}$$

$$\Rightarrow \frac{R_2}{R_1} V_{in} = V_1 \left(1 + \frac{R_2}{R_1} \right) - V_o$$

* sub. by V_1 from (1) :

$$\Rightarrow \frac{R_2}{R_1} V_{in} = \left[1 + \frac{R_2}{R_1} \right] \left(-\frac{V_o}{A(s)} \right) - V_o$$

$$\Rightarrow \frac{R_2}{R_1} V_{in} = \left(\left[1 + \frac{R_2}{R_1} \right] \cdot \frac{1}{A_1} + 1 \right) (-V_o)$$

$$\Rightarrow H(s) = \frac{V_o}{V_{in}} = \frac{-\frac{R_2}{R_1}}{1 + \left(\frac{1 + \frac{R_2}{R_1}}{A(s)} \right)}$$

$$\because V_o = A(s)(V_2 - V_1)$$

$$\text{but, } V_2 = 0$$

$$\Rightarrow \boxed{V_o = -A(s)V_1} \quad (1)$$

$$A(s) = \frac{A_o}{1 + \frac{s}{\omega_b}}$$

$$\Rightarrow H(s) = \frac{V_o}{V_{in}} = \frac{-\frac{R_2}{R_1}}{1 + \left[\frac{1 + \frac{R_2}{R_1}}{\frac{A_o}{1 + \frac{s}{\omega_b}}} \right]} = \frac{-R_2/R_1}{1 + \frac{(1 + \frac{R_2}{R_1})(1 + \frac{s}{\omega_b})}{A_o}}$$

$$= \frac{-R_2/R_1}{1 + \underbrace{\frac{(1 + \frac{R_2}{R_1})}{A_o}}_{\text{negligible}} + \frac{(1 + \frac{R_2}{R_1})(\frac{s}{\omega_b})}{A_o}}$$

($A_o \gg 1 + \frac{R_2}{R_1}$)

$$\Rightarrow H(s) \approx \frac{-R_2/R_1}{1 + \frac{(1 + \frac{R_2}{R_1})(\frac{s}{\omega_b})}{A_o}}$$

$$= \frac{-R_2/R_1}{1 + \frac{s}{\frac{A_o \omega_b}{(1 + \frac{R_2}{R_1})}}}$$

compare
with

$$\frac{A_m}{1 + \frac{s}{\omega_c}}$$

↳ standard form
for a simple single
pole system.

$$\Rightarrow A_m = \frac{R_2}{R_1} = 10$$


$$\Rightarrow \omega_c = \frac{A_o \omega_b}{1 + \frac{R_2}{R_1}} = \frac{(10^5)(10)}{1 + 10} = 90909.09 \text{ rad/sec}$$

$$\Rightarrow \text{GBP}_{\text{open loop}} = A_o \omega_b = (10^5)(10) = 10^6 \text{ rad/sec}$$

$$\Rightarrow \text{GBP}_{\text{closed loop}} = A_m \omega_c = (10)(90909.09) = 909090.9 \text{ rad/sec}$$

For the non-inverting Amplifier :
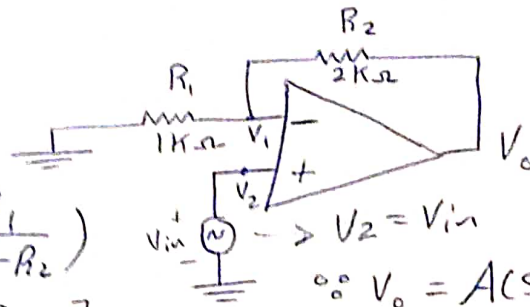
$$\Rightarrow V_1 = V_o \frac{R_1}{R_1 + R_2}$$



$$\Rightarrow V_o = A(s) (V_{in} - V_o \frac{R_1}{R_1 + R_2})$$

$$\Rightarrow A(s) V_{in} = V_o \left[1 + \frac{A(s) R_1}{R_1 + R_2} \right]$$

$$\Rightarrow H(s) = \frac{V_o}{V_{in}} = \frac{A(s)}{1 + A(s) \frac{R_1}{R_1 + R_2}}$$

$$\Rightarrow H(s) = \frac{A(s)}{1 + \frac{A(s)}{1 + R_2/R_1}} = \frac{1 + R_2/R_1}{\left(1 + \frac{R_2}{R_1}\right) + \frac{1}{A(s)}}$$

$$\therefore A(s) = \frac{A_o}{1 + \frac{s}{\omega_b}}$$

$$\Rightarrow H(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1 + R_2/R_1}{\left(\frac{A_o}{1 + \frac{s}{\omega_b}}\right)}} = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{(1 + \frac{R_2}{R_1})(1 + \frac{s}{\omega_b})}{A_o}}$$

$$\Rightarrow H(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1 + \frac{R_2}{R_1}}{A_o} + \frac{(1 + \frac{R_2}{R_1}) \frac{s}{\omega_b}}{A_o}} \approx \frac{1 + \frac{R_2}{R_1}}{1 + \frac{(1 + \frac{R_2}{R_1}) s}{\omega_b A_o}}$$

negligible.


$$\Rightarrow A_{mid} = 1 + \frac{R_2}{R_1}, \quad \omega_c = \frac{\omega_b A_o}{1 + \frac{R_2}{R_1}}$$

2. Analyze the circuits using ideal op-amp :

- Drive an expression for the closed loop gain (A_v)
- Find Max DC gain (A_m) & cut-off freq. (f_c).
- Find the unity gain freq. (f_T).
- Sketch the Freq. response Magnitude.

Solⁿ

for the HPF :

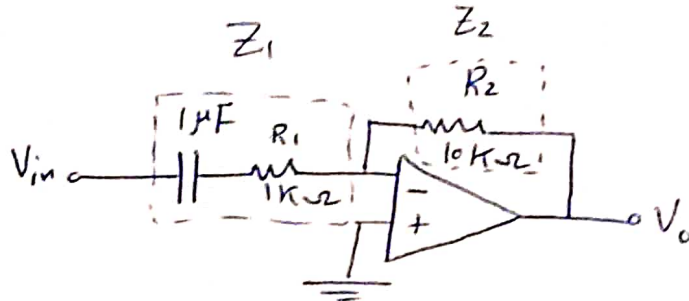

$$\Rightarrow A_v = - \frac{Z_2}{Z_1}$$

$$Z_2 = R_2, \quad Z_1 = \frac{1}{sC} + R_1$$

$$\Rightarrow A_v = - \frac{R_2}{R_1 + \frac{1}{sC}} = \frac{-R_2/R_1}{1 + \frac{1}{sR_1C}} = \frac{-R_2/R_1}{1 + \frac{(1/R_1C)}{s}} = \frac{A_m}{1 + \frac{\omega_c}{s}}$$

$$\Rightarrow A_m = \frac{R_2}{R_1} = 10, \quad \omega_c = \frac{1}{R_1C} = \frac{1}{(1k)(10^{-6})} = 1000 \quad = 1$$

$$\Rightarrow f_c = \frac{1}{2\pi R_1C} = 159.15 \text{ Hz}$$

* to get unity gain freq.:

$$\Rightarrow \text{at } |A_m| = 1 = \left| \frac{10}{1 + \frac{1000}{j\omega}} \right|$$


$$1 = \frac{10}{\sqrt{1 + \left(\frac{1000}{\omega}\right)^2}}$$

$$\Rightarrow 1 + \left(\frac{1000}{\omega}\right)^2 = (10)^2$$


$$\Rightarrow \omega^2 + (1000)^2 = 100 \omega^2$$

$$\Rightarrow \omega_t^2 = \frac{10^6}{99} \Rightarrow \omega_t = 100.5 \text{ Hz}$$
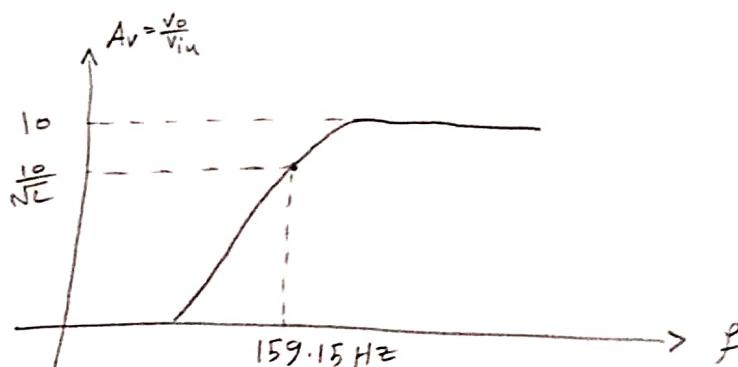
$$\Rightarrow f_t = \frac{\omega_t}{2\pi} = 16 \text{ Hz}$$



For the LPF :

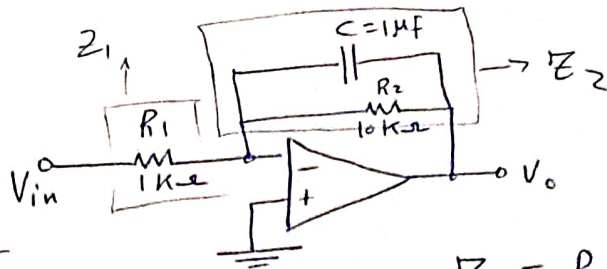

$$\Rightarrow A_v = \frac{V_o}{V_{in}} = -\frac{Z_2}{Z_1}$$

$$\Rightarrow A_v = -\frac{\frac{R_2}{1+R_2 sC}}{\frac{R_1}{1+R_2 sC}} = -\frac{R_2/R_1}{1+\frac{s}{\frac{1}{R_2 C}}}$$

$$Z_1 = R_1$$

$$Z_2 = \frac{1}{sC} \parallel R_2 = \frac{\frac{R_2}{sC}}{R_2 + \frac{1}{sC}} = \frac{R_2}{1+R_2 sC}$$

$$\Rightarrow A_m = \frac{R_2}{R_1} = 10, \quad \omega_c = \frac{1}{R_2 C} = \frac{1}{10 \times (10^3)(10^{-6})} = 10^2 \text{ rad/sec}$$


$$\Rightarrow f_c = \frac{\omega_c}{2\pi} = 15.915 \text{ Hz}$$

$$\Rightarrow |A_m| = 1 = \left| \frac{10}{1 + \frac{j\omega_t}{10^2}} \right| = \frac{10}{\sqrt{1 + \frac{\omega_t^2}{10^4}}}$$


$$\Rightarrow 1 + \frac{\omega_t^2}{10^4} = 10^2$$

$$\Rightarrow \omega_t = 994.98 \text{ rad/sec}$$
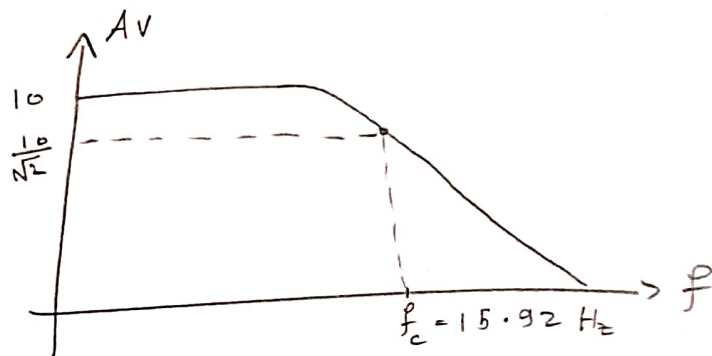
$$\Rightarrow f_t = 158.357 \text{ Hz} \Rightarrow \text{unity gain frequency}$$



3.

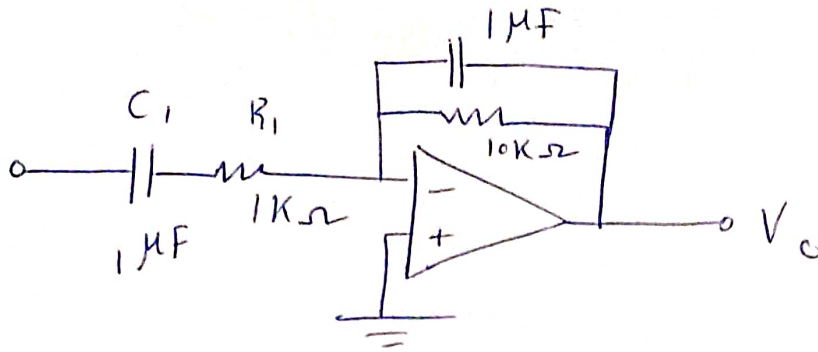

$$\Rightarrow A_V = -\frac{Z_2}{Z_1}, \quad Z_2 = \frac{1}{sC_2} \parallel R_2 = \frac{R_2}{1 + R_2 sC_2}$$


$$Z_1 = R_1 + \frac{1}{sC_1}$$

$$A_V = \frac{-\frac{R_2}{1 + R_2 sC_2}}{R_1 + \frac{1}{sC_1}} = -\frac{R_2}{(1 + R_2 sC_2)(R_1 + \frac{1}{sC_1})}$$

$$= -\frac{R_2/R_1}{\underbrace{(1 + R_2 sC_2)}_{\text{LPF}} \underbrace{(1 + \frac{1}{R_1 sC_1})}_{\text{HPF}}}$$


$$\Rightarrow f_{c_L} = \frac{1}{2\pi(10 \times 10^3)(10^{-6})} = 15.915 \text{ Hz}$$
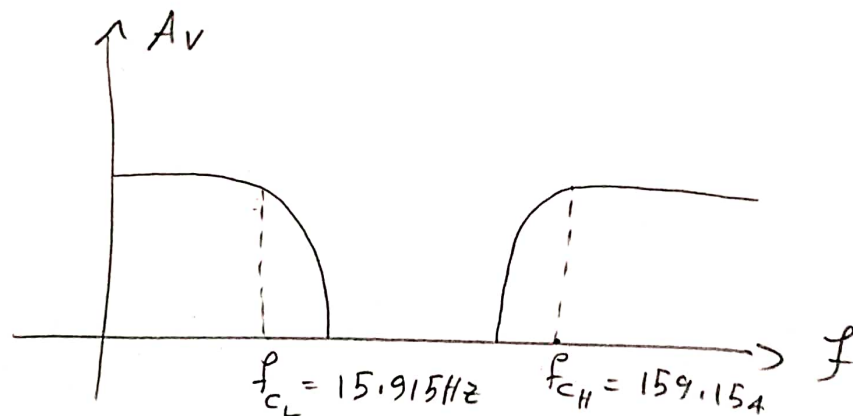
$$\Rightarrow f_{c_H} = \frac{1}{2\pi(10^3)(10^{-6})} = 159.154$$




() B5f

4

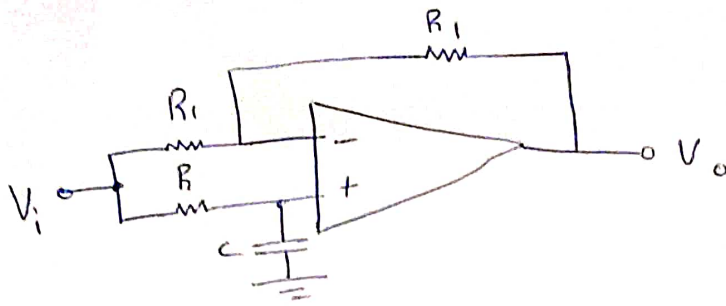

Sol:

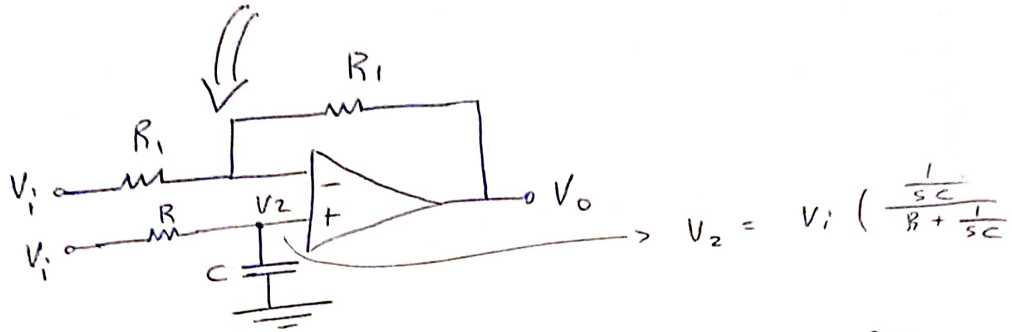


$$\Rightarrow V_0 = V_i \left(-\frac{R_1}{R_1} \right) + V_i \left(\frac{\frac{1}{sC}}{R + \frac{1}{sC}} \right) \left(1 + \frac{R_1}{R_1} \right)$$

$$= -V_i + V_i \left(\frac{1}{1 + RSC} \right) (2) = \left(-1 + \frac{2}{1 + RSC} \right) V_i$$

$$\Rightarrow A_v = \frac{V_0}{V_i} = \frac{2}{1 + RSC} - 1 = \frac{2 - (1 + RSC)}{1 + RSC}$$

$$\Rightarrow A_v = \frac{+1 - RSC}{1 + RSC} = - \left[\frac{s - \frac{1}{RC}}{s + \frac{1}{RC}} \right]$$

$|A_v| = 1$
 $\Rightarrow \frac{1}{RC} = \omega \Rightarrow \omega = \frac{1}{RC}$

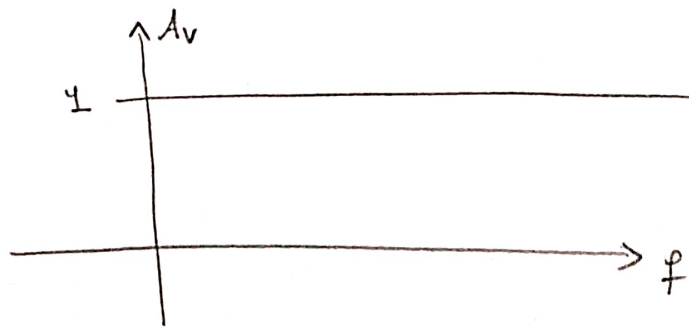

\Rightarrow gain is always equal to one for all ω .

\Downarrow
all-pass filter
 \Downarrow
used only to add phase shift