

Electronic Circuits

Operational Amplifier

Lecture 6

Dr. Roaa Mubarak

Op-Amp Applications

- Non linear Applications

9- Logarithmic Amplifier

10- Anti-Logarithmic Amplifier

11- Analog Multiplier

12- Analog Divider

13- Voltage Regulator

14- Comparator

15- Schmitt Trigger

16- Digital to Analog Converter


17- Rectifying using Op-Amp

18- Clipping using Op-Amp

19- Instrumentation Amplifier

9- The Logarithmic Amplifier

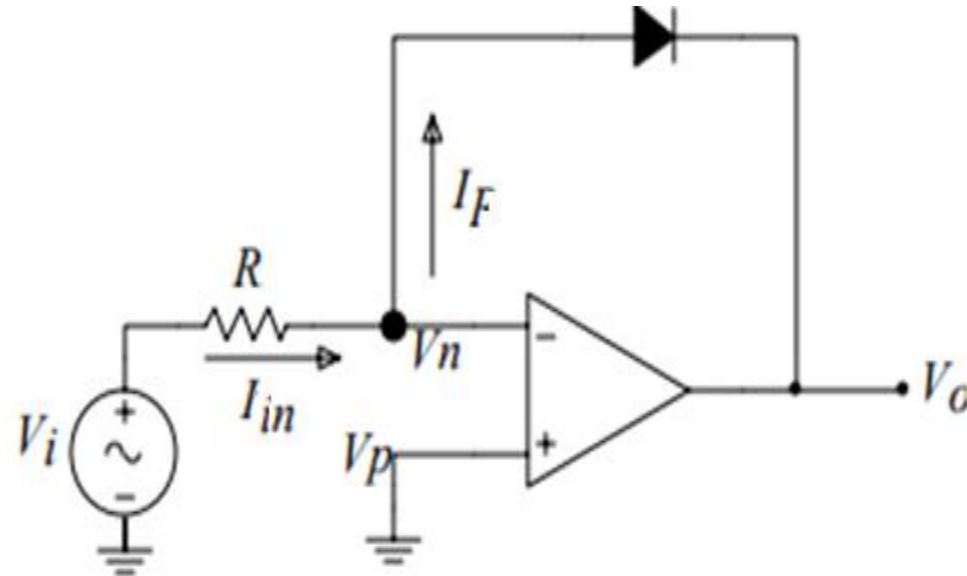- If we are interested in processing a signal that has a very wide dynamic range we take advantage of the exponential i-v characteristics of the diode and design an amplifier whose output is proportional to the logarithm of the input.



9- The Logarithmic Amplifier using Diode

- If we use this signal as the input to an inverting amplifier we may linearize the signal by using a diode in the feedback path of the amplifier.

$$I_F = I_0 \left(e^{\frac{V_F}{nV_T}} - 1 \right), \quad V_F = 0 - V_0 = -V_0$$

$$I_F \approx I_0 e^{\frac{-V_0}{nV_T}}, \quad I_F = I_{in} = \frac{V_{in}}{R}$$

$$\frac{V_{in}}{R} \approx I_0 e^{\frac{-V_0}{nV_T}} \rightarrow \frac{V_{in}}{R I_0} = e^{\frac{-V_0}{nV_T}}$$


$$\ln \frac{V_{in}}{I_0 R} = \ln e^{\frac{-V_0}{nV_T}}$$

$$\ln \frac{V_{in}}{I_0 R} = \frac{-V_0}{nV_T}$$

$$V_0 = -nV_T \ln \frac{V_{in}}{I_0 R}$$

$$\text{if } nV_T = 1, \quad I_0 R = 1$$

$$V_0 = -\ln V_{in}$$

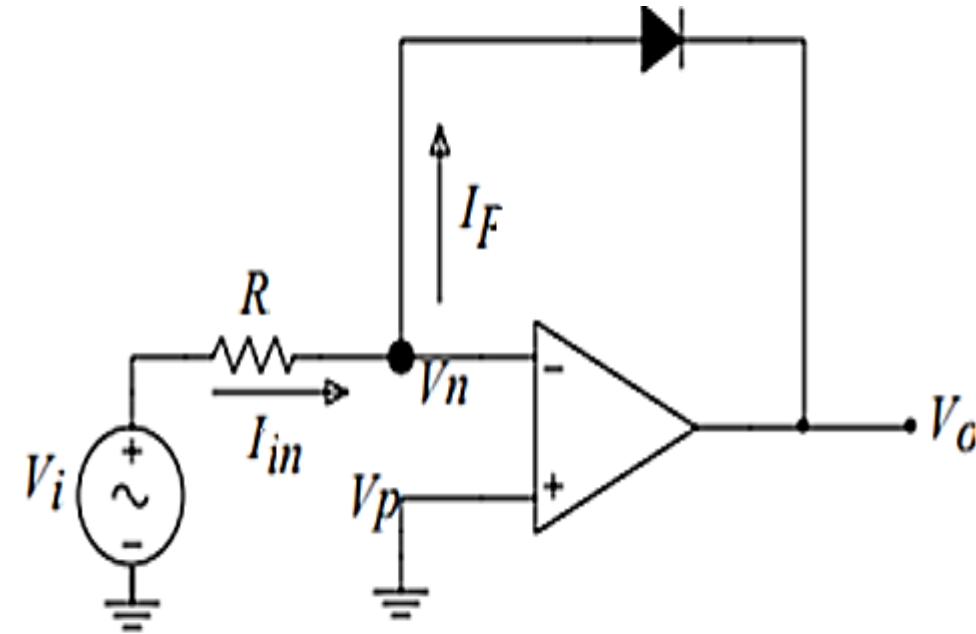

9- The Logarithmic Amplifier using Transistor

$$V_{be} = 0 - V_o = -V_o$$


$$I_{in} = I_c \approx I_e = I_{E0} e^{-\frac{V_o}{nV_T}}$$

$$\frac{V_{in}}{R} = I_{E0} e^{\frac{V_{be}}{nV_T}}$$

$$\frac{V_{in}}{I_{E0} R} = e^{\frac{V_{be}}{nV_T}}$$

$$\ln \frac{V_{in}}{I_{E0} R} = \frac{V_{be}}{nV_T}, \quad V_{be} = -V_o$$
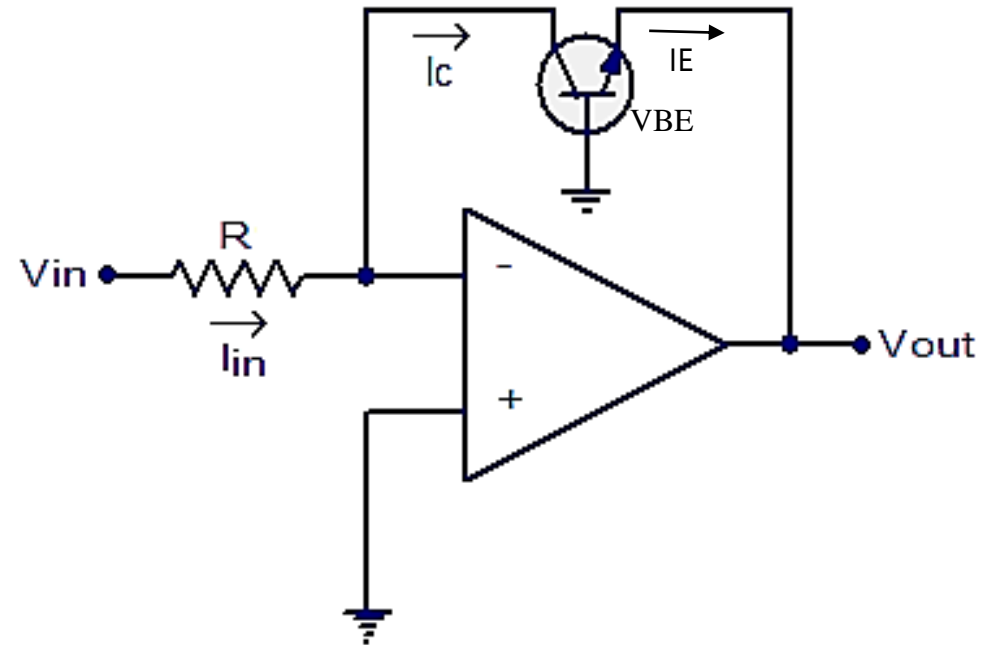
$$\therefore V_o = -nV_T \ln \frac{V_{in}}{I_{E0} R}$$



$$\text{if } nV_T = 1, \quad I_{E0} R = 1$$

$$\Rightarrow V_o = -\ln V_{in}$$

10- The Antilogarithmic Amplifier using Diode

- Similarly the antilogarithmic amplifier may be constructed by placing the diode in series with the signal source.

$$I_f \approx I_0 e^{\frac{V_f}{nV_T}}$$



$$\frac{-V_o}{R} = I_0 e^{\frac{V_{in}}{nV_T}}, \quad I_f = I = -\frac{V_o}{R}$$

$$V_o = -I_0 R e^{\frac{V_{in}}{nV_T}}$$

if $I_0 R = 1$, $nV_T = 1$

$$\Rightarrow V_o = -e^{V_{in}}$$

$$V_o = -\ln^{-1}(V_{in})$$

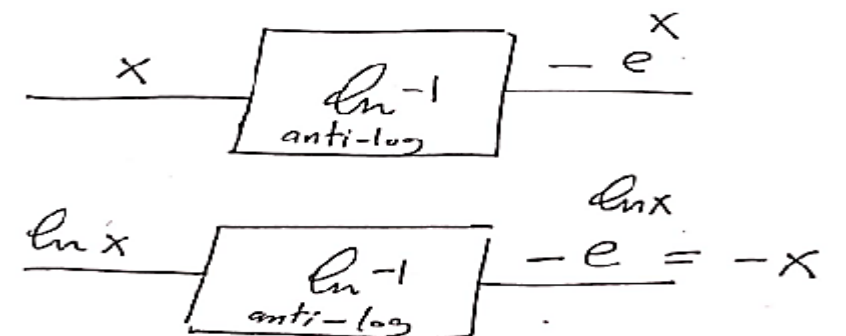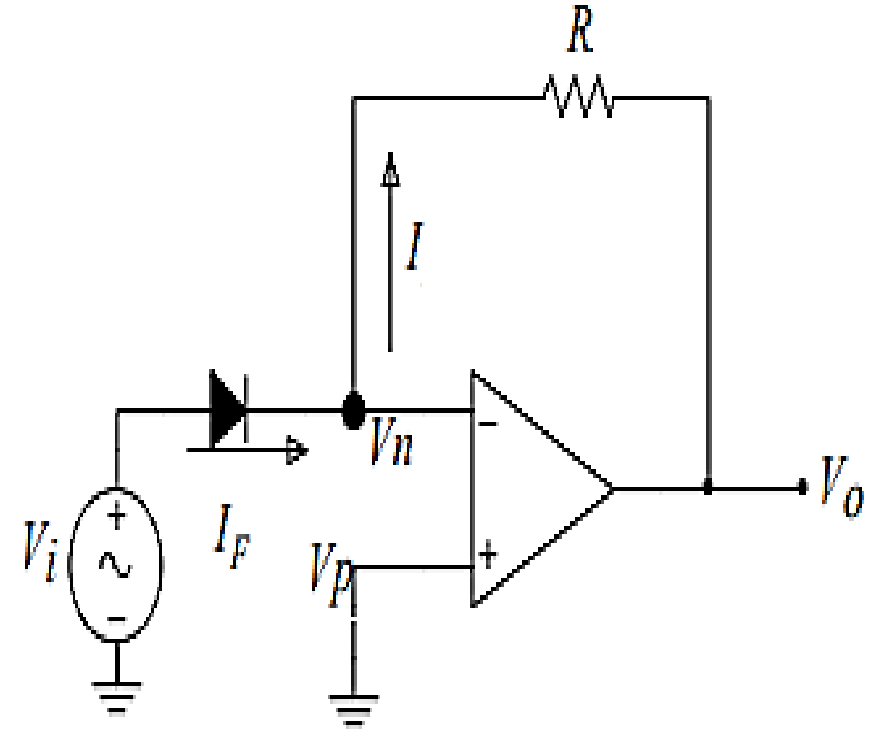

10- The Antilogarithmic Amplifier using Transistor


$$V_o = -I_c R \approx -I_E R$$

$$I_E = I_{E_0} e^{\frac{V_{cb}}{\eta V_T}}$$

$$, V_{cb} = V_{in} \Rightarrow I_E = I_{E_0} e^{\frac{V_{in}}{\eta V_T}}$$

$$\therefore V_o = -I_E R = -R \cdot I_{E_0} e^{\frac{V_{in}}{\eta V_T}}$$
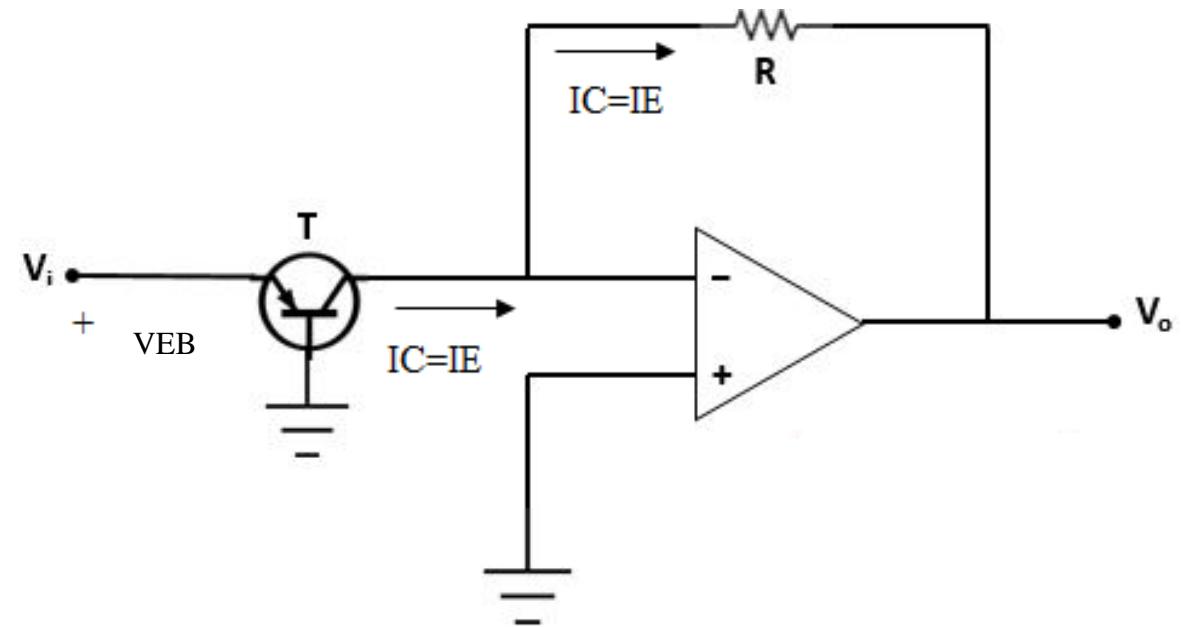
$$V_o = -I_{E_0} R e^{\frac{V_{in}}{\eta V_T}}$$




$$\text{if } I_{E_0} R = 1, \quad \eta V_T = 1$$

$$\therefore V_o = -e^{V_{in}}$$

$$V_o = -\ln^{-1}(V_{in})$$


11- The Analog Multiplier

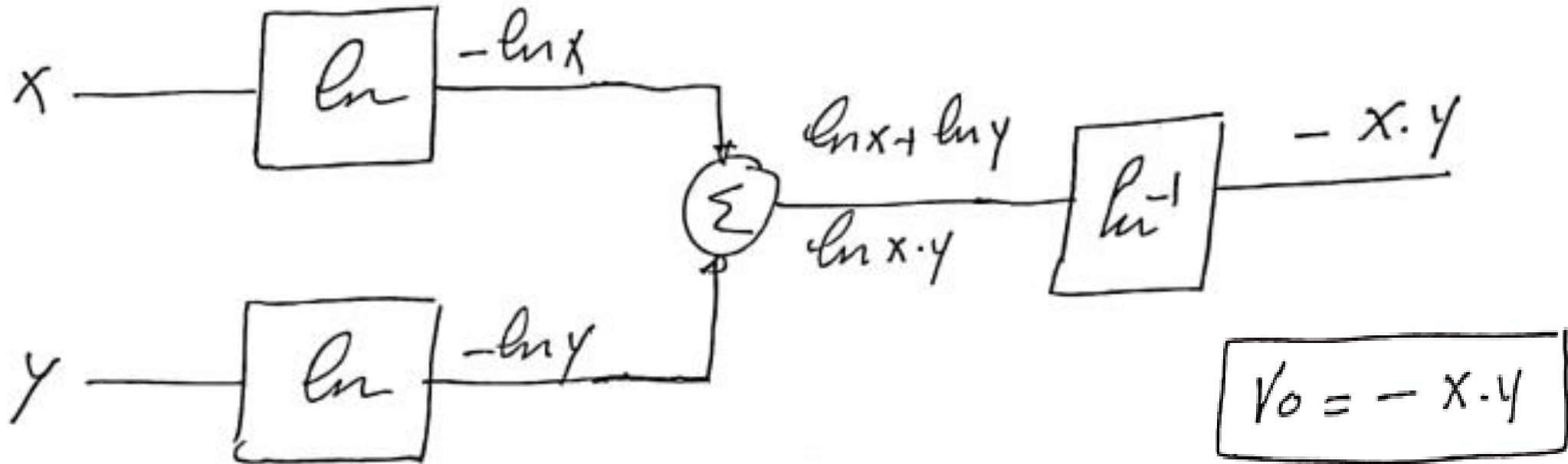- Combining between summing, logarithmic and antilogarithmic circuits and the output will be the multiply of two inputs.



11- The Analog Multiplier


- $V_b = -V_1 * V_2$

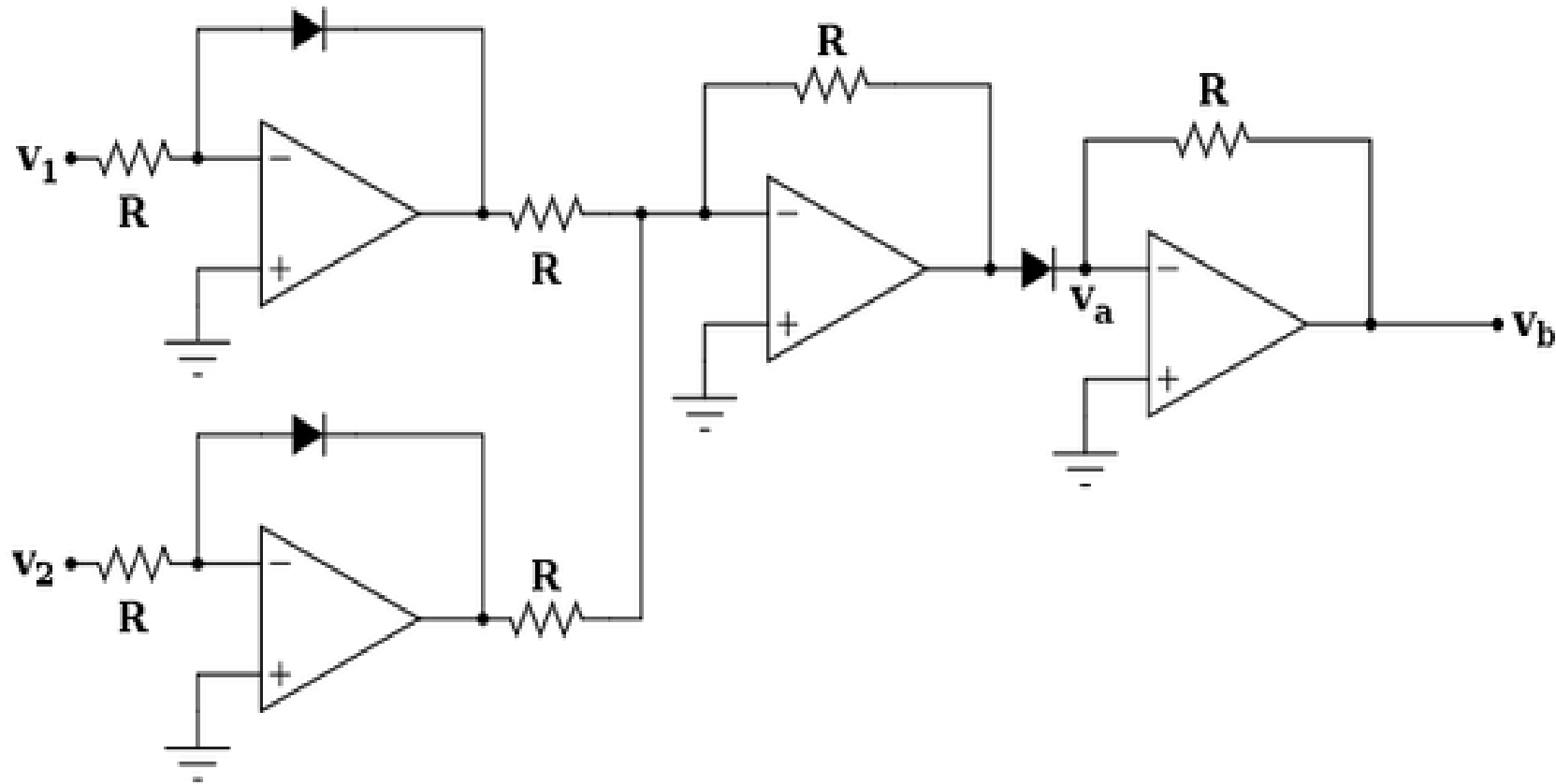

$$V_b = -V_1 * V_2$$



12- The Analog Divider

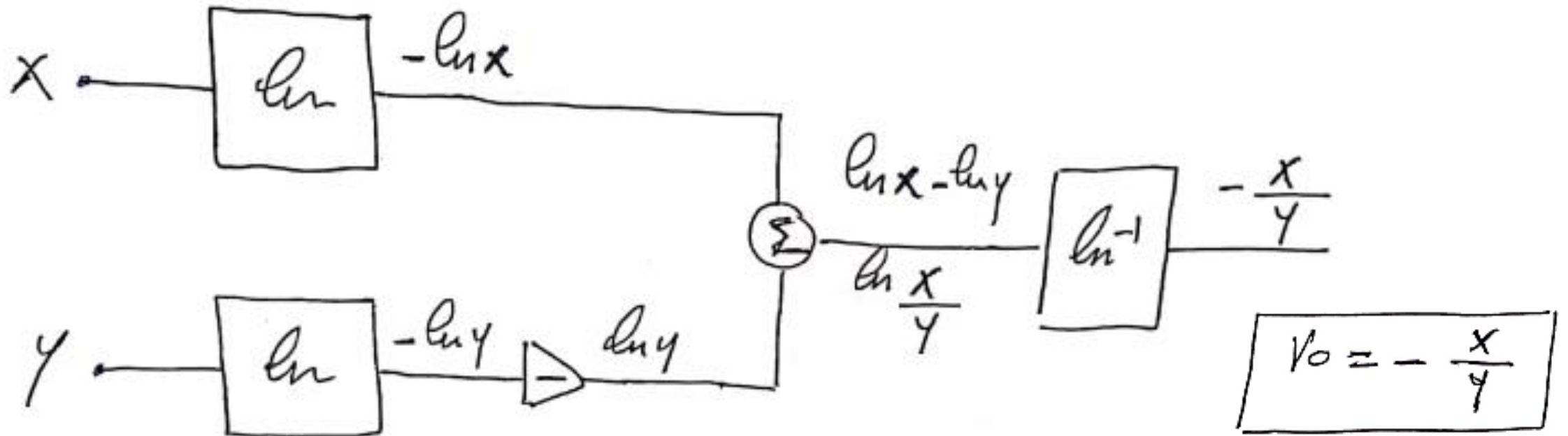- Combining between Difference amplifier with logarithmic and antilogarithmic circuits and the output will be the dividing of two inputs.




12- The Analog Divider

- $V_o = -V_1/V_2$

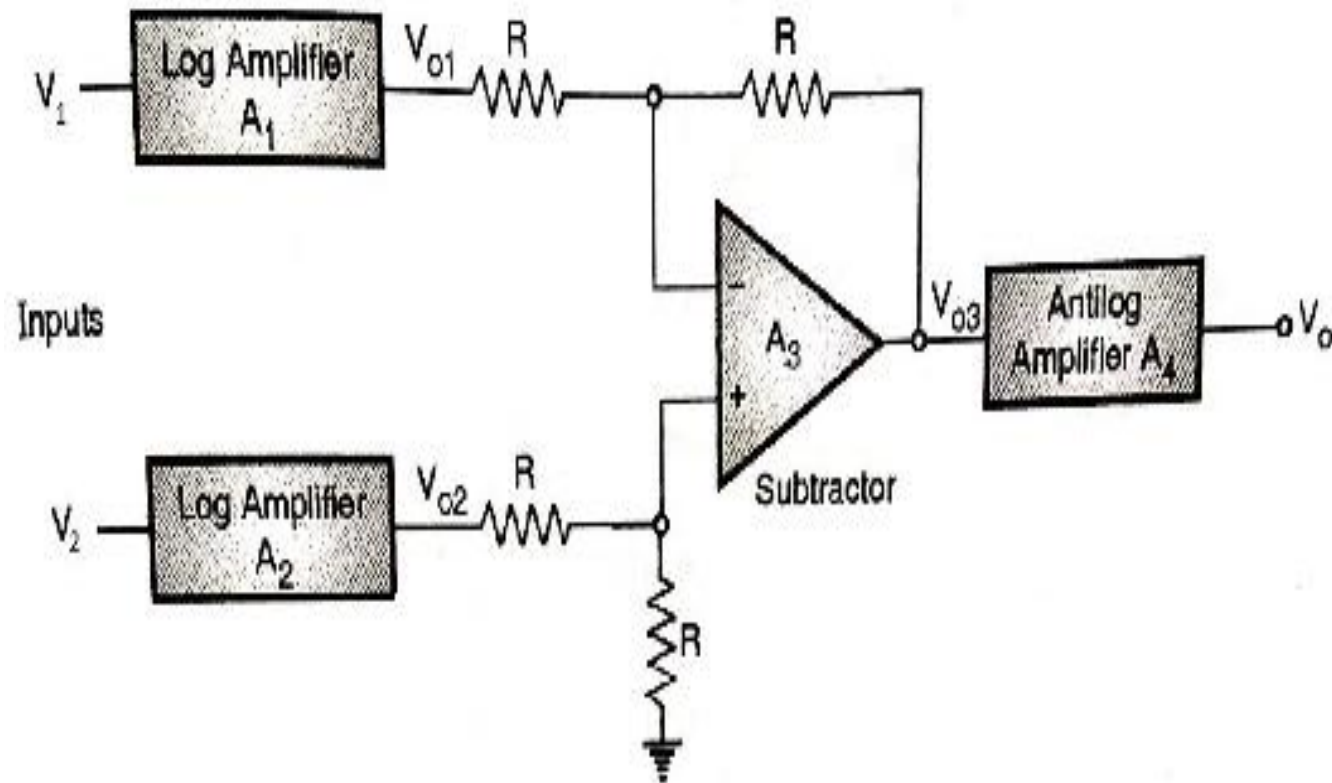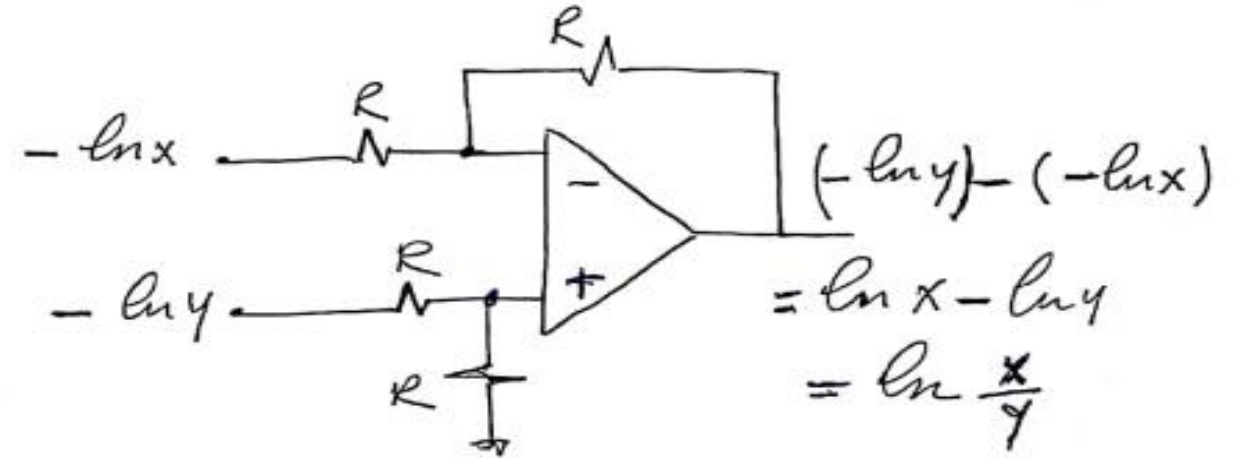



12- The Analog Divider

- $V_o = -V_1/V_2$

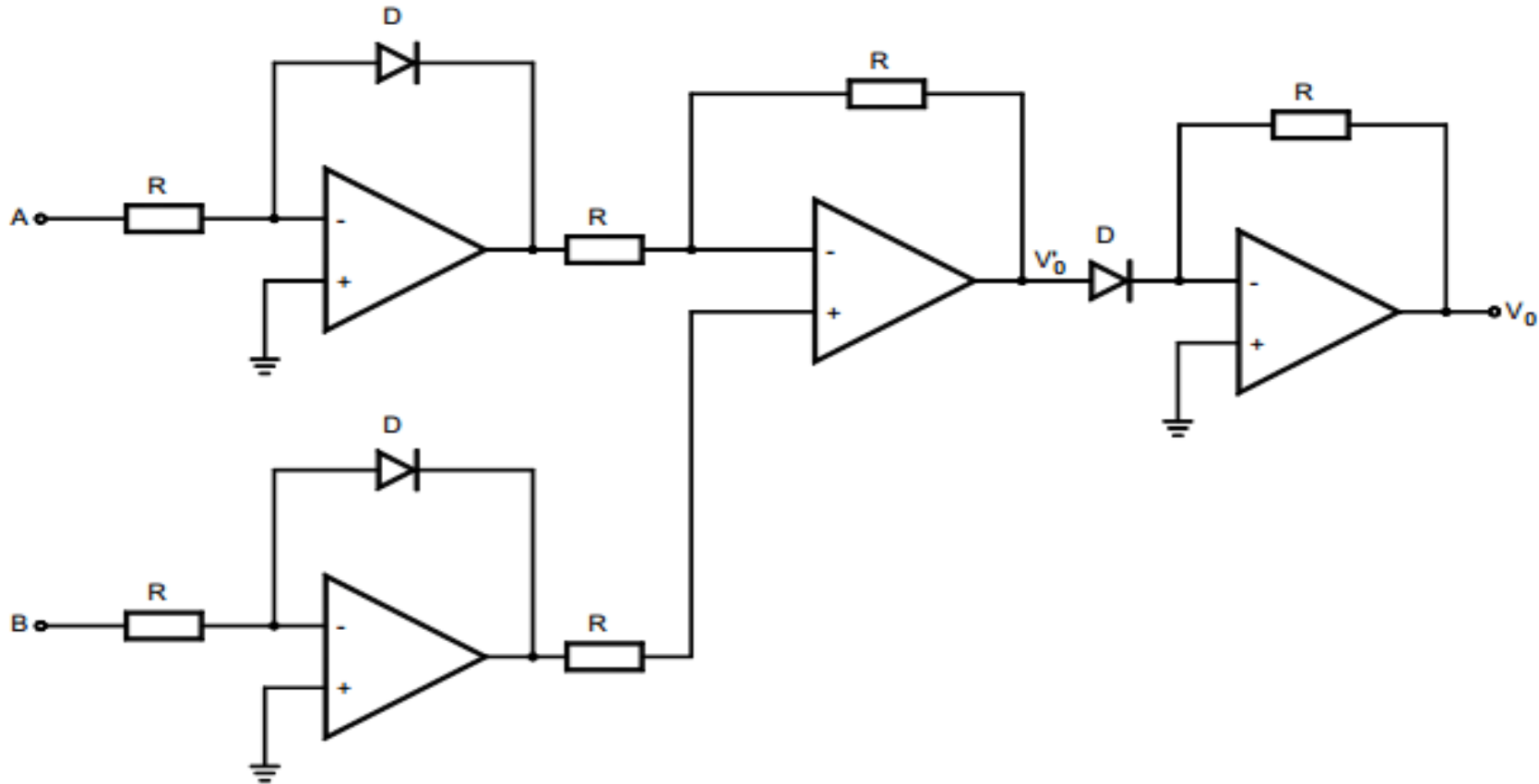


13- The Voltage Regulator

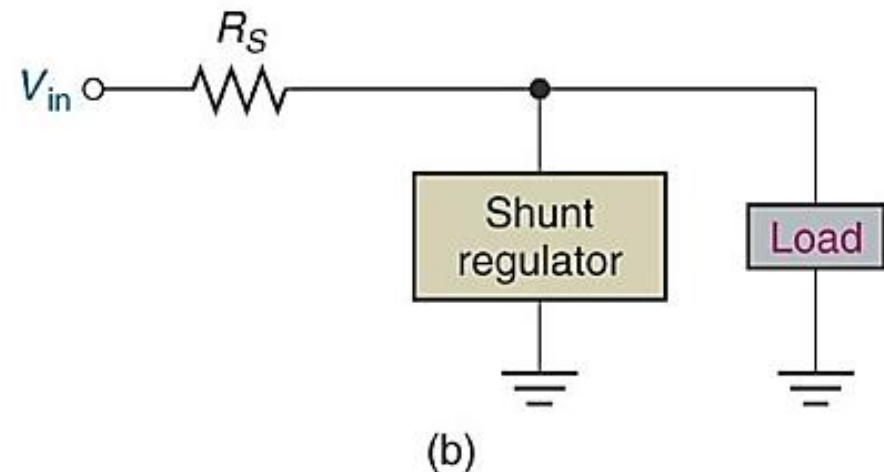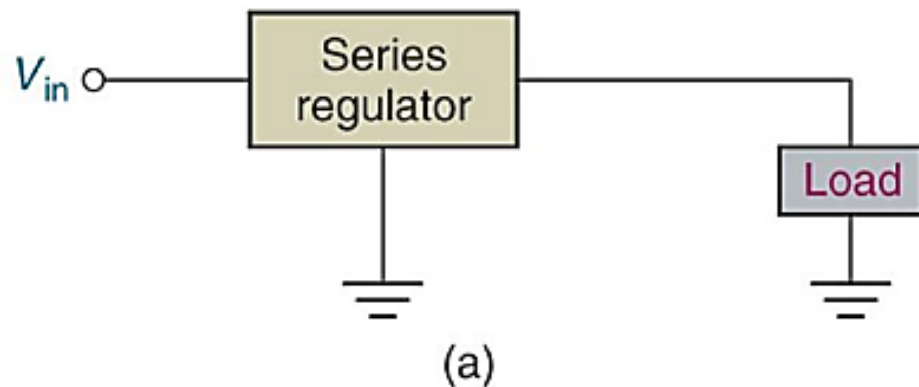- Fundamental classes of voltage regulators are linear regulators and switching regulators.
- Two basic types of linear regulator are the series regulator and the shunt regulator.
- The series regulator is connected in series with the load and the shunt regulator is connected in parallel with the load.




13- The Voltage Regulator

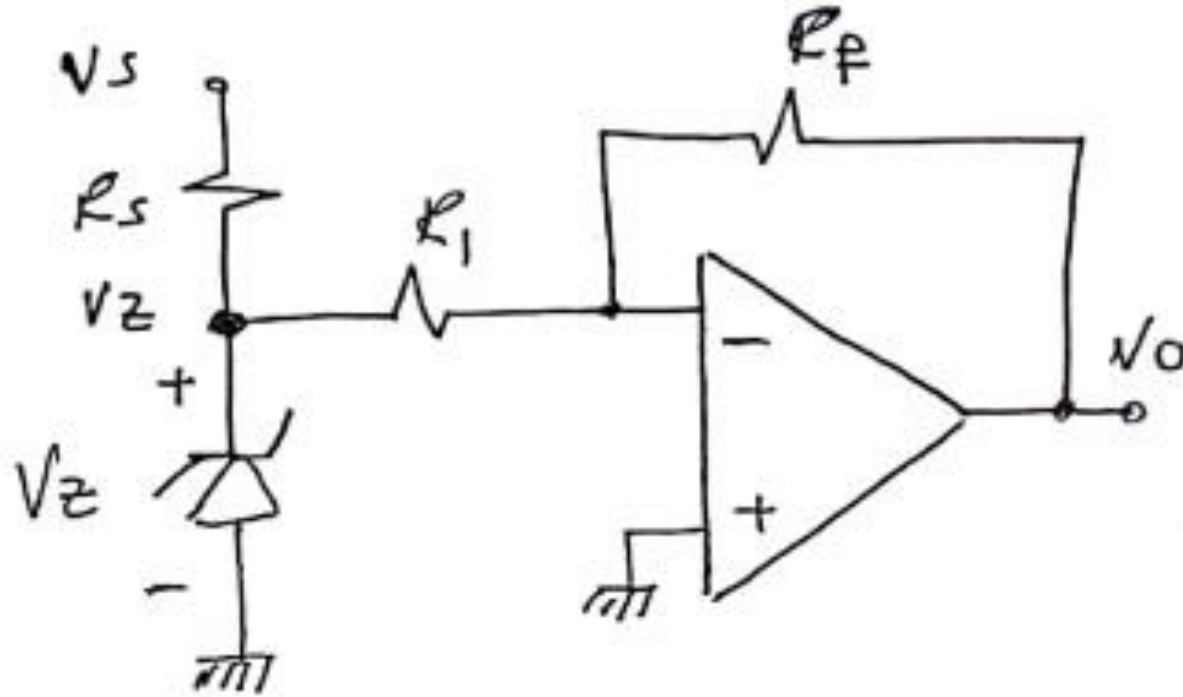

$$V_o = - \frac{R_f}{R_1} V_z$$

13- The Voltage Regulator

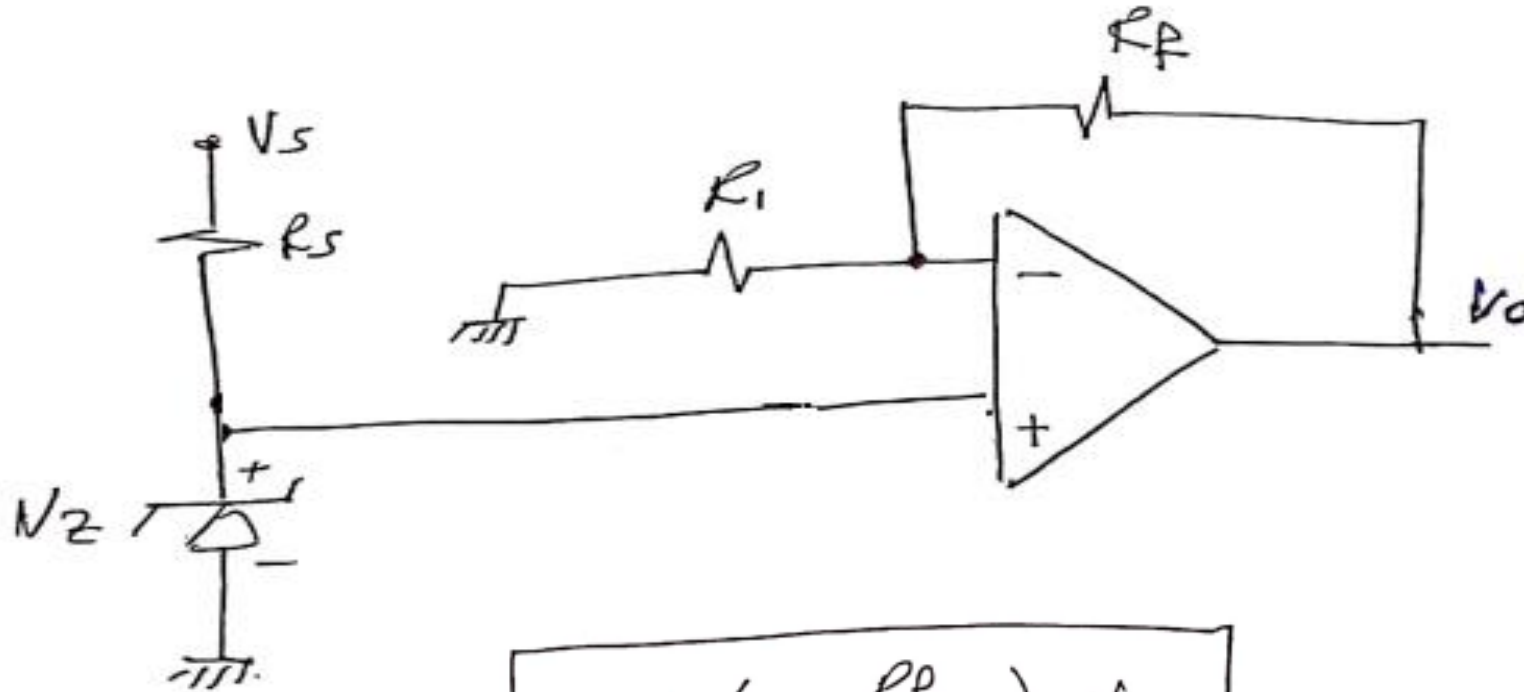

$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_z$$