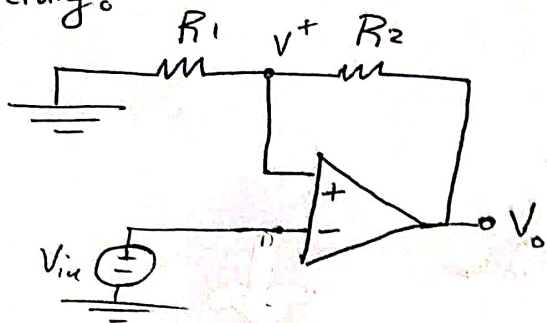


Bistable Multivibrator :


* Inverting :



$$\Rightarrow V^+ = V_o \left(\frac{R_1}{R_1 + R_2} \right) = V_o \beta$$

if $V_o = L^+$ (High) $\Rightarrow V^+ = \beta L^+ = V_{TH}$

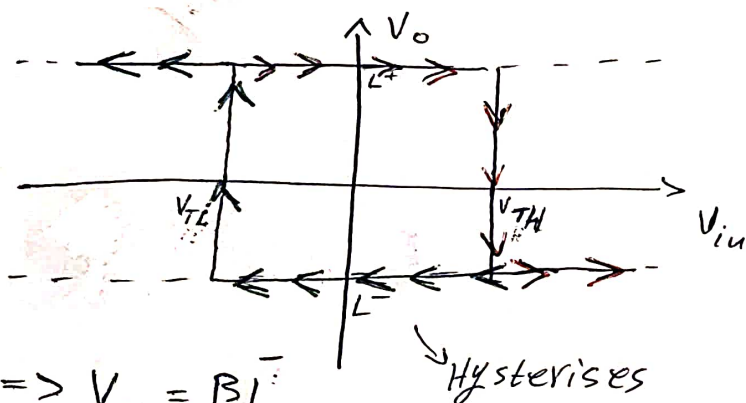if $V_o = L^-$ (Low) $\Rightarrow V^- = \beta L^- = V_{TL}$




$$\Rightarrow V_{TL} = \beta L^-$$

$$V_{TH} = \beta L^+$$

Hysteresis

* non-inverting :

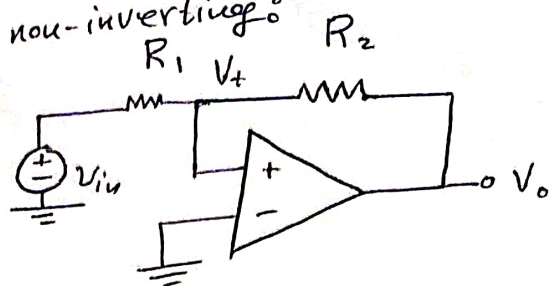

$$\Rightarrow V_+ = V_{in} \frac{R_2}{R_1 + R_2} + V_o \frac{R_1}{R_1 + R_2}$$

if $V_o = L^+$:

$$\Rightarrow V_+ = V_{in} \frac{R_2}{R_1 + R_2} + L^+ \frac{R_1}{R_1 + R_2}$$

L> To get V_{TL} : $V_+ = 0$

$$\Rightarrow V_{in} R_2 + L^+ R_1 = 0$$

$$\Rightarrow V_{TL} R_2 + L^+ R_1 = 0$$


$$V_{TL} = -L^+ \frac{R_1}{R_2}$$

if $V_o = L^-$:

\Rightarrow similarly :


$$V_{TH} = -L^- \frac{R_1}{R_2}$$

Hysteresis :

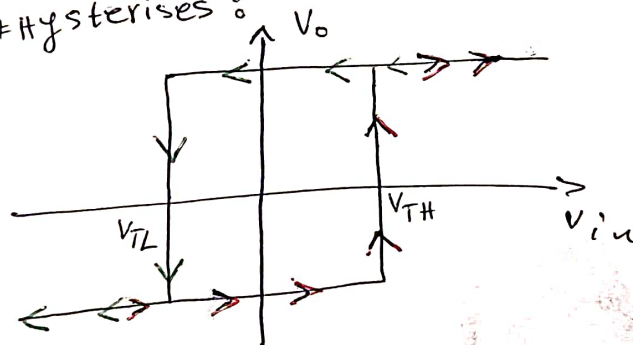


\Rightarrow Bistable circuits can be used as comparators

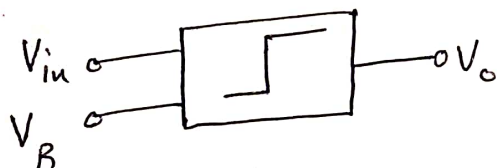\Rightarrow called schmitt triggers. \Rightarrow It prevents the signal that have fast changing noise from switching the comparator o/p between L^+ & L^- back & forth when fluctuating at the threshold voltage.



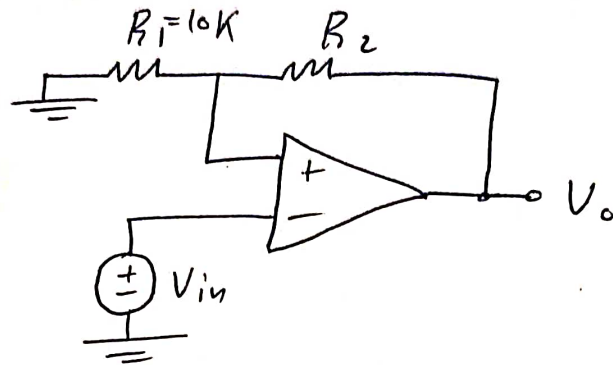Q₁: The op-amp in the shown bistable ct. has o/p saturation voltages of $\pm 13V$. Design the ct. to obtain threshold voltages of $\pm 5V$. For $R_1 = 10$ find the value of R_2 .



Sol: $\because V_{TH} = \beta L^+ , V_{TL} = \beta L^-$


$$\Rightarrow 5 = \left(\frac{R_1}{R_1 + R_2} \right) (13)$$

$$\Rightarrow 5(10 + R_2) = 130$$


$$\Rightarrow 50 + 5R_2 = 130$$

$$\boxed{R_2 = 16 \text{ K}\Omega}$$

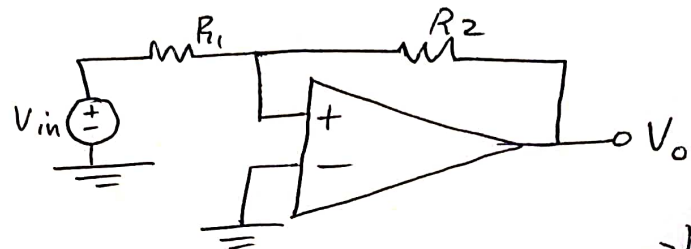Q₂: Consider the shown bistable circuit, let $L_+ = -L_- = 10V$ & $V_{TH} = -V_{TL} = 5V$. if V_i is a triangular wave with 0V average & 10V peak amplitude & 1ms period. sketch the o/p waveform. Find the time interval between the zero crossing of V_{in} & V_o .



Sol:

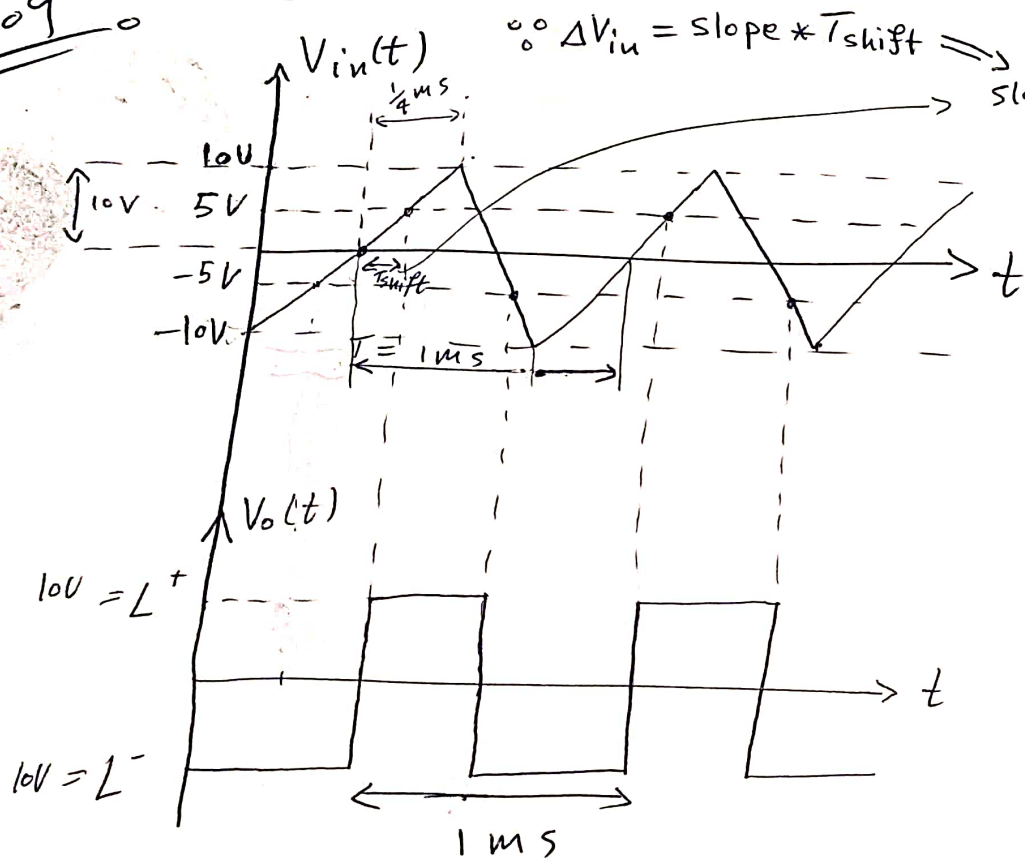


$\Delta V_{in} = \text{slope} \times T_{\text{shift}}$

$\text{slope} = \frac{10}{0.25 \times 10^{-3}}$ $\rightarrow \Delta V$ in $\frac{1}{4}$ cycle
 $\Rightarrow (T_{\text{shift}}) \cdot \left(\frac{10}{0.25 \times 10^{-3}} \right) = 5$
 $\Rightarrow T_{\text{shift}} = \frac{5}{\frac{10}{0.25 \times 10^{-3}}} = 0.125 \times 10^{-3}$

$T_{\text{shift}} = 0.125 \text{ ms}$

interval between zero crossing of V_{in} & V_o

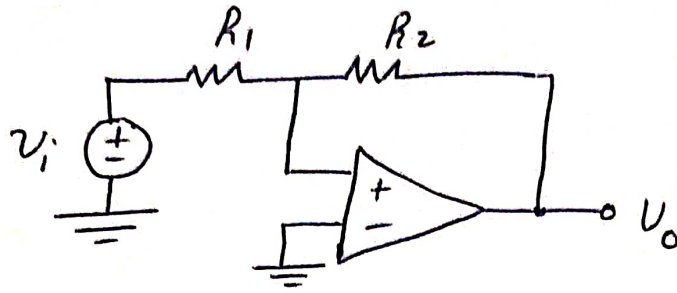Q₃ : For shown circuit, if the op amp has 3
 $\pm 10V$ output saturation levels, design
 the ct. to obtain $\pm 5V$ thresholds.




Sol :

\because the given ct. is a non-inverting bistable multivibrator.

$$\Rightarrow V_{TL} = -L^+ \frac{R_1}{R_2}, \quad V_{TH} = -L^- \frac{R_1}{R_2}$$

$$\because L^+ = 10, L^- = -10$$

$$V_{TL} = -5, V_{TH} = +5$$

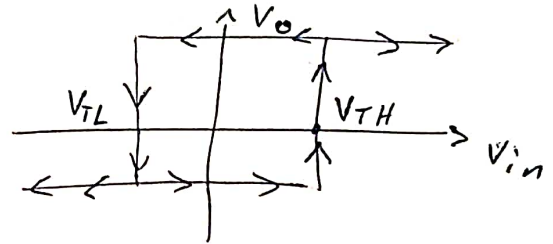

Let $R_1 = 10K\Omega$

$$\Rightarrow 5 = 10 \left(\frac{10K}{R_2} \right)$$


$$\Rightarrow R_2 = 20K\Omega$$

Q4 For the shown circuit. if $L_+ = -L_- = 10V$ & $R_1 = 1K\Omega$. Find the value of R_2 that gives a hysteresis of 100 mV width.


Sol:

$$L_+ = -L_- = 10V$$

$$R_1 = 1K\Omega$$

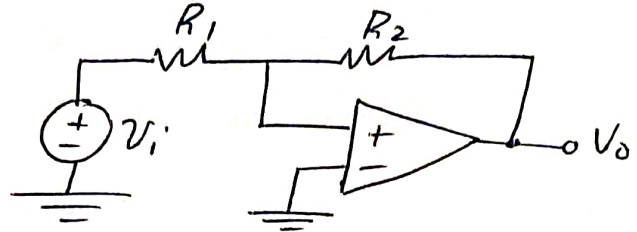

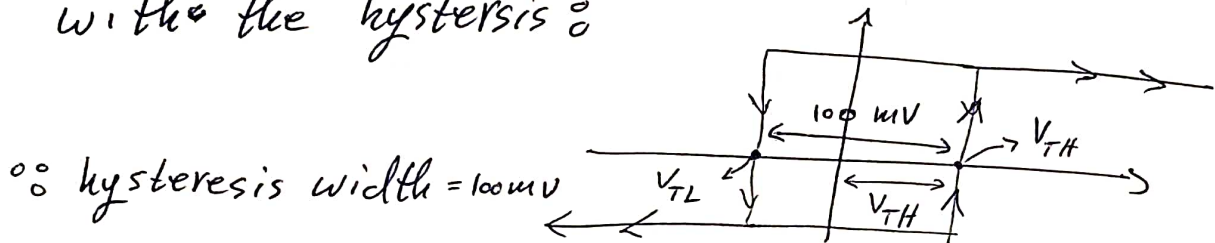∴ the ckt. is a non-inverting bistable multivibrator with the hysteresis ∴



∴ hysteresis width = 100 mV


$$\Rightarrow V_{TH} = -V_{TL} = \frac{100mV}{2} = 50mV$$

$$\therefore V_{TH} = -L \left(\frac{R_1}{R_2} \right)$$

$$\Rightarrow V_{TH} = 50 \times 10^{-3} = (10) \left(\frac{1K}{R_2} \right)$$

$$\Rightarrow \boxed{R_2 = 200K\Omega}$$

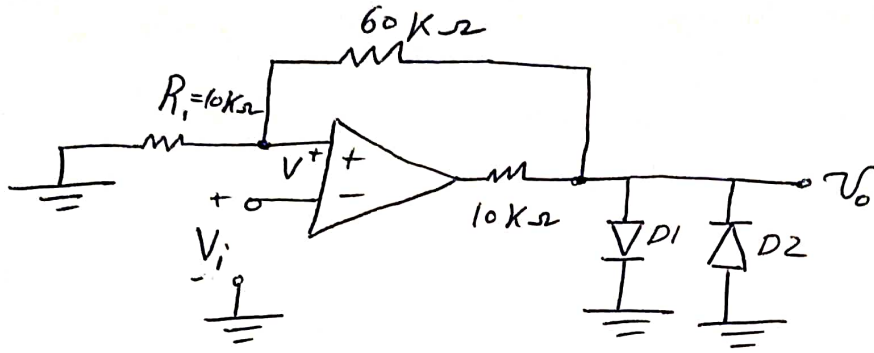Q₅ : For the shown circuit. sketch & Label the transfer characteristic $V_o - V_i$. The diodes are assumed to have a constant 0.7-drop when conducting, & the op-amp saturates at $\pm 12V$. what is the maximum diode current?



Sol:



- Because of the two diodes ($D1 - D2$) at the o/p node $\Rightarrow V_o = \pm 0.7$

$\begin{matrix} \nearrow +0.7 \\ \searrow -0.7 \end{matrix}$
 (if $D1 \rightarrow ON$) (if $D2 \rightarrow ON$)

$$\therefore \text{So, } V^+ = \pm 0.7 \left(\frac{10K}{(10K + 60K)} \right) = \pm 0.1V$$

$$\Rightarrow V_{TH} = 0.1V, \quad V_{TL} = -0.1V$$

* Max diode current:

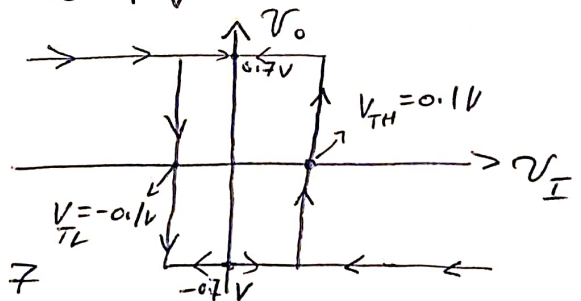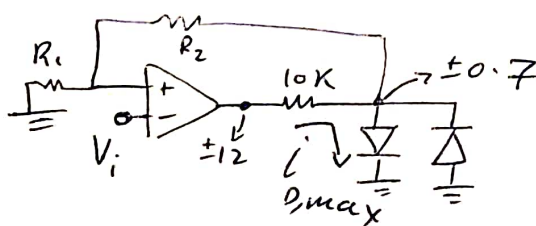


$$\Rightarrow i_{D_{max}} = \frac{12 - 0.7}{10K} = 1.12mA$$

Q6: Considering the same circuit of the last question (Q5). if R_1 is eliminated & R_2 is short circuited. sketch & label the transfer characteristic. Assume the diodes have a constant $0.7V$ drop when conducting & the op-amp saturates at $\pm 12V$.

Sol:

$$L_+ = 12V$$

$$L_- = -12V$$

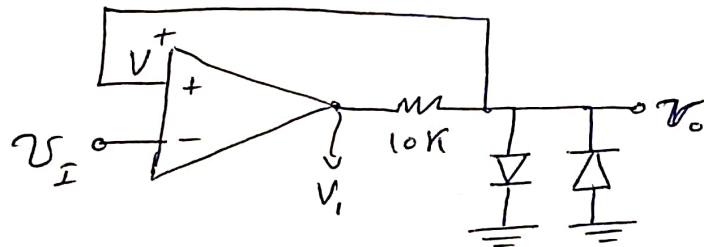

$\Rightarrow v_o = \pm 0.7 \Rightarrow$ depending on whether $v_i = +12$ or $-12V$.

$$\therefore v^+ = v_o = \pm 0.7$$

$$\Rightarrow V_{TH} = 0.7, \quad V_{TL} = -0.7$$

