
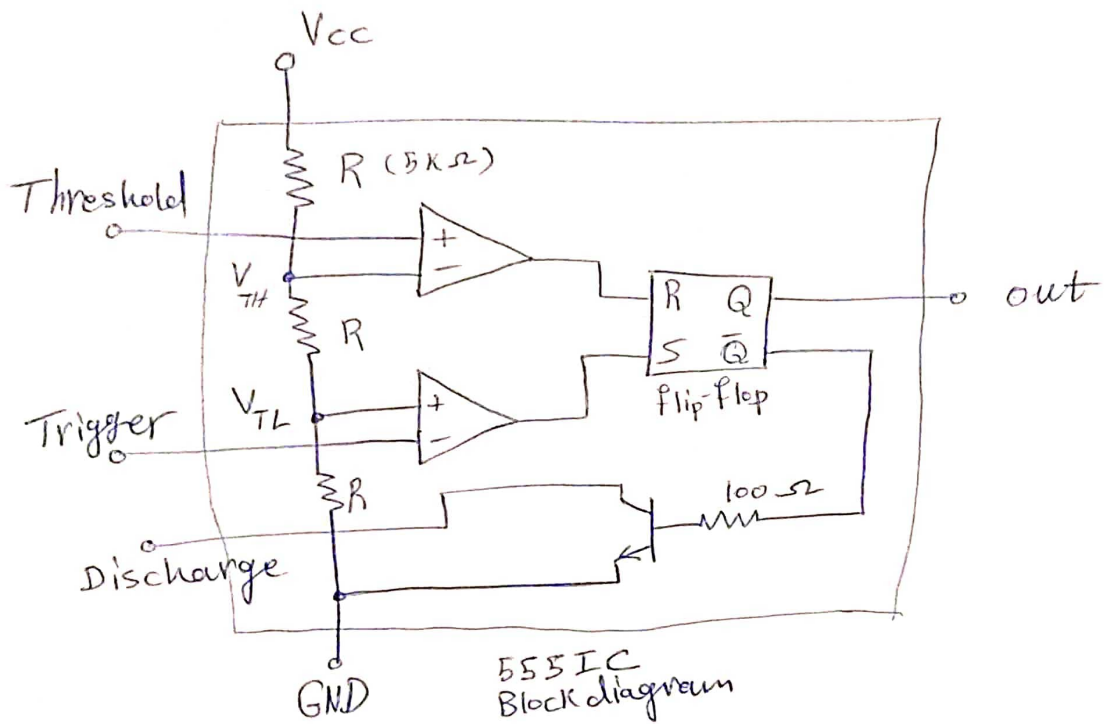


# # 555 Timer :

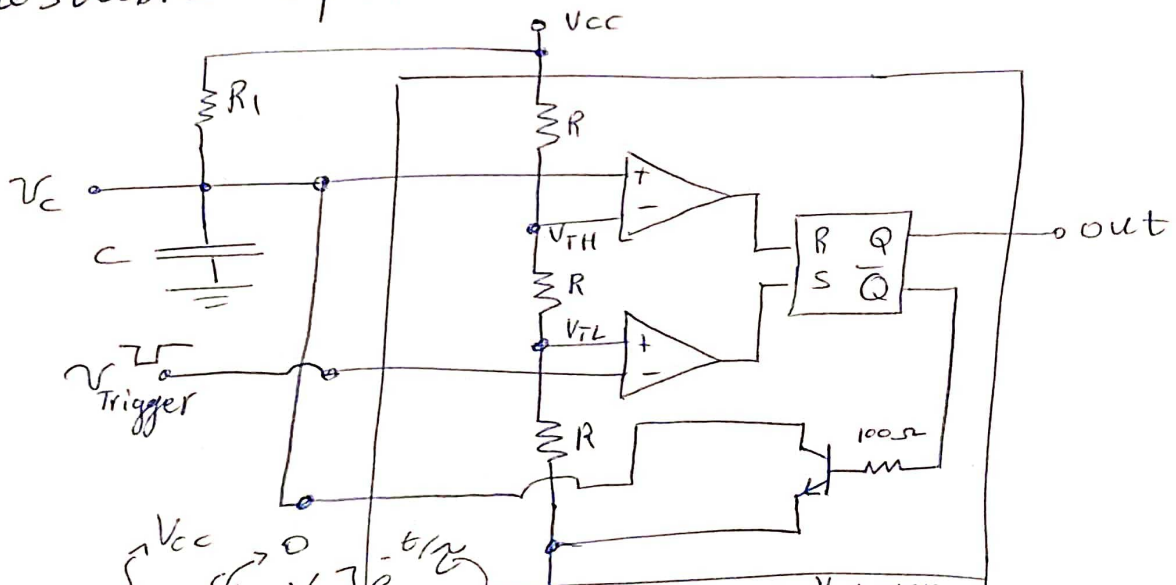

## \* Monostable operation :




$$V_C = V_{CC} - [V_{CC} - V_{TH}] e^{-t/R_1 C}$$

$$V_C = V_{CC} [1 - e^{-t/R_1 C}]$$



$$\text{at } t = T \Rightarrow V_C = \frac{2}{3} V_{CC} = V_{TH}$$

$$\Rightarrow \frac{2}{3} V_{CC} = V_{CC} [1 - e^{-T/R_1 C}]$$
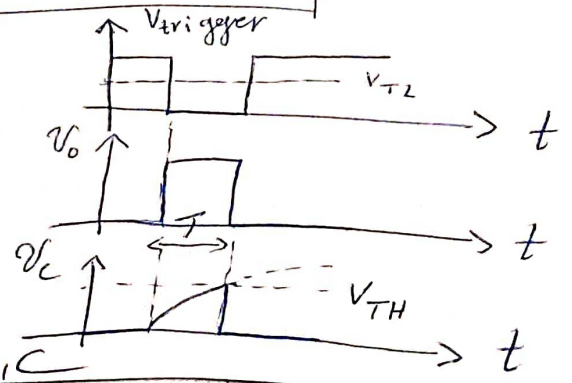
$$\Rightarrow T = R_1 C \ln(3) = 1.1 R_1 C$$



## \* Astable operation:

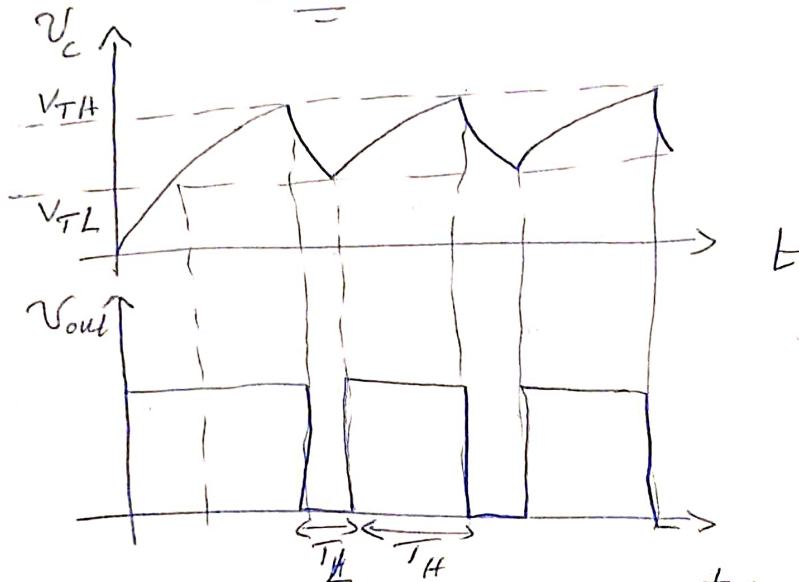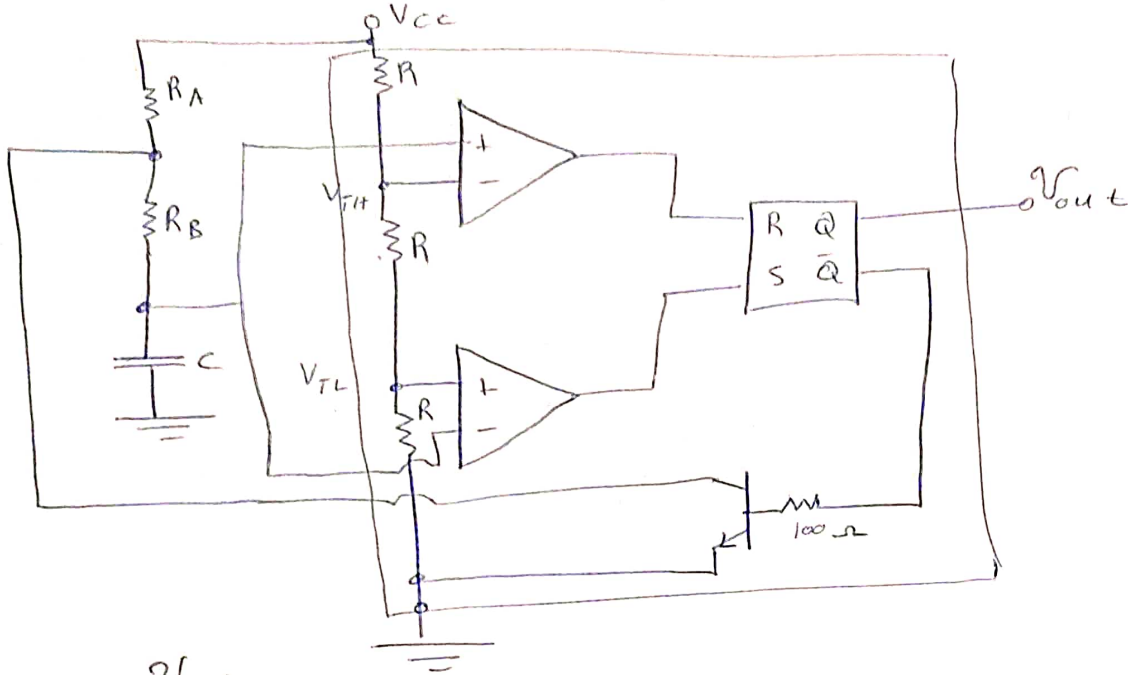

$$V_c = V_f + (V_{init} - V_f) e^{-\frac{t}{\tau}}$$

\* at charging :

$$(V_{out} = V_{cc}) \quad V_c = V_{cc} + (V_{TL} - V_{cc}) e^{-\frac{t}{\tau}}, \quad \tau = (R_A + R_B)C$$

$$\Rightarrow V_c = V_{TH} \text{ at } t = T_H$$

$$V_{TH} = \frac{2}{3} V_{cc}, \quad V_{TL} = \frac{1}{3} V_{cc}$$

$$\Rightarrow \frac{2}{3} V_{cc} = V_{cc} + (\frac{1}{3} V_{cc} - V_{cc}) e^{-\frac{T_H}{(R_A + R_B)C}}$$

$$\Rightarrow \frac{1}{3} = \frac{2}{3} e^{-\frac{T_H}{\tau}}$$

$$\Rightarrow T_H = (R_A + R_B)C (\ln 2) = 0.69 (R_A + R_B)C$$

\* at discharging ( $V_{out} = 0$ ):

$$V_c = 0 + (V_{TH} - 0) e^{-t/\tau}, \quad \tau = R_B C$$

$\downarrow$                        $\downarrow$   
 $V_f$                        $V_{init}$

$$V_c = V_{TH} e^{-t/\tau} = \frac{2}{3} V_{cc} e^{-\frac{t}{R_B C}}$$

at  $V_c = \frac{1}{3} V_{cc}$ ,  $\Rightarrow t = T_L$

$$\frac{1}{3} V_{cc} = \frac{2}{3} V_{cc} e^{-\frac{T_L}{R_B C}}$$

$$\Rightarrow T_L = \ln(2) R_B C = 0.69 R_B C$$

$\Rightarrow$  Duty cycle =  $\frac{T_H}{T_H + T_L} = \frac{R_A + R_B}{R_A + 2R_B}$

period.  $\Rightarrow T = T_H + T_L \Rightarrow f = \frac{1}{T}$

EX 1 : using 10 nF capacitor, find the value of  $R_1$  that yields an o/p pulse of 100  $\mu s$  in monostable ct.

sol :

$$T = R_1 C \ln(3)$$

$$\Rightarrow R_1 = \frac{100 \times 10^{-6}}{10 \times 10^{-9} \ln(3)} = 9.1 \text{ K}\Omega$$

EX 2: For the 555-Astable multivibrator based ct. with a 1000 pF cap. find the values of  $R_A$  &  $R_B$  that results in oscillation freq. of 100 KHz & duty cycle 75%.

Sol:

$$f = 100 \text{ KHz} \Rightarrow T = \frac{1}{f} = 10 \mu\text{sec.}$$

$$\Rightarrow \text{duty cycle} = 75\% \Rightarrow T_H = 7.5 \mu\text{sec}$$
$$\Rightarrow T_L = 2.5 \mu\text{sec}$$
$$\therefore \text{duty cycle} = \frac{R_A + R_B}{R_A + 2R_B} = 0.75 \quad (1)$$

$$\therefore T = \ln(2) [R_A + 2R_B] C$$

$$\Rightarrow 10 \times 10^{-6} = 0.69 (1000 \times 10^{-12}) (R_A + 2R_B)$$


$$\Rightarrow \boxed{R_A = 14.5 \times 10^3 - 2R_B} \quad \text{sub. in (1)}$$

$$\Rightarrow 0.75 = \frac{14.5 \times 10^3 - R_B}{14.5 \times 10^3}$$

$$\Rightarrow R_B = 3.62 \text{ K}\Omega$$

$$\Rightarrow R_A = 7.26 \text{ K}\Omega$$

# Astable ct. for PWM (constant Freq.)

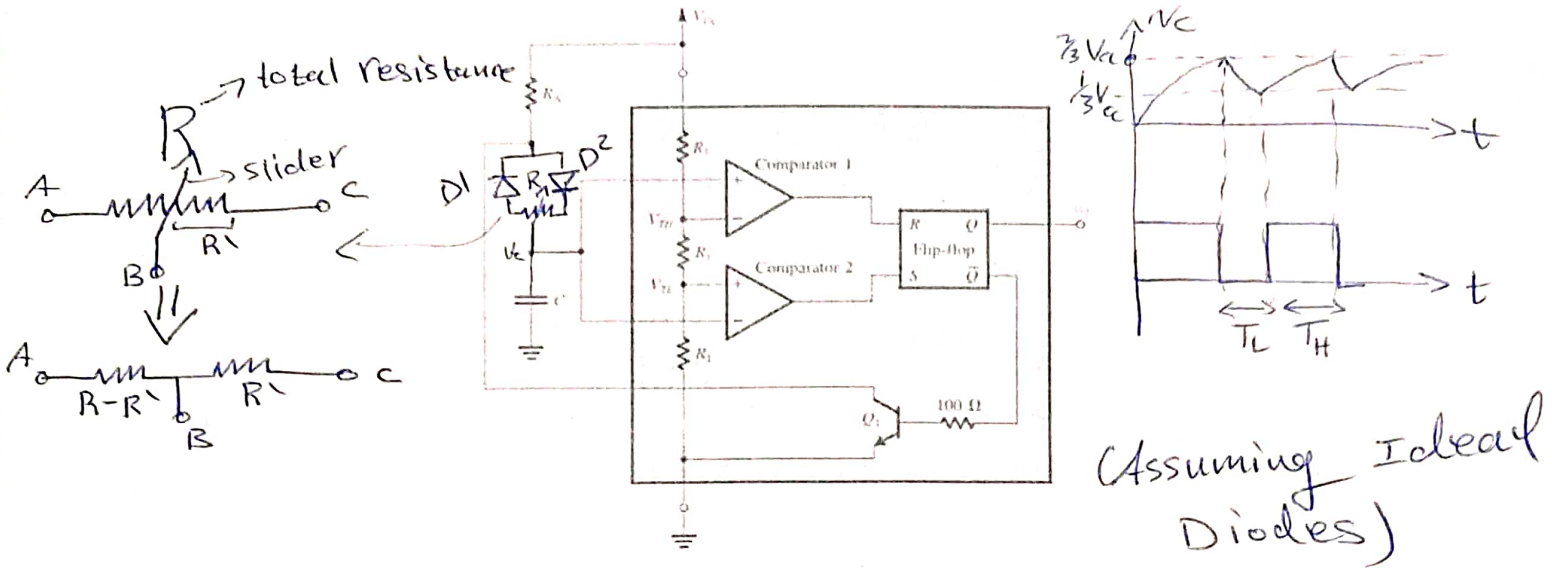

# At changing :  $D_1 \rightarrow \text{off} \rightarrow$

$$D_2 \rightarrow ON \rightsquigarrow$$

$$\Rightarrow Z = (R_A + R') C$$

$$\Rightarrow \psi_c = (V_F) + (V_{init} - V_F) e$$

at  $t = T_H \rightarrow V_C = \frac{2}{3} V_{CC}$

$$\frac{2}{3} V_{CC} = \frac{V_{CC}}{\frac{1}{F_1}} + (\frac{1}{3} V_{CC} - V_{CC}) e$$

$$\frac{2}{3} V_{CC} e^{-t/T_{H/2}} = \frac{1}{3} V_{CC}$$

$$\Rightarrow e^{\pi} = 2$$


$$T_H = r \ln(z) = \ln(z) (R' + R_A) C$$

### # A discharging :

$$\Rightarrow \tau = (R - R')C$$

$$\Rightarrow v_c = (V_F) + (V_{init} - V_F) e^{-t/\tau}$$
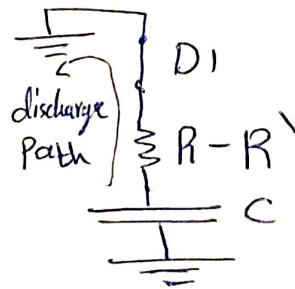
$$\Rightarrow V_{cc} = \frac{2}{3} V_{cc} e^{-t/\tau}$$





$$\Rightarrow \text{at } t = T_L \rightarrow v_C = \frac{1}{3} V_{CC}$$

$$\Rightarrow \frac{1}{3} V_{CC} = \frac{2}{3} V_{CC} e^{-\frac{T_L}{\tau}}$$

$$\Rightarrow e^{\frac{T_L}{\tau}} = 2$$


$$\Rightarrow T_L = \ln(2) \tau$$

$$\Rightarrow T_L = \ln(2) (R - R') C$$

$$\begin{aligned} \Rightarrow T &= T_L + T_H = \ln(2) (R - R') C + \ln(2) (R' + R_A) C \\ &= \ln(2) (R + R_A) C \end{aligned}$$

$$\begin{aligned} \Rightarrow \text{duty cycle} &= \frac{T_H}{T_L + T_H} \\ &= \frac{R' + R_A}{R + R_A} \end{aligned}$$

$$\Rightarrow f = \frac{1}{T}$$

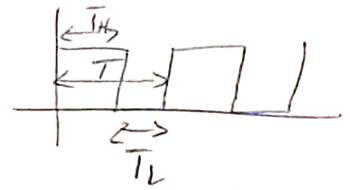

$\hookrightarrow$  independent on  $R'$

$\hookrightarrow$  changing  $R'$  (potentiometer slider) only changes the duty cycle, but does not change the frequency

18.45 Consider the 555 circuit of Fig. 18.29 when the Threshold and the Trigger input terminals are joined together and connected to an input voltage  $v_i$ . Verify that the transfer characteristic  $v_o-v_i$  is that of an inverting bistable circuit with thresholds  $V_{TH} = \frac{1}{3} V_{CC}$  and  $V_{TL} = \frac{2}{3} V_{CC}$  and output levels of 0 and  $V_{CC}$ .

Sol:

\* at  $v_i > \frac{2}{3} V_{CC}$  :

$$\Rightarrow v_i = V_{comp1}^+ > \frac{2}{3} V_{CC}$$

$$\Rightarrow V_{comp1}^- = \frac{2}{3} V_{CC}$$

$$\Rightarrow V_{comp1}^+ > V_{comp1}^- \Rightarrow v_o = V_{CC} \text{ (logic 1)}$$

Figure 18.29 A block diagram representation of the internal circuit of the 555 integrated-circuit timer.

For Comp 2 :

$$v_i = V_{comp2}^- \Rightarrow V_{comp2}^- > V_{comp2}^+$$

$$\Rightarrow v_o = 0V \text{ (logic 0)}$$

$$\Rightarrow R \rightarrow 1, S \rightarrow 0 \Rightarrow v_o = 0$$

\* at  $v_i < \frac{1}{3} V_{CC}$  :

For comp 1 :


$$v_i = V_{comp1}^+ < \frac{2}{3} V_{CC} \Rightarrow v_o = 0 \text{ (logic 0)}$$

For Comp 2 :


$$v_i = V_{comp2}^- < \frac{1}{3} V_{CC} \Rightarrow v_o = V_{CC} \text{ (logic 1)}$$

$\downarrow$   
 $V_{comp2}^+$
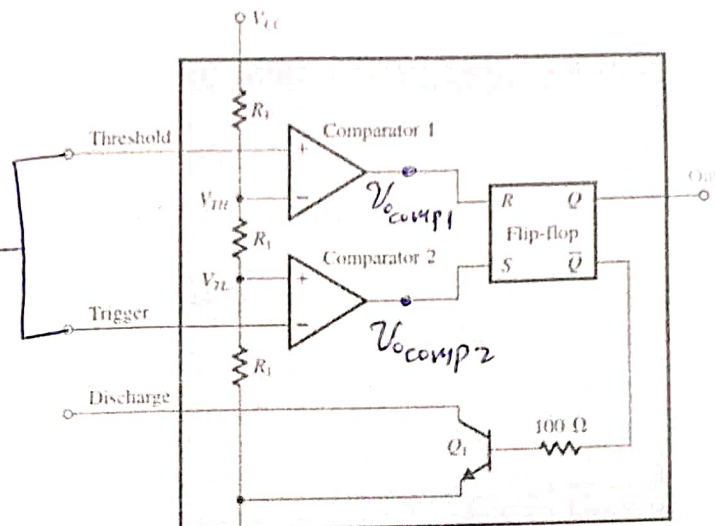
$$\Rightarrow R \rightarrow 0, S \rightarrow 1 \Rightarrow v_o = V_{CC}$$




\*  $V_I - V_O$  characteristic :

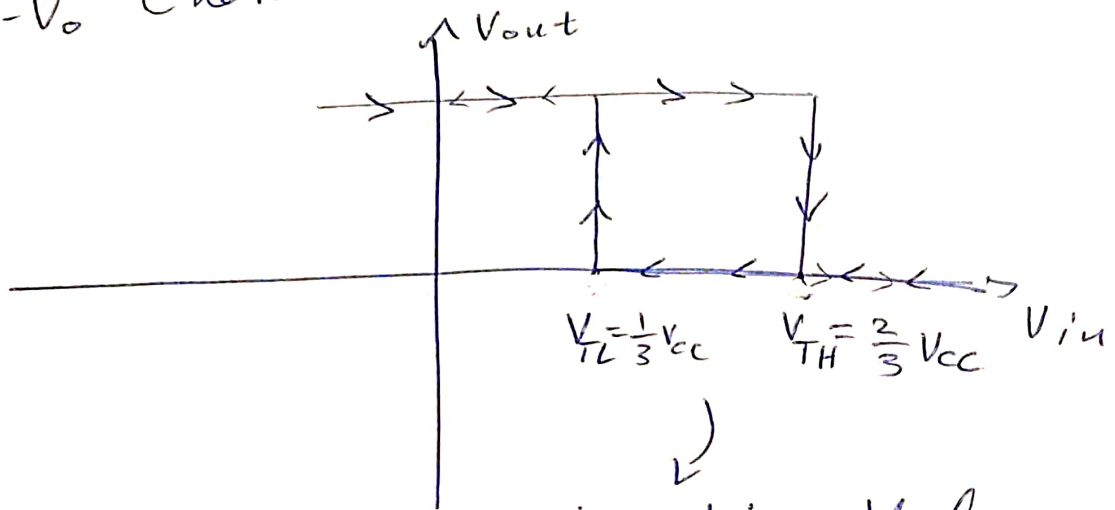

↓  
Bistable Mode



D 18.46 (a) Using a 0.5-nF capacitor  $C$  in the circuit of Fig. 18.30(a), find the value of  $R$  that results in an output pulse of 10- $\mu$ s duration.  
 (b) If the 555 timer used in (a) is powered with  $V_{CC} = 12$  V, and assuming that  $V_{TH}$  can be varied externally (i.e., it need not remain equal to  $\frac{2}{3}V_{CC}$ ), find its required value so that the pulse width is increased to 20  $\mu$ s, with other conditions the same as in (a).

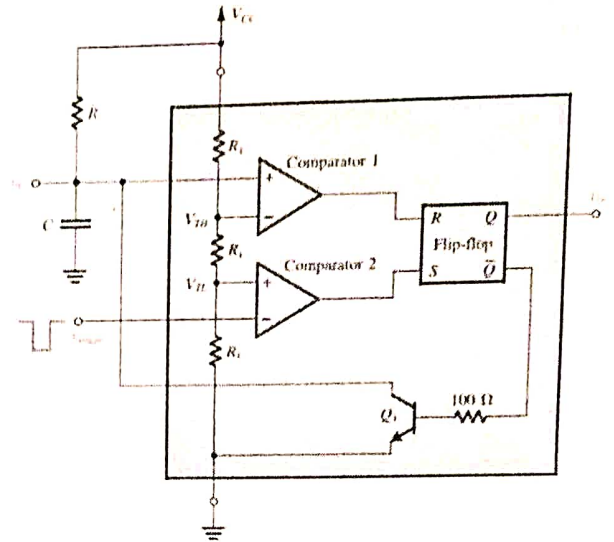

Sol<sup>n</sup>

a)  $C = 0.5 \text{ nF}$   
 $T = 10 \mu\text{s}$

∴ For Monostable:

$$T = RC \ln(3)$$

$$\Rightarrow R = \frac{T}{\ln(3)C} = \frac{10 \times 10^{-6}}{\ln(3) \times 0.5 \times 10^{-9}} = 18.2 \text{ k}\Omega$$

b) adjusting  $V_{TH}$  externally so that  $T = 20 \mu\text{s}$

$$V_{CC} = 12 \text{ V}$$


∴ at charging:

$$V_C = V_{CC} + (V_{init} - V_{CC}) e^{-t/RC}, \quad \tau = RC$$

$$\Rightarrow V_C = V_{CC} [1 - e^{-t/RC}]$$

at  $t = T \rightarrow$

$$\hookrightarrow V_C = V_{TH}$$

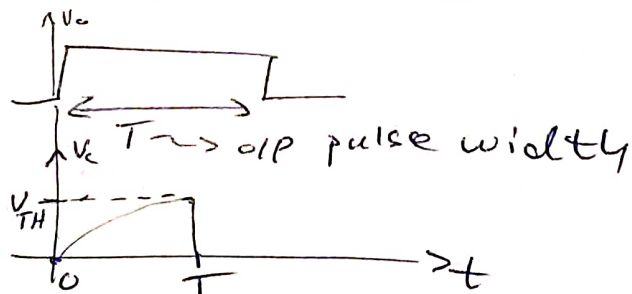

$\Rightarrow$

$$V_{TH} = V_{CC} [1 - e^{-T/RC}]$$

$$\Rightarrow V_{TH} = 12 [1 - e^{-\frac{20 \times 10^{-6}}{18.2 \times 10^3 \times 0.5 \times 10^{-9}}}] = 10.6 \text{ V}$$